

EEE205 – Digital Electronics (II)

Lecture 18

A Revision Class

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

1

Reference Books

1. A. Marcovitz, *Introduction to Logic Design*, McGraw Hill, 2005. (M)
2. R. Tocci, N. Widmer and G. Moss, *Digital Systems: Principles and Applications*, 10th Edition, Pearson Education, 2007. (T)
3. T. Floyd, *Digital Fundamentals*, Pearson Education, 7th Edition, 2000. (F)
4. C. H. Roth, *Fundamentals of Logic Design*, 5th Edition, Thomson Learning, 2004. (R)
5. S. Brown and Z. Vranesic, *Fundamentals of Digital Logic with Verilog Design*, 3rd Edition, McGraw-Hill Education, 2014. (B)

2

Reference Books

Lecture 1	F	Lecture 11	F	Statistics	
Lecture 2	F	Lecture 12	R	T	6.5
Lecture 3	B	Lecture 13	B, R	R (M)	4.5
Lecture 4	F, T	Lecture 14	UoL	F	3.5
Lecture 5	T	Lecture 15	T	B	1.5
Lecture 6	T	Lecture 16	T		
Lecture 7	T	Lecture 17	T		
Lecture 8	R				
Lecture 9	R				
Lecture 10	R				

3

This Module

Contents:

1. Programmable Logics Devices (PLDs)
2. Hardware Design Languages (HDLs)
3. Large Combinational and Sequential Circuits
4. Algorithmic State Machines (ASMs)
5. Processor Interface Circuits

4

Programmable Logic Devices (PLDs)

Types

- SPLDs — Simple Programmable Logic Devices,
- CPLDs — Complex Programmable Logic Devices,
- FPGAs — Field Programmable Gate Arrays.

SPLDs and CPLDs are based on **AND-OR arrays**, which are ideally for SOP and POS expressions.

FPGAs are based on **LUTs** (Look-Up Tables), which are ideally for truth tables.

5

SPLDs

Types


- Programmable Read-Only Memory (**PROM**) consists of a **fixed** AND array and a **programmable** OR array.
- Programmable Logic Array (**PLA**) consists of a **programmable** AND array and a **programmable** OR array.
- Programmable Array Logic (**PAL**) consists of a one-time **programmable** AND array and a **fixed** OR array with output logic.
- Generic Array Logic (**GAL**) consists of a **reprogrammable** AND array and a **fixed** OR array with programmable output logic.

6

Field Programmable Gate Arrays (FPGA)

x_1	x_2	f_1
0	0	1
0	1	0
1	0	0
1	1	1

$$f_1 = \bar{x}_1 \bar{x}_2 + x_1 x_2$$

 

- First decide the truth table.
- An LUT contains storage cells. The output values are copied to the storage cells in the same order.
- The outputs of such cells are multiplexed with the input variables as the data select. **The MSB controls the last MUX. The LSB controls the first MUX.**

7

AHDL Overview

AHDL vs. Programming Languages

- The statements are evaluated **constantly** and **concurrently** (at the same time). The order in which they are listed makes no difference.
- In the contrast, a computer programming language follows instructions in **sequential** order. Each instruction is processed **once** unless a loop is being used.

8

AHDL Overview

```
SUBDESIGN fig3_50
(
  a,b,c      :INPUT;
  y          :OUTPUT;
)
VARIABLE
  m          :NODE;
BEGIN
  m = a & b;
  y = m # c;
END;
```

Format of AHDL files:

- Start with **SUBDESIGN**
- 1. **I/O definitions**
- 2. **VARIABLE** section used to define intermediate nodes and devices using primitives
- 3. **Functional description:** state description or behaviour description

9

Synchronous Counters

Behavioral Description – A Full Feature Counter

```
1 SUBDESIGN fig7_42
2 (
3   clock, clear, load, cntenabl, down, din[3..0] :INPUT;
4   q[3..0], term_ct :OUTPUT; -- declare 4-bit array of output bits
5 )
6 VARIABLE
7   count[3..0] :DFF; -- declare a register of D flip flops
8
9 BEGIN
10  count[].clk = clock; -- connect all clocks to synch source
11  count[].clrn = !clear; -- connect for asynch active HIGH clear
12  IF load THEN count[].d = din[]; -- synchronous load
13  ELSIF !cntenabl THEN count[].d = count[].q; -- hold count
14  ELSIF !down THEN count[].d = count[].q + 1; -- increment
15  ELSE count[].d = count[].q - 1; -- decrement
16  END IF;
17  IF ((count[].q == 0) & down # (count[].q == 15) & !down) & cntenabl
18  THEN term_ct = VCC; -- synchronous cascade output signal
19  ELSE term_ct = GND;
20  END IF;
21  q[] = count[]; -- transfer register contents to outputs
22 END;
```

10

Synchronous Counters

- For behaviour description, always use DFFs for sequential circuits.
- “.q” is the present state, while “.d” is the next state.
- The order of the controls in the IF.....ELSEIF structure reflects the priority order of these control signals. The first control to check has the highest priority.
- Don't use non-plain text characters or C programming language.
- For falling-edge triggered FFs, the input is sometimes inverted with !.

11

A Revision of Some Terminology

	Boolean Algebra View	Karnaugh Map View
Minterm	a product term with all variables	a 1 cell
Implicant	a product term	a rectangle of 2^n 1's
Prime Implicant	a shortest product term	a group of 1's that is not fully contained in another group of 1's
Essential Prime Implicant	product terms that must appear in a minimized SOP	has at least a 1 not shared with others


12

Karnaugh Maps

- Boolean functions with five variables can be simplified using **two** 4-variable maps.
- Squares directly above or below each other are adjacent.

$$F(A,B,C,D,E)$$
 
$$= \sum m(1,3,8,9,11,12,14,17,19,20,22,24,25,27)$$




Karnaugh Maps

Pitfalls

- Variable values should be sorted in 00, 01, **11**, 10.
- Variables are sorted according to alphabetical order or magnitude, e.g. AB/C, WX/YZ, Q₂Q₁/Q₀
- 1's groups are not fully maximized - forget warp-around adjacency.
- Don't know how to use don't cares.

Karnaugh Maps

 

(b) Without "don't cares" $Y = \bar{A}BCD + ABCD$
With "don't cares" $Y = A + BCD$

"Don't Care"

- Can be used to simplify Boolean expressions.
- When an X can be grouped with 1s, then it is thought as 1.
- Otherwise, it is thought as 0.

Quine-McCluskey Method

Step 1: Finding prime implicants


- Sort the product terms into groups according to the number of 1's.
- Terms which have dashes in the same place and differ in only one variable can be combined.

	Column I	Column II	Column III
group 0	0 0000 ✓	0, 1 000- ✓	0, 1, 8, 9 -00-
group 1	1 0001 ✓	0, 2 00-0 ✓	0, 2, 8, 10 -0-0
	2 0010 ✓	0, 8 -000 ✓	0, 8, 1, 9 -00-
group 2	8 1000 ✓	1, 5 0-01 ✓	0, 8, 2, 10 -0-0
	5 0101 ✓	1, 9 -001 ✓	2, 6, 10, 14 --10
group 3	6 0110 ✓	2, 6 0-10 ✓	2, 10, 6, 14 --10
	9 1001 ✓	2, 10 -010 ✓	
group 3	10 1010 ✓	8, 9 100- ✓	
	7 0111 ✓	8, 10 10-0 ✓	
group 3	14 1110 ✓	5, 7 01-1 ✓	
		6, 7 011- ✓	
group 3		6, 14 -110 ✓	
		10, 14 1-10 ✓	

Quine-McCluskey Method

Step 2: Prime implicant chart.

 - The essential prime implicants are chosen first.
- Then additional non-essential prime implicants are selected by trial.
- They should cover as many minterms as possible.



17

Quine-McCluskey Method


Pitfalls:

- In finding the prime implicants, the don't cares are treated as minterms.
- When forming the prime implicant chart, the **don't cares should not be listed at the top.**
- **All** alternative solutions must be provided.
- Frequently miss some combinations or forget column three.

18

Design of Synchronous Counters

 Step 1: State diagram Step 2: Next-state table




Present State			Next State		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0


19

Design of Synchronous Counters

 Step 3: Flip-flop transition tables and equations



J-K flip-flop $Q^+ = JQ' + K'Q$

 

D flip-flop $Q^+ = D$

JK flip flop design table.

q	q^*	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

D flip flop design table.


q	q^*	D
0	0	0
0	1	1
1	0	0
1	1	1

20


Design of Synchronous Counters

Step 4: Karnaugh Maps

 - Determine the logic required for the inputs of each flip-flop.



Moore- and Mealy-Type FSMs

 

- Sequential circuits are called **finite state machines (FSM)**.
- Moore-type FSMs are those whose outputs depend only on the state of the circuits.
- Mealy-type FSMs are those whose outputs depend on both the state and the inputs.

22

Representation of FSMs



Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1

1. State table

2. State graph

3. ASM chart



A Moore-type FSM

  

Representation of FSMs

A Mealy-type FSM

Present state	Next state		Output z	
	w = 0	w = 1	w = 0	w = 1
A	A	B	0	0
B	A	B	0	1

  

24

Design and Analysis of FSMs

Analysis of FSMs

Given a sequential circuit, sketch the state graph

1. Determine FF input (excitations) and output equations
2. Decide the next-state equation
3. The state table

25

Design and Analysis of FSMs

Design of FSMs


Given a state graph, design the sequential circuit

1. State table
2. State assignment
3. Use present state, next state and FF design table to deduce FF inputs.
4. K-map to find the input (excitation) and output equations

26

Design and Analysis of FSMs

Pitfalls

 

1. Don't have a clear picture about the deduction process.
2. Forget FF next-state equations, e.g. $Q^+ = JQ' + K'Q$
3. Forget FF design tables
4. Careless in the state table
5. Have no idea to cope with a Karnaugh map with don't cares.

27