

# EEE213 Power Electronics and Electromechanism

Lab arrangement (Room EE411)

11<sup>th</sup> April Thursday (9:00-12:00 & 2:00 -5:00) ✓

**Deadline: May 5th, 23:55pm**

TA (PhD students) :

1. Chu Guanying: Guanying.chu@xjtlu.edu.cn

1. Wang Yuanchen: Yuanchen.wang@xjtlu.edu.cn

# EEE213 Power Electronics and Electromechanism

## 8. DC-DC Converters

# Outline

---

- Step-down operation
  - Duty cycle generation
- Types of DC-DC converter
  - Buck converters
  - Boost converters
  - Buck-Boost converter
- Closed-loop control of DC-DC converters

# *Types of DC-DC converters*


---

- Step-down: Buck converters
  - the output voltage is less than the input voltage
- Step-up: Boost converters
  - the output voltage is higher than the input voltage
- Step-up/down: Buck-boost converters
  - the output voltage can be higher or less than the input voltage

There are different circuit topologies, having different names.
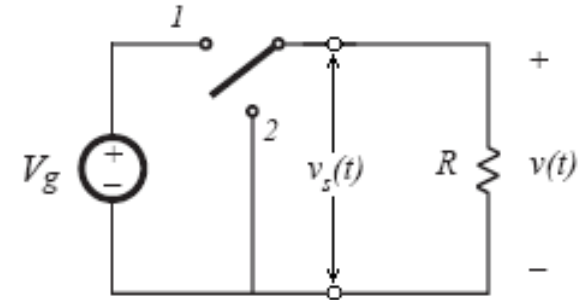
# 1.1 Step-down operation

- Operation principle:
  - Switch on (position 1) for  $t_1$ ,  $v_o = v_s = v_g$
  - Switch off (position 2) for  $t_2$ ,  $v_o = v_s = 0$ .



- Average output voltage:


$$V_o = \frac{1}{T} \int_0^T v_o dt = \frac{1}{T} \int_0^{t_1} V_g dt = \frac{t_1}{T} V_g = k V_g$$

where  $k$  is the duty cycle:

$$D = k = \frac{t_1}{T}$$

- RMS output voltage:


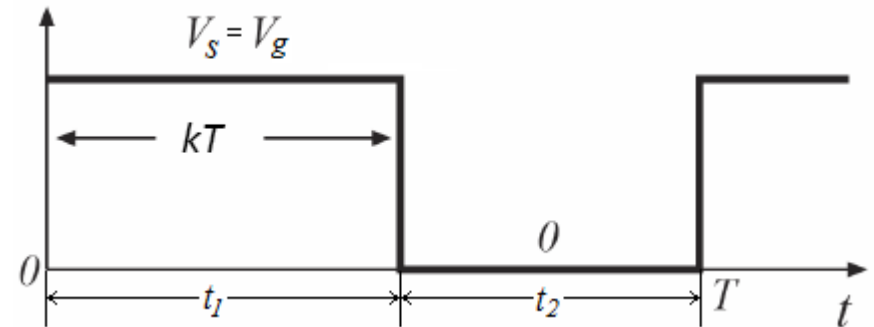
$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v_o^2 dt} = \sqrt{k} V_g$$



*$k$  is called the duty cycle.  
Sometimes using  $D$  instead of  $k$ .*

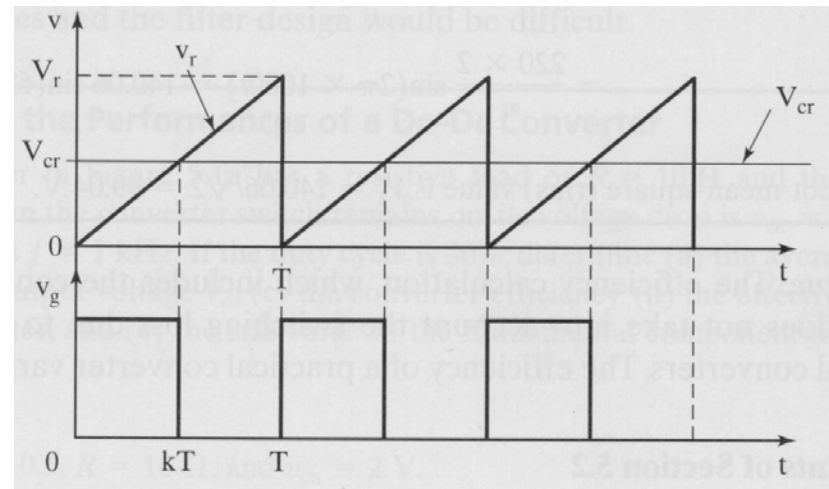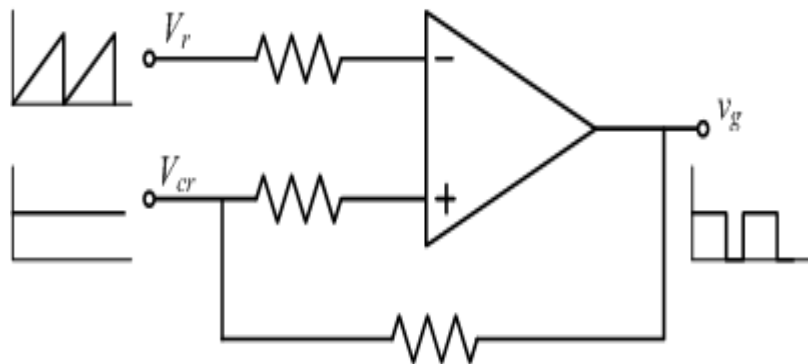
## 1.2 Generation of duty cycle

- If a saw-tooth signal  $V_r$  and a DC signal  $V_{cr}$  are supplied to a comparator, then the output of the comparator can be shown as  $v_g$ .
- The duty cycle of  $v_g$  will be changed if  $V_{cr}$  changes.
- This is how we control the voltage of a DC-DC converter.


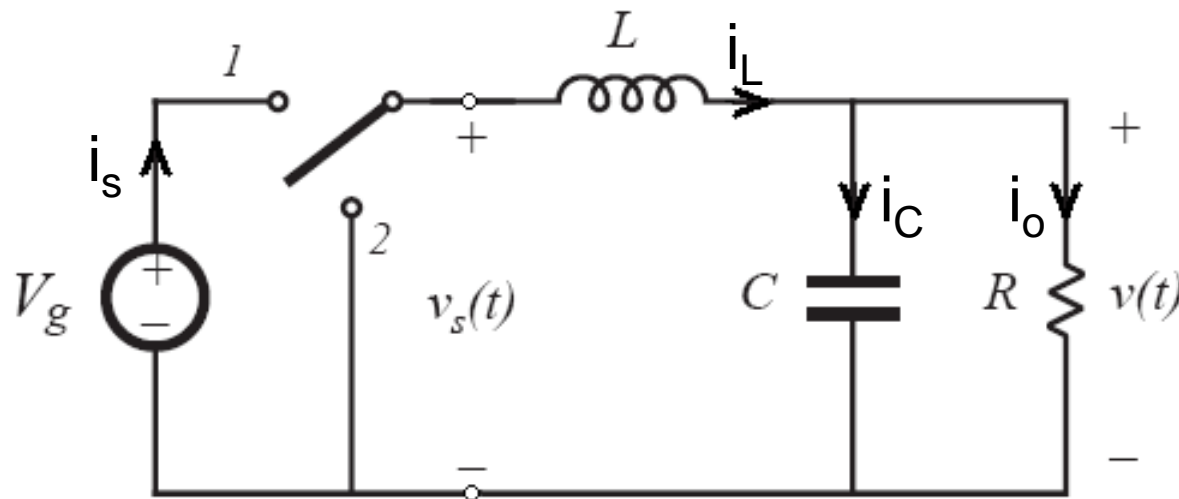
## 2.1 Buck converter

- Devices: one switch and one diode
- Filters: LC filter to remove the switching harmonics and to pass only the DC component so that the output voltage  $v$  is nearly a constant.





# Small ripple approximation

- The L-C form a practical low-pass filter
- Actual output voltage waveform:  

$$v(t) = V + v_{\text{ripple}}(t)$$
- In a well-designed converter, the output voltage ripple is small.
- Hence, the waveforms can be easily determined by ignoring the ripple:

$$\|v_{\text{ripple}}\| \ll V$$

$$v(t) \approx V$$

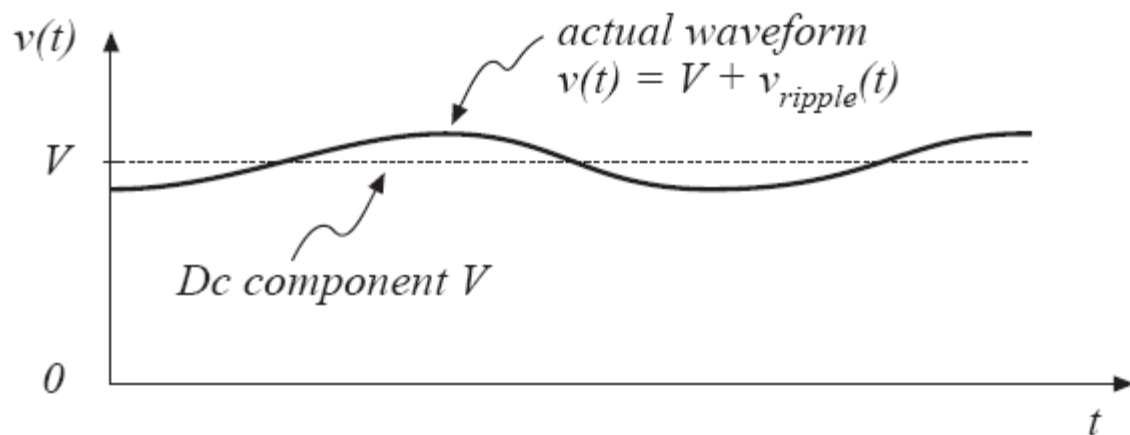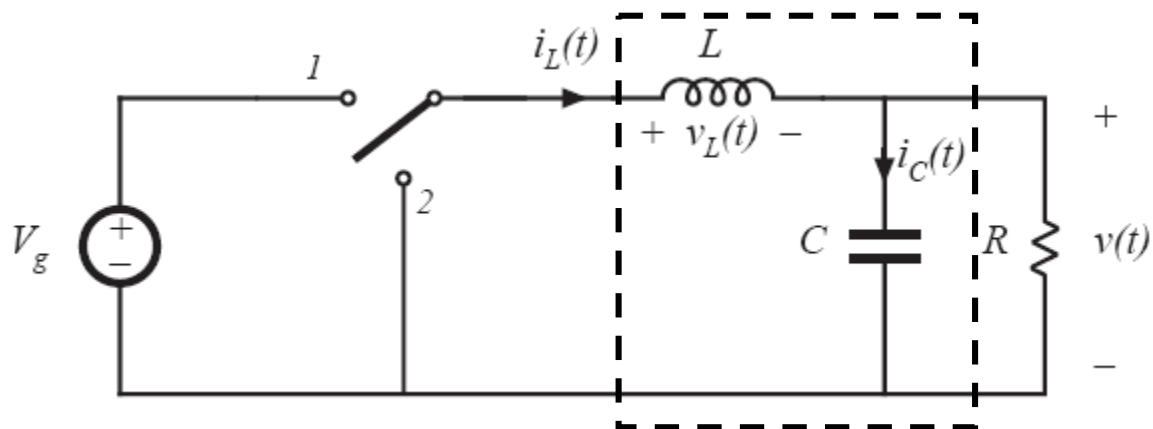



# Operation modes

- Mode 1

- Switch is on (position 1)

- Inductor voltage

$$v_L = V_g - v(t)$$

- Small ripple approximation

$$v_L \approx V_g - V$$

- Inductor current


$$v_L(t) = L \frac{di_L(t)}{dt}$$

- Solve for the slope:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} \approx \frac{V_g - V}{L}$$



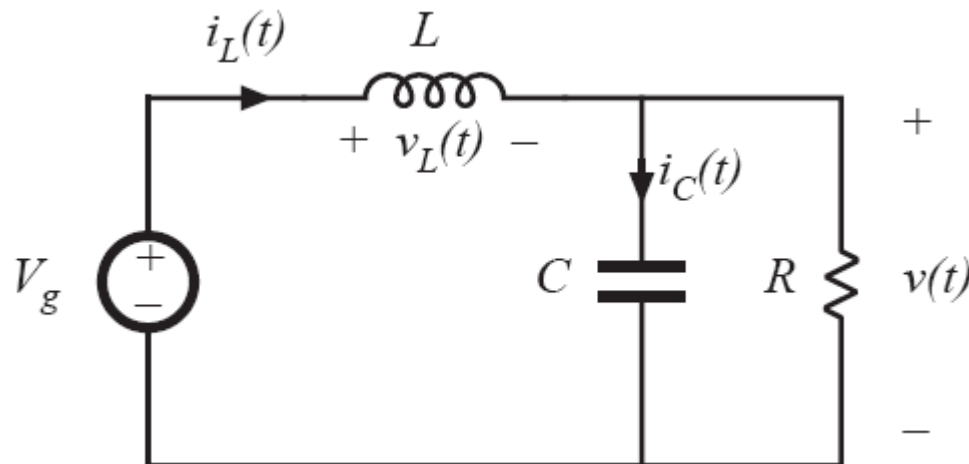The inductor current changes with an essentially constant slope



*Energy is transferred to L and the load;*

*In the first half period, C discharges and then is charged when the inductor current is bigger than the load current*

# Operation modes

- Mode 2

- Switch is off (position 2)

- Inductor voltage

$$v_L(t) = -v(t)$$

- Small ripple approximation

$$v_L(t) \approx -V$$

- Inductor current


$$v_L(t) = L \frac{di_L(t)}{dt}$$

- Solve for the slope:

$$\frac{di_L(t)}{dt} \approx -\frac{V}{L}$$



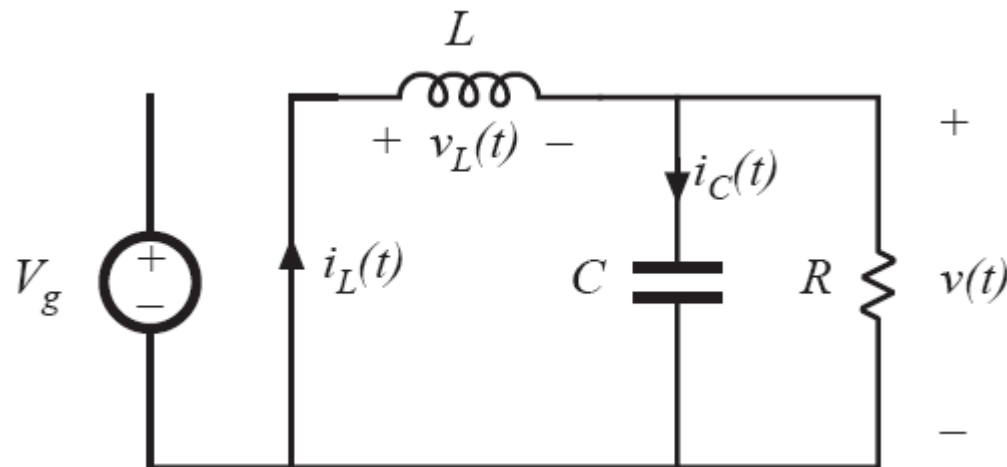
The inductor current changes with an essentially constant slope




*Energy is transferred from L to the load*

*In the first half period, C remains being charged and then discharges when the inductor current is smaller than the load current*


Diode voltage

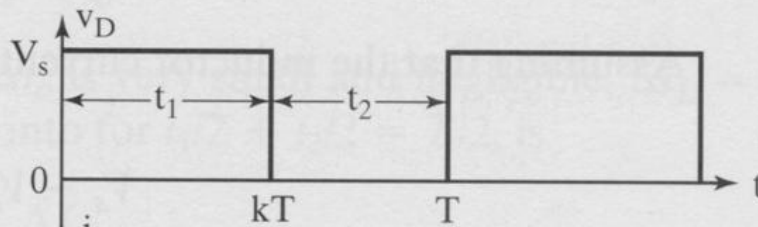


Inductor current

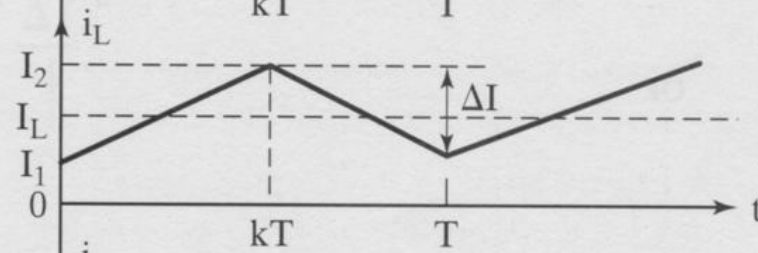


Input current

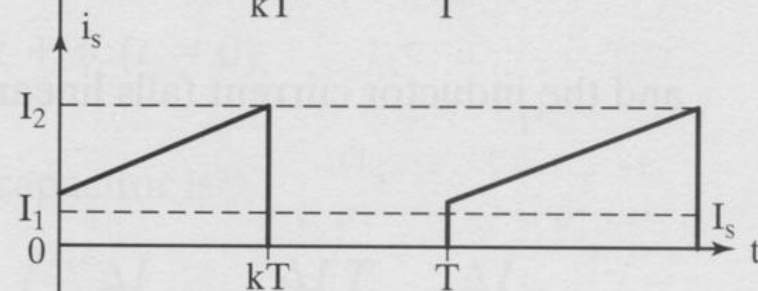


Capacitor current

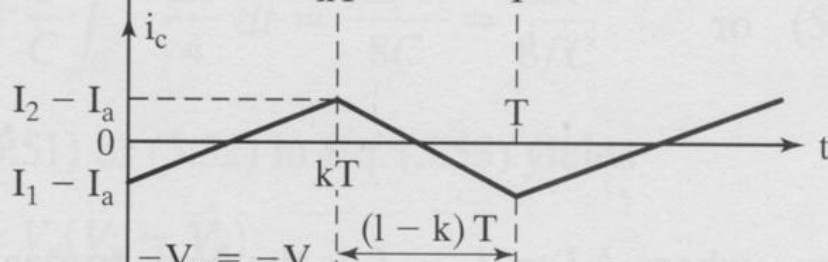

Output voltage with zoomed ripples

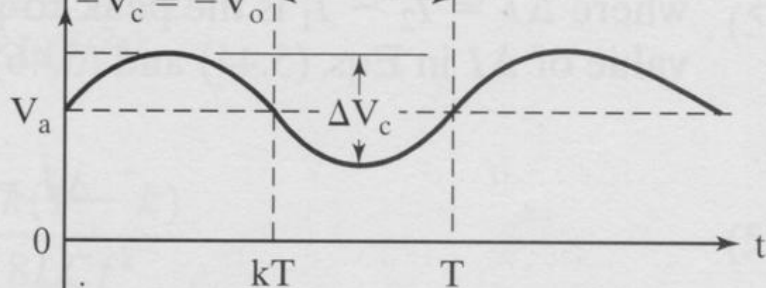

Output current

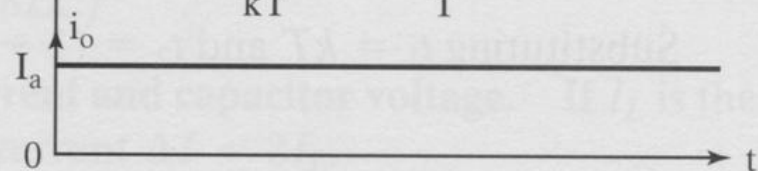

### ***Assumption for steady-state analysis:***

- *The components are all ideal.*
- *The ripple in the output voltage is negligible.*
- *The current in the inductor is continuous.*
- *Ripples in the load current is negligible.*

### ***Basic principles in the steady state***

- ***The inductor volt-second balance:*** *the average inductor voltage is zero in the steady state.*
- ***The capacitor ampere-second (charge) balance:*** *the average capacitor current is zero in the steady state.*

# Inductor volt-second balance: Derivation

- Inductor defining relation:

$$v_L(t) = L \frac{di_L(t)}{dt}$$

- Integrate over one complete switching period:

$$i_L(T_s) - i_L(0) = \frac{1}{L} \int_0^{T_s} v_L(t) dt$$

- In periodic steady state, the net change in inductor current is zero:

$$0 = \int_0^{T_s} v_L(t) dt$$

- Hence, the total area (or volt-second) under the inductor voltage waveform is zero whenever the converter operates in steady state.

An equivalent form:


$$0 = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = \langle v_L \rangle$$

***The average inductor voltage is zero in steady state.***


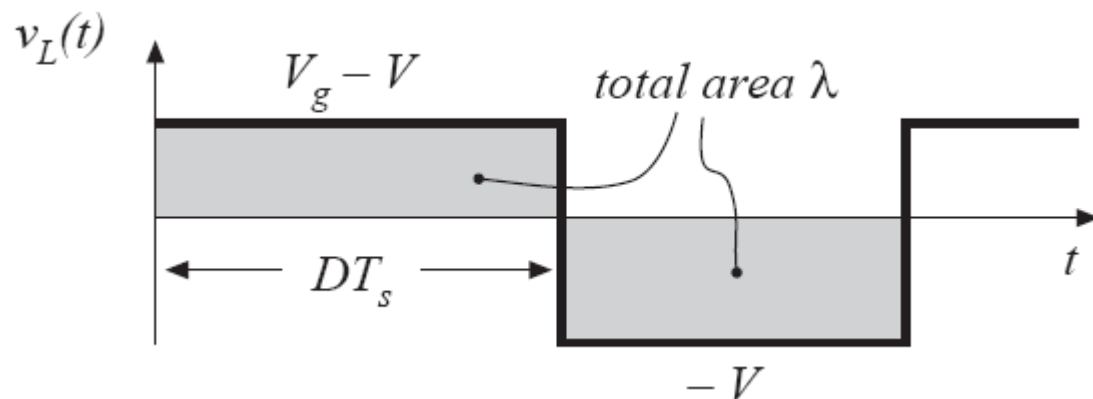
# Inductor volt-second balance: Example

Inductor voltage  
waveform  
previously derived:



$$0 = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = \langle v_L \rangle$$

- Integral of voltage waveform is area of rectangles:

$$\lambda = \int_0^{T_s} v_L(t) dt = (V_g - V)(DT_s) + (-V)(D'T_s)$$


- Average voltage is:

$$\langle v_L \rangle = \frac{\lambda}{T_s} = D(V_g - V) + D'(-V)$$

- Equate to zero and solve for V:

$$0 = DV_g - (D + D')V = DV_g - V$$

$$\Rightarrow V = DV_g$$

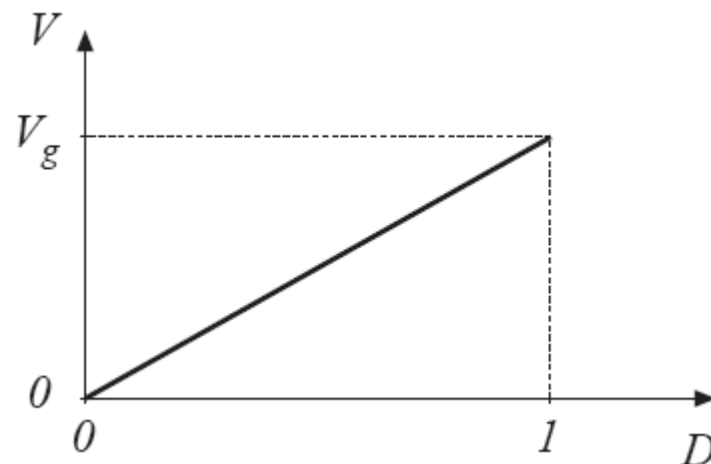

# Capacitor charge balance: Derivation

- Capacitor defining relation:

$$i_c(t) = C \frac{dv_c(t)}{dt}$$


- Integrate over one complete switching period:

$$v_c(T_s) - v_c(0) = \frac{1}{C} \int_0^{T_s} i_c(t) dt$$

- In periodic steady state, the net change in capacitor voltage is zero:


$$0 = \frac{1}{T_s} \int_0^{T_s} i_c(t) dt = \langle i_c \rangle$$

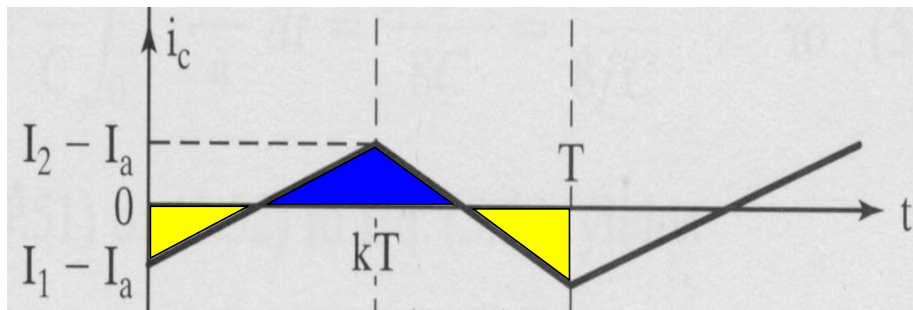- Hence, the total area (or charge) under the capacitor current waveform is zero whenever the converter operates in steady state.




*The average capacitor current is zero in steady state.*


# Inductor current ripples

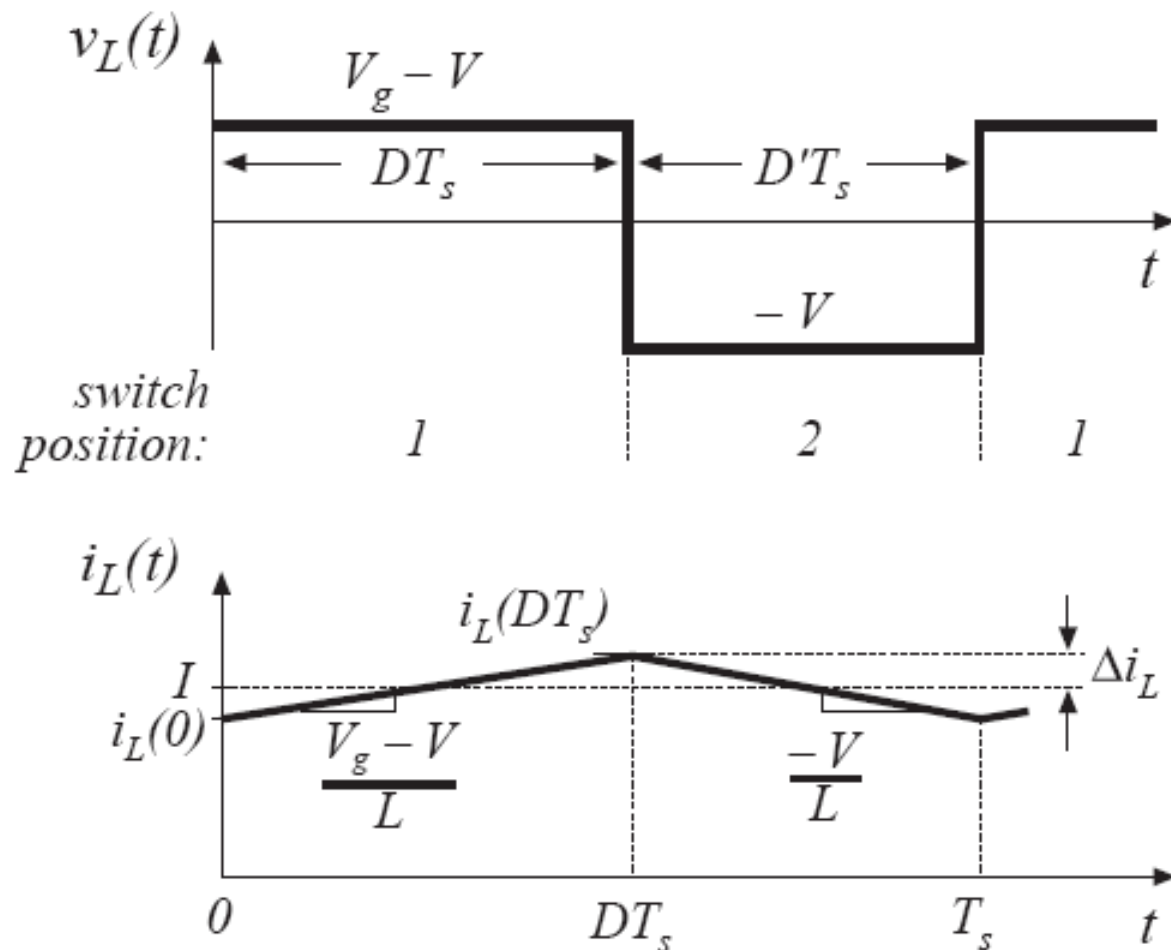
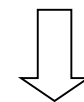
$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} \approx \frac{V_g - V}{L}$$


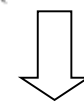
$$(2\Delta i_L) = \left( \frac{V_g - V}{L} \right) (DT_s)$$



$$\Delta i_L = \frac{V_g - V}{2L} DT_s$$

$$L = \frac{V_g - V}{2\Delta i_L} DT_s$$



$$V = DV_g$$

$$\Delta i_L = \frac{(1-D)VT_s}{2L} = \frac{(1-D)DV_g}{2f_s L}$$

*The higher the switching frequency and the bigger the inductor, the smaller the ripple*



# Capacitor voltage ripples

- Assume that the load ripple current is negligible (value  $I_a$ ), which means all the ripple (inductor) current flows through the capacitor. Then the capacitor current can be shown as:

$$i_c = i_L - I_a$$

- The total charge  $q$  is the area of the triangle, as shown:


$$q = \frac{1}{2} \frac{\Delta i_L}{2} \frac{T_s}{2}$$

- Current  $i_c(t)$  is positive for half of the switching period which is charging the capacitor  $C$ . The total charge  $q$  deposited on the capacitor (the grey area) is:

$$q = C(2\Delta v) \quad \Delta v = \frac{\Delta i_L T_s}{8C}$$

$$\Delta i_L = \frac{(1-D)VT_s}{2L} = \frac{(1-D)DV_g}{2f_s L}$$
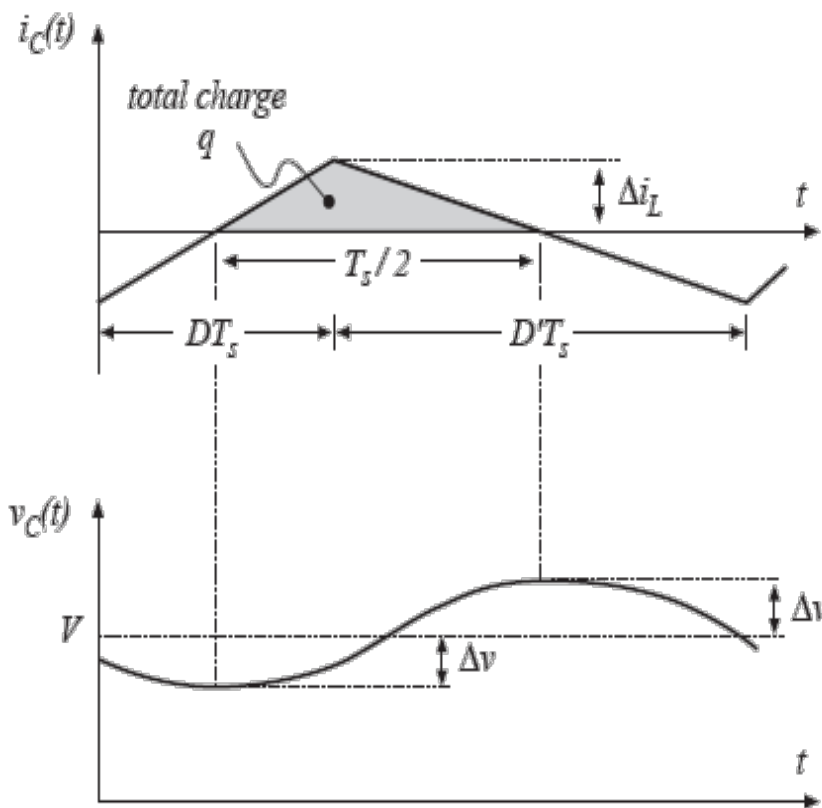
$$\Delta v_c = \frac{\Delta i_L}{8f_s C} = \frac{(1-D)DV_g}{16f_s^2 LC}$$





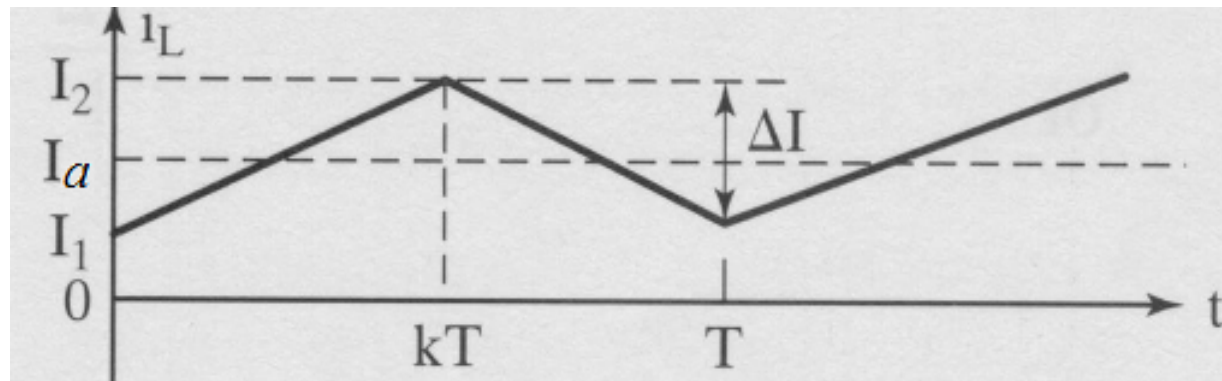
# Discontinuous inductor current

- If the average load (inductor) current  $I_a$  is less than  $\Delta I/2$ , then the inductor current will become discontinuous. Assume that the load is a resistor  $R$ , in order to guarantee a continuous inductor current the following condition needs to be satisfied


$$I_a = \frac{V_a}{R} > \frac{\Delta I}{2} = \frac{(1-k)V_a}{2fL} \implies L > \frac{1-k}{2f} R$$


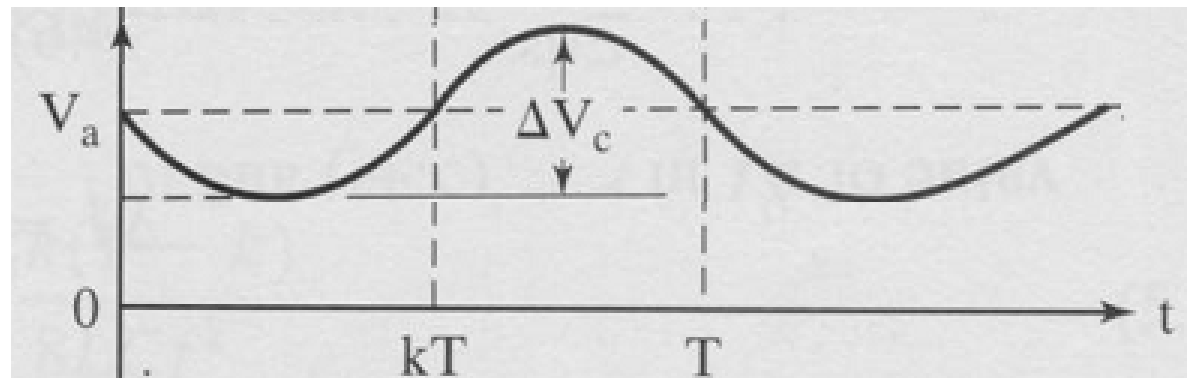
# Discontinuous capacitor voltage


- If the average output (capacitor) voltage  $V_a$  is less than  $\Delta V_c/2$ , then the capacitor voltage will become discontinuous. In order to guarantee a continuous capacitor voltage the following condition needs to be satisfied

$$V_a > \frac{1}{2} \Delta V_c \quad \text{or} \quad kV_s > \frac{(1-k)k}{16f^2LC} V_s \quad \Rightarrow \quad C > \frac{1-k}{16f^2L}$$





## 2.2 Boost converter

- Boost converter with ideal switch

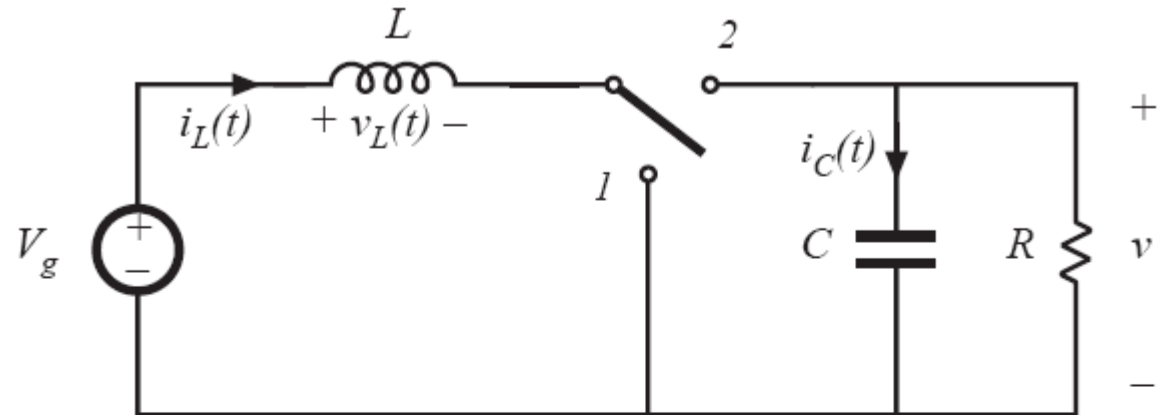

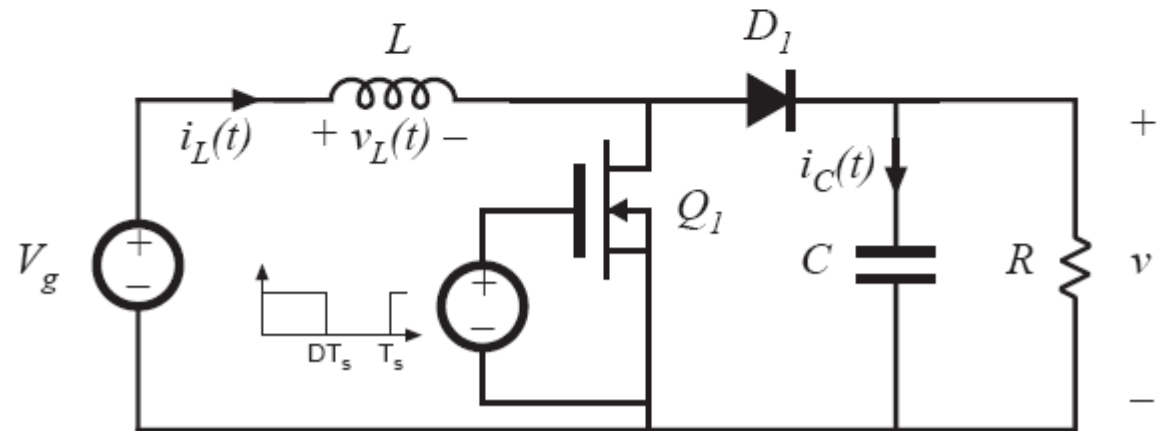
- Realization using power MOSFET and diode



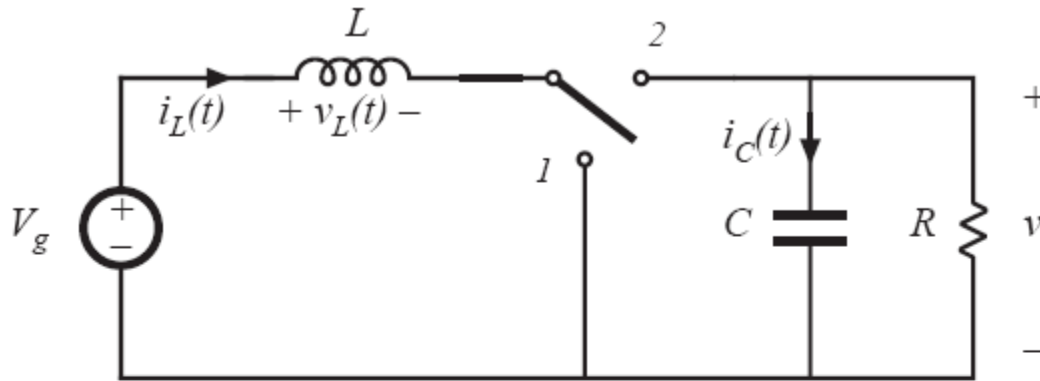

*switch in position 1*


Mode 1:

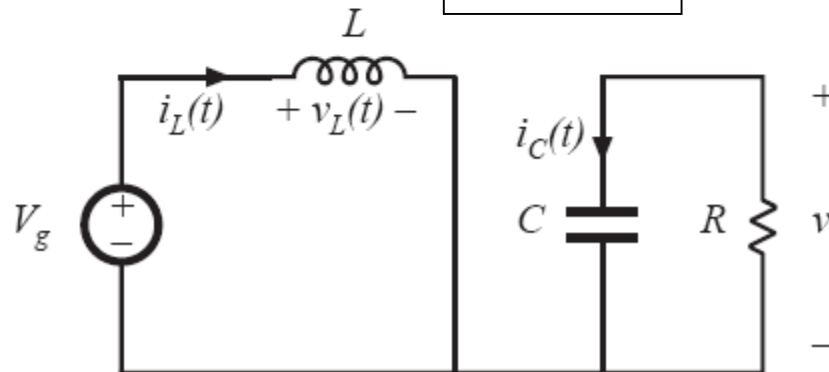

- Energy is being stored in  $L$  and the inductor current increases
- $C$  discharges to supply the load

*switch in position 2*

Mode 2:

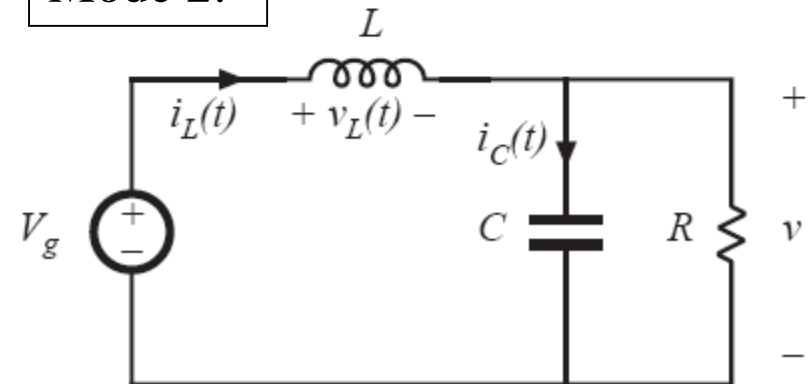

- Energy is transferred from  $L$  and  $V_s$  to the load
- $C$  is being charged

*Inductor voltage and capacitor current*

$$v_L = V_g$$


$$i_C = -v / R$$

Mode 1:

*Small ripple approximation:*

$$v_L = V_g$$

$$i_C = -V / R$$

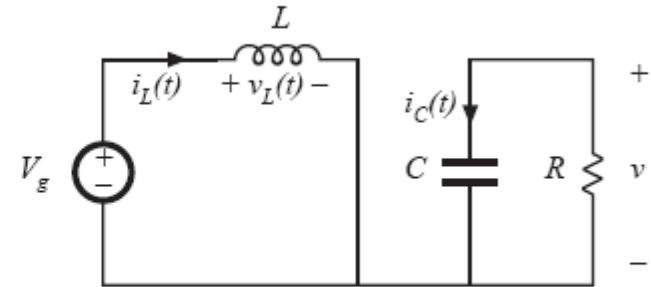

*Inductor voltage and capacitor current*

$$v_L = V_g - v$$


$$i_C = i_L - v / R$$

Mode 2:

*Small ripple approximation:*

$$v_L = V_g - V$$

$$i_C = I - V / R$$

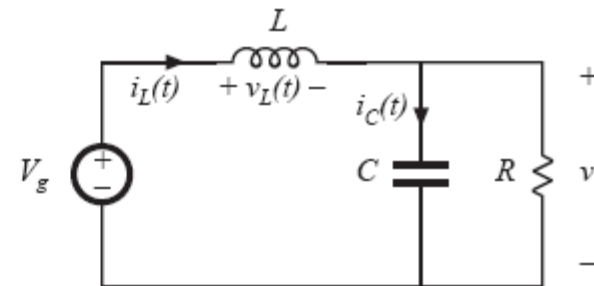


$I$ : average inductor current

$V$ : average output voltage



# Inductor voltage and capacitor current

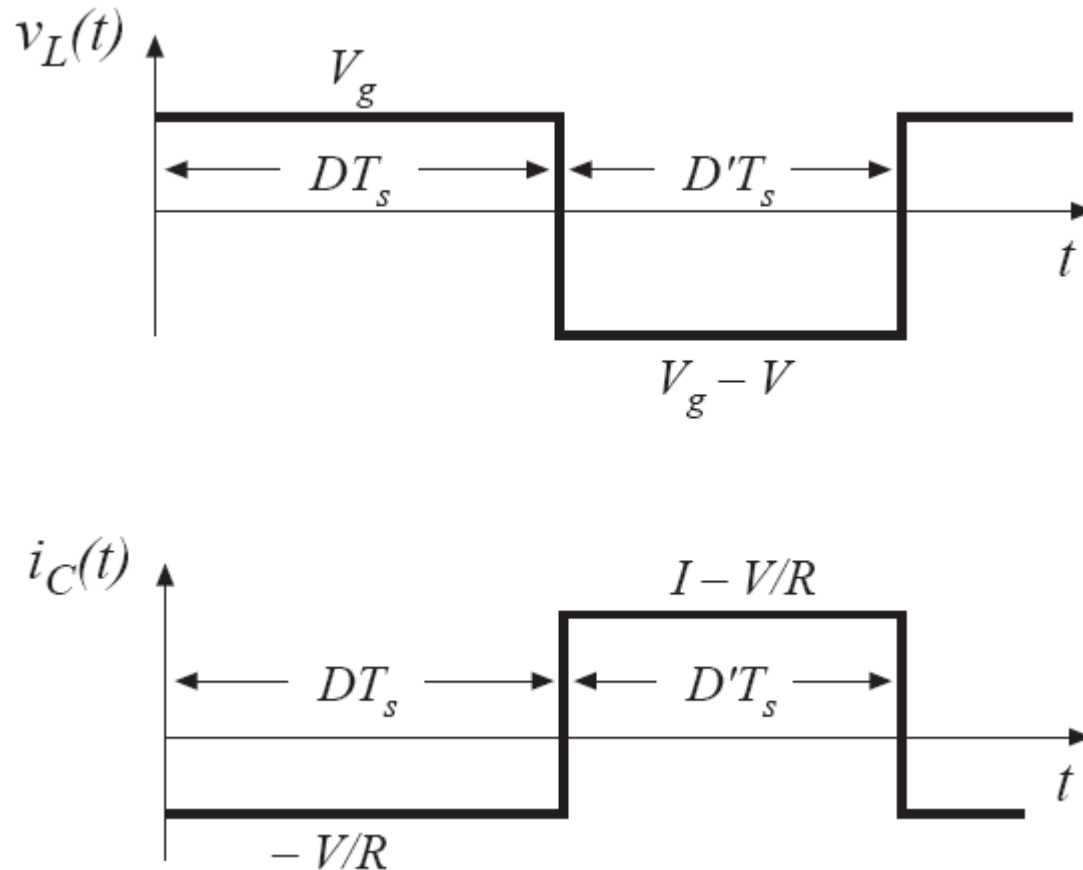

# Inductor volt-second balance: average voltage

- Net volt-seconds applied to inductor over one switching period:

$$\int_0^{T_s} v_L(t) dt = (V_g) DT_s + (V_g - V) D'T_s$$

- Equate to zero and collect terms:


$$V_g (D + D') - V D' = 0$$

- Solve for V:

$$V = \frac{V_g}{D'}$$

- The voltage conversion ratio is:
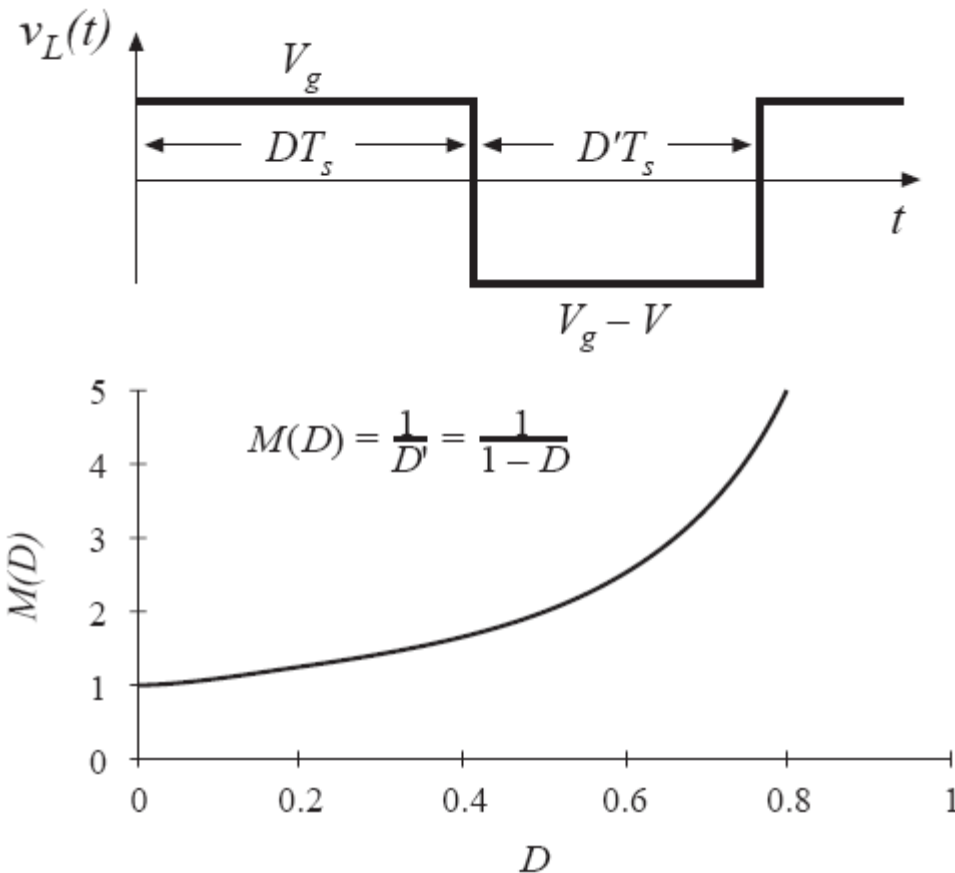
$$M(D) = \frac{V}{V_g} = \frac{1}{D'} = \frac{1}{1 - D}$$



# Capacitor charge balance: average current

- Capacitor charge balance:

$$\int_0^{T_s} i_c(t) dt = \left(-\frac{V}{R}\right) DT_s + \left(I - \frac{V}{R}\right) D'T_s$$

- Collect terms and equate to zero:



$$-\frac{V}{R} (D + D') + I D' = 0$$

- Solve for I:

$$I = \frac{V}{D' R}$$

- Eliminate V to express in terms of  $V_g$ :

$$I = \frac{V_g}{D'^2 R}$$

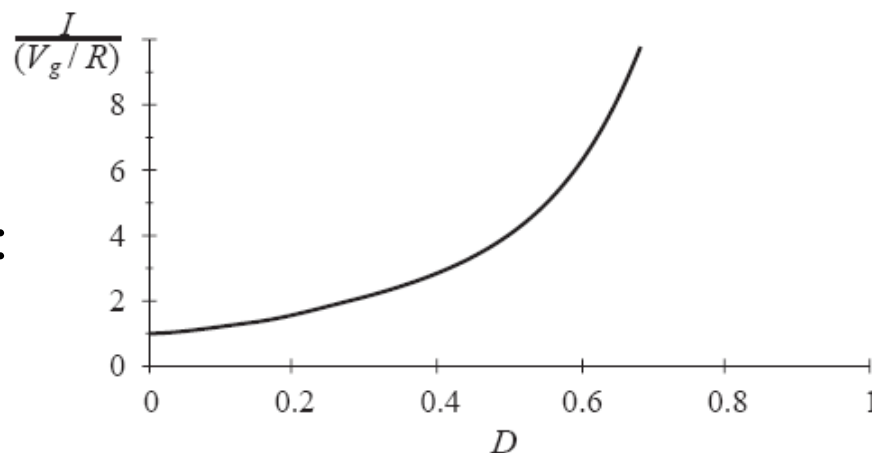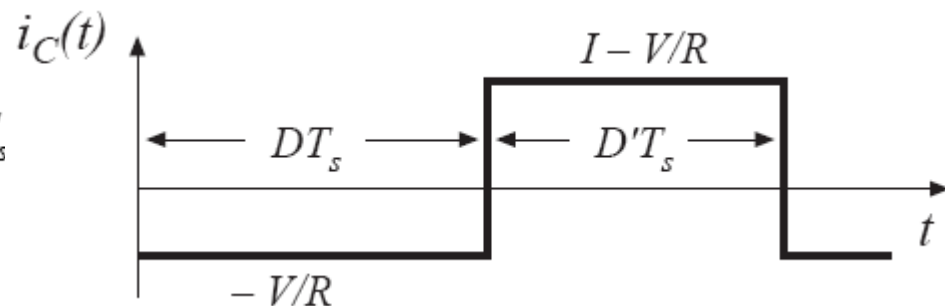



# Determination of inductor current ripple

Inductor current slope during subinterval 1:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g}{L}$$

Inductor current slope during subinterval 2:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g - V}{L}$$


Change in inductor current during subinterval 1 is (slope) (length of subinterval):

$$2\Delta i_L = \frac{V_g}{L} DT_s$$

Solve for peak ripple:

$$\Delta i_L = \frac{V_g}{2L} DT_s$$

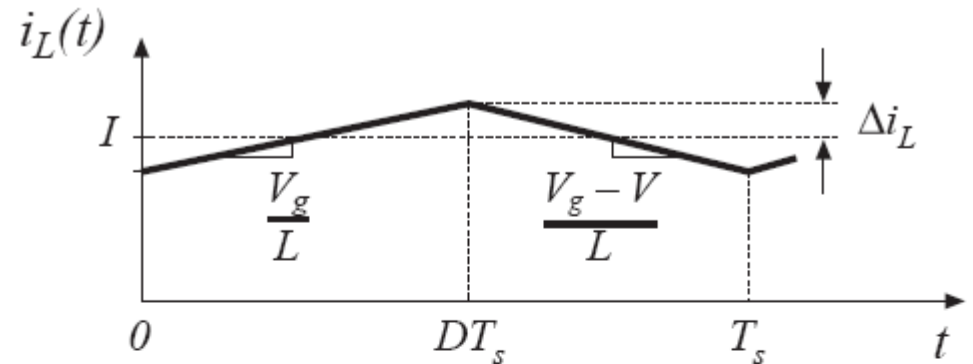- Choose  $L$  such that desired ripple magnitude is obtained




# Determination of capacitor voltage ripple

Capacitor voltage slope during subinterval 1:

$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = -\frac{V}{RC}$$

Capacitor voltage slope during subinterval 2:
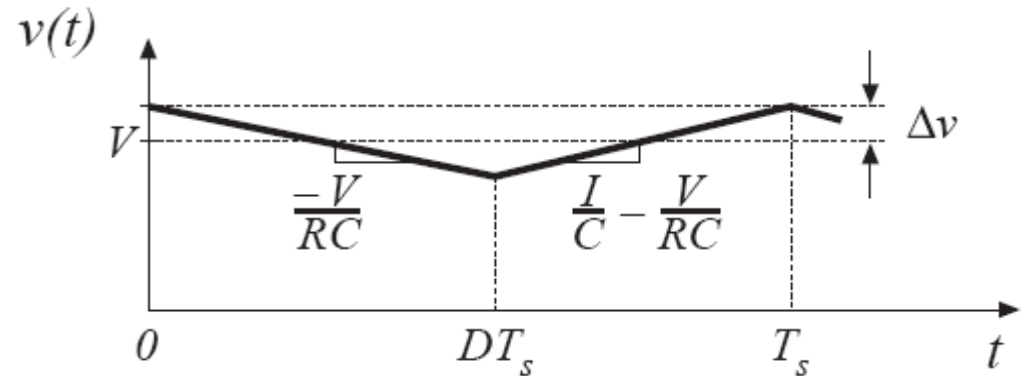
$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = \frac{I}{C} - \frac{V}{RC}$$



Change in capacitor voltage during subinterval 1 is (slope) (length of subinterval):

$$-2\Delta v = \frac{-V}{RC} DT_s$$




Solve for peak ripple:

$$\Delta v = \frac{V}{2RC} DT_s$$

- Choose  $C$  such that desired voltage ripple magnitude is obtained
- In practice, capacitor *equivalent series resistance* (esr) leads to increased voltage ripple




## 2.3 Buck-Boost converter

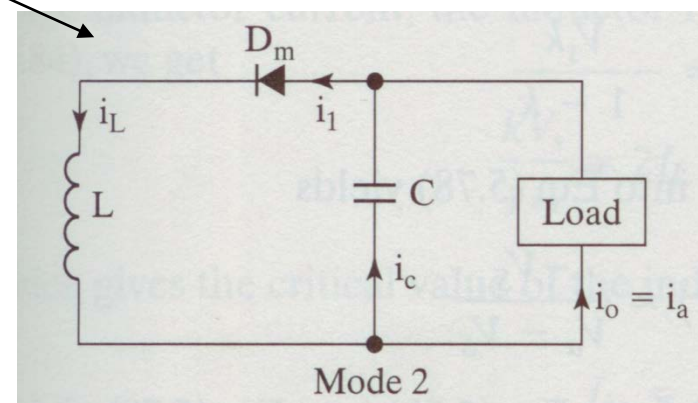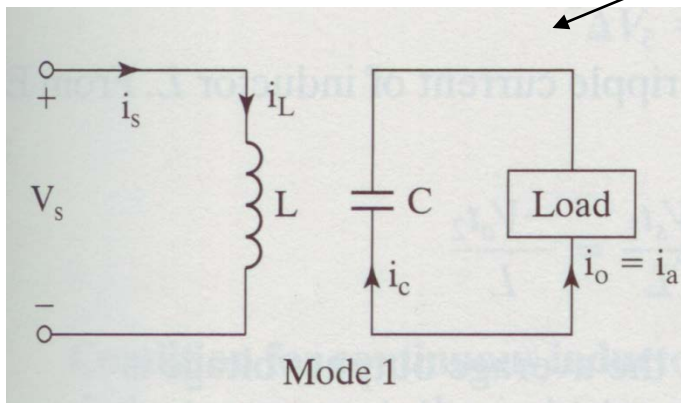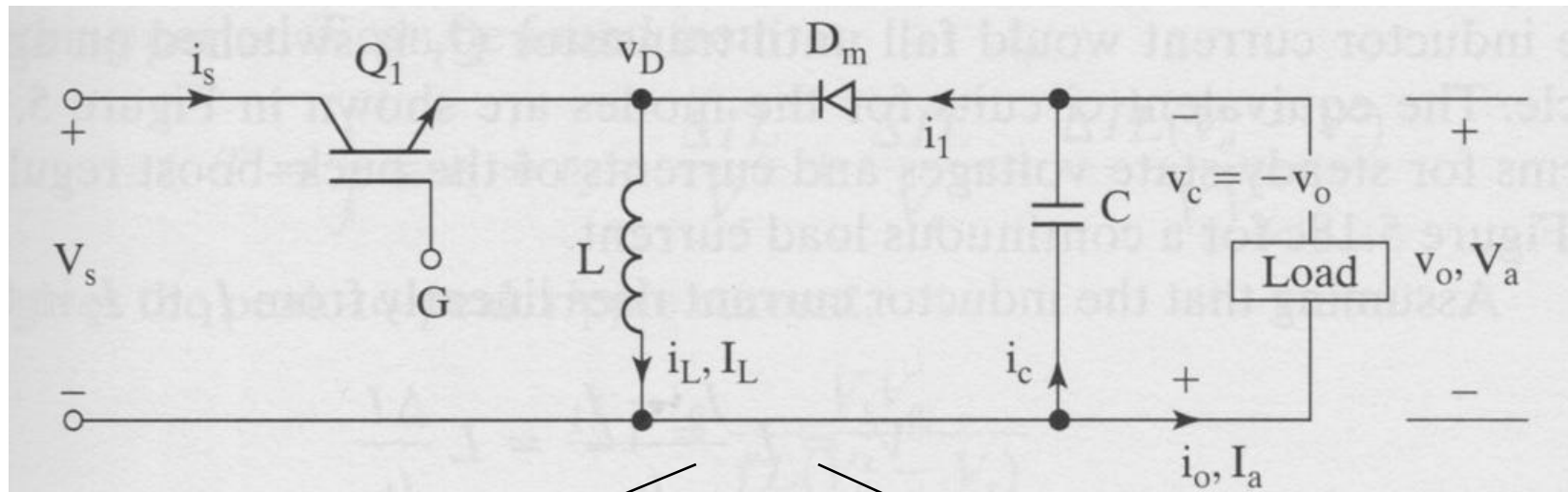


$$V_a = -\frac{k}{1-k} V_s \longrightarrow \text{Voltage polarity is changed}$$

# Comparison of basic converters

Buck

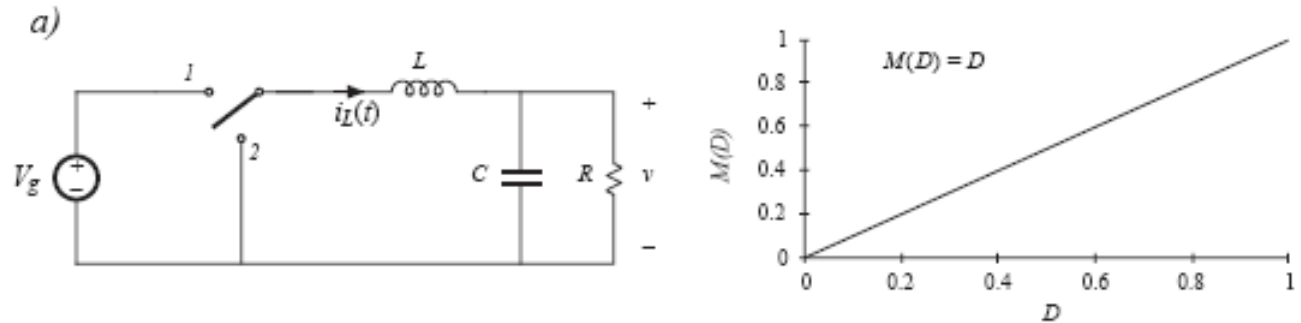

Boost

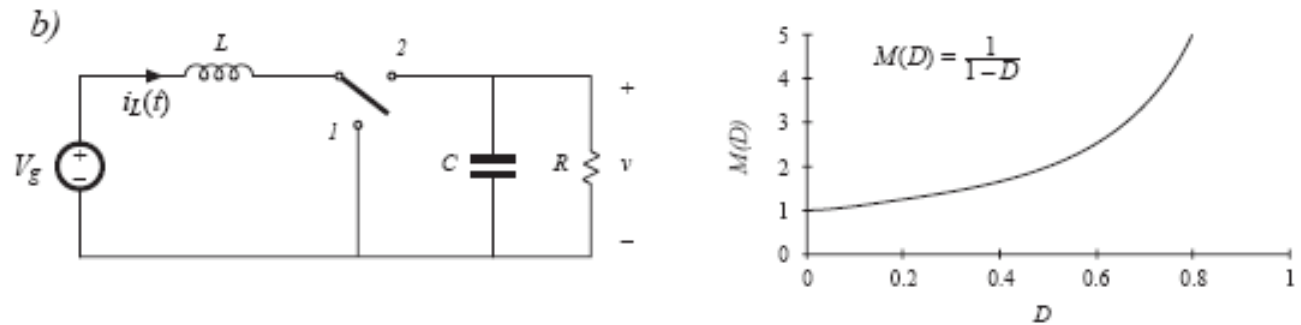

Buck-boost



### 3. Closed-loop control of DC-DC converters

- As have been seen, the output voltage of a DC-DC converter is related to the duty cycle  $k$  (or  $D$ ). In practice, one will never get an accurate output voltage if the duty cycle is fixed at the calculated value because
  - The components are not ideal: switching losses, diode voltage drop, inductor resistance etc
  - The load might change
  - There are fluctuations in the supply voltage  $V_s$
  - ...
- A closed-loop controller to regulate the output voltage is needed!

