

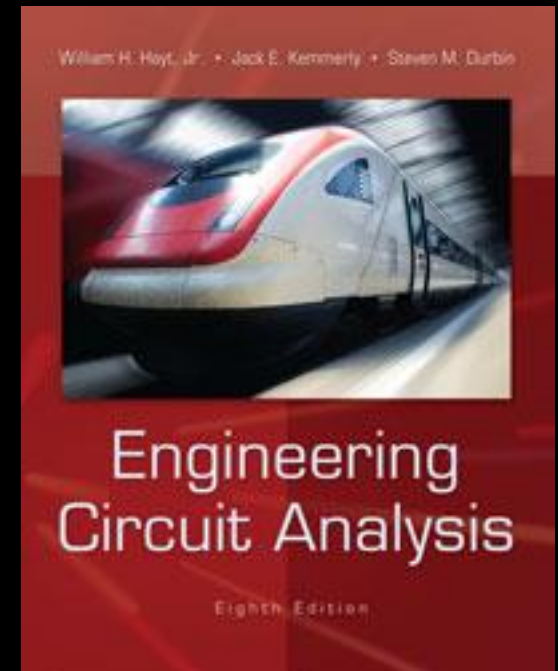


Chapter 3

Voltage and Current Laws

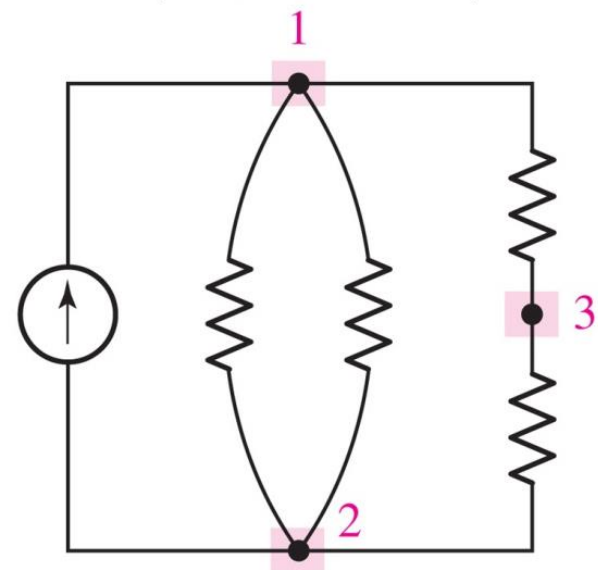


Nodes, Paths, Loops, Branches

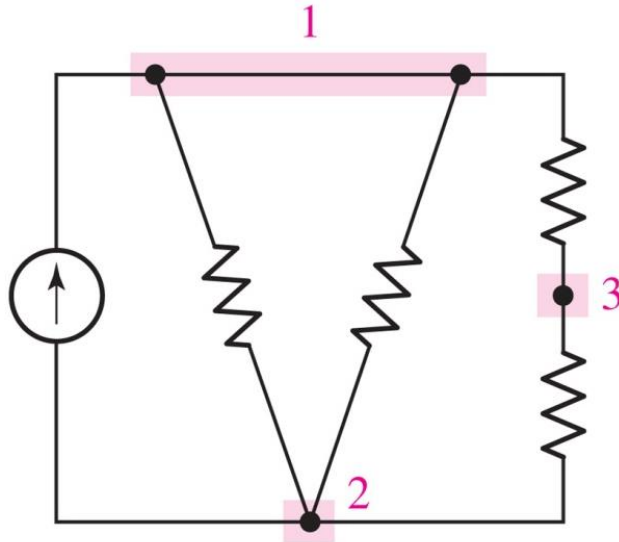

- these two networks are equivalent
- there are three *nodes* and five *branches*
- a *path* is a sequence of nodes
- a *loop* is a closed (circular) path

Kirchhoff's Current Law

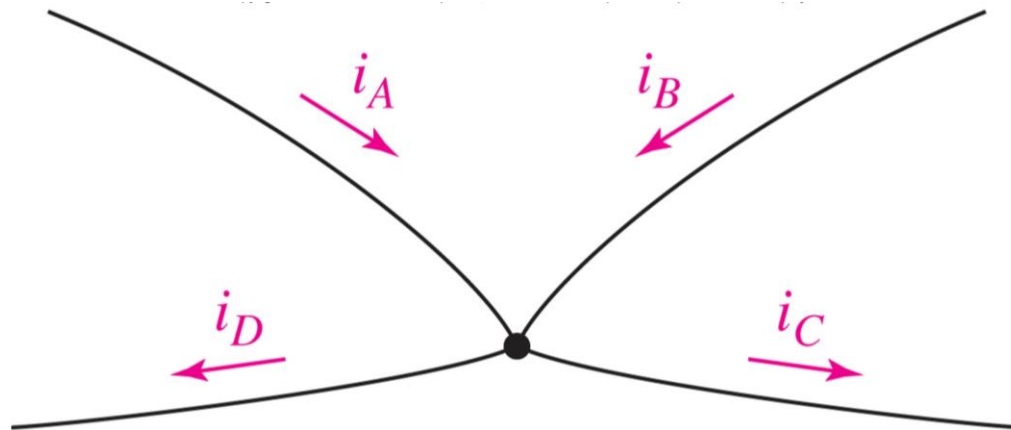KCL: The algebraic sum of the currents entering any node is zero.



$$i_A + i_B + (-i_C) + (-i_D) = 0$$

KCL: Alternative Forms

- Current *IN* is zero:


$$i_A + i_B + (-i_C) + (-i_D) = 0$$

- Current *OUT* is zero:

$$(-i_A) + (-i_B) + i_C + i_D = 0$$


- Current *IN*=*OUT*:

$$i_A + i_B = i_C + i_D$$

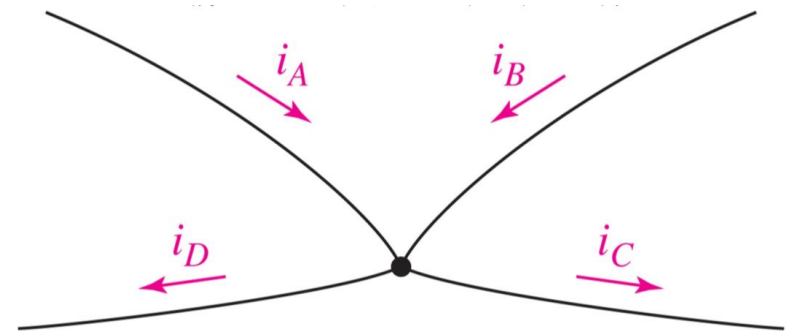

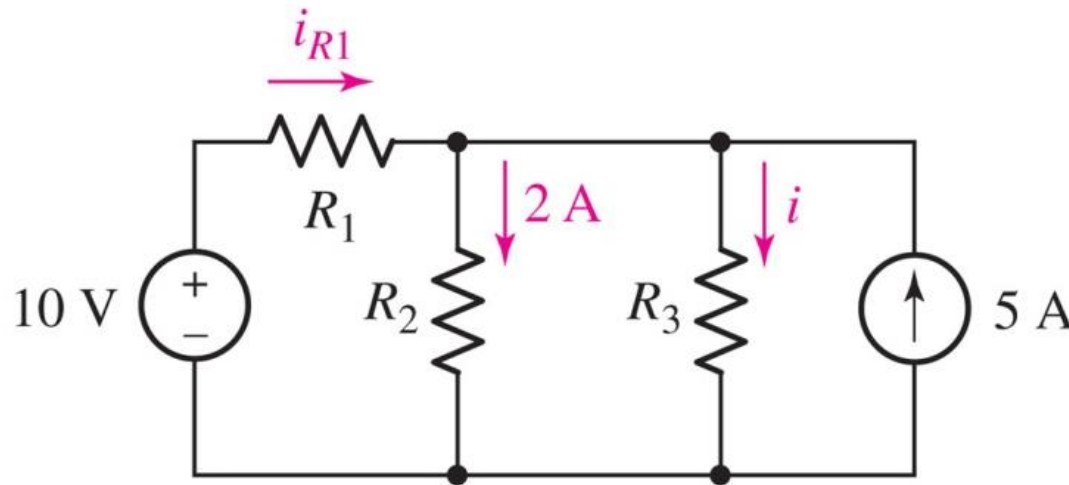Example of KCL Application

Find the current through resistor R_3 if it is known that the voltage source supplies a current of 3 A.




Answer: $i = 6\text{ A}$

E.g. 3.1

Kirchhoff's Voltage Law

KVL: The algebraic sum of the voltages around any closed path is zero.

$$v_1 + (-v_2) + (-v_3) = 0$$

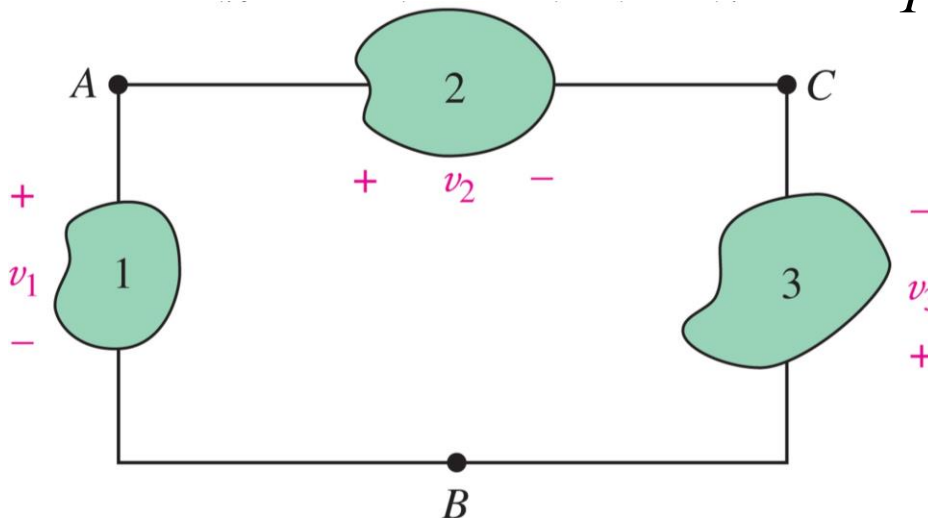

KVL: Alternative Forms

- Sum of *RISES* is zero (clockwise from B):


$$v_1 + (-v_2) + v_3 = 0$$

- Sum of *DROPS* is zero (clockwise from B):

$$(-v_1) + v_2 + (-v_3) = 0$$


- Two paths, same voltage (A to B):

$$v_1 = (-v_3) + v_2$$

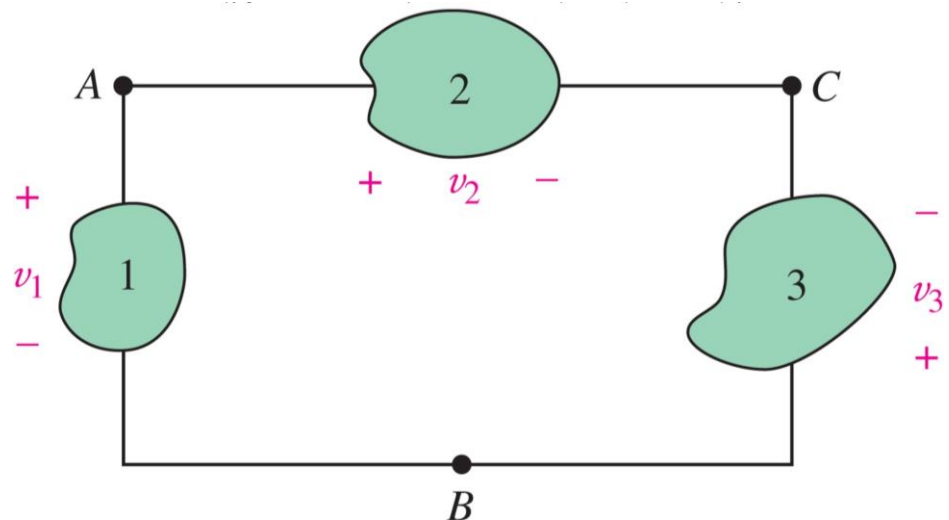

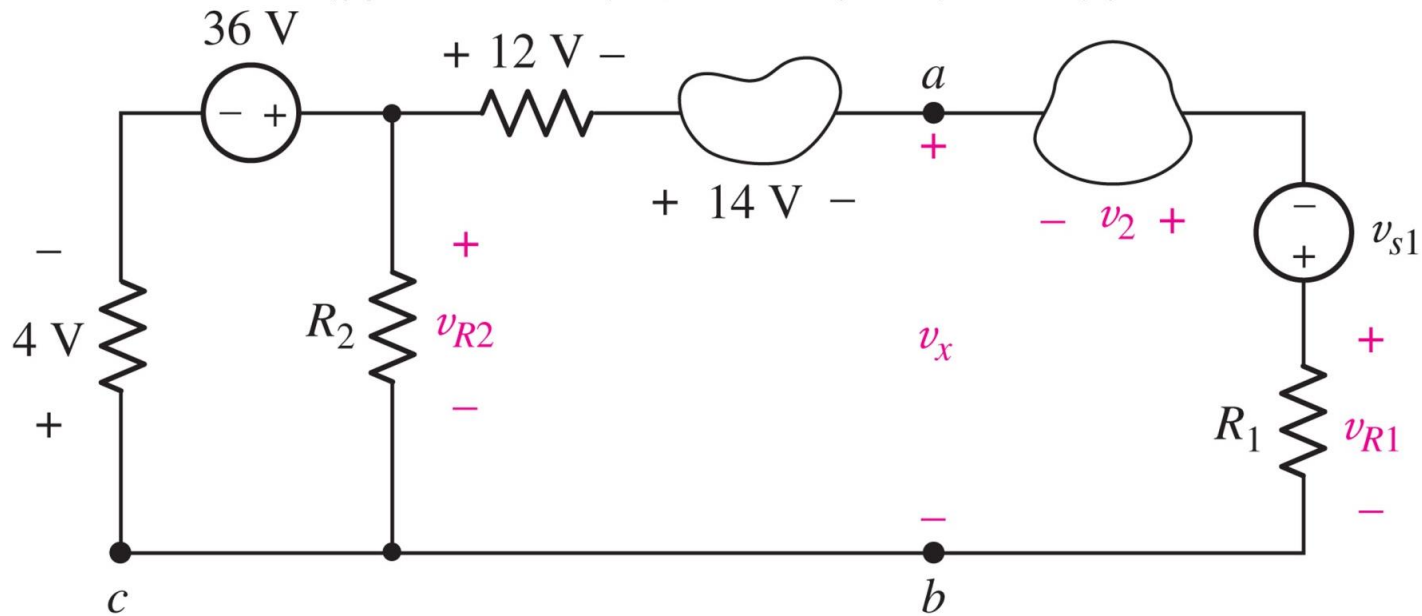Example: Applying KVL

Find v_{R2} (the voltage across R_2) and the voltage v_x .




E.g. 3.3

Answer: $v_{R2} = 32 \text{ V}$ and $v_x = 6 \text{ V}$.

Applying KVL, KCL, Ohm's

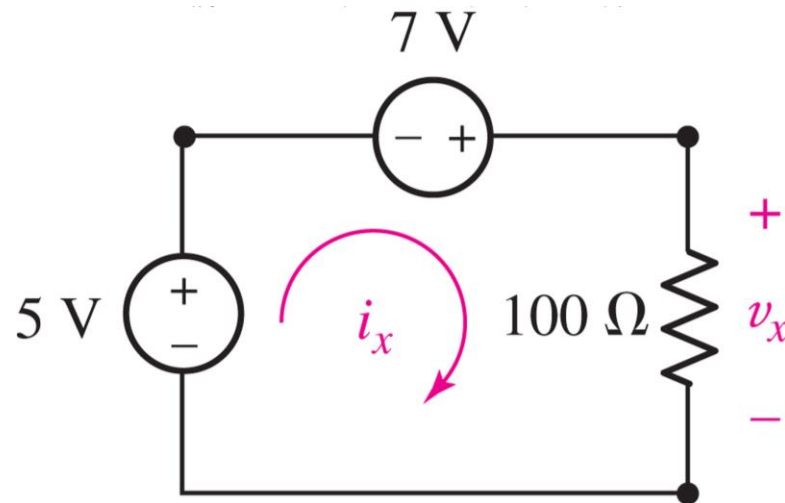
Example: find the current i_x and the voltage v_x



Answer: $v_x = 12\text{ V}$ and $i_x = 120\text{ mA}$

Applying KVL, KCL, Ohm's

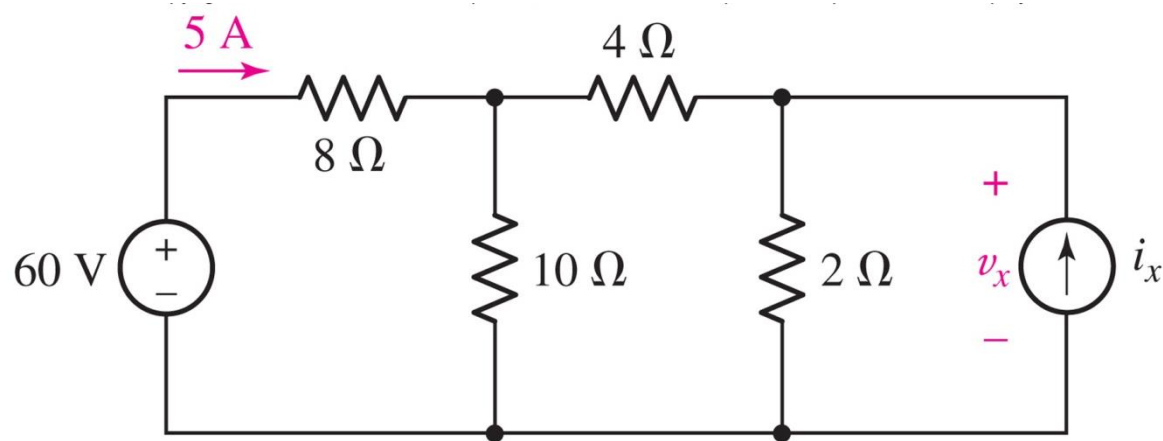Solve for the voltage v_x and the current i_x




Answer: $v_x = 8\text{ V}$ and $i_x = 1\text{ A}$

E.g. 3.4


Series Connections

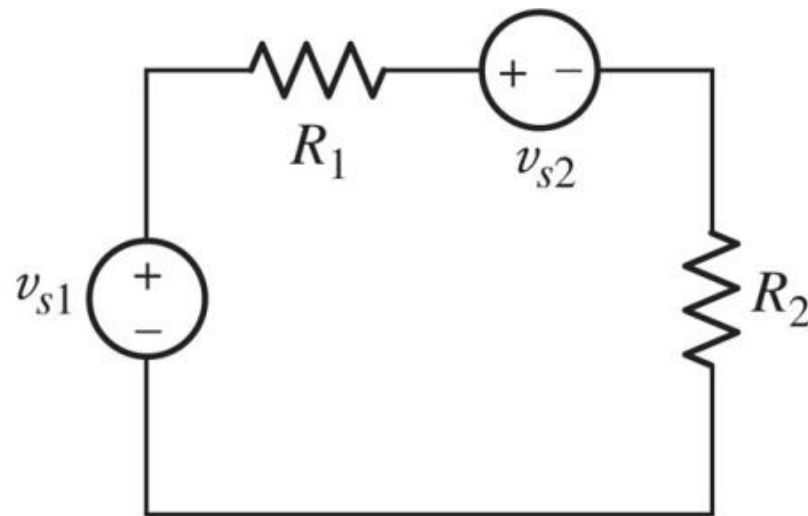All of the elements in a circuit that carry the same current are said to be connected in **series**.




Parallel Connections

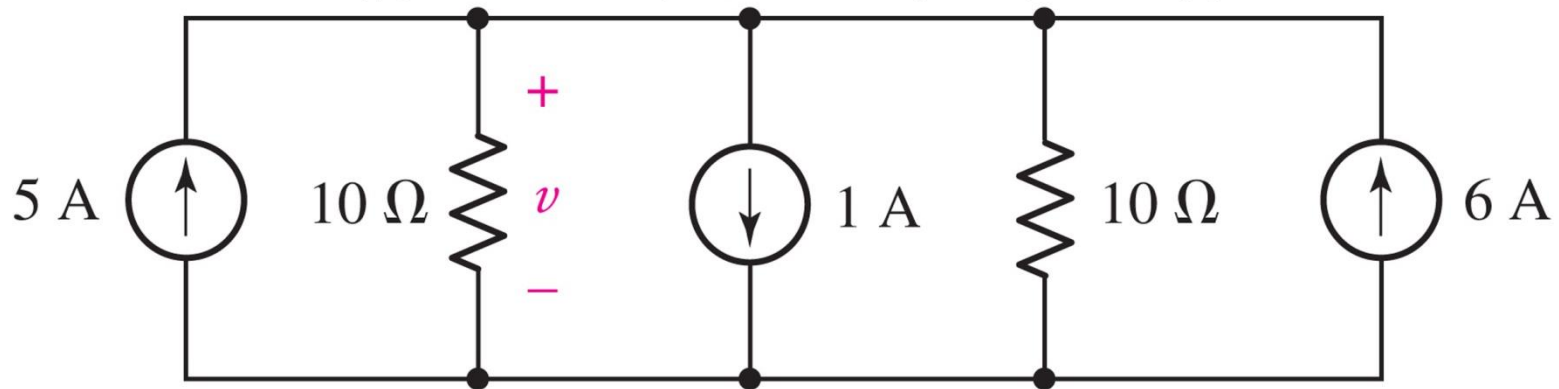Elements in a circuit having a common voltage across them are said to be connected in **parallel**.



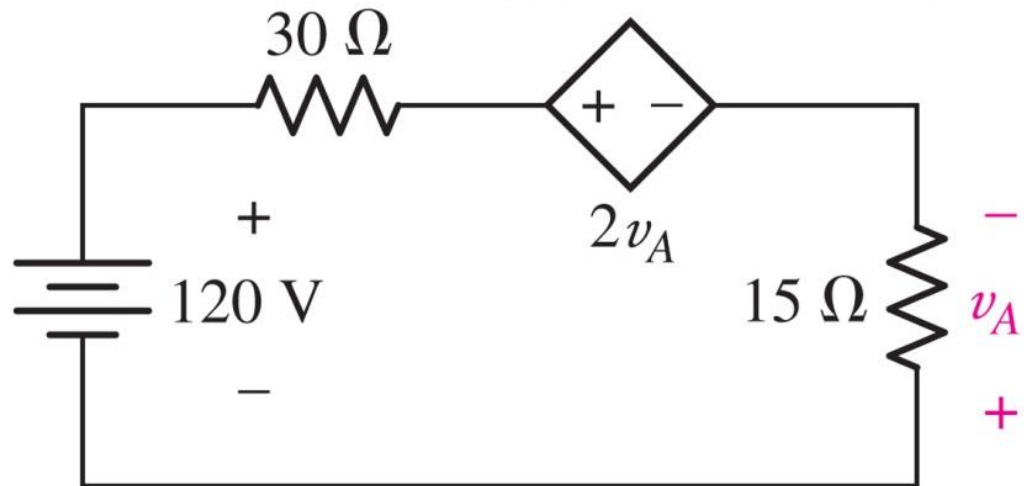Example: Single Loop Circuit

Calculate the power absorbed by each circuit element.



Answer:


$$p_{120V} = -960 \text{ W}, p_{30} = 1920 \text{ W}$$

$$p_{dep} = -1920 \text{ W}, p_{15} = 960 \text{ W}$$

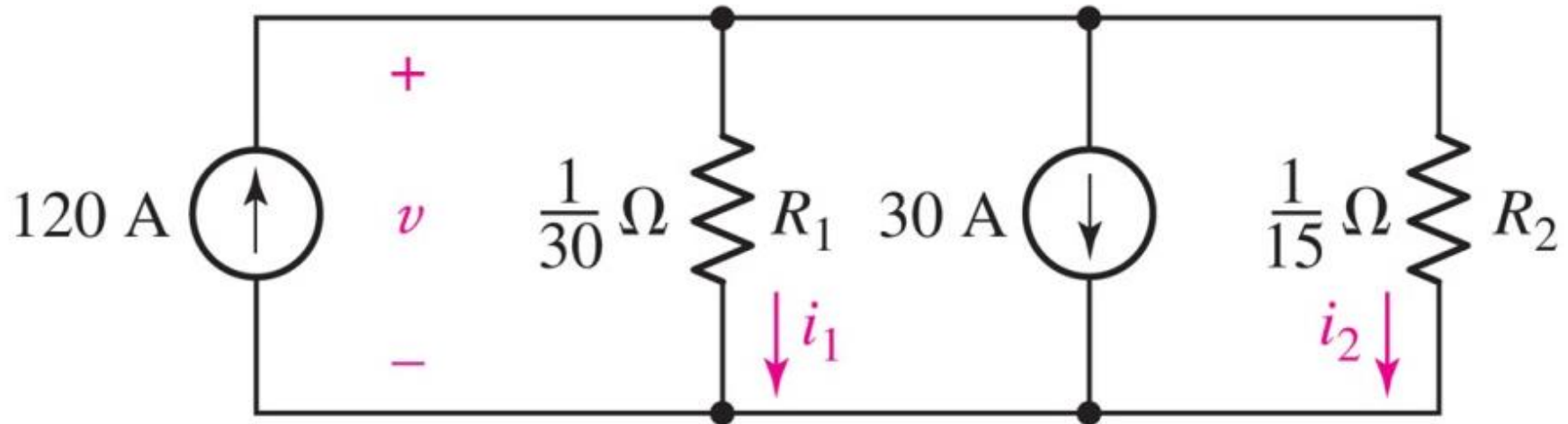Example:

Single Node-Pair Circuit

Find the voltage v and the currents i_1 and i_2 .




Answer: $v = 2 \text{ V}$, $i_1 = 60 \text{ A}$, and $i_2 = 30 \text{ A}$

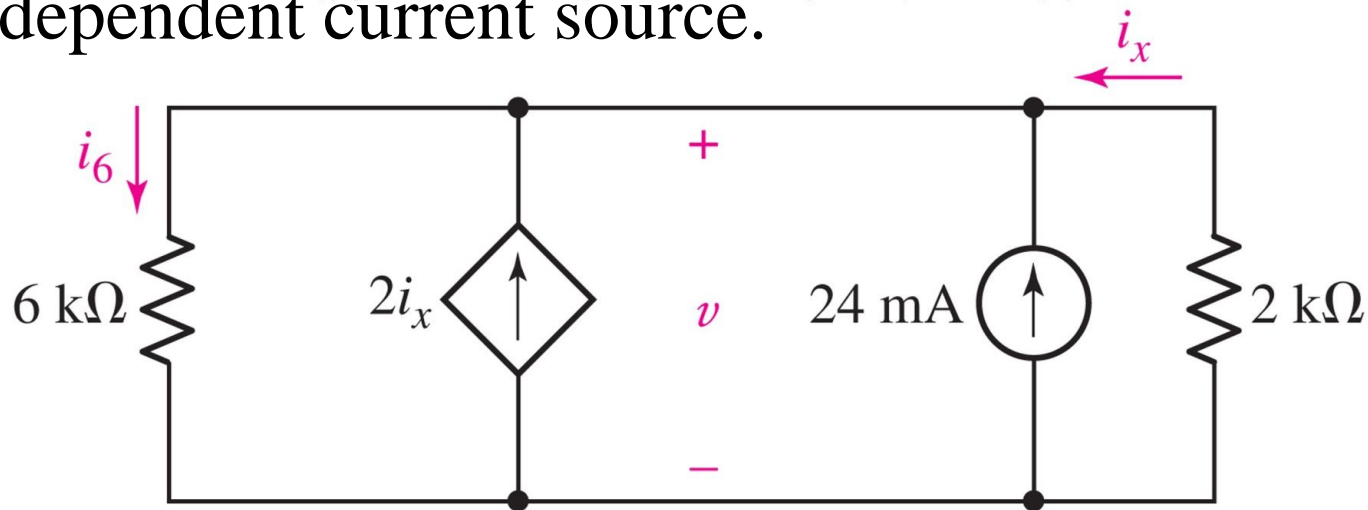Example:

Single Node-Pair Circuit


Determine the value of v and the power supplied by the independent current source.



Answer: $v = 14.4\text{ V}$, power from current source is 345.6 mW


Series and Parallel Sources

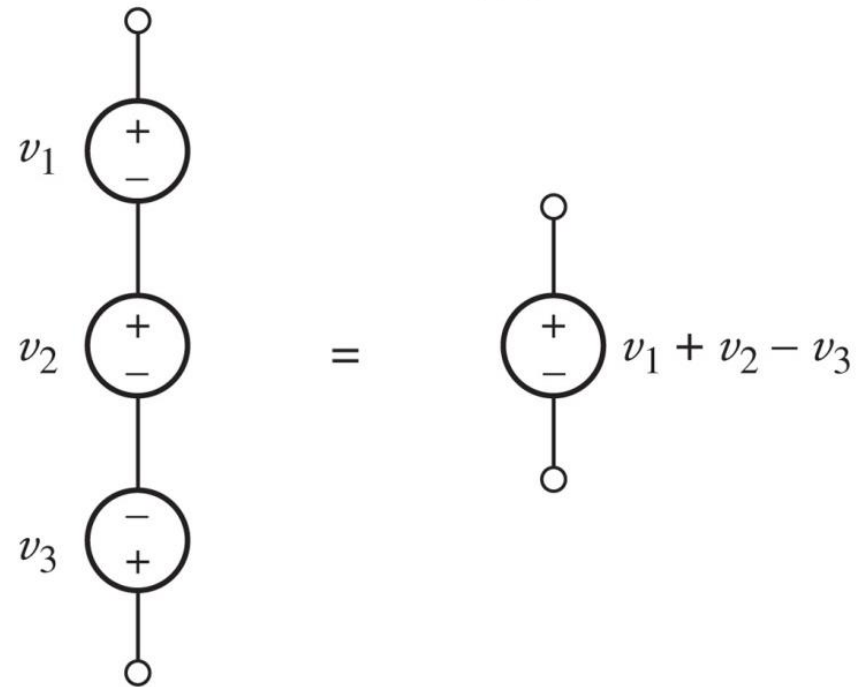Voltage sources
connected in series
can be combined
into an equivalent
voltage source:




Series and Parallel Sources

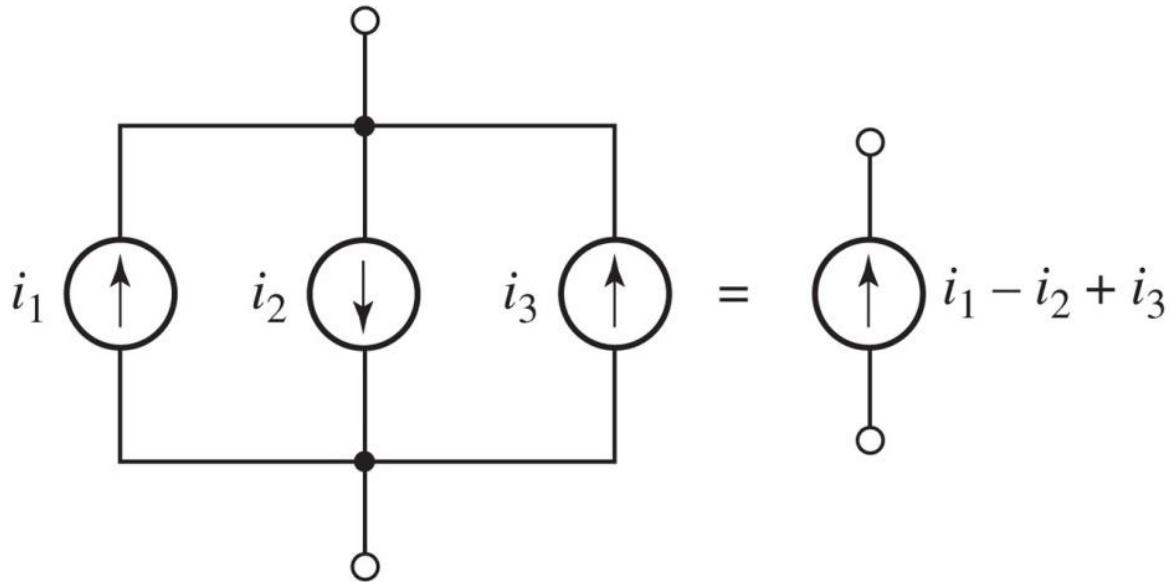Current sources connected in parallel can be combined into an equivalent current source:




Impossible Circuits

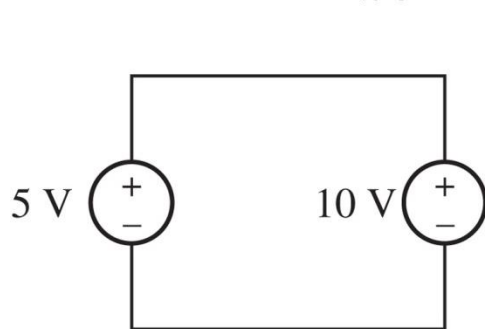
- Our circuit models are idealizations that can lead to apparent physical absurdities:



(a)

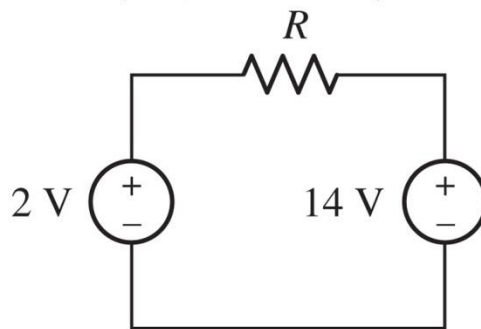



(b)

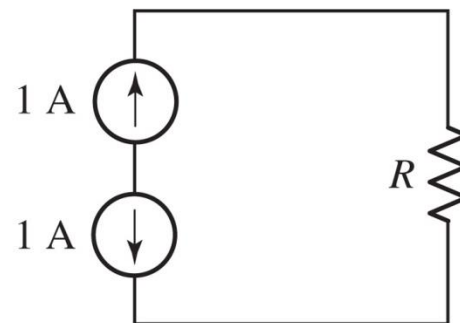

(c)

- V_s in parallel (a) and I_s in series (c) can lead to “impossible circuits”

Resistors in Series


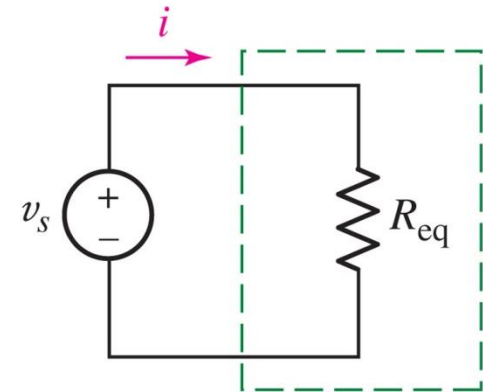
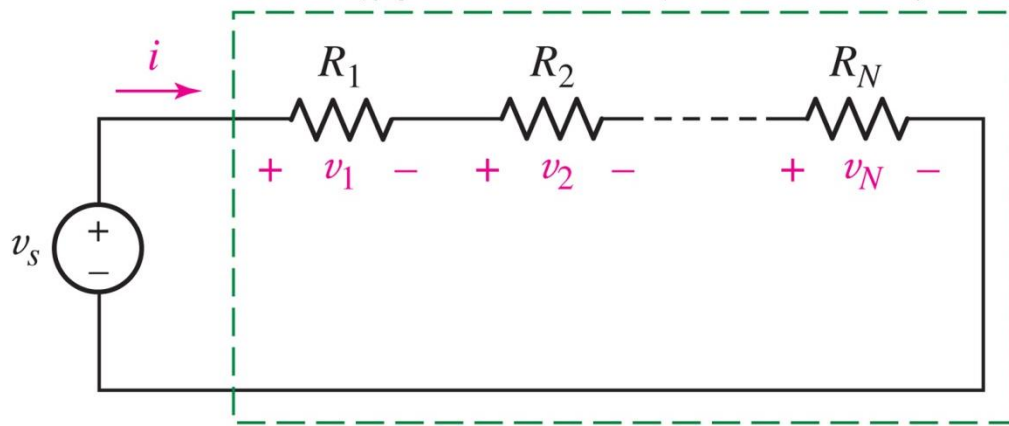


Using KVL shows:

$$R_{eq} = R_1 + R_2 + \dots + R_N$$

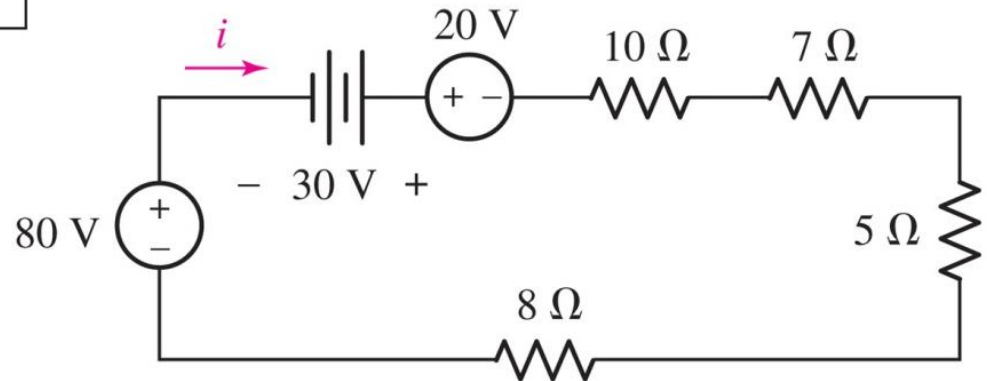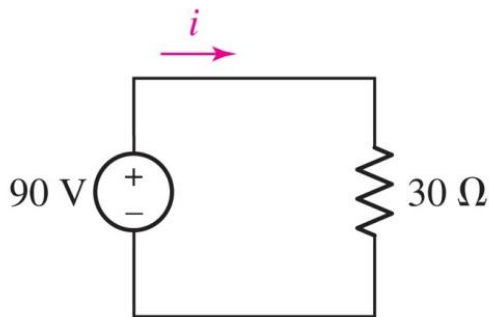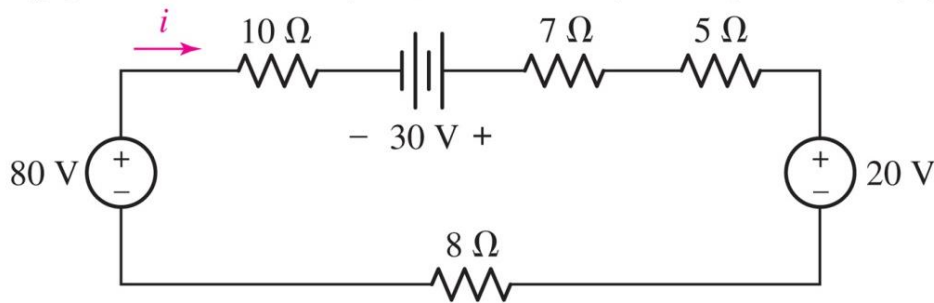
Example: Circuit Simplifying

Find i and the power supplied by the 80 V source.



Answer: $i = 3\text{ A}$ and $p = 240\text{ W}$ supplied

Resistors in Parallel

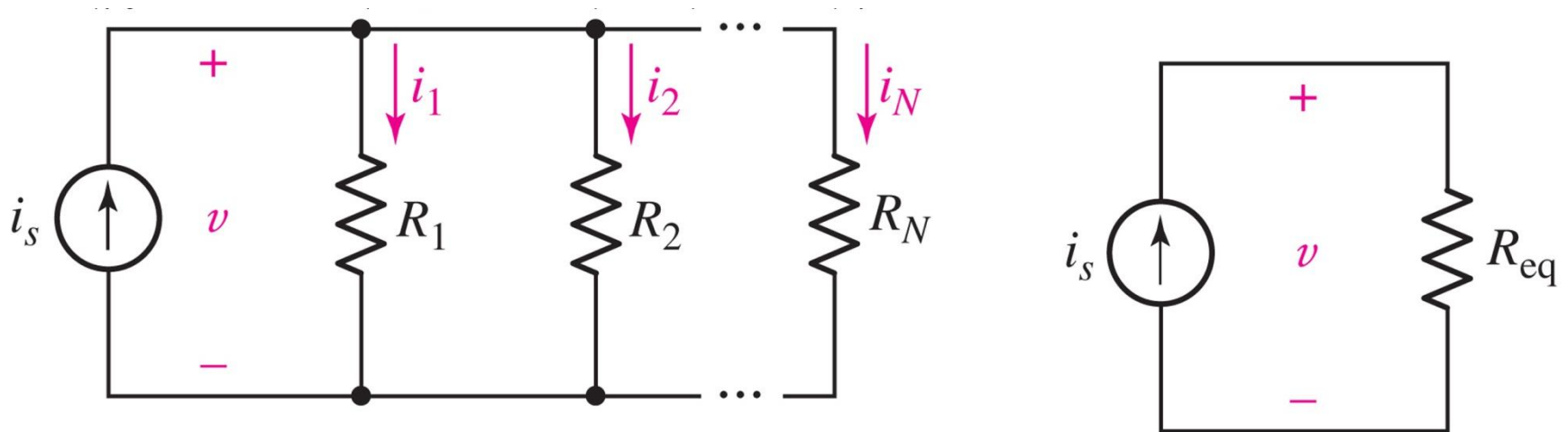

Using KCL shows:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

Two Resistors in Parallel

$$R_{\text{eq}} = R_1 \parallel R_2$$

$$= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

Two resistors in parallel can be combined using the **product / sum** shortcut.


Connecting resistors in parallel makes the result *smaller* :

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$

$$0.5 \min(R_1, R_2) < R_1 \parallel R_2 < \min(R_1, R_2)$$

Voltage Division

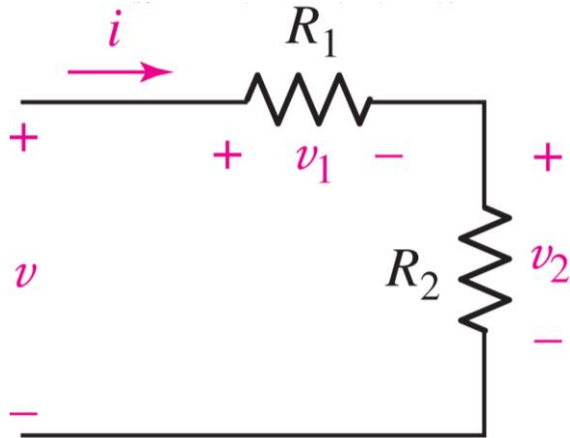Resistors in series “share” the voltage applied to them.





$$v_1 = \frac{R_1}{R_1 + R_2} v$$

$$v_2 = \frac{R_2}{R_1 + R_2} v$$

Example: Voltage Division


Find v_x

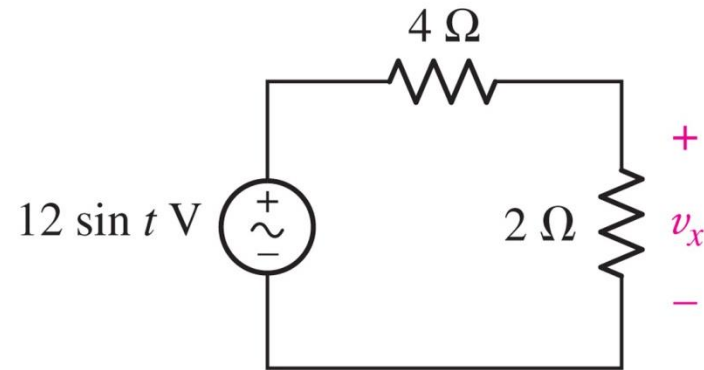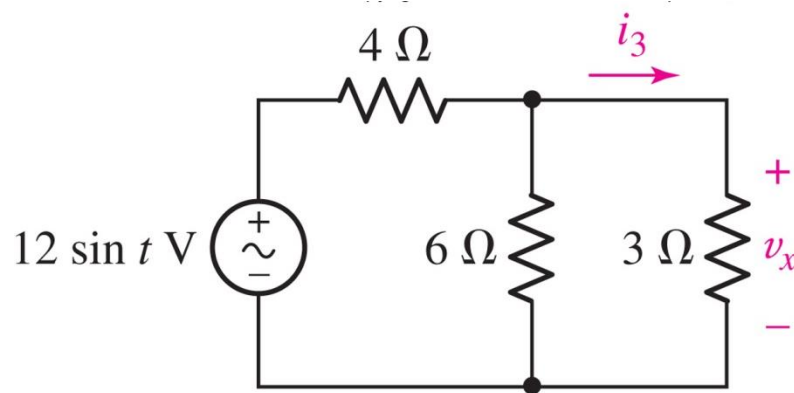

Answer: $v_x(t) = 4 \sin t\text{ V}$

Current Division

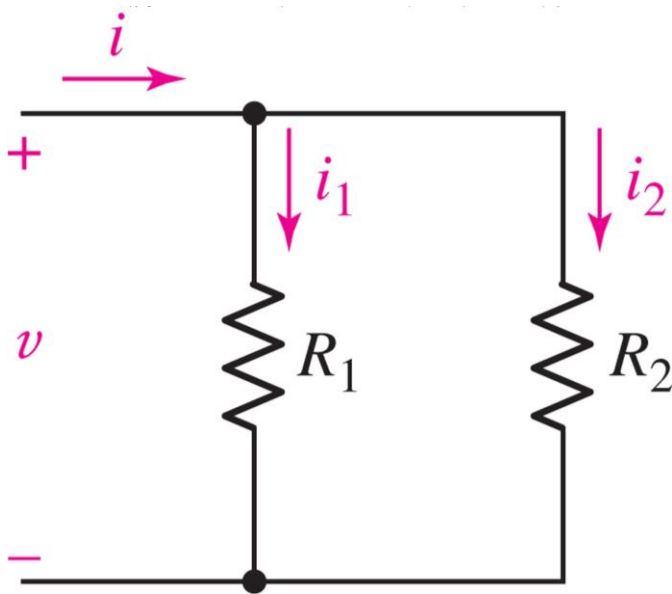Resistors in parallel “share” the current through them.




$$i_1 = i \frac{R_2}{R_1 + R_2}$$

$$i_2 = i \frac{R_1}{R_1 + R_2}$$

Example: Current Division

Find $i_3(t)$

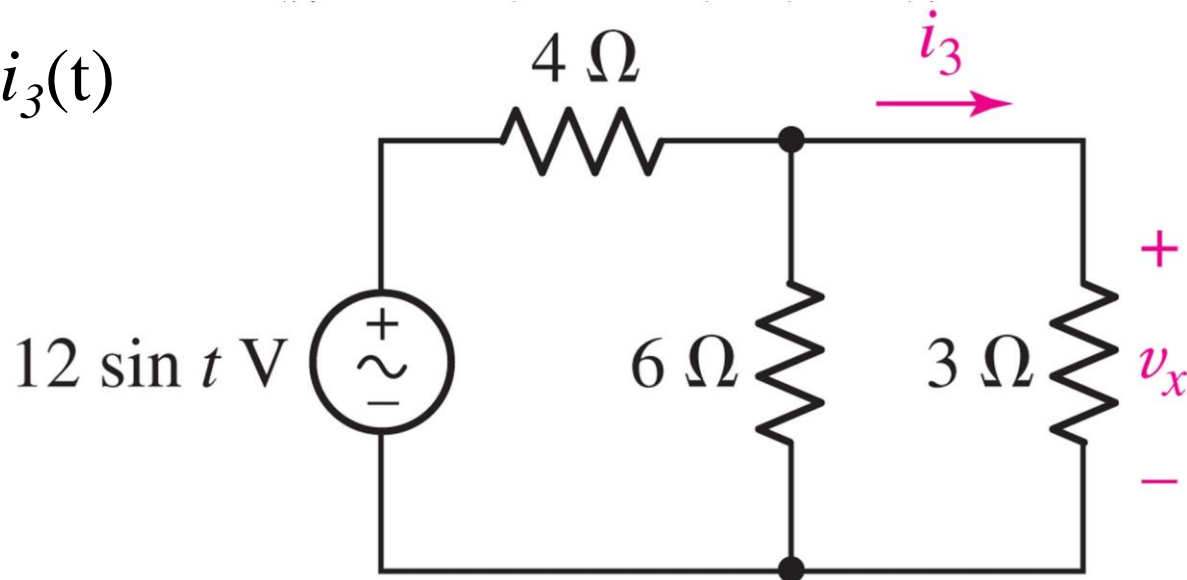

Answer: $i_3(t) = 1.333 \sin t \text{ V}$