

EEE104 – Digital Electronics (I)

Lecture 13

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

1


In This Session

Flip-Flops and Related Devices

- Latches
- Edge-Triggered Flip-Flops
- Flip-Flop Applications

2


Latches – The S-R Latch

 

- A latch is a bistable digital circuit used for storing a bit.
- An S-R latch with active – LOW inputs is formed with two NAND gates.
- The output of one gate is fed back to the input of the other.

3

Latches – The S-R Latch

 


How does it work?

1. Suppose that \bar{S} and \bar{R} are both 1 originally.
2. When a negative pulse appears at \bar{S} , i.e. $\bar{S} = 0$, then $Q = 1$, $\bar{Q} = 0$.
3. When the pulse finishes, i.e. $\bar{S} = 1$, Q is still 1 and \bar{Q} is still 0.

So the low-level pulse at \bar{S} **sets** the output Q to 1.

4

Latches – The S-R Latch

 


How does it work?

1. Suppose that /S and /R are both 1 originally.
2. When a negative pulse appears at /R, i.e. /R = 0, then /Q = 1 and Q = 0.
3. When the pulse finishes, i.e. /R = 1, Q is still 0 and /Q is still 1.

So the low-level pulse at /R **resets** the output Q to 0.

5

Latches – The S-R Latch

 

How does it work? $Q = 1 \cdot \overline{Q} = \overline{Q} = Q$
 $\overline{Q} = 1 \cdot \overline{Q} = \overline{Q}$


1. When both /S and /R are 1, the outputs will not be changed.
2. What will happen when both /S and /R are 0?

- Both Q and /Q will become 1.
- When /S and /R become HIGH simultaneously, the outputs are ideally LOW but uncertain due to the competition in gate speed.

6

Latches – The S-R Latch

 An S-R latch with active-LOW inputs is formed using NAND gates.




INPUTS		OUTPUTS		COMMENTS
\overline{S}	\overline{R}	Q	\overline{Q}	
1	1	NC	NC	No change. Latch remains in present state.
0	1	1	0	Latch SET.
1	0	0	1	Latch RESET.
0	0	1	1	Invalid condition

7

Latches – The S-R Latch

 An S-R latch with active-HIGH inputs is formed using NOR gates.




INPUTS		OUTPUTS		COMMENTS
S	R	Q	\overline{Q}	
0	0	NC	NC	No change. Latch remains in present state.
0	1	0	1	Latch RESET.
1	0	1	0	Latch SET.
1	1	0	0	Invalid condition

8

Latches – The S-R Latch

 
- A NAND gate is equivalent to a negative-OR gate.
- Hence the S-R Latch equivalent implementation.
- It will be used extensively later.



9

Latches – The S-R Latch

 An Example: For a latch with active-LOW inputs




10

Latches – The S-R Latch

Application Example


The latch as a contact-bounce eliminator

 

11

Latches – The Gated S-R Latch

 
- A gated latch is a latch with an enable input EN.
- The latch will not change until EN is HIGH. Otherwise it is like an S-R latch with active-LOW inputs $/S = 1$ and $/R = 1$.



12

Latches – The Gated S-R Latch

 
An Example: For a latch with active-HIGH inputs



13

Latches – The Gated D Latch

 
- It has only one input in addition to EN.
- When $D = 1$ and $EN = 1$, $Q = 1$.
- When $D = 0$ and $EN = 1$, $Q = 0$.
- Output Q follows the input D when EN is HIGH.



14

Latches – The Gated D Latch

An Example:

 

15