

Lecture 7
of
EEE307

Electronics for Communications

**Department of Electrical & Electronic Engineering
Xi'an Jiaotong-Liverpool University (XJTLU)**

Friday, 1st November 2019

- ❑ Mixer in transceivers
- ❑ Mixer mathematics
 - frequency translation by switching action
- ❑ MOSFET & diode implementations
 - single-balanced & double-balanced
 - diode as a switch




Wireless Communication Systems

(frequency translation)

- ❑ In wireless communication systems, there is a common need to **translate** signals from one **frequency** to another.
 - The **carrier frequency** at which data is transmitted using **electromagnetic (EM) waves** propagating in air (or in space) can be from about 30 MHz to 300 GHz.
 - The frequency of the baseband signals is typically below 10 MHz: bandwidth for analogue voice signals ≈ 3.1 kHz;

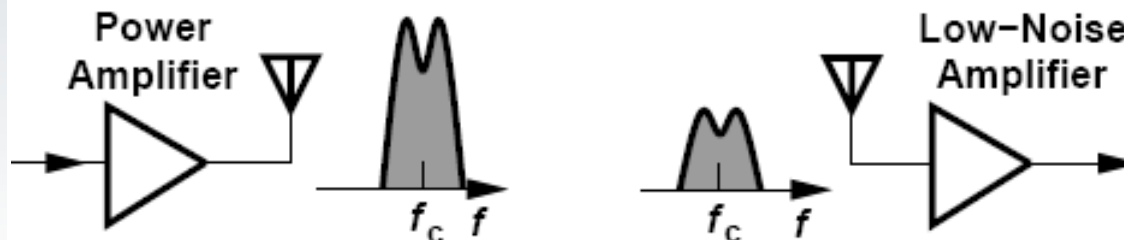≈ 6 MHz (4.2 MHz if video only) for TV signals.




From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.

Wireless Communication Systems

(frequency translation)

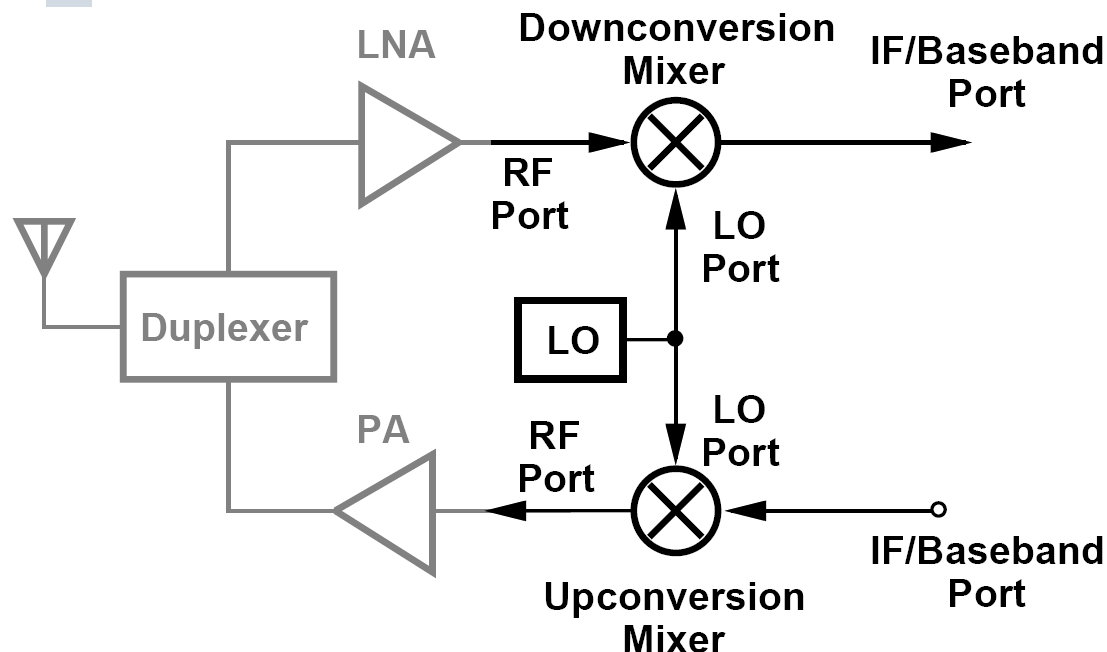- ❑ To **translate** radio frequency (RF) signals from the **carrier frequency** to lower frequencies (e.g. baseband or intermediate frequency) and vice versa, a **mixer** is needed. From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.




- A mixer appears in the receive path and the transmit path, respectively called **downconversion mixer** and **upconversion mixer**.

RF Mixer

(frequency translation)

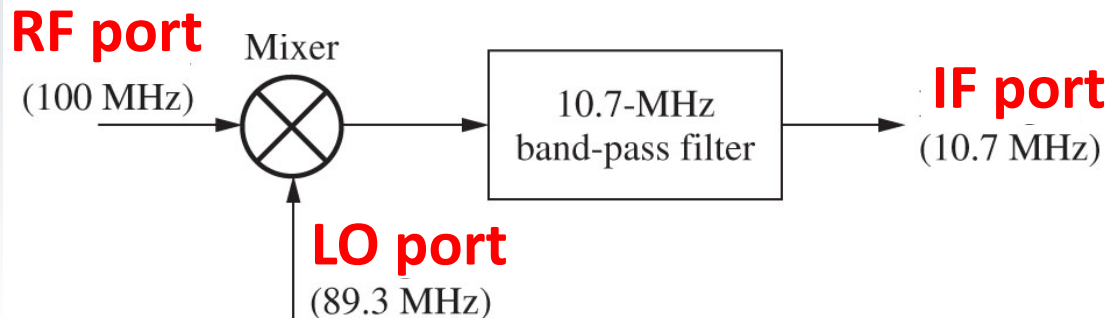- A **mixer** perform **frequency translation** by *multiplying* two waveforms (and perhaps their harmonics too).
 - For this reason, a mixer has three distinctly different ports.
 - In a wireless transmitter or receiver, the three ports of a mixer are typically called the **RF port**, **LO port** and **IF port**, where **LO**: local oscillator, **IF**: intermediate frequency.



Adapted from: R. C. Jaeger & T. N. Blalock,
Microelectronic Circuit Design, 4e,
© 2010 McGraw-Hill, USA.



Xi'an Jiaotong-Liverpool University
西交利物浦大學


RF Mixer – frequency translation

(multiplication of two waveforms)

- The **frequency translation** performed by the **multiplication** of two waveforms in a **mixer** is obvious by looking at the product of two sinusoidal waveforms.

➤ Using standard trigometric identities,
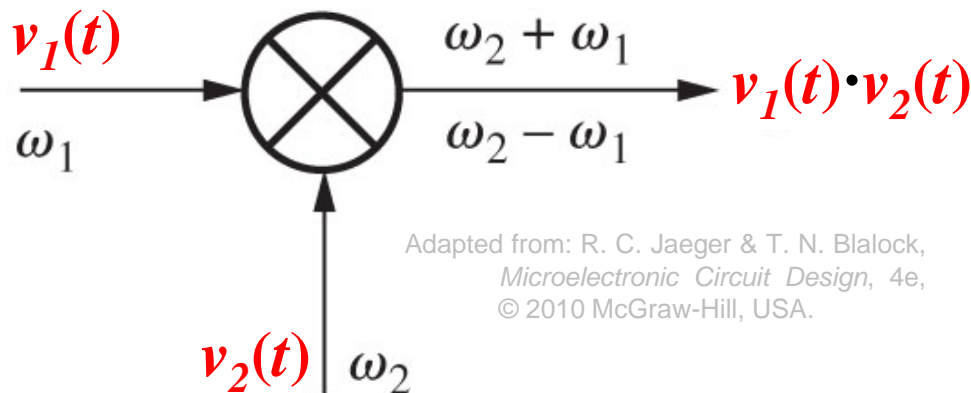
$$v_1(t) \cdot v_2(t) = A_1 \sin(\omega_1 t) \cdot A_2 \sin(\omega_2 t) = A_1 A_2 \frac{\cos[(\omega_2 - \omega_1)t] - \cos[(\omega_2 + \omega_1)t]}{2}$$



Adapted from: R. C. Jaeger & T. N. Blalock,
Microelectronic Circuit Design, 4e,
© 2010 McGraw-Hill, USA.

- The ideal mixer output contains signal components at frequencies $(\omega_2 - \omega_1)$ & $(\omega_2 + \omega_1)$.




Xi'an Jiaotong-Liverpool University
西交利物浦大学

RF Mixer – frequency translation

(downconversion & upconversion)

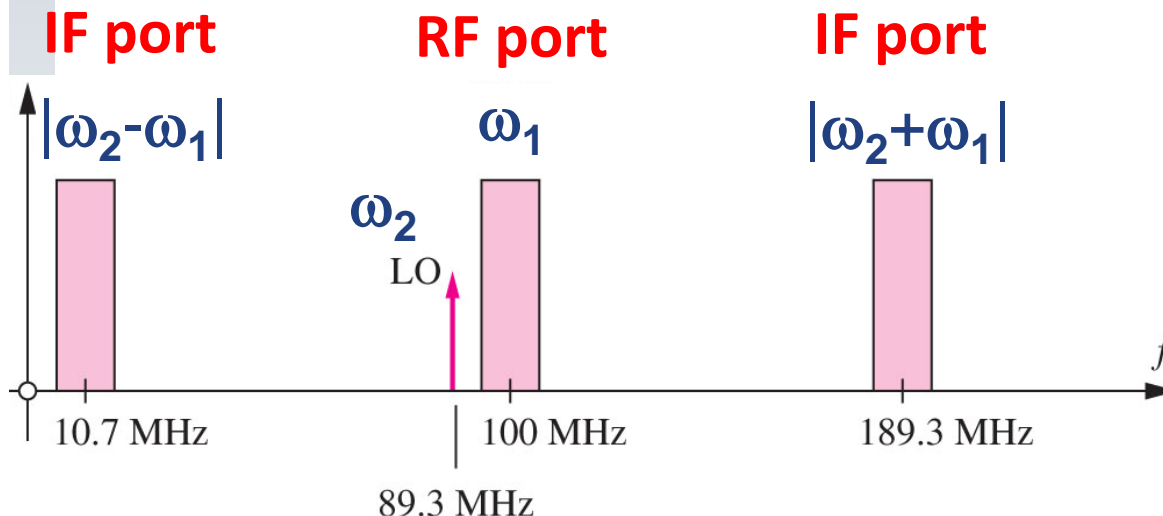- ❑ In a **downconversion mixer** in the receive path, the signal component of the frequency difference ($\omega_2 - \omega_1$) is selected using a filter.
- ❑ In an **upconversion mixer**, the signal component of the frequency sum ($\omega_2 + \omega_1$) is selected.



Adapted from: R. C. Jaeger & T. N. Blalock,
Microelectronic Circuit Design, 4e,
© 2010 McGraw-Hill, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大学


RF Mixer – signal multiplication

(switch as a non-linear device)

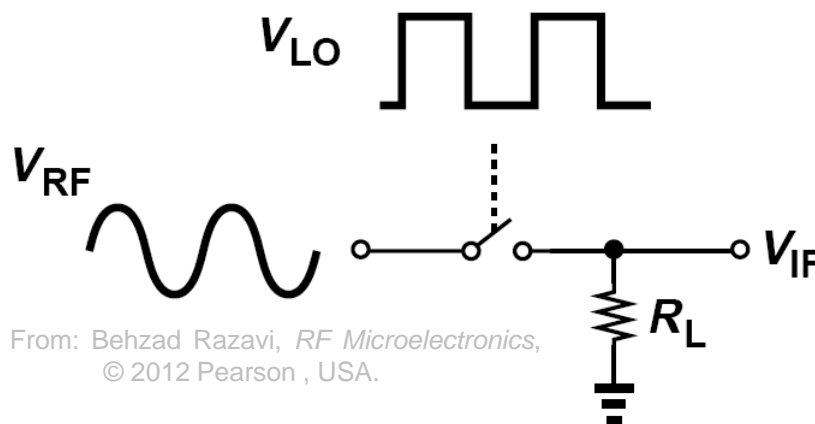- ❑ In general, any **non-linear** device can be used for **multiplying** of two waveforms and hence can work as a **mixer**.
- ❑ A **switch** is such a **non-linear device** for **multiplying** two signals to achieve the **frequency translation**.



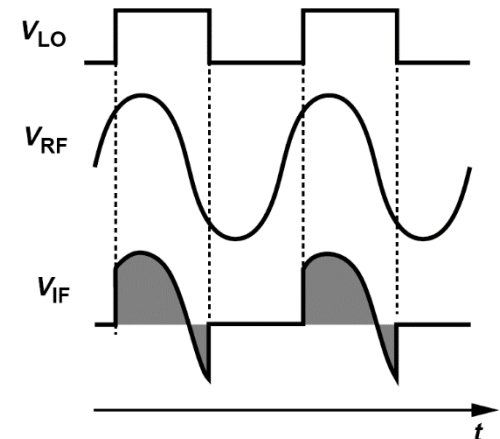From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.



➤ What is the frequency spectrum like?





Xi'an Jiaotong-Liverpool University
西交利物浦大学

RF Mixer – signal multiplication

(mixer mathematics)

- The action of the switch in the time domain is equivalent to a square waveform.

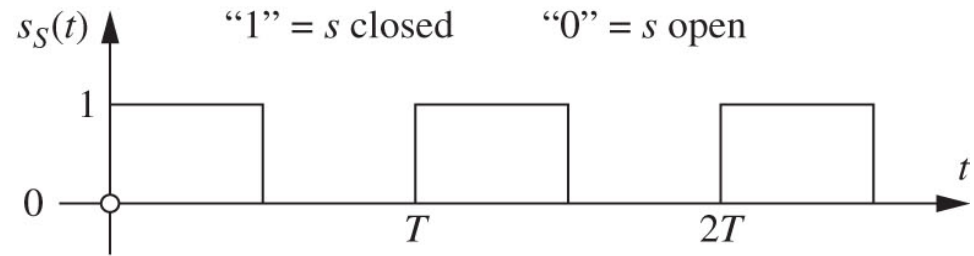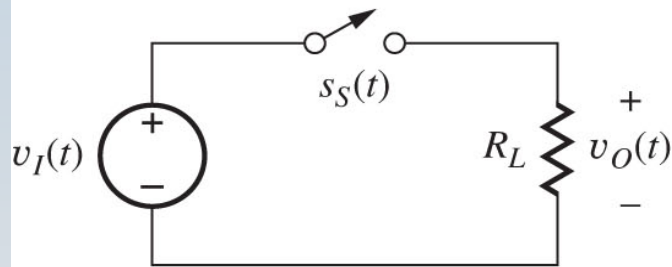Adapted from: R. C. Jaeger & T. N. Blalock,
Microelectronic Circuit Design, 4e,
 © 2010 McGraw-Hill, USA.



$$v_I(t) = A_1 \sin(\omega_1 t)$$

$$s_S(t) = \frac{1}{2} + \frac{2}{\pi} \sum_{n=1,3,\dots} \frac{1}{n} \sin(n\omega_2 t), \text{ with } \omega_2 = \frac{2\pi}{T}$$

$$v_O(t) = v_I(t) \cdot s_S(t) = \frac{A_1}{2} \sin(\omega_1 t) + \frac{2A_1}{\pi} \sum_{n=1,3,\dots} \frac{1}{n} \sin(n\omega_2 t) \sin(\omega_1 t)$$

$$v_O(t) = \frac{A_1}{2} \sin(\omega_1 t) + \frac{2A_1}{\pi} \sum_{n=1,3,\dots} \frac{1}{n} \frac{\cos[(n\omega_2 - \omega_1)t] + \cos[(n\omega_2 + \omega_1)t]}{2}$$




Xi'an Jiaotong-Liverpool University
 西交利物浦大學


RF Mixer – signal multiplication

(spectrum)

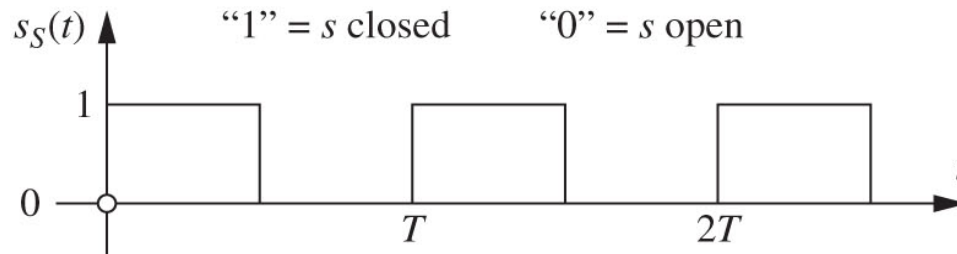- The action of the switch in the time domain is equivalent to a square waveform.


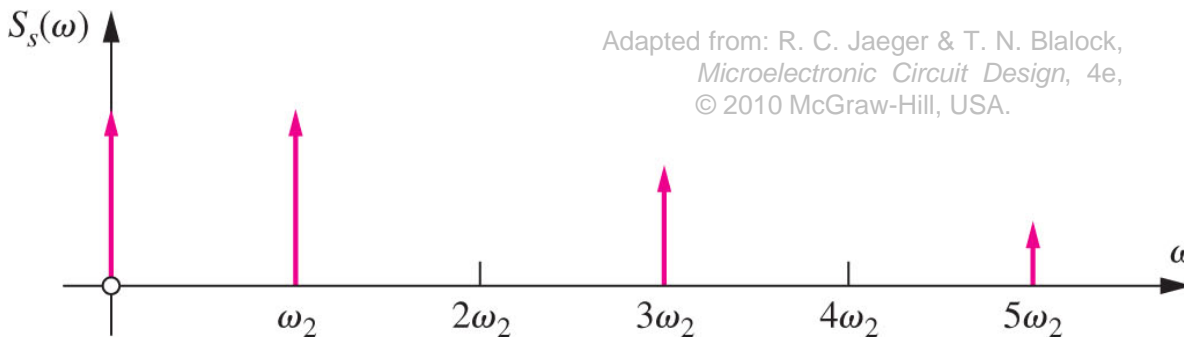
$$s_S(t) = \frac{1}{2} + \frac{2}{\pi} \sum_{n=1,3,\dots} \frac{1}{n} \sin(n\omega_2 t), \text{ with } \omega_2 = \frac{2\pi}{T}$$



Adapted from: R. C. Jaeger & T. N. Blalock,
Microelectronic Circuit Design, 4e,
© 2010 McGraw-Hill, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大学

RF Mixer – signal multiplication

(spectrum)

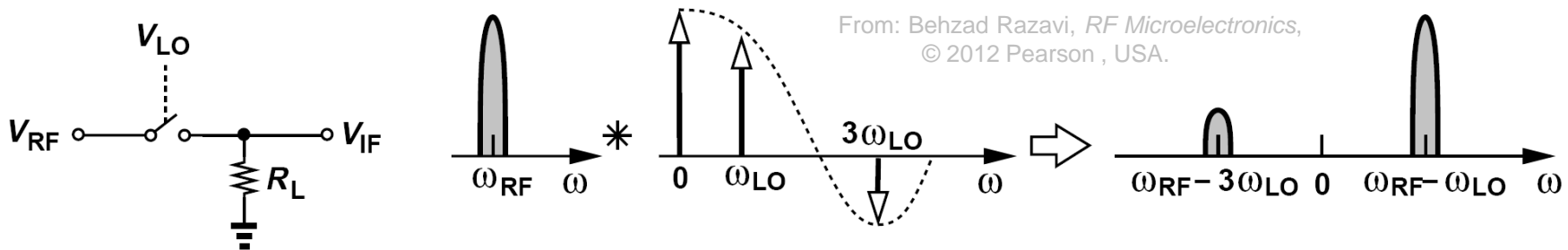
- ❑ In general, any **non-linear** device can be used for **multiplying** of two waveforms and hence can work as a **mixer**.
- ❑ A **switch** is such a **non-linear device** for **multiplying** two signals to achieve the **frequency translation**.



Simple RF Mixer

(using MOS transistor as a switch)

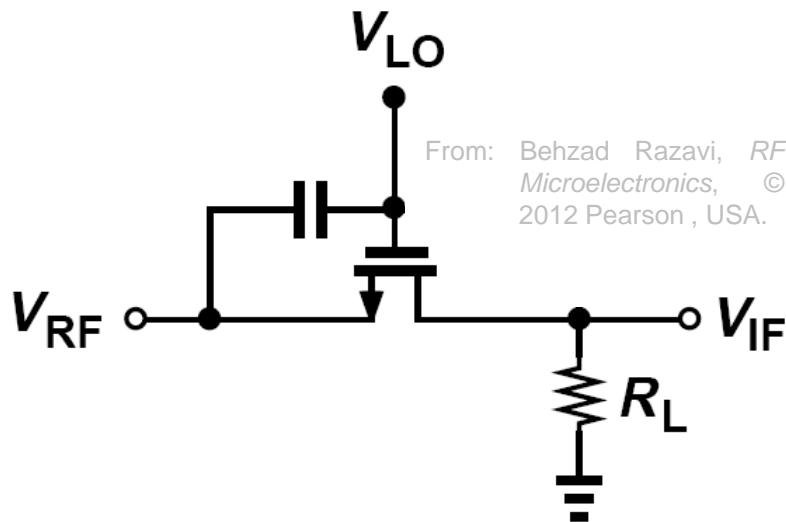- ❑ As a MOS transistor can serve as a switch, it can be used to build a very simple **mixer**.



- Such a mixer operates with a single-ended RF input and a single-ended LO signal.
- It is not an efficient approach as the RF signal is discarded for half of the LO period.

$$v_{IF}(t) = v_{RF}(t) \times \frac{2}{\pi} \sum_{n=1,3,\dots} \frac{1}{n} \sin(n\omega_{LO})t = v_{RF}(t) \times \frac{2}{\pi} \sin(n\omega_{LO})t + \dots$$




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Single-Balanced Passive Mixer

(balanced LO waveforms)

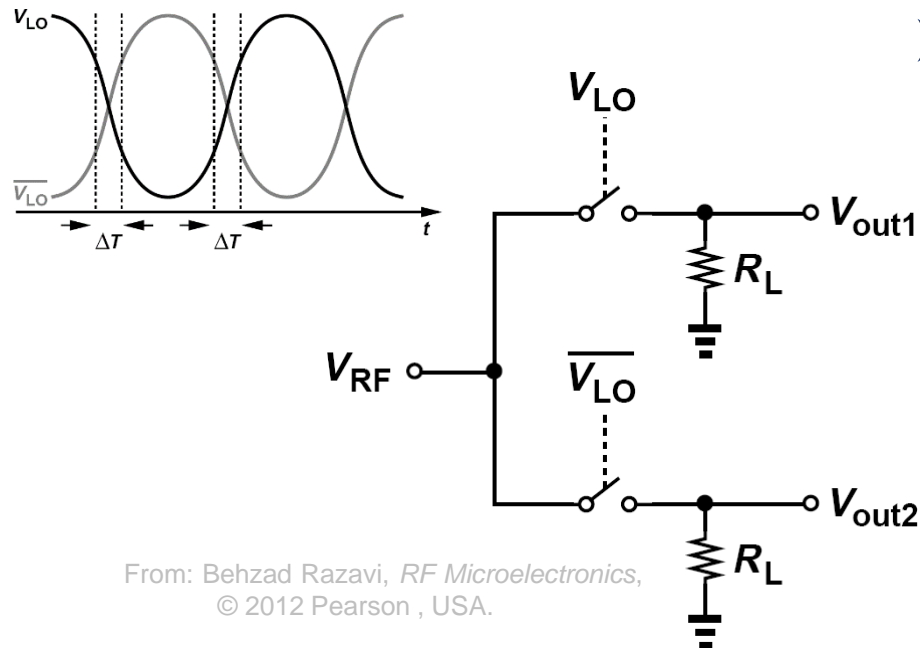- A more efficient approach to the construction of a **mixer** in using the MOS transistor as a switch is to have a differential LO signal to drive two MOS transistor switches.



- The differential LO signal then commutates the RF input to the two outputs.


From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.

Single-Balanced Passive Mixer

(balanced LO waveforms)

- Such a **passive mixer** is called **single-balanced mixer** because of the **balanced** LO waveform in the multiplication with the RF signal.

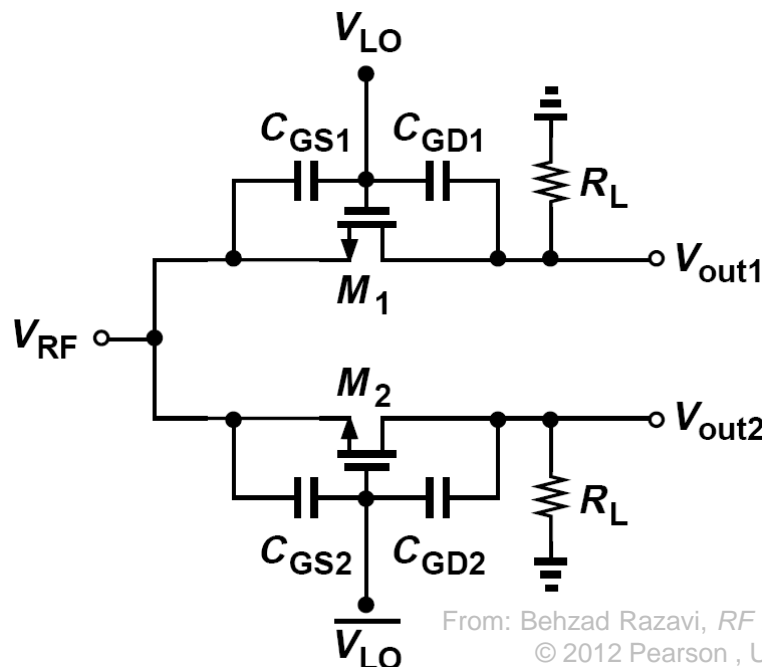➤ The configuration provides twice the conversion gain of the mixer using only one MOS transistor switch.




From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.

Double-Balanced Passive Mixer

(combining two single-balanced mixers)

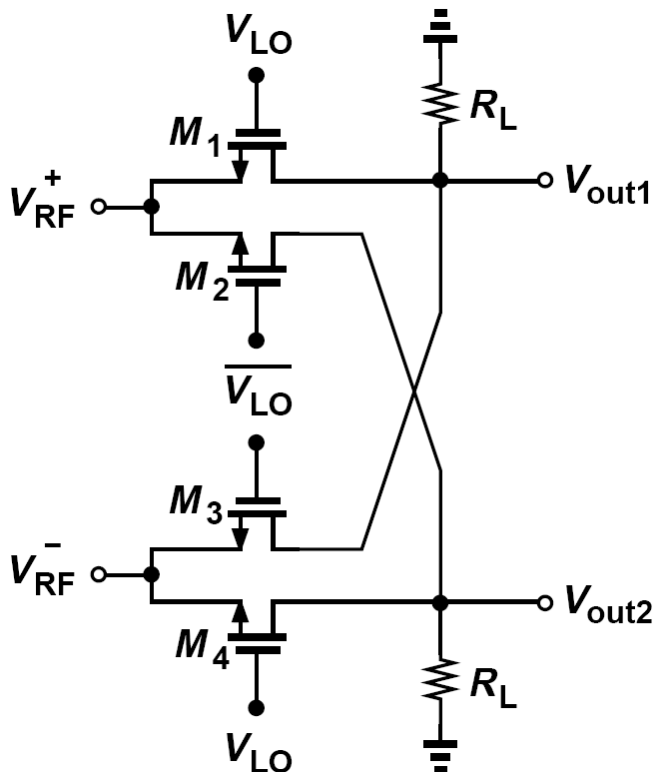- An improved configuration is to have the **balanced** RF input in addition to the **balanced** LO waveforms.




- This is called a **double-balanced mixer**, formed by connecting two **single-balanced mixers** such that their output LO feedthrough cancel but their output signals do not.

Double-Balanced Passive Mixer

(single-ended RF input)

- ❑ The double-balanced mixer can also be configured in a slightly different way.
 - Note that the RF input is single-ended which is not an uncommon output from the LNA.

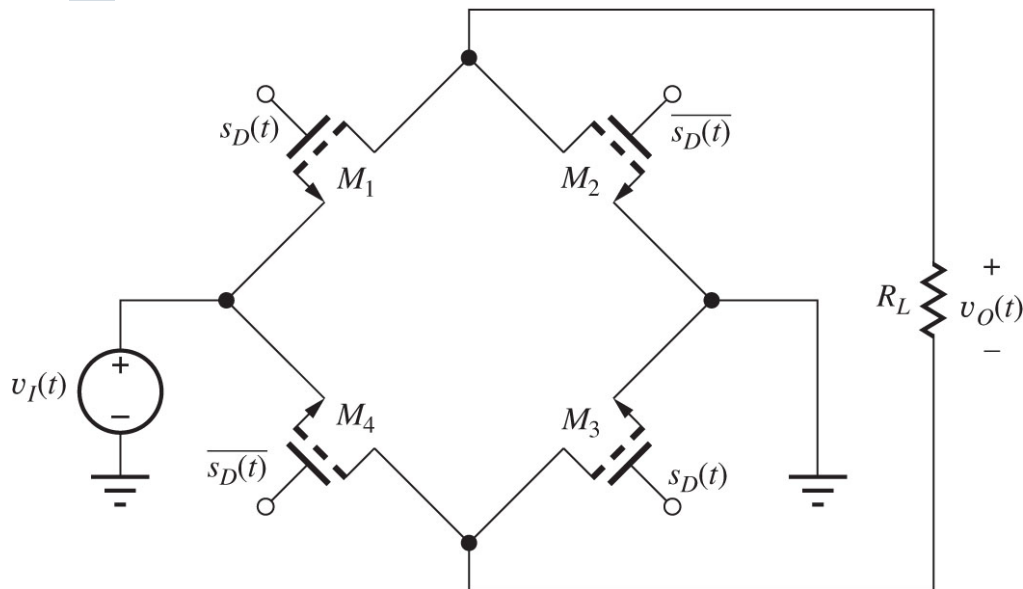Adapted from: R. C. Jaeger & T. N. Blalock, *Microelectronic Circuit Design*, 4e, © 2010 McGraw-Hill, USA.




- With one differential input grounded to accommodate a single-ended RF input, the input-referred noise is higher.

Active Mixer

(I-V & V-I conversion)

- While **passive mixers** using MOS transistors as switches provide no conversion gain (except with a large-amplitude LO signal), **active mixers** can be built by using transistors to

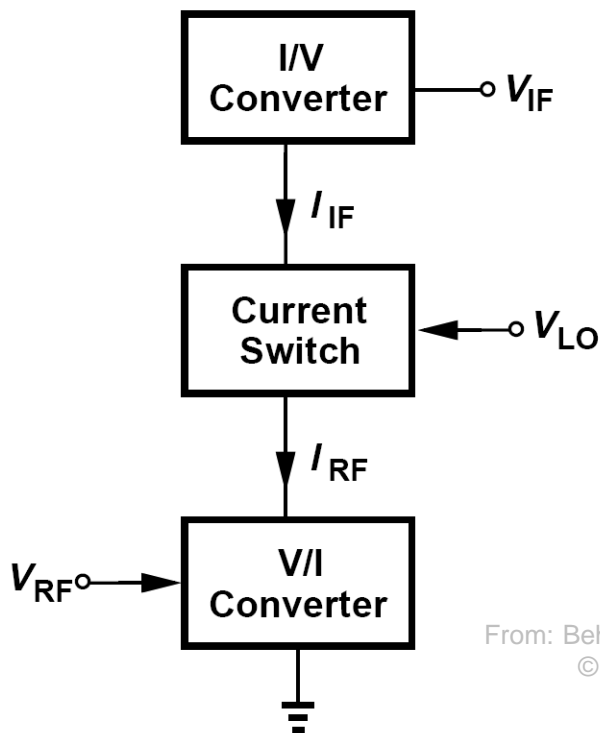- convert the RF signal into a current,
- commutate (steer) the RF current signal by the LO signal,
- convert the IF current signal to a voltage signal.




From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.

Active Mixer

(switching current signal)

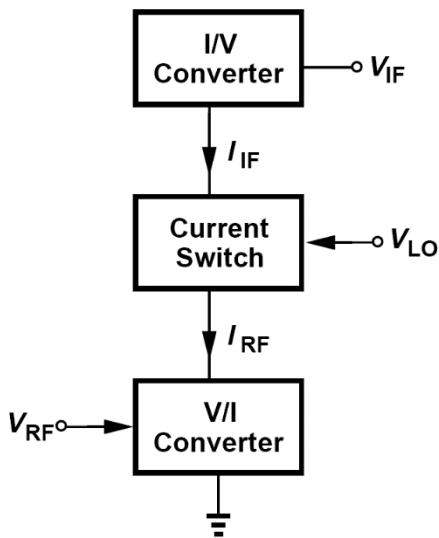- ❑ Such an **active** mixers incorporates **switching** for **frequency translation** after the voltage-to-current conversion but before the current-to-voltage conversion.



- In the input I - V conversion, the input transconductance I_{RF}/V_{RF} can be arbitrarily high.
- In the output V - I conversion, the output transresistance V_{IF}/I_{IF} can also be arbitrarily high.
- A high signal gain can be obtained from such an active mixer in the whole process while the switching provides no gain.




Xi'an Jiaotong-Liverpool University
西交利物浦大学

Single-Balanced Active Mixer

(use of 3 transistors & 2 resistors)

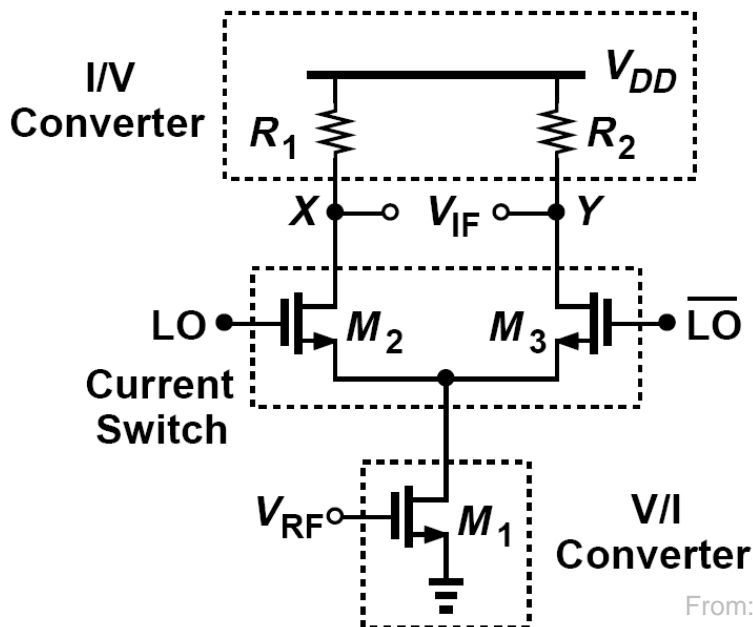- A typical *single-balanced* realisation of such an **active mixers** uses at least three transistors.
 - Transistor M_1 converts the input RF voltage to a current signal.




- The differential transistor pair M_2 and M_3 commutates (steers) the RF current signal to the left and to the right.
- The resistors R_1 and R_2 convert the output currents to a voltage signal.

Double-Balanced Active Mixer

(combining two single-balanced mixers)

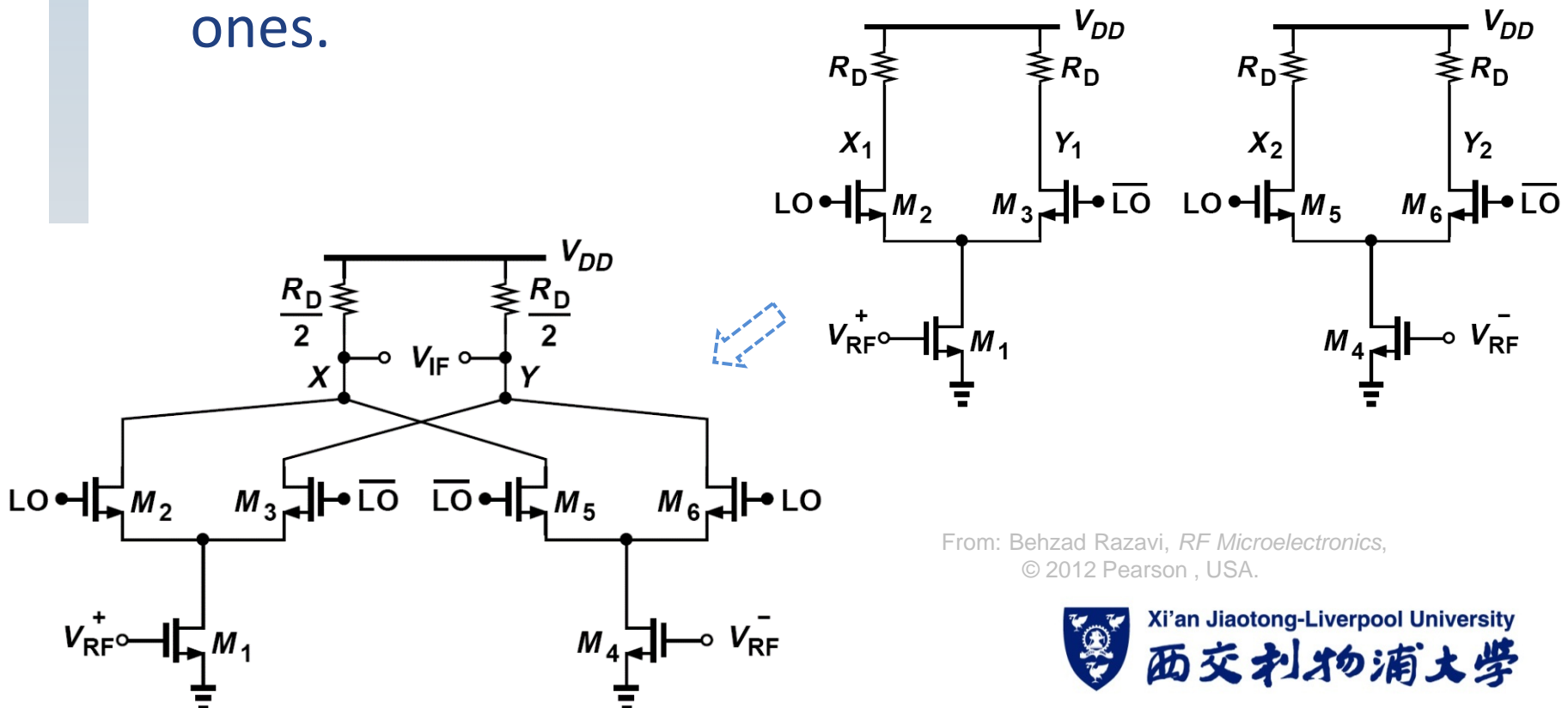- A **double-balanced** realisation of the active mixer can be obtained by combining two single-balanced ones.




From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.

Double-Balanced Active Mixer

(Gilbert cell)

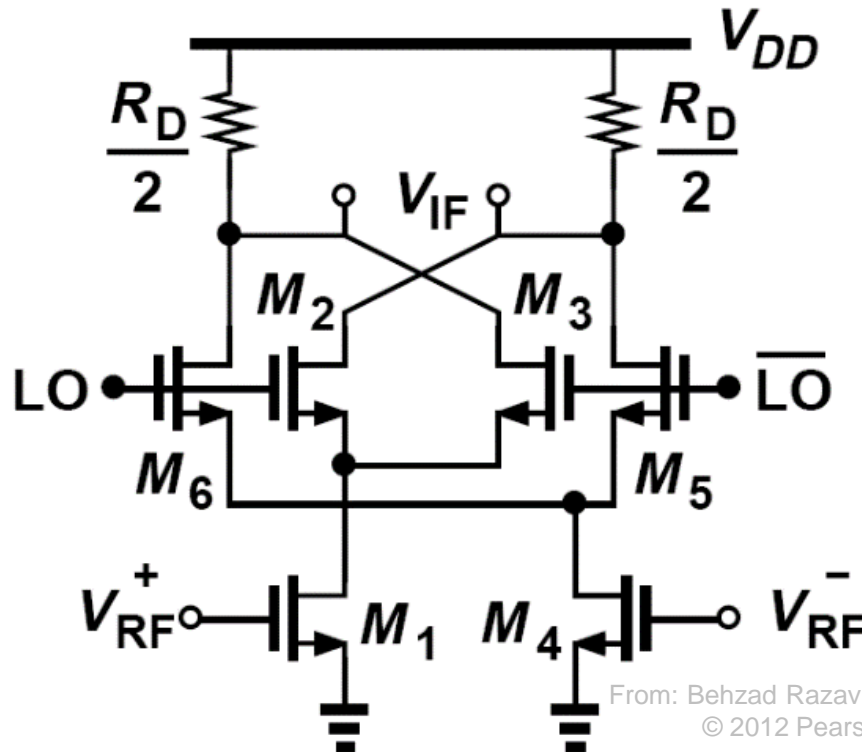- The transistor configuration in the double-balanced active mixer is commonly referred to the **Gilbert cell** or **Gilbert multiplier**.



- It was invented in 1960's by B. Gilbert (and also by H. Jones). Bipolar junction transistors (BJTs) were used in the initial circuit.

From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大学

Switching Action – key in mixers

(switching in voltage or current modes)

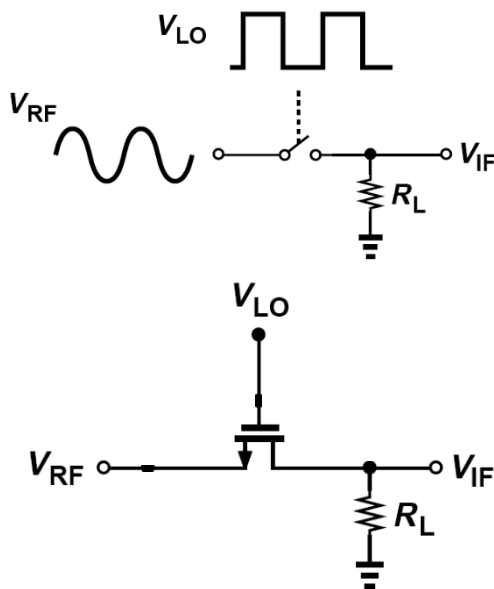- ❑ In the operation of mixers to achieve **frequency translation** by the **multiplication** of two electrical signals, the key is the **switching** action.



- It can be **switching** in the **voltage mode** or **current mode** (e.g. in the Gilbert cell).
- When used as a **switch** in the voltage mode, the MOSFET can be used to build passive mixers (e.g. a simple single-balanced mixer using only one MOSFET).
- A reasonably large enough **voltage swing** (a few 100 mV) is needed for driving the **switch**.

From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.

- Such passive mixers have signal loss.




Xi'an Jiaotong-Liverpool University

西交利物浦大学

Diode as a Switch

(2-terminal device)

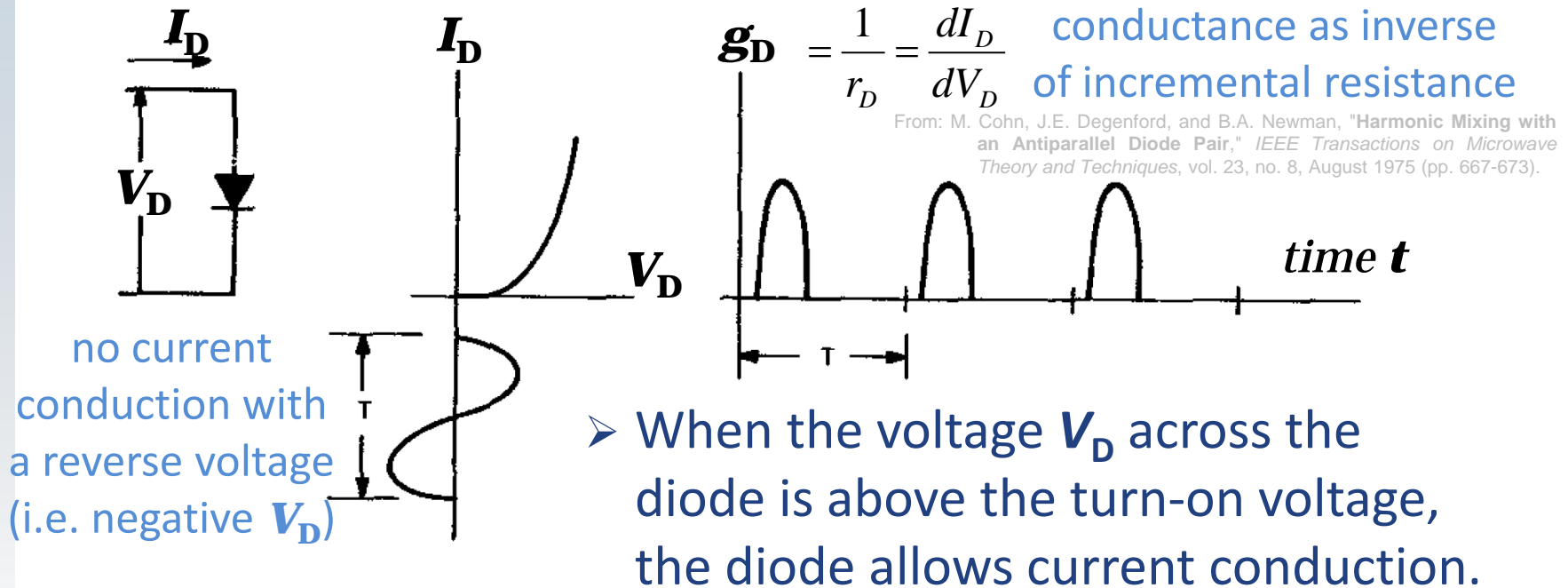- Apart from the MOSFET (or other three-terminal devices), the two-terminal **diode** can also serve as a switch and hence it can be used to build a **mixer**.




- Do you know the turn-on voltages of typical diodes?

Diode Mixer

(single-balanced)

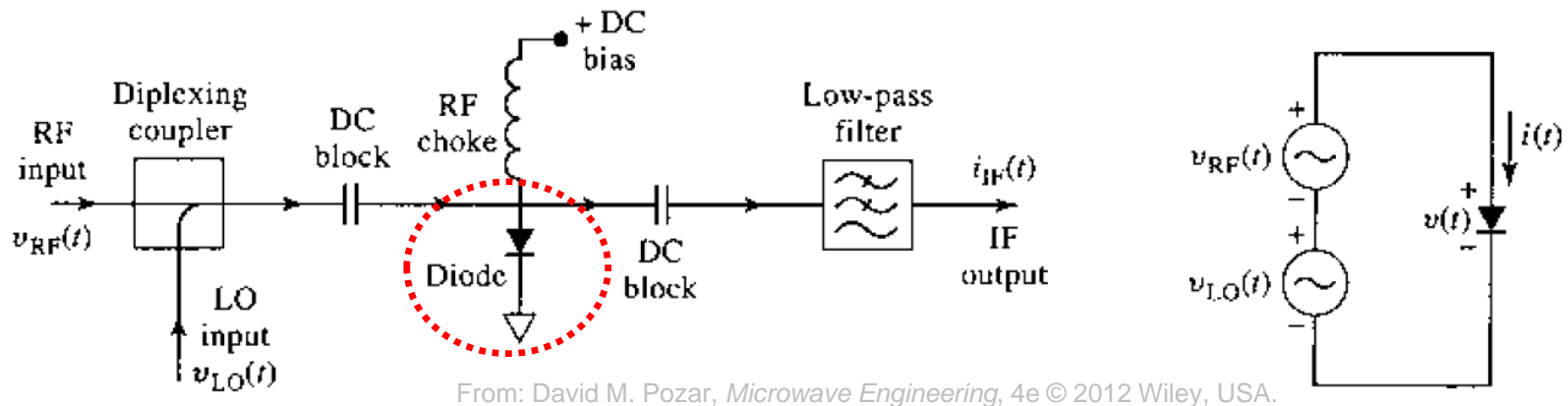- A simple implementation of a **diode mixer** requires only one **diode** serving as the **switch**.



- The LO signal $v_{LO}(t)$ is coupled with a small signal $v_{RF}(t)$ and then the signals added together will either turn on or off the diode \Rightarrow **switching action**.
- If the diode is turned on, the signals will go to ground.
- If it is turned off, the signals will pass to the IF port.




Xi'an Jiaotong-Liverpool University
西交利物浦大学

Diode Mixer


(diode in the signal path)

- ❑ A slightly different implementation has the diode connecting the RF port (and the LO port) to the IF port.
- A passive LC network can be used to separate the RF port and LO port.

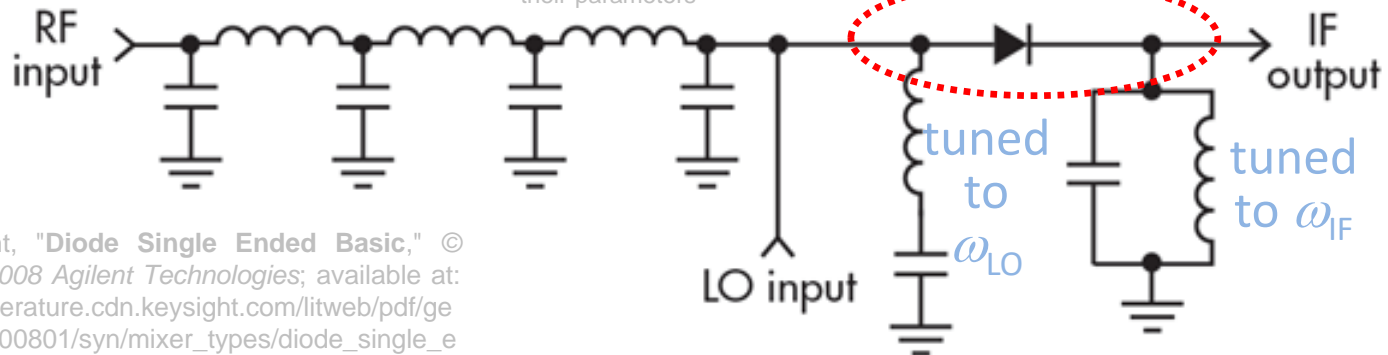From: Chris DeMartino, "Understanding Mixers and Their Parameters," *Microwaves & RF*, July 08, 2015; available at: <https://www.mwrf.com/components/understanding-mixers-and-their-parameters>



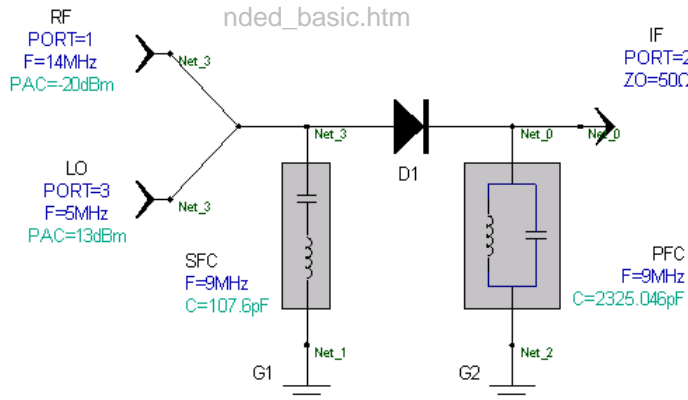From: Keysight, "Diode Single Ended Basic," © 1994-2008 Agilent Technologies; available at: http://literature.cdn.keysight.com/litweb/pdf/genesys200801/syn/mixer_types/diode_single_ended_basic.htm




- The LO signal presumably has a large enough **voltage swing** to turn on or off the **diode** in such an design.

Diode as a Switch

(single-balanced signal)

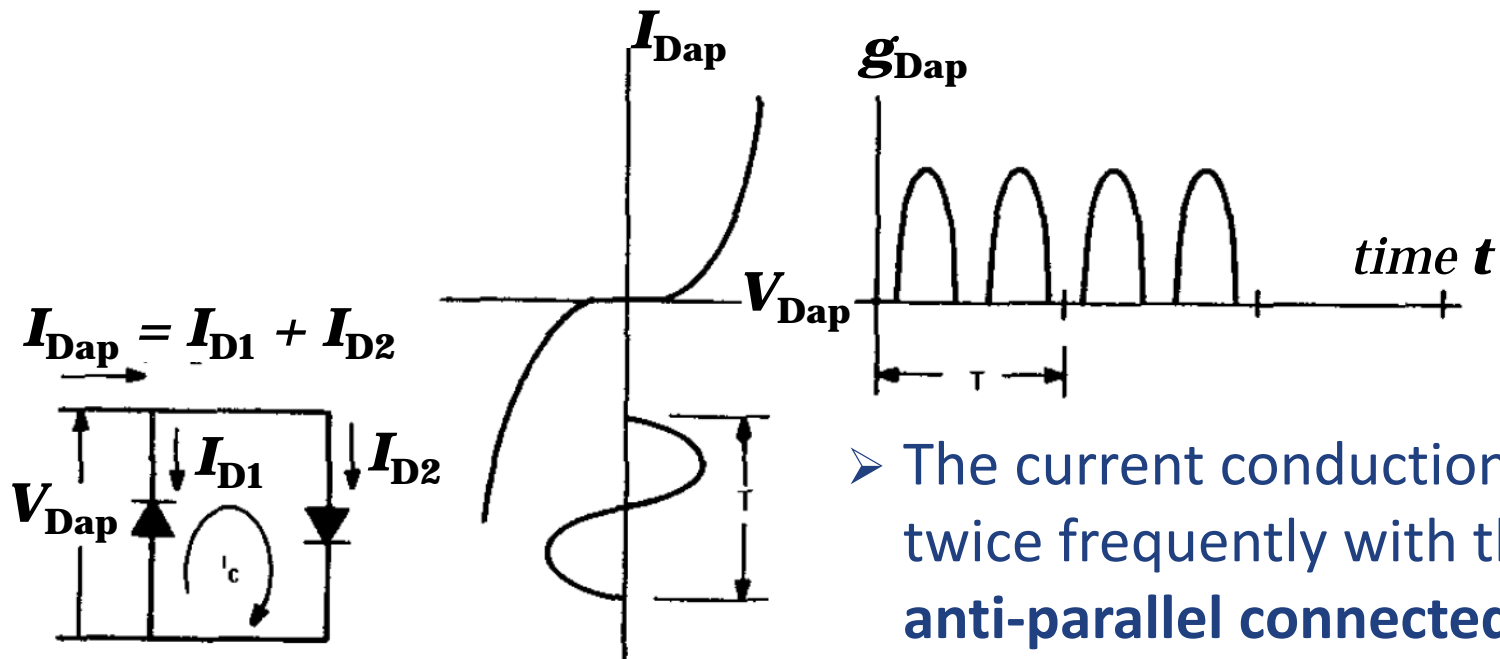- ❑ The **diode mixer** using only one diode can be improved to have a *single-balanced* LO signal for the **switching action**.
 - It is by the anti-parallel connection of two diodes.



- The current conduction is twice frequently with the **anti-parallel connected diodes**.

From: M. Cohn, J.E. Degenford, and B.A. Newman, "Harmonic Mixing with an Antiparallel Diode Pair," *IEEE Transactions on Microwave Theory and Techniques*, vol. 23, no. 8, August 1975 (pp. 667-673).




Xi'an Jiaotong-Liverpool University
西交利物浦大学

Double-Balanced Diode Mixer

(bridge configuration of 4 diodes)

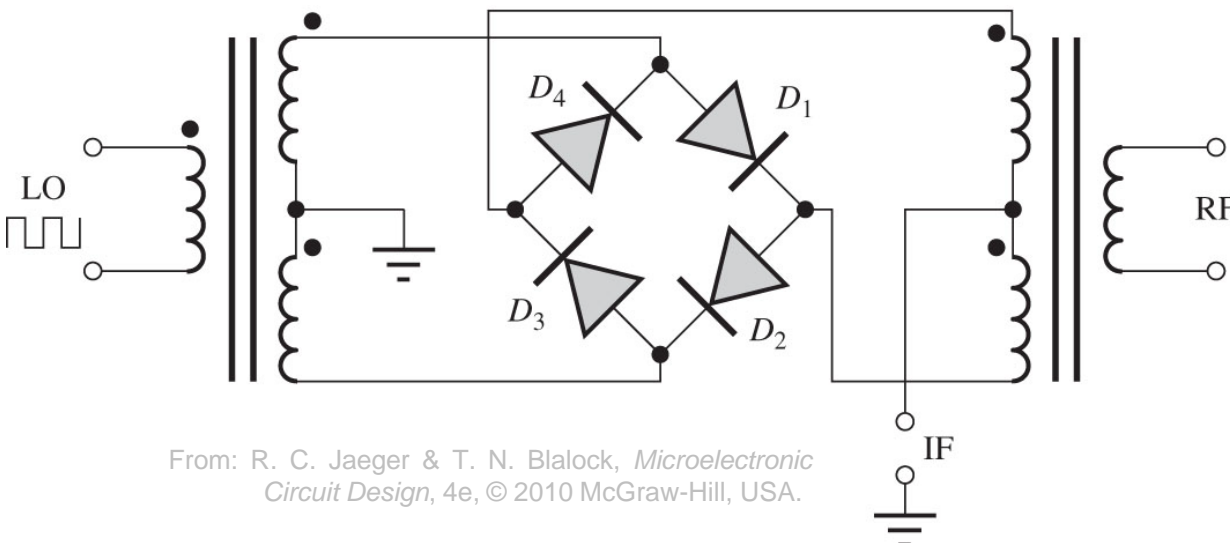- ❑ A double-balanced **diode mixer** can be obtained using a bridge configuration of four diodes. It is also called a ring design.
 - Transformers are needed to couple the balanced LO signal and also the balanced RF signal to the ring-connected diodes.




- The IF output can be tapped from either transformer for the LO or RF signals.

From: R. C. Jaeger & T. N. Blalock, *Microelectronic Circuit Design*, 4e, © 2010 McGraw-Hill, USA.

Double-Balanced Diode Mixer

(connection with single-ended signals)

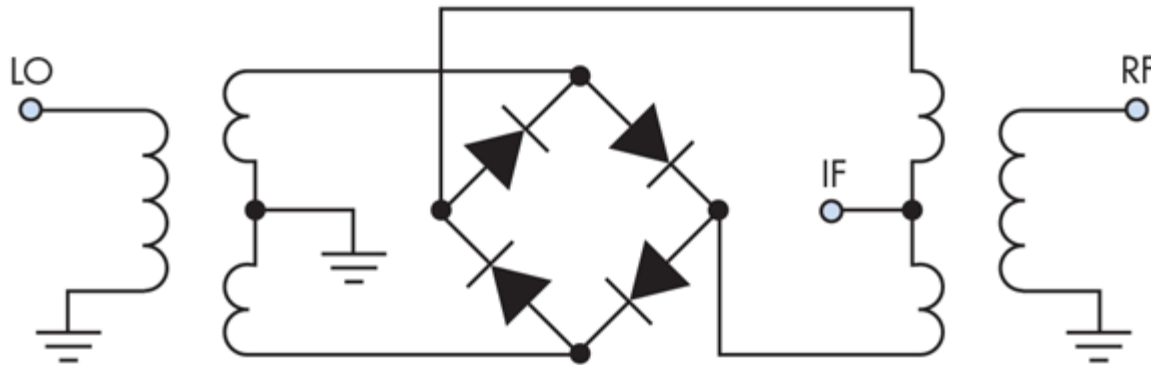- ❑ The double-balanced **diode mixer** can also be used in the single-balanced way (i.e. with the single-ended LO and RF signals).
- In each of the transformers for the LO and RF signals, one terminal can simply be grounded.




From: Chris DeMartino, "Understanding Mixers and Their Parameters," *Microwaves & RF*, July 08, 2015; available at: <https://www.mwrf.com/components/understanding-mixers-and-their-parameters>


Double-Balanced Diode Mixer

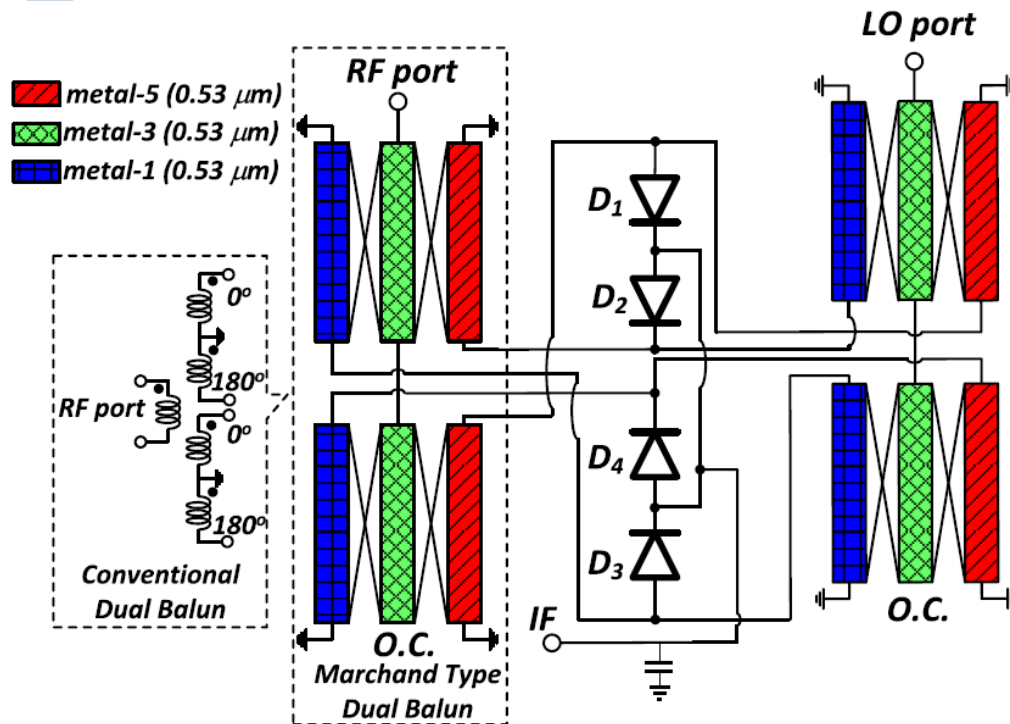(example in CMOS technology)

- The double-balanced **diode mixer** can be implemented in CMOS technology using Schottky diodes.



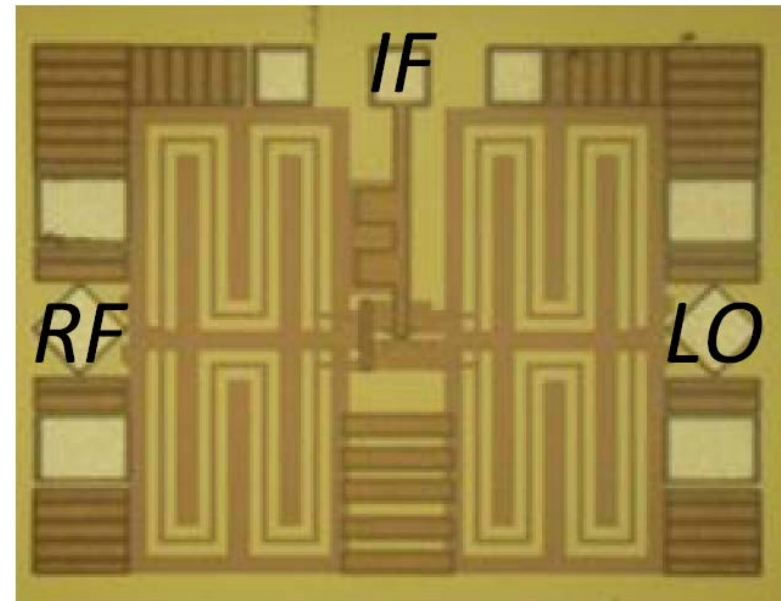30GHz diode mixer in
0.18 μm CMOS technology




From: Yu-Chih Hsiao *et al.*, "Broadband CMOS Schottky-Diode Star Mixer Using Coupled-CPW Marchand Dual-Baluns," *IEEE Microwave and Wireless Components Letters*, vol. 27, no. 5, May 2017 (pp. 500-502).

Double-Balanced Diode Mixer

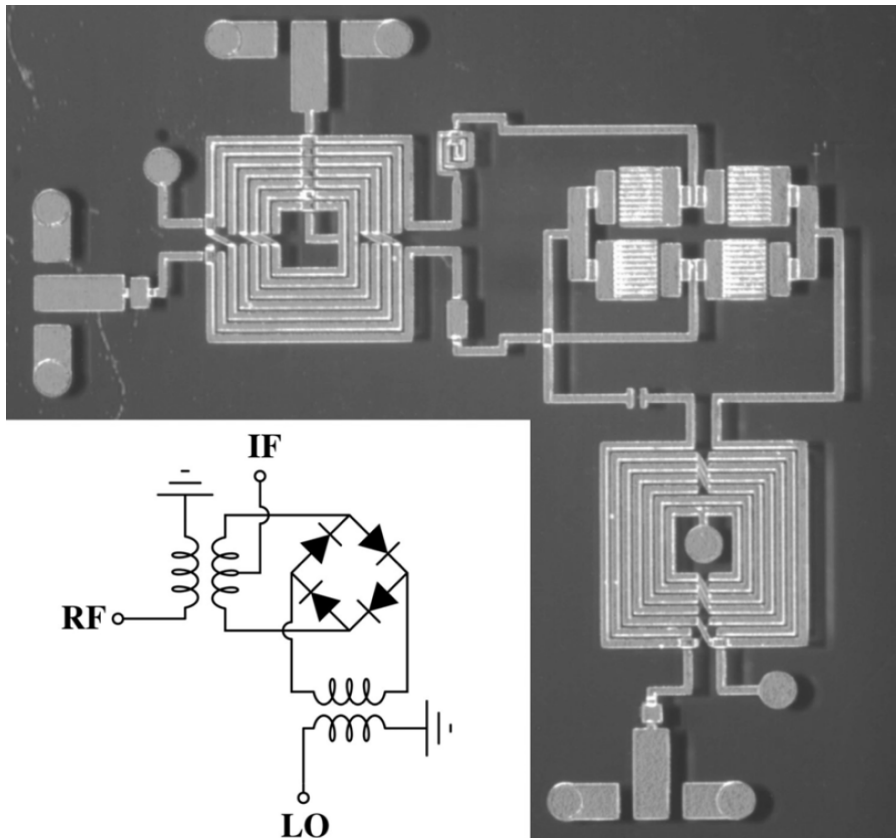(example using transformers)

- ❑ Transformers can be used in the diode mixers. Other types of Schottky diodes (e.g. silicon carbide) can be also used.



3.3GHz diode mixer using
SiC Schottky diodes

From: M. Sudow, K. Andersson *et al.*, "A highly linear double balanced Schottky diode S-band mixer," *IEEE Microwave and Wireless Components Letters*, vol. 16, no. 6, June 2017 (pp. 336-338).




Xi'an Jiaotong-Liverpool University
西交利物浦大学

Double-Balanced Diode Mixer

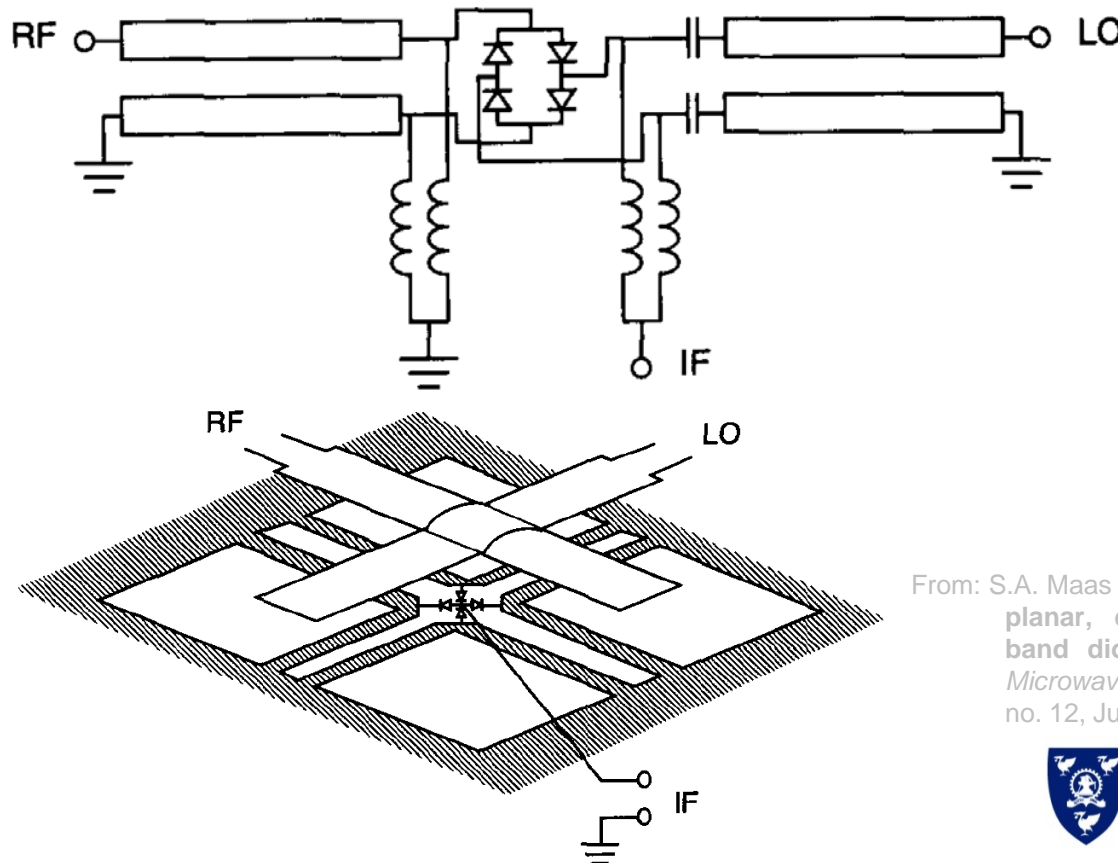(example using transformers)

- ❑ Transformers can be used in the diode mixers. Other types of Schottky diodes (e.g. silicon carbide) can be also used.



From: S.A. Maas and Kwo Wei Chang, "A broadband, planar, doubly balanced monolithic Ka-band diode mixer," *IEEE Transactions on Microwave Theory and Techniques*, vol. 41, no. 12, June 1993 (pp. 2330-2335).



Xi'an Jiaotong-Liverpool University
西交利物浦大學