

EEE304 – Digital Design with HDL (II)

Lecture 6

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

1

In This Session

- The Processor

2

Introduction

- We will examine two MIPS implementations
 - A simplified version
 - A more realistic pipelined version
- Simple subset, shows most aspects
 - Memory reference: lw, sw
 - Arithmetic/logical: add, sub, and, or, slt
 - Control transfer: beq, j

§ 4.1 Introduction


3

Instruction Execution

- PC → instruction memory, fetch instruction
- Register numbers → register file, read registers
- Depending on instruction class
 - Use ALU to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch target address
 - Access data memory for load/store
 - PC ← target address or PC + 4


4

CPU Overview

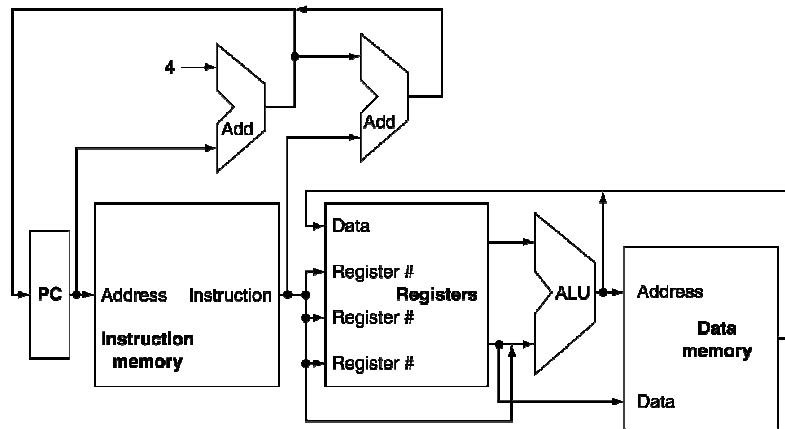

5


Multiplexers

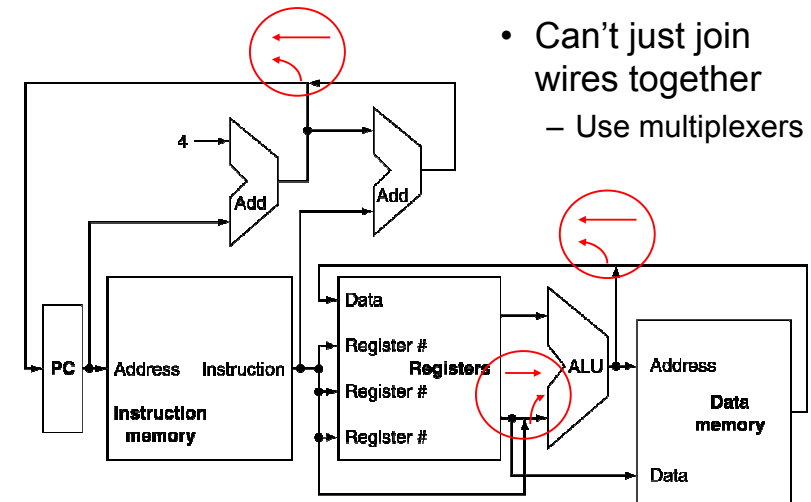

- Can't just join wires together
 - Use multiplexers

6

Control

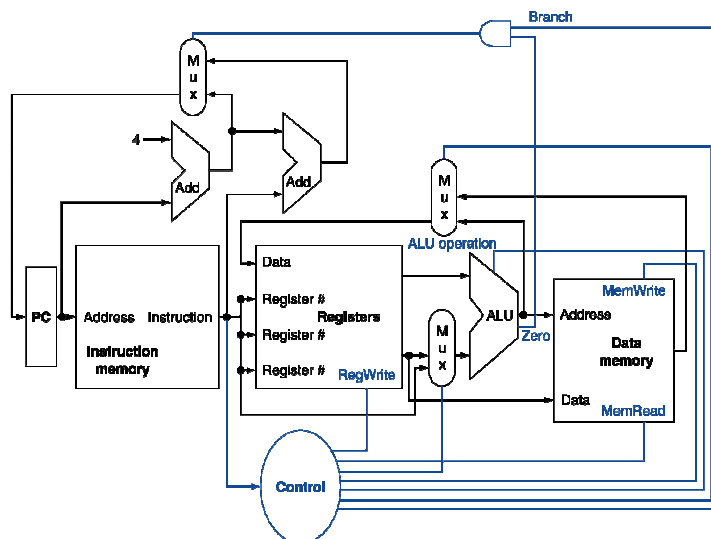

7

Logic Design Basics


- Information encoded in binary
 - Low voltage = 0, High voltage = 1
 - One wire per bit
 - Multi-bit data encoded on multi-wire buses
- Combinational element
 - Operate on data
 - Output is a function of input
- State (sequential) elements
 - Store information

8

Combinational Elements


- AND-gate

– $Y = A \& B$

 


- Adder

– $Y = A + B$

 


- Multiplexer

– $Y = S ? I1 : I0$

 

- Arithmetic/Logic Unit

– $Y = F(A, B)$

 


9

Sequential Elements

- Register: stores data in a circuit

– Uses a clock signal to determine when to update the stored value

 – Edge-triggered: update when Clk changes from 0 to 1




10

Sequential Elements

- Register with write control

– Only updates on clock edge when write control input is 1

 – Used when stored value is required later



11

Building a Datapath

- Datapath

– Elements that process data and addresses in the CPU


• Registers, ALUs, mux's, memories, ...

- We will build a MIPS datapath incrementally

– Refining the overview design

12


Instruction Fetch

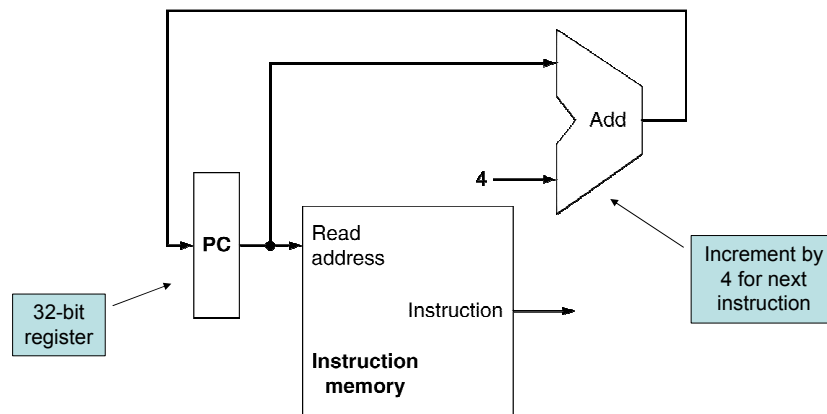

13

R-Format Instructions

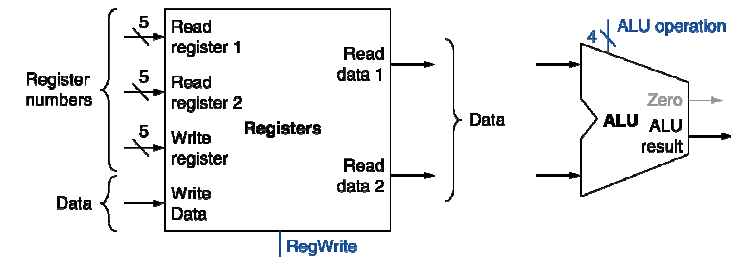- Read two register operands
- Perform arithmetic/logical operation
- Write register result




a. Registers

b. ALU

14

Load/Store Instructions

 - Read register operands
- Calculate address using 16-bit offset
 - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory




a. Data memory unit

b. Sign extension unit

15

R-Type/Load/Store Datapath

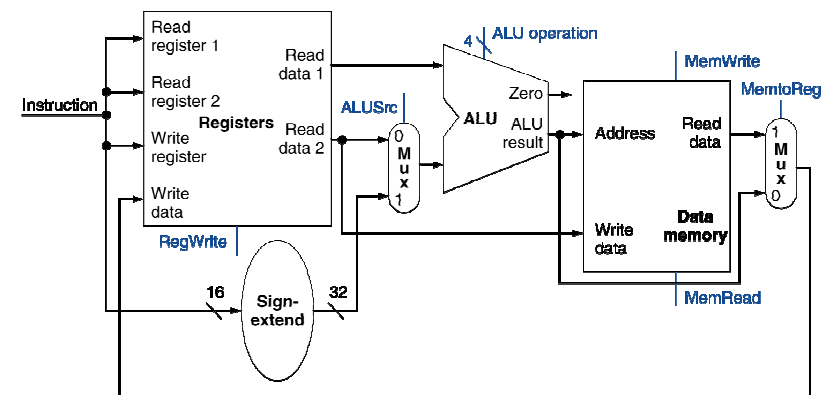


16

Branch Instructions

- Read register operands
- Compare operands
 - Use ALU, subtract and check Zero output
- Calculate target address
 - Sign-extend displacement
 - Shift left 2 places (word displacement)
 - Add to PC + 4
 - Already calculated by instruction fetch


17

Branch Instructions

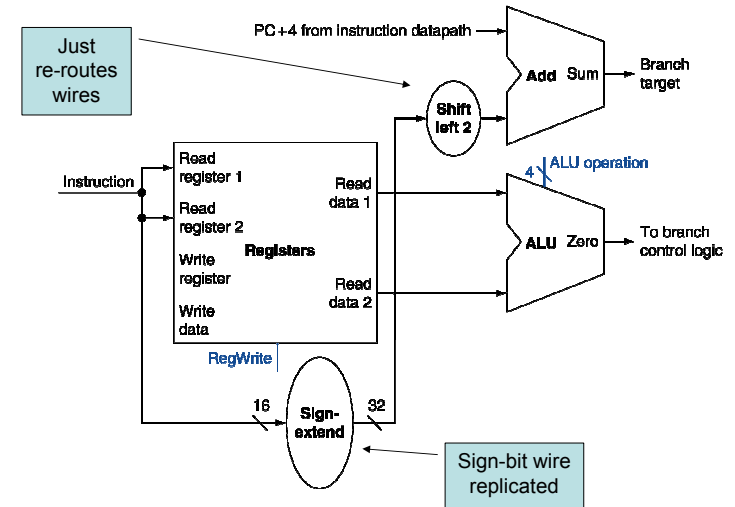

18

Full Datapath

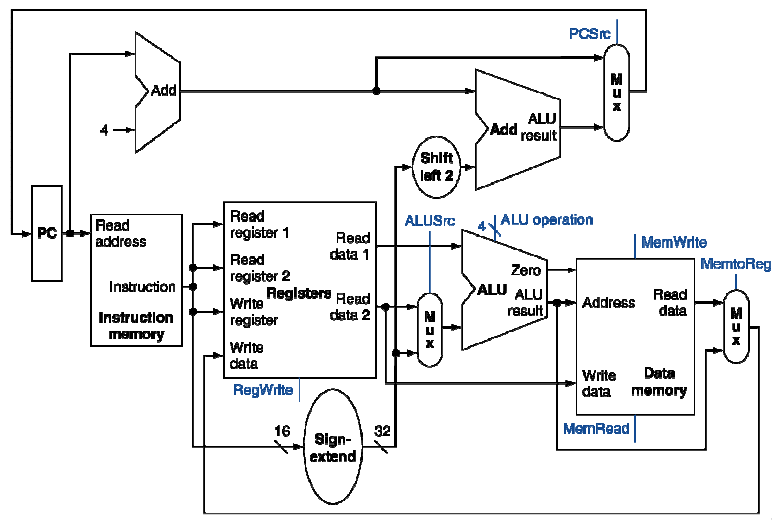

19

Composing the Elements

- First-cut data path does an instruction in one clock cycle
 - Each datapath element can only do one function at a time
 - Hence, we need separate instruction and data memories
- Use multiplexers where alternate data sources are used for different instructions

20