

# EEE205 – Digital Electronics (II)

## Lecture 3

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

1

## In This Session

- More Powerful PLDs
  - Complex Programmable Logic Devices (CPLD)
  - Field Programmable Gate Arrays (FPGA)


2

## Programmable Logic Devices (PLDs)

### Types

- SPLDs — up to 600 *equivalent gates* each.
- CPLDs — up to thousands of *equivalent gates* each.
- FPGAs — hundreds of thousands of *equivalent gates* each.

*equivalent gates*: 2-input NAND gates

 


3

## Complex Programmable Logic Devices (CPLD)

- A CPLD comprises multiple circuit blocks, each is similar to a PLA or a PAL and called a *PAL-like block*.
- These PAL-like blocks are connected to a set of *interconnection wires*.
- Each PAL-like block is also connected to a subcircuit called *I/O block*, which corresponds to the chip's input and output pins.

4

 
## Complex Programmable Logic Devices (CPLD)



5
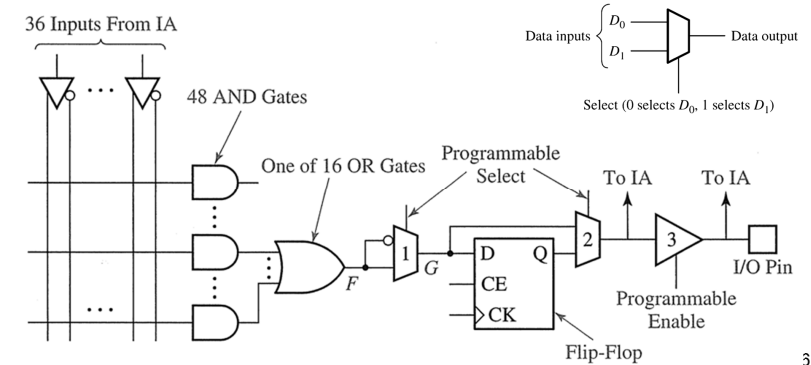
## Complex Programmable Logic Devices (CPLD)

- Each PAL-like block includes multiple (typically 16) macrocells.
- A signal in one block can be used as an input to another block.




3

## CPLDs

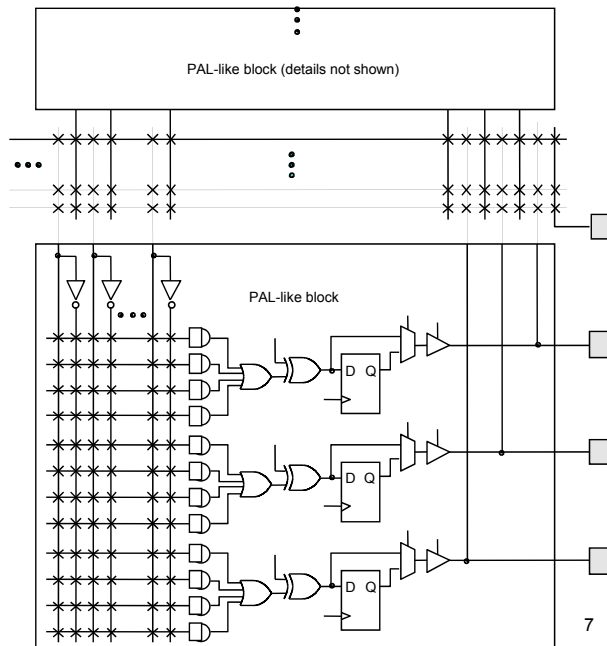
Example:

An I/O pin may be used as an input - the buffer must be disabled



7


## Field Programmable Gate Arrays (FPGA)

 

- An FPGA consists of an array of configurable logic blocks (CLBs).
- Interconnects are available between the CLBs.
- The CLBs are surrounded by I/O blocks.

8

## Field Programmable Gate Arrays (FPGA)

 

Configuration Logic Block (CLB):


- It often consists of an **LUT (lookup table)** that can generate any logic function — a truth-table based approach.
- Different from **AND-OR arrays** in SPLDs and CPLDs — an SOP Boolean-expression based approach.

9


## Field Programmable Gate Arrays (FPGA)

$x_1$	$x_2$	$f_1$
0	0	1
0	1	0
1	0	0
1	1	1

$$f_1 = \bar{x}_1 \bar{x}_2 + x_1 x_2$$

 

 
- An LUT contains storage cells, each stores an entry of the truth table.
- The outputs of such cells are multiplexed with the input variables as the data select.
- LUTs usually have 4-5 inputs in commercial FPGAs.



10


## Field Programmable Gate Arrays (FPGA)

 Example: an LUT to implement a multiplexer




Truth table

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 

11

## Field Programmable Gate Arrays (FPGA)

 


1. Normal LUT mode performs read operations.
2. Address decoder with write enable generates clock signals to latches for write operations.

12
 
## Field Programmable Gate Arrays (FPGA)

Flip-flops may be included in an FPGA logic block to facilitate registered outputs.



13

## Field Programmable Gate Arrays (FPGA)

### A Programmed FPGA


- Each switch (X) in blue is turned on and each switch in black is turned off.
- The top row implements the function  $f_1 = x_1x_2$  and  $f_2 = \overline{x_2}x_3$ .
- The bottom row produces  $f = f_1 + f_2 = x_1x_2 + \overline{x_2}x_3$ .

$x_1$	$x_2$	$f_1$	$x_2$	$x_3$	$f_2$	$f_1$	$f_2$	$f$
0	0	0	0	0	0	0	0	0
0	1	0	0	1	1	0	1	1
1	0	0	1	0	0	1	0	1
1	1	1	1	1	0	1	1	1

$f_1 = x_1x_2$ 
 $f_2 = \overline{x_2}x_3$ 
 $f = f_1 + f_2$

14

## Field Programmable Gate Arrays (FPGA)

 

15

## Field Programmable Gate Arrays (FPGA)

Recent trend is to incorporate specialized cores:

- RAMs – single-port, dual-port, FIFOs
  - 128 bits to over 36K bits per RAM
  - 4 to over 575 per FPGA
- DSPs – 18x18-bit multiplier, 48-bit accumulator, etc.
  - up to 512 per FPGA
- Microprocessors and/or microcontrollers
  - up to 2 per FPGA

16