

EEE225 Advanced Electrical Circuits and Electromagnetics

Lecture 9 Two-port Networks

Dr. Zhao Wang

zhao.wang@xjtlu.edu.cn

Room EE322


Content

- (Pre-lecture reading) Review of matrix operation
- 1-port and 2-port networks
- Four sets of parameters
 - Z-parameter
 - Y-parameter
 - T-parameter
 - ~~H-parameter~~
- Relationship between them
 - z and y parameters
- Interconnections
 - Series, parallel and cascade



One-port Network

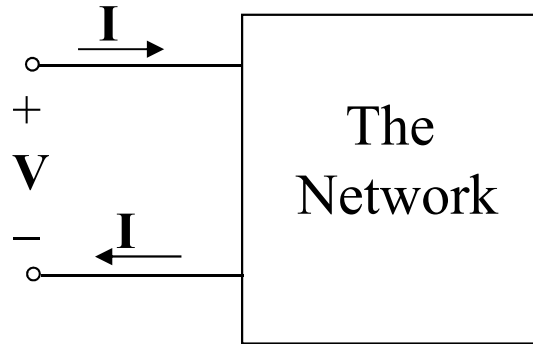- A port : A pair of terminals through which a signal (voltage or current) may enter or leave.
- Port condition: The same current must enter and leave a port.




- One port network: a network has only one pair of terminals: two terminals
- For one-port network:
 - Current entering the port = current leaving the port
 - May be modeled by Thevenin or Norton equivalents




One-port Network – Example

- Input impedance of this one-port network is:

$$Z_{in} = \frac{V_1}{I_1}$$

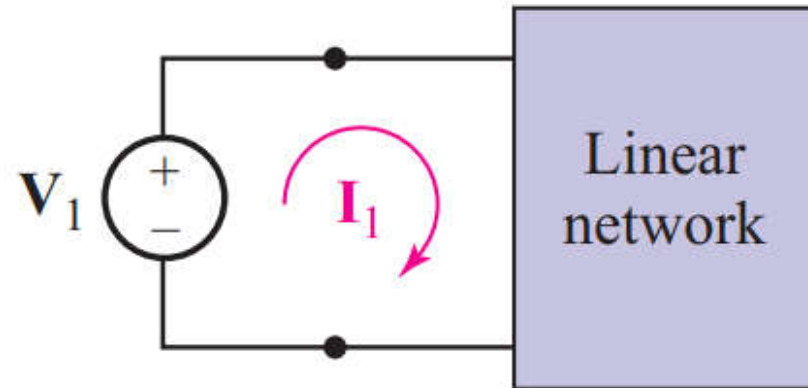

- Example:
 - Get Z_{in}

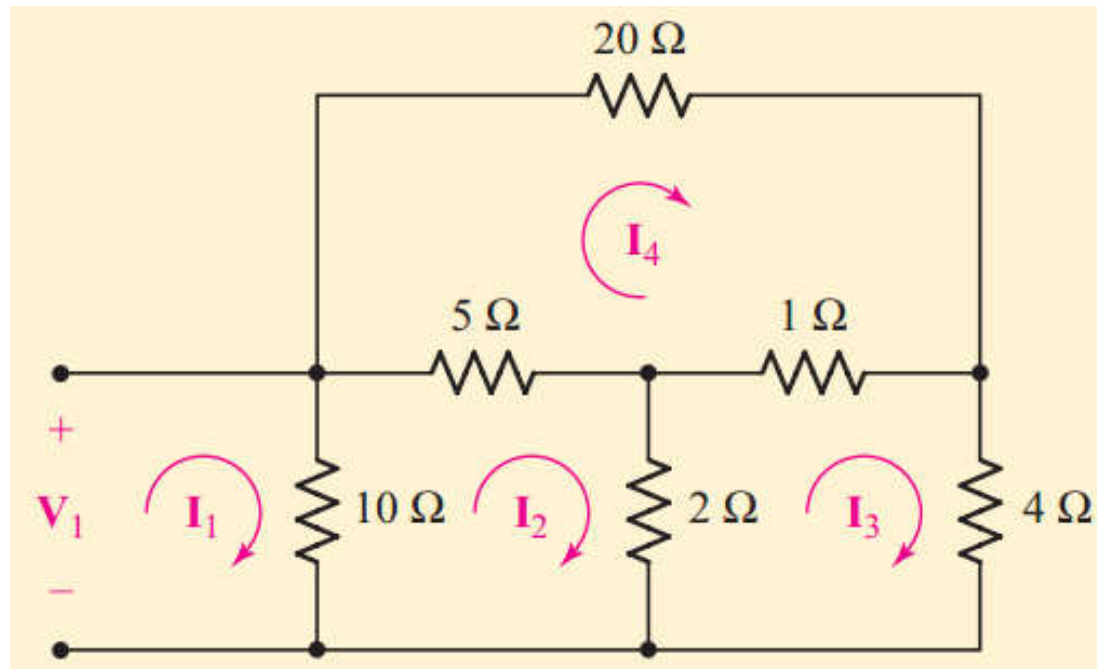

Two-port Network

- A two-port network is an electrical network with two separate ports for input and output.

The standard configuration of a two port:



- Any linear circuit with four terminals can be transformed into a two-port network provided that it does not contain an independent source and satisfies the port conditions.
- The voltages and currents at one port may be expressed as linear combinations of the voltages and currents at the other port, i.e. V_1 , V_2 , I_1 , and I_2 , are related by using two-port network *parameters*.


Two-port Network – Why?

- 1. The network are useful, typically in communications, control systems, power system and electronics
- 2. Know how to model two-port network will help in the analysis of larger network (two-port network can be treated as ‘black box’.)

Two-port Network – Four Sets of Network Parameters

In EEE207 we will study on four sets of network parameters


**Impedance
Z parameters**

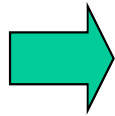

Commonly used in the synthesis of filters, and are useful in the design and analysis of impedance-matching networks and power distribution networks

**Admittance
Y parameters**

**Transmission
A, B, C, D
parameters**

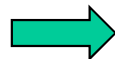

The A,B,C,D parameters are best used when we want to cascade two networks together


**Hybrid
H parameters**



H parameters are used almost solely in electronics -- in the equivalent circuit of a transistor.




Z Parameters – Definition

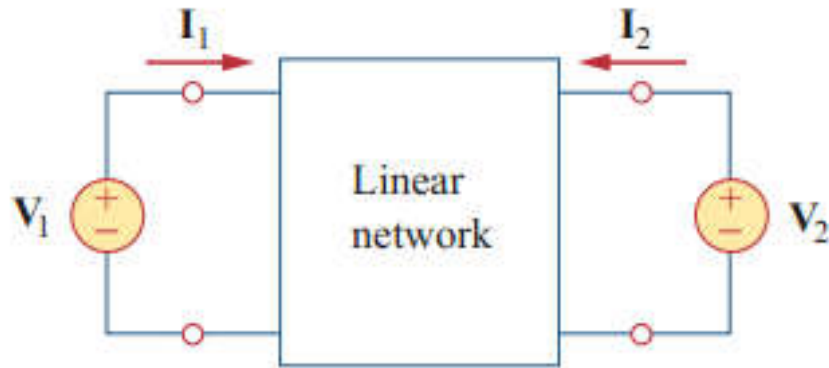

(a)

Voltage source driven 2-port network

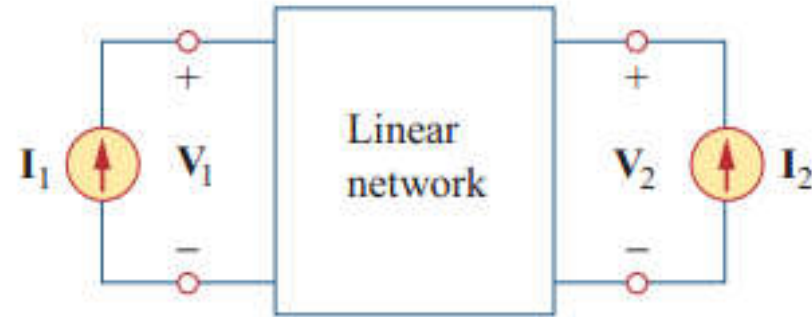

(b)

Current source driven 2-port network


The terminal voltages can be related to the terminal currents as

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$


Notice: Only two of the four variables (V_1 , V_2 , I_1 , and I_2) are independent. The other two can be found using above eq.s

Z Parameters – Expression

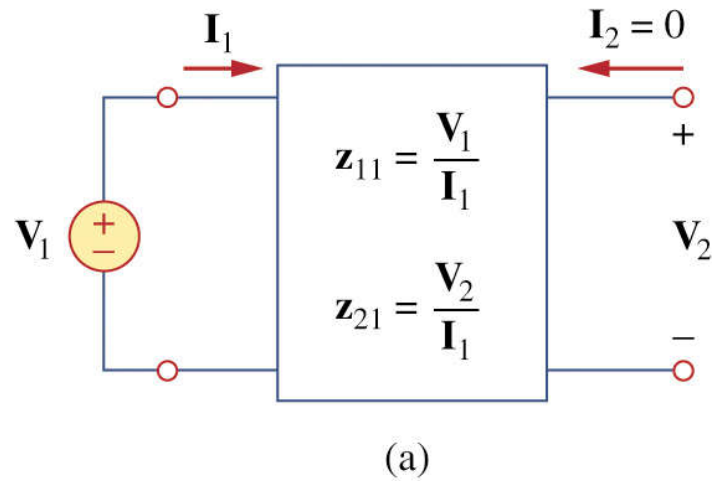

$$z_{11} = \frac{V_1}{I_1}, \quad z_{21} = \frac{V_2}{I_1}$$
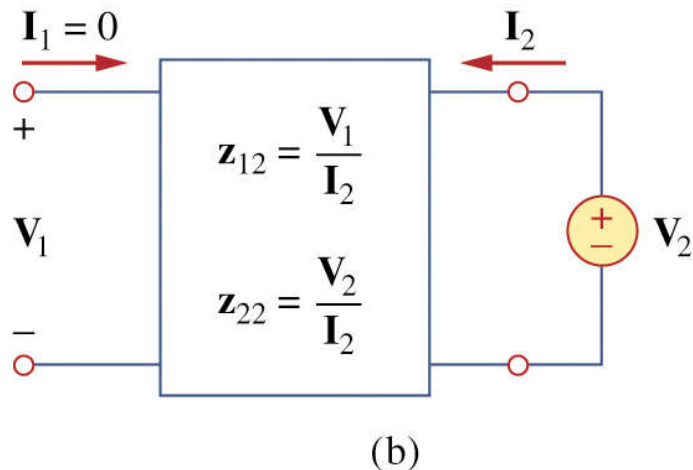
$$z_{12} = \frac{V_1}{I_2}, \quad z_{22} = \frac{V_2}{I_2}$$



$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [\mathbf{z}] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

z_{11} and z_{22} : called driving-point impedances

z_{12} and z_{21} : called transfer impedances



Z Parameters – Expression



$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

z_{11} is the impedance seen looking into port 1 when port 2 is open.

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

z_{12} is a transfer impedance. It is the ratio of the voltage at port 1 to the current at port 2 when port 1 is open.

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

z_{21} is a transfer impedance. It is the ratio of the voltage at port 2 to the current at port 1 when port 2 is open.


$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

z_{22} is the impedance seen looking into port 2 when port 1 is open.



Z Parameters – Reciprocal

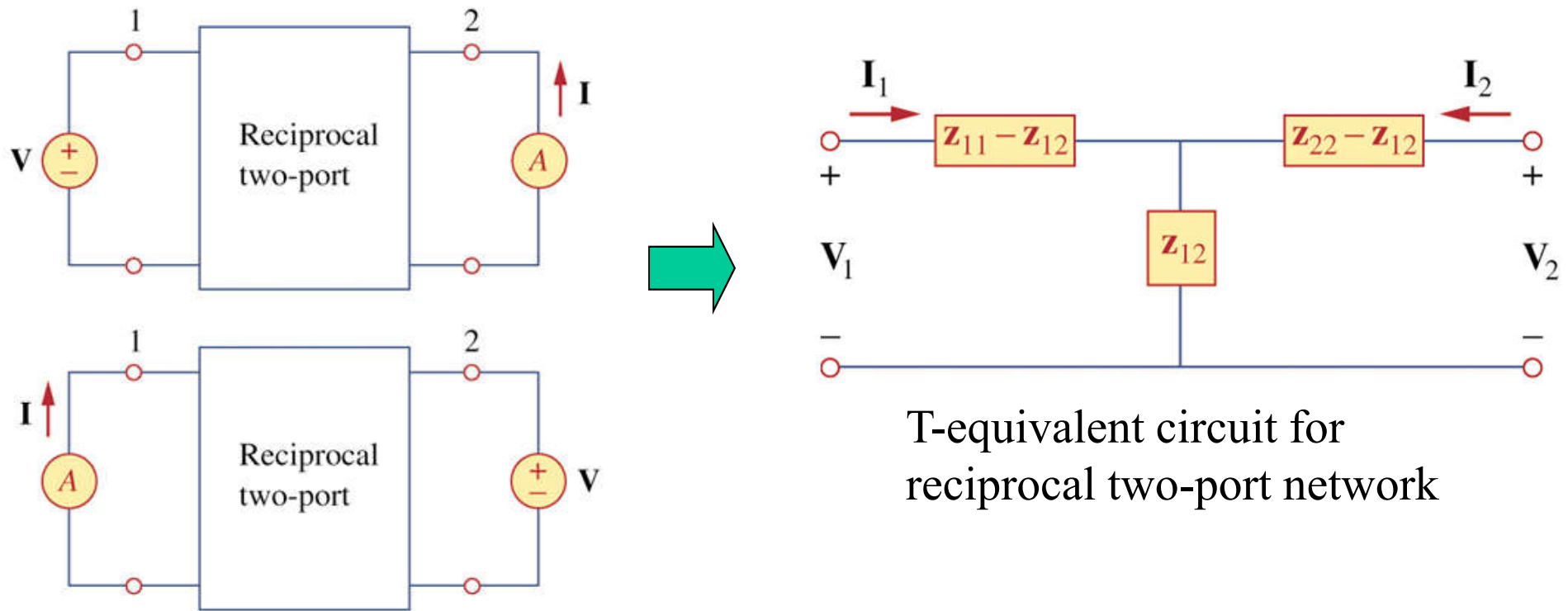When the two-port network is linear and has no dependent sources: $z_{12} = z_{21}$, and the two-port is said to be reciprocal – **Reciprocal Two-port Network**



Any two-port made entirely of resistors, capacitors and inductors must be reciprocal.

Z Parameters – Symmetrical

$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2$$

When $\mathbf{z}_{11} = \mathbf{z}_{22}$, the two-port network is said to be symmetrical – mirror-like.

If the two-port network is reciprocal and symmetrical, only 2 parameters need to be determined.

Z Parameters – Example 1

Given the following circuit. Determine the **Z** parameters.

Solution

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$z_{11} = 8 + 20 \parallel 30 = 20 \, \Omega$$


$$z_{22} = 20 \parallel 30 = 12 \, \Omega$$

$$V_1 = \frac{20 \times I_2 \times 20}{20 + 30} = 8 \times I_2$$

$$z_{12} = \frac{8 \times I_2}{I_2} = 8 \, \Omega$$

Reciprocal Two-Port Network

$$z_{21} = z_{12} = 8 \, \Omega$$

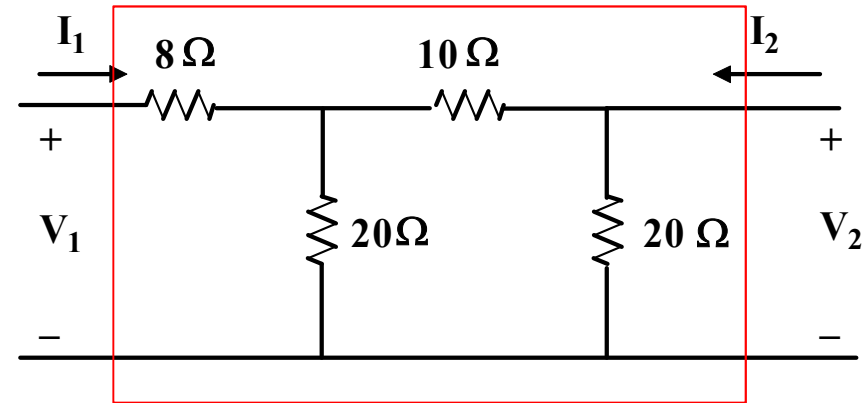

The **Z** parameter equations can be expressed in matrix form as follows:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 & 8 \\ 8 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



Z Parameters – Example 2

Find the **Z** parameters the following circuit.

Solution

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$


$$V_x = \left(I_1 - \frac{V_x}{1} \right) \times (4 + 2) - 2V_x$$

$$3V_x = 6I_1 - 6V_x \Rightarrow I_1 = \frac{3V_x}{2}$$

$$V_x = V_1 - I_1 \times 1$$

Substituting gives
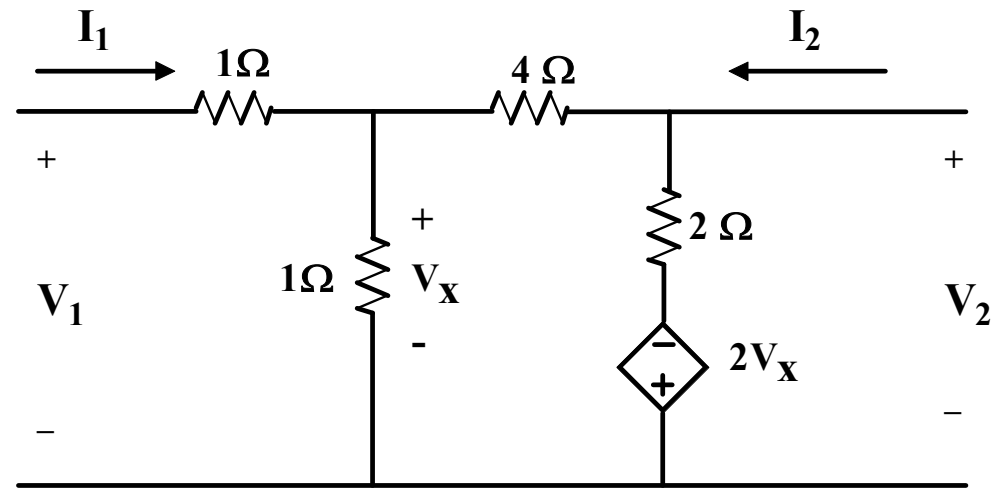
$$I_1 = \frac{3(V_1 - I_1)}{2} \quad \text{or} \quad \frac{V_1}{I_1} = z_{11} = 1.667 \, \Omega$$



$$z_{21} = -0.667 \, \Omega$$

$$z_{12} = 0.222 \, \Omega$$

$$z_{22} = 1.111 \, \Omega$$



Admittance Parameters – Definition

$$y_{11} = \frac{I_1}{V_1} \bigg|_{V_2=0}$$

y_{11} is the admittance seen looking into port 1 when port 2 is shorted.

$$y_{12} = \frac{I_1}{V_2} \bigg|_{V_1=0}$$

y_{12} is a transfer admittance. It is the ratio of the current at port 1 to the voltage at port 2 when port 1 is shorted.


$$y_{21} = \frac{I_2}{V_1} \bigg|_{V_2=0}$$

y_{21} is a transfer admittance. It is the ratio of the current at port 2 to the voltage at port 1 when port 2 is shorted.

$$y_{22} = \frac{I_2}{V_2} \bigg|_{V_1=0}$$

y_{22} is the admittance seen looking into port 2 when port 1 is shorted.


Admittance Parameters – Expression

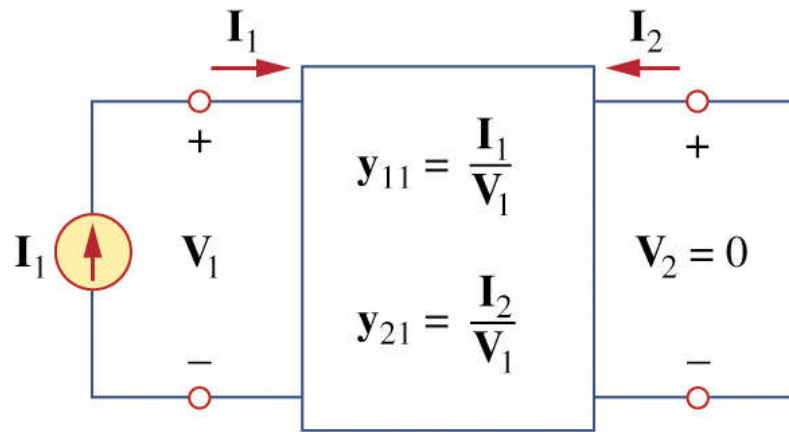

(a)

$$y_{11} = \frac{I_1}{V_1}, \quad y_{12} = \frac{I_1}{V_2}$$
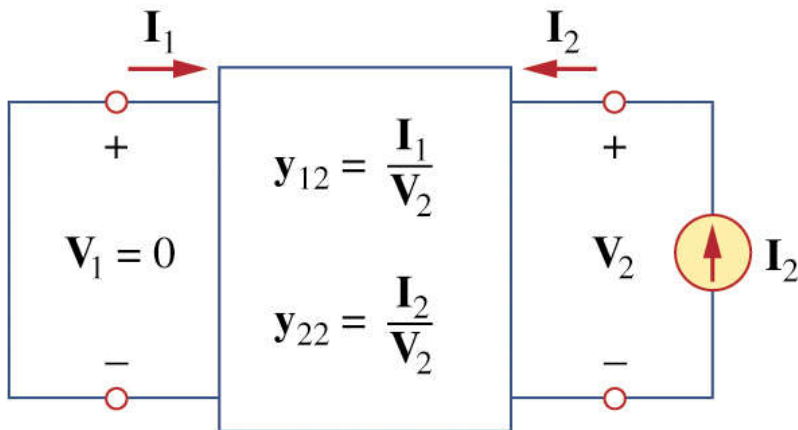
$$y_{21} = \frac{I_2}{V_1}, \quad y_{22} = \frac{I_2}{V_2}$$



(b)

$$I_1 = y_{11} V_1 + y_{12} V_2$$


$$I_2 = y_{21} V_1 + y_{22} V_2$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Admittance Parameters – Reciprocal & Symmetrical

When the two-port network is linear and has no dependent sources: $\mathbf{y}_{12} = \mathbf{y}_{21}$, Reciprocal Two-Port Network

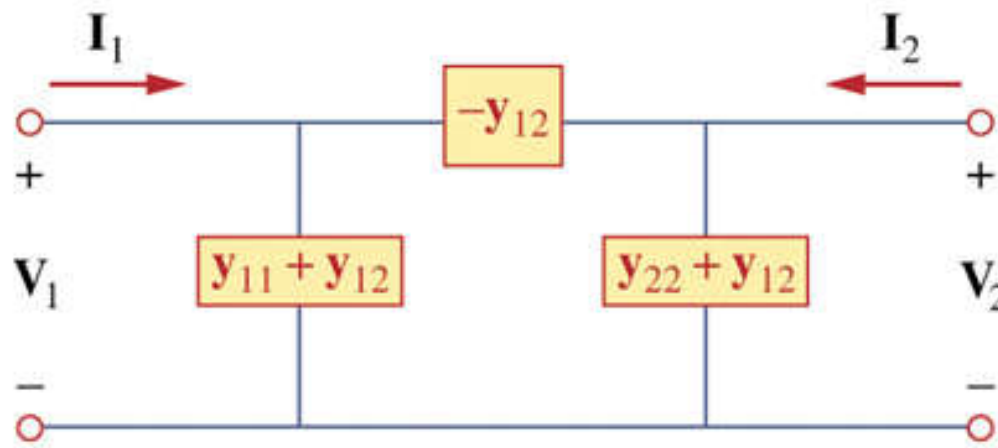
Π -equivalent circuit for reciprocal two-port network



When $\mathbf{y}_{11} = \mathbf{y}_{22}$, the two-port network is said to be symmetrical – mirror-like

Admittance Parameters – Example

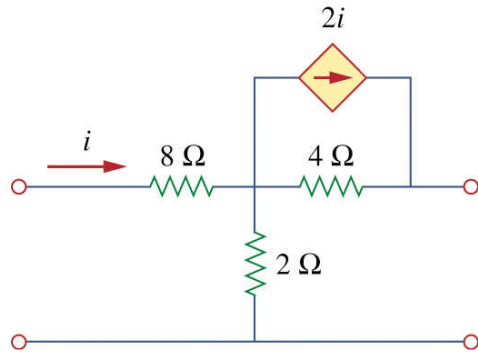Determine the y parameters in the circuit.




Solution

Find y_{11} and y_{21}

$$y_{11} = \frac{I_1}{V_1} \quad \left| \quad V_2 = 0 \right.$$

$$y_{21} = \frac{I_2}{V_1} \quad \left| \quad V_2 = 0 \right.$$

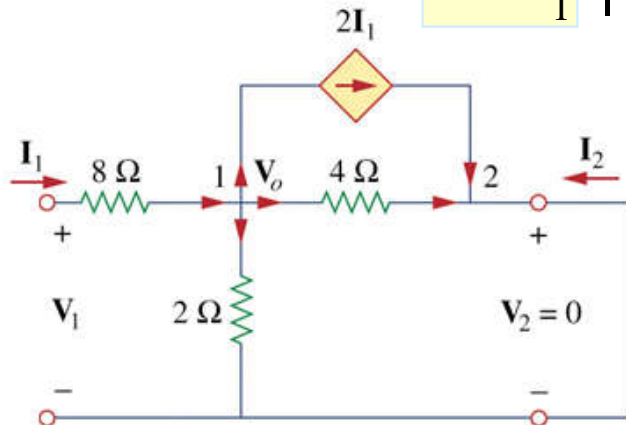

$$\text{At node 1, } \frac{V_1 - V_o}{8} = 2I_1 + \frac{V_o}{2} + \frac{V_o}{4}$$

$$\text{But } I_1 = \frac{V_1 - V_o}{8}, \text{ therefore, } 0 = \frac{V_1 - V_o}{8} + \frac{3V_o}{4}$$

$$0 = V_1 - V_o + 6V_o \Rightarrow V_1 = -5V_o$$

$$\text{Hence, } I_1 = \frac{-5V_o - V_o}{8} = -0.75V_o$$

$$\text{and } y_{11} = \frac{I_1}{V_1} = \frac{-0.75V_o}{-5V_o} = 0.15 \text{ S}$$

$$V_1 = -5V_o, \quad I_1 = 0.75V_o$$

$$\text{At node 2, } \frac{V_o - 0}{4} + 2I_1 + I_2 = 0$$

$$\text{or } -I_2 = 0.25V_o - 1.5V_o = -1.25V_o$$

$$\text{Hence, } y_{21} = \frac{I_2}{V_1} = \frac{1.25V_o}{-5V_o} = -0.25 \text{ S}$$



Admittance Parameters – Example cont.

Find y_{22} and y_{12}

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} \quad y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

Similarly, at node 1: $\frac{0 - V_o}{8} = 2I_1 + \frac{V_o}{2} + \frac{V_o - V_2}{4}$

And $I_1 = \frac{0 - V_o}{8}, \Rightarrow 0 = -\frac{V_o}{8} + \frac{V_o}{2} + \frac{V_o - V_2}{4}$


$\Rightarrow 0 = -V_o + 4V_o + 2V_o - 2V_2 \Rightarrow V_2 = 2.5V_o$

Hence: $y_{12} = \frac{I_1}{V_2} = \frac{-V_o/8}{2.5V_o} = -0.05 \text{ S}$

At node 2: $\frac{V_o - V_2}{4} + 2I_1 + I_2 = 0$

$\Rightarrow -I_2 = 0.25V_o - \frac{1}{4}(2.5)V_o - \frac{2V_o}{8} = -0.625V_o$

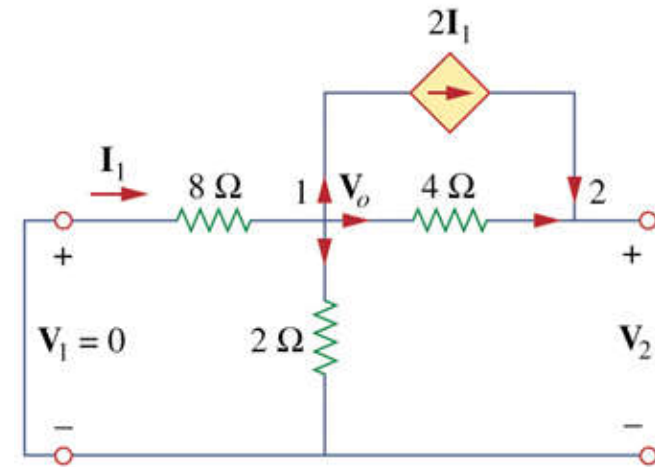Thus: $y_{22} = \frac{I_2}{V_2} = \frac{0.625V_o}{2.5V_o} = 0.25 \text{ S}$



The \mathbf{Y} parameter equations can be expressed in matrix form as follows:

$$\mathbf{Y} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

$$\mathbf{Y} = \begin{bmatrix} 0.15 & -0.05 \\ -0.25 & 0.25 \end{bmatrix}$$

Transmission Parameters (A, B, C, D)

The defining equations are:

$$\mathbf{A} = \left. \frac{\mathbf{V}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_2 = 0}$$

$$\mathbf{V}_1 = \mathbf{A}\mathbf{V}_2 - \mathbf{B}\mathbf{I}_2$$

$$\mathbf{I}_1 = \mathbf{C}\mathbf{V}_2 - \mathbf{D}\mathbf{I}_2$$

$$\mathbf{B} = \left. \frac{\mathbf{V}_1}{-\mathbf{I}_2} \right|_{\mathbf{V}_2 = 0}$$

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix} = [\mathbf{T}] \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix}$$

$$\mathbf{C} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_2 = 0}$$

\mathbf{A} and \mathbf{D} are dimensionless, \mathbf{B} is in Ohms, and \mathbf{C} is in siemens.

$$\mathbf{D} = \left. \frac{\mathbf{I}_1}{-\mathbf{I}_2} \right|_{\mathbf{V}_2 = 0}$$

When $\mathbf{AD} - \mathbf{BC} = 1$, the two-port is reciprocal and $\mathbf{A} = \mathbf{D}$, symmetrical.



Transmission Parameters – Example 1


Given the network below with assumed voltage polarities and current directions. Find the transmission parameters.

Solution

$$V_1 = (R_1 + R_2)I_1 + R_2I_2$$

$$V_2 = R_2I_1 + R_2I_2$$

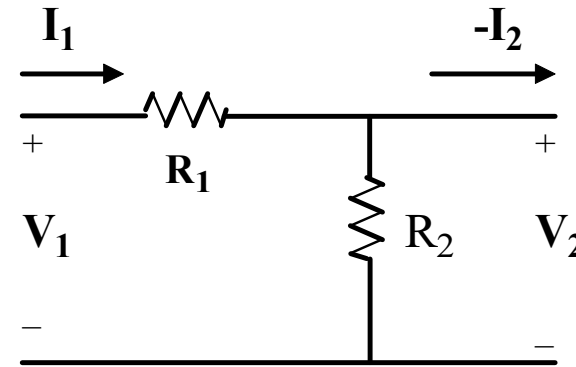From these equations we can directly evaluate the **A,B,C,D** parameters.



$$A = \left. \frac{V_1}{V_2} \right|_{I_2 = 0} = \frac{R_1 + R_2}{R_2}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2 = 0} = R_1$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2 = 0} = \frac{1}{R_2}$$



$$D = \left. \frac{I_1}{-I_2} \right|_{V_2 = 0} = 1$$

Transmission Parameters – Example 2

Find the transmission parameters.

Solution

$$A = \left. \frac{V_1}{V_2} \right|_{I_2 = 0} \quad C = \left. \frac{I_1}{V_2} \right|_{I_2 = 0}$$

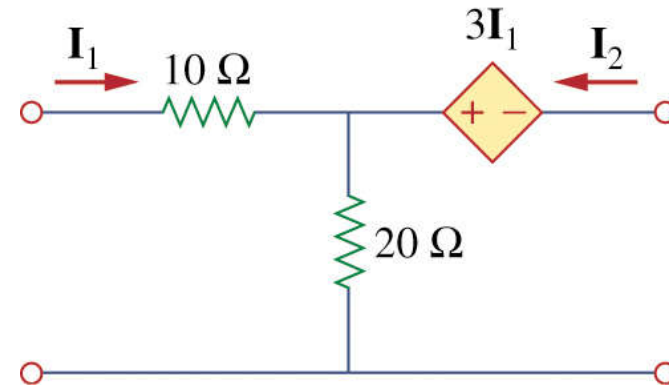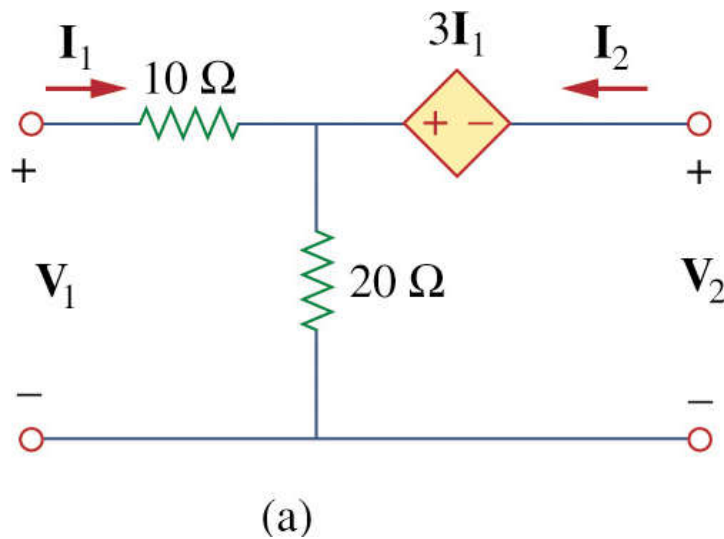

From Fig. (a)

$$V_1 = (10 + 20)I_1 = 30I_1$$

$$V_2 = 20I_1 - 3I_1 = 17I_1$$

Thus

$$A = \frac{V_1}{V_2} = \frac{30I_1}{17I_1} = 1.765, \quad C = \frac{I_1}{V_2} = \frac{I_1}{17I_1} = 0.0588 \text{ S}$$



Transmission Parameters – Example 2 cont.

$$\mathbf{B} = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad \mathbf{D} = \left. \frac{I_1}{-I_2} \right|_{V_2=0}$$

From Fig. (b):

$$\frac{V_1 - V_a}{10} - \frac{V_a}{20} + I_2 = 0$$

$$V_a = 3I_1 \text{ and } I_1 = (V_1 - V_a)/10$$


$$\Rightarrow V_1 = 13I_1$$

$$\Rightarrow I_1 - \frac{3I_1}{20} + I_2 = 0 \Rightarrow \frac{17}{20}I_1 = -I_2$$

Therefore,

$$\mathbf{D} = -\frac{I_1}{I_2} = \frac{20}{17} = 1.176$$
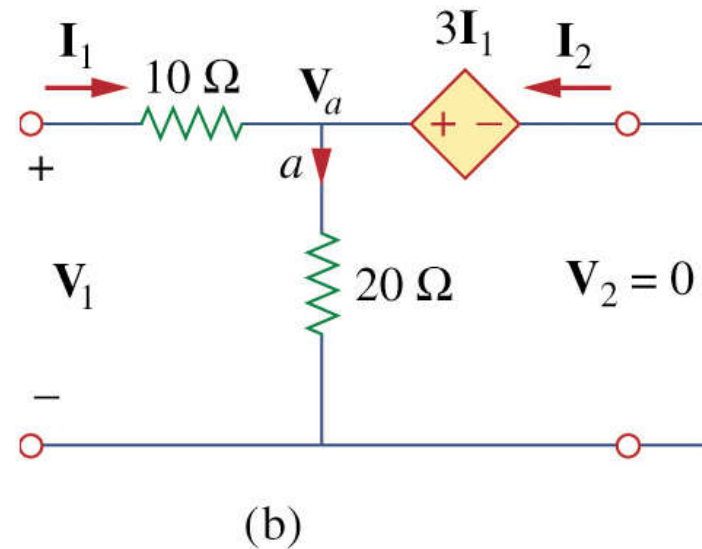
$$\mathbf{B} = -\frac{V_1}{V_2} = \frac{-13I_1}{(17/20)I_1} = 15.29 \text{ } \Omega$$



$$[\mathbf{T}] = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} = \begin{bmatrix} 1.765 & 15.29 \text{ } \Omega \\ 0.0588 \text{ S} & 1.176 \end{bmatrix}$$

Summary

z parameters	y parameters	T parameters (A,B,C,D)
$z_{11} = \frac{V_1}{I_1} \mid I_2=0$		
$z_{12} = \frac{V_1}{I_2} \mid I_1=0$		
$z_{21} = \frac{V_2}{I_1} \mid I_2=0$		
$z_{22} = \frac{V_2}{I_2} \mid I_1=0$		




Relationship between y and z Parameters

Given the z parameters, find the y parameters:

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = [\mathbf{z}] \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} \Rightarrow \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = [\mathbf{z}]^{-1} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

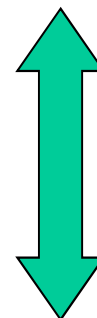$[\mathbf{z}]^{-1}$ is the inverse of $[\mathbf{z}]$



$$[\mathbf{y}] = [\mathbf{z}]^{-1}$$

$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{y}_{11} & \mathbf{y}_{12} \\ \mathbf{y}_{21} & \mathbf{y}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = [\mathbf{y}] \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

Relationship between y and z Parameters

$$[\mathbf{z}] = \begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} \Rightarrow \Delta_z = \mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21}$$

$$[\mathbf{y}] = [\mathbf{z}]^{-1}$$

$$\begin{bmatrix} \mathbf{y}_{11} & \mathbf{y}_{12} \\ \mathbf{y}_{21} & \mathbf{y}_{22} \end{bmatrix} = \frac{\begin{bmatrix} \mathbf{z}_{22} & -\mathbf{z}_{12} \\ -\mathbf{z}_{21} & \mathbf{z}_{11} \end{bmatrix}}{\Delta_z} = \frac{\begin{bmatrix} \mathbf{z}_{22} & -\mathbf{z}_{12} \\ -\mathbf{z}_{21} & \mathbf{z}_{11} \end{bmatrix}}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21}}$$

$$\begin{aligned} \mathbf{y}_{11} &= \frac{\mathbf{z}_{22}}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21}} \\ \mathbf{y}_{12} &= -\frac{\mathbf{z}_{12}}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21}} \\ \mathbf{y}_{21} &= -\frac{\mathbf{z}_{21}}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21}} \\ \mathbf{y}_{22} &= \frac{\mathbf{z}_{11}}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21}} \end{aligned}$$


Relationship between y and z Parameters

For the y parameters we have

$$\mathbf{I} = \mathbf{Y} \mathbf{V}$$

For the \mathbf{Z} parameters we have

$$\mathbf{V} = \mathbf{Z} \mathbf{I}$$

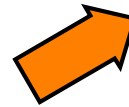

From above

$$\mathbf{V} = \mathbf{Y}^{-1} \mathbf{I} = \mathbf{Z} \mathbf{I}$$

Therefore

$$\mathbf{Z} = \mathbf{Y}^{-1} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} \frac{y_{22}}{\Delta_{\mathbf{Y}}} & \frac{-y_{12}}{\Delta_{\mathbf{Y}}} \\ \frac{-y_{21}}{\Delta_{\mathbf{Y}}} & \frac{y_{11}}{\Delta_{\mathbf{Y}}} \end{bmatrix}$$


where

$$\Delta_{\mathbf{Y}} = y_{11}y_{22} - y_{12}y_{21}$$

Interconnection

Three ways that two ports are interconnected


* Series

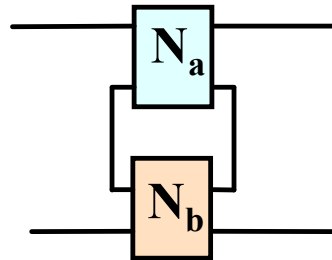

***Z** parameters*

$$[\mathbf{z}] = [\mathbf{z}_a] + [\mathbf{z}_b]$$


* Parallel

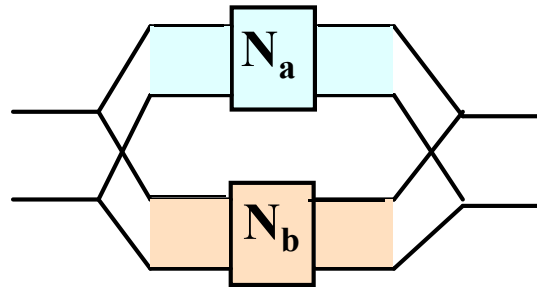

***Y** parameters*

$$[\mathbf{y}] = [\mathbf{y}_a] + [\mathbf{y}_b]$$

* Cascade

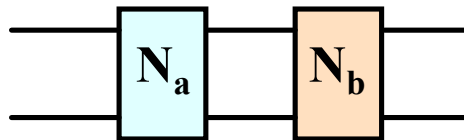


***ABCD** parameters*

$$[\mathbf{T}] = [\mathbf{T}_a][\mathbf{T}_b]$$

Interconnection – Series Connection
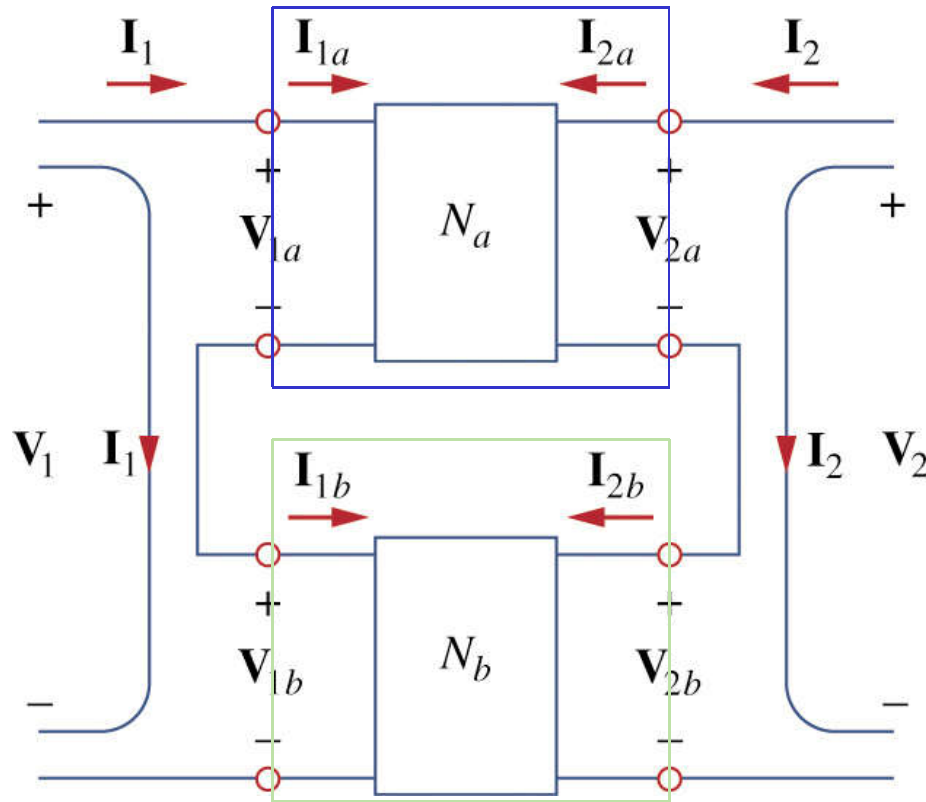
$$\begin{aligned} \mathbf{V}_1 &= \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 &= \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 \end{aligned}$$



For network N_a

$$\mathbf{V}_{1a} = \mathbf{z}_{11a}\mathbf{I}_{1a} + \mathbf{z}_{12a}\mathbf{I}_{2a}$$

$$\mathbf{V}_{2a} = \mathbf{z}_{21a}\mathbf{I}_{1a} + \mathbf{z}_{22a}\mathbf{I}_{2a}$$

For network N_b

$$\mathbf{V}_{1b} = \mathbf{z}_{11b}\mathbf{I}_{1b} + \mathbf{z}_{12b}\mathbf{I}_{2b}$$

$$\mathbf{V}_{2b} = \mathbf{z}_{21b}\mathbf{I}_{1b} + \mathbf{z}_{22b}\mathbf{I}_{2b}$$

From the diagram :

$$\mathbf{I}_1 = \mathbf{I}_{1a} = \mathbf{I}_{1b}, \quad \mathbf{I}_2 = \mathbf{I}_{2a} = \mathbf{I}_{2b}$$

Interconnection – Series Connection

From the diagram

$$\mathbf{V}_1 = \mathbf{V}_{1a} + \mathbf{V}_{1b} = (\mathbf{z}_{11a} + \mathbf{z}_{11b})\mathbf{I}_1 + (\mathbf{z}_{12a} + \mathbf{z}_{12b})\mathbf{I}_2$$

$$\mathbf{V}_2 = \mathbf{V}_{2a} + \mathbf{V}_{2b} = (\mathbf{z}_{21a} + \mathbf{z}_{21b})\mathbf{I}_1 + (\mathbf{z}_{22a} + \mathbf{z}_{22b})\mathbf{I}_2$$

So


$$\begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11a} + \mathbf{z}_{11b} & \mathbf{z}_{12a} + \mathbf{z}_{12b} \\ \mathbf{z}_{21a} + \mathbf{z}_{21b} & \mathbf{z}_{22a} + \mathbf{z}_{22b} \end{bmatrix}$$

$$[\mathbf{z}] = [\mathbf{z}_a] + [\mathbf{z}_b]$$

This can be extended to n networks in series.


$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$
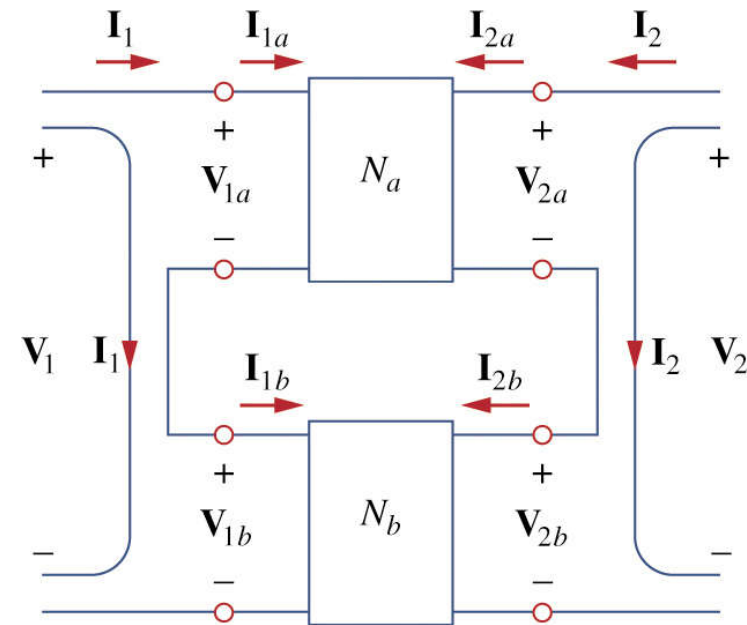
$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2$$



Interconnection – Series Connection Example

Find V_2/V_s in the circuit

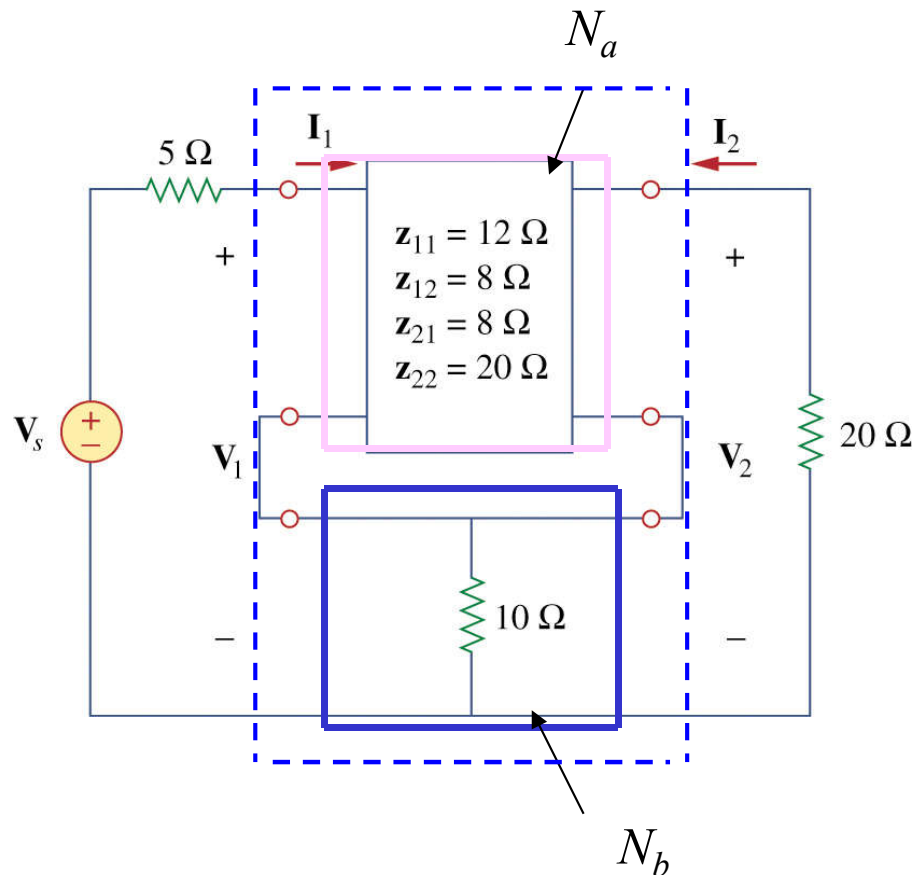

Solution

This can be regarded as two - ports in series.

For N_b ,

$$z_{12b} = z_{21b} = 10 = z_{11b} = z_{22b}$$

Thus,

$$\begin{aligned} [\mathbf{z}] &= [\mathbf{z}_a] + [\mathbf{z}_b] \\ &= \begin{bmatrix} 12 & 8 \\ 8 & 20 \end{bmatrix} + \begin{bmatrix} 10 & 10 \\ 10 & 10 \end{bmatrix} = \begin{bmatrix} 22 & 18 \\ 18 & 30 \end{bmatrix} \end{aligned}$$

And

$$V_1 = z_{11}I_1 + z_{12}I_2 = 22I_1 + 18I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2 = 18I_1 + 30I_2$$

Interconnection – Series Connection Example cont.

Also, at the input port $\mathbf{V}_1 = \mathbf{V}_s - 5\mathbf{I}_1$

and at the output port $\mathbf{V}_2 = -20\mathbf{I}_2 \Rightarrow \mathbf{I}_2 = -\frac{\mathbf{V}_2}{20}$

$$\Rightarrow \mathbf{V}_s - 5\mathbf{I}_1 = 22\mathbf{I}_1 - \frac{18}{20}\mathbf{V}_2 \Rightarrow \mathbf{V}_s = 27\mathbf{I}_1 - 0.9\mathbf{V}_2$$


$$\mathbf{V}_2 = 18\mathbf{I}_1 - \frac{30}{20}\mathbf{V}_2 \Rightarrow \mathbf{I}_1 = \frac{2.5}{18}\mathbf{V}_2$$

$$\Rightarrow \mathbf{V}_s = 27 \times \frac{2.5}{18}\mathbf{V}_2 - 0.9\mathbf{V}_2 = 2.85\mathbf{V}_2$$

$$\text{So: } \underline{\underline{\frac{\mathbf{V}_2}{\mathbf{V}_s} = \frac{1}{2.85} = 0.3509}}$$

$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 = 22\mathbf{I}_1 + 18\mathbf{I}_2$$
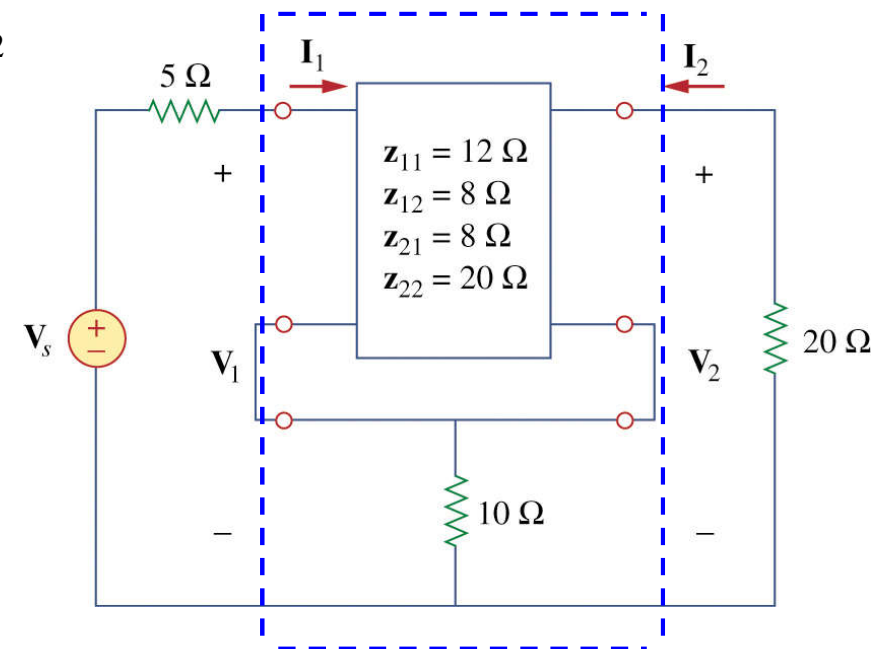
$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 = 18\mathbf{I}_1 + 30\mathbf{I}_2$$



Interconnection – Parallel Connection

$$\begin{aligned} \mathbf{I}_1 &= \mathbf{y}_{11} \mathbf{V}_1 + \mathbf{y}_{12} \mathbf{V}_2 \\ \mathbf{I}_2 &= \mathbf{y}_{21} \mathbf{V}_1 + \mathbf{y}_{22} \mathbf{V}_2 \end{aligned}$$

For network N_a

$$\mathbf{I}_{1a} = \mathbf{y}_{11a} \mathbf{V}_{1a} + \mathbf{y}_{12a} \mathbf{V}_{2a}$$

$$\mathbf{I}_{2a} = \mathbf{y}_{21a} \mathbf{V}_{1a} + \mathbf{y}_{22a} \mathbf{V}_{2a}$$

For network N_b


$$\mathbf{I}_{1b} = \mathbf{y}_{11b} \mathbf{V}_{1b} + \mathbf{y}_{12b} \mathbf{V}_{2b}$$

$$\mathbf{I}_{2b} = \mathbf{y}_{21b} \mathbf{V}_{1b} + \mathbf{y}_{22b} \mathbf{V}_{2b}$$

From the diagram :

$$\mathbf{V}_1 = \mathbf{V}_{1a} = \mathbf{V}_{1b}, \quad \mathbf{V}_2 = \mathbf{V}_{2a} = \mathbf{V}_{2b}$$
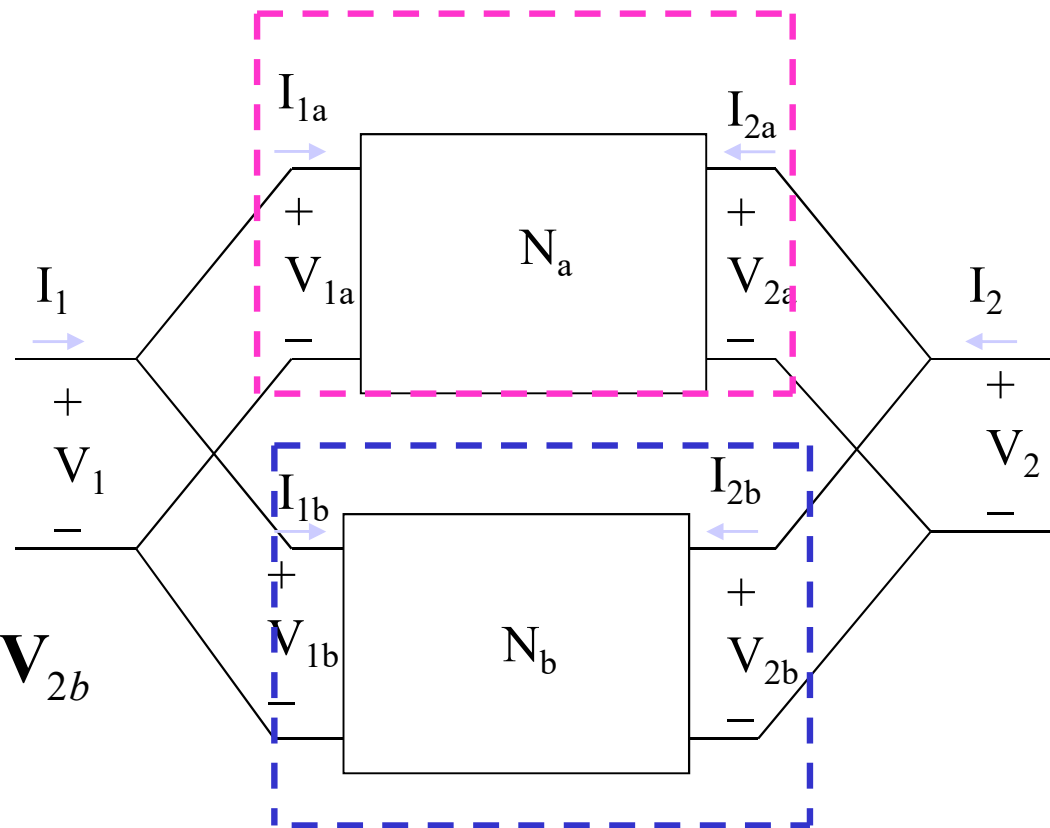
$$\mathbf{I}_1 = \mathbf{I}_{1a} + \mathbf{I}_{1b}, \quad \mathbf{I}_2 = \mathbf{I}_{2a} + \mathbf{I}_{2b}$$



Interconnection – Parallel Connection

$$\mathbf{I}_1 = \mathbf{I}_{1a} + \mathbf{I}_{1b} = (\mathbf{y}_{11a} + \mathbf{y}_{11b})\mathbf{V}_1 + (\mathbf{y}_{12a} + \mathbf{y}_{12b})\mathbf{V}_2$$

$$\mathbf{I}_2 = \mathbf{I}_{2a} + \mathbf{I}_{2b} = (\mathbf{y}_{21a} + \mathbf{y}_{21b})\mathbf{V}_1 + (\mathbf{y}_{22a} + \mathbf{y}_{22b})\mathbf{V}_2$$


$$\mathbf{I}_1 = \mathbf{y}_{11}\mathbf{V}_1 + \mathbf{y}_{12}\mathbf{V}_2$$

$$\mathbf{I}_2 = \mathbf{y}_{21}\mathbf{V}_1 + \mathbf{y}_{22}\mathbf{V}_2$$

So

$$\begin{bmatrix} \mathbf{y}_{11} & \mathbf{y}_{12} \\ \mathbf{y}_{21} & \mathbf{y}_{22} \end{bmatrix} = \begin{bmatrix} \mathbf{y}_{11a} + \mathbf{y}_{11b} & \mathbf{y}_{12a} + \mathbf{y}_{12b} \\ \mathbf{y}_{21a} + \mathbf{y}_{21b} & \mathbf{y}_{22a} + \mathbf{y}_{22b} \end{bmatrix}$$
$$[\mathbf{y}] = [\mathbf{y}_a] + [\mathbf{y}_b]$$

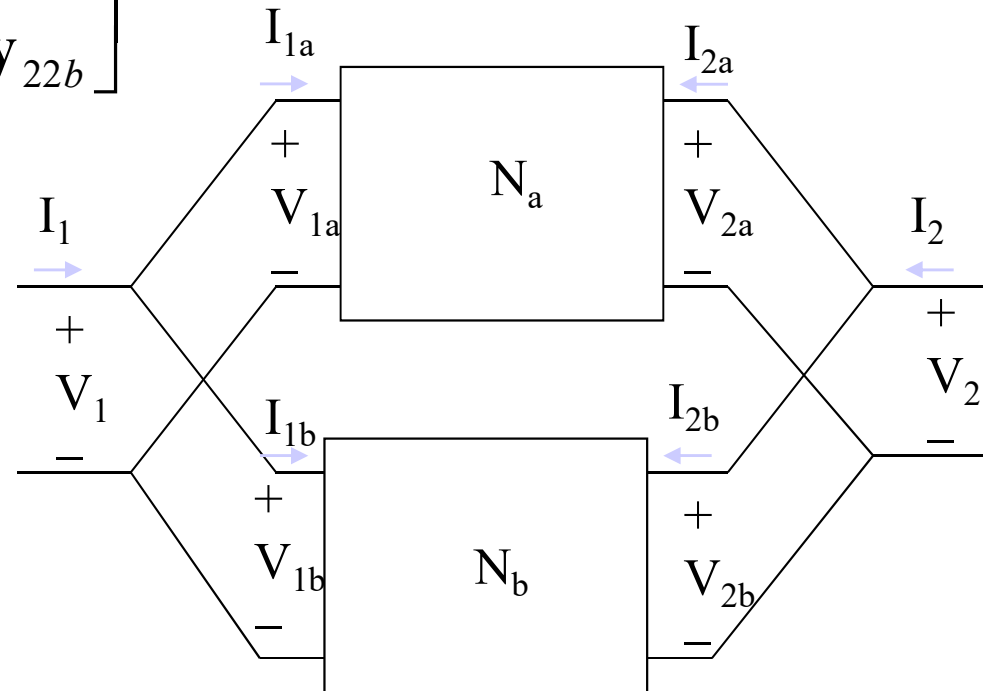This can be extended to n networks in parallel.





Interconnection – Parallel Connection Example

Find the y parameters of the two-port

Recall

When the two-port network is linear and has no dependent sources: $\mathbf{y}_{12} = \mathbf{y}_{21}$, Reciprocal Two-Port Network

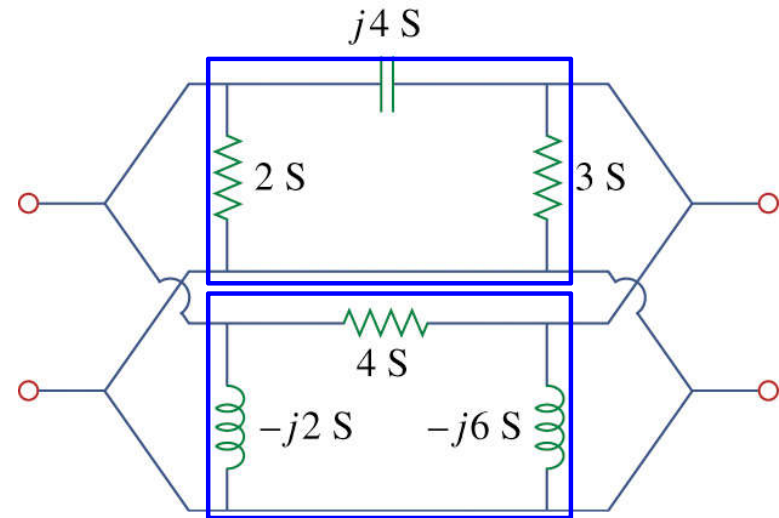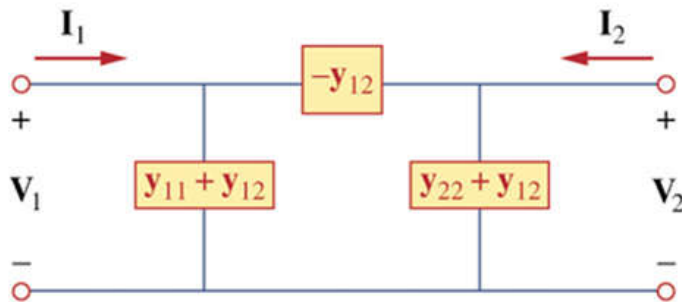Π -equivalent circuit for reciprocal two-port network





Recall

Any two-port made entirely of resistors, capacitors and inductors must be reciprocal.

Interconnection – Parallel Connection Example cont.

Solution

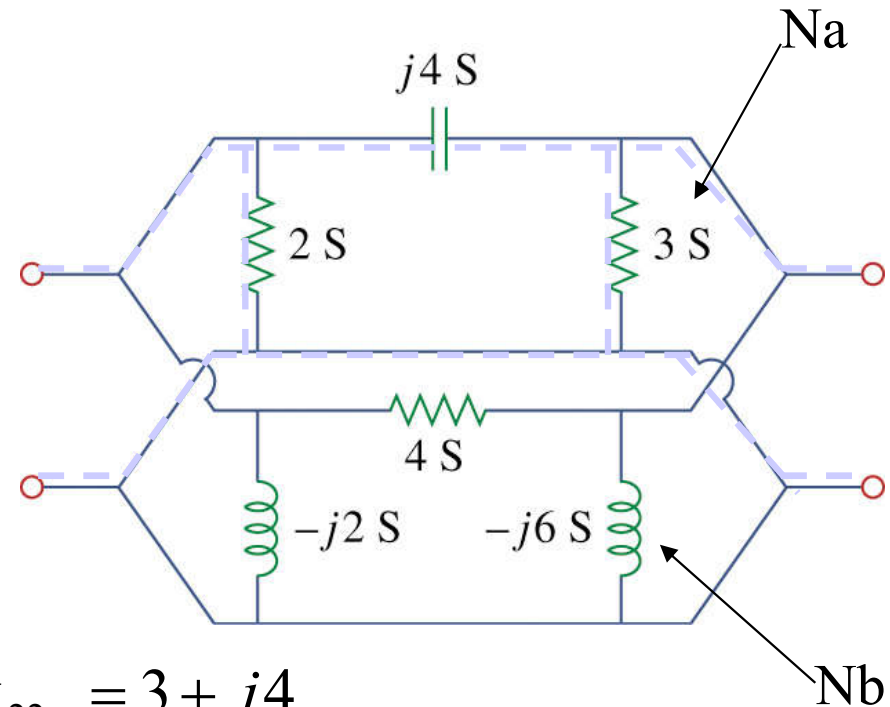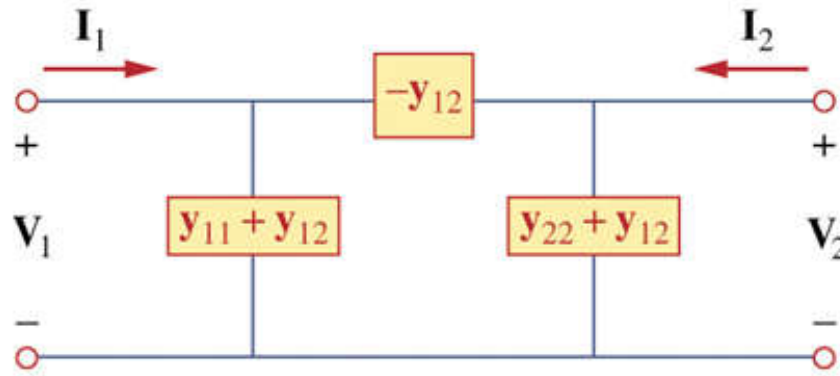

$$y_{12a} = -j4 = y_{21a} \quad y_{11a} = 2 + j4 \quad y_{22a} = 3 + j4$$


$$y_{12b} = -4 = y_{21b} \quad y_{11b} = 4 - j2 \quad y_{22b} = 4 - j6$$

$$[y] = [y_a] + [y_b] = \begin{bmatrix} 6 + j2 & -4 - j4 \\ -4 - j4 & 7 - j2 \end{bmatrix} \text{ S}$$

Interconnection - Cascade Connection

Cascade connection of two 2-port networks: the output of one is the input of the other.
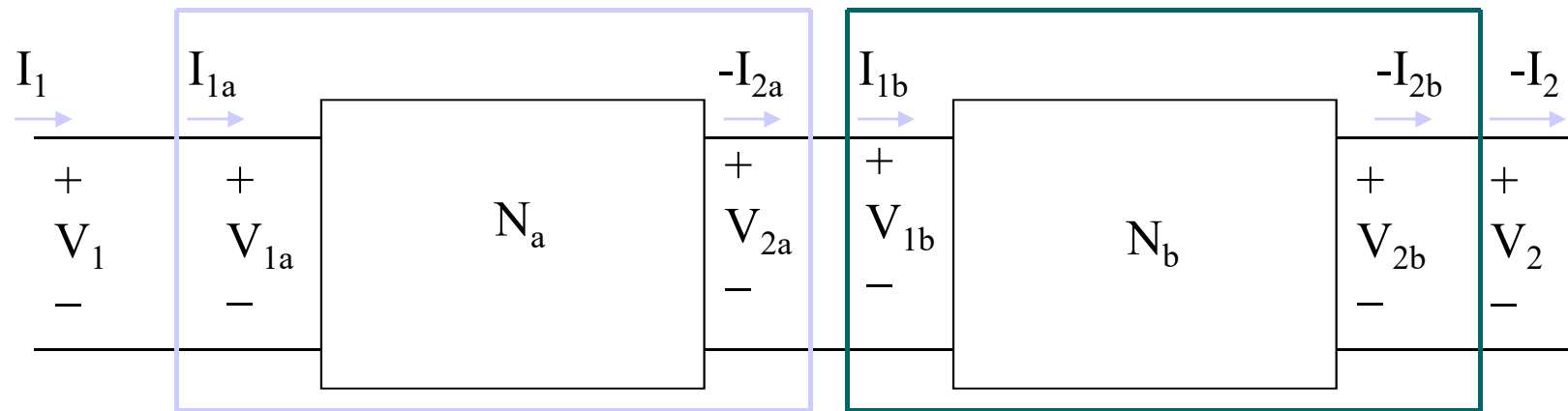
$$\begin{aligned}\mathbf{V}_1 &= \mathbf{A}\mathbf{V}_2 - \mathbf{B}\mathbf{I}_2 \\ \mathbf{I}_1 &= \mathbf{C}\mathbf{V}_2 - \mathbf{D}\mathbf{I}_2\end{aligned}$$




For the two networks

$$\begin{bmatrix} \mathbf{V}_{1a} \\ \mathbf{I}_{1a} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_a & \mathbf{B}_a \\ \mathbf{C}_a & \mathbf{D}_a \end{bmatrix} \begin{bmatrix} \mathbf{V}_{2a} \\ -\mathbf{I}_{2a} \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{V}_{1b} \\ \mathbf{I}_{1b} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_b & \mathbf{B}_b \\ \mathbf{C}_b & \mathbf{D}_b \end{bmatrix} \begin{bmatrix} \mathbf{V}_{2b} \\ -\mathbf{I}_{2b} \end{bmatrix}$$



Interconnection - Cascade Connection

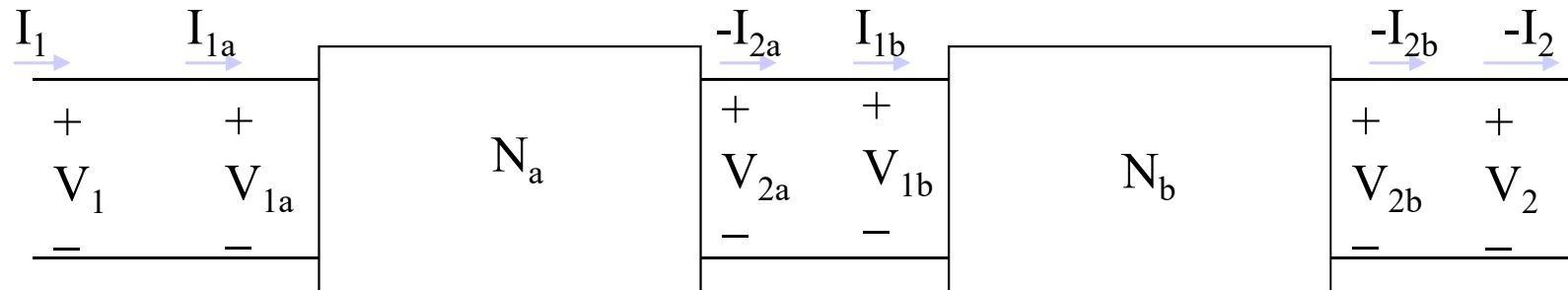

$$\begin{bmatrix} \mathbf{V}_{1a} \\ \mathbf{I}_{1a} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_a & \mathbf{B}_a \\ \mathbf{C}_a & \mathbf{D}_a \end{bmatrix} \begin{bmatrix} \mathbf{V}_{2a} \\ -\mathbf{I}_{2a} \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{V}_{1b} \\ \mathbf{I}_{1b} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_b & \mathbf{B}_b \\ \mathbf{C}_b & \mathbf{D}_b \end{bmatrix} \begin{bmatrix} \mathbf{V}_{2b} \\ -\mathbf{I}_{2b} \end{bmatrix}$$

From the diagram


$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{V}_{1a} \\ \mathbf{I}_{1a} \end{bmatrix} \quad \begin{bmatrix} \mathbf{V}_{2a} \\ -\mathbf{I}_{2a} \end{bmatrix} = \begin{bmatrix} \mathbf{V}_{1b} \\ \mathbf{I}_{1b} \end{bmatrix} \quad \begin{bmatrix} \mathbf{V}_{2b} \\ -\mathbf{I}_{2b} \end{bmatrix} = \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix}$$

So we have

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{A}_a & \mathbf{B}_a \\ \mathbf{C}_a & \mathbf{D}_a \end{bmatrix} \begin{bmatrix} \mathbf{V}_{2a} \\ -\mathbf{I}_{2a} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_a & \mathbf{B}_a \\ \mathbf{C}_a & \mathbf{D}_a \end{bmatrix} \begin{bmatrix} \mathbf{A}_b & \mathbf{B}_b \\ \mathbf{C}_b & \mathbf{D}_b \end{bmatrix} \begin{bmatrix} \mathbf{V}_{2b} \\ -\mathbf{I}_{2b} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_a & \mathbf{B}_a \\ \mathbf{C}_a & \mathbf{D}_a \end{bmatrix} \begin{bmatrix} \mathbf{A}_b & \mathbf{B}_b \\ \mathbf{C}_b & \mathbf{D}_b \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix}$$



Interconnection - Cascade Connection

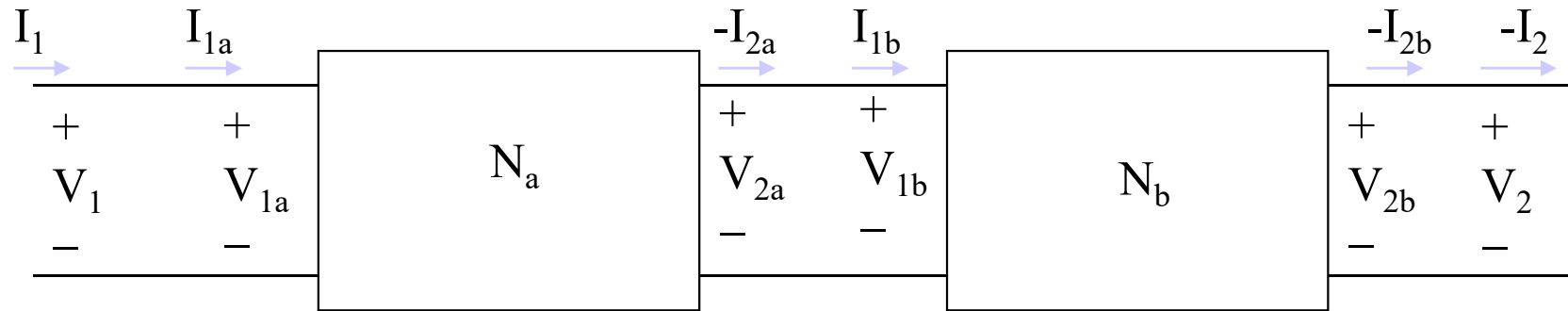

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{A}_a & \mathbf{B}_a \\ \mathbf{C}_a & \mathbf{D}_a \end{bmatrix} \begin{bmatrix} \mathbf{A}_b & \mathbf{B}_b \\ \mathbf{C}_b & \mathbf{D}_b \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix}$$

$$\begin{aligned} \mathbf{V}_1 &= \mathbf{A}\mathbf{V}_2 - \mathbf{B}\mathbf{I}_2 \\ \mathbf{I}_1 &= \mathbf{C}\mathbf{V}_2 - \mathbf{D}\mathbf{I}_2 \end{aligned}$$


Then

$$\begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_a & \mathbf{B}_a \\ \mathbf{C}_a & \mathbf{D}_a \end{bmatrix} \begin{bmatrix} \mathbf{A}_b & \mathbf{B}_b \\ \mathbf{C}_b & \mathbf{D}_b \end{bmatrix} \quad \text{or} \quad [\mathbf{T}] = [\mathbf{T}_a][\mathbf{T}_b]$$

$$[\mathbf{T}_a][\mathbf{T}_b] \neq [\mathbf{T}_b][\mathbf{T}_a]$$

Interconnection - Cascade Connection (Example)

Find the A,B,C,D parameters

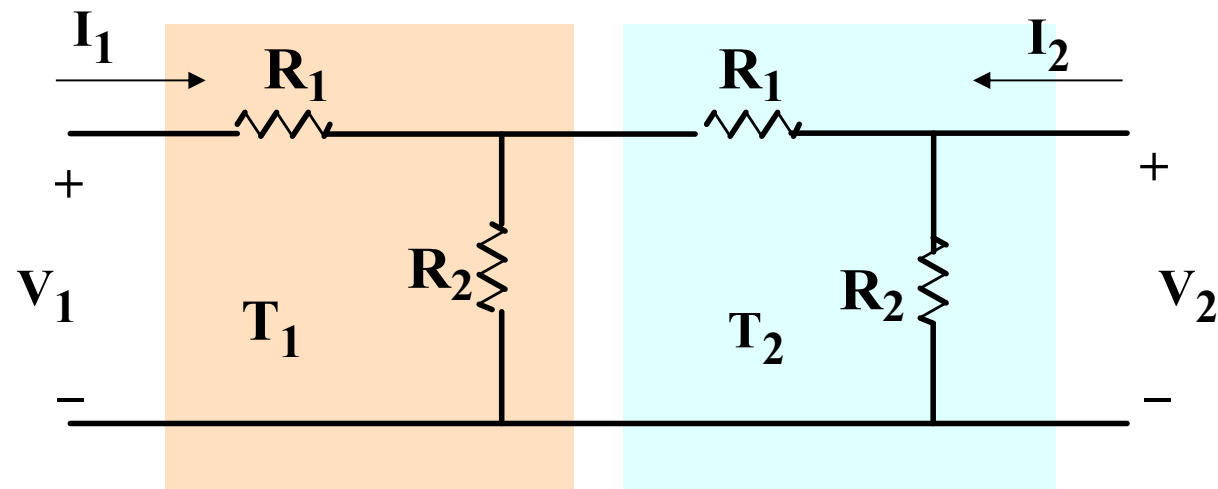

Transmission Parameters – Example 1 cont.


Given the network below with assumed voltage polarities and current directions. Find the transmission parameters.

Solution

$$V_1 = (R_1 + R_2)I_1 + R_2I_2$$

$$V_2 = R_2I_1 + R_2I_2$$

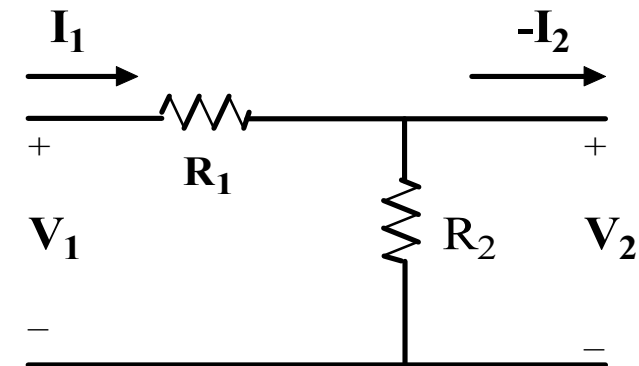From these equations we can directly evaluate the **A,B,C,D** parameters.



$$A = \left. \frac{V_1}{V_2} \right|_{I_2 = 0} = \frac{R_1 + R_2}{R_2}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2 = 0} = R_1$$


$$C = \left. \frac{I_1}{V_2} \right|_{I_2 = 0} = \frac{1}{R_2}$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2 = 0} = 1$$

Transmission Parameters – Example 1 cont.

Solution

$$\begin{aligned}
 A = \frac{V_1}{V_2} \bigg|_{I_2 = 0} &= \frac{R_1 + R_2}{R_2} \\
 C = \frac{I_1}{V_2} \bigg|_{I_2 = 0} &= \frac{1}{R_2} \\
 B = \frac{V_1}{-I_2} \bigg|_{V_2 = 0} &= R_1 \\
 D = \frac{I_1}{-I_2} \bigg|_{V_2 = 0} &= 1
 \end{aligned}$$

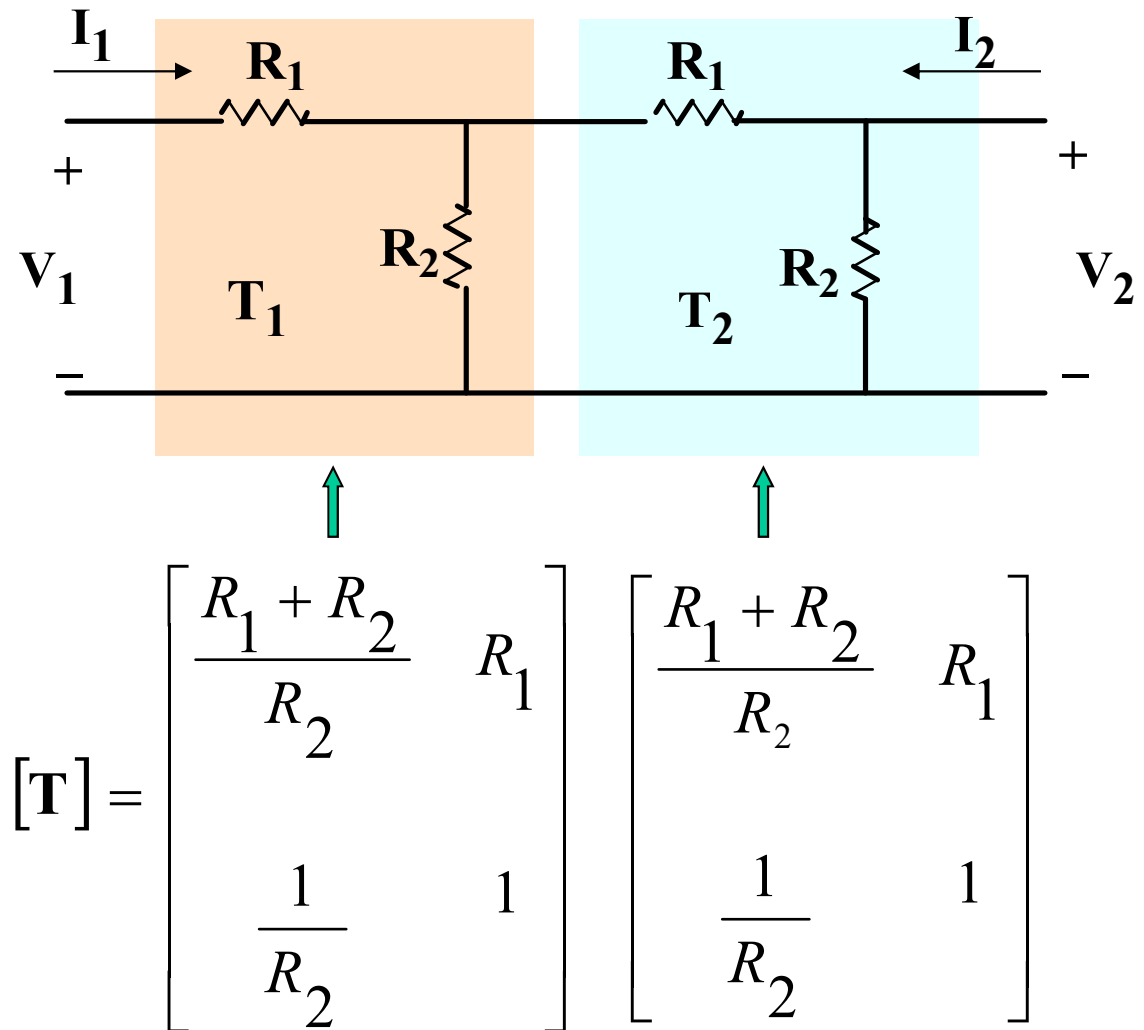

Transmission Parameters – Example 1 cont.

$$[\mathbf{T}] = \begin{bmatrix} \frac{R_1 + R_2}{R_2} & R_1 \\ \frac{1}{R_2} & 1 \end{bmatrix} \begin{bmatrix} \frac{R_1 + R_2}{R_2} & R_1 \\ \frac{1}{R_2} & 1 \end{bmatrix}$$

$$[\mathbf{T}] = \begin{bmatrix} \left(\frac{R_1 + R_2}{R_2} \right)^2 + \frac{R_1}{R_2} & \frac{R_1 + R_2}{R_2} R_1 + R_1 \\ \frac{R_1 + R_2}{R_2} \frac{1}{R_2} + \frac{1}{R_2} & \frac{R_1}{R_2} + 1 \end{bmatrix} = \begin{bmatrix} \frac{(R_1 + R_2)^2 + R_1^2}{R_2^2} & \frac{R_1^2 + 2R_1R_2}{R_2} \\ \frac{R_1 + 2R_2}{R_2^2} & \frac{R_1 + R_2}{R_2} \end{bmatrix}$$

Summary

- Two-port networks consist of input port and output port.
- Four parameters were discussed to model the two-port network, they are impedance $[z]$, admittance $[y]$, hybrid $[h]$ and transmission $[T]$ parameters.
- The relationships between the four sets of parameters (especially z and y parameters).
- Two-port network can be connected in series, parallel and cascade. In series connection, z -parameters are added, in parallel, y -parameters are added, and in cascade, T -parameters are multiplied.

Quiz

- 1. When port 1 of a two-port circuit is short-circuited, $\mathbf{I}_1 = 4 \mathbf{I}_2$ and $\mathbf{V}_2 = 0.25 \mathbf{I}_2$. Which of the following is true?
 - (a) $y_{11} = 4$; (b) $y_{12} = 16$;
 - (c) $y_{21} = 16$; (d) $y_{22} = 0.25$.

- 2. A two-port is described by the following equations:

$$\mathbf{V}_1 = 50 \mathbf{I}_1 + 10 \mathbf{I}_2$$

$$\mathbf{V}_2 = 30 \mathbf{I}_1 + 20 \mathbf{I}_2$$

Which of the following is *not* true?

- (a) $z_{12} = 10$; (b) $y_{12} = -0.0143$
- (c) $z_{21} = 30$; (d) $A = 50$.

