

# EEE213 Power Electronics and Electromechanism

## 6. AC-AC Controller

# **EEE213 Power Electronics and Electromechanism**

**Lab arrangement (Room EE411)**

**11<sup>th</sup> April Thursday (9:00-12:00 & 2:00 -5:00)**

**Deadline: May 5th, 23:55pm**

TA (PhD students) :

1. Chu Guanying: [Guanying.chu@xjtlu.edu.cn](mailto:Guanying.chu@xjtlu.edu.cn)

1. Wang Yuanchen: [Yuanchen.wang@xjtlu.edu.cn](mailto:Yuanchen.wang@xjtlu.edu.cn)

# EEE213 Power Electronics and Electromechanism

## Assignment 1

Deadline: ~~21st April~~, 12th May 2019. Time: 23.55.

## Assignment 2

Deadline: 19th May 2019. Time: 23.55.

**ALL Tutorial questions (week11 &12)**

TA (PhD student) :


1. Yujie Liu: Yujie.liu@xjtlu.edu.cn

# Outline

---

- 1. AC-AC Voltage Converters
  - 1.1 Phase control
    - Resistive load
    - Inductive load
    - Three-phase system
  - 1.2 On-off control
    - Principles
    - Static switches (AC)
    - Bus transfer
- 2. Cycloconverters
  - 2.1 Basic operation principle
  - 2.2 Single phase system
  - 2.3 Three phase system
    - Three-phase to single phase
    - Three-phase to three phase

# Classification of AC to AC converters

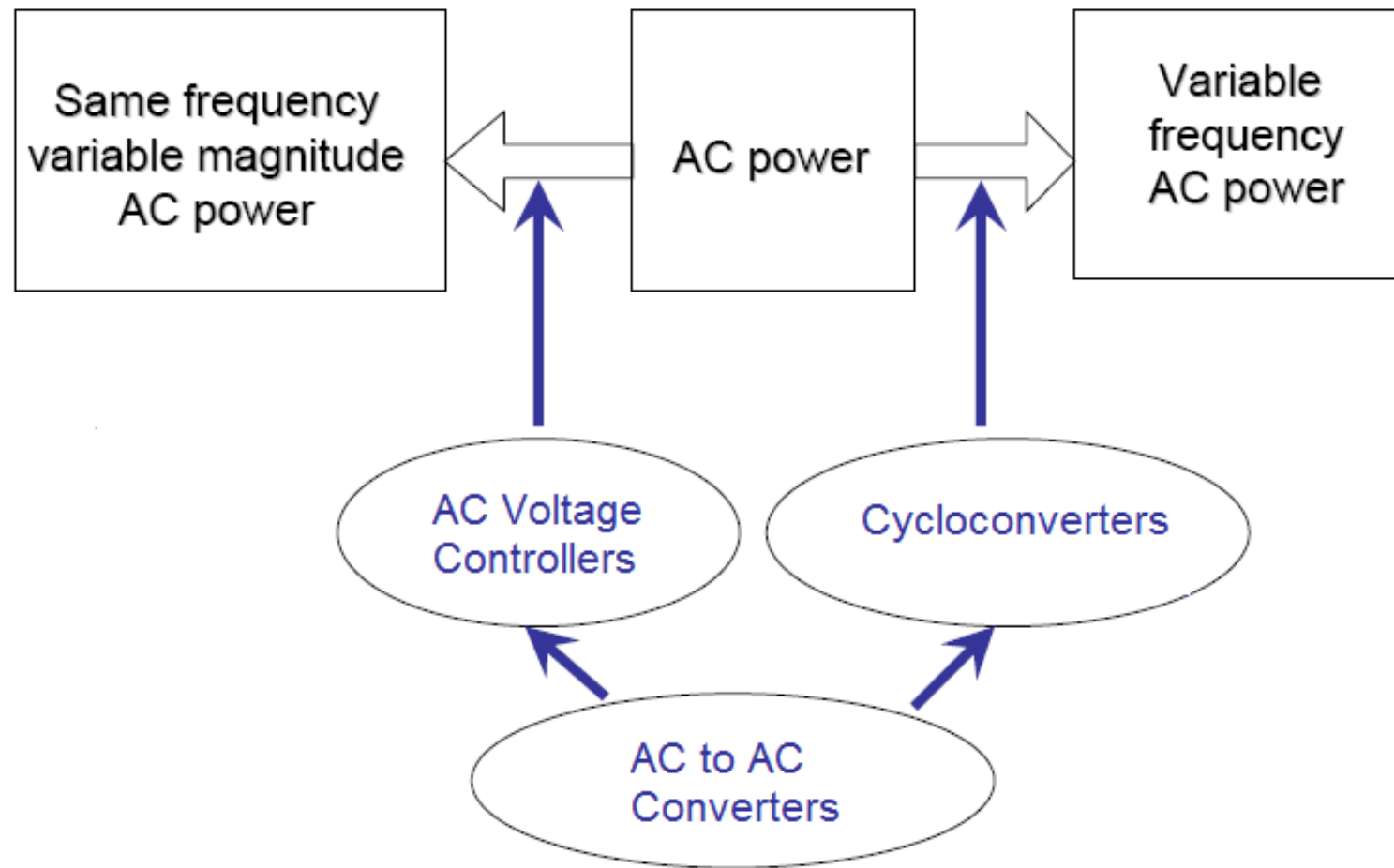



# 1. AC-AC voltage control


---

In order to get variable AC voltage from an AC source, two techniques are often used:


- Phase control
  - Similarly in AC-DC converters, the firing angle of the devices are controlled.
  - The devices conduct a portion of each cycle
- On-off control
  - The devices conduct some cycles in a period of time and then disconnect some cycles
  - The firing angle of devices is 0. But for some cycles, the firing pulses are turned off.
  - Lower switching losses
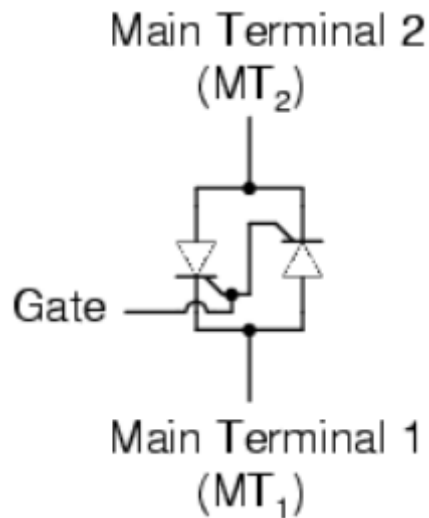
# 1.1 Phase control



- The strategy is to use anti-parallel connected thyristors or TRIACS (Triode AC Switch).
  - Two SCRs connected in anti-parallel with a common gate
  - Can conduct in both ways



TRIAC schematic symbol

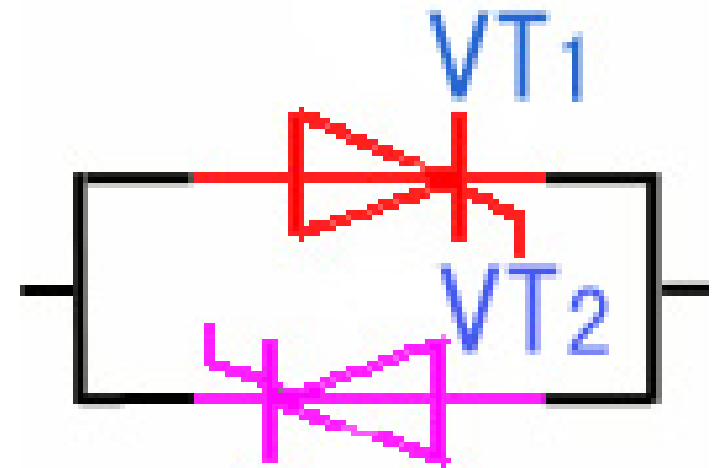

## 1.1.1 Single-phase, resistive load

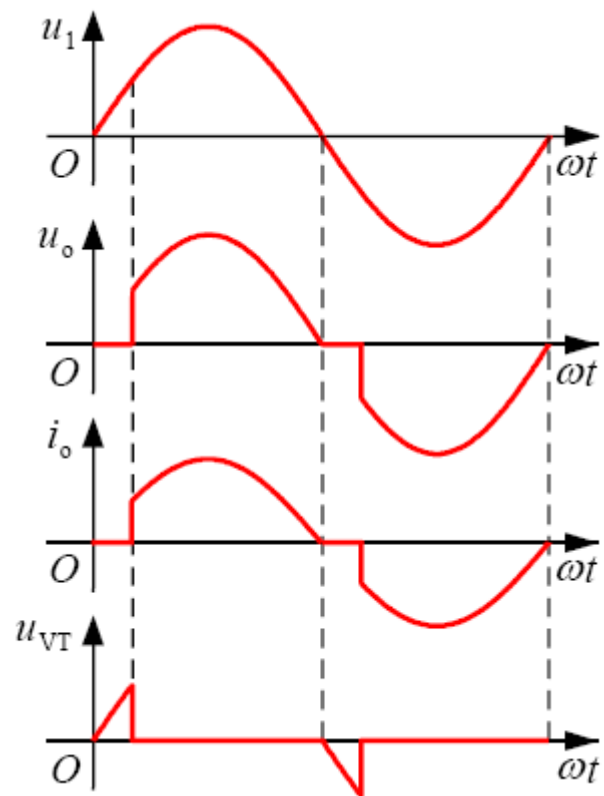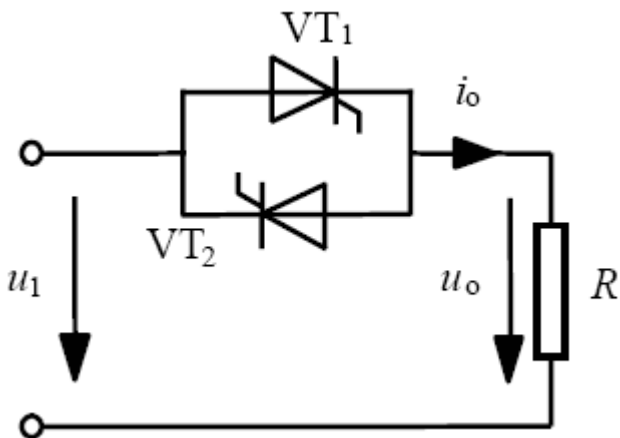

The phase shift range  
(operation range of phase  
delay angle):  $0 \leq \alpha \leq \pi$

Very similar to the case of rectifiers. Instead of having a DC output voltage, the output is alternative.



## 1.1.1 Single-phase, resistive load

- The rms value of the output voltage is

$$\begin{aligned} V_{RMS} &= \sqrt{\frac{2}{2\pi} \int_{\alpha}^{\pi} (\sqrt{2}V_s \sin \omega t)^2 d(\omega t)} \\ &= \sqrt{\frac{4V_s^2}{4\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) d(\omega t)} \\ &= V_s \sqrt{\frac{\pi - \alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} \end{aligned}$$

- By varying  $\alpha$  from 0 to  $\pi$ ,  $V_{RMS}$  can be varied from 0 to  $V_s$ .

## 1.1.1 Single-phase, resistive load

- The rms value of the output current is

$$I_{RMS} = \frac{V_{RMS}}{R}$$

- The rms value of thyristor current

$$I_{VT} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} \left( \frac{\sqrt{2}V_s \sin \omega t}{R} \right)^2 d(\omega t)} = \frac{I_{RMS}}{\sqrt{2}}$$


- Power factor of the circuit

$$\begin{aligned} f_p &= \frac{P_{RMS}}{P_s} = \frac{V_{RMS} I_{RMS}}{V_s I_s} = \frac{V_{RMS} I_{RMS}}{V_s I_{RMS}} \\ &= \sqrt{\frac{\pi - \alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} \end{aligned}$$




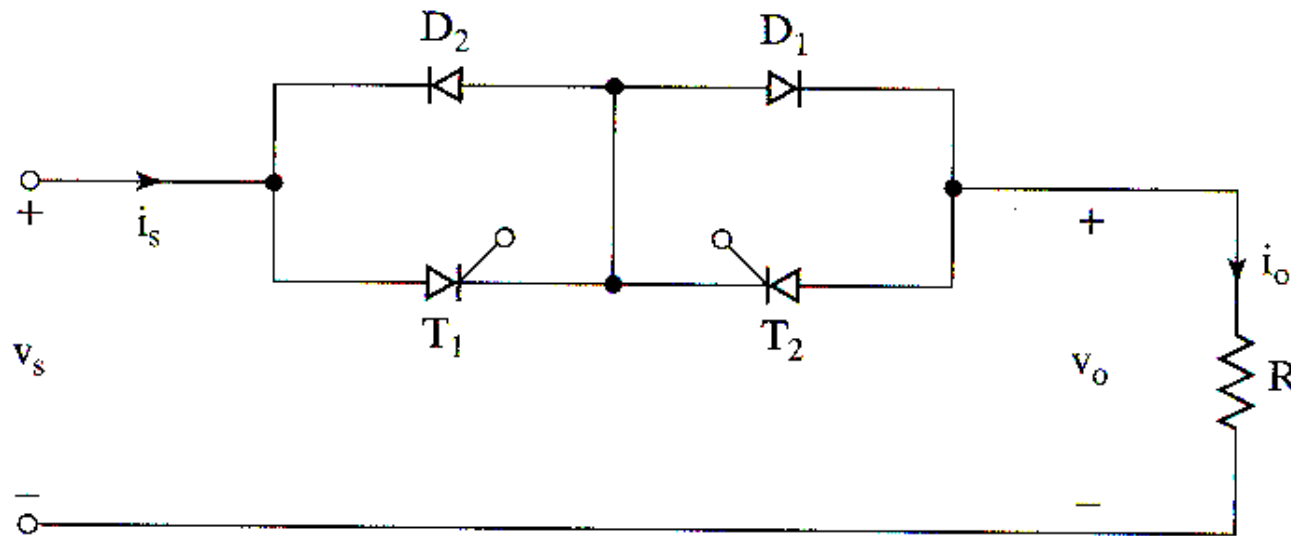
## *With common cathode*

- One isolated gating circuit is needed, at the cost of two extra diodes
- Conduction losses will increase and efficiency will drop, due to two devices conduct at the same time.



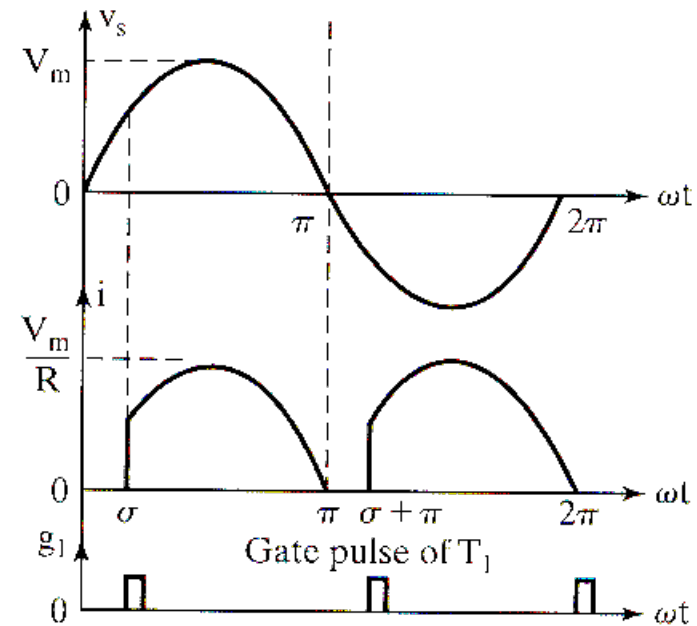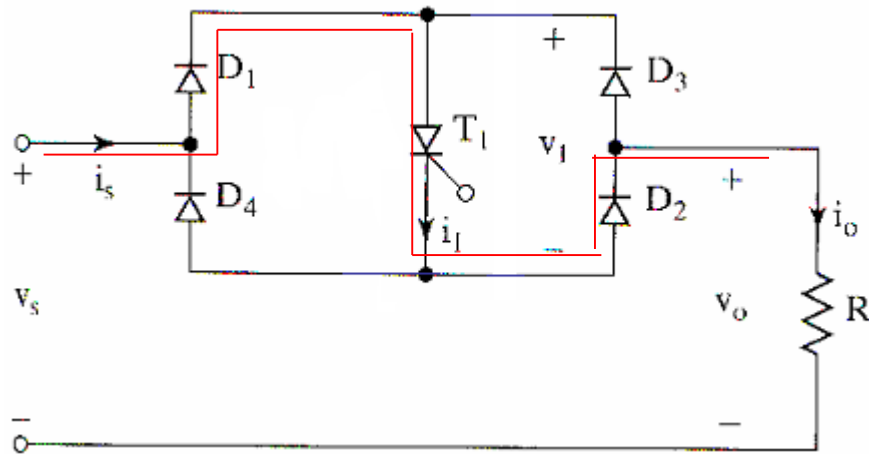
# With one switch


- Only works well for a resistive load.
  - With large inductance in the circuit, thyristor may not be turned off in every half-cycle, and this may result in a loss of control.
- Conduction loss is high, due to the fact that three devices conduct at the same time.



## 1.1.2 Single-phase, inductive load

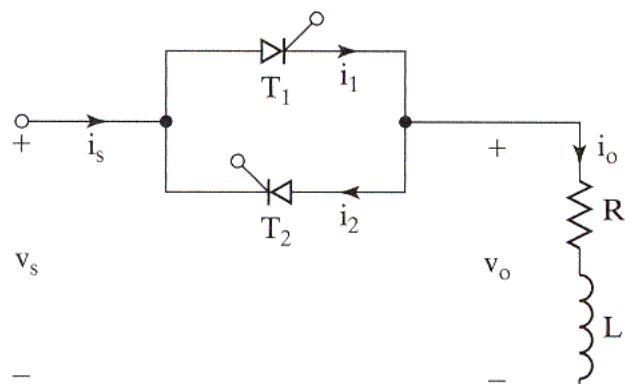

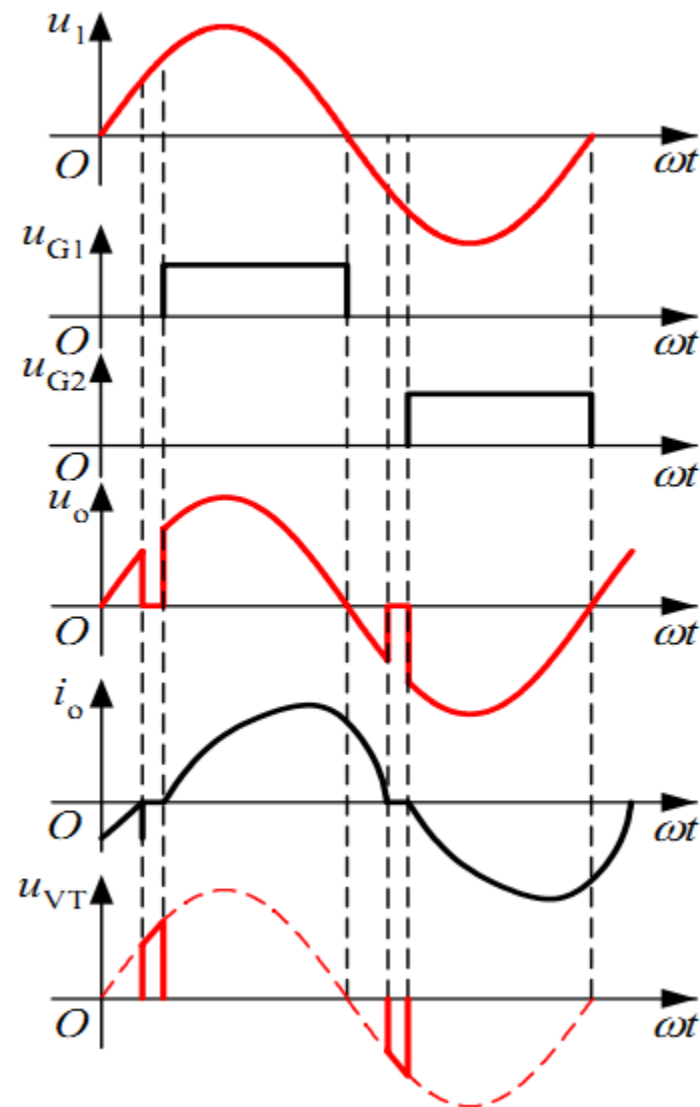- The device does not turn off at  $\omega t = \pi$ , but continues conducting till the current falls to 0.
- Phase shift range:  $\theta \leq \alpha \leq \pi$



# Quantitative analysis

- Solving the differential equation

$$L \frac{di_0}{dt} + Ri_0 = \sqrt{2}U_2 \sin \omega t$$

$$i_0|_{\omega t=\alpha} = 0$$

$$\Rightarrow i_0 = \frac{\sqrt{2}U_2}{Z} \left[ \sin(\omega t - \theta) - \sin(\alpha - \theta) e^{\frac{\alpha - \omega t}{\tan \theta}} \right]$$


- Considering  $i_0=0$  when  $\omega t=\beta$

$$\Rightarrow \sin(\beta - \theta) = \sin(\alpha - \theta) e^{\frac{\alpha - \beta}{\tan \theta}}$$

- So we can get extinction angle  $\beta$
- and conduction angle  $\delta = \beta - \alpha$


- Phase shift range
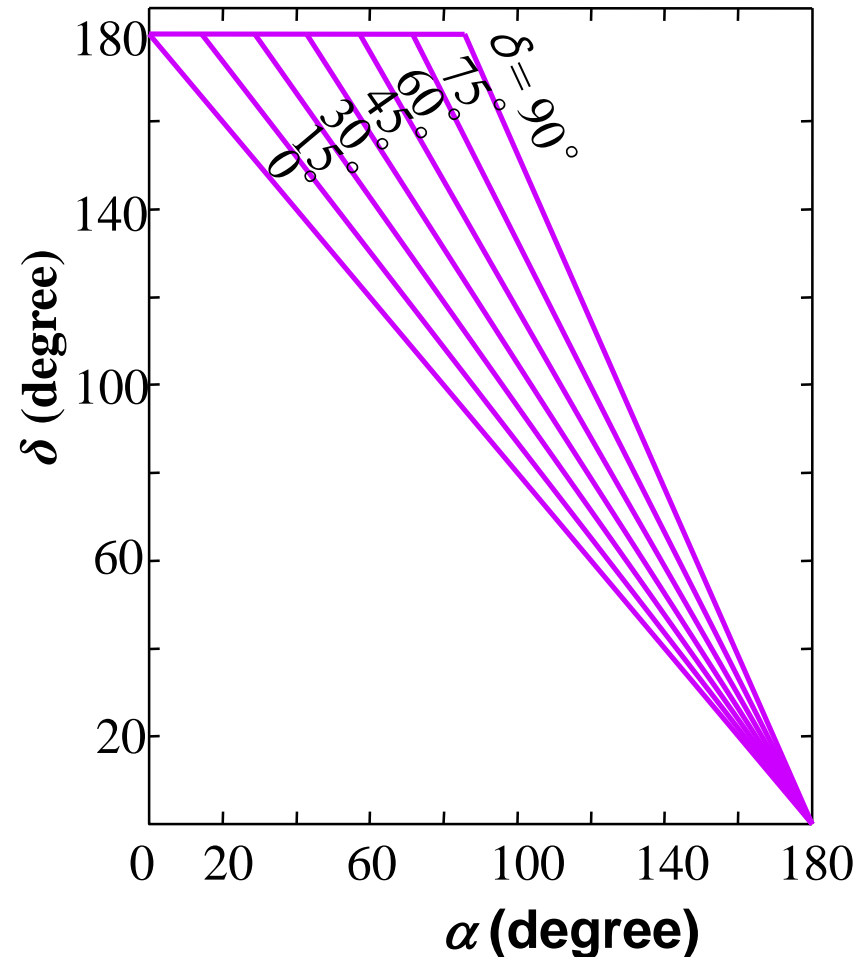
$$\theta = \arctan \frac{\omega L}{R} \leq \alpha \leq \pi$$


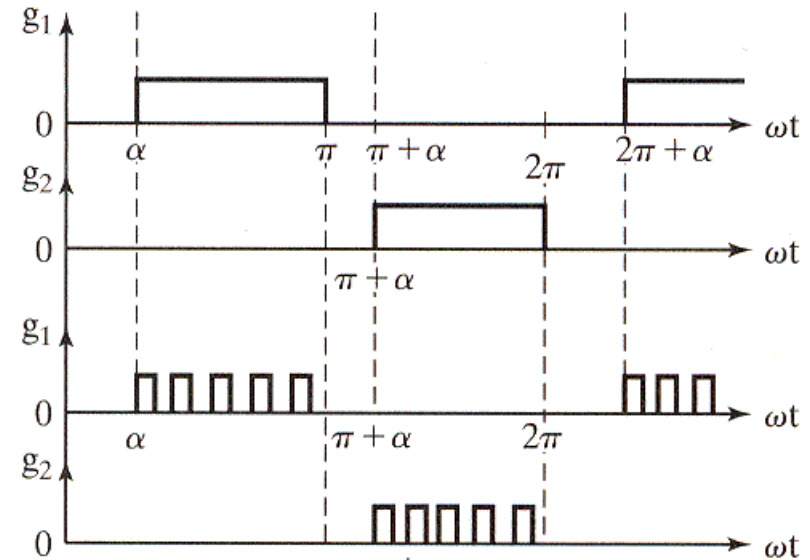
# Quantitative analysis

- The larger the inductance, the longer the switch conducts. If the firing pulse for the other switch arrives earlier than this switch turns off, then it may not be fired.
  - Continuous pulse firing: increased conduction losses and a larger isolating transformer
  - A train of pulses with short duration



## 1.2. On-off control


---

The main problem of phase control is the high THD

- On-off control
  - The switch conducts for some cycles and then turn off for some cycles: duty cycle
  - Zero-voltage/zero-current crossing to reduce the THD
  - Very good for applications having high mechanical inertia or high thermal time constant



## 1.2.1 Basic On-off control

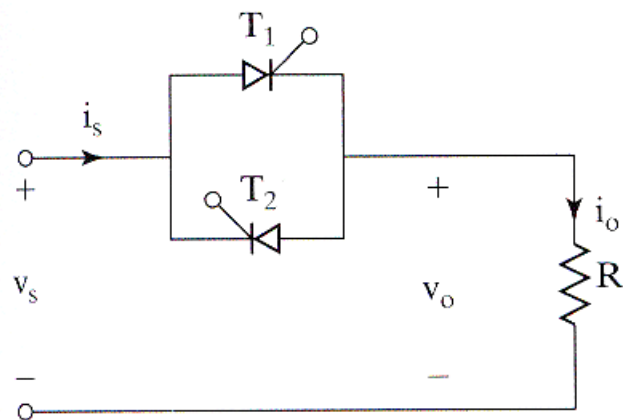


Duty cycle

$$k = \frac{nT}{(n+m)T} = \frac{n}{n+m}$$

$T$  – Line period

$(n+m)T$  – Control period

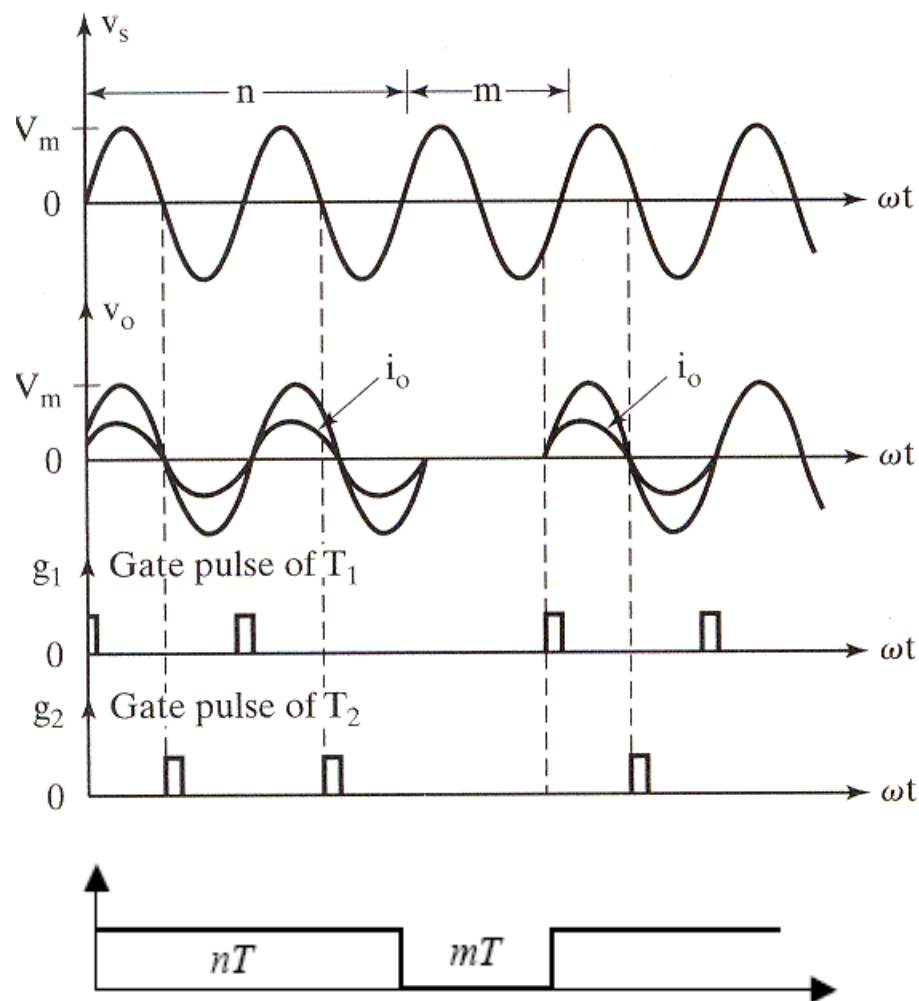


## 1.2.1 Basic On-off control

- The rms output voltage is

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \frac{n}{n+m} \int_0^{2\pi} 2V_s^2 \sin^2 \omega t d(\omega t)} = V_s \sqrt{\frac{n}{n+m}} = V_s \sqrt{k}$$

- The input power factor is
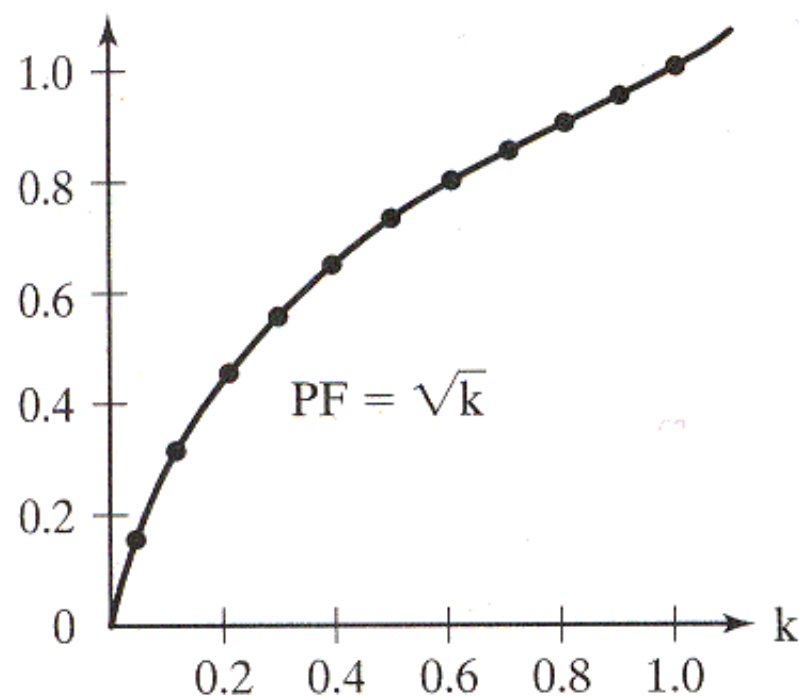
$$f_P = \frac{V_{RMS} I_{RMS}}{V_s I_s} = \frac{V_{RMS}}{V_s} = \sqrt{k}$$






## 1.2.2 Static switches

---

- The on-off control strategy can be easily extended to build static switches, which
  - Have very high switching speeds
  - Have no moving parts
  - Have no contacting bounce on closing


# 1.2.2 Single phase

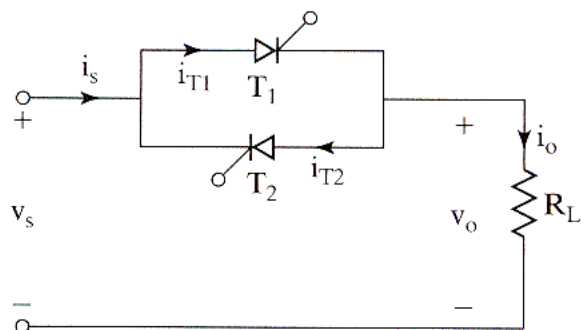

The switch reaction time:  
it can stop the current  
flow in every half-cycle  
(10ms for 50Hz supply).


**Resistive load:**

**zero-voltage/current crossing**

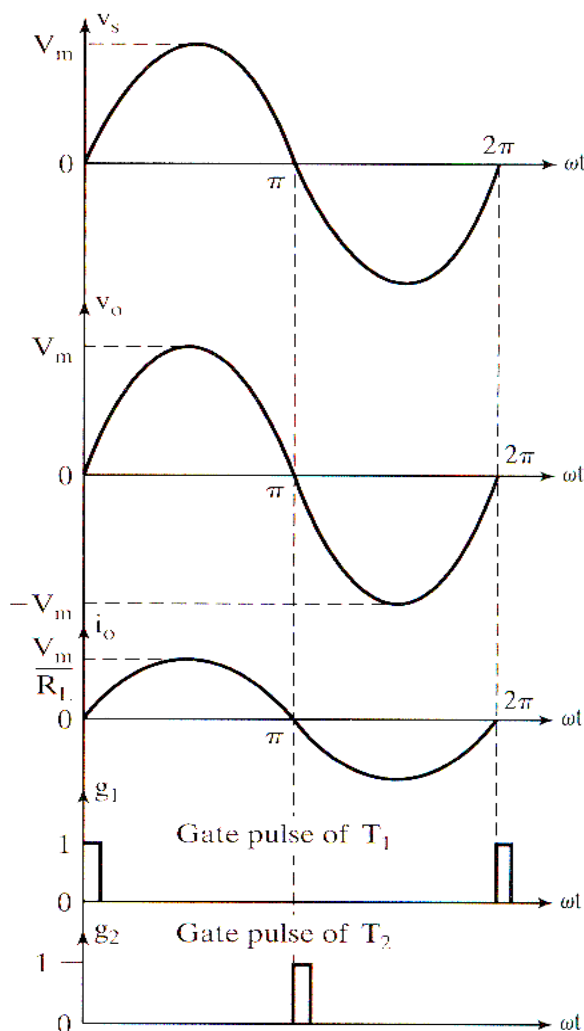



**Inductive load:**

**zero-current crossing**

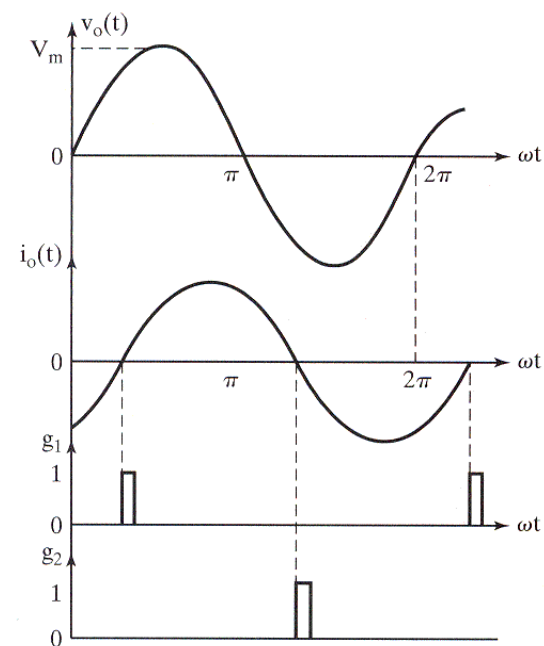

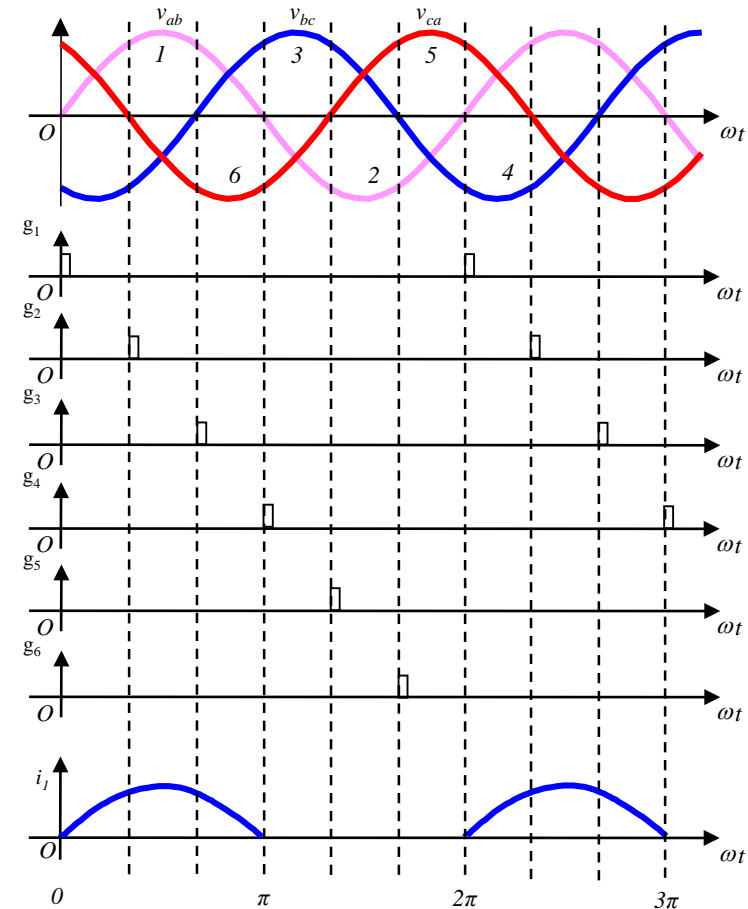
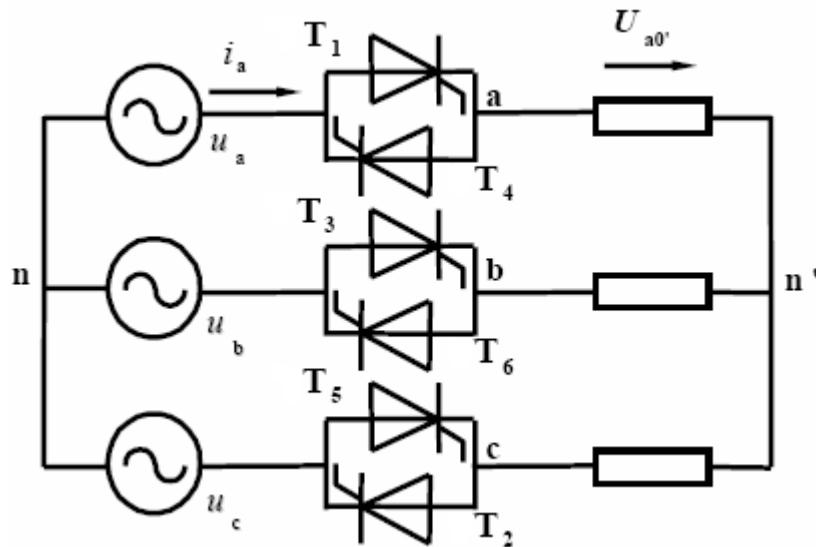
## 1.2.2 Three-phase switches

- The gating signals for thyristors are still at the current zero-crossing of each phase.
  - The switch speed: it can stop the current flow in every half-cycle (10ms for 50Hz supply).


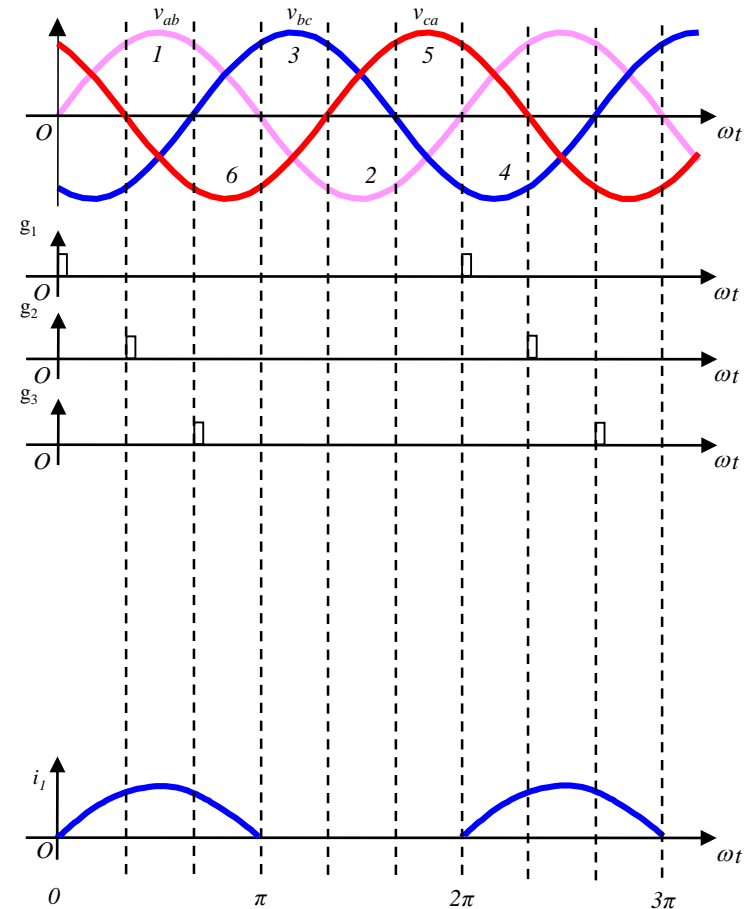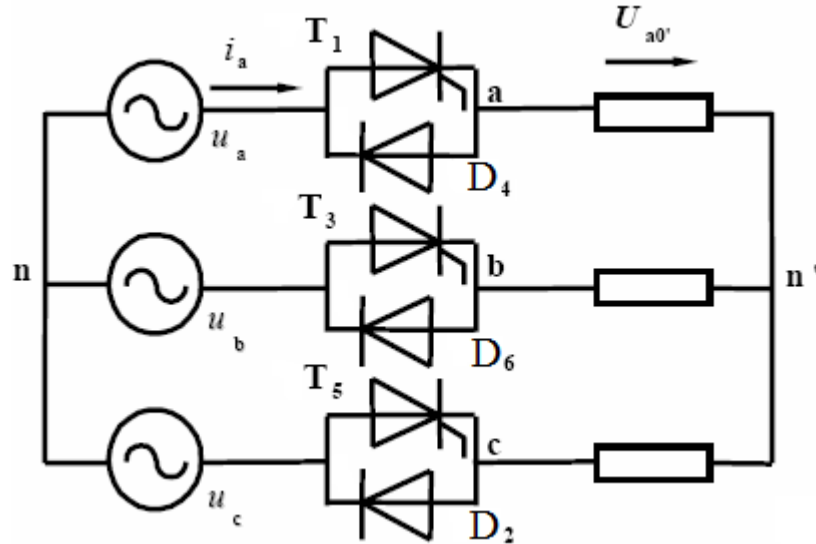
## 1.2.2 Three-phase switches


- A diode and a thyristor can also be used to form a three-phase switch.
  - The current flow can only be stopped in every whole cycle of input voltage, and the reaction time becomes slow (20ms for 50Hz supply.)




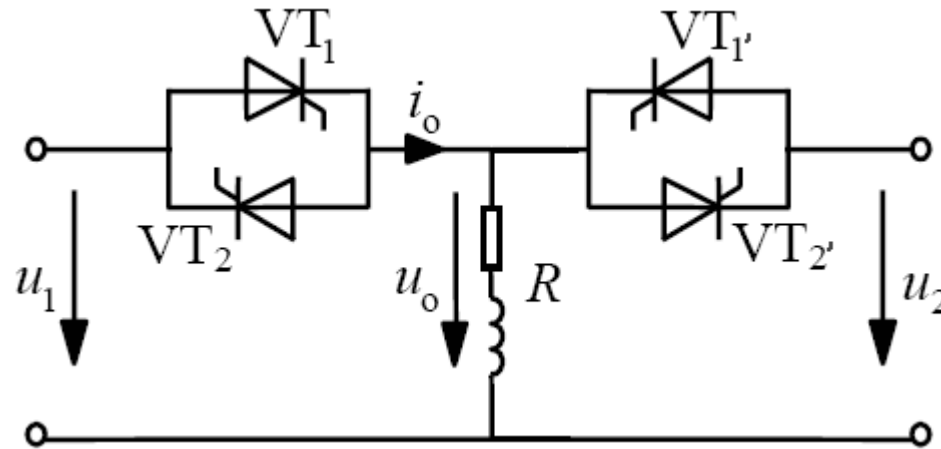
## 1.2.3 Bus Transfer

- The static switches can be used for bus transfer from one source to another.



# Cycloconverters (*private learning activity*)



---

- Thyristor AC to AC frequency converter
  - Another name—direct frequency converter (as compared to AC-DC-AC frequency converter)
    - Directly converting the input high frequency AC power to AC power with lower frequency
  - Can be classified into single-phase and three-phase according to the number of phases at output



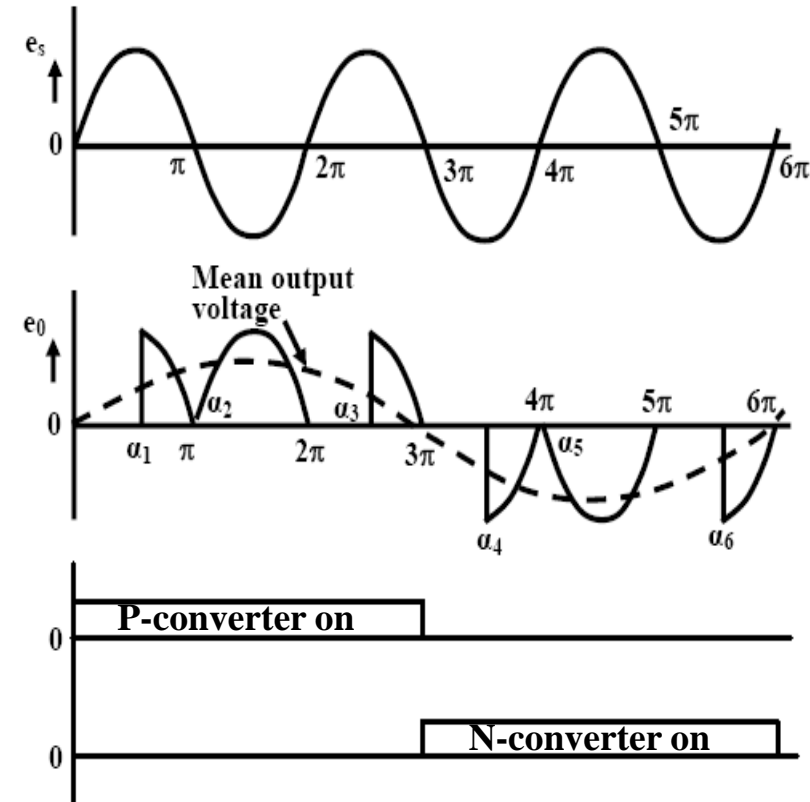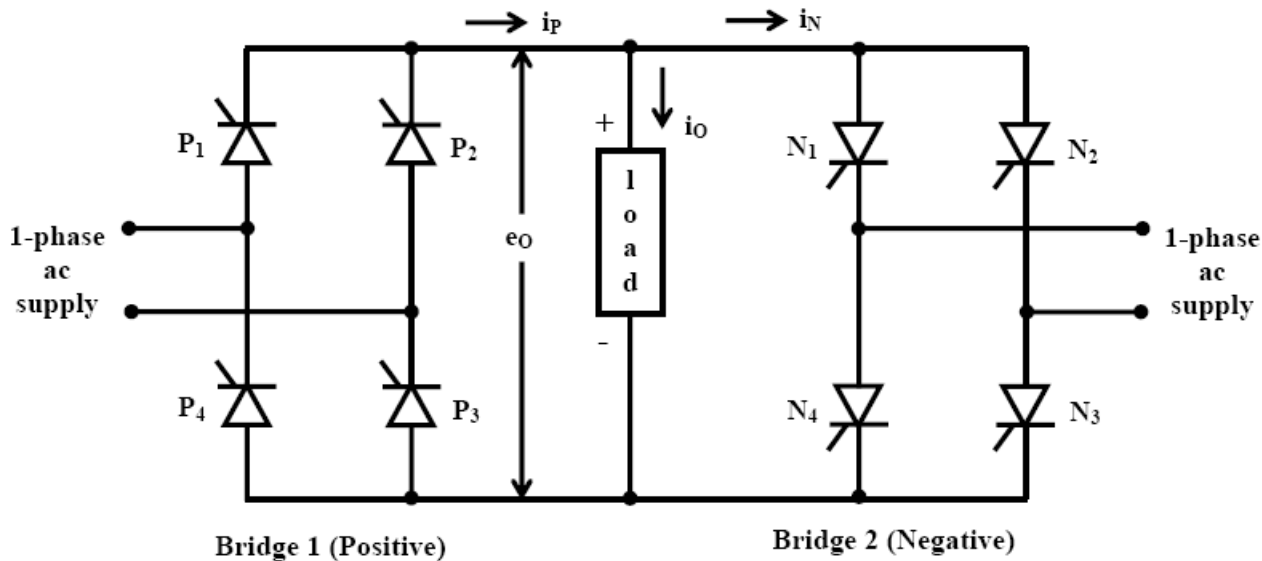
## 2.1 Single-phase to single-phase converter

- Circuit configuration and operation principle
- Resistive load


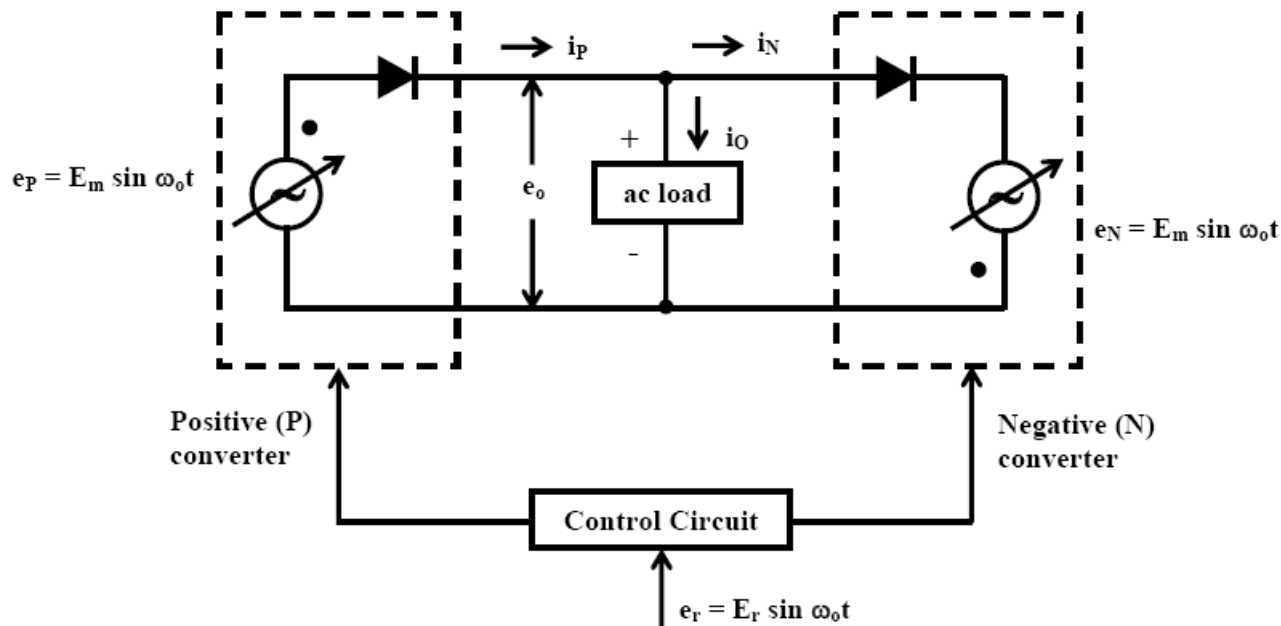
## 2.1 Single-phase to single-phase converter

- Equivalent circuit and triggering principle




$$f_s = 60\text{Hz}$$

$$f_o = f_s/3 = 20\text{Hz}$$

Ripple frequency:

$$f_R = 2f_s = 120\text{Hz}$$

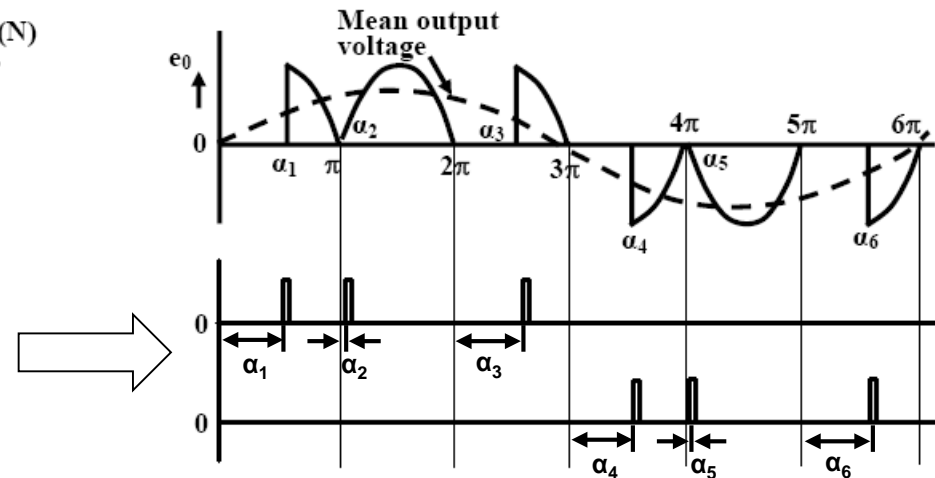*To make the output voltage close to sin wave, we trigger the delay angle according to sinusoidal pattern*






$$f_s = 60\text{Hz}$$

$$f_o = f_s/4 = 15\text{Hz}$$


Ripple frequency:

$$f_R = 2f_s = 120\text{Hz}$$

- Inductive loading

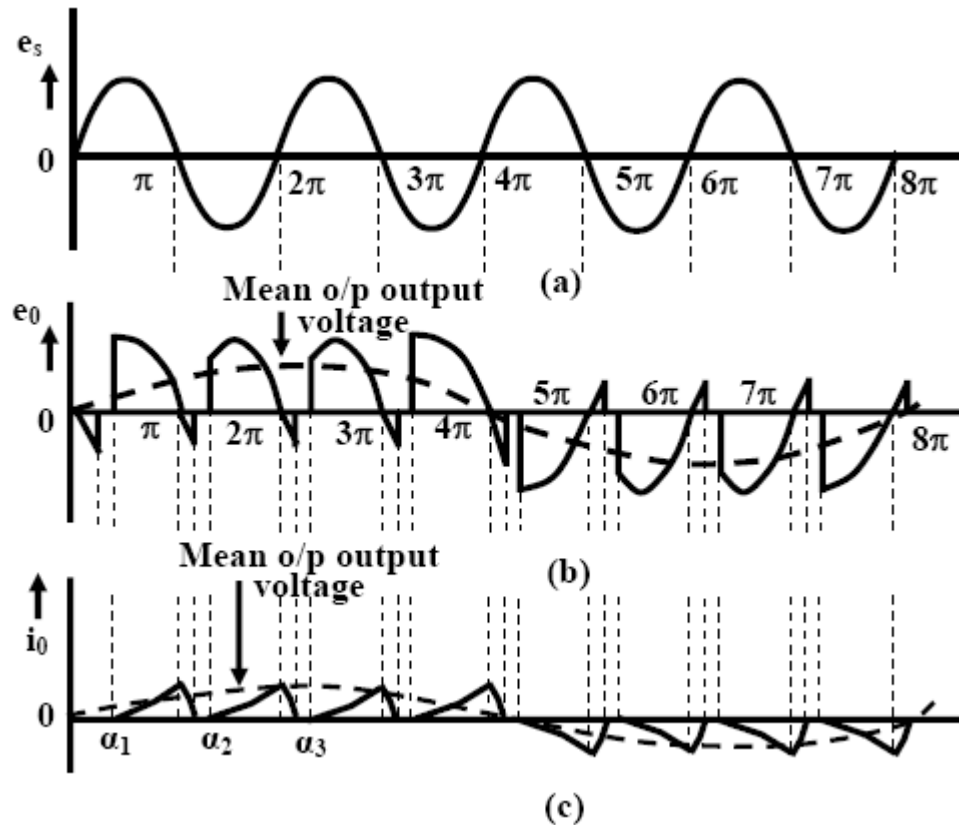

Small L

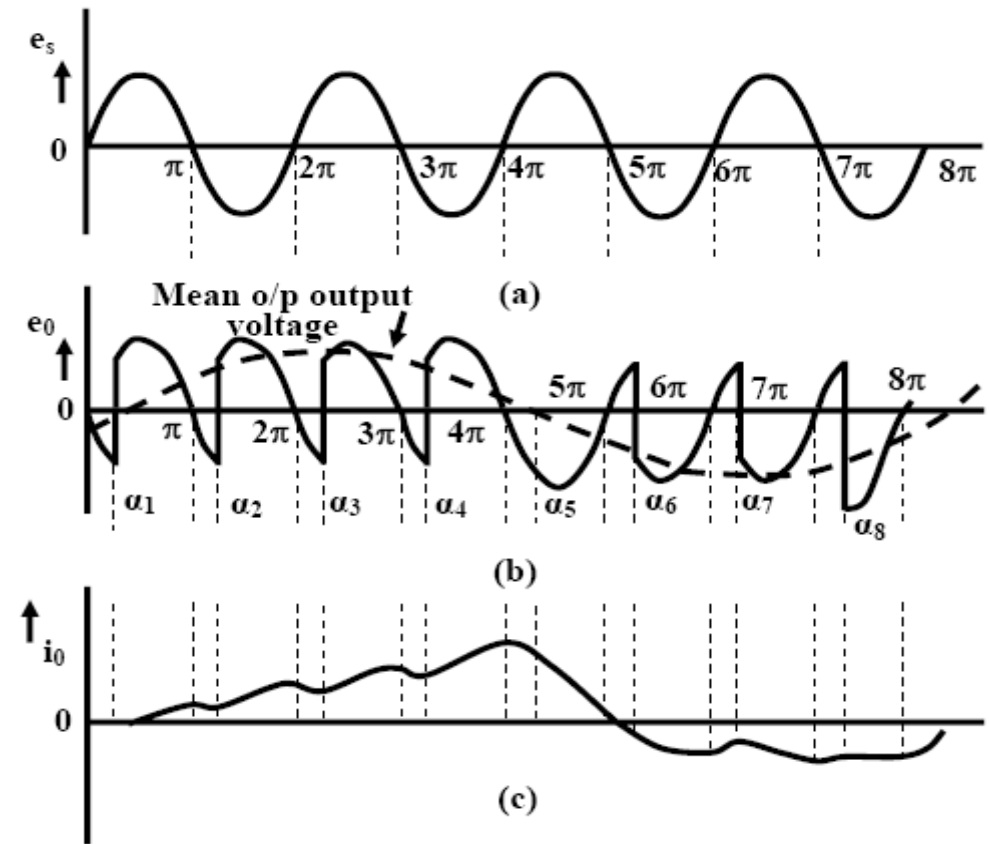


Large L



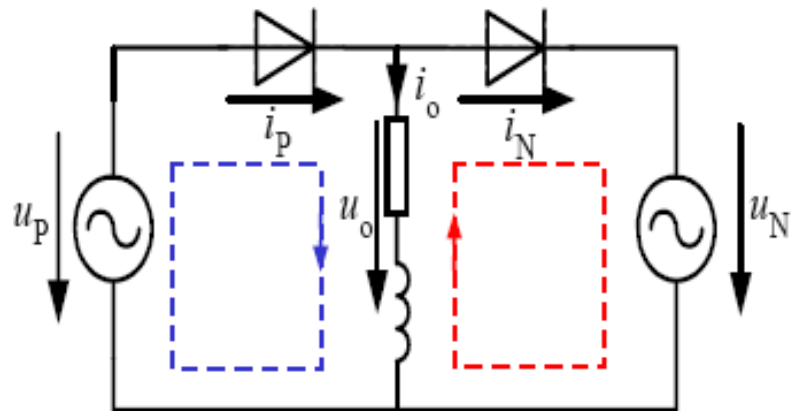
## 2.1 Single-phase to single-phase converter


- Operating modes
  - Rectification
  - Inversion
  - Blocking (Idle)



**R-load**

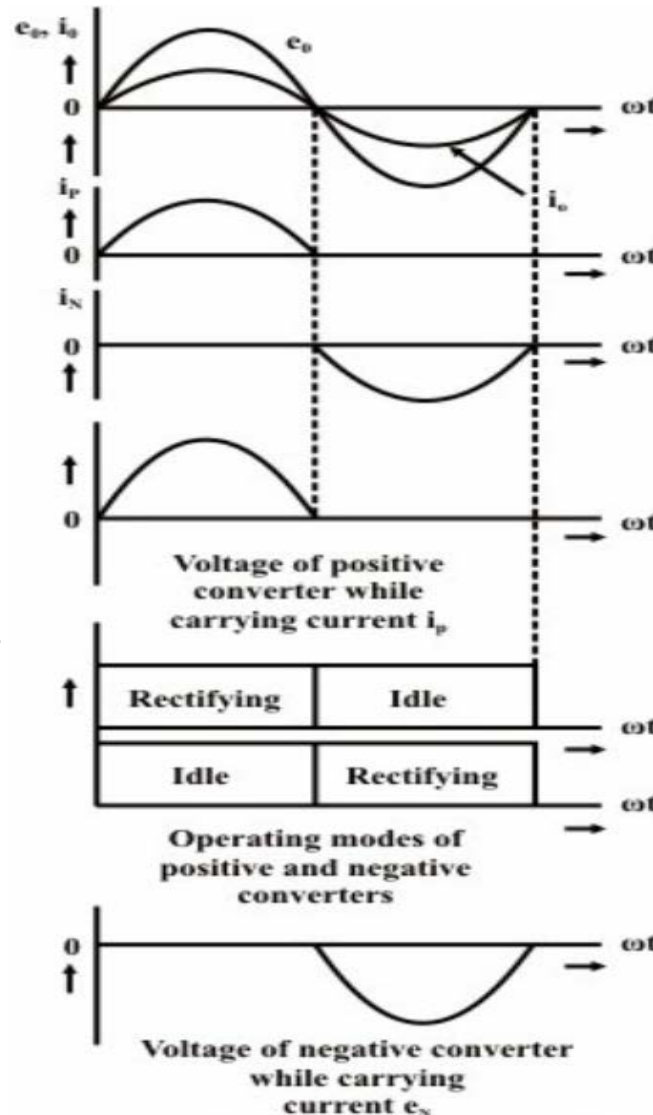


**RL-load**

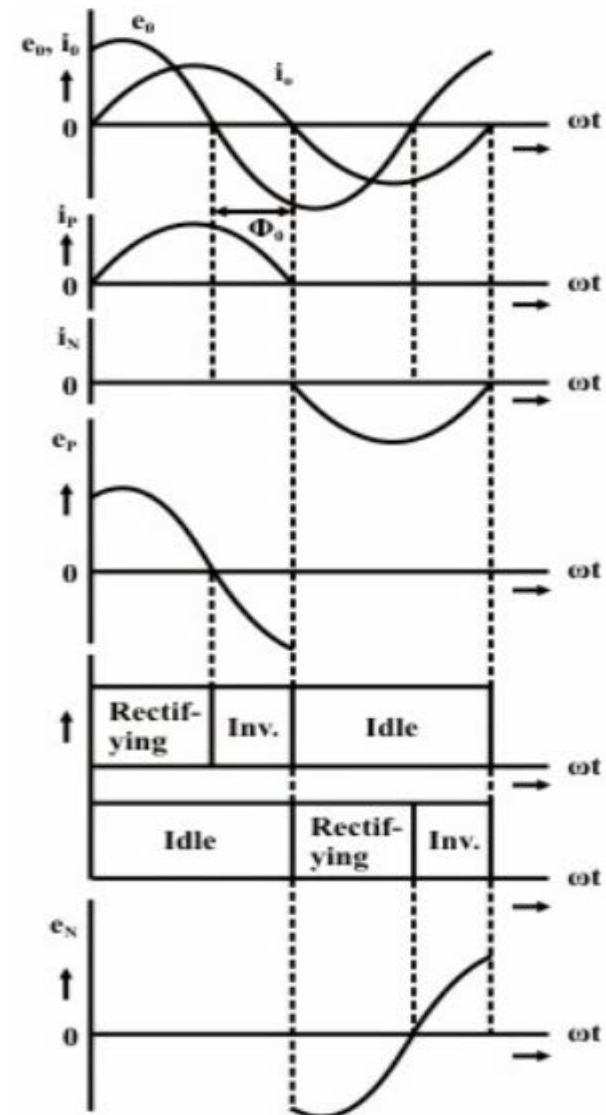
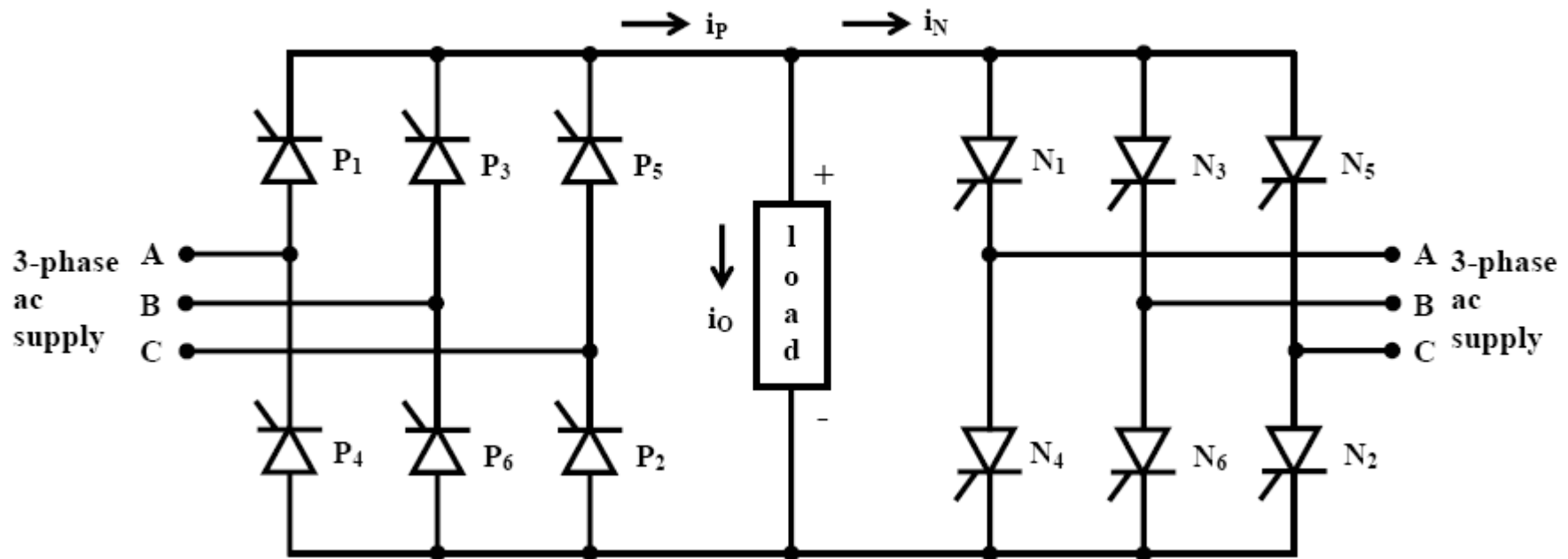
## 2.2 Three-phase to single-phase converter

- Circuit configuration and operation principle
  - Inductive load



## 2.2 Three-phase to single-phase converter


- Left-bridge: positive half
- Right-bridge: negative half

$$f_s = 60\text{Hz}$$

$$f_o = f_s/4 = 15\text{Hz}$$

Ripple frequency:

$$f_R = 6f_s = 360\text{Hz}$$

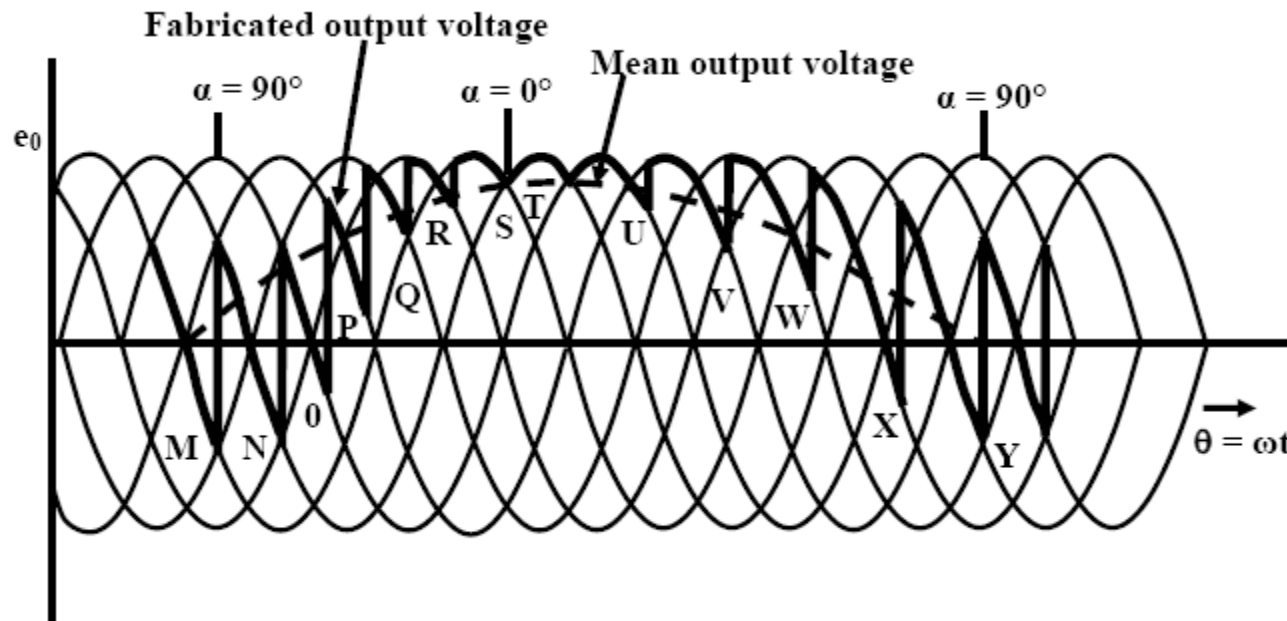

- More segments used  $\Rightarrow$  lower output frequency
- More segments used  $\Rightarrow$  closer to sinusoidal wave


- Typical waveforms of output voltage and current

$$f_s = 60\text{Hz}$$

$$f_o = f_s/5 = 12\text{Hz}$$

Ripple frequency:

$$f_R = 6f_s = 360\text{Hz}$$

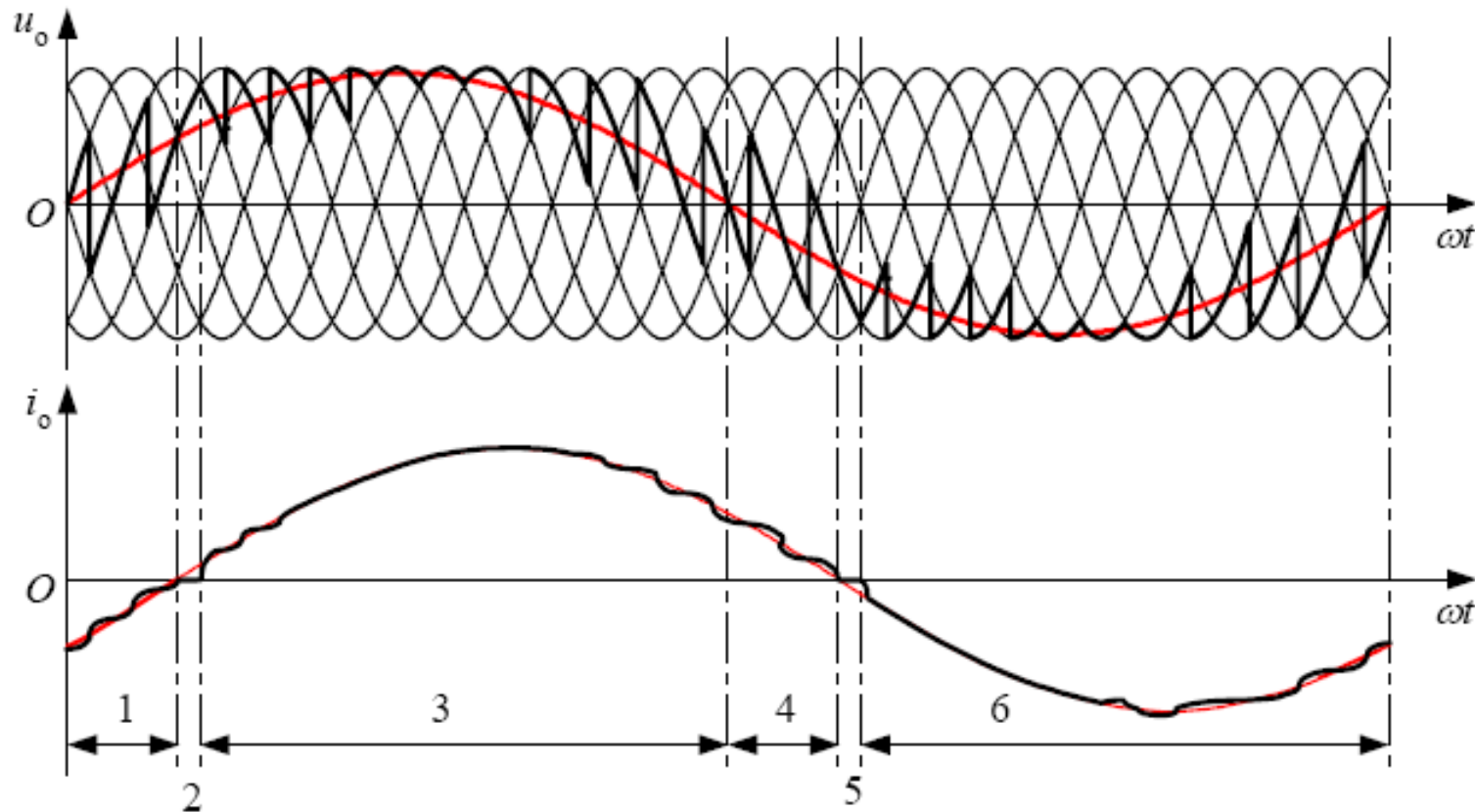


- 
- The maximum output frequency is limited to a value that is only a fraction of the source frequency.
  - As a result the major applications of cycloconverters are low-speed, ac motor drives ranging up to 15,000 kW with frequencies from 0 to 20Hz.
  - Cycloconverter can deliver a high quality sinusoidal waveform at low output frequencies, since it is fabricated from a large number of segments of the supply waveform. This is often preferable for very low speed applications.



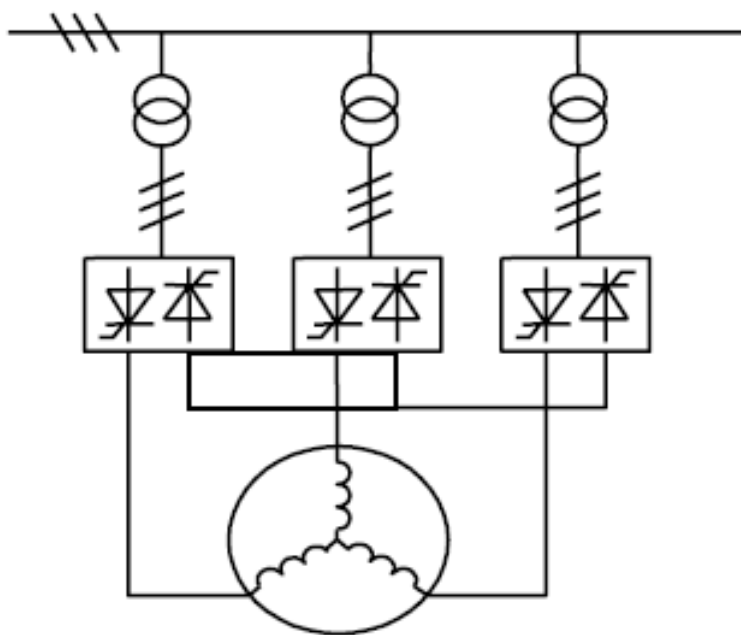
## 2.3 Three-phase to three-phase converter

- The configuration with star-connected output




(a) simplified

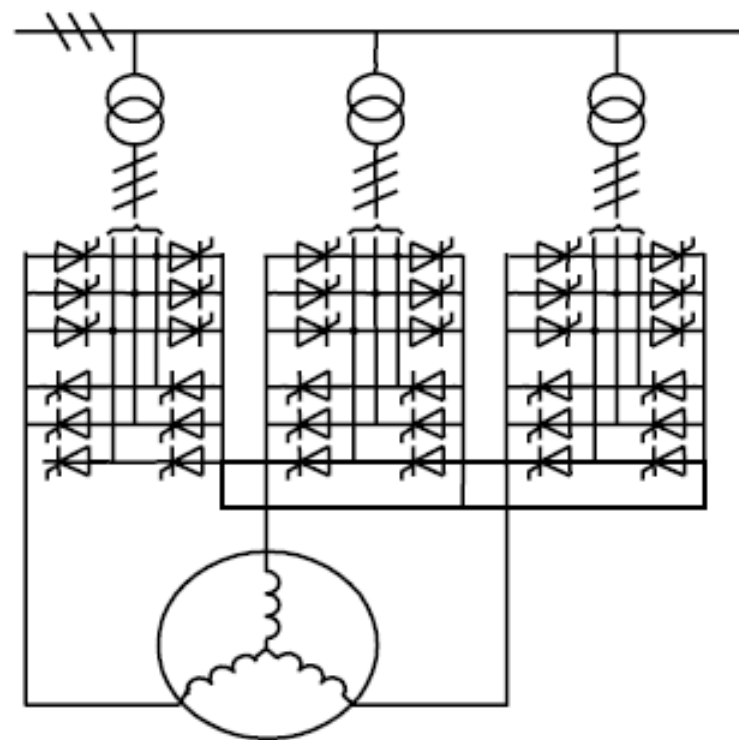

(b) detailed
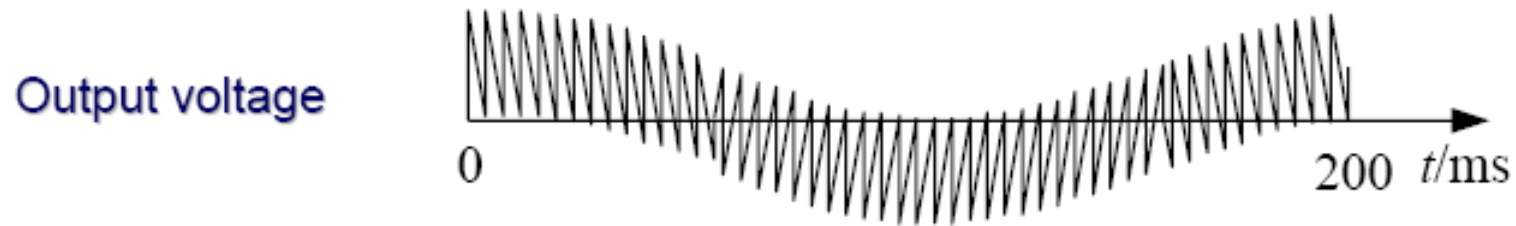
## 2.3 Three-phase to three-phase converter

- Typical waveforms of output voltage and current



- The maximum output frequency and the harmonics in the output voltage are the same as in single phase circuit.
- Input power factor is a little higher than single phase circuit.
- Harmonics in the input current is a little lower than the single-phase circuit due to the cancellation of some harmonics among the 3 phases.