

EEE205 – Digital Electronics (II)

Lecture 17

DAC and ADC


Dr. Ming Xu

Dept of Electrical & Electronic Engineering
XJTLU

1

Interfacing With the Analog World

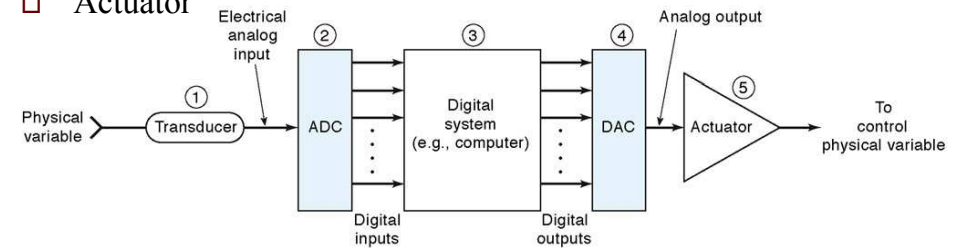
- Transducer
- ADC
- Computer
- DAC
- Actuator



2

Digital to Analog Conversion

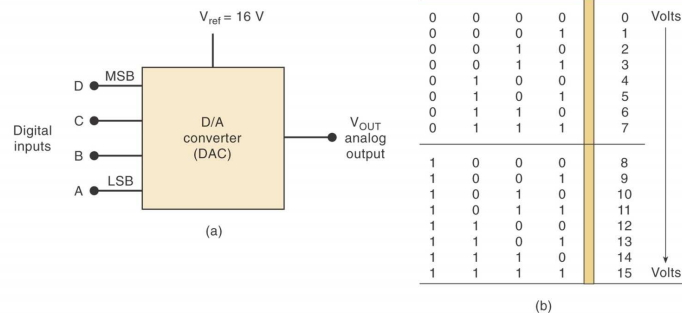
- The conversion process:
 - Digital code is converted to a proportional voltage/current
 - Reference voltage determines the max DAC output
- Analog (pseudo analog) output



3

Digital to Analog Conversion

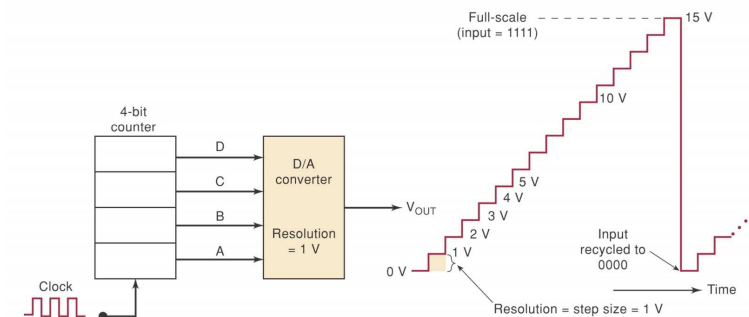- Resolution (step size) = analog full-scale output divided by $2^n - 1$, where n is the number of bits.
- Analog output = resolution × digital input



4


Digital to Analog Conversion

- Bipolar DACs
 - Many DACs produce both positive and negative values
 - 2's complement can be used to represent negative voltages

5

D/A Converter Circuitry

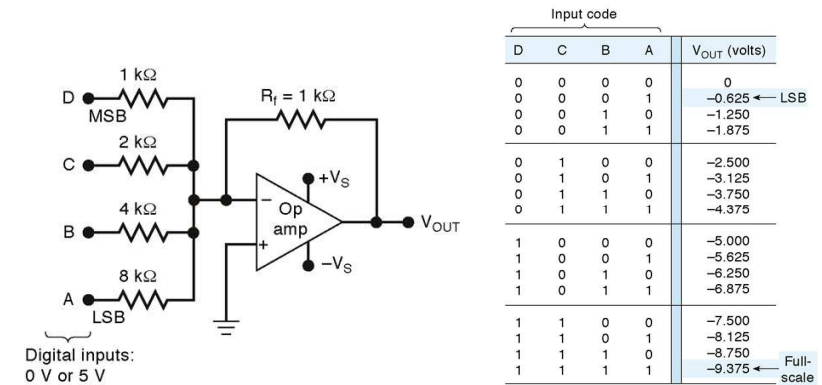
- A summing operational amplifier with a resolution of .625 V. $V_{OUT} = -(V_D + V_C/2 + V_B/4 + V_A/8)$



6

D/A Converter Circuitry

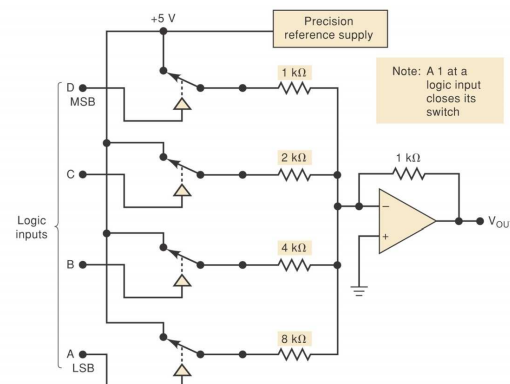- The digital inputs cannot be taken directly from FFs or logic gates
- Each digital input controls a semi-conductor switch to a precision reference supply.



7


D/A Converter Circuitry

- R/2R ladder
 - Circuits with binary weighted resistors cause a problem due to the large difference in R values between LSB and MSB
 - The R/2R ladder uses resistances that span only a 2 to 1 range

8

D/A Converter Circuitry

□ R/2R ladder DAC

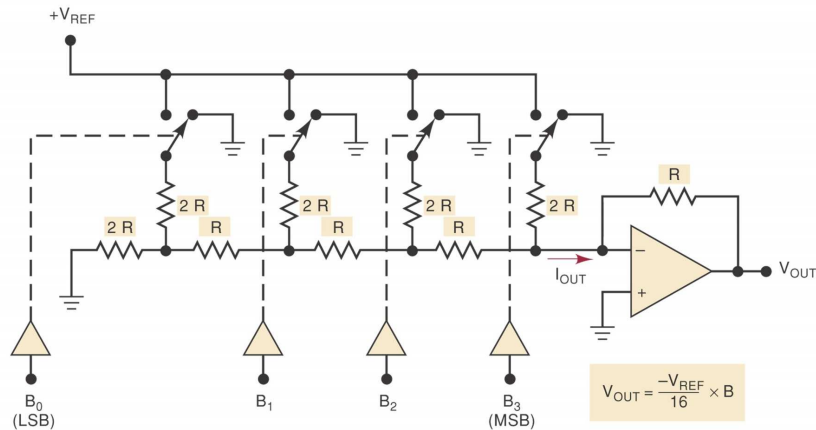

9

DAC Specifications

□ Many DACs are available as ICs or self contained packages. Key specifications are:

- Resolution
- Accuracy
- Offset error
- Settling time
- Monotonicity

10


Analog to digital Conversion

- ADC – digital code represents the analog input
- Generally more complex and time consuming than DAC
- Several types of ADC use DAC circuits
- The Op amp comparator ADC
 - Variations differ in how the control section continually modifies numbers in the register

11

Digital Ramp ADC

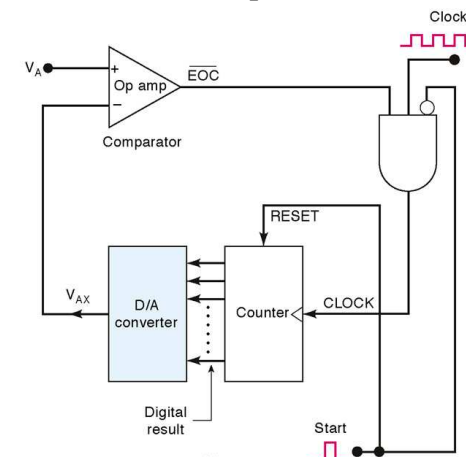
- A binary counter is used as the register and allows clock to increment the counter a step at a time until $V_{AX} \geq V_A$



12

Digital Ramp ADC

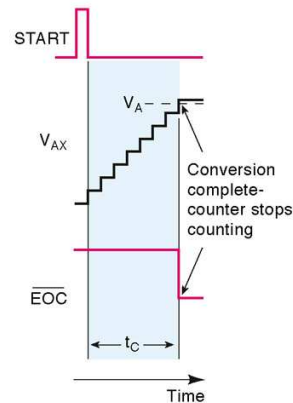
- A/D resolution and accuracy
 - Measurement error is unavoidable
 - Reducing the step size can reduce but not eliminate potential error
 - This is called quantization error



13

Data Acquisition

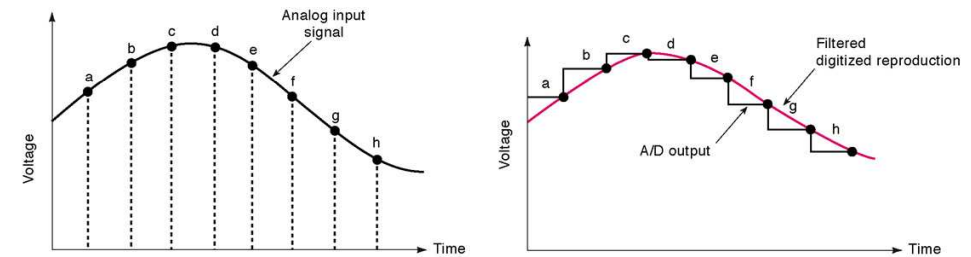
- Digitizing analog data and transferring to memory is data acquisition
- Acquiring a single data point value is sampling
- Reconstructing a digitized signal



14

Data Acquisition

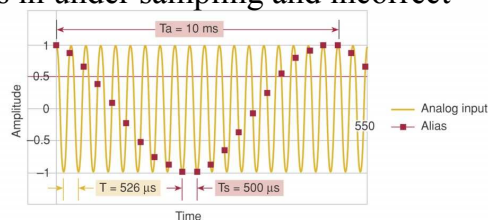- Aliasing
 - Caused by under sampling
 - Harry Nyquist
 - The sampling frequency must be at least twice the highest input frequency
 - Sampling at a frequency less than twice the input frequency results in under sampling and incorrect reproduction




15

Successive Approximation ADC

- Widely used ADC
- More complex than digital ramp but has a shorter conversion time
- Conversion time is fixed and not dependent on the analog input
- Many SACs are available as ICs.

16

Successive Approximation ADC

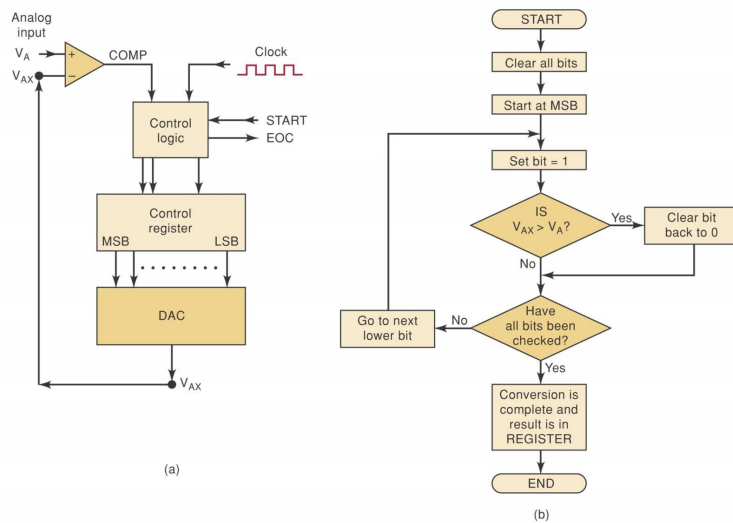


17

Flash ADCs

- High speed conversion
- Much more complex circuitry
 - 6 bit flash ADC requires 63 analog comparators
 - 8 bit flash ADC requires 255 comparators
 - 10 bit flash ADC requires 1023 comparators
- A 3 bit flash converter is described in figure 11-22
- Conversion time – No clock signal is used, so the conversion is continuous. This makes for very short conversion times, typically under 17 ns.

18

Flash ADCs

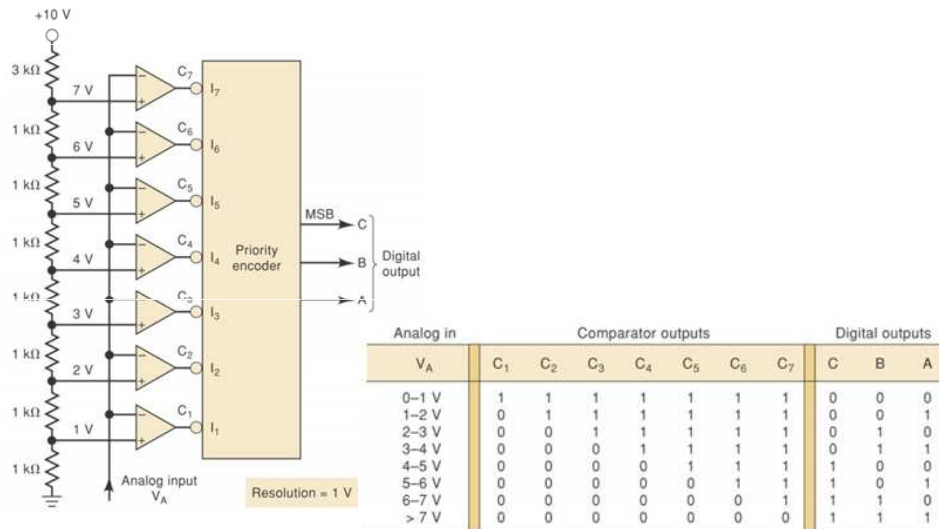

20

Other A/D Conversion Methods

- There are many other methods of A/D conversion. Each has pros and cons:
 - Up/down digital-ramp ADC (tracking ADC)
 - Dual slope integrating ADC
 - Voltage to frequency ADC
 - Sigma/delta modulation
- The method used will depend on the application