
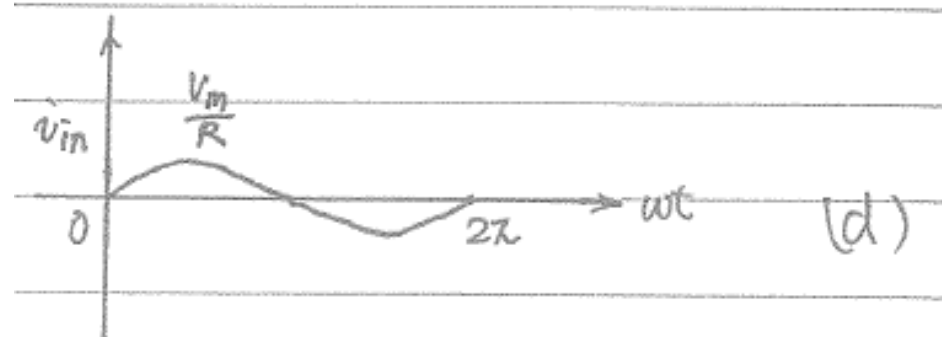
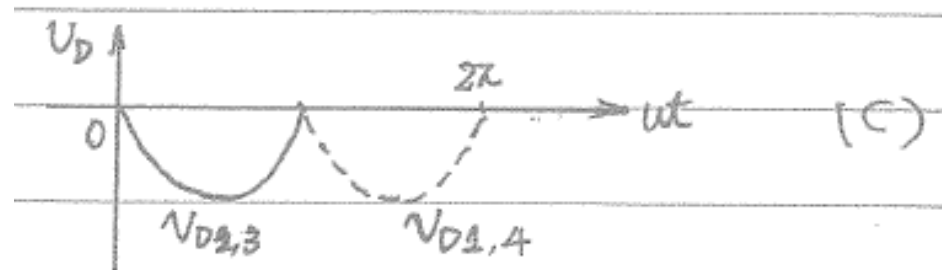
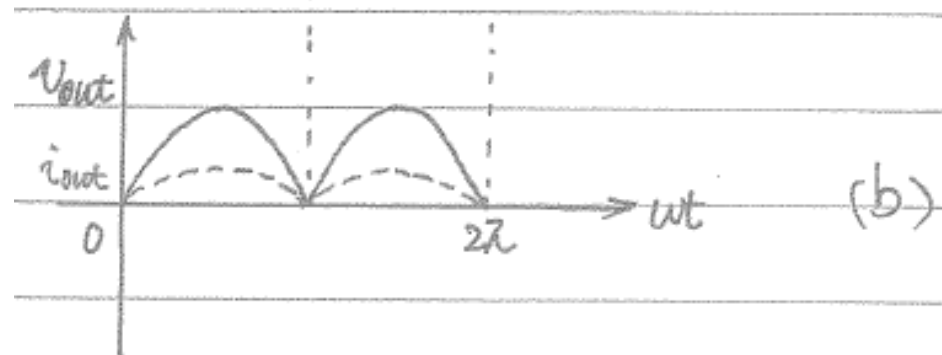


EEE213 Power Electronics and Electromechanism

Tutorial 1






Problem 2.1

- A single-phase bridge rectifier is required to supply an average voltage of 110V to a resistive load $R=10\ \Omega$. The main supply is 220V RMS. Determine
 - 1) The rms value of the input voltage for the rectifier and then the turns ratio of the transformer;
 - 2) The voltage and current ratings of the diodes;
 - 3) The power rating of the transformer;
 - 4) The power consumed by the load;
 - 5) The THD of the line current.

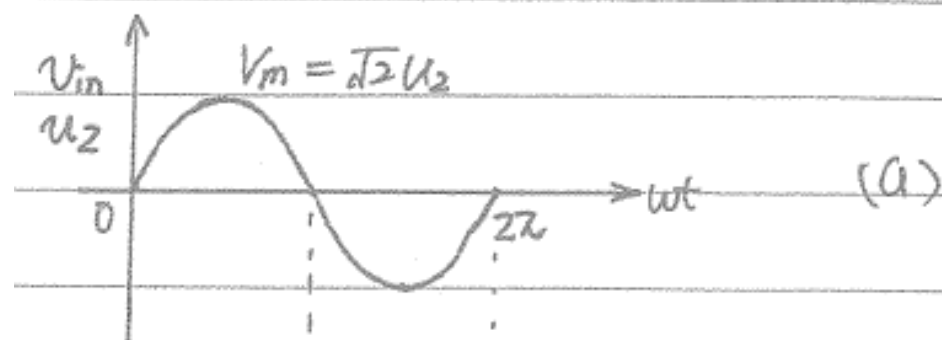

Problem 2.2

- A battery charger is supplied by a single-phase bridge rectifier. The battery voltage is $E=20\text{V}$ and the capacity is 10Ah . The current-limiting resistor is 10Ω . The input voltage is 30V RMS . Draw the waveforms and then calculate
 - 1) The conduction angle of a diode;
 - 2) The average charging current;
 - 3) The charging time;
 - 4) The power dissipated on R ;
 - 5) The peak reverse voltage across a diode.

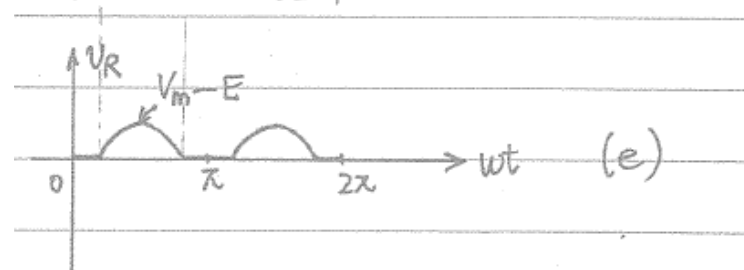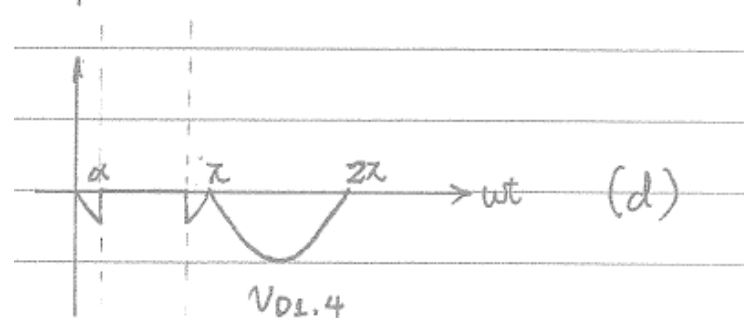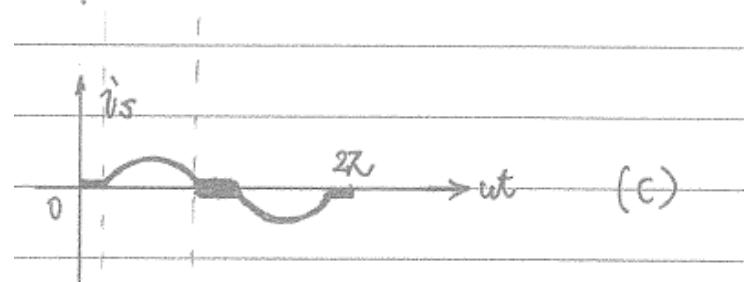
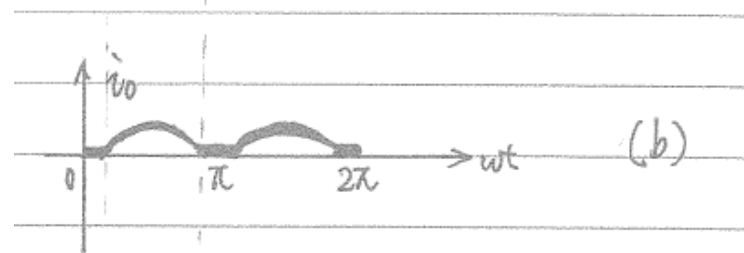
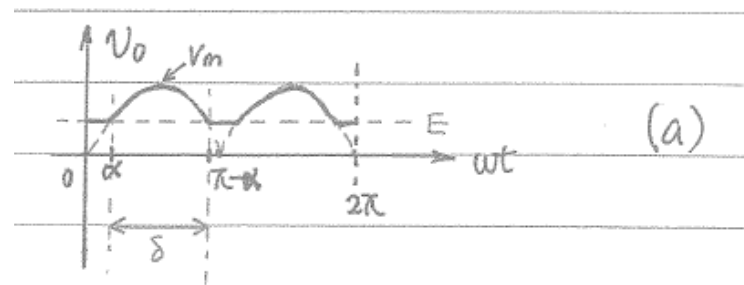


Problem 3.1

- A three-phase bridge rectifier supplies a ripple-free current $I_0=10\text{A}$ and an average voltage $V_0=110\text{V}$ to the load.


Assume $v_A=V_m\sin\omega t$.

- 1) Determine the rms value of the phase voltage;
- 2) Draw the current and voltage waveforms for D1, D3, D5;
- 3) Draw the current waveform for phase A and determine the rms value;
- 4) Determine the diode ratings.

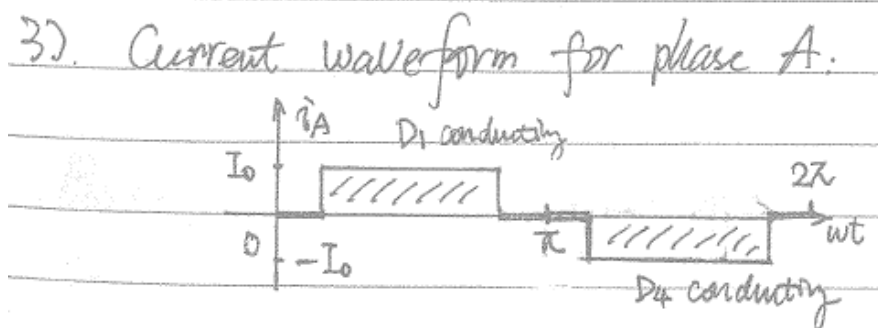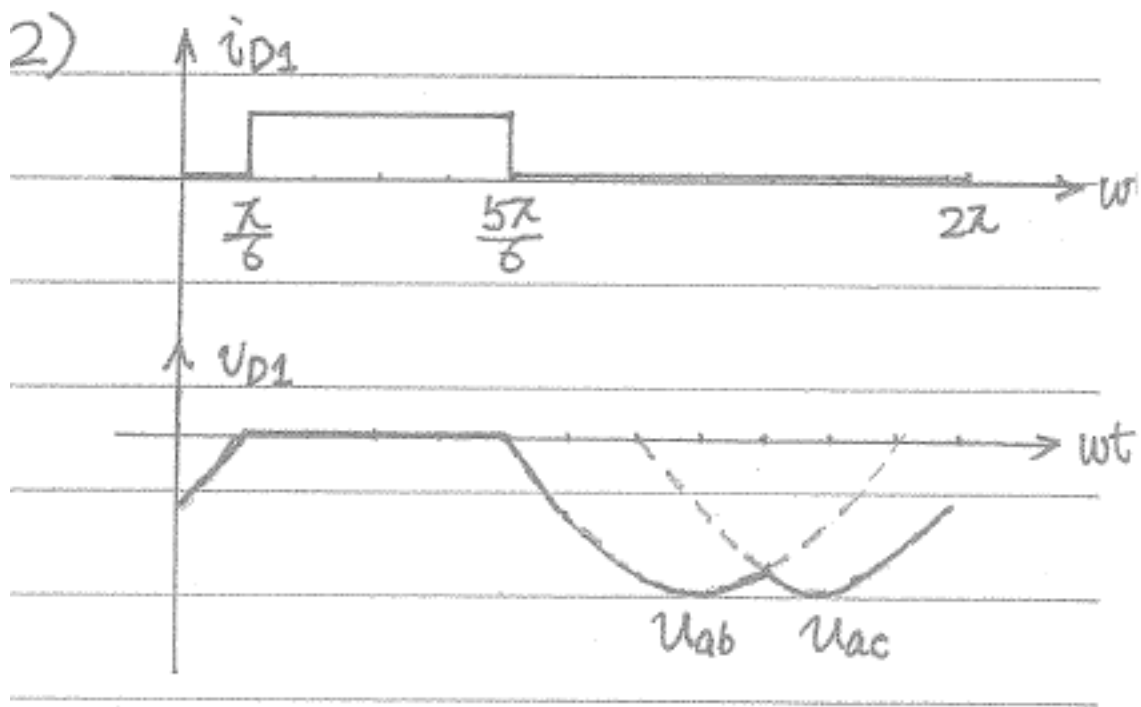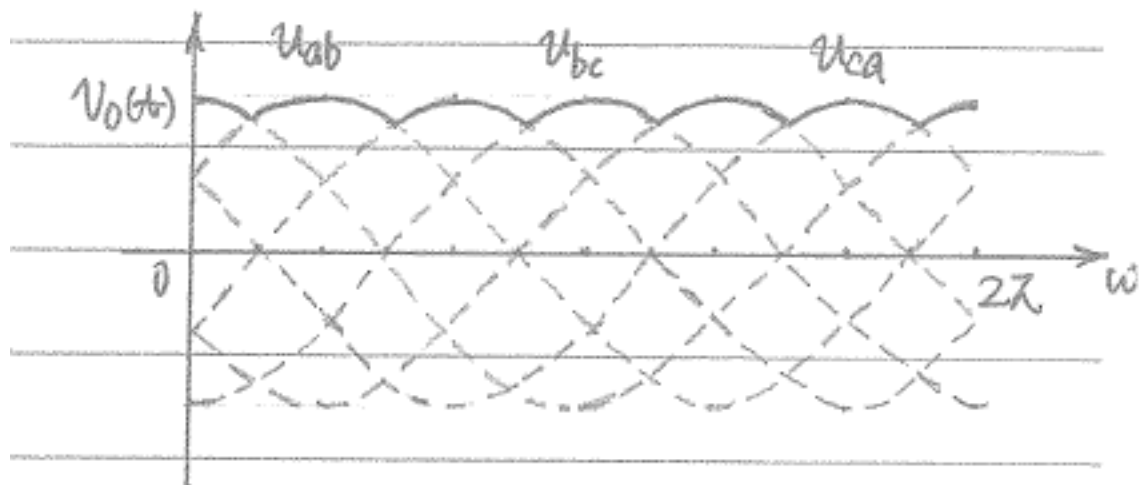

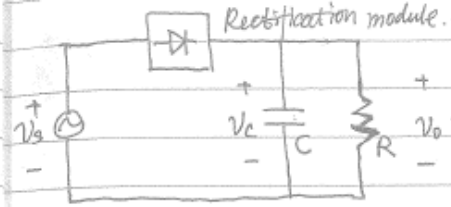Problem 3.2


- The single phase bridge rectifier is supplied from a 120V, 60Hz source. The load resistance is $R=500\Omega$.
 - a) Design a capacitive filter so that the ripple factor of the output voltage is less than 5%;
 - b) With the value of capacitor C in part a), calculate the average load voltage V_{dc} .



Single phase, bridge, rectification.

$$V_s = 120V, f = 60Hz.$$

$$R = 500\Omega.$$

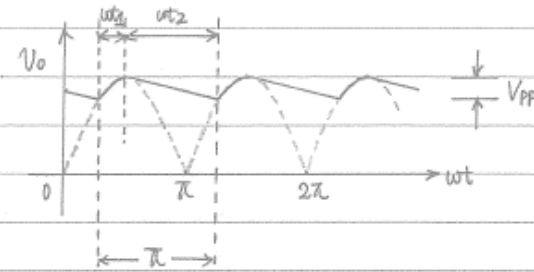

First, analyse the discharge procedure.

$$t_1 \rightarrow t_1 + t_2$$

$$\frac{1}{C} \int i_o(t) dt + V_c(t_1) + R i_o(t) = 0$$

$$\Rightarrow i_o(t) = \frac{V_c(t_1)}{R} e^{-\frac{t-t_1}{RC}}$$

$$* t_1 + t_2 = T/2.$$

$$\omega t_1 + \omega t_2 = \pi.$$

$$V_c(t_1) = V_m, \text{ the peak voltage.}$$

$$\Rightarrow V_o(t) = i_o(t) \cdot R$$

$$= V_m e^{-\frac{t-t_1}{RC}} \quad (\Delta t = t - t_1)$$

The peak-to-peak ripple is

$$V_{pp} = V_o(t_1) - V_o(t_1 + t_2)$$

$$= V_m (1 - e^{-\frac{t_2}{RC}})$$

Based on the power series of e^{-x}

$$e^{-x} \approx 1 - x$$

$$\Rightarrow V_{pp} \approx V_m \cdot \frac{t_2}{RC}$$

Assume the capacitor is large enough, then $t_1 \rightarrow 0, t_2 \rightarrow T/2$.

$$\text{So } V_{pp} \approx V_m \cdot \frac{T/2}{RC} = \frac{V_m}{2fRC}$$

$$V_{dc} = V_m - \frac{V_{pp}}{2}$$

$$V_{ac} \approx \frac{1}{\sqrt{2}} V_{pp}$$

$$\Rightarrow f_R = \frac{V_{ac}}{V_{dc}} = \frac{\frac{1}{\sqrt{2}} \cdot \frac{V_m}{2fRC}}{(4fRC - 1) \cdot \frac{V_m}{2fRC}} = 5$$

$$\Rightarrow C = 126.2 \mu F.$$

2). With $C = 126.2 \mu F$.

$$V_{dc} = V_m (1 - \frac{1}{4fRC})$$

$$= 158.5V.$$

