

Lecture 4
of
EEE307

Electronics for Communications

Department of Electrical & Electronic Engineering
Xi'an Jiaotong-Liverpool University (XJTLU)

Friday, 27th September 2019


- ❑ LNA in Wireless Receiver
- ❑ Transistor Amplifiers
 - fundamental configurations
- ❑ Equivalent Circuit at RF
 - transistor parasitic circuit elements



Receiver in Communication

(amplification of weak RF signals)

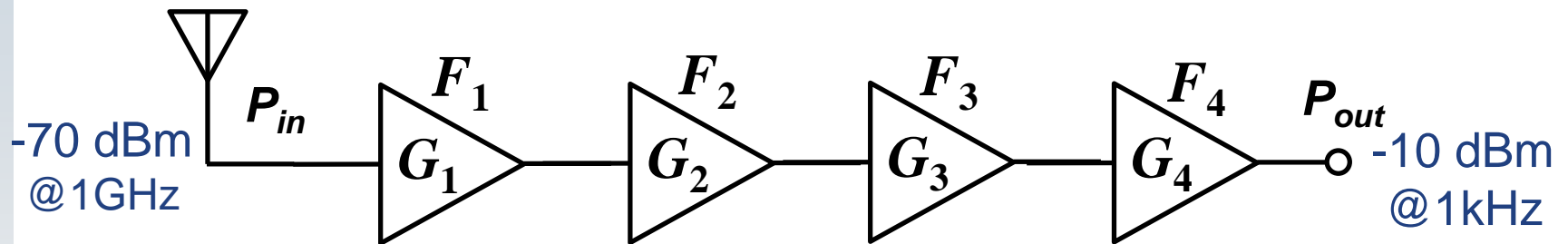- ❑ In the receiver of a wireless communication system, very weak RF signals are received from the antenna and then amplified and filtered subsequently.



- F_1 is the **noise factor** of the first-stage amplification with a signal gain G_1 so on and so forth.
- The RF signals are typically down-converted from the **carrier frequency** to the **baseband**.



Xi'an Jiaotong-Liverpool University
西交利物浦大學

Amplifying Received RF Signals

(noise factor & noise figure)

- The front-end amplification has a dominant impact on the receiver's performance, especially in terms of the sensitivity.

$$F_{overall} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \frac{F_4 - 1}{G_1 G_2 G_3} \dots$$

$$F_{noise} = \frac{SNR_{in}}{SNR_{out}} \quad SNR = \frac{P_{signal}}{P_{noise}} \quad NF = 10 \log_{10} \left(\frac{SNR_{in}}{SNR_{out}} \right)$$

- Since an amplification circuit always adds noise to the input signal, the input **signal-to-noise ratio (SNR)** is always larger than the output SNR. $\Rightarrow F > 1$ & $NF > 0$ dB

- NF: noise figure (noise factor in dB)




Xi'an Jiaotong-Liverpool University

西交利物浦大学

Low-Noise Amplifier

(first stage amplification in receiver)

- ❑ With its dominant impact on the overall noise performance (hence the sensitivity) of the whole receiver circuit, the first-stage amplification therefore needs to have a very low **noise factor** F_1 and also preferably a high signal gain G_1 .
- ❑ Such an amplifier in a radio receiver is called the **low-noise amplifier (LNA)**.
 - A typical LNA has a **noise figure** of less than 2 dB and a signal gain of about 15-20 dB.

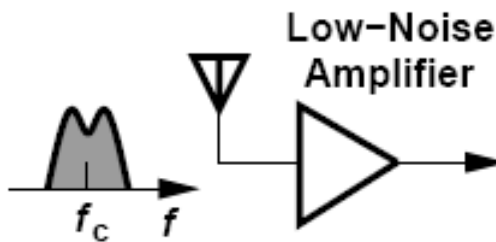

From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.

Low-Noise Amplifier

(design consideration)

- ❑ To design and construct an LNA, there are other considerations apart from the **noise factor** and **signal gain**.
 - input matching, output matching, gain stability, non-linearity (measured by the input or output **IP3**)
- ❑ In this module, only basic analysis of LNA circuits will be taught for essential understanding.
 - Interested students can refer to the recommended textbooks and papers for detailed theoretical analysis and design considerations.

Low-Noise Amplifier

(from basic transistor amplifiers)

- Regardless of the apparent variety of circuit configurations for the LNA, they can be viewed as just different combinations of the fundamental transistor amplifiers:
 - Using the MOS transistors, the three fundamental transistor amplifiers are the common-source (CS), common-gate (CG) and common-drain (CD) configurations.
 - In the bipolar junction transistor (BJT) case, the counterparts are the common-emitter (CE), common-base (CB) and common-collector (CC) configurations.




Transistor Amplifiers

(fundamental configurations)

- ❑ An LNA is a key building block of an electronic communication system. An LNA circuit itself is constructed from building-block transistor circuits.

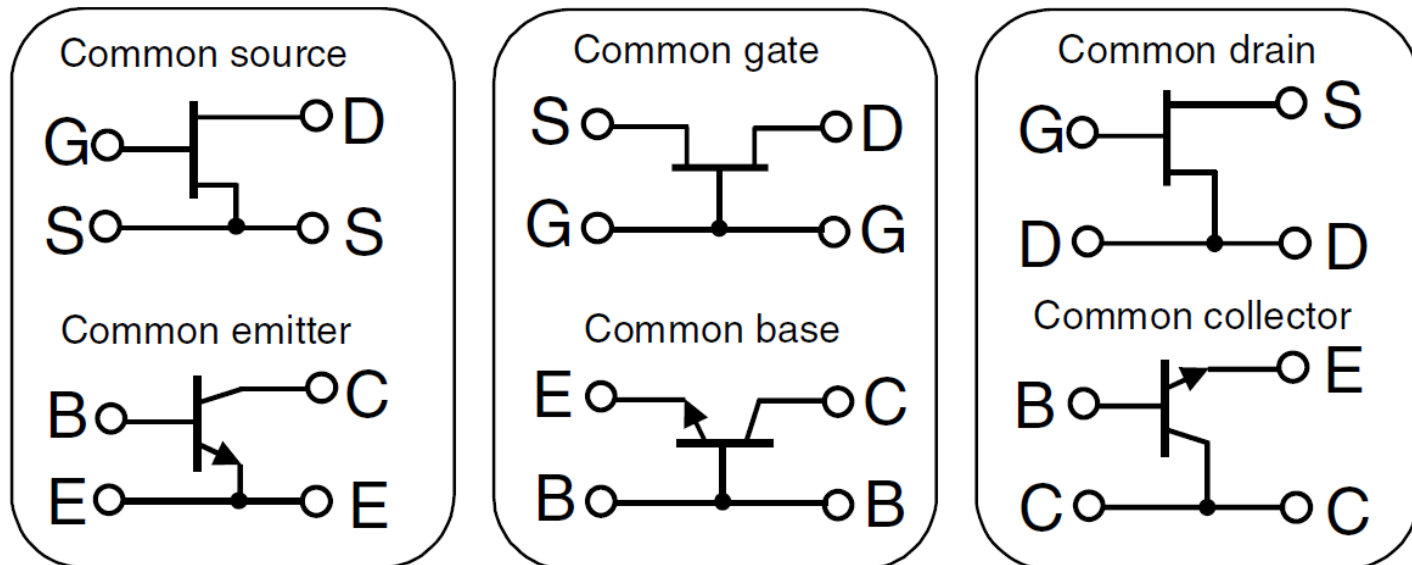From: Frank Ellinger, *Radio Frequency Integrated Circuits and Technologies*, © 2007 Springer, Germany.




- Starts from basics in engineering.

Transistor Amplifiers

(common-source configuration)

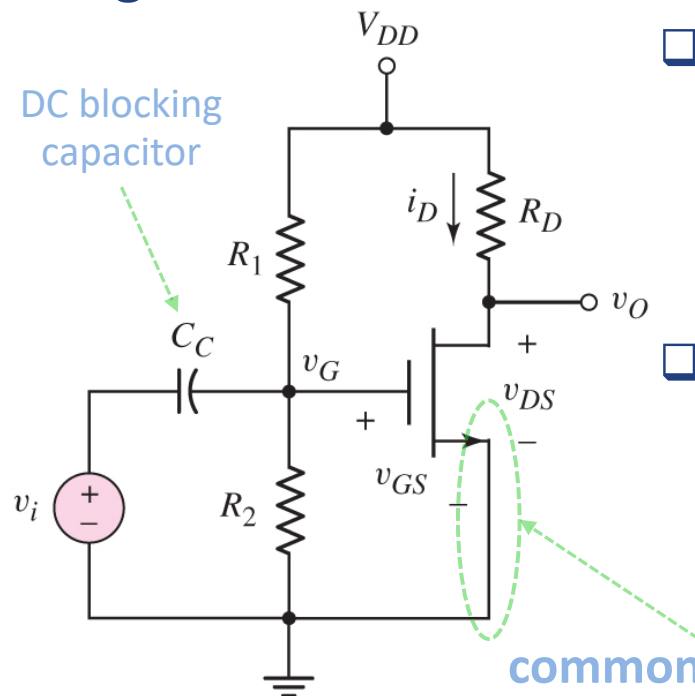- A basic **common-source (CS) amplifier** can be formed by configuring a single MOSFET with the source terminal as the common signal ground for both the input and output signals.



- For small signals, the MOSFET converts the input voltage variations to proportional drain current changes.
- Then the resistor R_D at the drain terminal transforms the drain currents to the output voltage (according to Ohm's law).





Xi'an Jiaotong-Liverpool University
西交利物浦大學

Transistor Amplifiers

(multi-stage amplifiers)

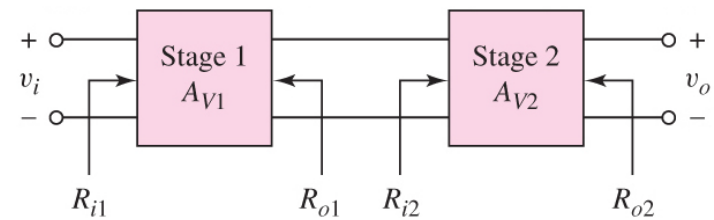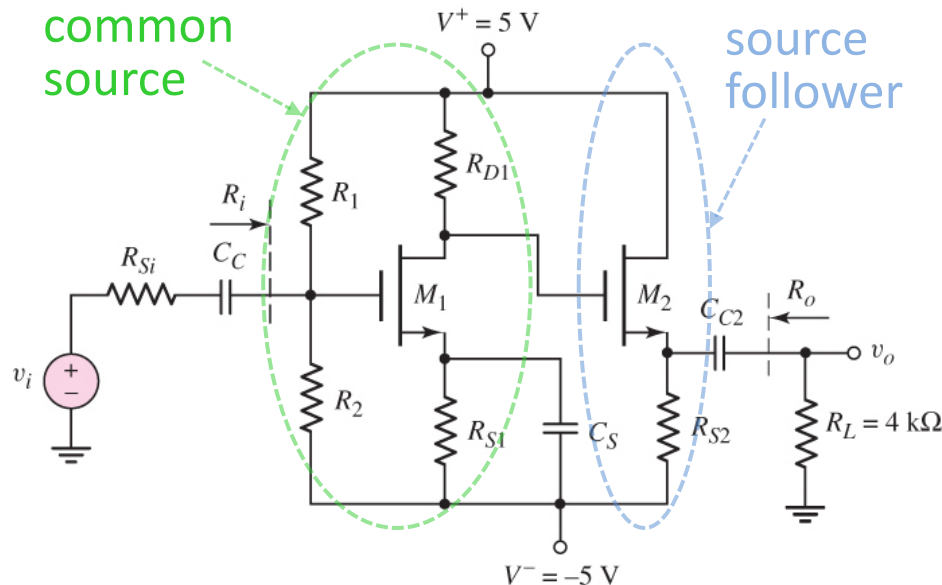- ❑ In most applications, a single-transistor amplifier will not be able to meet the combined specifications of e.g. a given signal gain and output impedance.
- ❑ Multiple single-transistor amplifiers can be connected together to obtain the desirable circuit performance.





- The amplifier circuit on the left is called a **cascade** configuration.

Transistor Amplifiers

(cascode configuration)

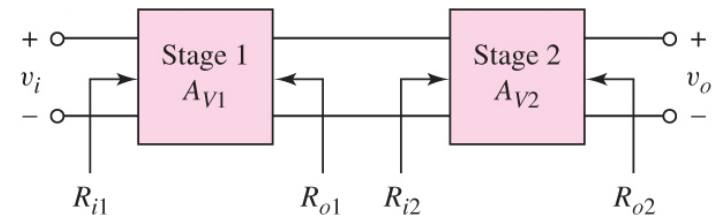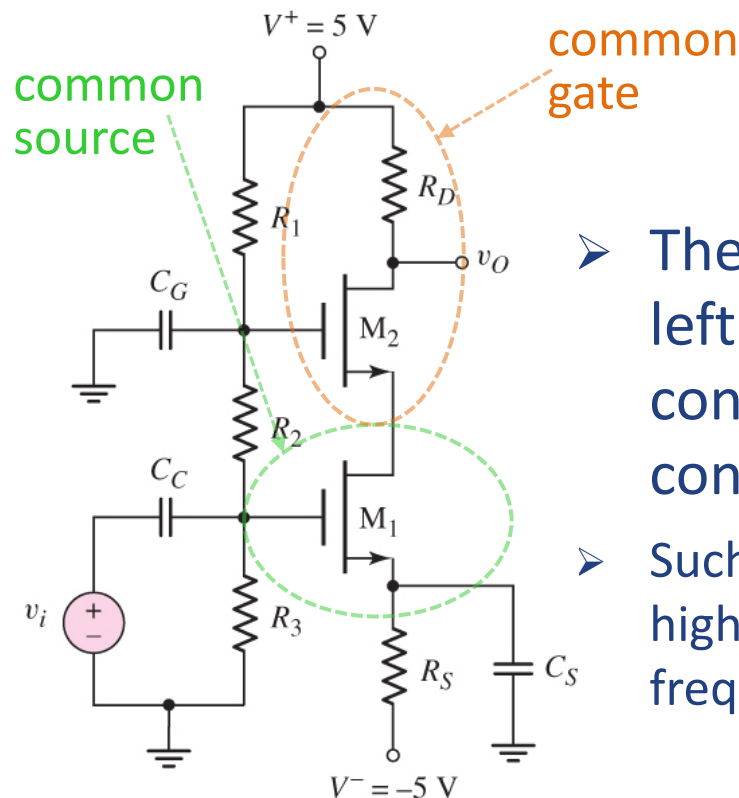- Another common design for multi-stage amplifier circuits is the use of the **cascode** configuration.



- The amplifier circuit shown on the left is essentially a **common-source** configuration and a **common-gate** configuration combined together.
- Such a **cascode** configuration allows very high output resistance and better high frequency response.


From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition,
© 2010 McGraw-Hill, USA.

EEE307 Electronics for Communications
Semester 1, 2019/2020 by S.Lam@XJTLU

LNA Example

(3-stage transistor amplifier)

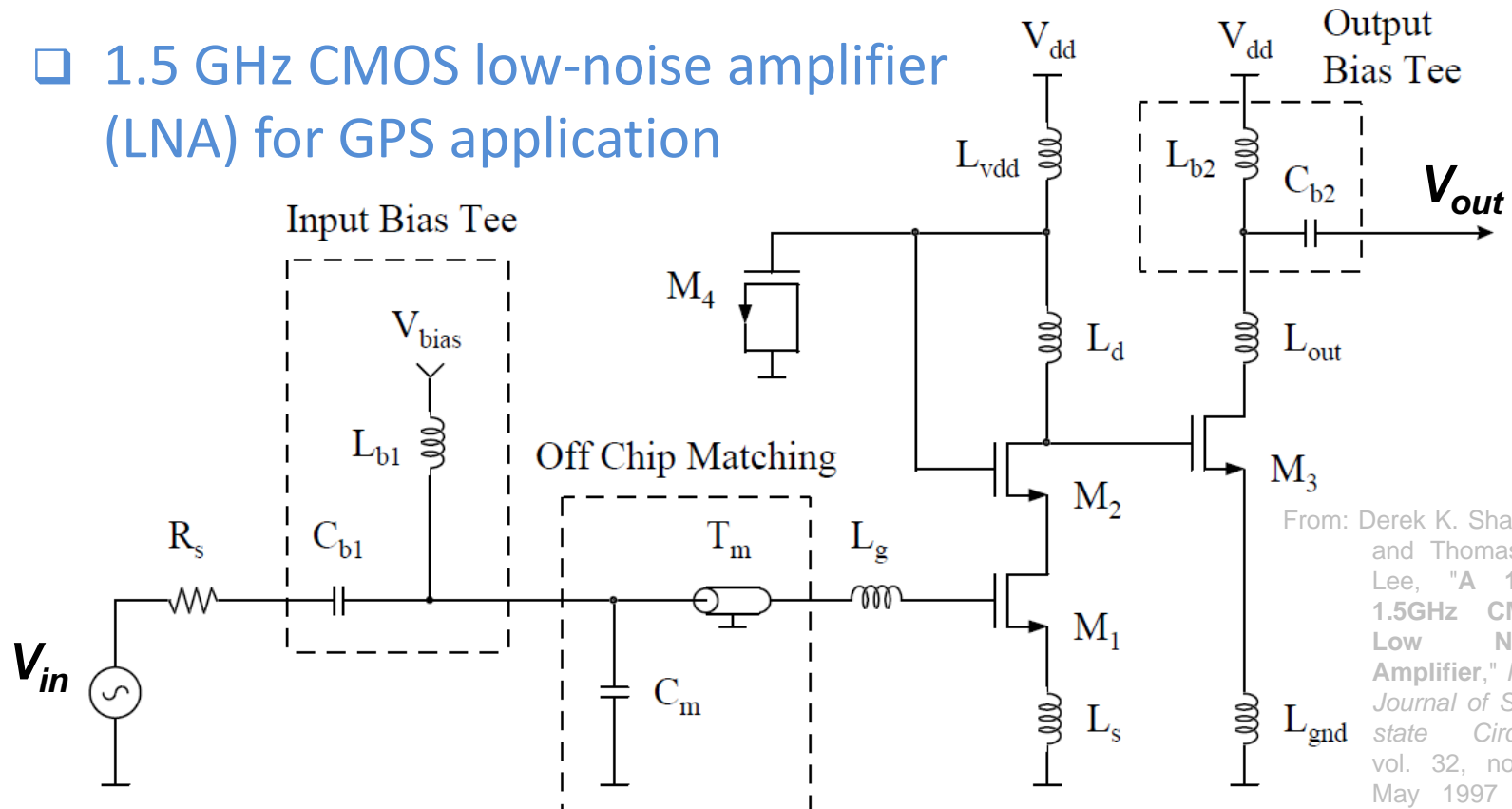- 1.5 GHz CMOS low-noise amplifier (LNA) for GPS application



From: Derek K. Shaeffer and Thomas H. Lee, "A 1.5V, 1.5GHz CMOS Low Noise Amplifier," *IEEE Journal of Solid-state Circuits*, vol. 32, no. 5, May 1997 (pp. 745-759).

- CS, CG and CS amplifiers connected together
 - Note the source-degeneration CS configuration.



Xi'an Jiaotong-Liverpool University
西交利物浦大学

Analysis of Transistor Amplifiers

(analysis of DC biasing)

- ❑ To understand the LNA circuits, the constituent transistor circuits in DC operation need to be analysed using the basic transistor characteristics and properties.
- ❑ **DC circuit analysis** is the first step both in hand calculation and computer simulation.
 - In particular, analysis of the DC biasing of transistor circuits is important for analogue circuit design.
- ❑ Note that the MOSFET has three regions of operation: cut-off, **triode** and **saturation**.
- ❑ For circuit applications, we need to set a well-defined biasing condition or called **quiescent operating point** (or **Q-point** for short) for the MOSFET in a particular region of operation.



Xi'an Jiaotong-Liverpool University

西交利物浦大學

AC Analysis of Amplifier Circuits

(guidelines applicable to transistor circuits)

- ❑ In carrying out **AC analysis** of transistor circuits, the following guidelines are suggested.
 1. Analyze the circuit with only the DC sources to find the **quiescent** solution. Transistors must be biased in **saturation region** for linear amplifiers.
 2. Replace the transistors (or other electronic devices e.g. diodes) with small-signal models.
 3. Analyse the small-signal equivalent circuit, setting DC sources to zero (i.e. short-circuited), to produce the circuit to the time-varying input signals only.
 - $r_{AC} = (\Delta V_{DC})/(\Delta I_{DC}) = 0/(\Delta I_{DC}) = 0 \Rightarrow$ a DC voltage source becomes short-circuited in the small signal equivalent circuit.
 - How about the case for a DC current source?




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Common-Source Amplifier


(small-signal equivalent circuit)

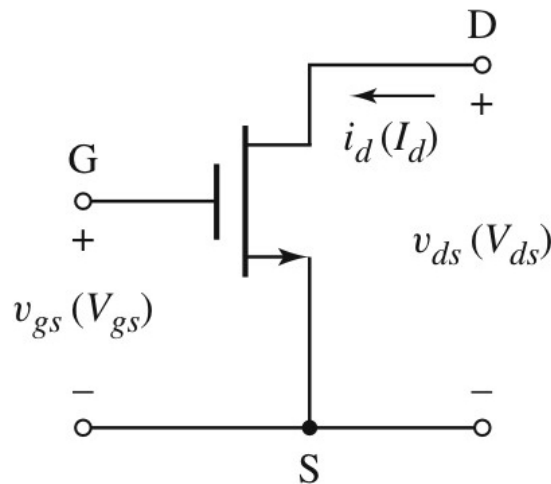- ❑ In the AC analysis of transistor circuits, the MOSFET (or in general any transistors) can be represented by a small-signal equivalent circuit (Fig. (b)):



(a)

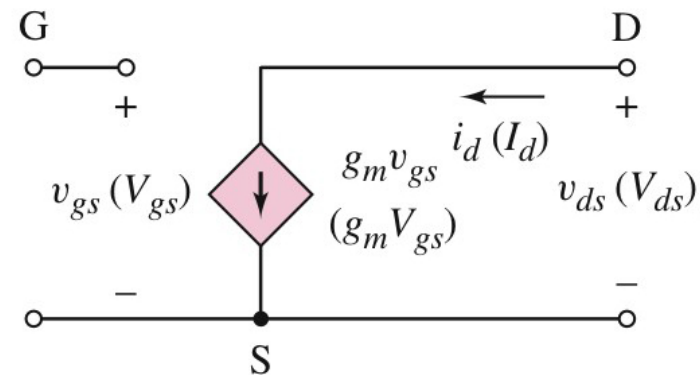From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition, © 2010 McGraw-Hill, USA.



(b)


- ❑ Initially, we assume that the signal frequency is sufficiently low so that the capacitance at the gate terminal can be neglected \Rightarrow *open circuit* for the gate terminal.

Common-Source Amplifier

(AC analysis using the equivalent circuit)

- By representing the common-source amplifier using the small-signal equivalent circuit, the **voltage gain** can be determined easily.

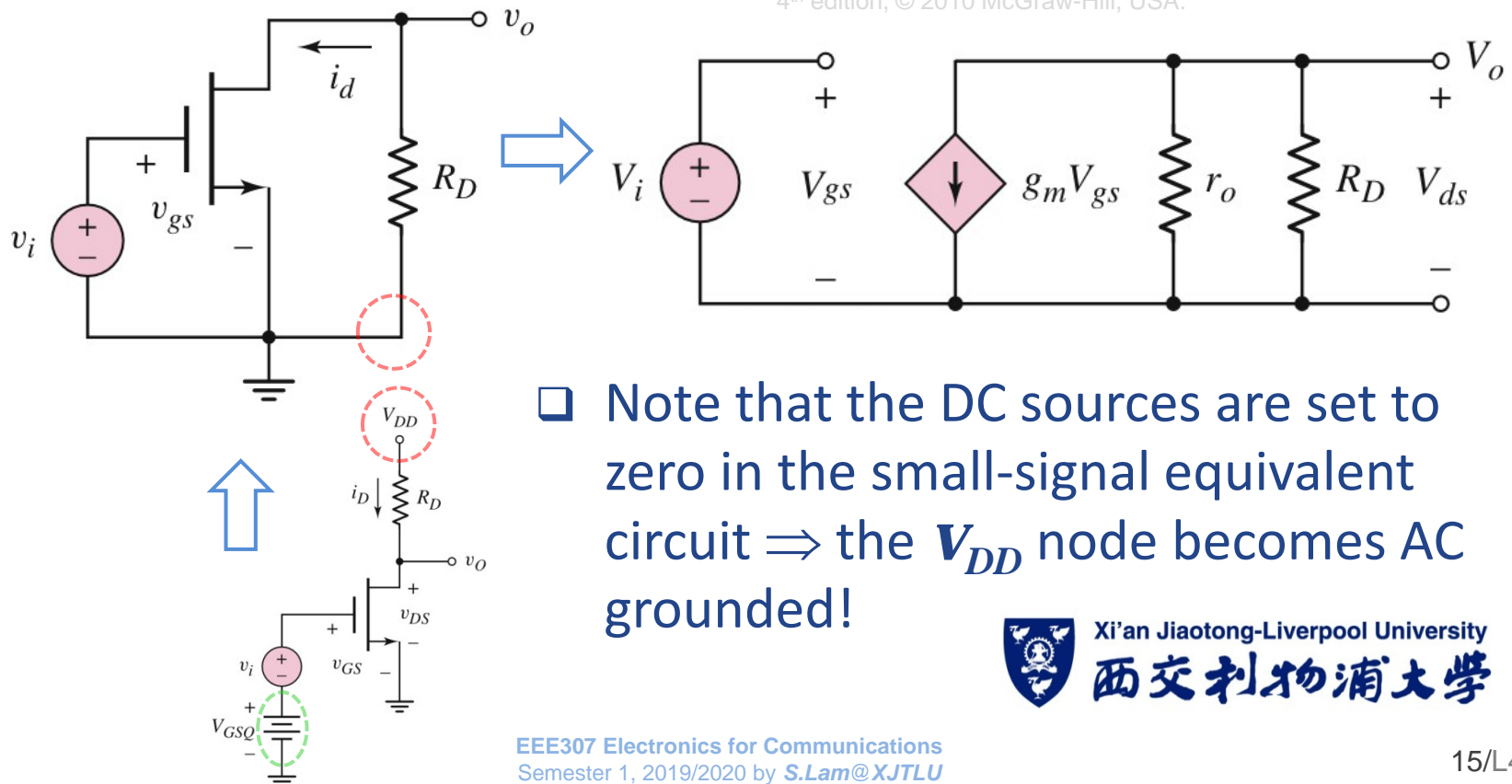From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition, © 2010 McGraw-Hill, USA.




- Note that the DC sources are set to zero in the small-signal equivalent circuit \Rightarrow the V_{DD} node becomes AC grounded!

Common-Source Circuit

(voltage gain)

- The small-signal equivalent circuit can be analysed using circuit theorems and laws.

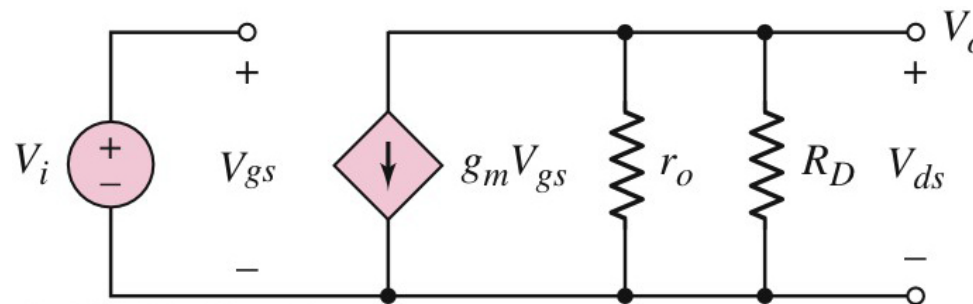From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition, © 2010 McGraw-Hill, USA.



$$g_m = 2K_n(V_{GSQ} - V_{TN}) = 2\sqrt{K_n I_{DSQ}}$$

$$r_o = [\lambda K_n (V_{GSQ} - V_{TN})^2]^{-1} \approx (\lambda I_{DSQ})^{-1}$$


- At the output, $v_o = -i_{ds}(r_o \parallel R_D)$ (according to **Ohm's law**).
- But $i_{ds} = g_m v_{gs}$ (according to **Kirchhoff's current law**)
- So $v_o = -(g_m v_{gs})(r_o \parallel R_D) = -(g_m v_i)(r_o \parallel R_D)$
- the small-signal **voltage gain** for the CS circuit is

$$A_v = \frac{v_o}{v_i} = -g_m (r_o \parallel R_D)$$

Common-Source Amplifier

(with voltage divider biasing)

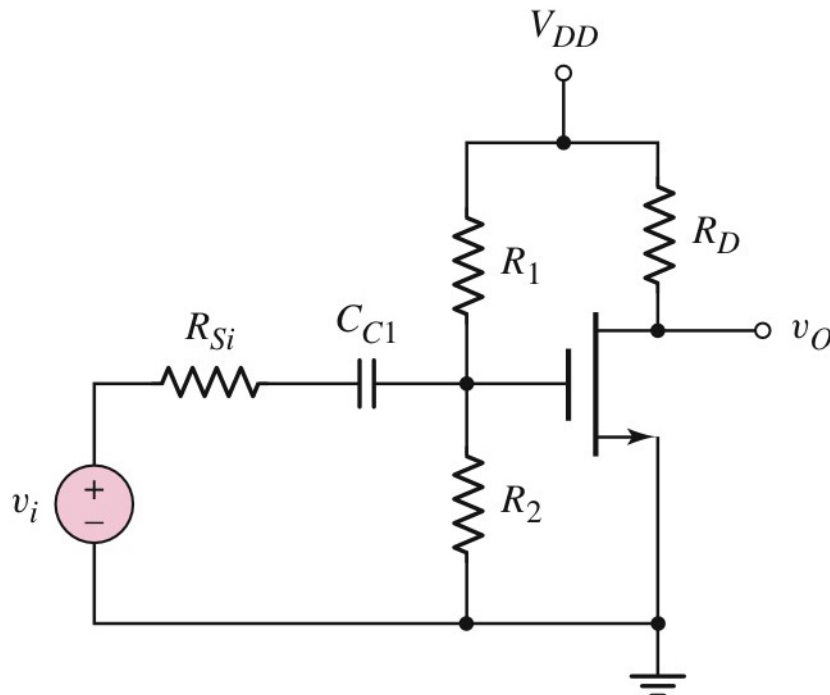- Consider a practical common-source amplifier in which the MOSFET is biased at a certain quiescent point with voltage divider biasing and there is a coupling capacitor to provide DC isolation between the amplifier and the signal source.




- The coupling capacitor usually has a high enough capacitance C_C so that the magnitude of the capacitor impedance is negligible (short-circuited) at the signal frequency (e.g. 20 kHz $\Rightarrow |Z_C| \approx 0.8 \Omega$ with $C_C = 10 \mu\text{F}$):
$$|Z_C| = \frac{1}{2\pi f C_C}$$

Common-Source Amplifier

(AC circuit analysis)

- Representing the practical CS amplifier by a small-signal equivalent circuit, the voltage gain can be determined straightforwardly, especially by “breaking” the whole circuit into two amplification stages.

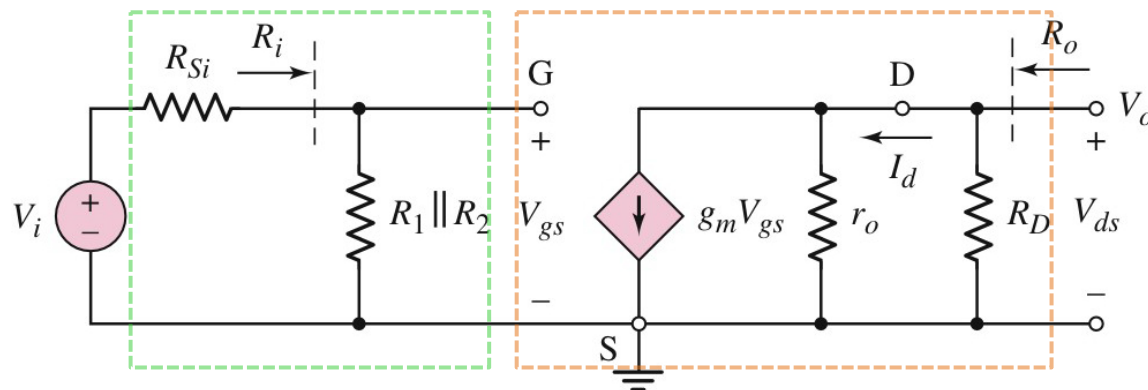From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition, © 2010 McGraw-Hill, USA.




$$A_{v1} = v_{gs}/v_i = \frac{R_i}{R_i + R_{Si}}$$

$$A_{v2} = v_o/v_{gs} = -g_m(r_o \parallel R_D)$$

$$A_v = v_o/v_i = -g_m(r_o \parallel R_D) \left(\frac{R_i}{R_i + R_{Si}} \right)$$

$R_i = R_1 \parallel R_2$

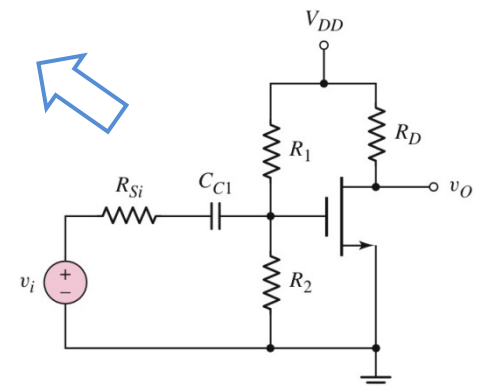


Xi'an Jiaotong-Liverpool University
西交利物浦大學

CS Amplifier with Source Resistor

(source degeneration)

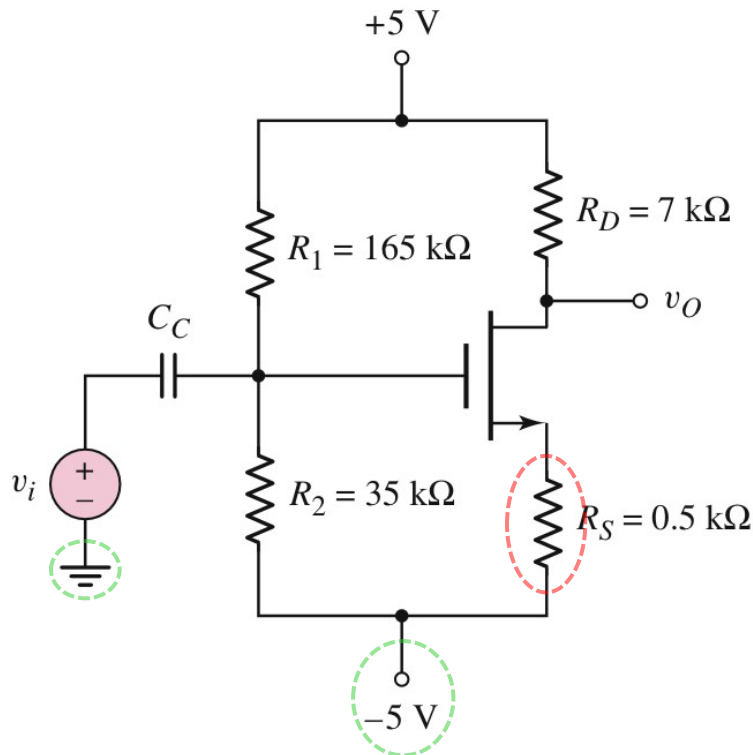- ❑ In the CS amplifier, a source resistor (or an inductor) is sometimes added achieve certain purposes e.g. to stabilise the Q -point against transistor variations.



- In the circuit shown on the left, it has positive and negative supply voltages.
⇒ different **DC biasing** from the previous CS amplifier
- The negative supply voltage node however becomes grounded in the **AC analysis**.

Why?




Xi'an Jiaotong-Liverpool University
西交利物浦大學

From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition,
© 2010 McGraw-Hill, USA.

CS Amplifier with Source Resistor

(AC analysis)

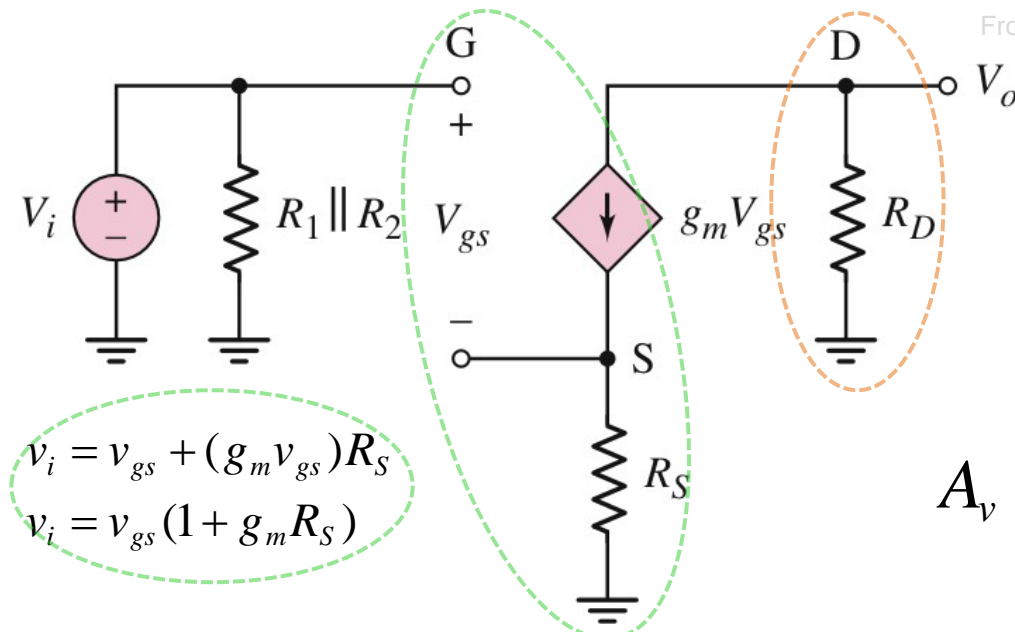- After the DC analysis (to calculate V_{GSQ} and I_{DSQ}) to obtain the small-signal parameters (g_m and r_o), the circuit can be represented by a small-signal equivalent circuit.



From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition, © 2010 McGraw-Hill, USA.

$$v_o = -(g_m v_{gs}) R_D$$

- The small-signal voltage gain is v_o/v_i

$$A_v = \frac{-g_m R_D}{1 + g_m R_S} = -G_m R_D$$


- $G_m = g_m / (1 + g_m R_S)$ is the effective transconductance.

Source Bypass Capacitor

(minimise the loss in the CS signal gain)

- ❑ Instead of using a resistor in the source-degeneration CS amplifier, a source bypass capacitor can be added to minimise the loss in the small-signal voltage gain while maintaining the Q-point stability.

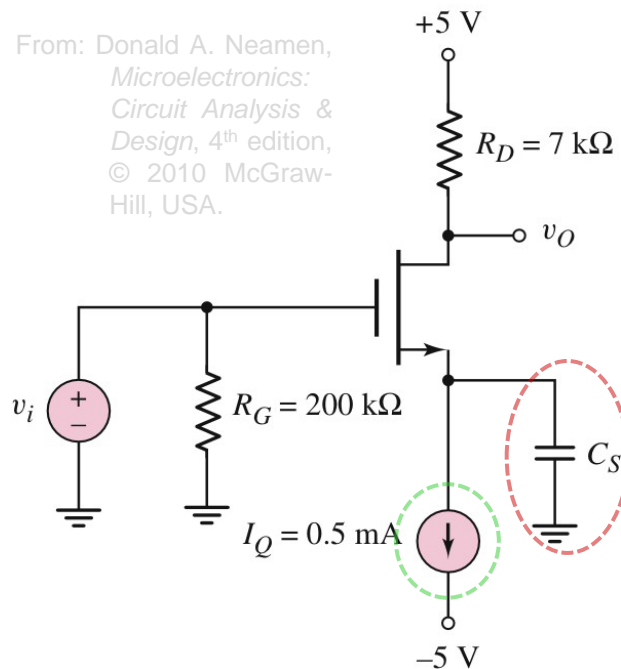From: Donald A. Neamen,
*Microelectronics:
Circuit Analysis &
Design*, 4th edition,
© 2010 McGraw-
Hill, USA.



- ❑ The source bypass capacitor needs to have a high enough capacitance C_S so that it can be regarded as an AC short-circuit.
- ❑ The Q-point stability can be further increased by replacing the source-degeneration resistor with a constant current source.




Xi'an Jiaotong-Liverpool University

西交利物浦大學



Source Bypass Capacitor

(minimise the loss in the CS signal gain)

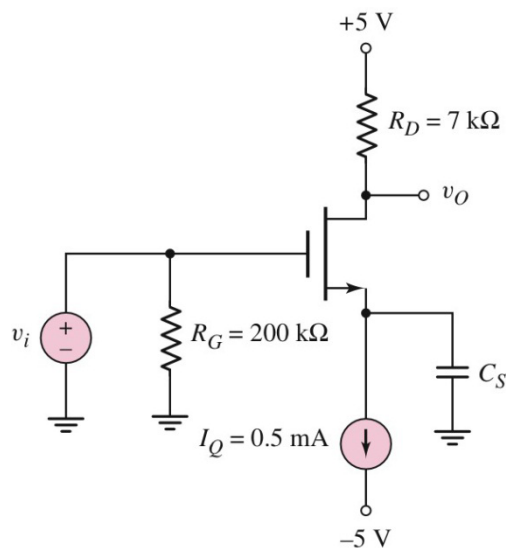- ❑ The same as before, the DC analysis needs to be carried out first (to calculate V_{GSQ} and I_{DSQ}) to determine the small-signal parameters (g_m and r_o).
- ❑ The circuit can then be represented by a small-signal equivalent circuit for AC analysis:
 - The source is held at the AC signal ground with the bypass capacitor.



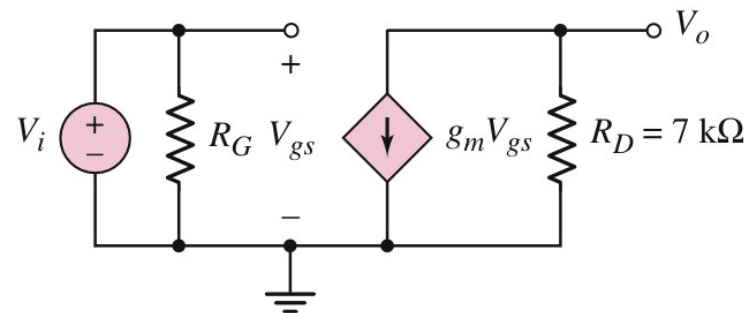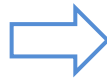- The constant DC current source becomes an AC open-circuit.



From: Donald A. Neamen,
*Microelectronics:
Circuit Analysis &
Design*, 4th edition,
© 2010 McGraw-
Hill, USA.



Xi'an Jiaotong-Liverpool University
西交利物浦大学


(gate at signal ground)



Common-Gate Configuration

(small-signal equivalent circuit & voltage gain)

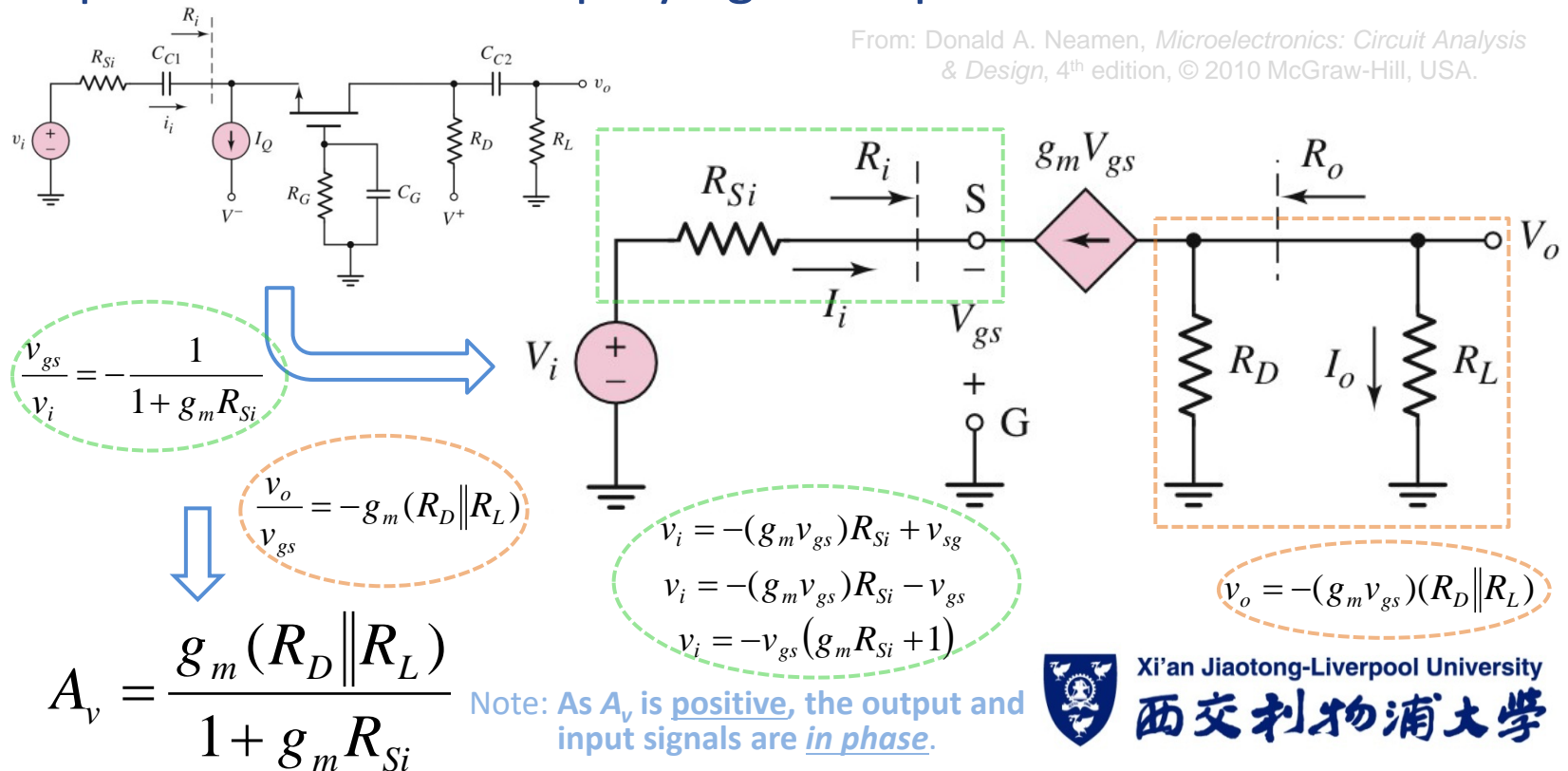- Same as before, representing the common-gate circuit by a **small-signal equivalent circuit**, **AC analysis** can be performed after simplifying the equivalent circuit further.




Common-Gate Configuration

(small-signal current gain)

- In some cases, the signal input to a common-gate circuit is a current. Then we need to calculate the current gain also using the **small-signal equivalent circuit**, but with a **Norton equivalent circuit** as the signal source.

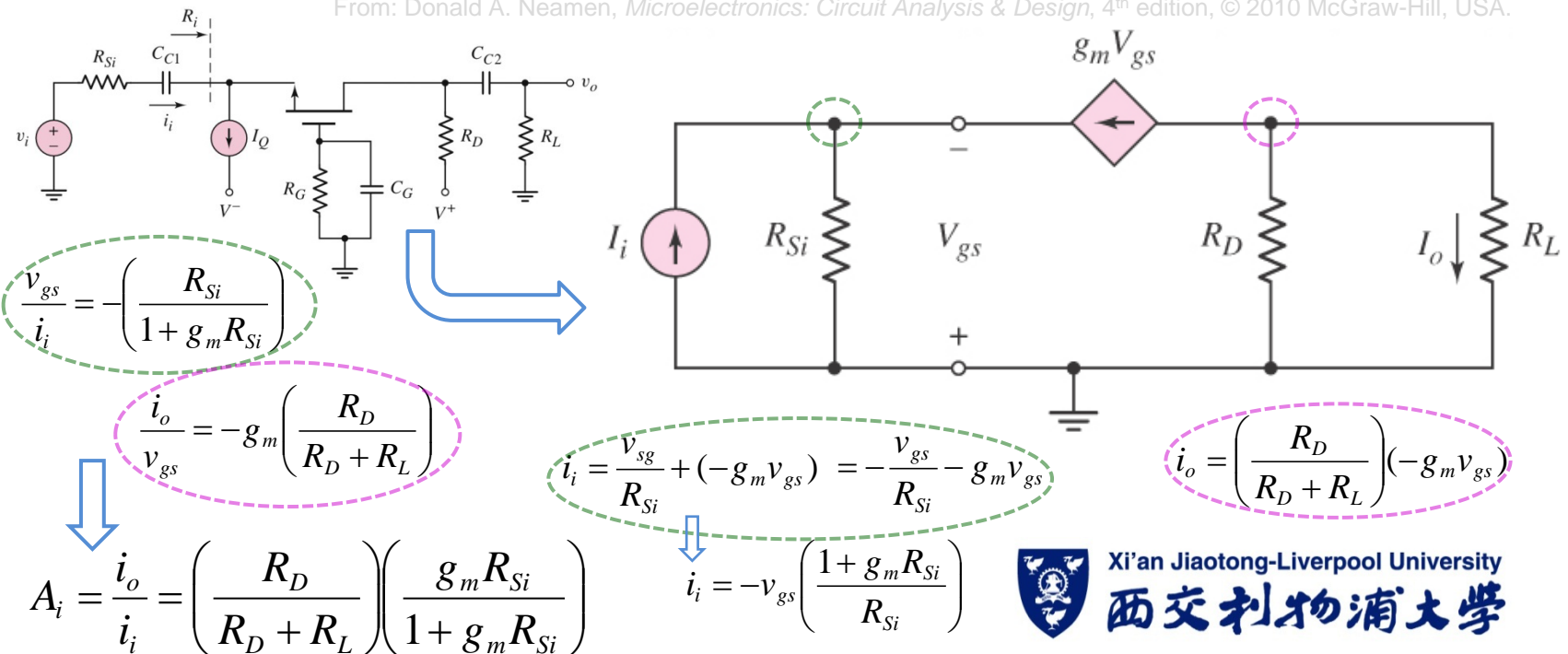From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition, © 2010 McGraw-Hill, USA.




Common-Gate Configuration

(current gain & summary notes)

- In the common-gate amplifier circuit, the current gain is close to unity if $R_D \gg R_L$ and $g_m R_{Si} \gg 1$:
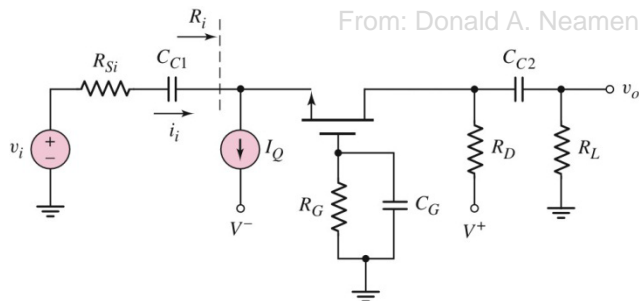
$$A_i = \frac{i_o}{i_i} = \left(\frac{R_D}{R_D + R_L} \right) \left(\frac{g_m R_{Si}}{1 + g_m R_{Si}} \right) \approx 1 \quad \text{if } R_D \gg R_L \text{ and } g_m R_{Si} \gg 1$$



From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition, © 2010 McGraw-Hill, USA.

- Advanced notes: the common-gate amplifier suffers from the **trade-off** between the **voltage headroom** and the **signal gain**.


- To achieve a high gain, it is necessary to have a high biasing drain current I_D or a high R_D .
- However, the drain voltage, $V_{DS} = V_{DD} - I_D R_D$, must remain above $(V_{GSQ} - V_{TN})$ to ensure that the MOSFET is in the saturation region (i.e. $V_{DS} > V_{DSsat}$).

Common-Drain Amplifier

(output taken off at the source)

- The second topology of basic FET amplifiers is the common-drain configuration: the output signal is taken off the source with respect to ground and the drain is connected directly to V_{DD} .

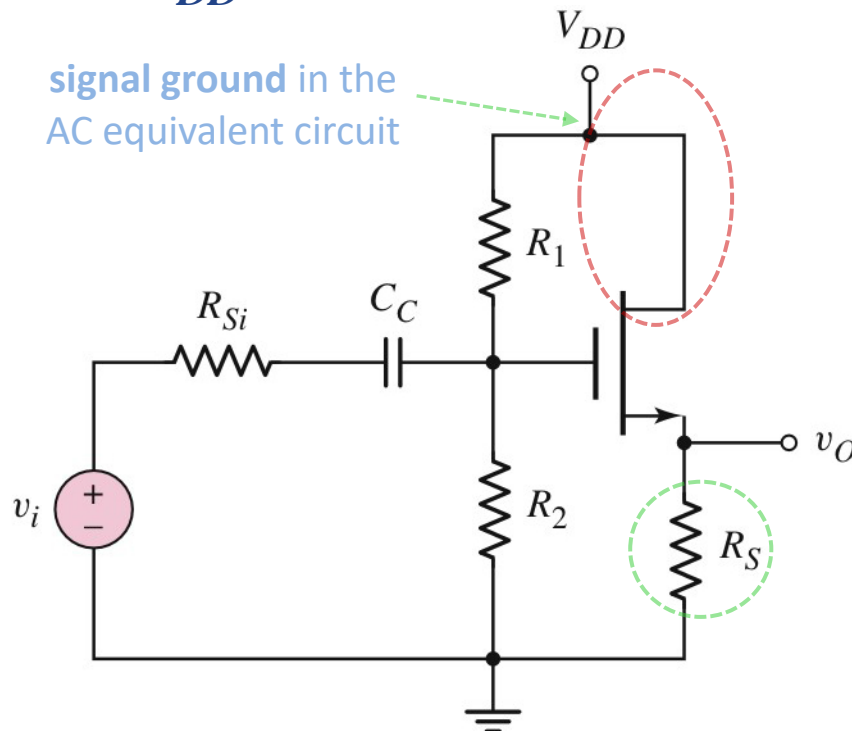From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition, © 2010 McGraw-Hill, USA.




- Since the node becomes signal ground in the small-signal equivalent circuit, the drain terminal of the MOSFET is the common signal ground for both the input and output signals.

Common-Drain Amplifier

(AC analysis)

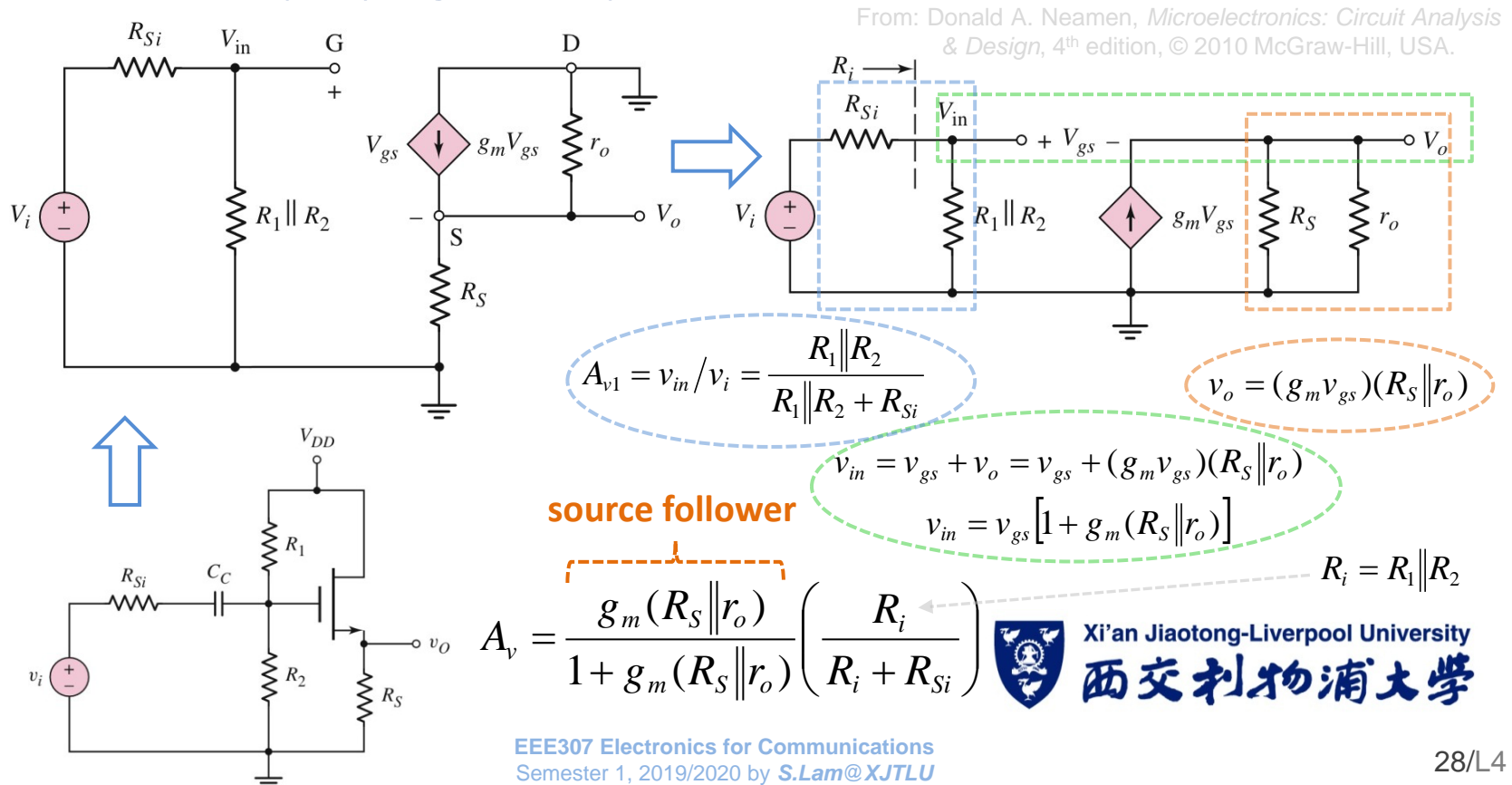
- Representing the common-drain circuit by a **small-signal equivalent circuit, AC analysis** can be performed as usual after simplifying the equivalent circuit further.



Transistor at Radio Frequencies

(parasitic circuit elements)

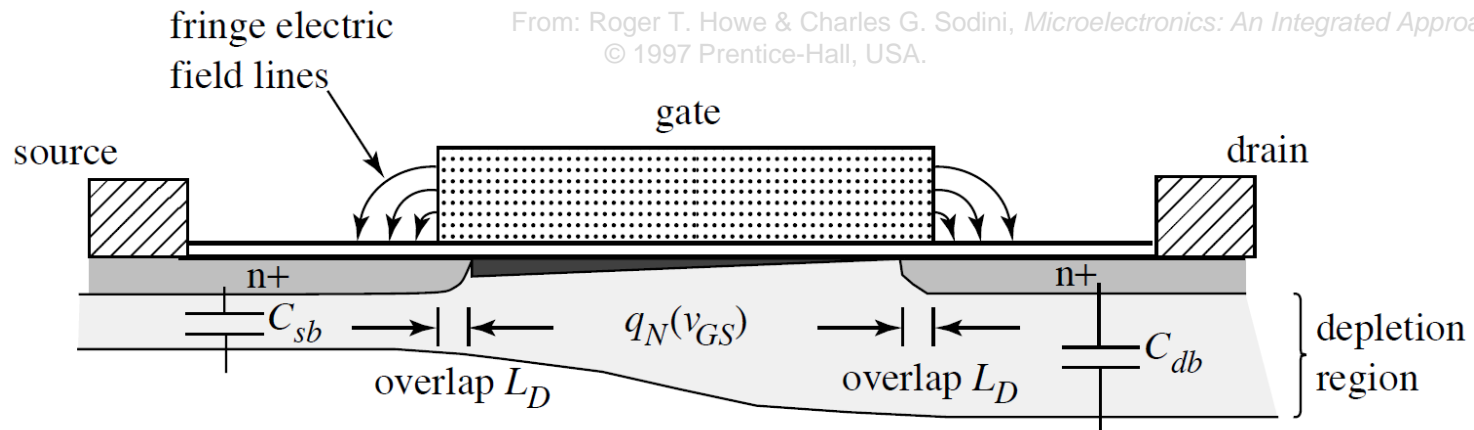- ❑ To analyse LNA circuits which operate well beyond the multi-hundred kHz range, the low-frequency transistor circuit analysis need to be modified.
- ❑ In the radio frequency range, the parasitic circuit elements (especially capacitors) cannot be ignored.




- The transistor's equivalent circuit needs to be modified.

Transistor at Radio Frequencies

(small-signal equivalent circuit)

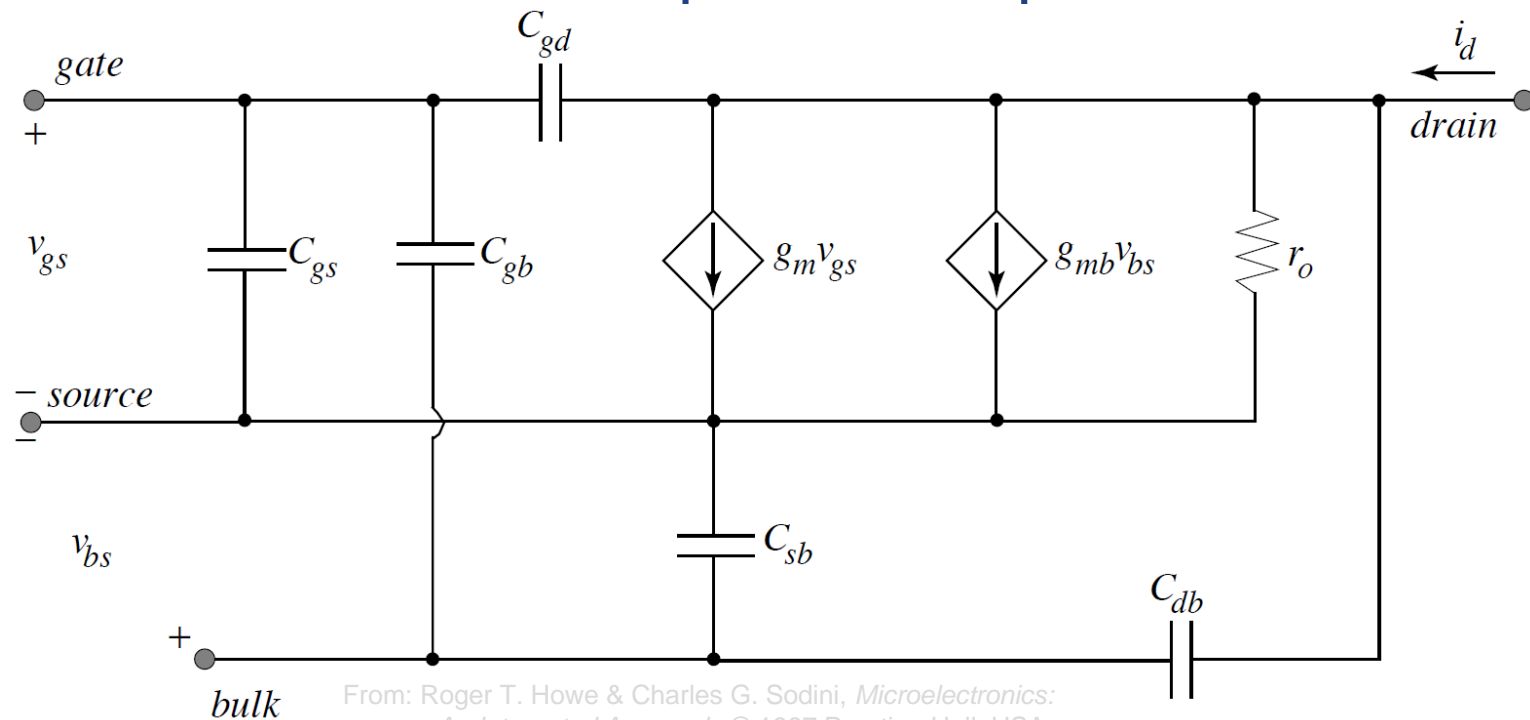- ❑ The small-signal equivalent circuit for the transistor needs to include the parasitic capacitance.



From: Roger T. Howe & Charles G. Sodini, *Microelectronics: An Integrated Approach*, © 1997 Prentice-Hall, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大学

Transistor at Radio Frequencies

(small-signal equivalent circuit)

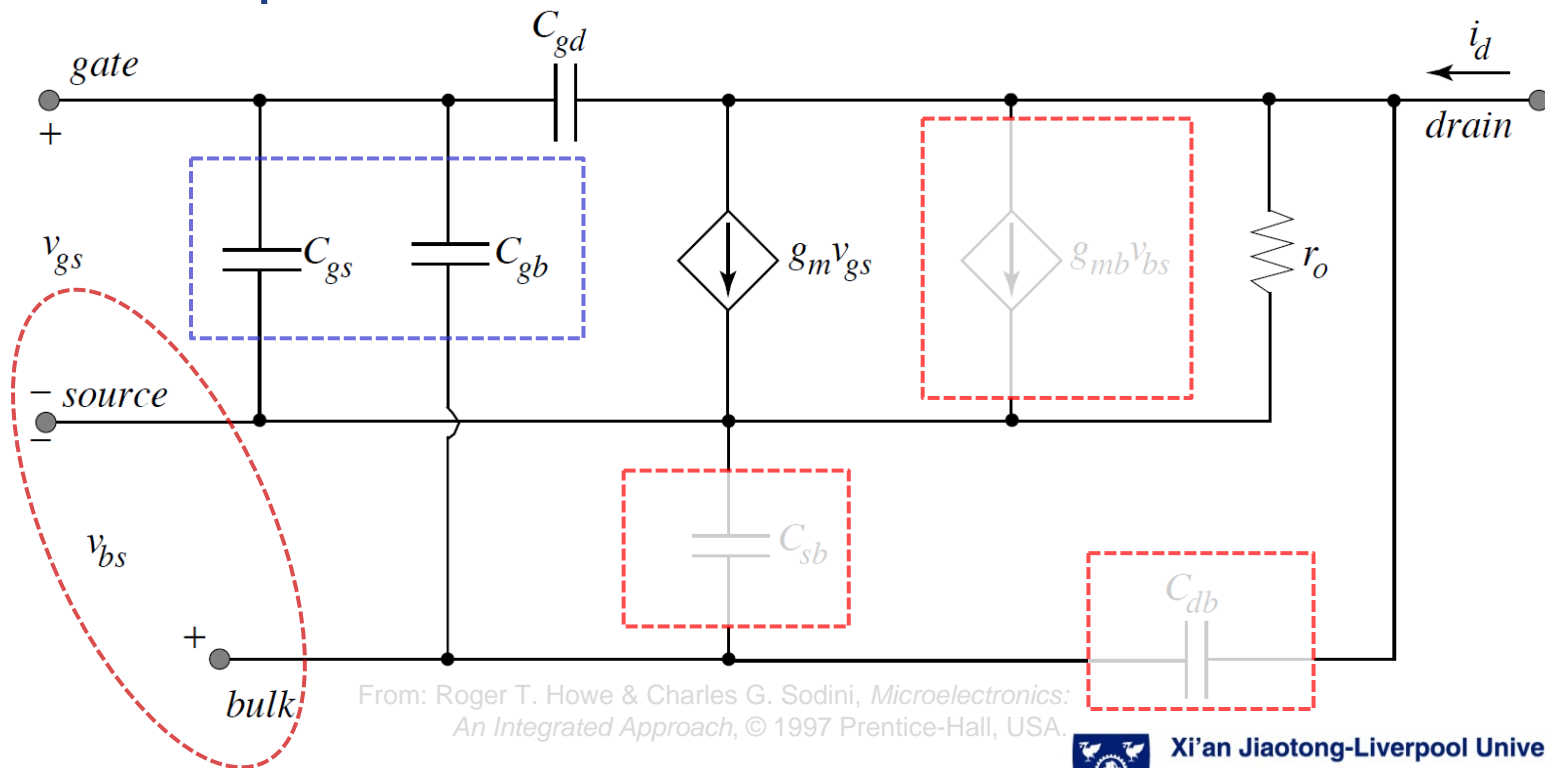- ❑ In the CS configuration, the equivalent circuit can be simplified.



From: Roger T. Howe & Charles G. Sodini, *Microelectronics: An Integrated Approach*, © 1997 Prentice-Hall, USA.



Xi'an Jiaotong-Liverpool University
西交利物浦大学

RF Transistor Amplifiers

(AC analysis & circuit construction)

- ❑ With the small-signal equivalent circuits including the capacitors and inductors, similar AC analysis of the LNA circuit can be performed.
- ❑ In the circuit construction (using discrete components in this EEE307 module), suitable transistors need to be selected first.
 - The transistors can operate at high enough frequency of interest.
 - One parameter of interest is f_T , called the unity gain frequency. f_T is the frequency at which the current gain is one (i.e. 0 dB).
 - Refer to the transistor's data sheet