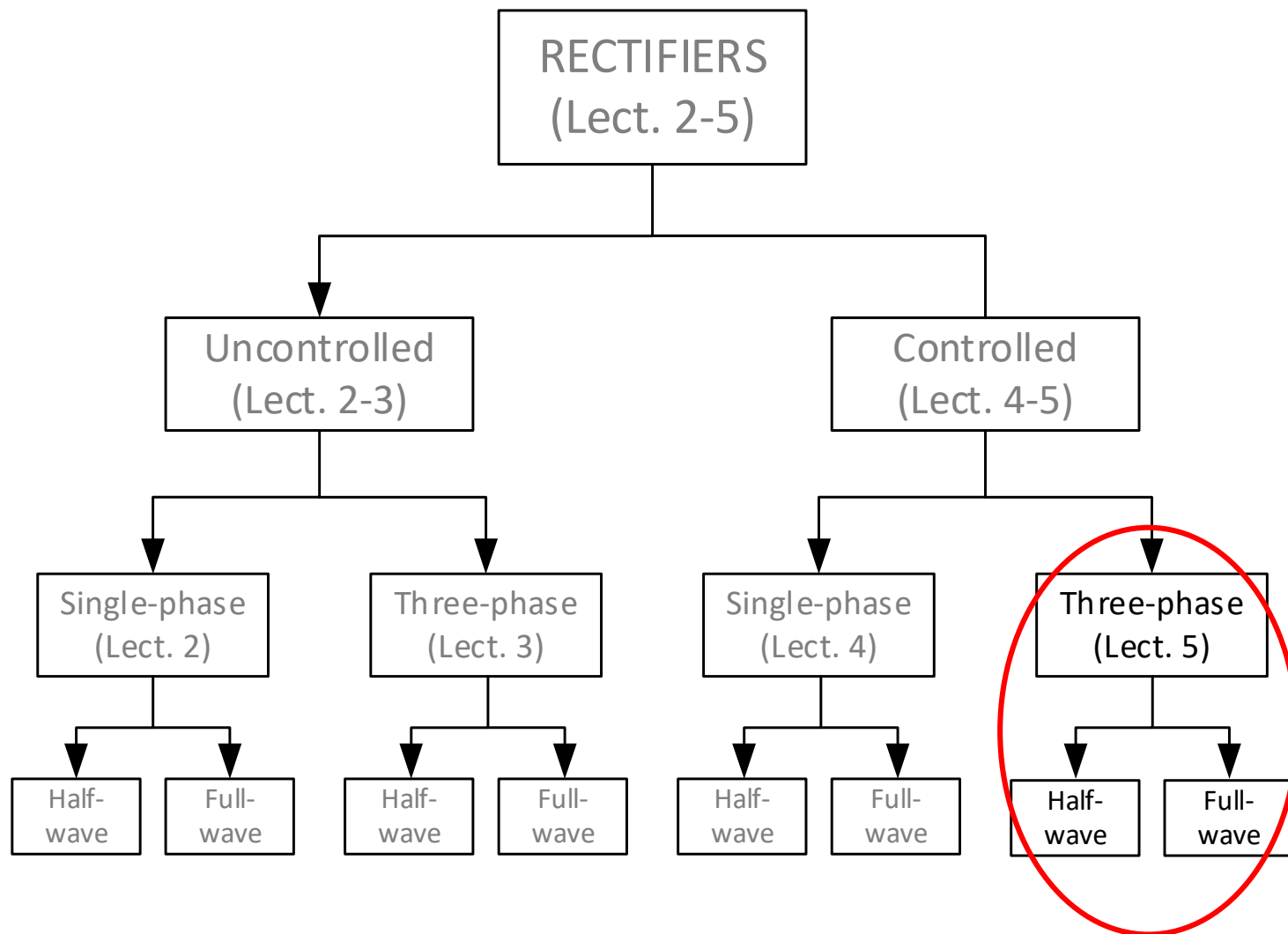


EEE213 Power Electronics and Electromechanism

5. Controlled Rectifier – Three Phase

Classification




Outline

- Three-phase, controlled rectifiers
 - Half-wave
 - Firing angle (triggering angle) α ;
 - Resistive loading;
 - Inductive loading;
 - Full-wave (bridge)
 - Resistive loading;
 - Inductive loading.
- Comparison


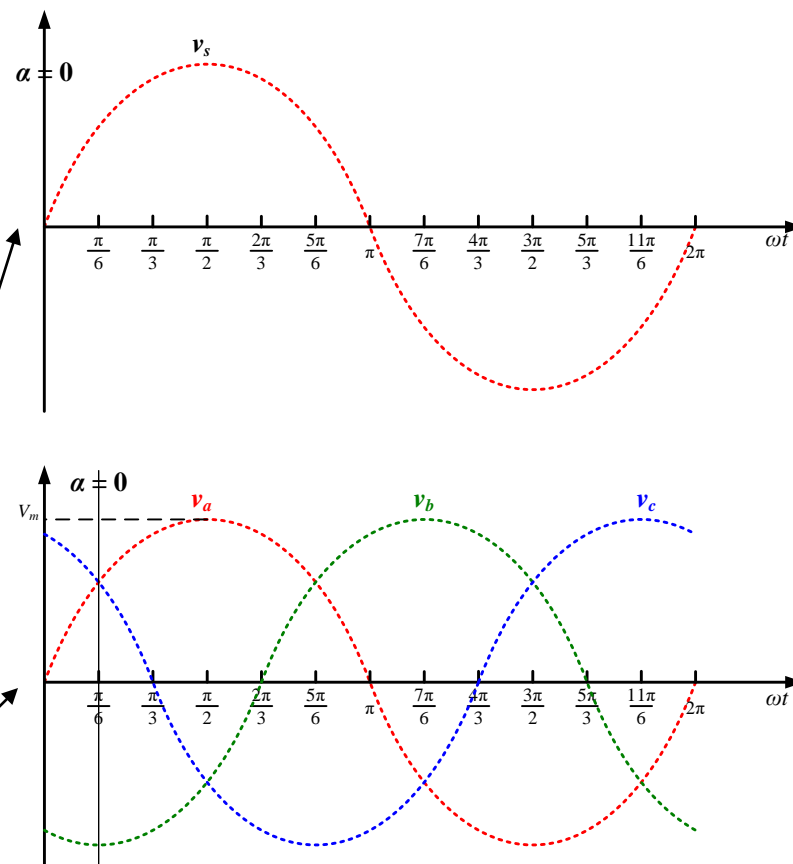
1.1 Firing angle (triggering angle)

- In the controlled rectifier, the controllability of the circuit is realized by triggering the thyristors at different phase, which is called the **firing angle**, or **triggering angle**. It is usually represented by “ α ”;
 - This trigger signal is a current (or voltage) pulse at the “gate” terminal of thyristors;
 - For single phase circuit, $\alpha = 0$ means trigger signal is sent at $\omega t = 0$;
 - For three-phase circuit, $\alpha = 0$ means trigger signal is sent at $\omega t = \pi/6$, which is the first **natural commutation (phase changing) point**.



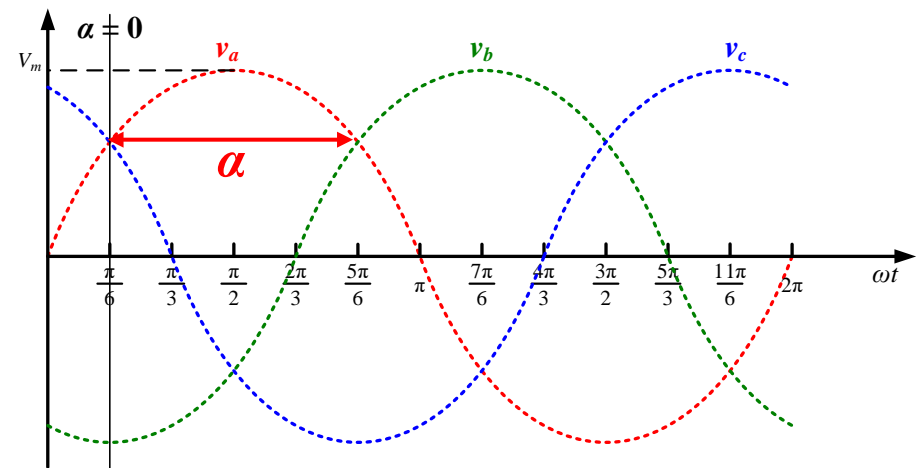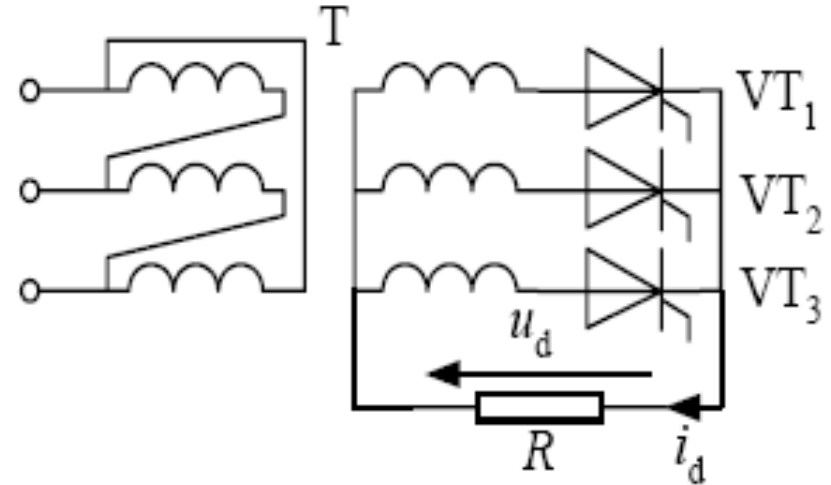
1.1 Three-phase, half-wave, R-load

- Resistive load
 - Three phase supply - star connection
 - Common-cathode connection
- Natural commutation (phase-changing) point
 - The earliest trigger angle for each phase
 - It is considered as the starting point for thyristor triggering angle α , i.e. $\alpha = 0^\circ$
 - Phase-shift range: $\alpha \leq 120^\circ$



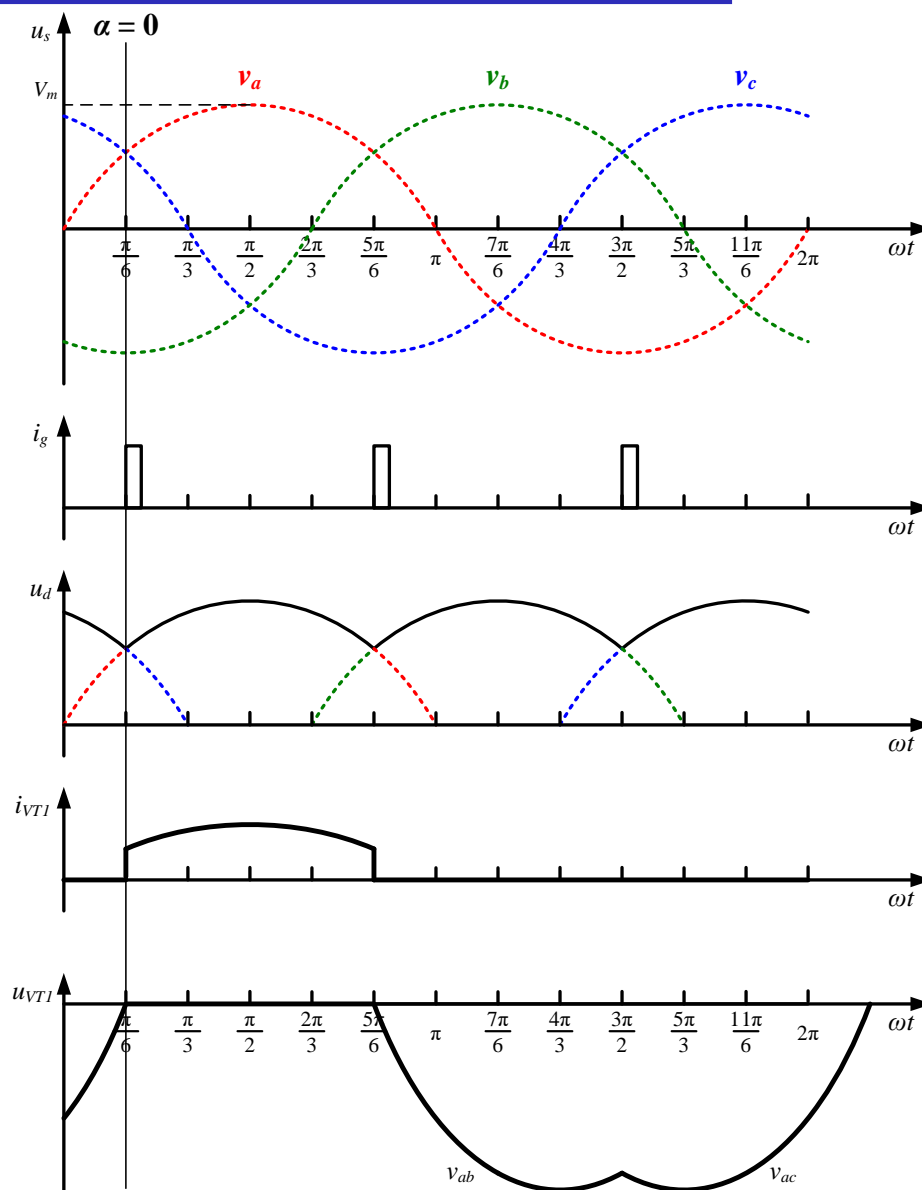
1.1 Three-phase, half-wave, R-load

- When $\alpha = 0^\circ$ (Same as the uncontrolled circuit);
 - For example: at $\alpha = 0$ ($\omega t = \pi/6$), as soon as VT1 is forward biased (red line v_a becomes the largest one), a trigger signal is provided to VT1, so VT1 starts to conduct;
 - $2\pi/3$ after, when v_b becomes the largest one, another trigger signal is provided to VT2, so VT2 starts to conduct;
 - At $\omega t = 3\pi/2$, when v_c becomes the largest one, the trigger signal to VT3 is provided, so VT3 starts to conduct.



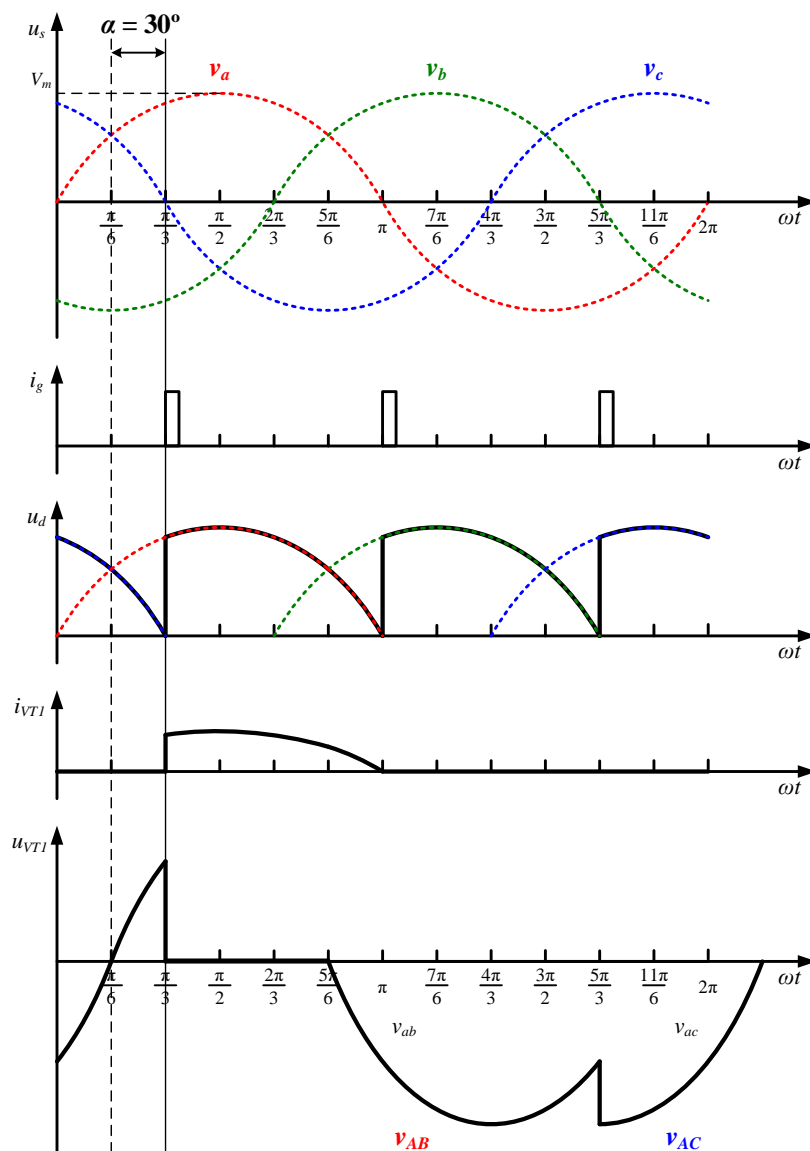
1.1 Three-phase, half-wave, R-load

- When $\alpha = 30^\circ$
 - From $\omega t = \pi/6$ to $\pi/3$, although VT1 is forward biased (red line v_a is the largest one), no trigger signal is provided to VT1, so VT1 cannot conduct;
 - At $\alpha = 30^\circ$ ($\omega t = \pi/3$), a trigger signal is provided to VT1, so VT1 starts to conduct;
 - At $\omega t = 5\pi/6$, when v_b becomes the largest one, since no trigger signal is provided to VT2, VT2 will not conduct until $\omega t = \pi$, when the trigger signal provided.



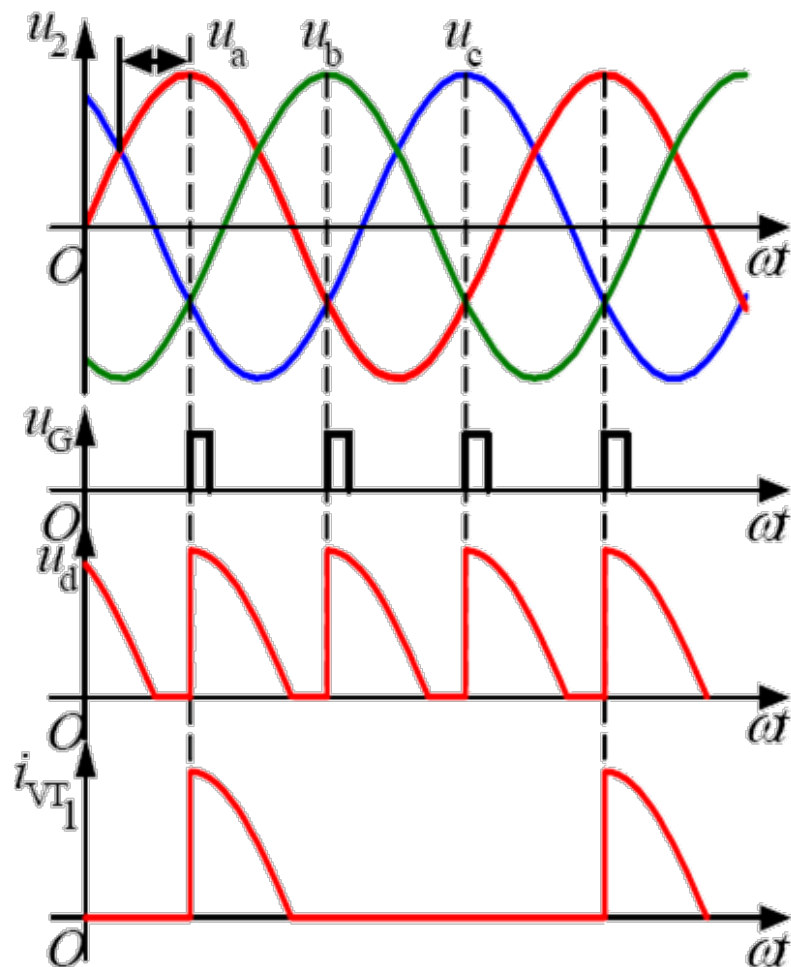1.1 Three-phase, half-wave, R-load

- When $\alpha = 60^\circ$
 - From $\omega t = \pi/6$ to $\pi/2$, although VT1 is forward biased (red line v_a is the largest one), no trigger signal is provided to VT1, so VT1 cannot conduct;
 - At $\alpha = 60^\circ$ ($\omega t = \pi/2$), a trigger signal is provided to VT1, so VT1 starts to conduct;
 - From $\omega t = \pi$ to $7\pi/6$, v_a is no longer the largest one, VT1 stops; since no trigger signal is provided to VT2, VT2 will not conduct either;
 - At $\omega t = 7\pi/6$, VT2 is forward biased and triggered, so it conducts.



Resistive load, quantitative analysis

- When $\alpha \leq 30^\circ$, load current i_d is continuous.

$$U_d = \frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} \sqrt{2}U_2 \sin \omega t d(\omega t) = \frac{3\sqrt{6}}{2\pi} U_2 \cos \alpha = 1.17U_2 \cos \alpha$$

- When $\alpha > 30^\circ$, load current i_d is discontinuous.

$$U_d = \frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\pi} \sqrt{2}U_2 \sin \omega t d(\omega t) = \frac{3\sqrt{2}}{2\pi} U_2 \left[1 + \cos\left(\frac{\pi}{6} + \alpha\right) \right] = 0.675 \left[1 + \cos\left(\frac{\pi}{6} + \alpha\right) \right]$$

- Average load current

$$I_d = \frac{U_d}{R}$$

- Thyristor voltages: reverse voltage = peak line voltage

$$U_{RM} = \sqrt{2} \times \sqrt{3}U_2 = \sqrt{6}U_2 = 2.45U_2$$



forward voltage = peak phase voltage

$$U_{FM} = \sqrt{2}U_2$$



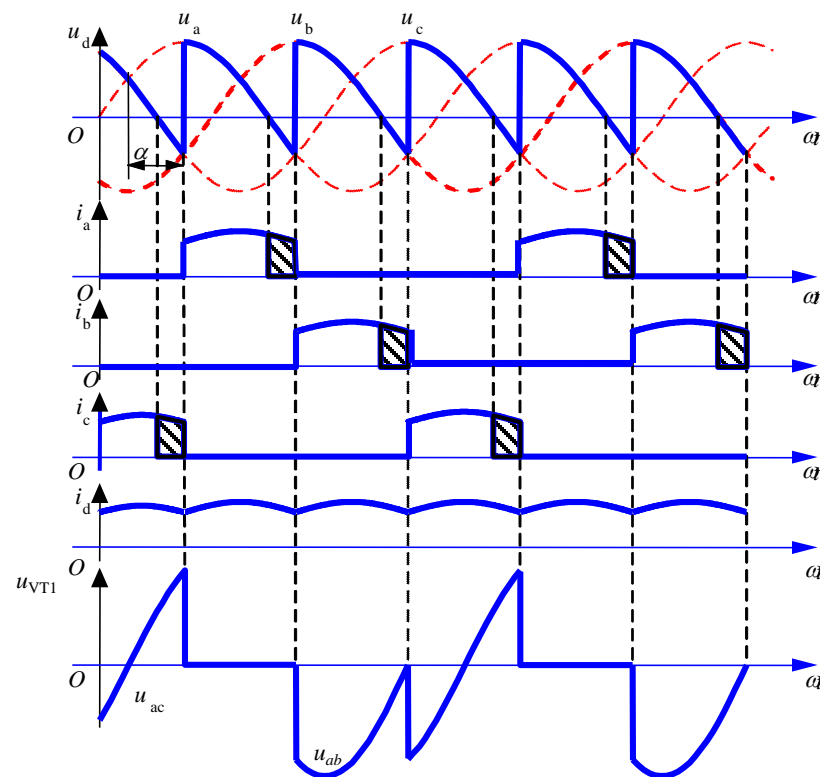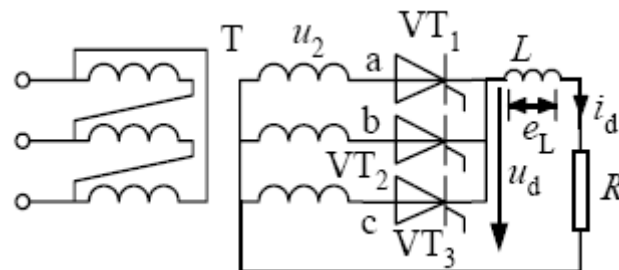1.2 Three-phase, half-wave, RL-load

- Inductive load (R-L)
 - When L is large enough, the output current i_d is almost flat;
 - When $\alpha \leq 30^\circ$, the rectified voltage waveform is similar to resistive load;
 - When $\alpha > 30^\circ$ (eg. $\alpha = 60^\circ$ as shown on right):
 - u_2 passes zero to negative, V_{T1} keeps conducting until the pulse for V_{T2} comes.
 - u_d has negative values.
 - Phase-shift range: $\alpha \leq 90^\circ$



Inductive load, quantitative analysis

- Load current i_d is always continuous, so

$$U_d = \frac{3}{2\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha} \sqrt{2}U_2 \sin \omega t d(\omega t) = \frac{3\sqrt{6}}{2\pi} U_2 \cos \alpha = 1.17U_2 \cos \alpha$$

- Thyristor current:


$$I_2 = I_{VT} = \frac{1}{\sqrt{3}} I_d = 0.577 I_d$$

- Thyristor voltages:

forward voltage = reverse voltage = peak line voltage

$$U_{FM} = U_{RM} = \sqrt{2} \times \sqrt{3}U_2 = \sqrt{6}U_2 = 2.45U_2$$

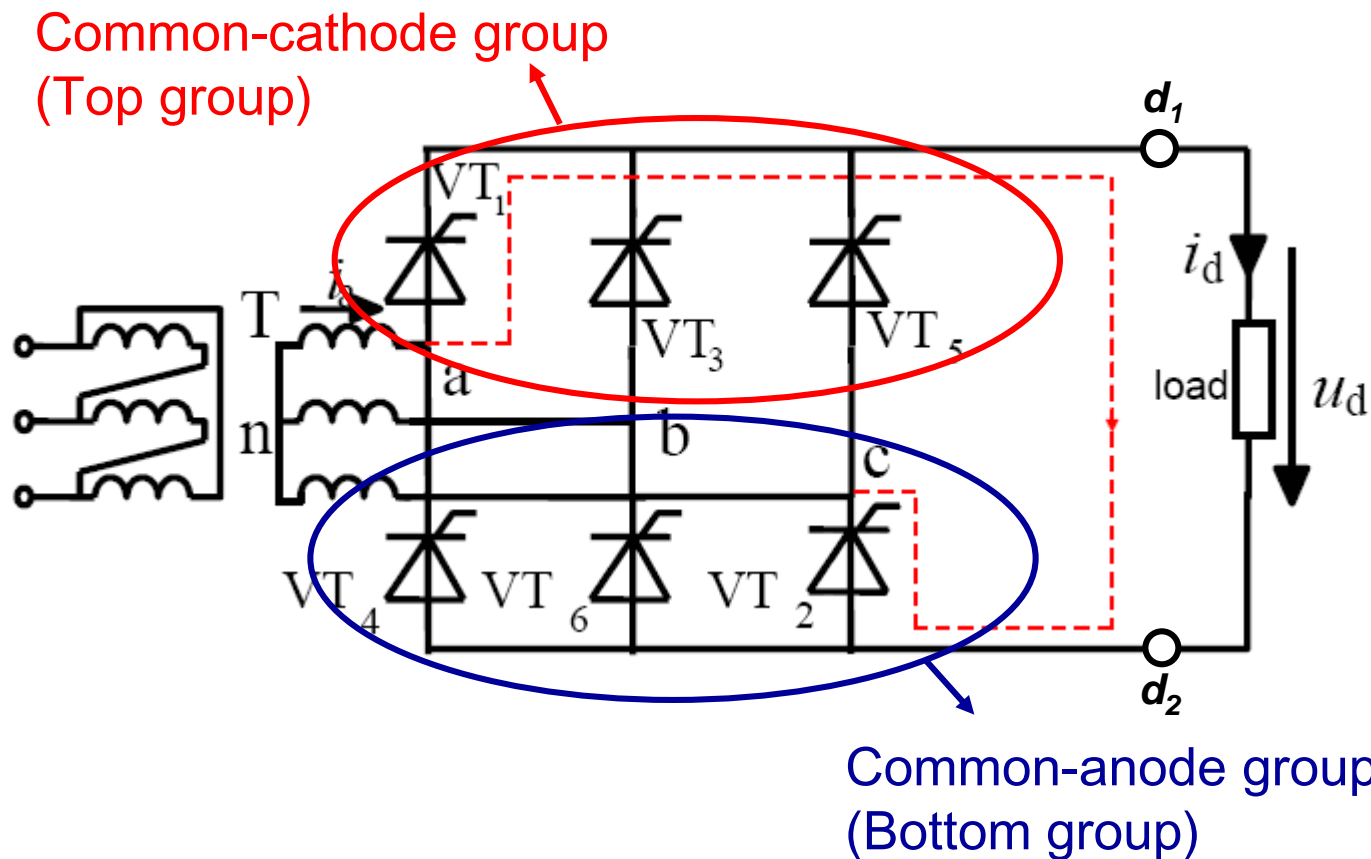2 Three-phase bridge fully-controlled rectifier




- Numbering of the 6 thyristors indicates the trigger sequence:


$$V_{T1} \rightarrow V_{T2} \rightarrow V_{T3} \rightarrow V_{T4} \rightarrow V_{T5} \rightarrow V_{T6}$$

2.1 Resistive load


- Resistive load
 - $\alpha = 0^\circ$

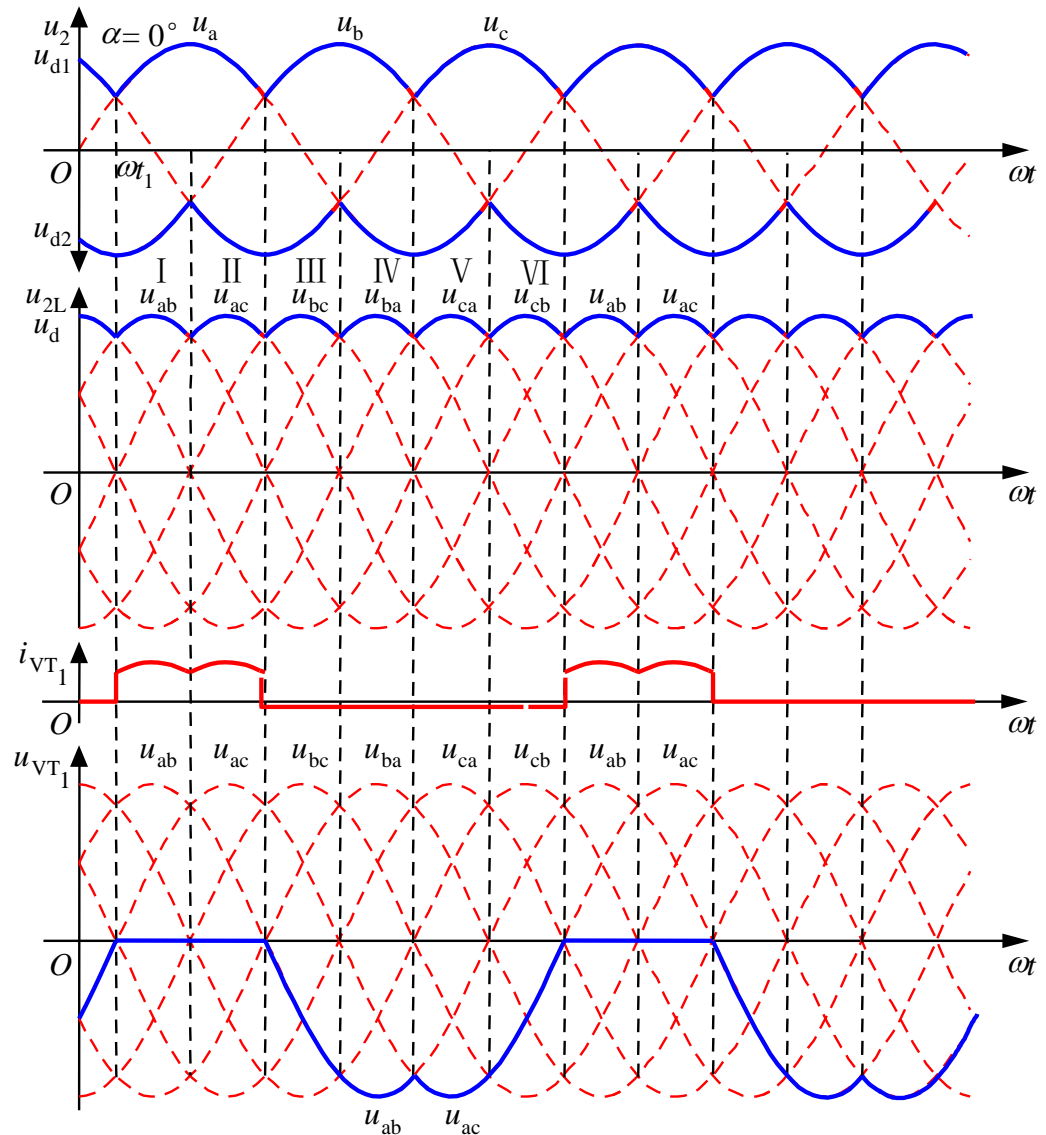


- Resistive load
 - $\alpha = 30^\circ$

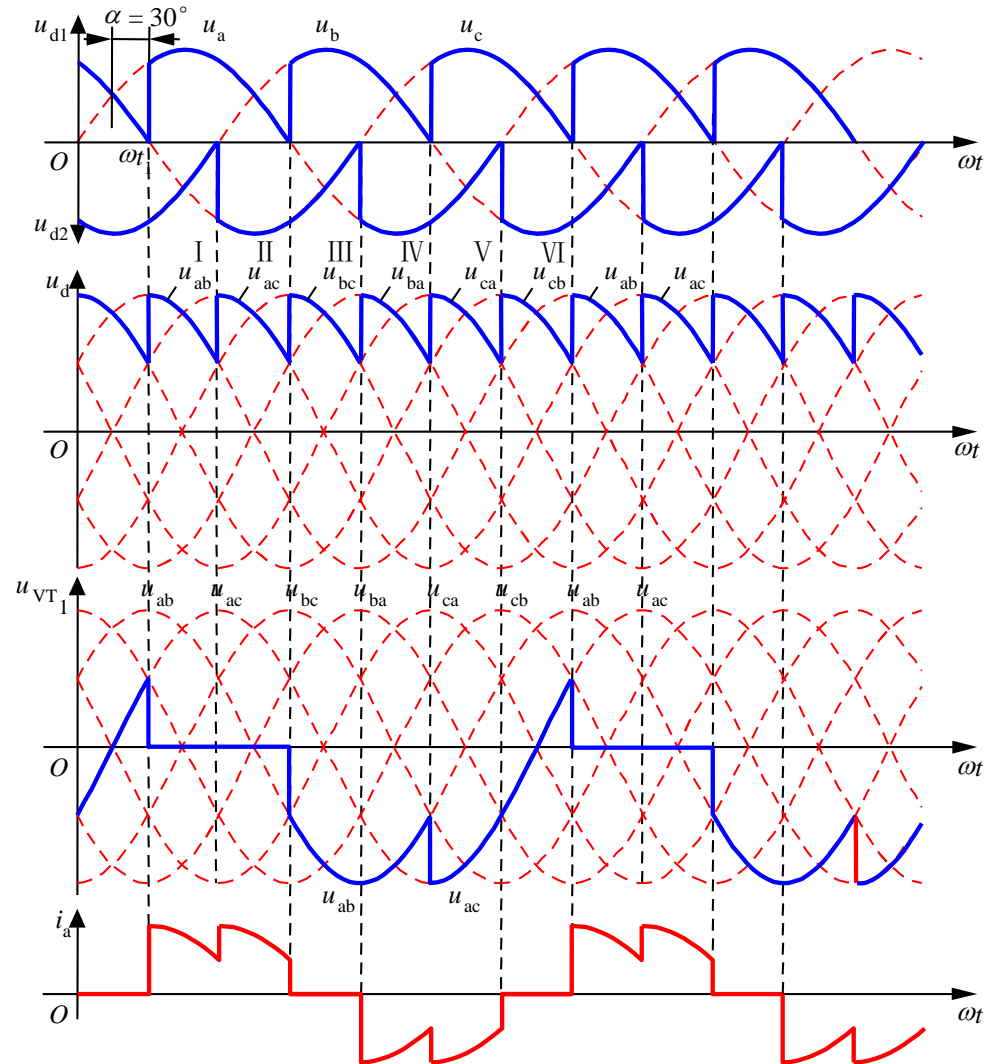

- Resistive load
 - $\alpha = 60^\circ$

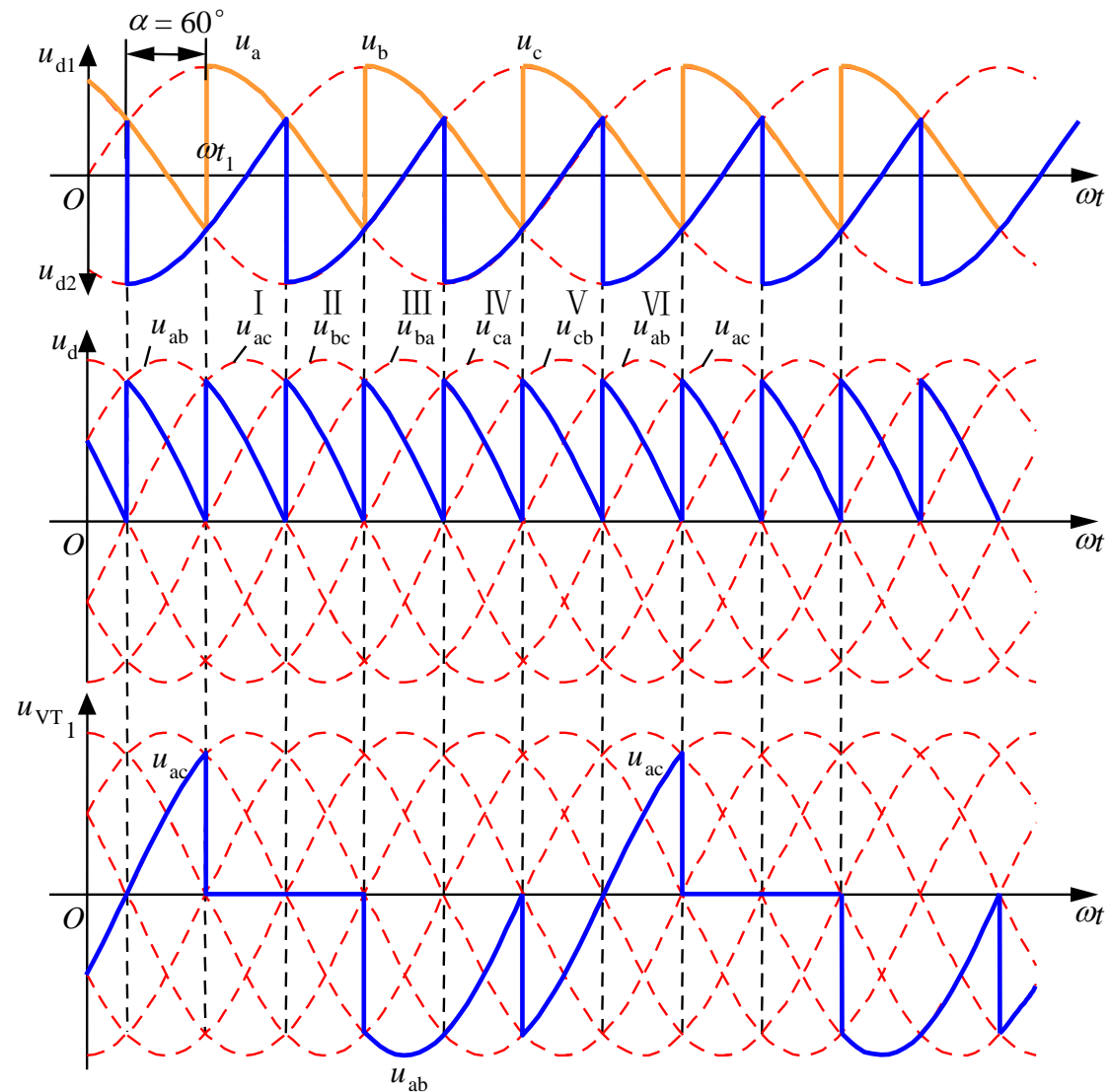

- Resistive load
 - $\alpha = 90^\circ$

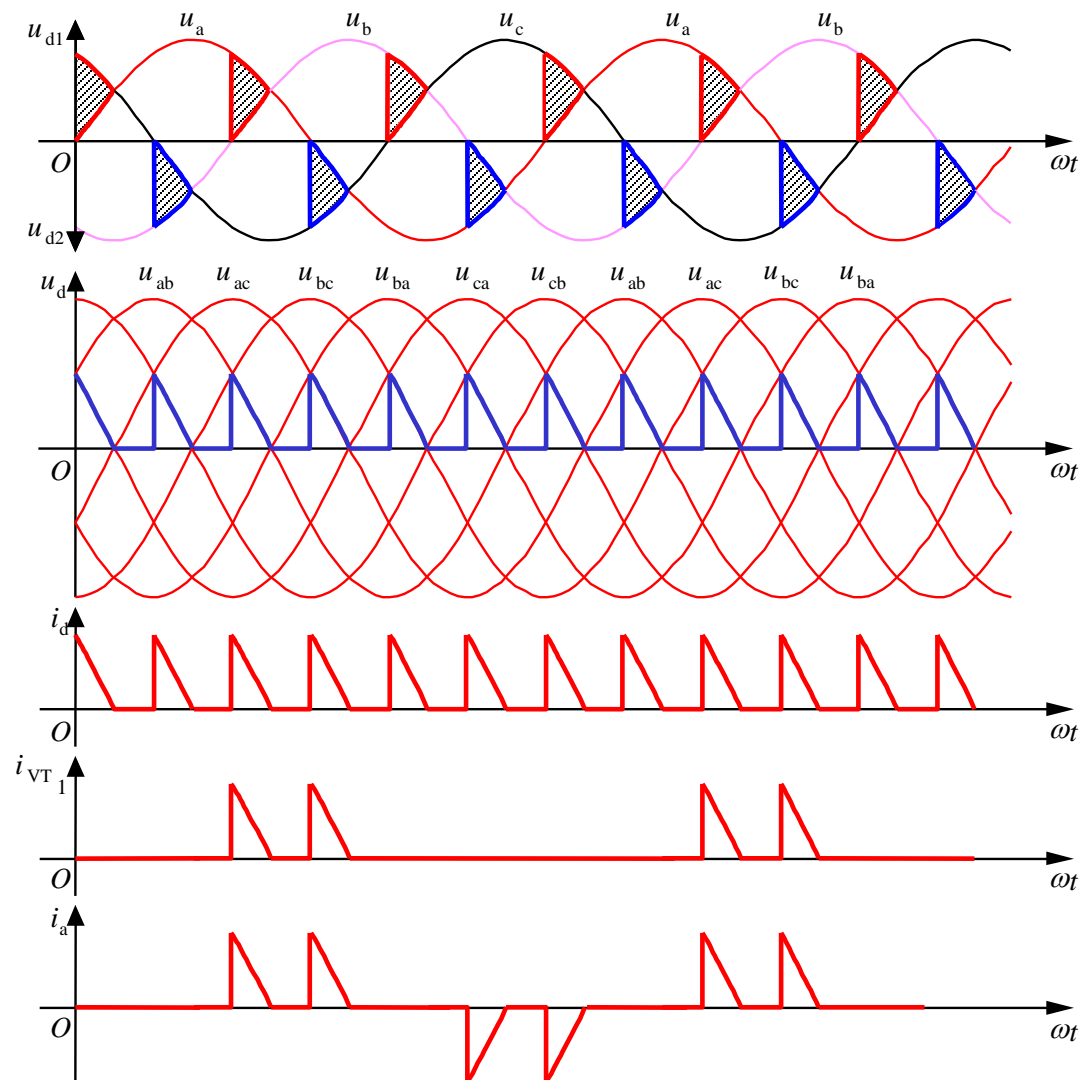


Summary


- Two thyristor from each group (top or bottom group) form the current loop;
- Trigger the two thyristor simultaneously;
- Trigger pulses should be:
 - According the sequence of $V_{T1} \rightarrow V_{T2} \rightarrow V_{T3} \rightarrow V_{T4} \rightarrow V_{T5} \rightarrow V_{T6}$
 - With 60° phase difference
- 6 pulses in one period;
- Voltage waveform across the thyristor is the same as three-phase half-wave circuit, so do the forward and inverse peak voltages.

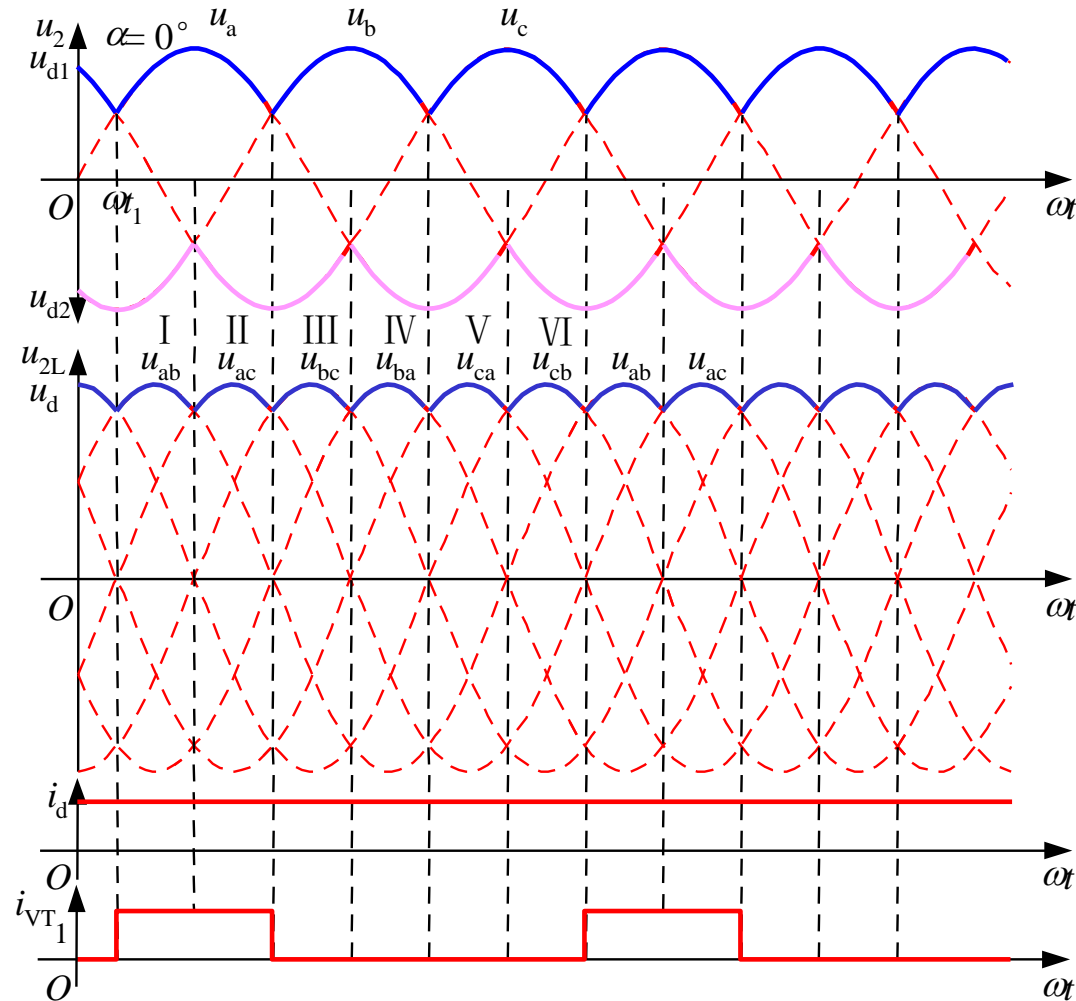2.2 Inductive load


- Inductive load
(R-L load)
 - $\alpha = 0^\circ$



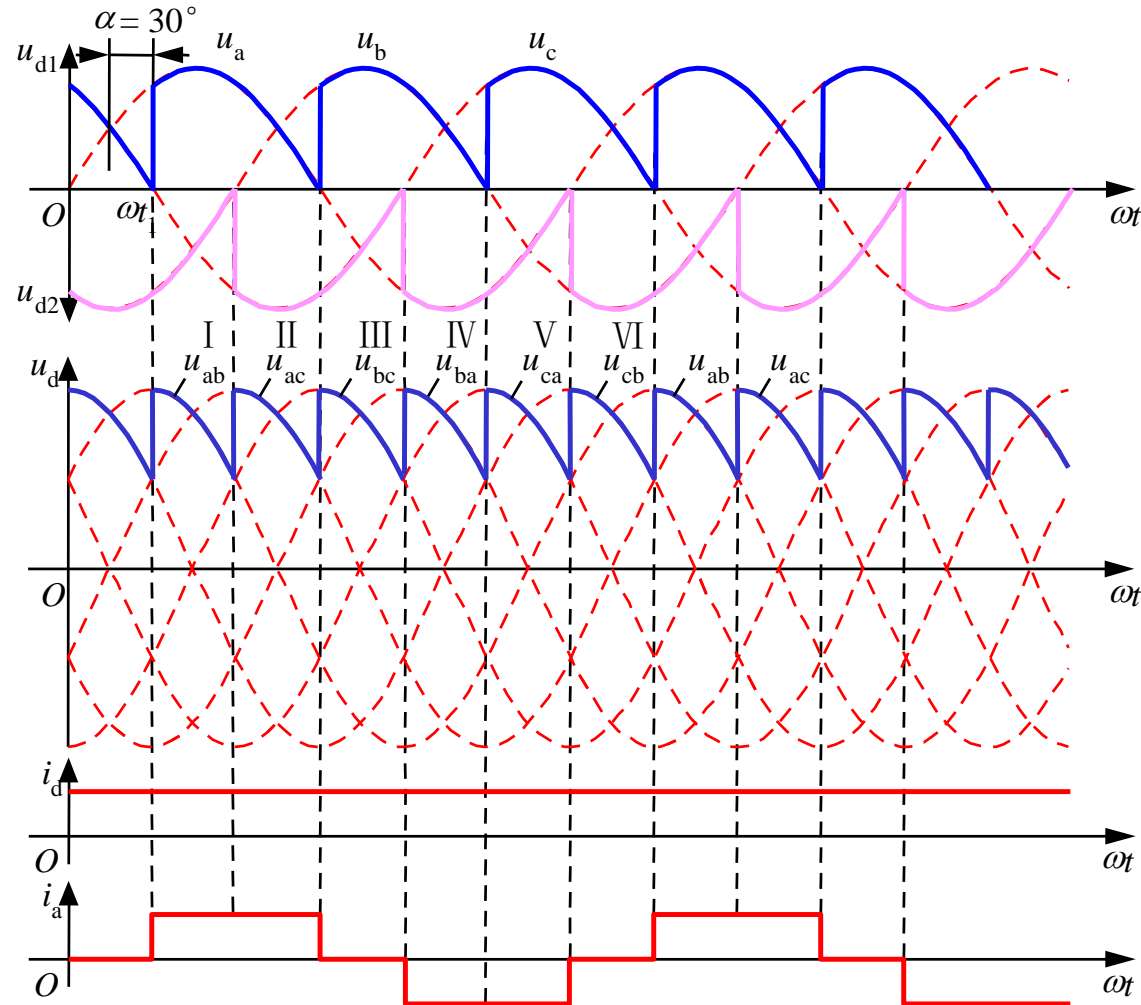
- Inductive load
(R-L load)
– $\alpha = 30^\circ$



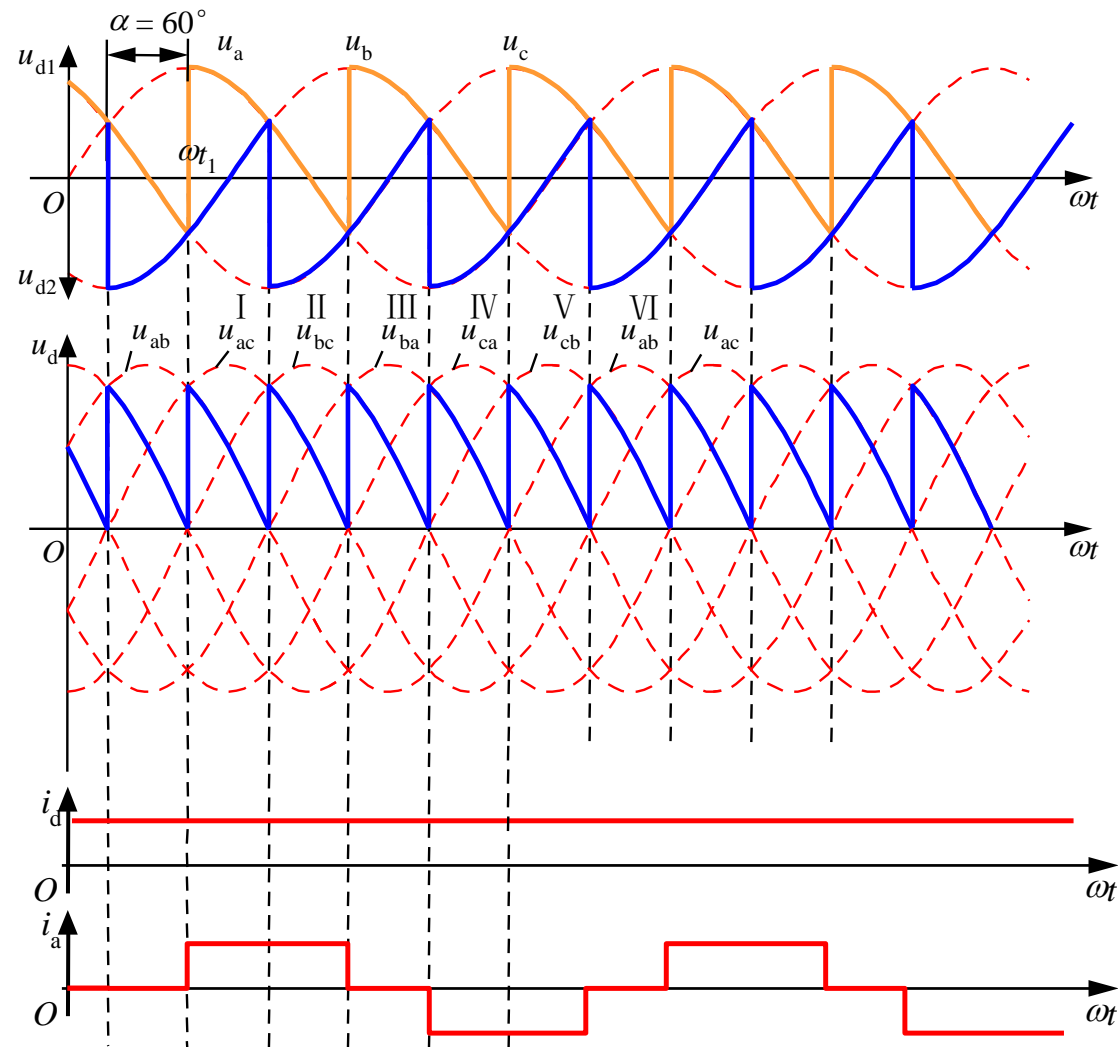
- Inductive load
(R-L load)
– $\alpha = 60^\circ$



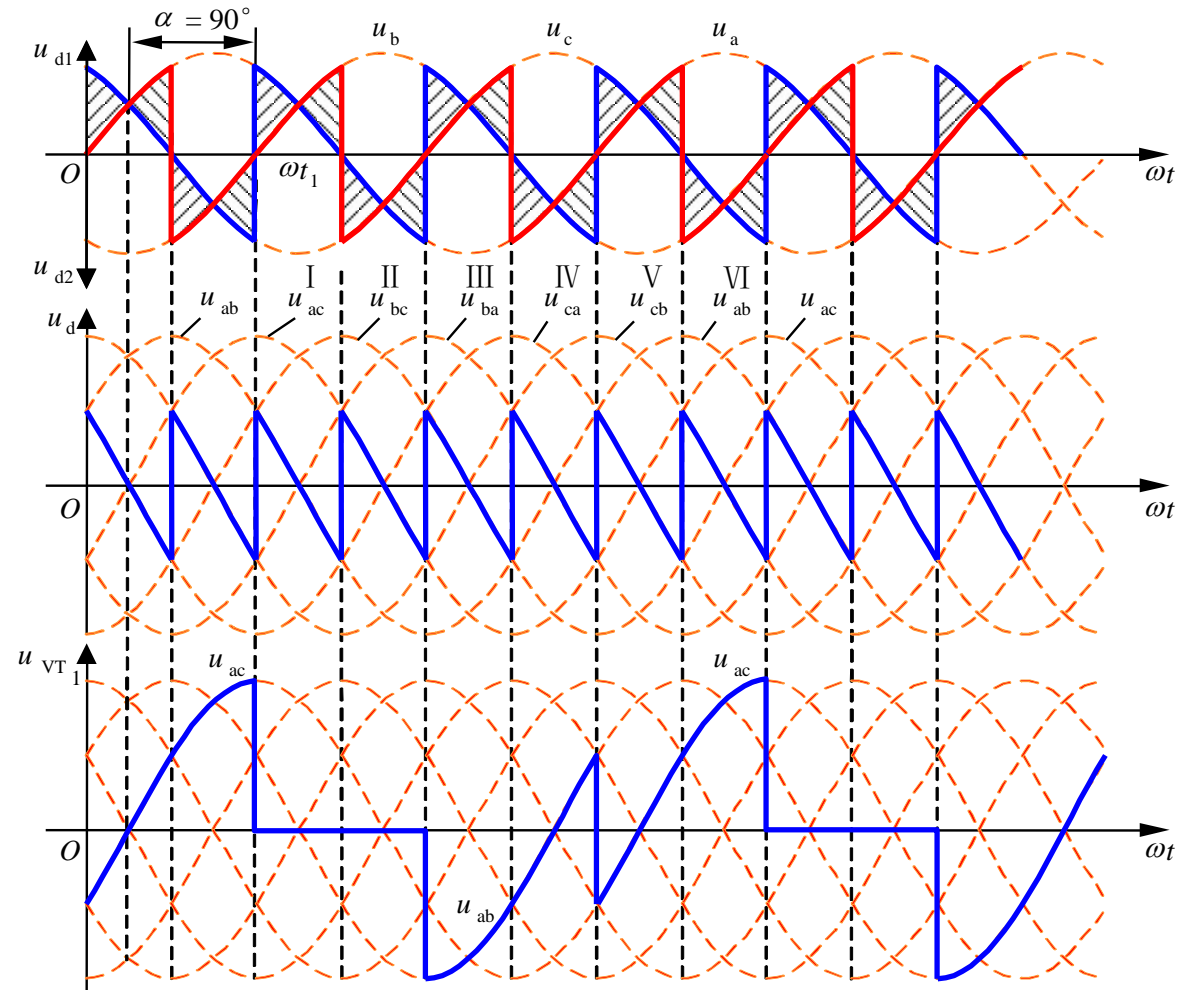
- Inductive load
(R-L load)
– $\alpha = 90^\circ$



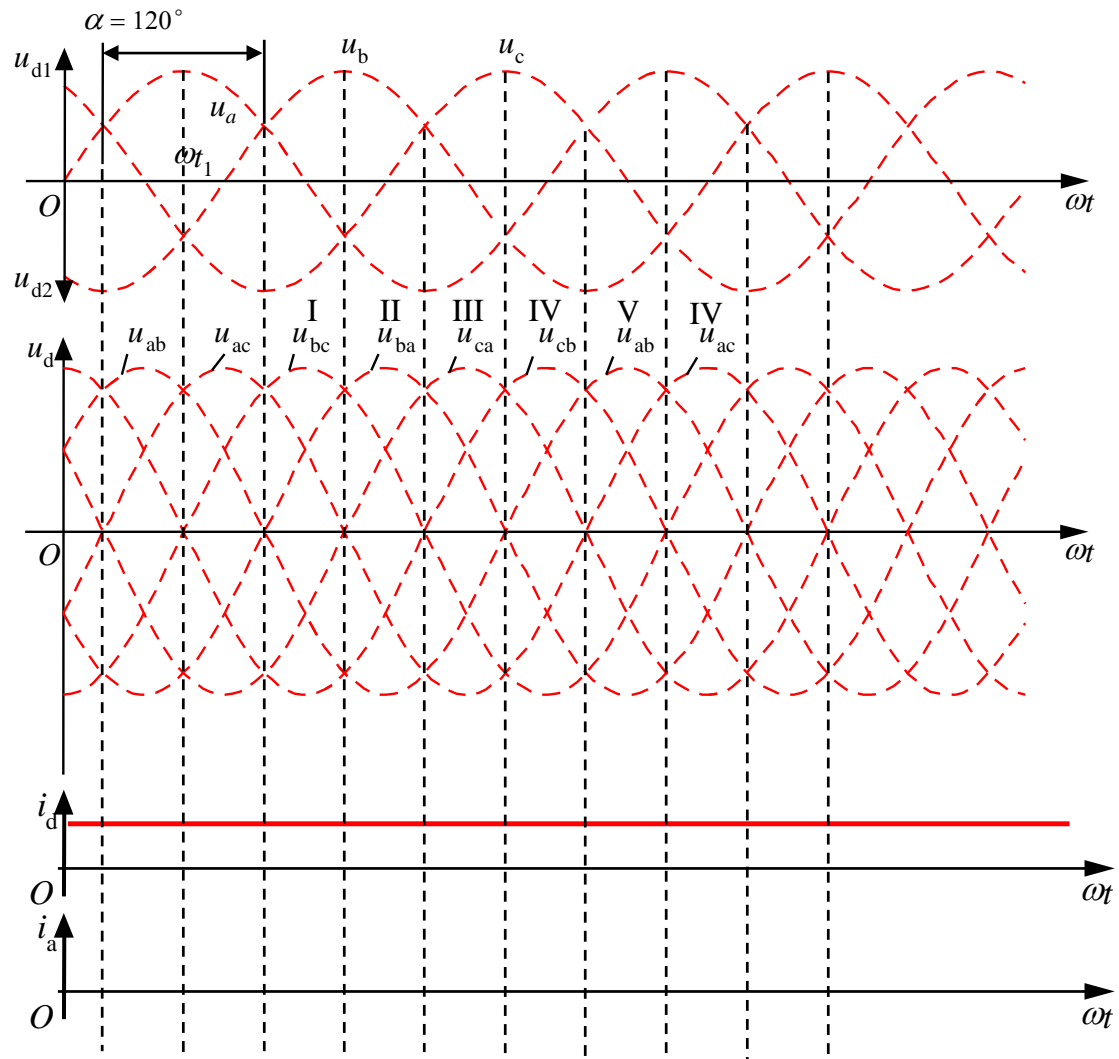- Inductive load
(R-L load)
– $\alpha = 120^\circ$



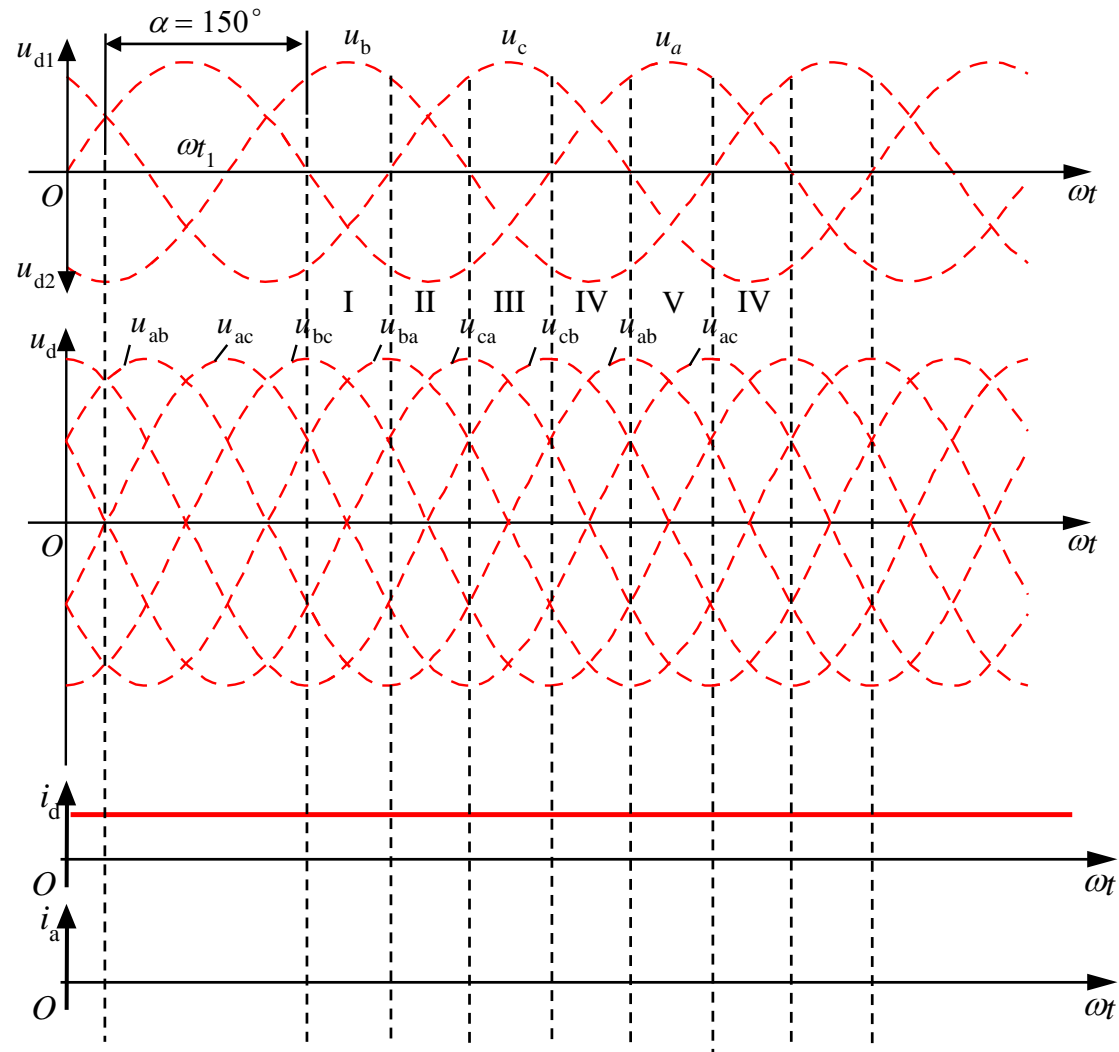- Inductive load
(R-L load)
– $\alpha = 150^\circ$



Quantitative analysis

- Average output voltage

$$U_{d0} = \frac{3}{\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{\pi}{2}+\alpha} v_{ab} d(\omega t) = \frac{3}{\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{\pi}{2}+\alpha} \sqrt{6}U_2 \sin\left(\omega t + \frac{\pi}{6}\right) d(\omega t) = \frac{3\sqrt{6}U_2}{\pi} \cos \alpha = 2.34U_2 \cos \alpha$$

– For resistive load, When $\alpha > 60^\circ$, load current i_d is discontinuous.

$$U_{d0} = \frac{3}{\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}} \sqrt{6}U_2 \sin\left(\omega t + \frac{\pi}{6}\right) d(\omega t) = 2.34U_2 \left[1 + \cos\left(\frac{\pi}{3} + \alpha\right)\right]$$

- RMS output voltage

$$U_{dRMS} = \sqrt{\frac{3}{\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{\pi}{2}+\alpha} \left(\sqrt{6}U_2 \sin\left(\omega t + \frac{\pi}{6}\right)\right)^2 d(\omega t)} = \sqrt{3}U_2 \sqrt{1 + \frac{3\sqrt{3}}{2\pi} \cos 2\alpha}$$

- Average output current (load current) for resistive load

$$I_d = \frac{U_d}{R}$$

- Thyristor voltage and current
 - Same as three-phase half-wave rectifier
- Transformer current

$$I_2 = \sqrt{\frac{1}{2\pi} \left(I_d^2 \times \frac{2\pi}{3} + (-I_d^2) \times \frac{2\pi}{3} \right)} = \sqrt{\frac{2\pi}{3}} I_d = 0.816 I_d$$

- EMF load, L is large enough
 - All the same as inductive load except the calculation of average output current

$$I_d = \frac{U_d - E}{R}$$

