

# nMOS logic IC design

**Material developed by Prof. C. Z. Zhao**

---


## **OUTLINE**

- **nMOS logic (examples)**
  - Truth table
  - Calculation
  - Layout
- **Design Exercise 2017 (15% marks)**

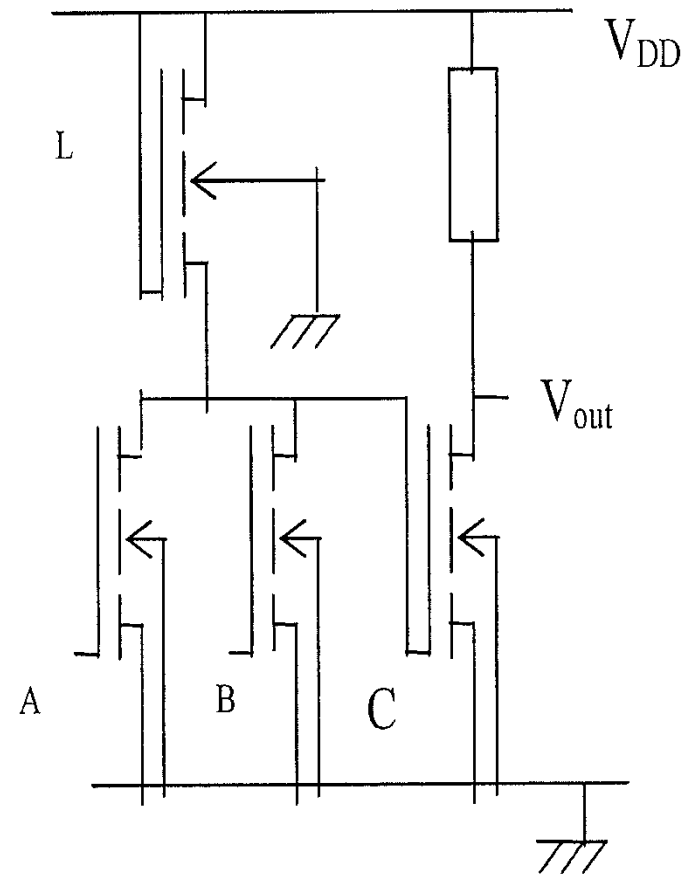
# nMOS IC logic family

---

- Inverters
- NAND gate
- NOR gate
- General gate
  - Complicated gate
  - Example →





# Switch Model of nMOS Transistor PL

 


**If  $V_{GS} = V_{DD}$ , the nMOSFET is on.**

# nMOS Logic (Inverters)

  

$$V_{in} = V_{GS}, V_{out} = V_{DS}$$

# nMOS Logic (Inverter)

 

$V_{in} = V_{DD}$  causes NMOS transistor to be on (in triode). Low effective resistance of transistor causes voltage divider with  $V_{out}$  **near 0V**.


If  $R_L \gg R_D$  (large  $R_L$ )

$$V_{out} = \frac{R_D}{R_L + R_D} V_{DD} \approx 0$$

$$V_{out} \ll V_T$$

$V_{in}$	$V_{out}$
0 (0V)	1 ( $V_{DD}$ )
<b>1 (<math>V_{DD}</math>)</b>	<b>0 (0V)</b>

# nMOS Logic (Inverter)

 

$V_{in} = V_{DD}$  causes NMOS transistor to be on (in triode). Low effective resistance of transistor causes voltage divider with  $V_{out}$  **near 0V**.


$$V_{out} = \frac{R_D}{R_L + R_D} V_{DD} \approx 0$$

$V_{in} = 0V$  causes NMOS transistor to be off (cutoff). High effective resistance of transistor causes voltage divider with  $V_{out}$  **near  $V_{DD}$** .

$V_{in}$	$V_{out}$
<b>0 (0V)</b>	<b>1 (<math>V_{DD}</math>)</b>
1 ( $V_{DD}$ )	0 (0V)

$$V_{out} \approx V_{DD} \quad \text{If } V_{in} \ll V_T$$

# nMOS Logic (NAND)

 


$V_1$	$V_2$	$V_{out}$
0	0	1
0	1	1
1	0	1
1	1	0

$V_1 = V_2 = 10V$  causes both NMOS transistors to be on (in triode). Low effective resistance of transistors causes voltage divider with  $V_{out}$  **near** 0V.

$V_1 = 0V$  or  $V_2 = 0V$  (or both) cause one or both NMOS transistors to be off (cutoff). High effective resistance of series transistors cause voltage divider with  $V_{out}$  near 10V.

# nMOS Logic (NAND)

 

$V_1 = V_2 = 10V$  causes both NMOS transistors to be on (in triode). Low effective resistance of transistors causes voltage divider with  $V_{out}$  **near** 0V.


$$V_{out} = \frac{R_1 + R_2}{R_L + R_1 + R_2} V_{DD} \approx 0 \text{ (Large } R_L \text{)}$$

$V_1$	$V_2$	$V_{out}$
0	0	1
0	1	1
1	0	1
<b>1</b>	<b>1</b>	<b>0</b>





# nMOS Logic (NAND)

 

$V_1 = V_2 = 10\text{V}$  causes both NMOS transistors to be on (in triode). Low effective resistance of transistors causes voltage divider with  $V_{out}$  **near** 0V.

$$V_{out} = \frac{R_1 + R_2}{R_L + R_1 + R_2} V_{DD} \approx 0 \quad (\text{Large } R_L)$$

$V_1 = 0\text{V}$  or  $V_2 = 0\text{V}$  (or both) cause one or both NMOS transistors to be off (cutoff).


High effective resistance of series transistors cause voltage divider with  $V_{out}$  **near** 10V.

$$V_{out} \approx V_{DD}$$

$V_1$	$V_2$	$V_{out}$
0	0	1
<b>0</b>	<b>1</b>	<b>1</b>
1	0	1
1	1	0

# nMOS Logic (NOR)


$V_1$	$V_2$	$V_{out}$
0	0	1
0	1	0
1	0	0
1	1	0

 

# nMOS Logic (NOR)

$$V_{out} \approx V_{DD}$$


$V_1$	$V_2$	$V_{out}$
<b>0</b>	<b>0</b>	<b>1</b>
0	1	0
1	0	0
1	1	0

 

# nMOS Logic (NOR)


$$V_{out} = \frac{R_1}{R_L + R_1} V_{DD} \approx 0 \text{ (Large } R_L \text{)}$$

$V_1$	$V_2$	$V_{out}$
0	0	1
0	1	0
<b>1</b>	<b>0</b>	<b>0</b>
1	1	0

 

# nMOS Logic (General)

---

 



Any combination of inputs  $V_1 V_2 \dots V_n$  that should result in an output of 0 should produce a low-resistance path from  $V_{out}$  to ground in the pull-down network.

Any combination of inputs that does not pull the output  $V_{out}$  to ground through the network will result in the output pulled high through the pull-up resistor  $R_D$ .


NMOS logic draws current continuously when  $V_{out}$  is low.

# nMOS Logic (General)

Example:

  

# Example: Design Exercise 2016

 

- It consists of an n channel NOR gate feeding an inverter.
- The transistors A and B are the termed driver MOSFETs.
- The process parameters are defined:

➤  $2\lambda = 1\mu\text{m}$

➤  $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$



➤  $V_T = 0.3\text{V}$

➤  $V_{DD} = 5\text{V}$


➤  $V_{in} = V_{DD}$

➤  $R_S = 100\Omega$

$V_A$	$V_B$	$V_C$	$V_C$	$V_{out}$
0	0	1	1	0
0	1	0	0	1
1	0	0	0	1
1	1	0	0	1

  


# Example 2016

 

- It consists of an n channel NOR gate feeding an inverter.
- The transistors A and B are the termed driver MOSFETs.
- The process parameters are defined:


- $2\lambda = 1\mu\text{m}$
- $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$
- $V_T = 0.3\text{V}$
- $V_{DD} = 5\text{V}$
- $V_{in} = V_{DD}$
- $R_S = 100\Omega$

$V_A$	$V_B$	$V_C$	$V_C$	$V_{out}$
0	0	1	1	0
0	1	0	0	1
1	0	0	0	1
1	1	0	0	1

 



# Example 2016

 

- It consists of an n channel NOR gate feeding an inverter.
- The transistors A and B are the termed driver MOSFETs.
- The process parameters are defined:

➤  $2\lambda = 1\mu\text{m}$

➤  $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$



➤  $V_T = 0.3\text{V}$

➤  $V_{DD} = 5\text{V}$

➤  $V_{in} = V_{DD}$

➤  $R_S = 100\Omega$

$V_A$	$V_B$	$V_C$	$V_{out}$
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

  

# OUTLINE

---

- **nMOS logic (examples)**
  - Truth table
  - **Calculation**
  - Layout
- Design Exercise 2017 (15% marks)

# nMOS Logic (Inverter): example1

Calculate  $W/L$  with the following specification:

- 1)  $R_L = 5k$ .
- 2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \cdot 10^{-4} \text{AV}^{-2}$ .
- 3)  $V_T = 0.3\text{V}$ .
- 4)  $V_{DD} = 5\text{V}$ .

**Solution:** The output of the driver when it is switched on must be significantly less than  $V_T$  say  $0.1\text{V}$ , that is, let  $V_{\text{out}} = 0.1\text{V}$ :

$$I_D = \beta[(V_G - V_T)V_D - V_D^2/2] \approx \beta[(V_G - V_T)V_D]$$

$$\text{or } I_D = \beta[(V_{DD} - V_T)V_{\text{out}}].$$

The effective resistance of the driver ( $R_D$ ) between source and drain is, therefore:

$$R_D = V_{\text{out}}/I_D = (\beta[(V_{DD} - V_T)])^{-1}$$

it is obtained as a potential divider


$$[R_D/(R_D + R_L)] = V_{\text{out}}/V_{DD} = 0.1/5 = 0.02 \text{ so } R_D \ll R_L$$

$$\text{and } R_L/R_D = 1/0.02 = 50 \rightarrow \mathbf{R_D = 100\Omega}$$

$$R_D = 1/[\beta(V_G - V_T)] = 1/[\beta(5 - 0.3)] = 100\Omega$$



$$\rightarrow \beta \approx 20 \cdot 10^{-4}$$

 Therefore, the aspect ratio,  $W/L$ , is 12.



# Transistor in Linear Mode

Assuming  $V_{GS} > V_T$

 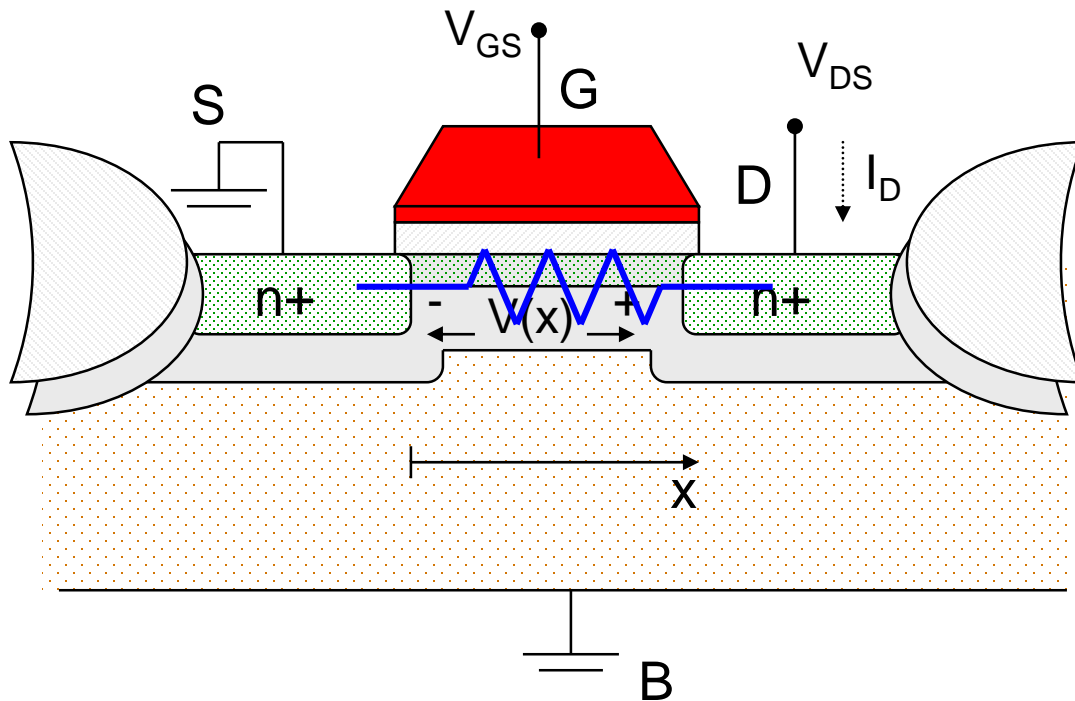

When  $V_{DS} \leq V_{GS} - V_T$ :  $I_D = \beta_0 W/L [(V_{GS} - V_T)V_{DS} - V_{DS}^2/2]$



$$\beta_0 = \mu_n C_{ox}$$

$$R = V_{DS} / I_D$$

# Transistor in Saturation Mode

PL

Assuming  $V_{GS} > V_T$

 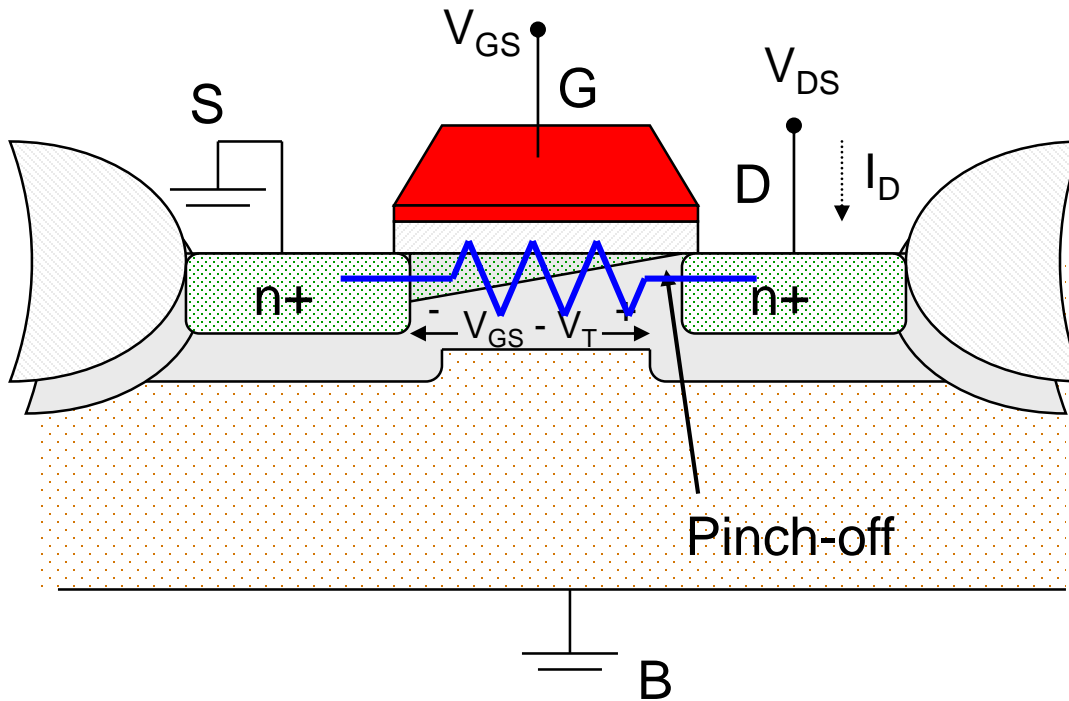

When  $V_{DS} \geq V_{GS} - V_T$  :  $I_D = (\beta_0/2) W/L [(V_{GS} - V_T)^2]$

$$R = V_{DS} / I_D$$


# nMOS Logic (Inverter): example1

Calculate  $W/L$  with the following specification:


- 1)  $R_L = 5k$ . 2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \times 10^{-4} A V^{-2}$ .  
3)  $V_T = 0.3V$ . 4)  $V_{DD} = 5V$ .

$$\beta_0 = \mu C_{ox}$$

**The aspect ratio,  $W/L$ , is ??**

 

Layout(版图)

 

# nMOS Logic (Inverter): example1

Calculate W/L with the following specification:

- 1)  $R_L = 5k$ .
- 2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \times 10^{-4} A V^{-2}$ .
- 3)  $V_T = 0.3V$ .
- 4)  $V_{DD} = 5V$ .

**Solution:**

If  $V_{in} = V_{DD}$ , let  $V_{out} = 0.1V \ll V_T$

**Potential divider:**


$$R_D / (R_D + R_L) = V_{out} / V_{DD} = 0.1 / 5 = 0.02$$

$$\rightarrow R_D \approx 100\Omega$$

$$I_D = \beta[(V_G - V_T)V_D - V_D^2/2] \approx \beta[(V_G - V_T)V_D]$$

$$R_D = V_{out} / I_D = \{\beta[(V_{DD} - V_T)]\}^{-1} = 1 / [\beta(5 - 0.3)] = 100\Omega$$

 $\rightarrow \beta \approx 20 \times 10^{-4}$ . Therefore, the aspect ratio, W/L, is 12.





# nMOS Logic (Inverter): example1

Calculate  $W/L$  with the following specification:

- 1)  $R_L = 5k$ .
- 2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \cdot 10^{-4} \text{AV}^{-2}$ .
- 3)  $V_T = 0.3\text{V}$ .
- 4)  $V_{DD} = 5\text{V}$ .

$$W/L = 12$$

  





# nMOS Logic (Inverter): example1

Calculate  $W/L$  with the following specification:


- 1)  $R_L = 5k$ .
- 2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \cdot 10^{-4} \text{AV}^{-2}$ .
- 3)  $V_T = 0.3\text{V}$ .
- 4)  $V_{DD} = 5\text{V}$ .

$$W/L = 12$$

  
 
# Example: Design Exercise 2016

- It consists of an n channel NOR gate feeding an inverter.
- The transistors A and B are the termed driver MOSFETs.
- The process parameters are defined:
  - $2\lambda = 1\mu\text{m}$
  - $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$
  - $V_T = 0.3\text{V}$
  - $V_{DD} = 5\text{V}$
  - $V_{in} = V_{DD}$
  - $R_s = 100\Omega/\text{sq}$
- HINTS: Liverpool notes.



# nMOS Logic (Inverter): example2

Calculate W/L of Load with the following specification:

**1) The aspect ratios of D is 12.**

2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$ .

3)  $V_T = 0.3\text{V}$ . 4)  $V_{DD} = 5\text{V}$ .

**Solution:** The output of the driver when it is switched on is  $V_{\text{out}} = 0.1\text{V}$ :

$$I_D = \beta[(V_{DD} - V_T)V_{\text{out}}].$$

The effective resistance of the driver is,

$$R_D = V_{\text{out}}/I_D = (\beta_D[(V_{DD} - V_T)])^{-1} = 100 \, \Omega$$

$R_L$  is obtained as a potential divider

$$[R_D/(R_D + R_L)] = V_{\text{out}}/V_{DD} = 0.1/5 = 0.02 \text{ so}$$


$$R_D \ll R_L \text{ and } R_L/R_D = 1/0.02 = 50$$

→  **$R_L = 5\text{k}\Omega$**  and the load current

- $I_D = \beta_L/2 (V_{DD} - V_T)^2$

$$R_L = (V_{DD} - V_{\text{out}})/I_D = 5 \times 2 / [\beta_L(5 - 0.3)^2] = 5\text{k}\Omega$$

 →  $\beta_L = 1 \times 10^{-4} \rightarrow$  aspect ratio of Load = **0.5**






# nMOS Logic (Inverter): example2

Calculate W/L of Load with the following specification:

**1) The aspect ratios of D is 12.**

2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$ .

   3)  $V_T = 0.3\text{V}$ . 4)  $V_{DD} = 5\text{V}$ .



# nMOS Logic (Inverter): example2

Calculate W/L of Load with the following specification:

1) The aspect ratios of D is 12.

2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$ .

3)  $V_T = 0.3\text{V}$ . 4)  $V_{DD} = 5\text{V}$ .

**Solution:**

If  $V_{in} = V_{DD}$ , let  $V_{out} = 0.1\text{V}$ :

$$I_D = \beta_D [(V_{in} - V_T)V_{out} - V_{out}^2/2]$$

$$R_D = V_{out}/I_D = (12\beta_0[(V_{DD} - V_T)])^{-1} = 100 \Omega$$


$$[R_D/(R_D + R_L)] = V_{out}/V_{DD} = 0.1/5 = 0.02$$

$$\rightarrow R_L \approx 5\text{k}\Omega$$

$$I_D = \beta_L (V_{DD} - V_T)^2/2$$

$$R_L = (V_{DD} - V_{out})/I_D = 4.9 \times 2 / [\beta_L (5 - 0.3)^2] = 5\text{k}\Omega$$
 
$$\rightarrow \beta_L = 8.9 \times 10^{-5} \rightarrow \text{aspect ratio of load} = \underline{0.5}$$





# nMOS Logic (Inverter): example2

Calculate W/L of Load with the following specification:

- 1) The aspect ratios of D is 12.
- 2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$ .
- 3)  $V_T = 0.3\text{V}$ . 4)  $V_{DD} = 5\text{V}$ .

**W/L of Load = 0.5**

 
 


# nMOS Logic (Inverter): example2

Calculate  $W/L$  of Load with the following specification:

- 1) **The aspect ratios of D is 12.**
- 2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \cdot 10^{-4} \text{AV}^{-2}$ .
- 3)  $V_T = 0.3\text{V}$ . 4)  $V_{DD} = 5\text{V}$ .

$$W/L = 0.5$$

 
 


# nMOS Logic (Inverter): example2

Calculate  $W/L$  of Load with the following specification:

- 1) **The aspect ratios of D is 12.**
- 2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \cdot 10^{-4} \text{AV}^{-2}$ .
- 3)  $V_T = 0.3\text{V}$ . 4)  $V_{DD} = 5\text{V}$ .

$$W/L = 0.5$$

  



# nMOS Logic (NOR): example3

Calculate W/L of Load with the following specification:

1) The aspect ratios of D is 12.

2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$ .

3)  $V_T = 0.3\text{V}$ . 4)  $V_{DD} = 5\text{V}$ .

**Solution:**

let  $V_{out} = 0.1\text{V}$ :

$$I_D = \beta_D [(V_{inA} - V_T)V_{out} - V_{out}^2/2]$$

$$R_D = V_{out}/I_D = (\beta_D [(V_{DD} - V_T)])^{-1} = 100 \Omega$$


$$[0.5R_D / (0.5R_D + R_L)] = V_{out}/V_{DD} = 0.1/5 = 0.02$$

$$\rightarrow R_L = 2.5\text{k}\Omega$$

$$I_D = \beta_L (V_{DD} - V_T)^2/2$$


$$R_L = (V_{DD} - V_{out})/I_D = 4.9 \times 2 / [\beta_L (5 - 0.3)^2] = 2.5\text{k}\Omega$$
 
$$\rightarrow \beta_L = 1.8 \times 10^{-4} \rightarrow \text{aspect ratio of Load} = 1.$$


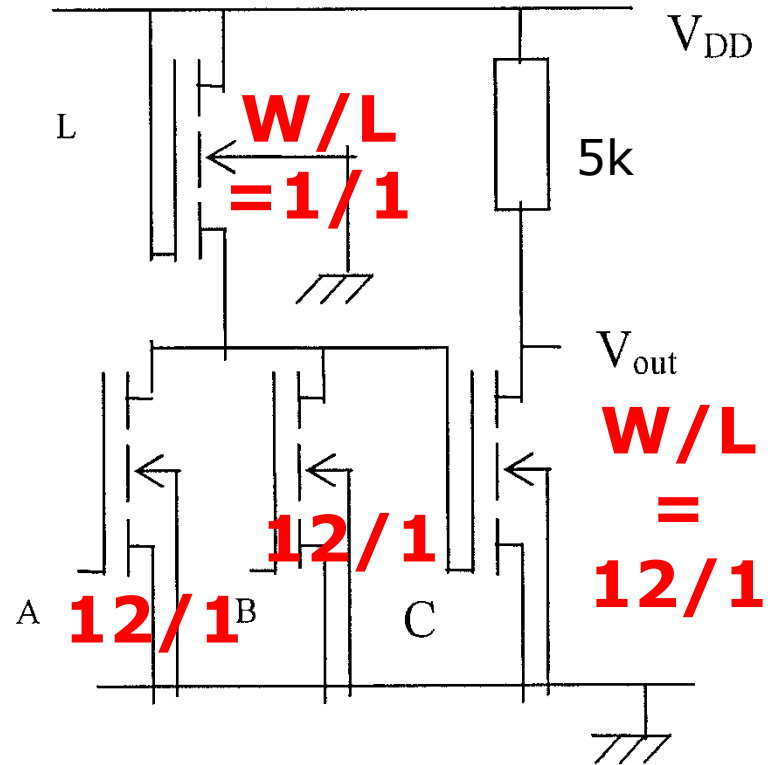
# Example: Design Exercise 2016

- It consists of an n channel NOR gate feeding an inverter.
- The transistors A and B are the termed driver MOSFETs.
- The process parameters are defined:
  - $2\lambda = 1\mu\text{m}$
  - $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$
  - $V_T = 0.3\text{V}$
  - $V_{DD} = 5\text{V}$
  - $V_{in} = V_{DD}$
  - $R_s = 100\Omega/\text{sq}$
- HINTS: Liverpool notes.



# Design Exercise 2017

## Layout design of the nMOS IC shown in Fig.1

- It consists of an n channel NOR gate feeding an inverter.
- The transistors A and B are the termed driver MOSFETs.
- The process parameters are defined:

➤  $2\lambda = 1\mu\text{m}$

➤  $\beta_0 = 1.8 \times 10^{-4} \text{A V}^{-2}$

➤  $V_T = 0.3\text{V}$

➤  $V_{DD} = 5\text{V}$

➤  $V_{in} = V_{DD}$

➤  $R_S = 100\Omega/\text{sq}$

$$\mu C_{ox} = \beta_0$$

 


Fig.1

# nMOS Logic (NOR): example4

Calculate  $W/L$  with the following specification:

- 1)  $R_L = 5k$ .
- 2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$ .
- 3)  $V_T = 0.3\text{V}$ .
- 4)  $V_{DD} = 5\text{V}$ .

**Solution:**

If  $V_A = V_B = V_{DD}$ , let  $V_{out} = 0.1\text{V} \ll V_T$

**Potential divider:**


$$0.5R_D / (0.5R_D + R_L) = V_{out} / V_{DD} = 0.1 / 5 = 0.02$$

$$\rightarrow R_D \approx 200\Omega$$

$$I_D = \beta[(V_G - V_T)V_D - V_D^2/2] \approx \beta[(V_G - V_T)V_D]$$

$$R_D = V_{out} / I_D = \{\beta[(V_{DD} - V_T)]\}^{-1} = 1 / [\beta(5 - 0.3)] = 200\Omega$$

 $\rightarrow \beta \approx 10 \times 10^{-4}$ . Therefore, the aspect ratio,  $W/L$ , is 6.



# Design Exercise 2017

## Layout design of the nMOS IC shown in Fig.1

- It consists of an n channel NOR gate feeding an inverter.
- The transistors A and B are the termed driver MOSFETs.
- The process parameters are defined:

- $2\lambda = 1\mu\text{m}$
- $\beta_0 = 1.8 \times 10^{-4} \text{A V}^{-2}$
- $V_T = 0.3\text{V}$
- $V_{DD} = 5\text{V}$
- $V_{in} = V_{DD}$
- $R_S = 100\Omega/\text{sq}$

 


Fig.1

# nMOS Logic (Inverter): example5

Calculate W/L of Load with the following specification:

- 1) The aspect ratios of D is **6**.
- 2)  $\beta = \beta_0(W/L)$ , and  $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$ .
- 3)  $V_T = 0.3\text{V}$ . 4)  $V_{DD} = 5\text{V}$ .

**Solution:**

If  $V_{in} = V_{DD}$ , let  $V_{out} = 0.1\text{V}$ :

$$I_D = \beta_D [(V_{in} - V_T)V_{out} - V_{out}^2/2]$$

$$R_D = V_{out}/I_D = (6\beta_0[(V_{DD} - V_T)])^{-1} = 200 \Omega$$


$$[R_D/(R_D + R_L)] = V_{out}/V_{DD} = 0.1/5 = 0.02$$

$$\rightarrow R_L \approx 10\text{k}\Omega$$

$$I_D = \beta_L (V_{DD} - V_T)^2/2$$

$$R_L = (V_{DD} - V_{out})/I_D = 4.9 \times 2 / [\beta_L (5 - 0.3)^2] = 10\text{k}\Omega$$
 
$$\rightarrow \beta_L = 4.4 \times 10^{-5} \rightarrow \text{aspect ratio of load} = \underline{\underline{0.25}}$$



# Design Exercise 2017

## Layout design of the nMOS IC shown in Fig.1

- It consists of an n channel NOR gate feeding an inverter.
- The transistors A and B are the termed driver MOSFETs.
- The process parameters are defined:

- $2\lambda = 1\mu\text{m}$
- $\beta_0 = 1.8 \times 10^{-4} \text{A V}^{-2}$
- $V_T = 0.3\text{V}$
- $V_{DD} = 5\text{V}$
- $V_{in} = V_{DD}$
- $R_S = 100\Omega/\text{sq}$

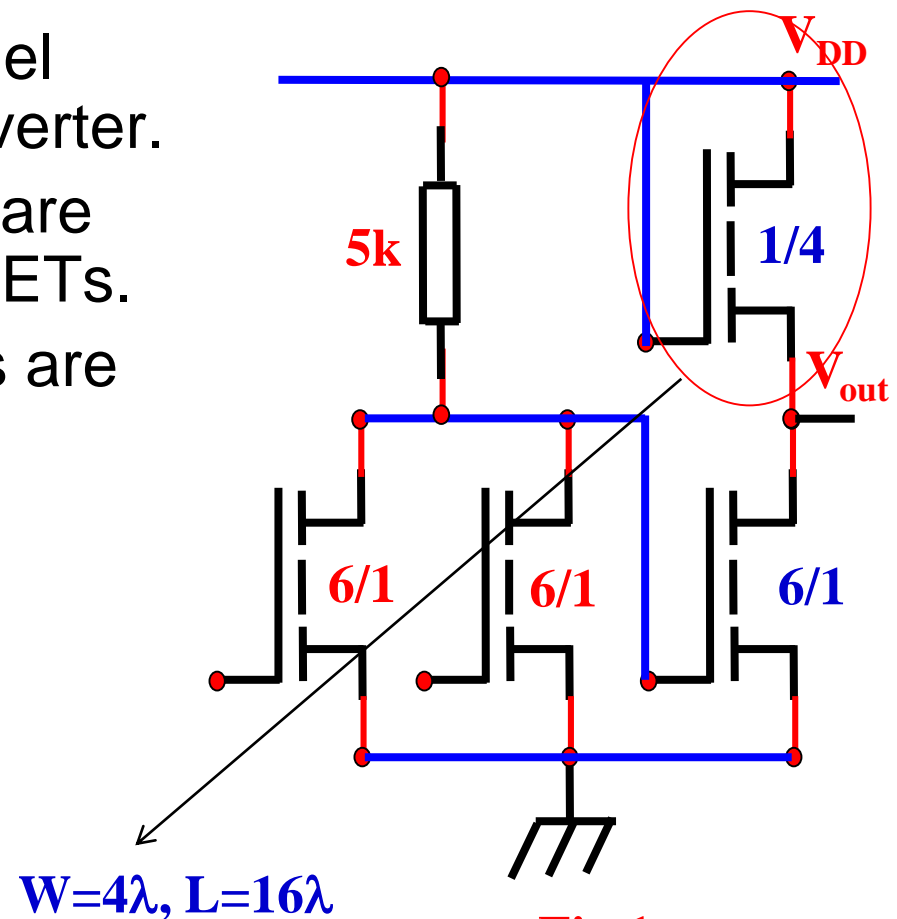


Fig.1

# Design Exercise 2017

## Layout design of the nMOS IC shown in Fig.1

- It consists of an n channel NOR gate feeding an inverter.
- The transistors A and B are the termed driver MOSFETs.
- The process parameters are defined:

- $2\lambda = 1\mu\text{m}$
- $\beta_0 = 1.8 \times 10^{-4} \text{A V}^{-2}$
- $V_T = 0.3\text{V}$
- $V_{DD} = 5\text{V}$
- $V_{in} = V_{DD}$
- $R_S = 100\Omega/\text{sq}$

 


Fig.1





# OUTLINE


---

- **nMOS logic (examples)**
  - Truth table
  - Calculation
  - **Layout**
- Design Exercise 2017 (15% marks)


# nMOS Logic (Inverter): example1

  


# nMOS Logic (Inverter): example1

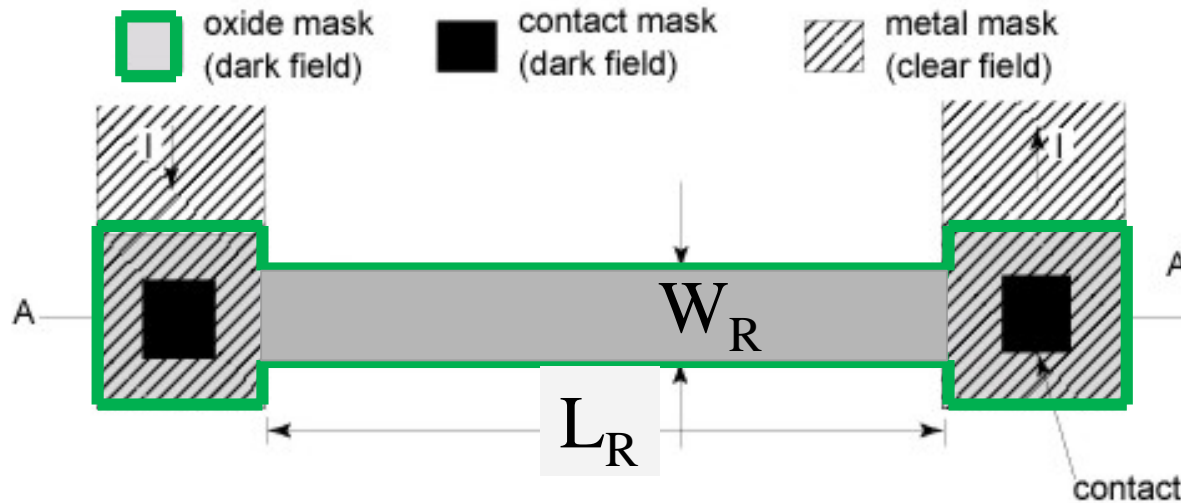

 For small  $L_R/W_R$ :  
(e.g.  $L_R/W_R=9$ )




 For large  $L_R/W_R$ :  
(e.g.  $L_R/W_R=20$ )



$2\lambda \times 2\lambda$


0.5 

 

**$W/L$   
 $= 12$**


Squares are used to calculate the length,  $L$ .

# nMOS Logic (Inverter): example1

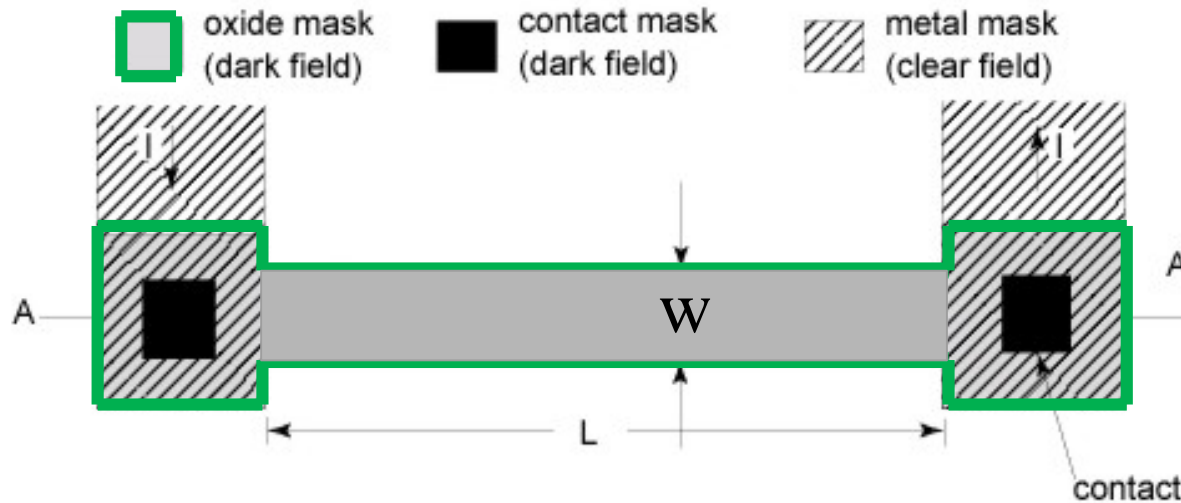



For small  $L_R/W_R$ :  
(e.g.  $L_R/W_R=9$ )

 For large  $L_R/W_R$ :  
(e.g.  $L_R/W_R=20$ )




**Every square must disappear  
when drawing your layout**


# nMOS Logic (Inverter): example1

  



# nMOS Logic (Inverter): example1

 

# NMOS Logic (Inverter): example1

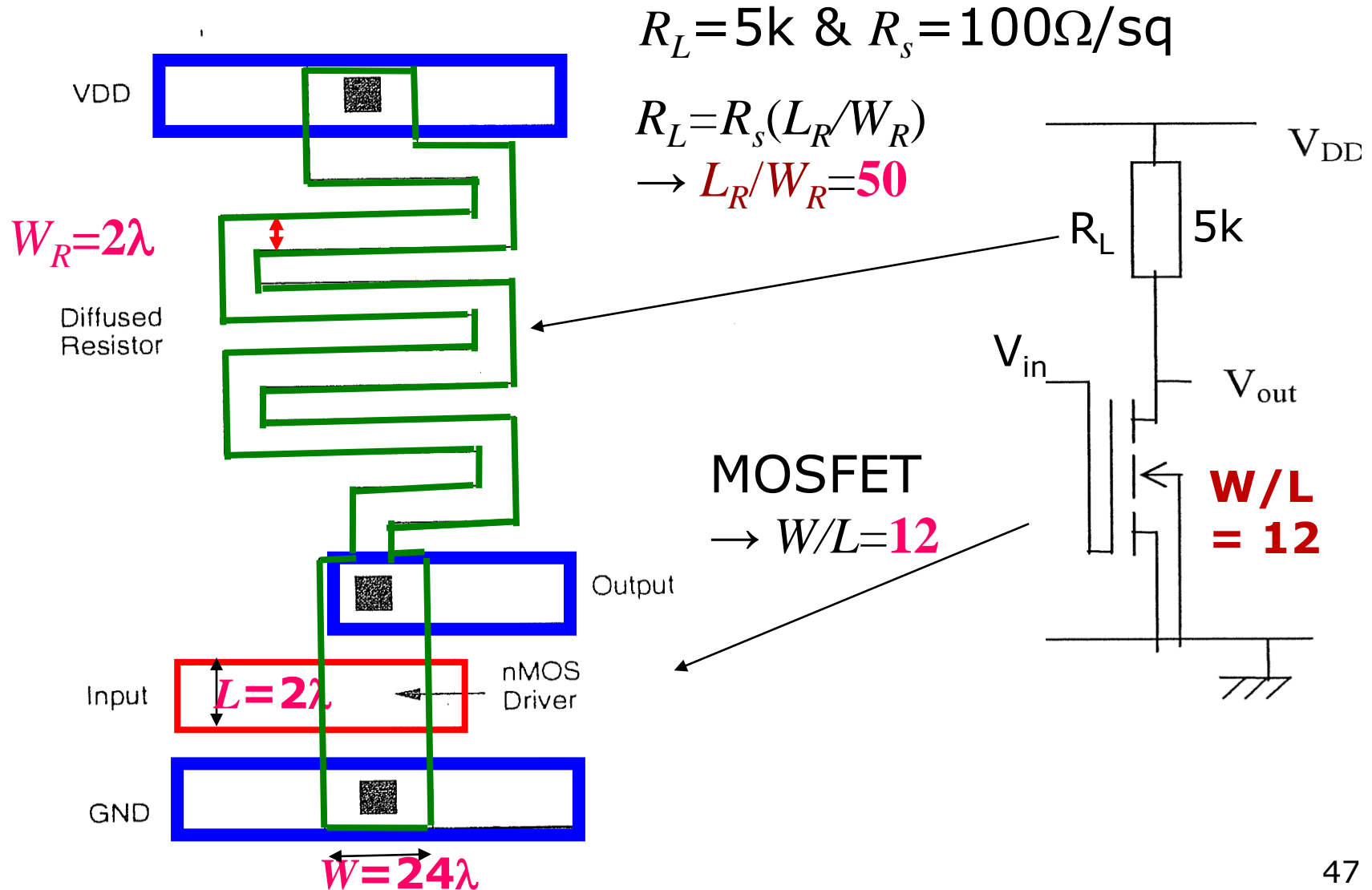



# nMOS Logic (Inverter): example2

 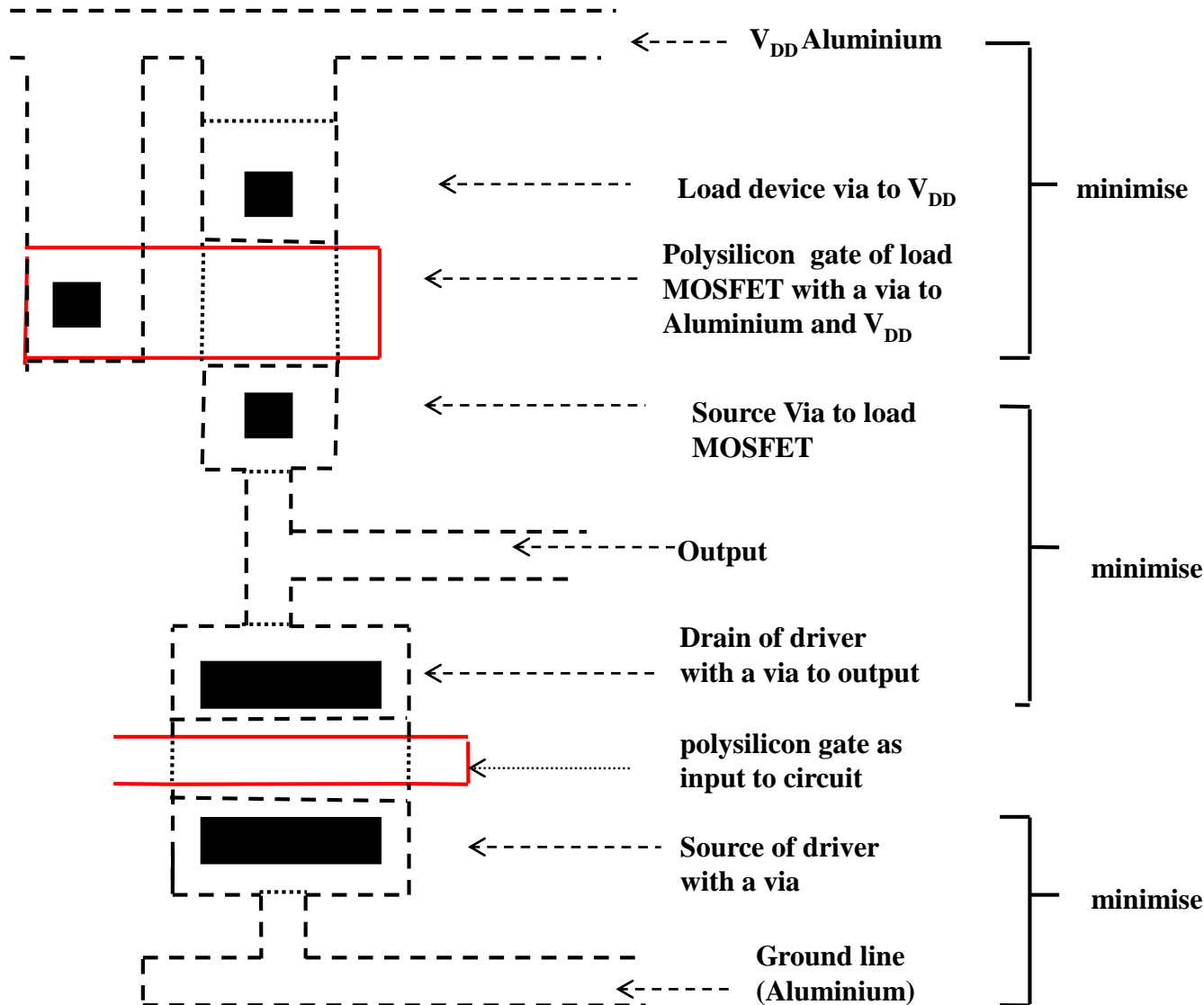




# nMOS Logic (Inverter): example2

## Mask1

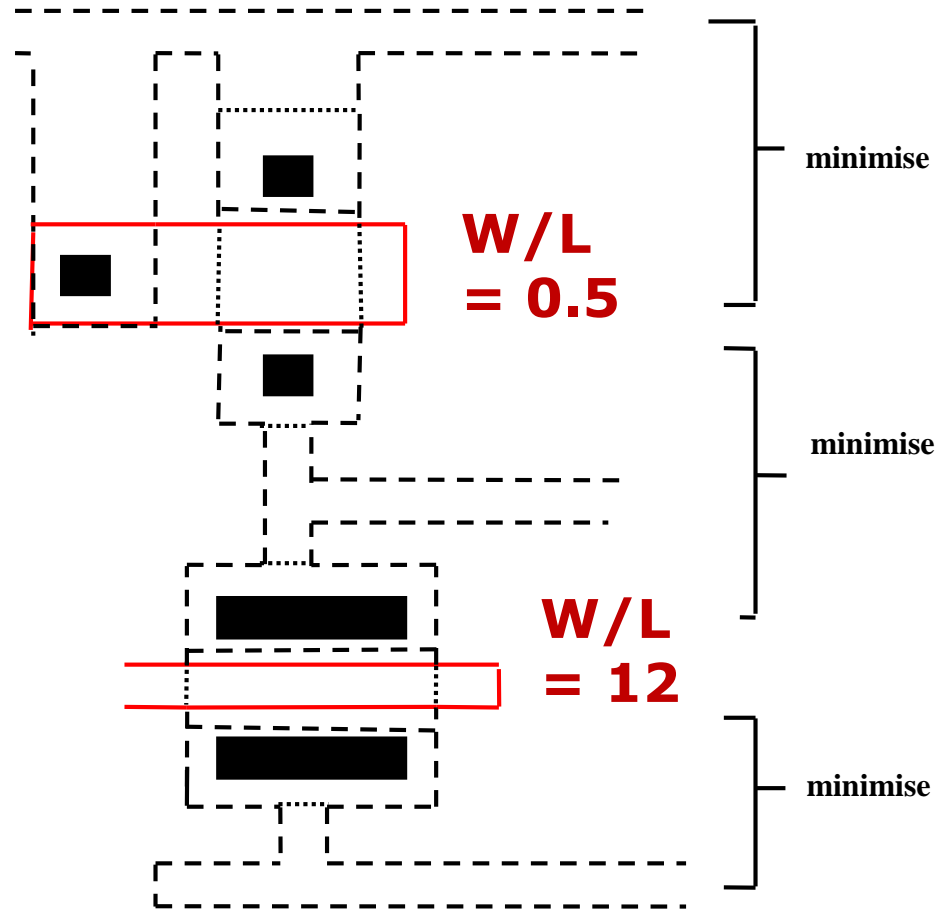 



# nMOS Logic (Inverter): example2

## Mask2

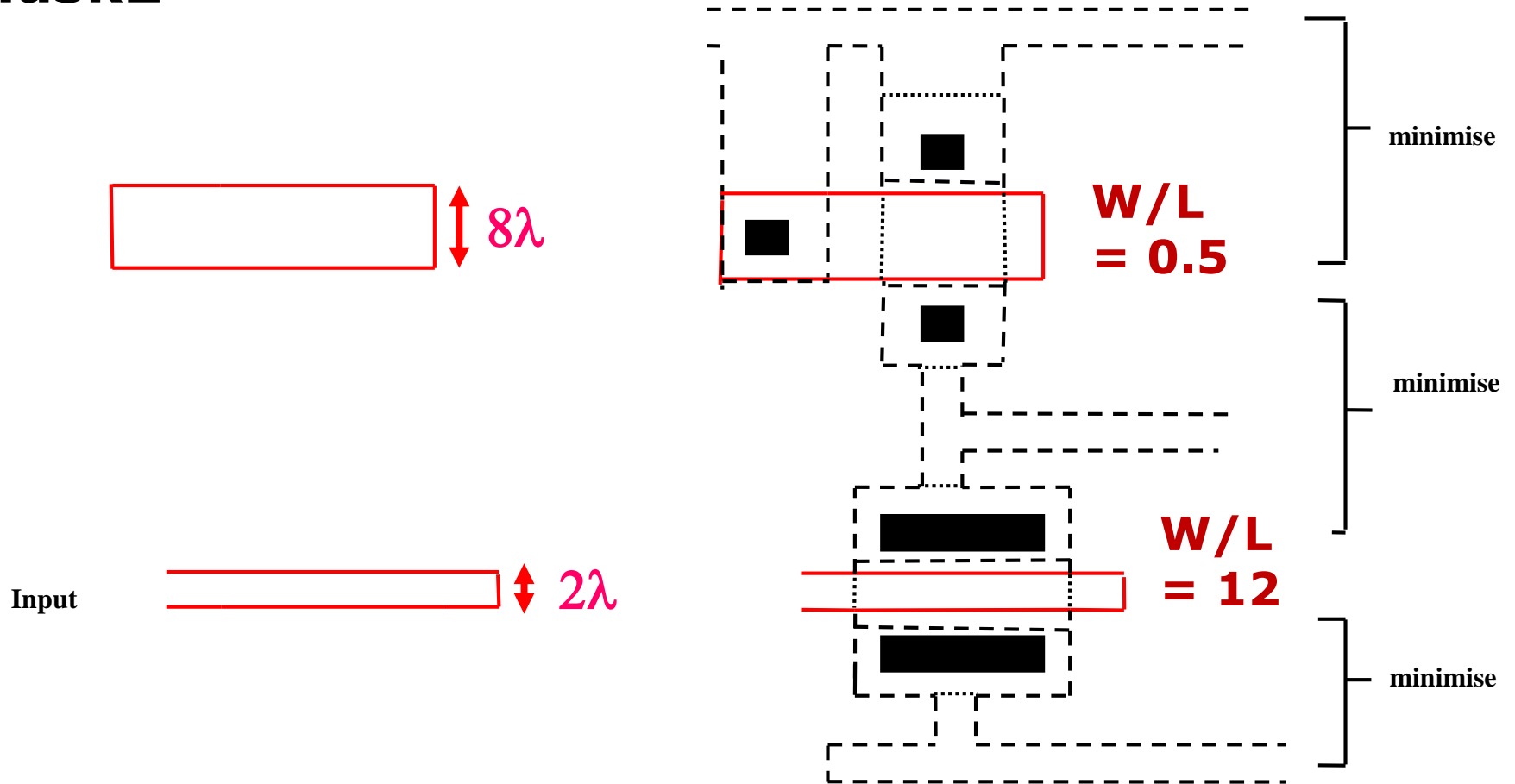



# nMOS Logic (Inverter): example2

## Mask3

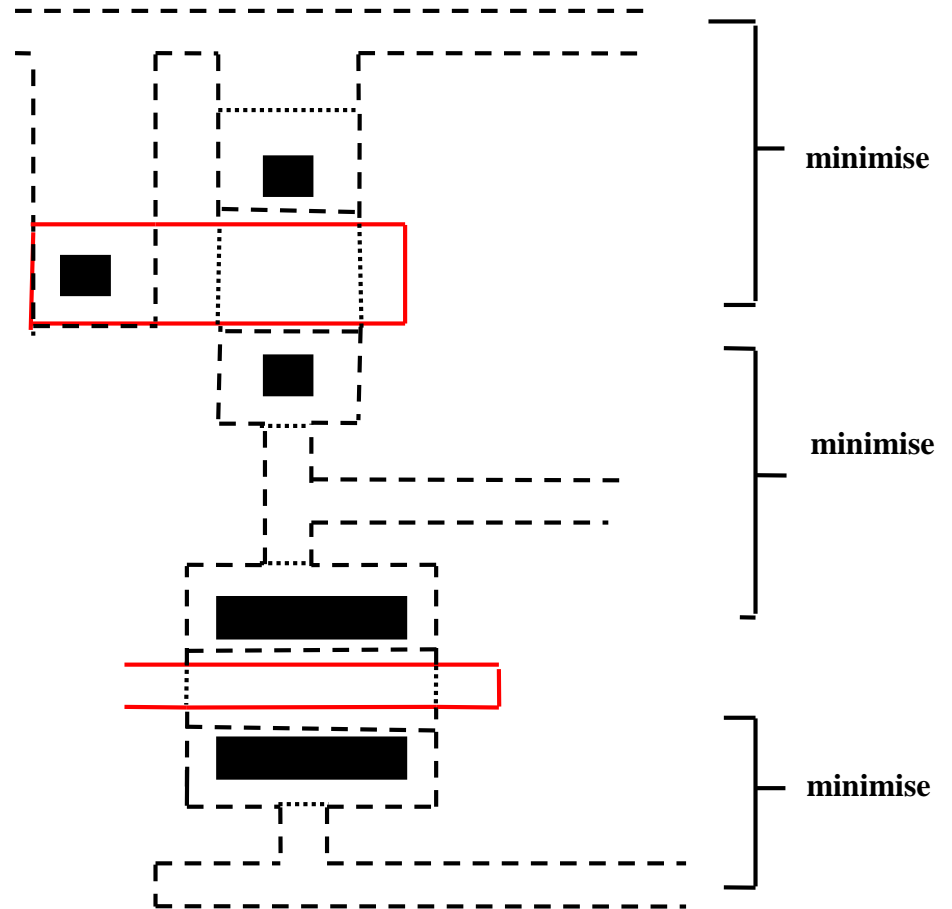
 


# nMOS Logic (Inverter): example2


## Mask4

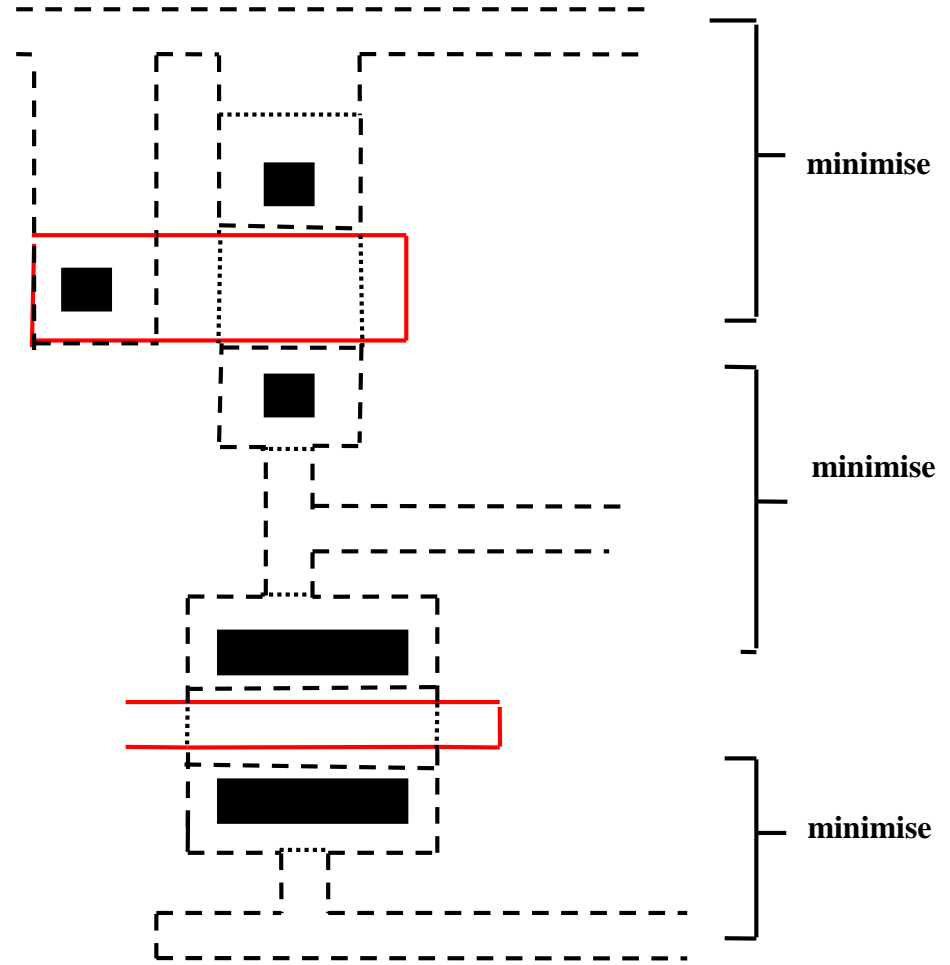 

# nMOS Logic (Inverter): example2

 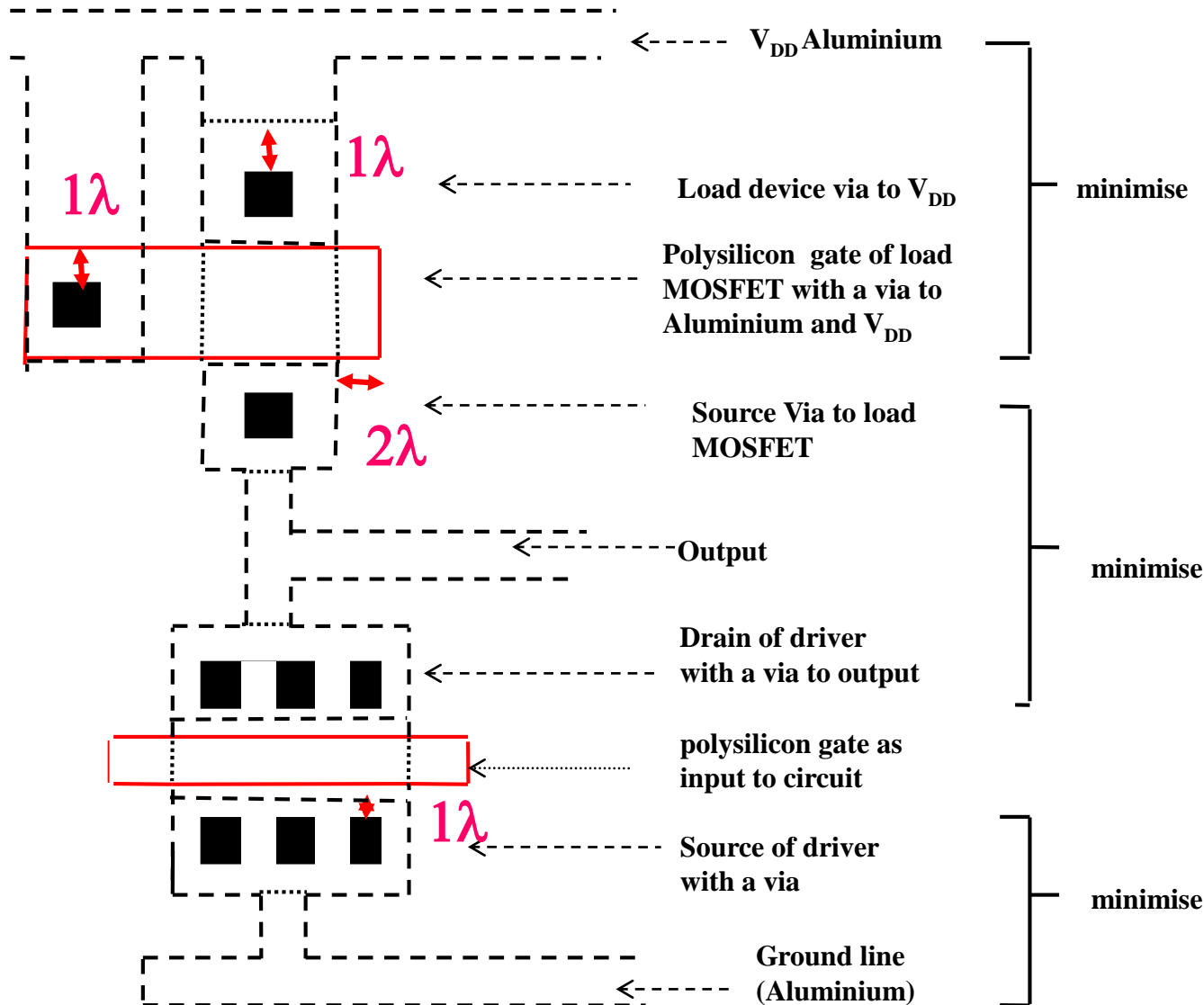

# nMOS NOR gate: example3

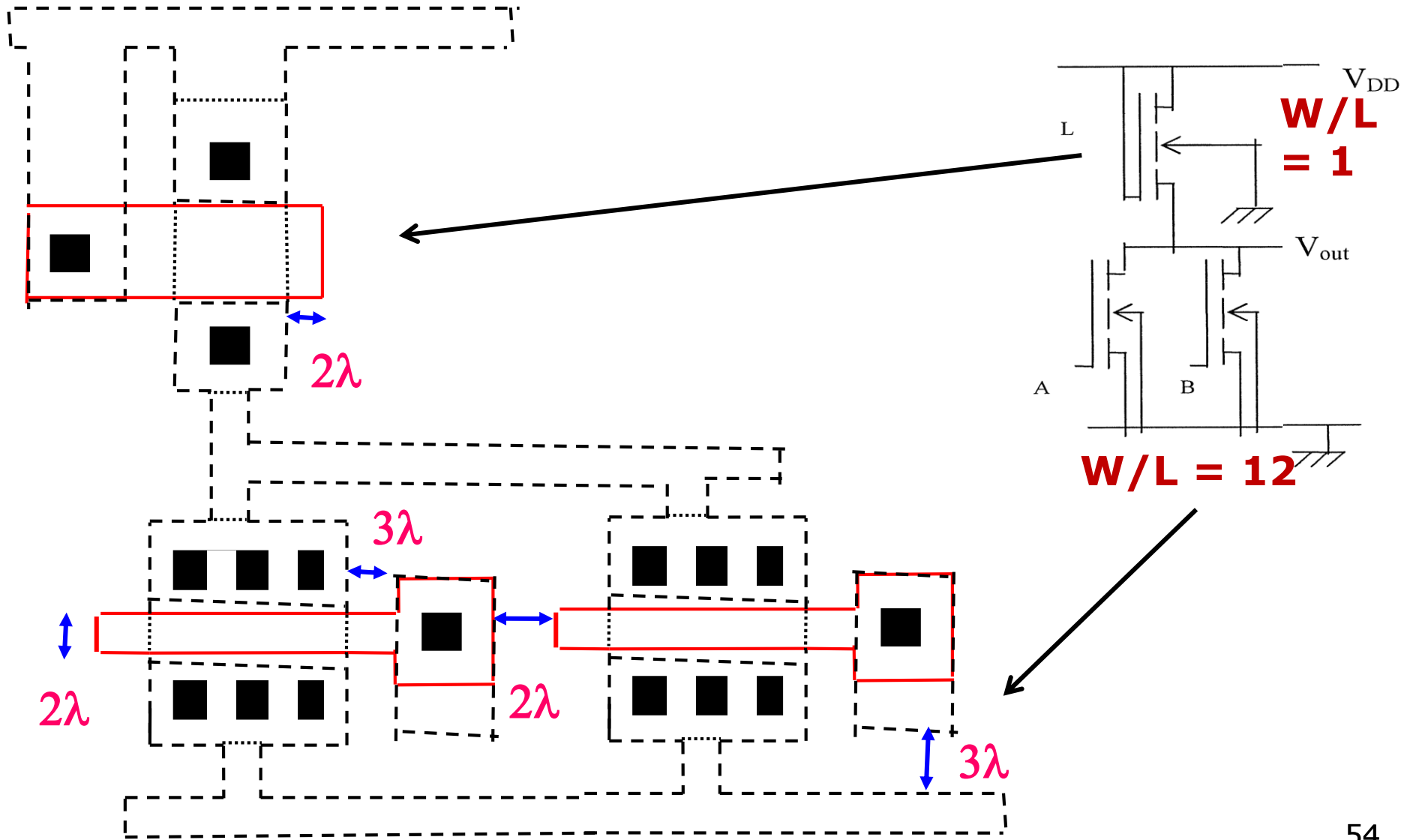

# OUTLINE

---

- nMOS logic (examples)
  - Truth table
  - Calculation
  - Layout
- **Design Exercise 2017 (15% marks)**

# Design Exercise 2017

## Layout design of the nMOS IC shown in Fig.1

- It consists of an n channel NOR gate feeding an inverter.
- The transistors A and B are the termed driver MOSFETs.
- The process parameters are defined:

➤  $2\lambda = 1\mu\text{m}$

➤  $\beta_0 = 1.8 \times 10^{-4} \text{A V}^{-2}$

➤  $V_T = 0.3\text{V}$

➤  $V_{DD} = 5\text{V}$

➤  $V_{in} = V_{DD}$

➤  $R_S = 100\Omega/\text{sq}$

$$\mu C_{ox} = \beta_0$$


 


Fig.1

 


# Design Exercise 2017

- Design rules:
- The driver transistors should have channel length  $L$  equal to the minimum feature size  $\lambda_m$ . The width of the drivers  $W$ , which must always be a whole number ( $n$ ) of minimum feature sizes ( $n\lambda_m$ ), and **the overall value of  $W$  must be chosen to give the required output voltage.** This must be significantly less than the threshold voltage of the third gate C if this transistor is to stay off.
- The layouts must take account of the alignment accuracy  $\lambda_a$ .
- $\lambda_m = 2\lambda_a$


 
# Design Exercise 2017

- Design rules:
- The driver transistors should have channel length  $L$  equal to the minimum feature size  $\lambda_m$ . The width of the drivers  $W$ , which must always be a whole number ( $n$ ) of minimum feature sizes ( $n\lambda_m$ ), and **the overall value of  $W$  must be chosen to give the required output voltage.** This must be significantly less than the threshold voltage of the third gate C if this transistor is to stay off.
- The layouts must take account of the alignment accuracy  $\lambda_a$ .
- $\lambda_m = 2\lambda_a$




# Design Exercise 2017

---

- 1) The Design involves producing the patterns corresponding to each of the stages of the process already discussed.
- 2) Each of the patterns should be drawn on graph paper with a stipulated scale. (e.g 1 $\mu$ m per cm.)
- 3) The patterns would be transferred at a later stage to glass masks, as opaque regions. There are 4 masks :
  - M1. define the device area**
  - M2. define the gate stripe**
  - M3. define the contacts**
  - M4. define the metal pattern**
- 4) Your design paper should include 5 parts: **4 masks and 1 layout**. Your report should include a brief explanation and calculations.
 
# Example: Design Exercise 2016

- It consists of an n channel NOR gate feeding an inverter.
- The transistors A and B are the termed driver MOSFETs.
- The process parameters are defined:
  - $2\lambda = 1\mu\text{m}$
  - $\beta_0 = 1.8 \times 10^{-4} \text{AV}^{-2}$
  - $V_T = 0.3\text{V}$
  - $V_{DD} = 5\text{V}$
  - $V_{in} = V_{DD}$
  - $R_s = 100\Omega/\text{sq}$
- HINTS: Liverpool notes.




# Design Exercise 2016

---

- 1) The Design involves producing the patterns corresponding to each of the stages of the process already discussed.
- 2) Each of the patterns should be drawn on graph paper with a stipulated scale. (e.g 1 $\mu$ m per cm.)
- 3) The patterns would be transferred at a later stage to glass masks, as opaque regions. There are 4 masks :
  - M1. define the device area**
  - M2. define the gate stripe**
  - M3. define the contacts**
  - M4. define the metal pattern**
- 4) Your design paper should include 5 parts: **4 masks and 1 layout**. Your report should include a brief explanation and calculations.


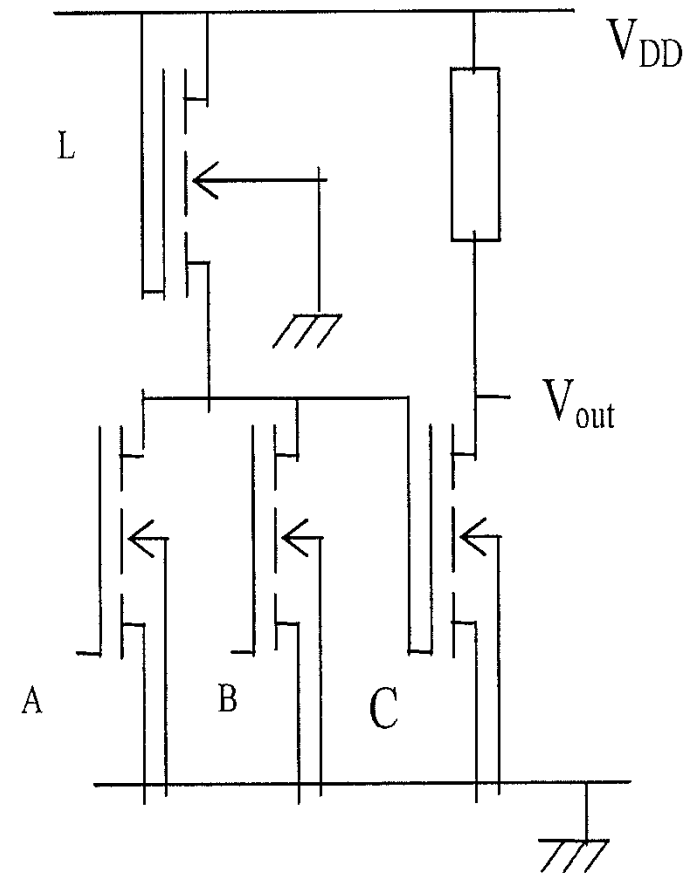
# Design Exercise 2016

- Design rules:
- The driver transistors should have channel length  $L$  equal to the minimum feature size  $\lambda_m$ . The width of the drivers  $W$ , which must always be a whole number ( $n$ ) of minimum feature sizes ( $n\lambda_m$ ), and **the overall value of  $W$  must be chosen to give the required output voltage.** This must be significantly less than the threshold voltage of the third gate C if this transistor is to stay off.
- The layouts must take account of the alignment accuracy  $\lambda_a$ .
- $\lambda_m = 2\lambda_a$  (correction needed)





# nMOS IC: example

$$\frac{W}{L} = 1$$

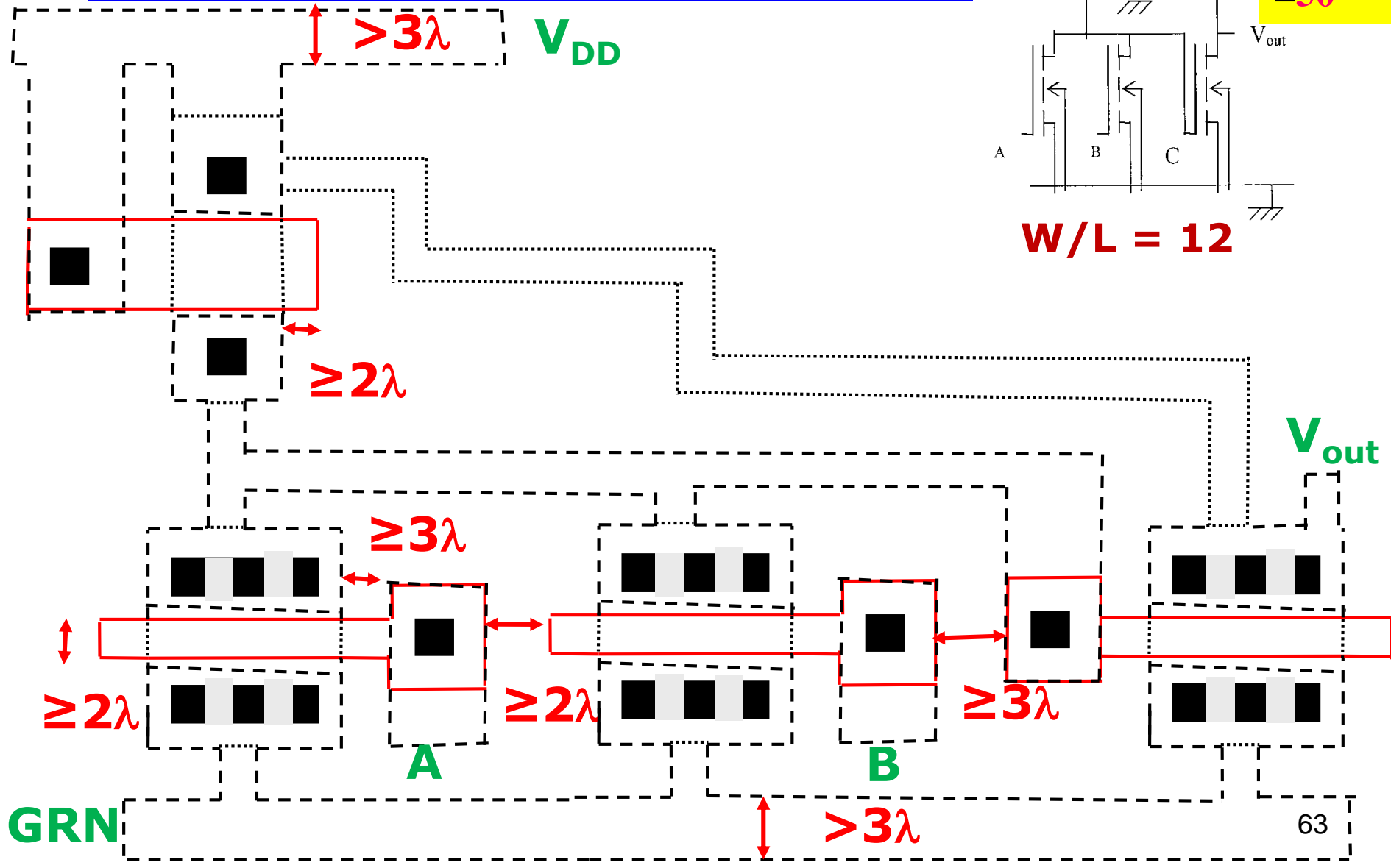 

# nMOS IC: example




## Mask1

  








# nMOS IC: example

## Mask2

   



# nMOS IC: example

## Mask3

     

# nMOS IC: example

**Mask4**

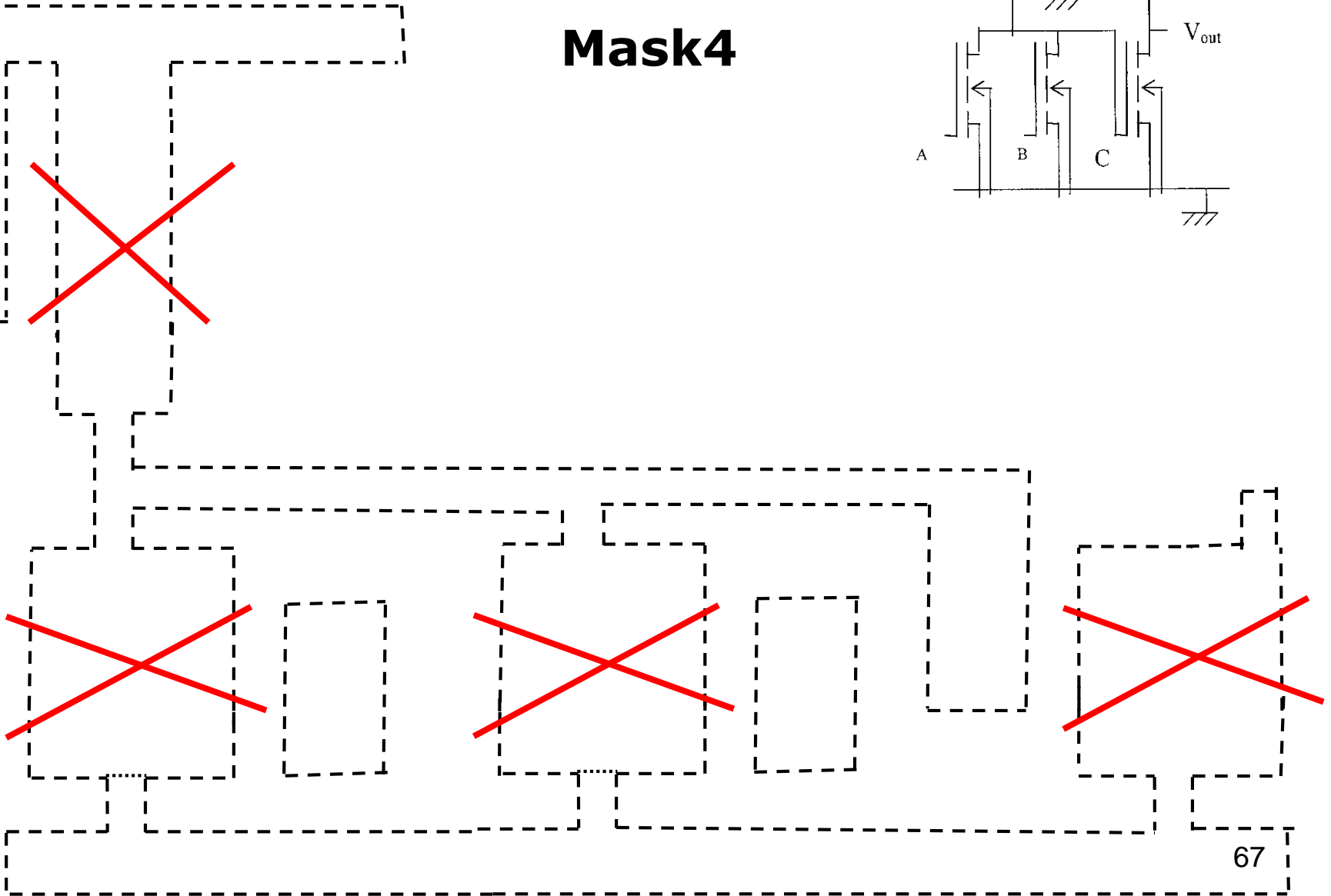 

# nMOS IC: example

**Mask4**

