

**Lecture 5**  
*of*  
**EEE307**

# Electronics for Communications

**Department of Electrical & Electronic Engineering**  
**Xi'an Jiaotong-Liverpool University (XJTLU)**

Friday, 11<sup>th</sup> October 2019


- ❑ Gain Calculation Example
- ❑ Amplifier Circuit Analysis
  - transistor amplifier
  - unity gain frequency


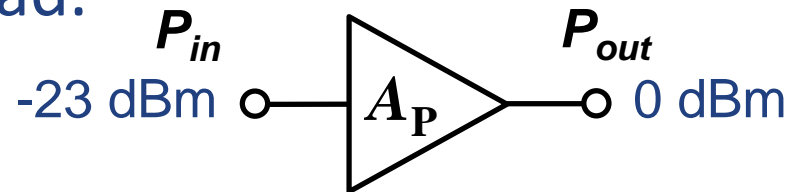
# Calculation Example - Amplifier

(power level & signal amplitude)

- An amplifier senses a sinusoidal signal and delivers a power of 0 dBm to a load resistance of 50  $\Omega$ . Determine the peak-to-peak voltage  $V_{pp}$  swing across the load.



Solution:

$$\text{➤ } 0 \text{ dBm} = 1 \text{ mW}; \quad P_{out} = \frac{V_{rms}^2}{R_L} = \frac{V_{pp}^2}{8R_L} = 10^{-3} \text{ W where } R_L = 50\Omega$$


$$\Rightarrow V_{pp} = \sqrt{8P_{out}R_L} = \sqrt{8(10^{-3})(50)} = 632 \text{ mV}$$

$$\Rightarrow V_p = V_{pp} / 2 = 316 \text{ mV and } V_{rms} = \frac{V_p}{\sqrt{2}} = 224 \text{ mV}$$
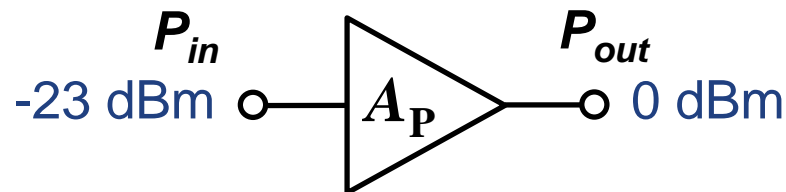
# Calculation Example – Amplifier (cont'd)

(amplifier gain & signal amplitude)

- What is the **power gain** of such an amplifier?  
Assuming matched input and **output impedance** of  $50\ \Omega$ , what is the **voltage gain**? What is the peak-to-peak voltage  $V_{inpp}$  swing at the input.



Solution:

$$\triangleright A_P = \frac{P_{out}}{P_{in}} \text{ or } A_P|_{dB} = 10 \log \left( \frac{P_{out}}{P_{in}} \right)$$

$$A_P|_{dB} = 0\text{ dBm} - (-23\text{ dBm}) = 23\text{ dB}$$

$$23\text{ dB} = 20\text{ dB} + 3\text{ dB} \Rightarrow A_P = 200$$

20 dB correspond to  $A_p = 100$

3 dB correspond to  $A_p = 2$




Xi'an Jiaotong-Liverpool University

西交利物浦大学

# Calculation Example – Amplifier (cont'd)


(amplifier gain & signal amplitude)

Solution: (cont'd)

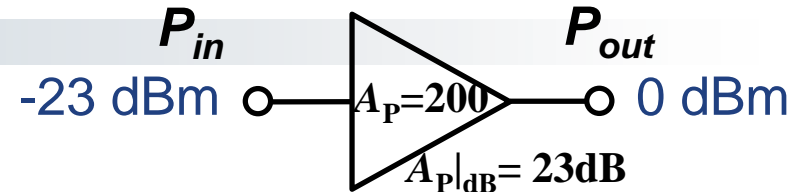

➤ Assume matched input and output impedance
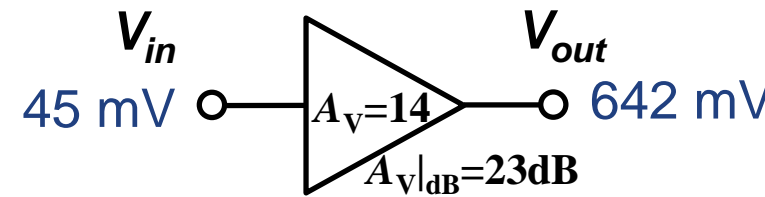
$$A_P = \frac{P_{out}}{P_{in}} = \frac{V_{out}^2 / R_{m0}}{V_{in}^2 / R_{m0}} = \left( \frac{V_{out}}{V_{in}} \right)^2$$



$$\Rightarrow A_P|_{dB} = 10 \log \left( \frac{V_{out}^2}{V_{in}^2} \right) = 20 \log \left( \frac{V_{out}}{V_{in}} \right) = A_V|_{dB}$$


$$A_V|_{dB} = A_P|_{dB} = 23 \text{ dB} \Rightarrow A_V = \sqrt{200} = 14 \quad A_P = \left( \frac{V_{out}}{V_{in}} \right)^2 = (A_V)^2$$

$$A_V = \frac{V_{out}}{V_{in}} \Rightarrow V_{inpp} = \frac{V_{outpp}}{A_V} = \frac{632 \text{ mV}}{14} = 45 \text{ mV}$$
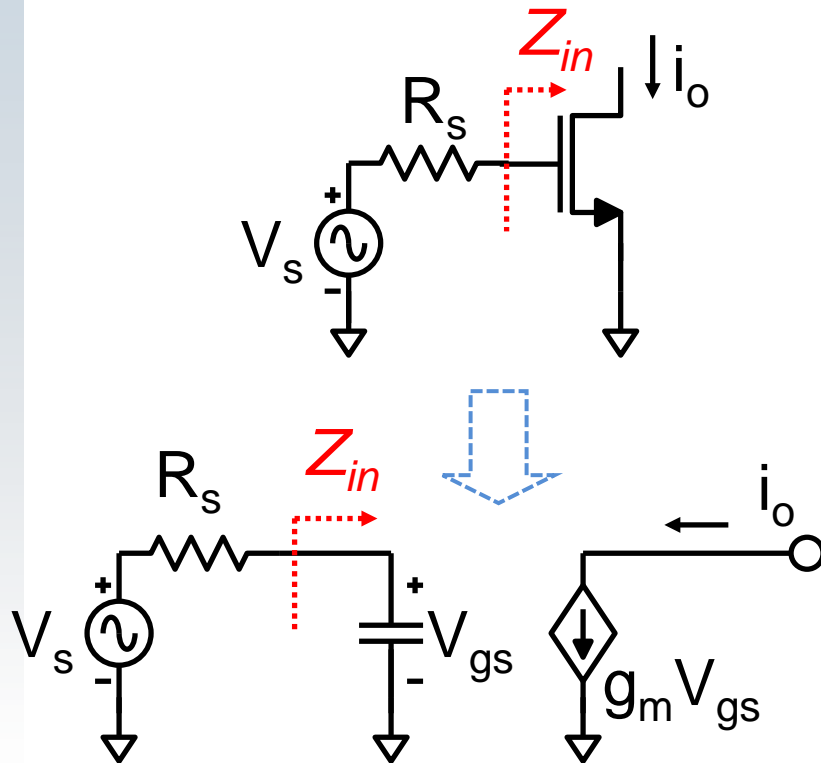
# Circuit Analysis - Amplifier Gain

(effective transconductance)

- In the common-source (CS) amplifier configuration, the **amplification gain** can be calculated first by determining the *effective transconductance*  $G_{meff}$ .



$$G_{meff} = \frac{i_o}{V_s} = \frac{g_m \cdot Z_{in}}{R_s + Z_{in}}$$

$$G_{meff} = \frac{g_m \left( \frac{1}{j\omega C_{gs}} \right)}{R_s + \frac{1}{j\omega C_{gs}}} = \frac{g_m}{j\omega C_{gs} R_s + 1}$$




Xi'an Jiaotong-Liverpool University  
西交利物浦大學
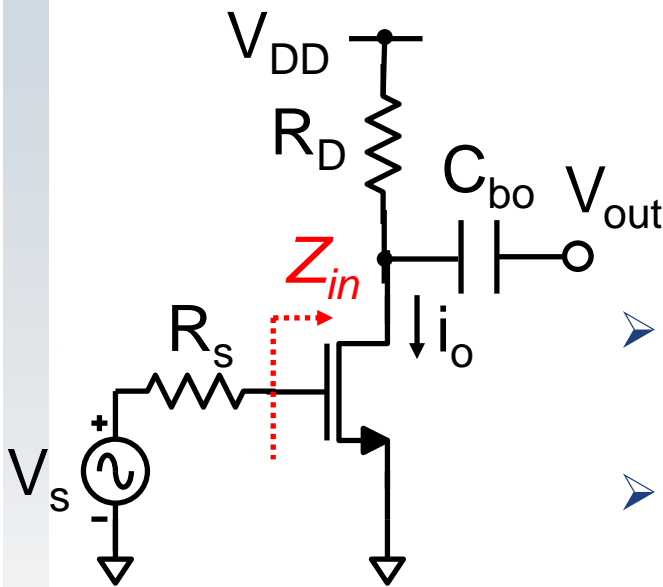
# Circuit Analysis - Amplifier Gain

(voltage gain)

- ❑ The overall **voltage gain** can then be calculated by multiplying the *effective* **transconductance**  $G_{meff}$  and the equivalent output impedance.



$$A_V = G_{meff} (R_D // r_o) = \frac{g_m}{j\omega C_{gs} R_s + 1} (R_D // r_o)$$
$$r_o = \frac{1}{\lambda I_{Dbias}}$$

- $r_o$  is the *small-signal* **drain output resistance** of the MOS transistor.
- $\lambda$  is the **channel-length modulation coefficient** of the MOS transistor.




Xi'an Jiaotong-Liverpool University  
西交利物浦大學
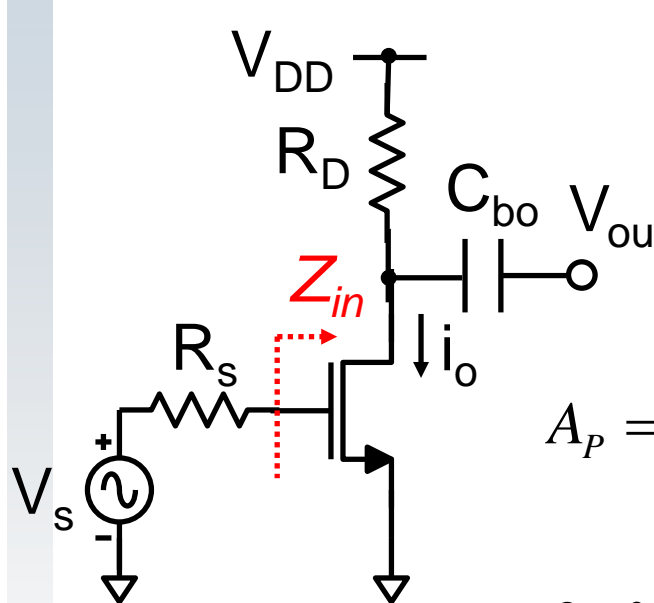
# Circuit Analysis - Amplifier Gain

(power gain from voltage gain)

- Assuming matched input and output impedance, the overall **power gain** would be the square of the magnitude of the **voltage gain**.



$$A_P = |A_V|^2 = \left| \frac{g_m}{j\omega C_{gs} R_s + 1} (R_D // r_o) \right|^2$$

$$A_P = \frac{g_m^2 (R_D // r_o)^2}{1 + \omega^2 (C_{gs} R_s)^2} \approx \frac{g_m^2 (R_D // r_o)^2}{\omega^2 (C_{gs} R_s)^2} \approx \frac{\omega_T^2 (R_D // r_o)^2}{\omega^2 R_s^2}$$

$$\omega_T = 2\pi f_T \approx \frac{g_m}{C_{gs} + C_{gd}} \approx \frac{g_m}{C_{gs}}$$

# Small-Signal Transistor Amplifier

(unity gain frequency  $f_T$ )

- From the circuit analysis of the common-source (CS) amplifier configuration, it can be inferred that the **power gain** decreases with the inverse square of the operation frequency  $f$ .

$$A_p \approx \frac{g_m^2 (R_D // r_o)^2}{\omega^2 (C_{gs} R_s)^2} \approx \left( \frac{\omega_T}{\omega} \right)^2 \left( \frac{R_D // r_o}{R_s} \right)^2 \propto \left( \frac{f_T}{f} \right)^2$$

- The **unity gain frequency  $f_T$**  of the transistor is an important parameter of consideration in the design of the radio-frequency (RF) amplifiers including

LNA. 
$$f_T \approx \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$



# Transistor Amplifiers

(trade-off of  $g_m$  &  $C_{gs}$ )

- ❑ In CMOS RF integrated circuits, MOSFETs are used for making LNA circuits. For a given technology (e.g. 90nm CMOS process), a large transistor size ( $W/L$ ) will cause larger  $C_{gs}$  (as well as  $C_{gd}$ ).

$$f_T \approx \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

- $f_T$  does not increase with the transistor size.
- $f_T$  may be increased by using a larger biasing current for increasing  $g_m$ . However, the improved signal gain comes at the expense of more power consumption.
- Such a **trade-off** between different **performance factors** is very common in engineering areas.
- Typically,  $f_T$  is more or less a constant in a given transistor technology.

# Large-Signal Amplifiers

(trade-off of  $g_m$  &  $C_{gs}$ )

- Note that  $f_T$  is a parameter of interest in **small-signal amplification**.
$$f_T \approx \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$
- In **large-signal** circuits (e.g. **power amplifiers**),  $f_T$  does not tell very much the maximum operation frequency of the transistors and hence how high the speed of the circuits built from the transistors.
  - In large-signal circuits with high current AC signals (1000 mA), the transistor is usually of very large size. While  $g_m$  is very high (e.g. 5000 mS) in such transistors, the capacitances (e.g.  $C_{gs}$  &  $C_{gd}$ ) are also very large (e.g. > 10 pF).

# RF Circuit Construction


(discrete transistors)

- ❑ In the construction of RF circuits using *discrete* transistors, choose the transistors with the specifications showing clearly that  $f_T$  is well above the operation frequency of the circuit.
- ❑ Pay attention to the  $g_m$  value(s) given in the transistor's data sheets and the corresponding biasing conditions (e.g. voltage & current).
  - Find out also the critical capacitances of the transistors ( $C_{gs}$  in MOSFETs and  $C_{be}$  in BJTs).
  - Always start with hand calculations of e.g. the amplifier gain before circuit construction.
  - Make good use of approximation!
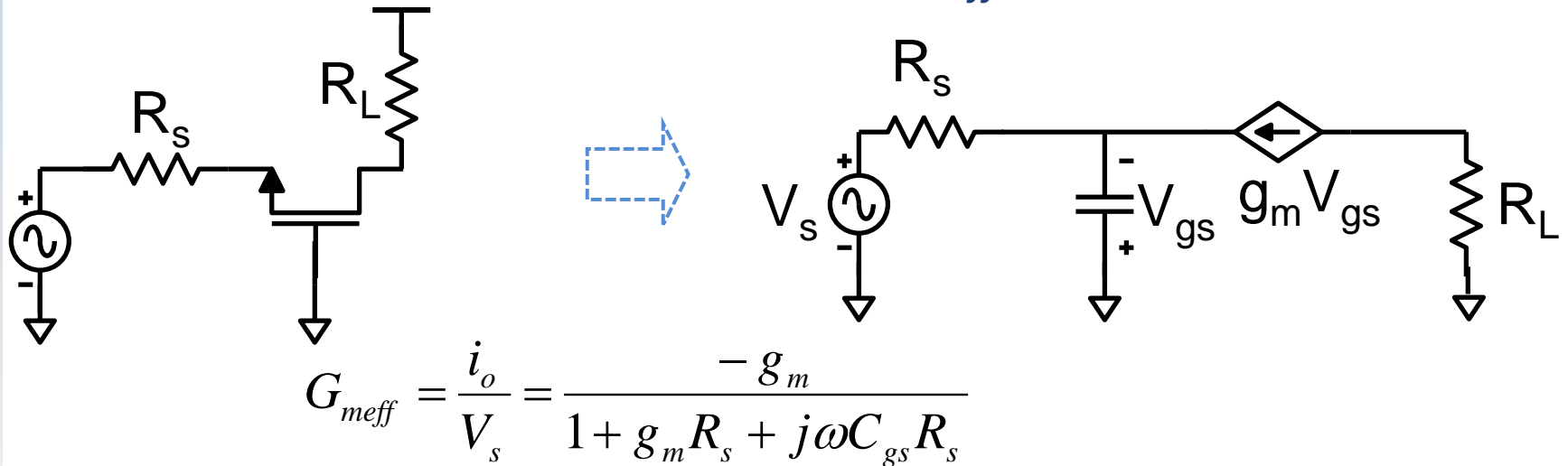
# Circuit Analysis – CG Amplifier

(effective transconductance)

- In the common-gate (CG) amplifier configuration, similar techniques can be used by determining the *effective transconductance*  $G_{meff}$ .




$$A_V = G_{meff} (R_L // r_o) = \frac{-g_m (R_L // r_o)}{1 + g_m R_s + j\omega C_{gs} R_s}$$

# LNA Example

(3-stage transistor amplifier)

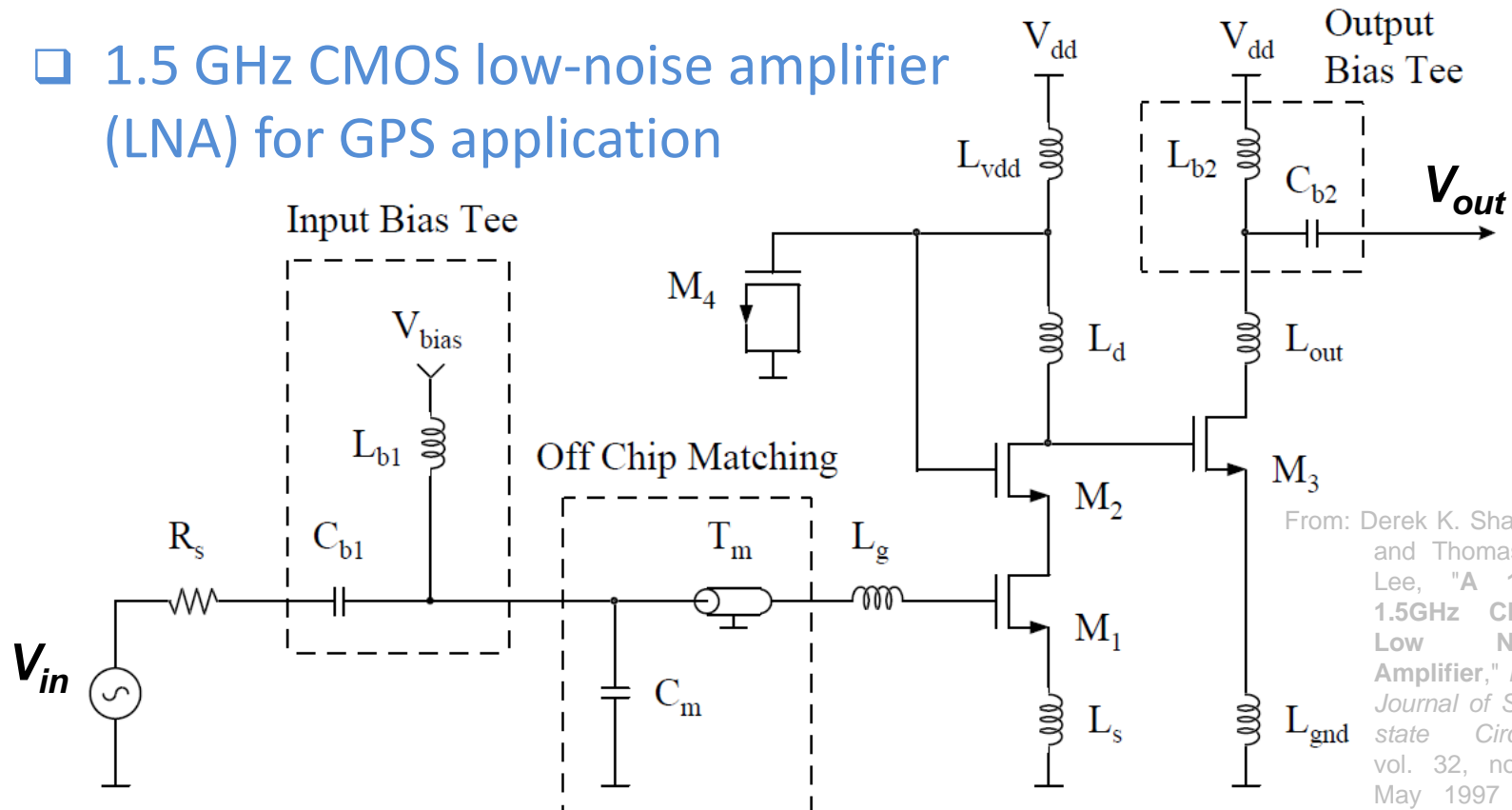- 1.5 GHz CMOS low-noise amplifier (LNA) for GPS application



From: Derek K. Shaeffer and Thomas H. Lee, "A 1.5V, 1.5GHz CMOS Low Noise Amplifier," *IEEE Journal of Solid-state Circuits*, vol. 32, no. 5, May 1997 (pp. 745-759).

- CS, CG and CS amplifiers connected together
  - Note the source-degeneration CS configuration.




Xi'an Jiaotong-Liverpool University  
西交利物浦大学
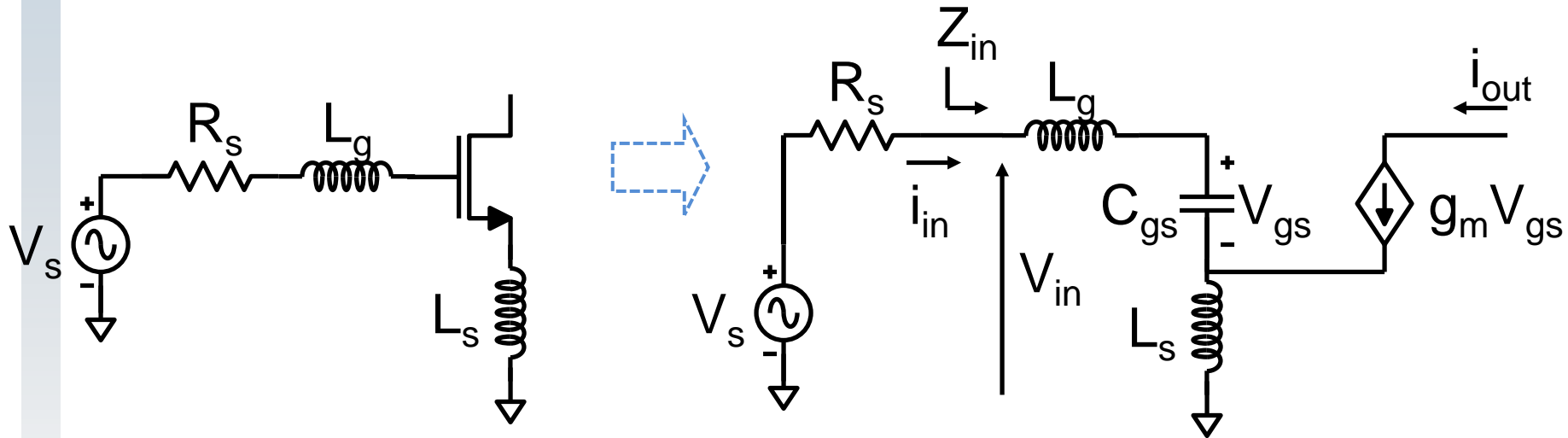
# Circuit Analysis – LNA


(inductor source-degeneration)

- ❑ In the CS LNA configuration with inductor source-degeneration, similar circuit analysis can be applied in the *small-signal* equivalent circuit.



# Circuit Analysis – LNA

(inductor source-degeneration)

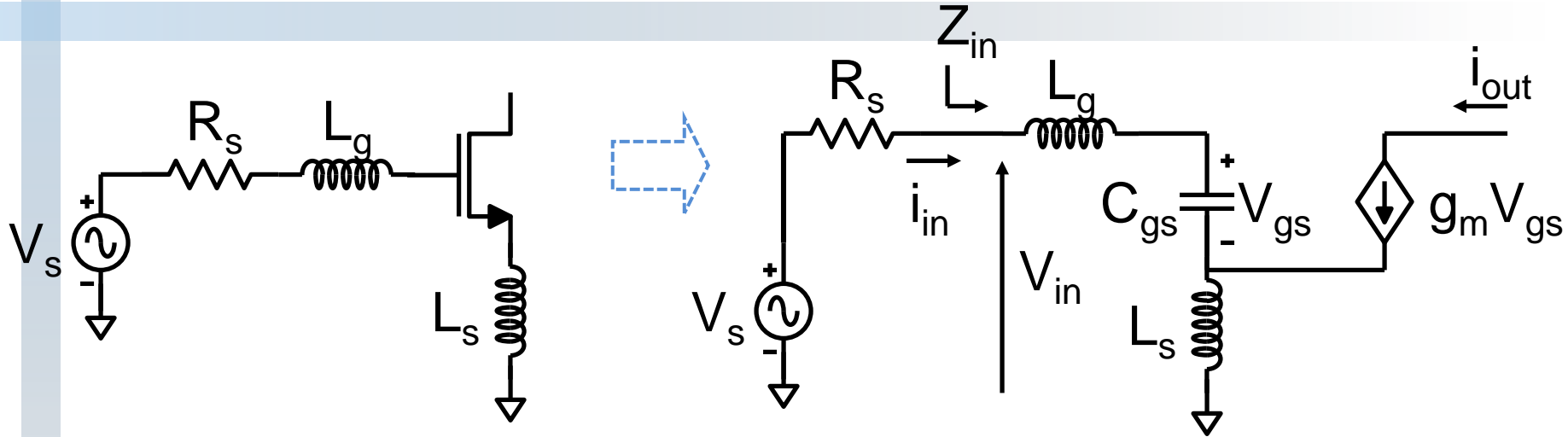


➤ The *effective* transconductance  $G_{meff}$  may be determined using the short-cut formula.

$$G_{meff} = \frac{I_{out}}{V_s} = \frac{g_m / (j\omega C_{gs})}{R_s + Z_{in}}$$

$$= \frac{g_m}{1 + j\omega(R_s C_{gs} + g_m L_s) - \omega^2 C_{gs}(L_g + L_s)}$$

# Circuit Analysis – LNA

(inductor source-degeneration)

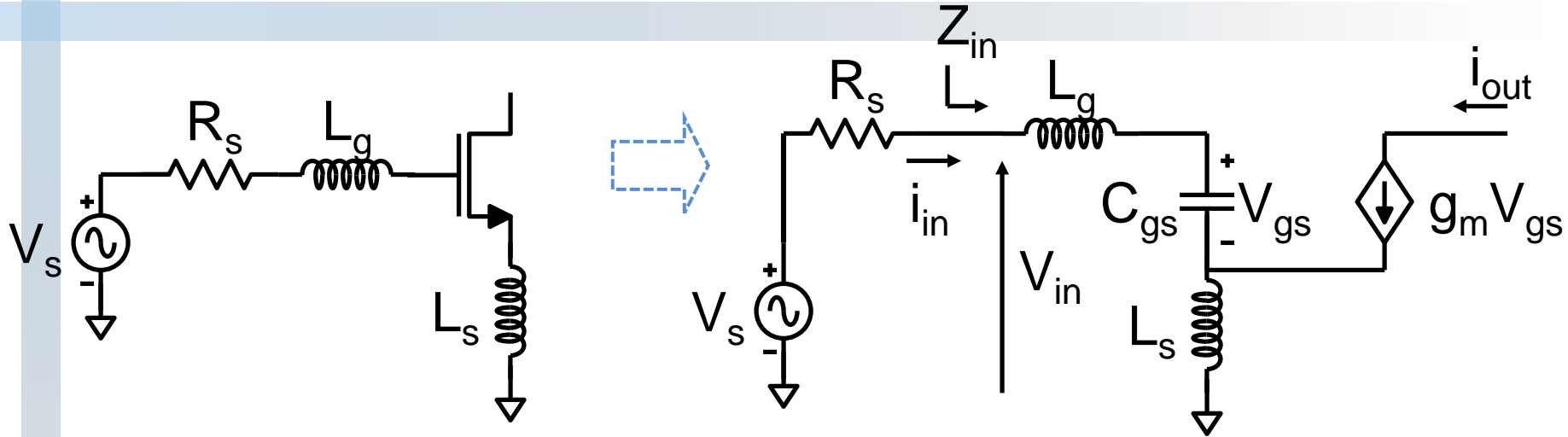


$$\begin{aligned}
 V_{in} &= I_{in}(j\omega L_g) + I_{in} \frac{1}{j\omega C_{gs}} + (I_{in} + g_m V_{gs})(j\omega L_s) \\
 &= I_{in}(j\omega L_g) + I_{in} \frac{1}{j\omega C_{gs}} + \left(I_{in} + g_m I_{in} \frac{1}{j\omega C_{gs}}\right)(j\omega L_s) \\
 &= I_{in} \left[ j\omega(L_g + L_s) + \frac{1}{j\omega C_{gs}} + \frac{g_m L_s}{C_{gs}} \right] \leftarrow Z_{in}
 \end{aligned}$$

➤ The input impedance can be optimised for matching e.g. 50Ω.



# Circuit Analysis – LNA

(input impedance matching)

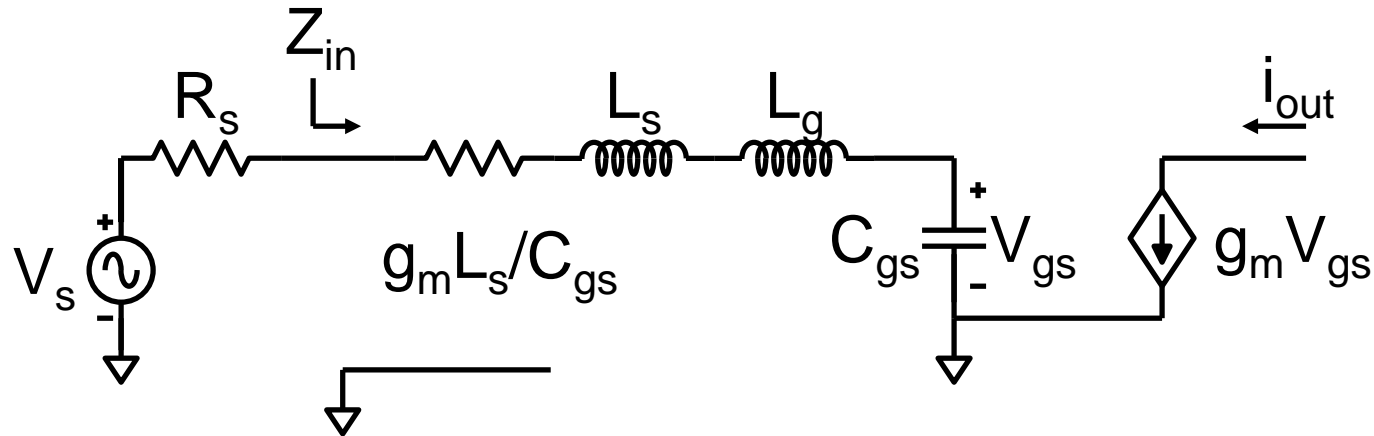

$$Z_{in} = j\omega(L_g + L_s) + \frac{1}{j\omega C_{gs}} + \frac{g_m L_s}{C_{gs}}$$





$$\omega_0^2 = \frac{1}{(L_g + L_s)C_{gs}}$$

$$\frac{g_m L_s}{C_{gs}} = R_s$$

➤ The input impedance matching can be achieved by the use of inductors by LC resonance.

# Circuit Analysis Tricks

(quick formulas in MOSFETs)

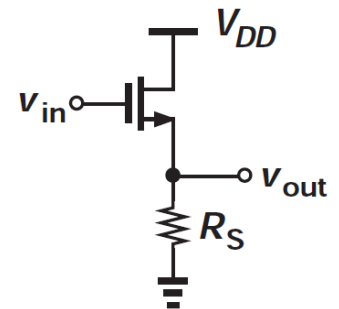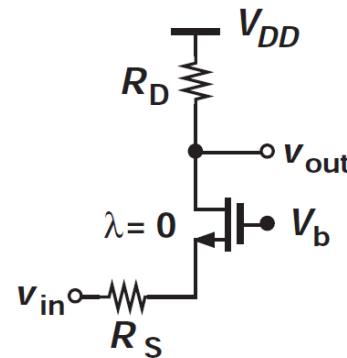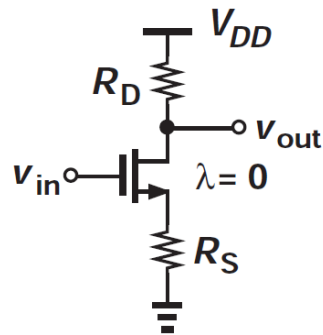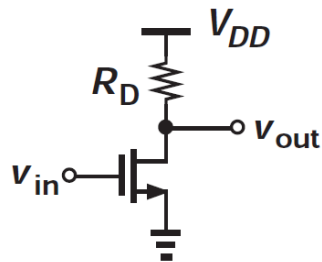

$$A_v = -g_m (R_D // r_o)$$

$$A_v = -\frac{g_m R_D}{1 + g_m R_S}$$

$$A_v = \frac{g_m R_D}{1 + g_m R_S}$$

$$A_v = \frac{g_m (R_S // r_o)}{1 + g_m (R_S // r_o)}$$


From: Behzad Razavi, *Fundamentals of Microelectronics*, © 2013 Wiley, USA.




Xi'an Jiaotong-Liverpool University  
西交利物浦大學

# Circuit Analysis Tricks


(quick formulas in BJTs)

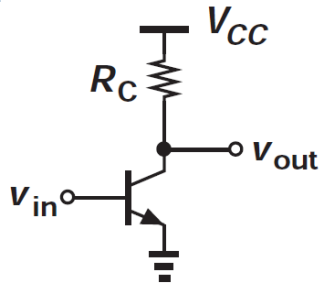


$$A_v = -g_m (R_C \parallel r_o)$$

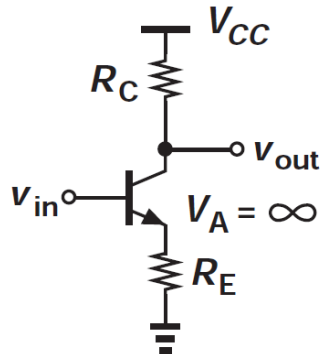

$$A_v = -\frac{g_m R_C}{1 + g_m R_E}$$

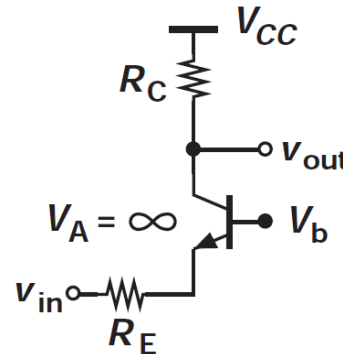

$$A_v = \frac{g_m R_C}{1 + g_m R_E}$$

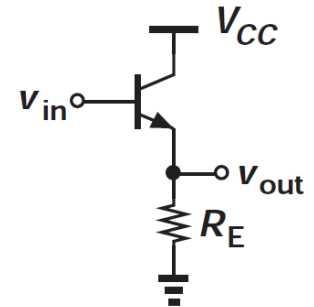

$$A_v = \frac{g_m (R_E \parallel r_o)}{1 + g_m (R_E \parallel r_o)}$$

From: Behzad Razavi, *Fundamentals of Microelectronics*, © 2013 Wiley, USA.



Xi'an Jiaotong-Liverpool University

西交利物浦大學