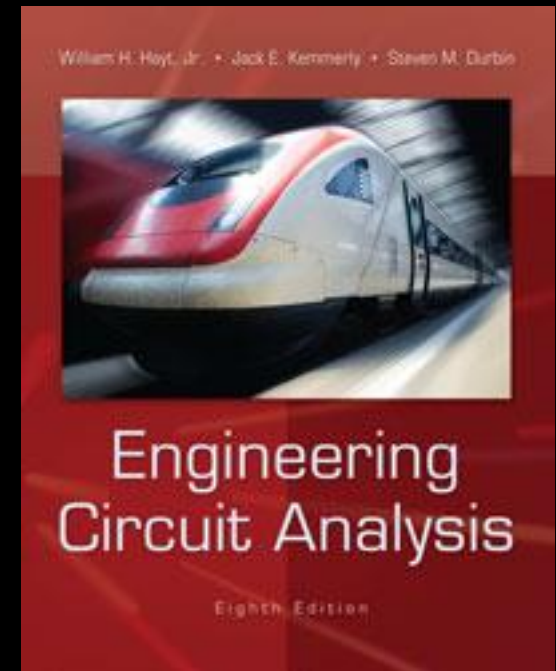




Chapter 6

The Operational Amplifier



The Operational Amplifier

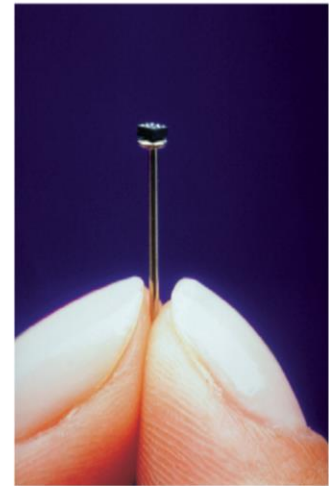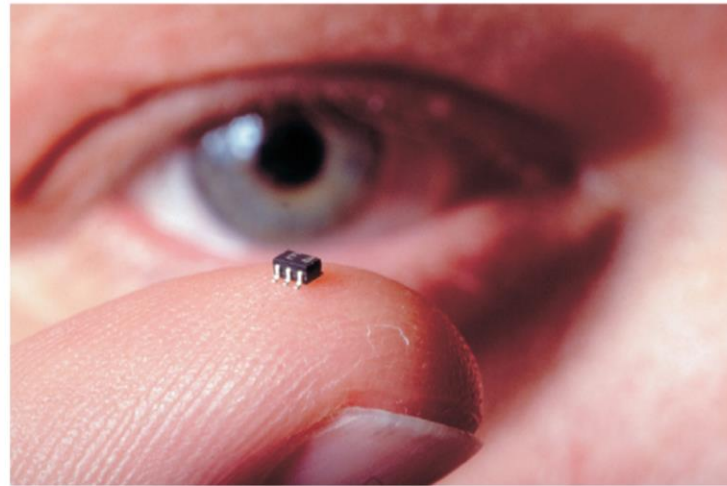- The *operational amplifier* or op amp for short, finds daily usage in a large variety of electronic applications.




The Op Amp Circuit Element

- op amps have three principal terminals:

the
inverting
input

the non-inverting input

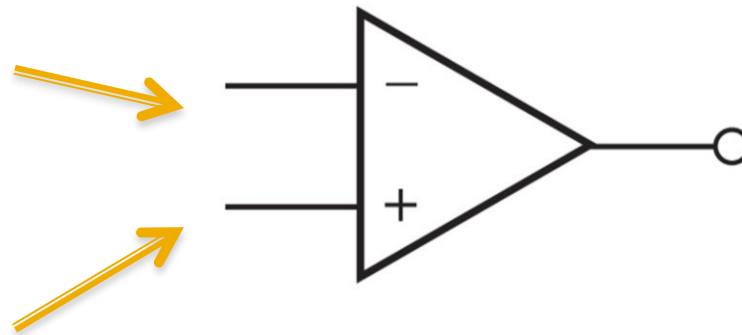


the output

The Ideal Op Amp

Ideal Op Amp Rules

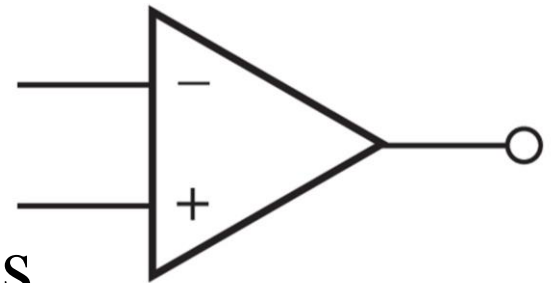- No current ever flows into either input terminal.
- There is no voltage difference between the two input terminals.




The op amp *acts* to make this happen!

The Inverting Amplifier



- Apply KVL, Ohm's law, and the ideal op amp rules to find
- More appropriately KCL

$$v_{out} = -\frac{R_f}{R_1} v_{in}$$

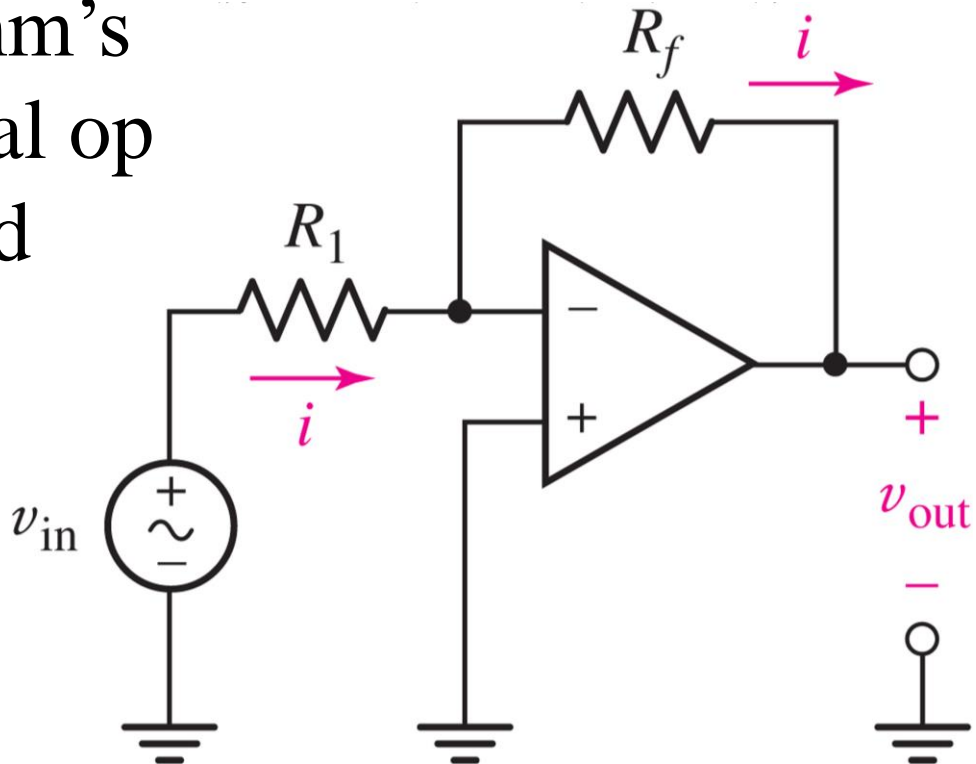


The Inverting Amplifier

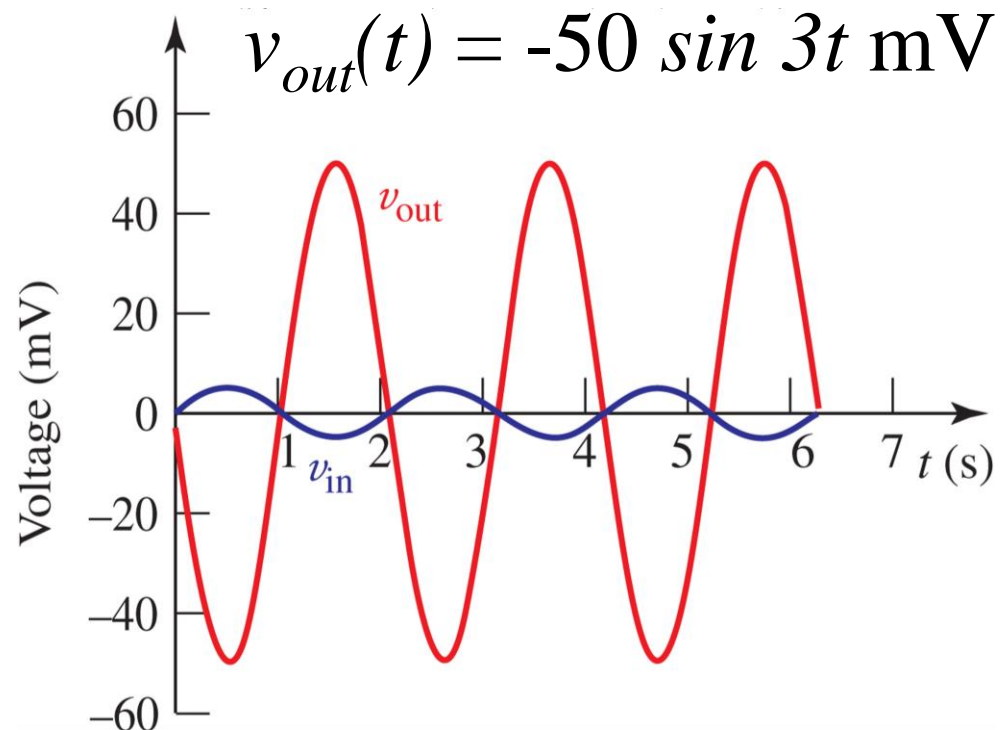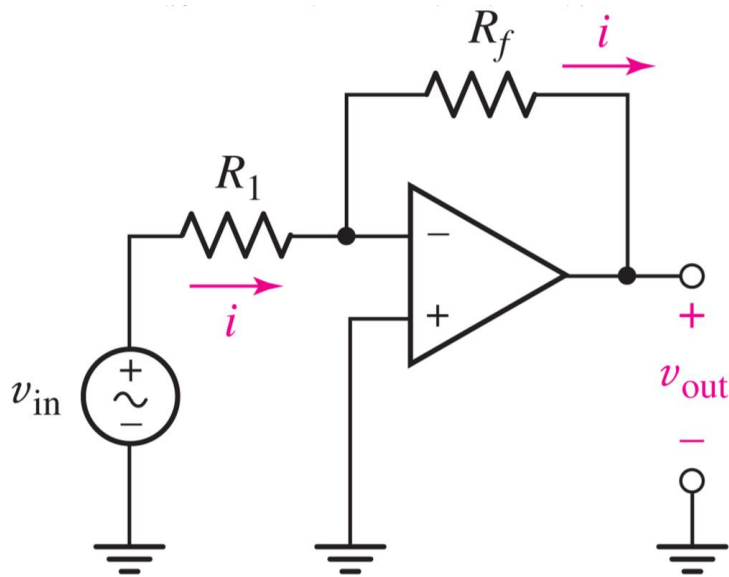Example: $v_{in}(t) = 5 \sin 3t$ mV, $R_f = 47$ k Ω , $R_1 = 4.7$ k Ω




The Non-inverting Amplifier

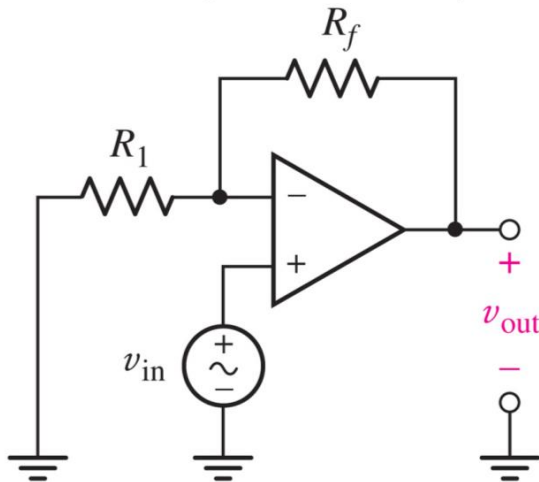



$$v_{out} = \left(1 + \frac{R_f}{R_1} \right) v_{in}$$

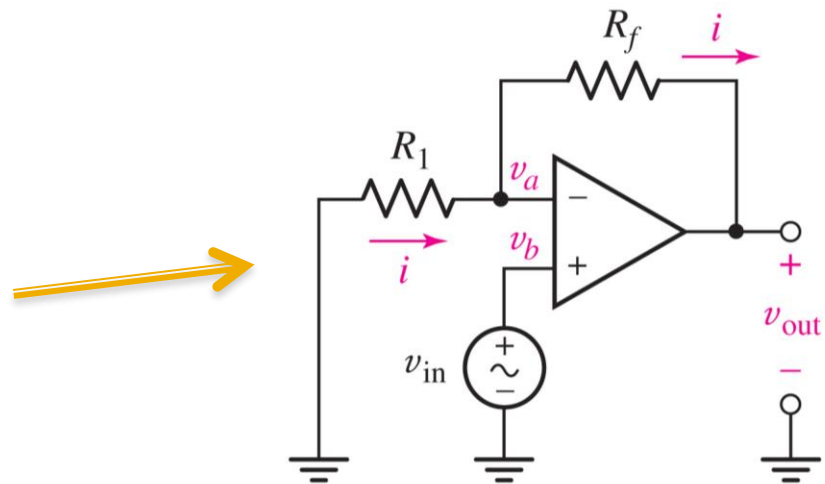To solve, use KVL, KCL,
and op amp rules.
Suggested circuit variables to
perform the circuit analysis




The Non-inverting Amplifier

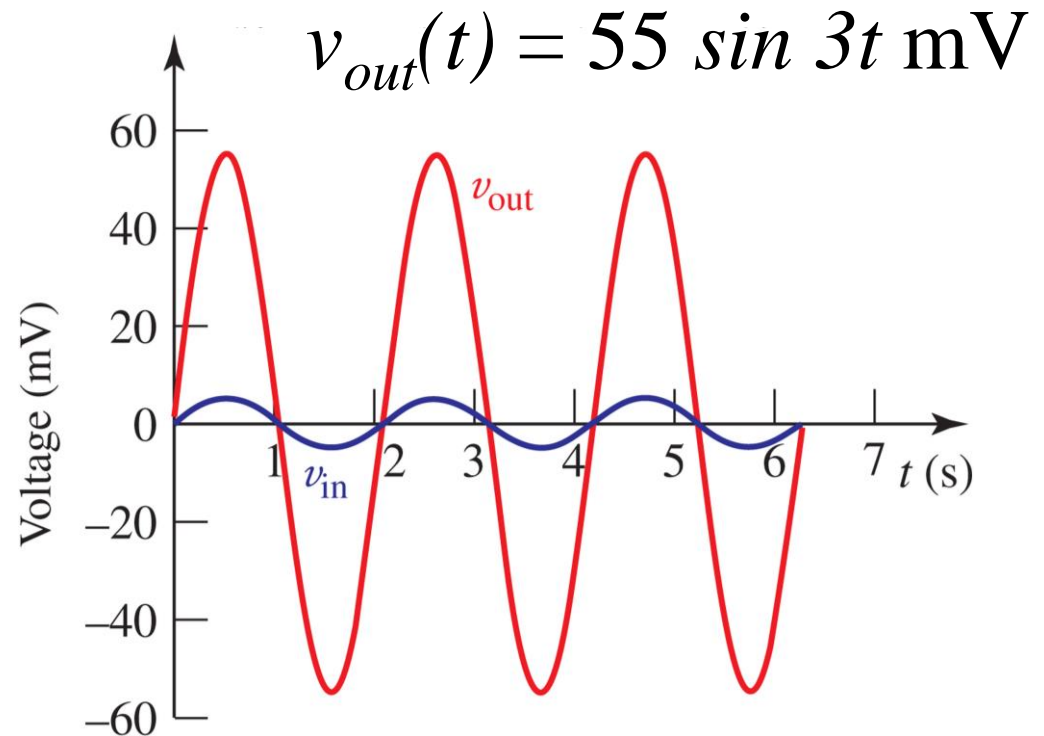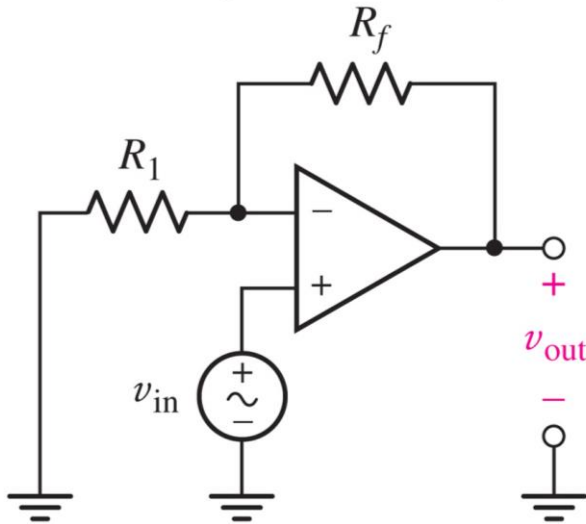Example: $v_{in}(t) = 5 \sin 3t$ mV, $R_f = 47$ k Ω , $R_1 = 4.7$ k Ω



The Voltage Follower


- $v_{out}(t) = v_{in}(t)$

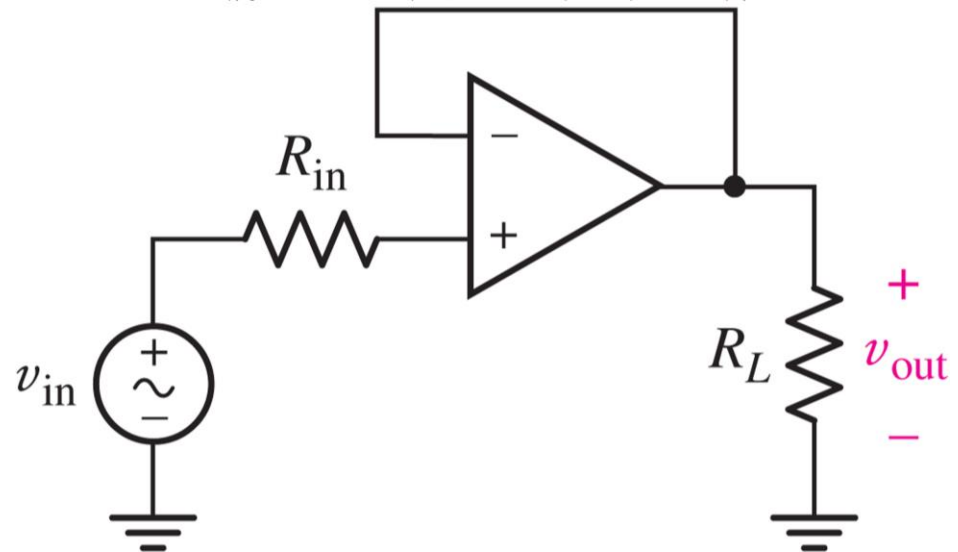

- this design allows connection of a practical voltage source to a load without experiencing voltage droop!


The Summing Amplifier
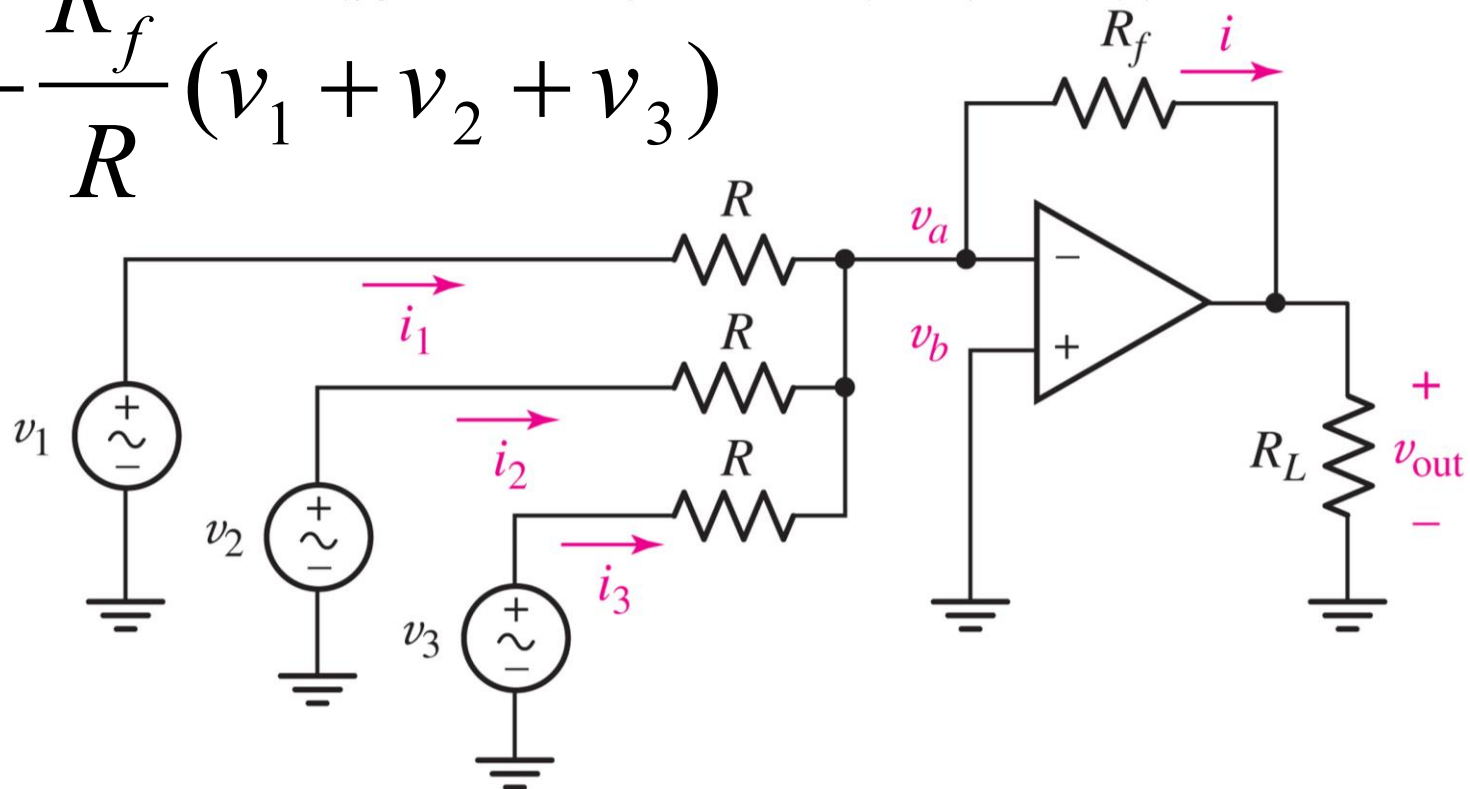
$$v_{out} = -\frac{R_f}{R}(v_1 + v_2 + v_3)$$



This amplifier performs the *operation* of adding.
It also introduces a gain of $-R_f/R$

Cascaded Stages

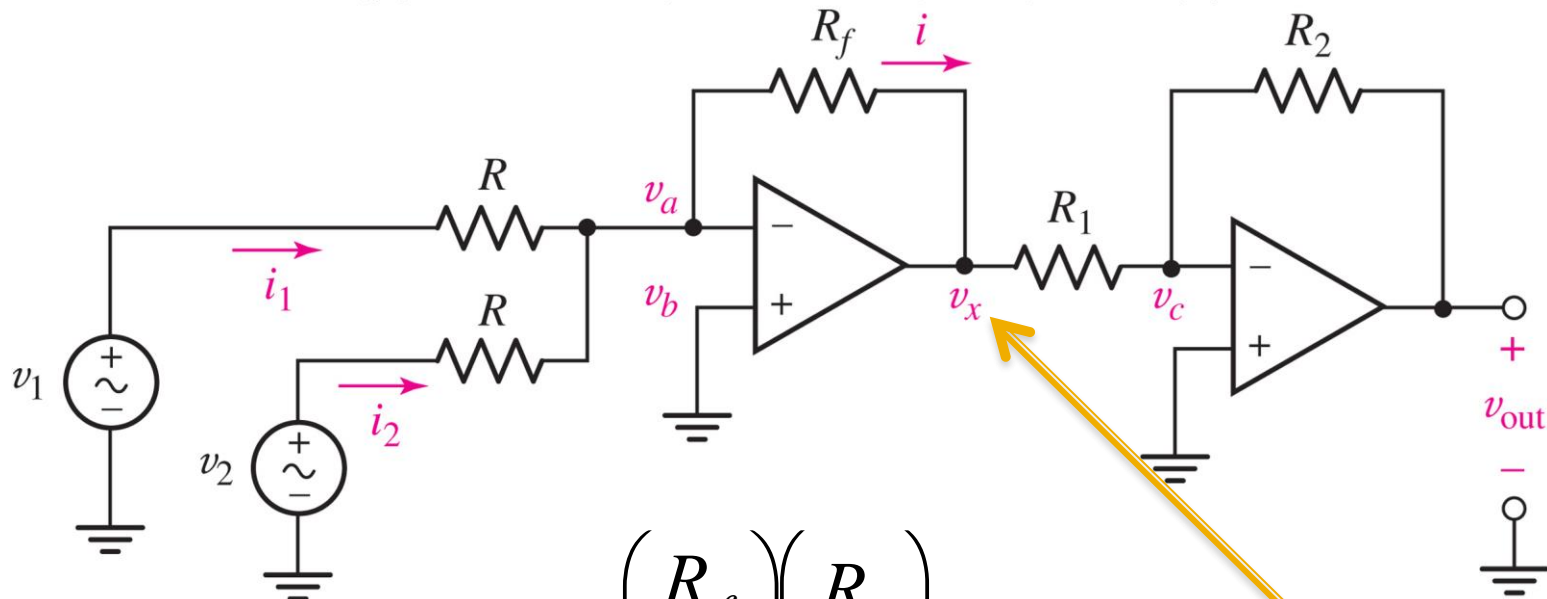


$$v_{out} = \left(\frac{R_f}{R} \right) \left(\frac{R_2}{R_1} \right) (v_1 + v_2)$$

This voltage is not affected by the circuit on the right.

Op amps can be combined in stages to create the desired relationship between the outputs and the inputs.


A Reliable Voltage Source

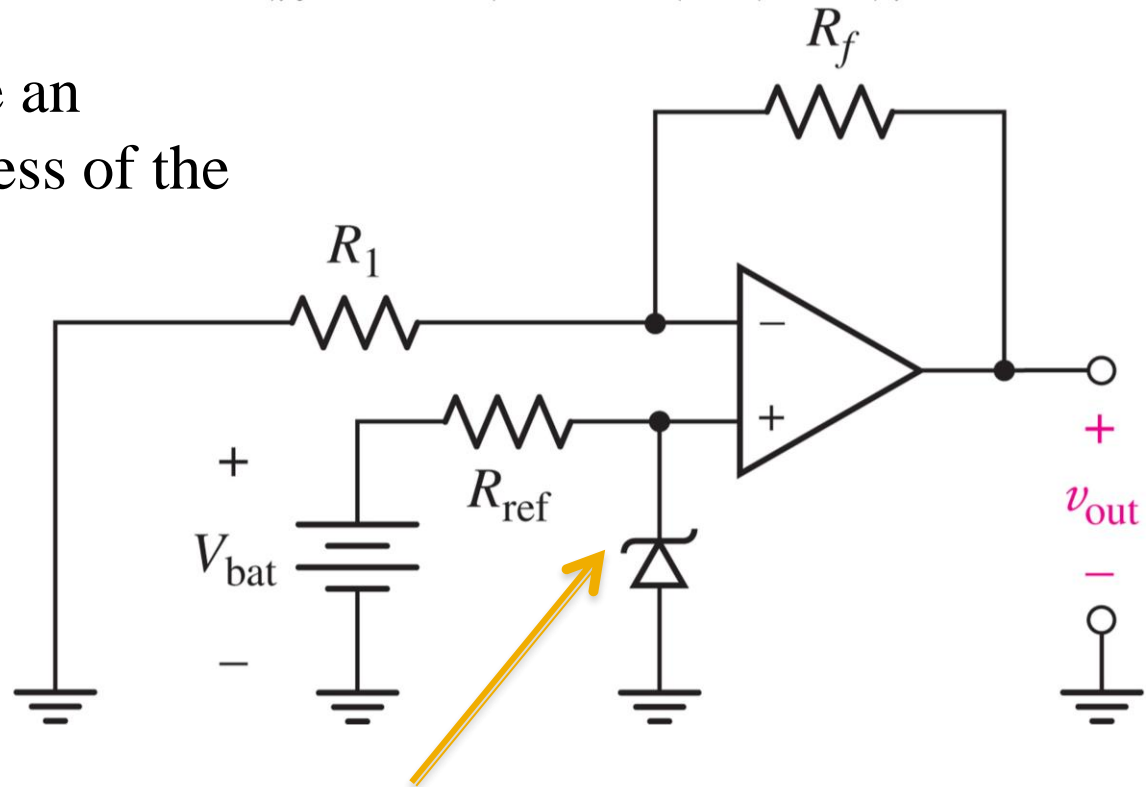This circuit will produce an accurate voltage regardless of the age of the battery V_{bat} .



Zener diode: $i=0$ if $v < 4.7$ volts

A Reliable Current Source

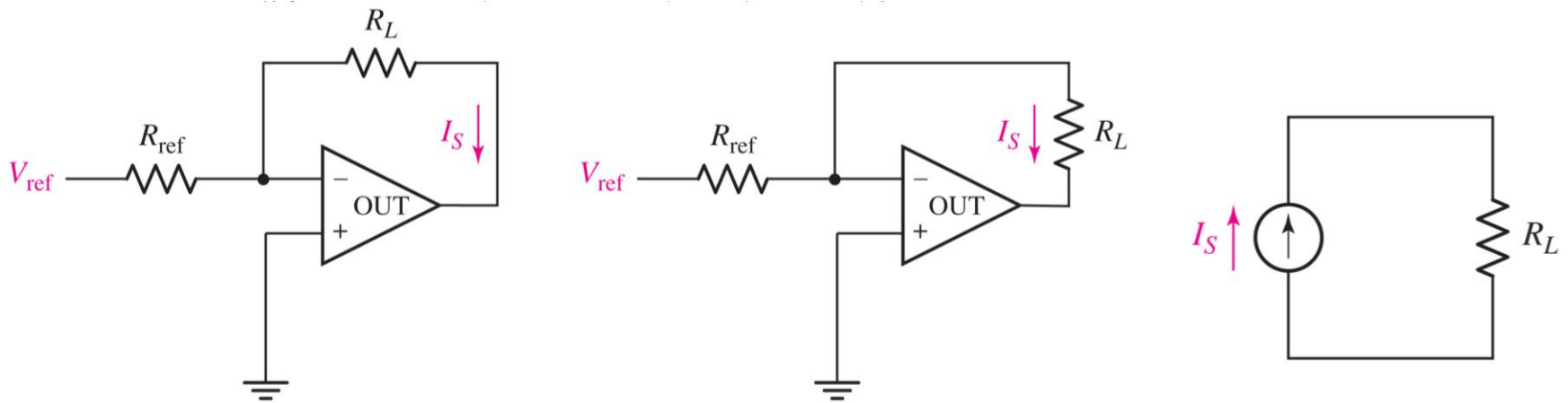


With a reference voltage source V_{ref} , we can drive a constant current $I_S = V_{\text{ref}} / R_{\text{ref}}$ through any load R_L .


A More Detailed Op Amp Model

The op amp can be modeled as a dependent voltage source, with the following components as shown:

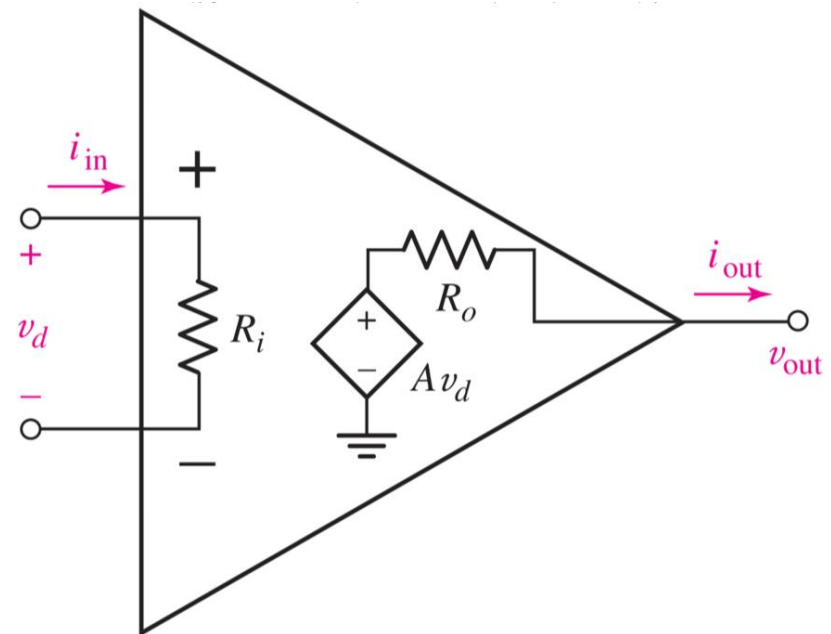- input resistance R_i
- output resistance R_o
- open loop gain A



Inverting Amplifier with a Real Op Amp

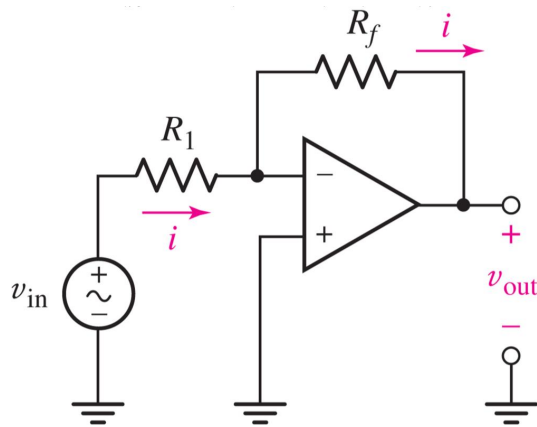

For a 741op amp ($A=200,000$, $R_i=2\text{M}\Omega$, $R_o=75\Omega$)

$$v_{out}(t) = -49.997 \sin 3t \text{ mV.}$$

An ideal op amp produces $v_{out}(t) = -50 \sin 3t \text{ mV.}$


[Analyze the detailed op amp model using nodal analysis.]

Example:

$$v_{in}(t) = 5 \sin 3t \text{ mV,}$$


$$R_f = 47 \text{ k}\Omega,$$

$$R_1 = 4.7 \text{ k}\Omega$$

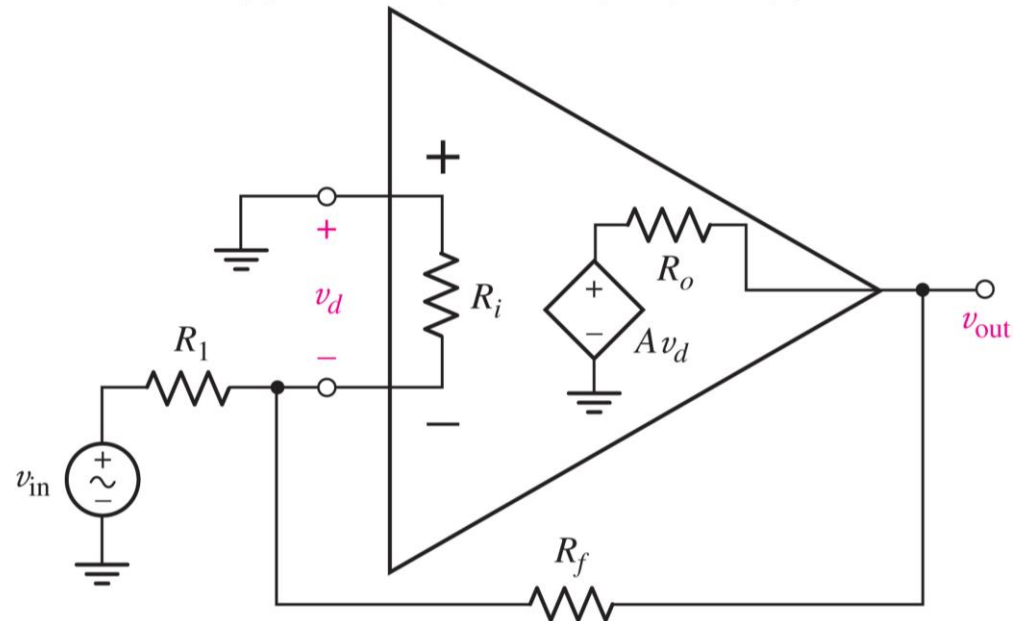

An Ideal Op Amp

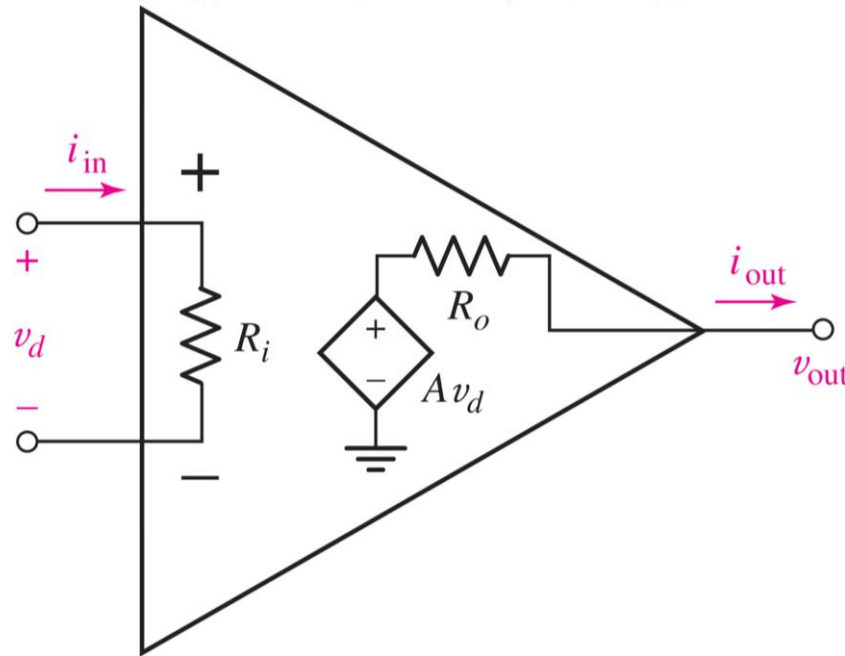
When $A=\infty$, $R_o=0\ \Omega$, and $R_i=\infty\ \Omega$, the op amp behaves according to the ideal op amp rules.
($v_d=0$ and $i_{in}=0$)



Common Mode Rejection

When $v_1 = v_2 = v_{CM}$, the output should be zero, but real op amps produce a small “common mode” voltage v_{oCM} .


$$A_{CM} = |v_{oCM} / v_{CM}|$$

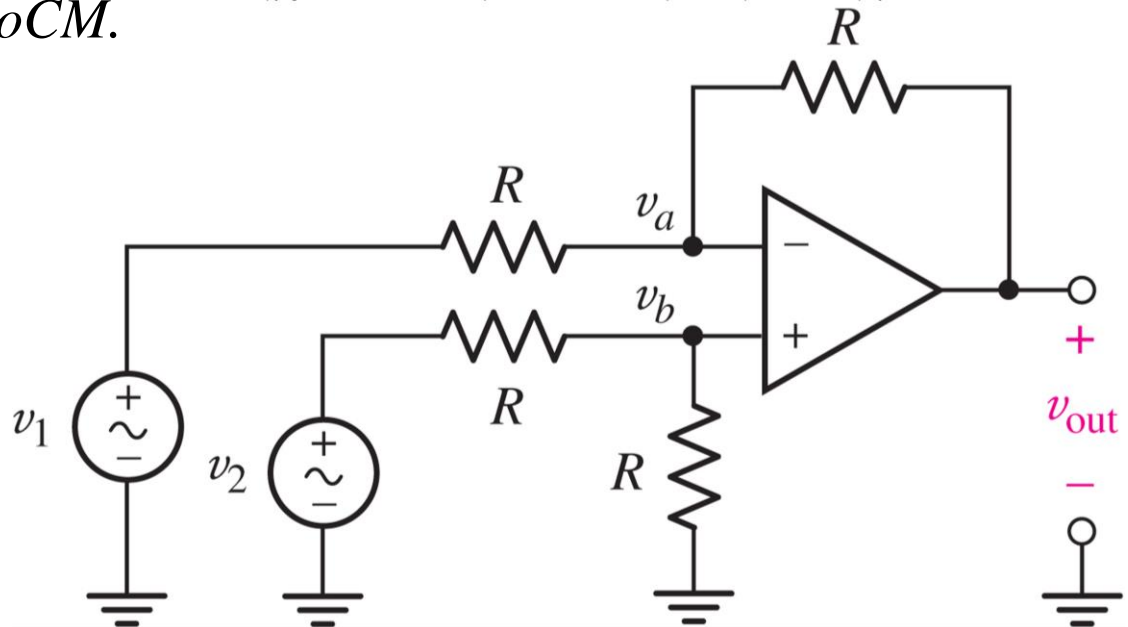

Negative Feedback

- The enormous but unpredictable gain of the op amp is made usable through negative feedback.
- When v_{in} goes up, v_d goes down, and the op amp reacts by lowering v_{out} until the “unwanted” non-zero v_d is pushed back to zero.

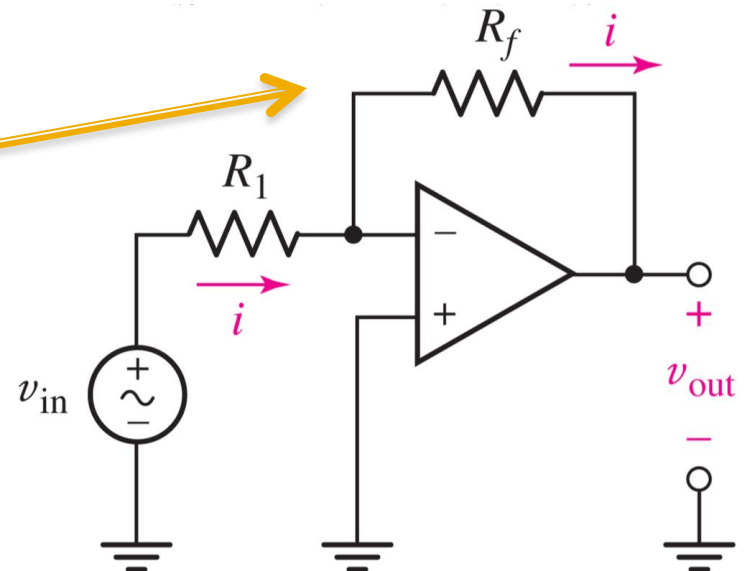
this “feedback” resistor allows the output to affect the input terminal.



Power Supplies


- An op amp requires power supplies.
- Usually, equal and opposite voltages are connect to the V^+ and V^- terminals.
- Typical values are 5 to 24 volts.
- The power supply ground must be the same as the signal ground.

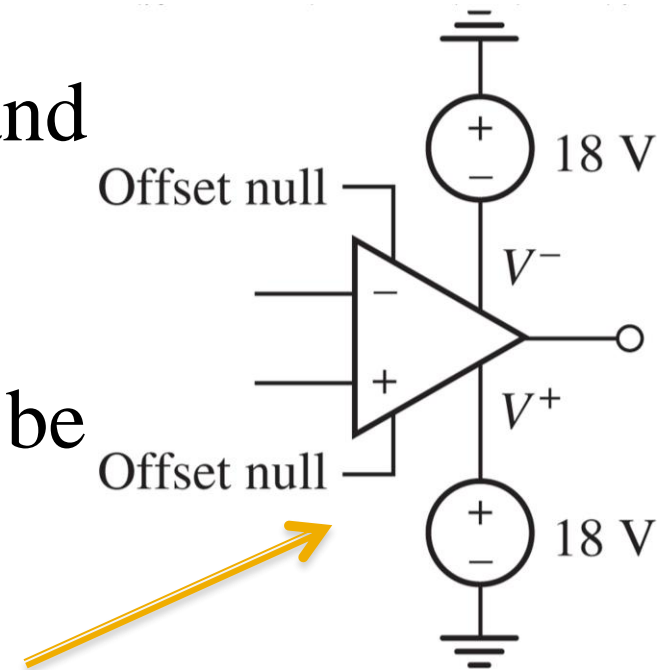in this example +18V is connected to V^+
and -18 V is connected to V^-




Saturation

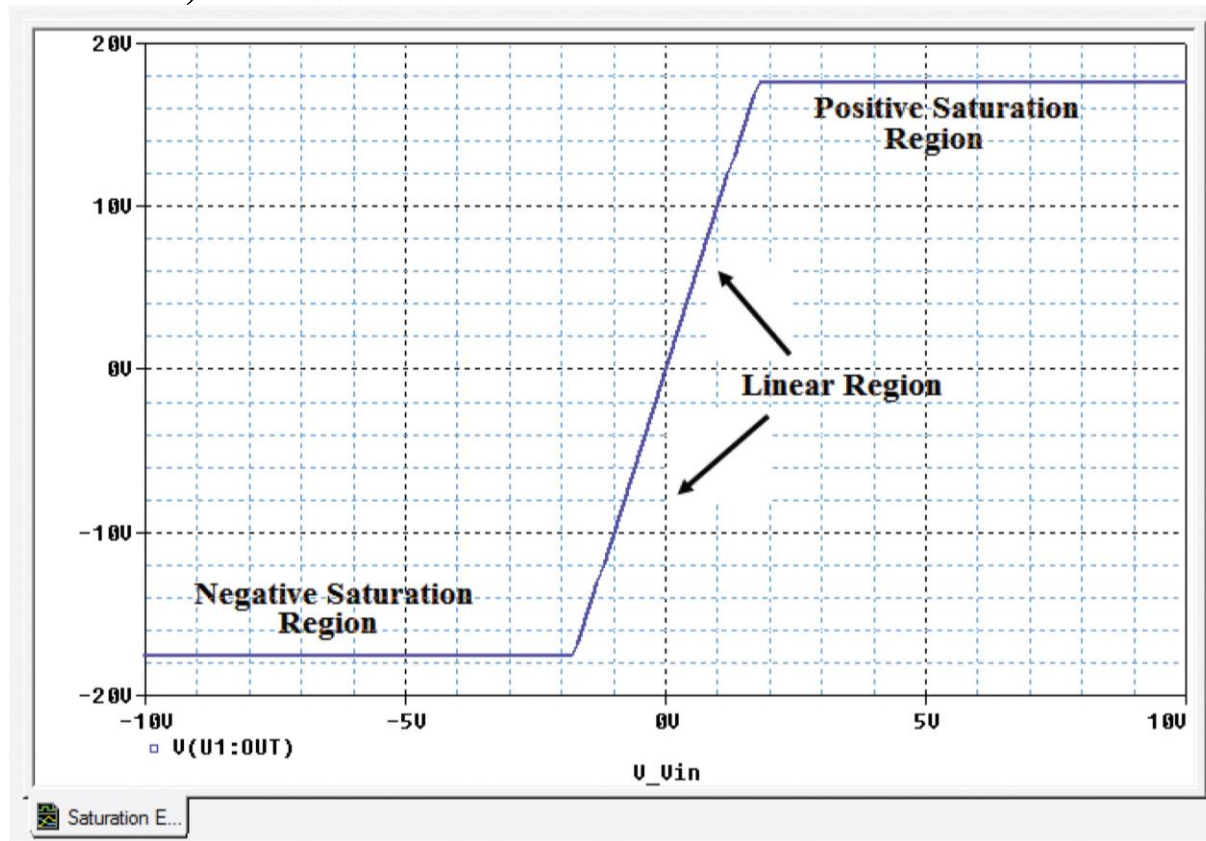$v_{out} = 10v_{in}$, but only up to the ± 18 V supplies




Input Offset Voltage

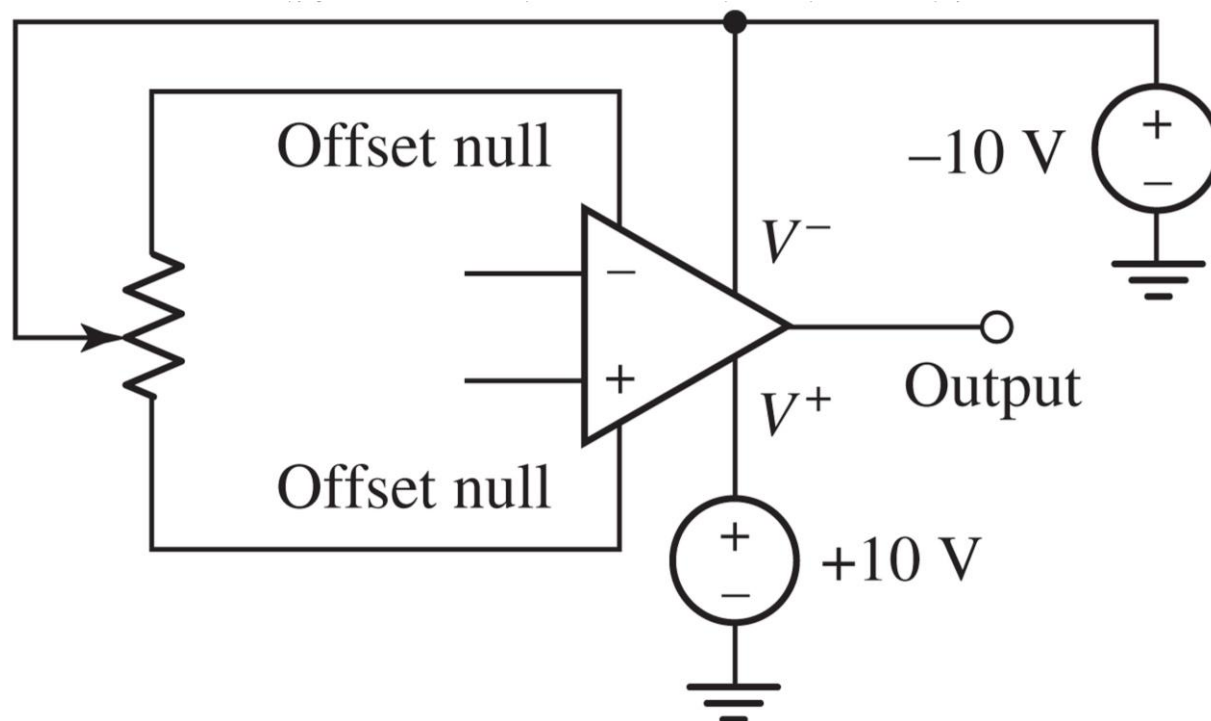Non-zero output “offsets” can be removed:



Slew Rate and Input Frequency


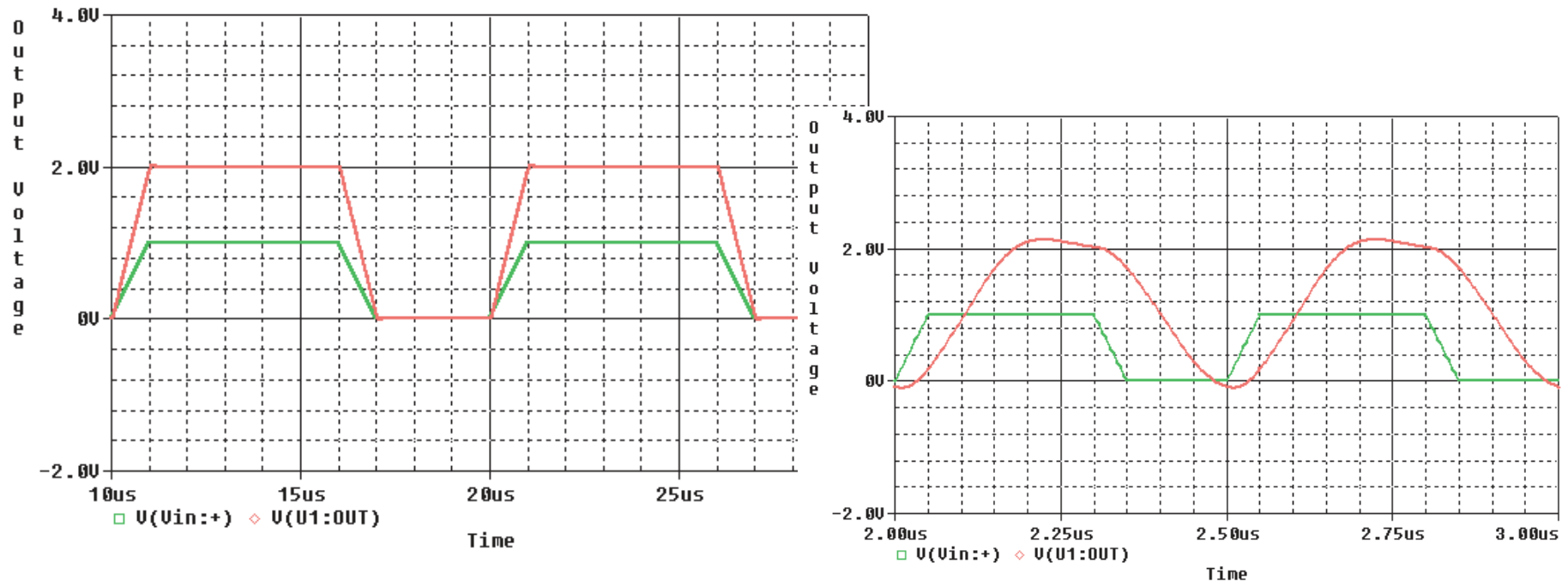
Slew rate is the maximum $V/\mu s$ for output.



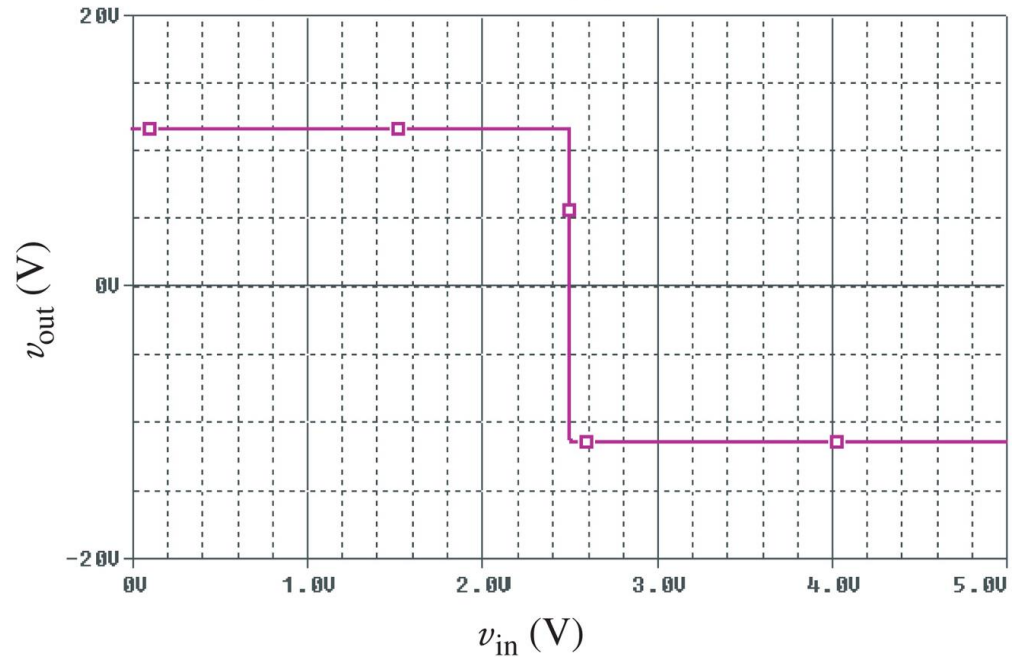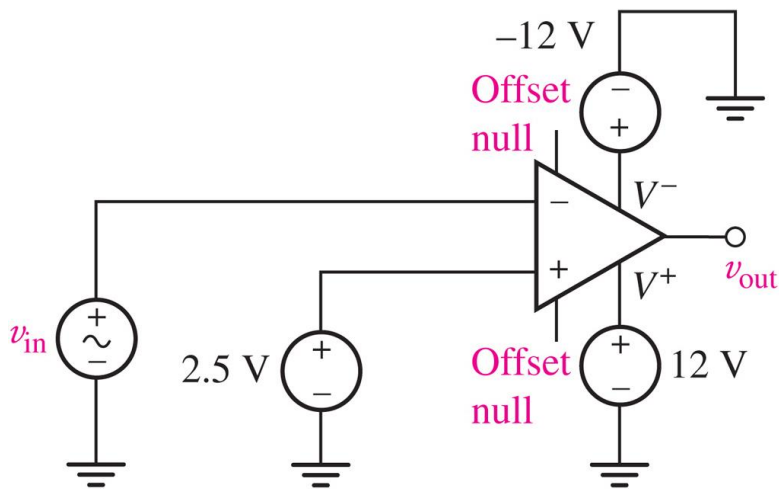- examples: input (green) and output (red)

The Comparator


- Op amps in open loop can be used to make decisions. In this case, is $v_{in} > 2.5 \text{ V}$?



Example: Comparator Design

Design a circuit that provides a “logic 1” 5 V output if a certain voltage signal drops below 3 V, and zero volts otherwise.

Answer:

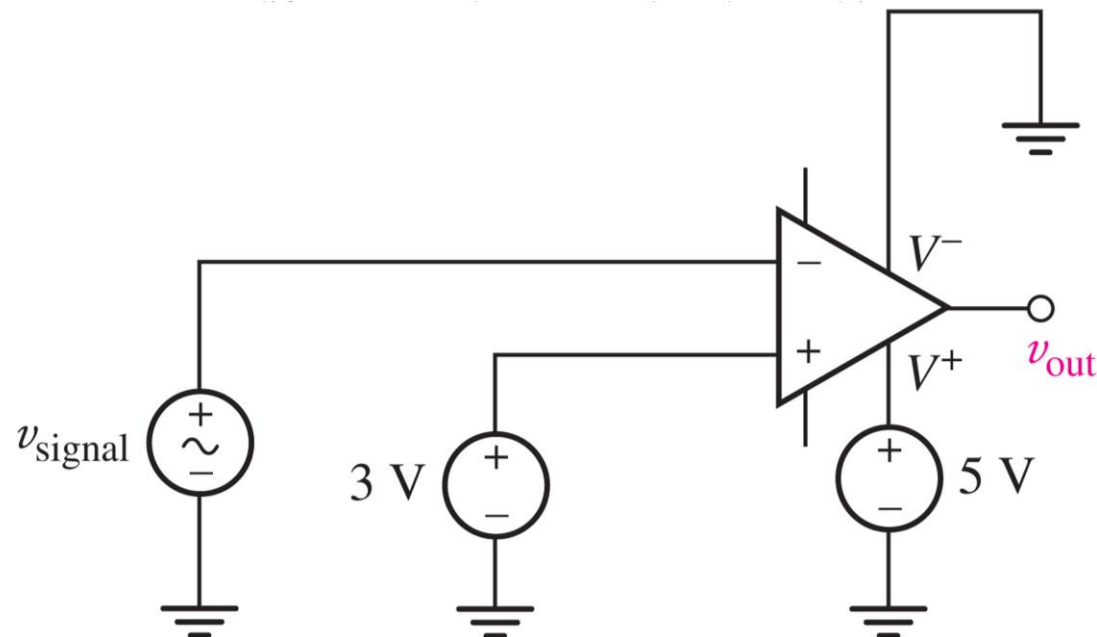

The Instrumentation Amplifier

This device allows precise amplification of small voltage differences:

$$v_{out} = K(v_+ - v_-)$$

