

Lecture 10
of
EEE307

Electronics for Communications

Department of Electrical & Electronic Engineering
Xi'an Jiaotong-Liverpool University (XJTLU)

Friday, 22nd November 2019

□ Phase Locked Loop

- phase detector & type I PLLs
- loop dynamics (phase domain)
- PFD & type II PLLs
- charge pump PLLs


□ Frequency Synthesizers



Radio Transmitters & Receivers

(local oscillator signal required)

 - ❑ In radio transmitters and receivers, a **local oscillator** (LO) signal is required as a mixer input for the upconversion and downconversion to and from the carrier frequencies of the radio waves.



From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.

- ❑ While a **voltage-controlled oscillator** (VCO) can generate such a required signal, it is not used alone to feed the LO port of the mixers.



Xi'an Jiaotong-Liverpool University
西交利物浦大学


Signal-Generation with VCO

(open-loop problems)


- ❑ A VCO is seldom used in the open-loop condition for signal generation in wireless transmitters and receivers:

From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.

 - open-loop: fix the input voltage V_{cont} and get a sinusoidal signal of the desired frequency



 - It is like the uncommon open-loop use of operational amplifiers. (What would be the problems?)




Frequency Synthesizer as LO

(VCO in phase locked loop)

- ❑ A VCO is usually used in the so-called **phase-locked loop (PLL)** for generating LO signals in a transceiver.

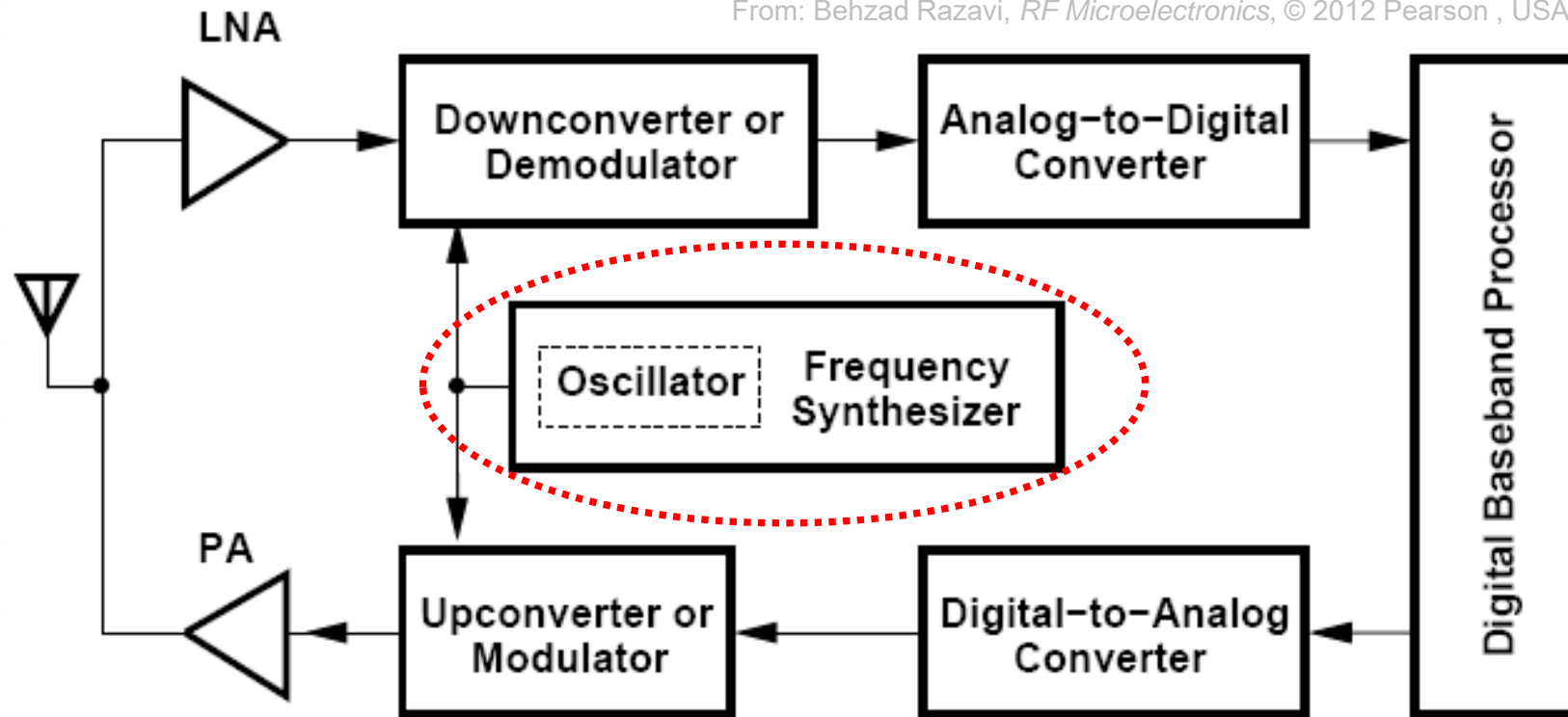From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.



- It is called a **frequency synthesizer**.



Xi'an Jiaotong-Liverpool University

西交利物浦大学

VCO in Phase Locked Loop

(stable synthesized frequencies)

- ❑ By using a VCO in a **PLL** for **frequency synthesis** (i.e. generating sinusoidal electrical signals of desirable frequencies), a highly stable yet tunable LO signal can be created for radio transceivers.
 - The VCO is treated as a linear time-invariant system and configured in a feedback system to form the PLL.
 - The **synthesized frequencies** of the **PLL** output are a multiple of a reference frequency (e.g. by a crystal oscillator), with the same **frequency stability** and precision as that of the reference input.
 - Do you remember **crystal oscillators**?
Signal generation with stable ω_{osc} .



Xi'an Jiaotong-Liverpool University
西交利物浦大学

Usefulness of Phase Locked Loops

(in FM communication & digital systems)

- ❑ Apart from **frequency synthesis** or **multiplication** from highly stable low-frequency signals, **PLLs** can also be used for **frequency modulation** (FM) and frequency demodulation which are important in FM communication.
- ❑ **PLLs** are also used in digital systems, especially in data communications, for signal **synchronisation**.
 - in microprocessors for **skew reduction** or **compensation** to overcome the delay between the buffered clock signal and the data stream; a delay locked loop is an alternative
 - also in harddisk drive electronics in reading and transferring data




Xi'an Jiaotong-Liverpool University
西交利物浦大學

PLLs in Clock & Data Recovery

(digital data streams)

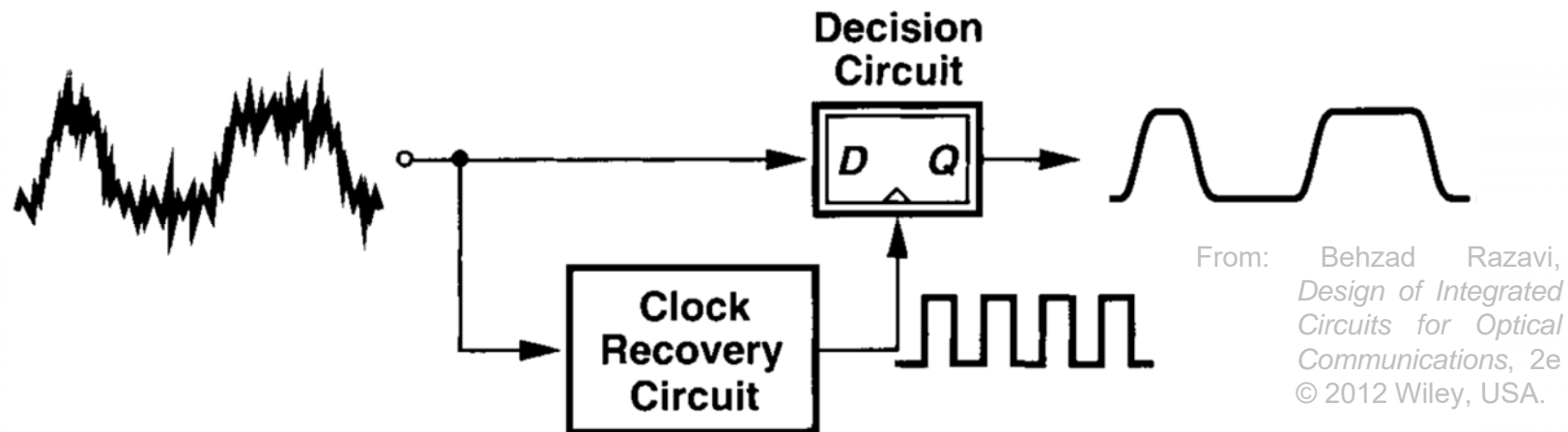
- ❑ An important application of PLLs is **clock recovery**, namely, **recovering clock timing** information from an **incoming data stream** corrupted by noise.
 - The incoming data is sometimes also cleaned up and the whole process is known as **clock and data recovery (CDR)**.



- CDR is necessary in high-speed asynchronous serial data links.

Optical Communication Systems

(frequency synthesis & clock recovery)

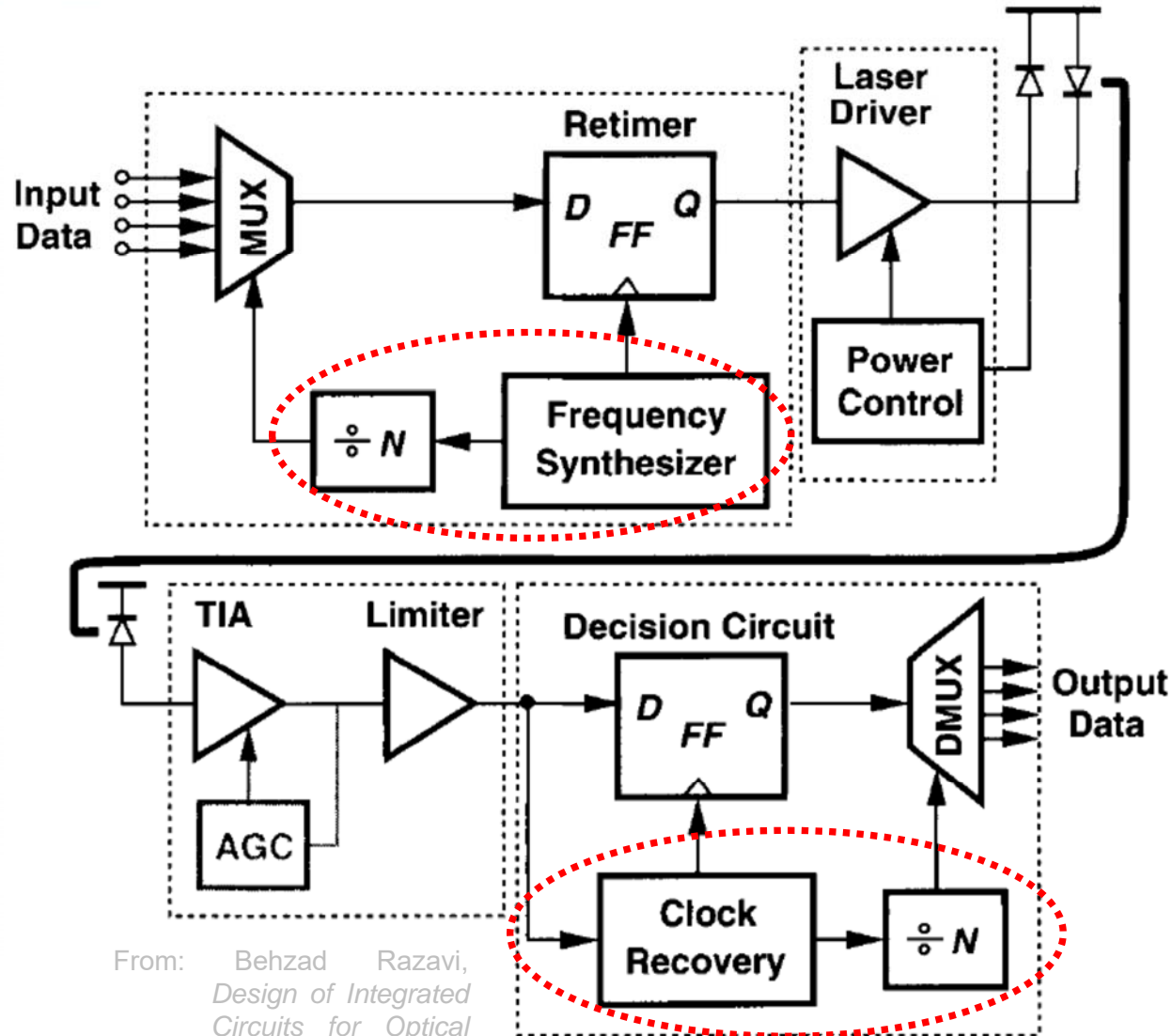

From: Behzad Razavi,
*Design of Integrated
Circuits for Optical
Communications*, 2e
© 2012 Wiley, USA.

□ Frequency synthesis and clock recovery are essential in fibre-optic communication systems.

⇒ importance of **PLLs** in modern communication systems.

Phase Locked Loop

(three basic constituents)

- ❑ A **phase-locked loop (PLL)** is a negative *feedback* system with the output signal tracking the input signal by comparing the phase (and frequency) of the output with that of the input.
- ❑ A PLL consists of three basic parts cascaded together and forming a closed loop:
 - a **phase detector** (a phase/frequency detector in better designs of PLLs)
 - a low-pass loop filter
 - a **voltage-controlled oscillator (VCO)**
 - a feedback divider in some cases




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Phase Detector

(detecting phase difference)

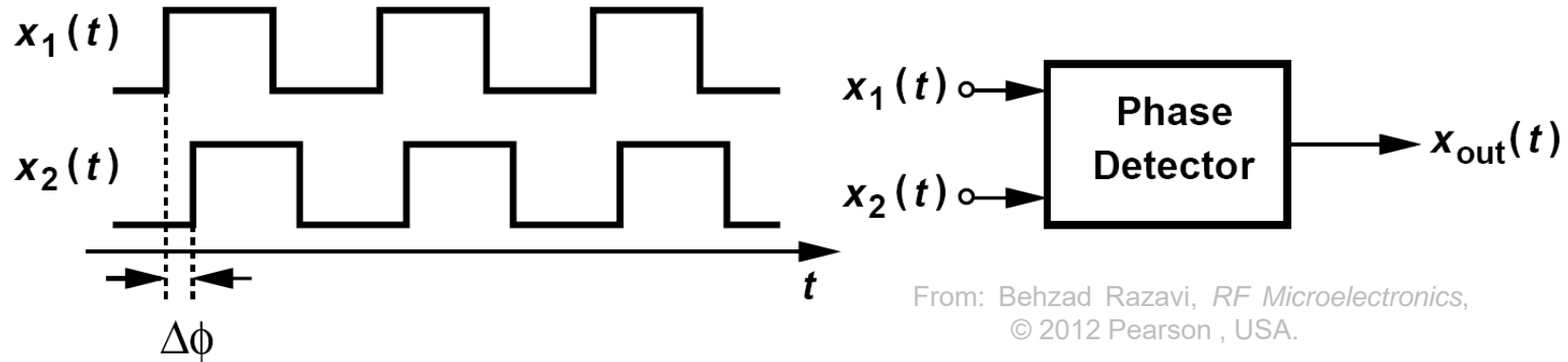- A **phase detector** is a circuit that senses two periodic inputs and produces an output which has an average value proportional to the difference between the phases of the inputs.




From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.

- The input/output characteristic of the PD is ideally a straight line, with its slope called the “gain” and denoted by K_{PD} .

Phase Detector


(implementation using XOR gate)

 - ❑ An **exclusive-OR (XOR)** gate can serve this purpose of phase difference detection. It generates pulses which have the pulse width equal to $\Delta\phi$.



$$F = A \oplus B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

 


From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.

- An **XOR gate** outputs a logic “1” only when the two inputs are different.

Implementation of XOR Gate


(5 logic gates & 12 MOSFETs)

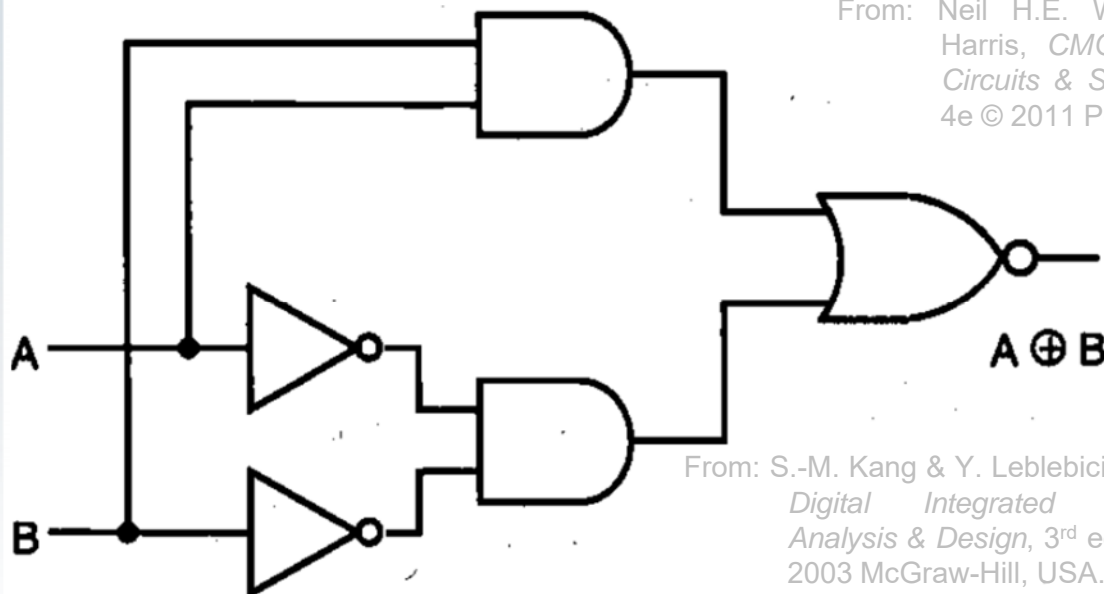- ❑ Based on the truth table and Boolean algebra, the **XOR** gate can be implemented using the fundamental logic gates: $F = A \oplus B = A'B + AB'$
- ❑ The XOR gate can be implemented by 12 CMOS transistors (4 for two inverters).



From: Neil H.E. Weste & David M. Harris, *CMOS VLSI Design: A Circuits & Systems Perspective*, 4e © 2011 Pearson, USA.

 From: S.-M. Kang & Y. Leblebici, *CMOS Digital Integrated Circuits: Analysis & Design*, 3rd edition, © 2003 McGraw-Hill, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大学

Implementation of XOR Gate


(transmission gate approach using 10 MOSFETs)

 - ❑ There can be improvement in the CMOS implementation of the **XOR** gate to make it more **compact** (i.e. smaller size):
 - modified interconnections of MOSFETs for slightly more area-efficient physical layout.






- design with two transmission gates

 From: Neil H.E. Weste & David M. Harris, *CMOS VLSI Design: A Circuits & Systems Perspective*, 4e © 2011 Pearson, USA.



save contacts
at two S/D
regions

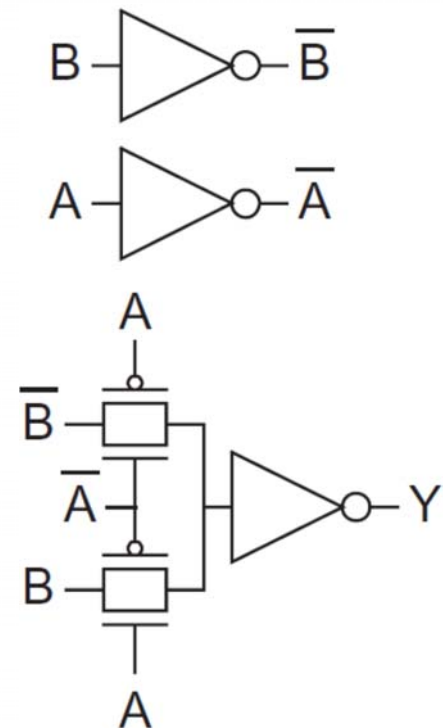  


Simple Phase Locked Loop

(dynamic negative feedback control)

- ❑ As the output of the **phase detector (PD)** is proportional to the **phase difference** $\Delta\phi$, it is fed to the input of the VCO to vary the frequency so that the VCO output will have zero $\Delta\phi$ through dynamic **feedback control**.

 From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.




- When $\Delta\phi$ is large, the VCO will be driven accordingly to vary the frequency in such a way to minimise $\Delta\phi$.
- When $\Delta\phi \approx 0$, the input voltage of the VCO is fixed and the frequency of the VCO output remains constant.
- It is a **negative feedback system**.



Xi'an Jiaotong-Liverpool University
西交利物浦大学

Simple Phase Locked Loop

(phase locking)

 

- ❑ The **phase locking** in the simple PLL through **dynamic negative feedback control** can be illustrated by trying to align the output phase of the VCO output with that of a reference clock.
 - At t_0 , the VCO output frequency increases with a larger V_{cont} and gradually decreases the phase error.
 - At t_1 , the phase alignment is achieved and the VCO frequency stops increasing with V_{cont} returned to its original value.




Xi'an Jiaotong-Liverpool University
西交利物浦大学

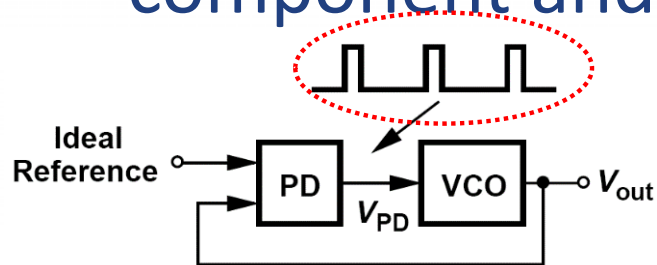Problem of Simple PLL


(sidebands at the output)

- ❑ In the simple PLL, the PD produces **repetitive pulses** at its output. Such a signal consists of a DC component and a high frequency component.




From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.

 From: "Spectrum Analysis Amplitude and Frequency Modulation," Keysight Technologies Application Note (July 31, 2014)..



 - The latter is undesirable because it **modulates** the VCO frequency and hence generate large **sidebands**.
- This is a situation of **frequency modulation (FM)**.




Xi'an Jiaotong-Liverpool University
西交利物浦大学

Basic PLL Topology

(with low-pass filter)

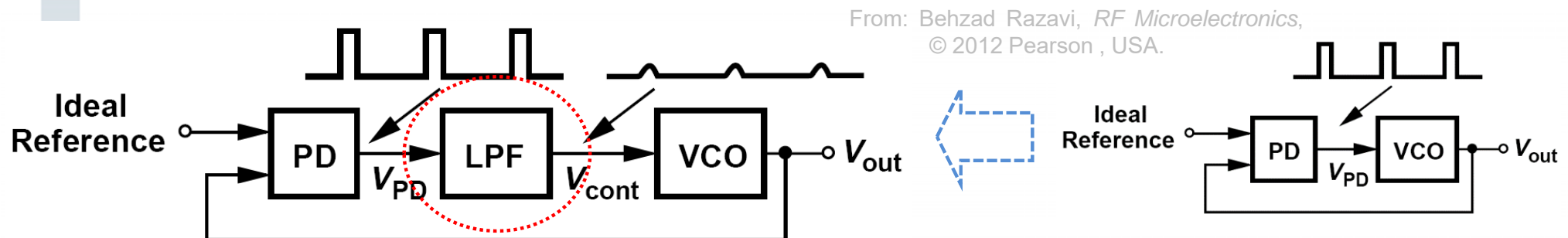- ❑ To resolve the problem of the **sidebands** at the VCO output, the high frequency component of the PD output can be *filtered*.
- ❑ A **low-pass filter** is placed between the PD and the VCO to suppress the *repetitive pulses*.



- ❑ This forms the basic PLL topology (called type I PLL).

- 3 essential constituent blocks:
PD, LPF and VCO in a feedback loop.





Xi'an Jiaotong-Liverpool University
西交利物浦大学

Phase Locked Loop

(simple implementation)

- ❑ A simple PLL can be implemented with an XOR gate, a *first-order* RC low-pass filter and a **cross-coupled LC oscillator**.

 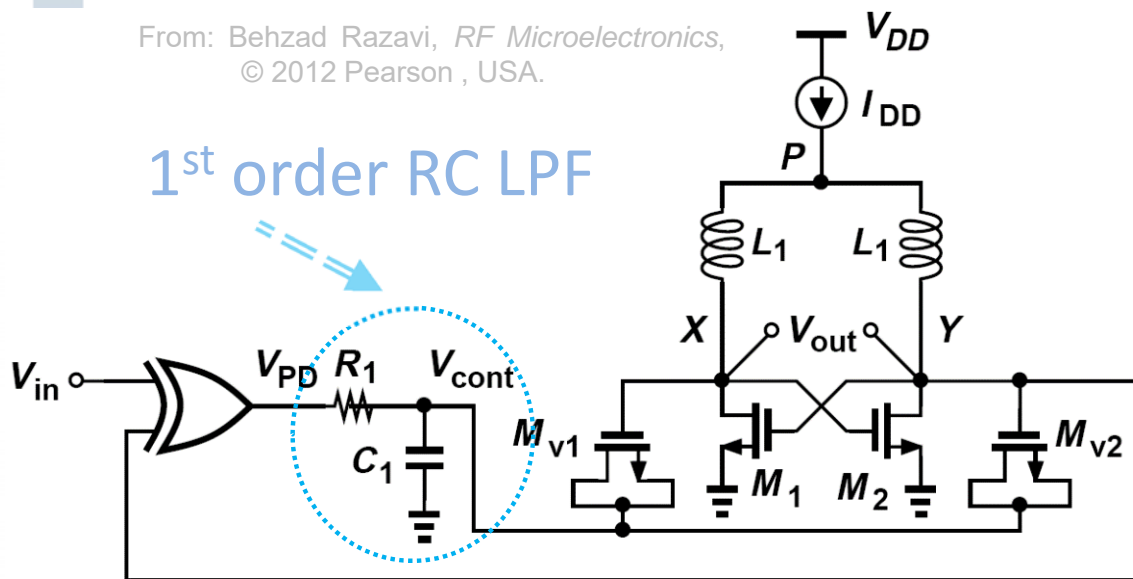From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.




- Note the differential output (at nodes X and Y) with the cross-coupled LC oscillator.

Phase Locking in PLL


(voltage follower analogy)

- ❑ We say a **PLL** is an electronic circuit that **locks** the **phase** of the output to that of the input.
 - To illustrate the **phase locking** concept, the voltage follower analogy can be used.
 - In the voltage follower configuration, if the op amp has a large enough voltage gain, the output voltage “**tracks**” the input voltage closely.

 From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.



 
- Similarly, a PLL ensures that $\phi_{out}(t)$ tracks $\phi_{in}(t)$, in other words, the output **locked** to the input in the **phase domain**.



Phase Locking in PLL

(exactly equal frequencies)

 - We say the loop is “locked” if $\phi_{out}(t) - \phi_{in}(t)$ is constant with time \Rightarrow the output is **synchronised** with the input.



- When **phase locking** is achieved, there is an important and unique consequence - the input and output frequencies of the PLL are precisely equal.

$$\phi_{out}(t) - \phi_{in}(t) = \text{constant}$$

$$\frac{d\phi_{out}}{dt} - \frac{d\phi_{in}}{dt} = 0 \Rightarrow \frac{d\phi_{out}}{dt} = \frac{d\phi_{in}}{dt} \Rightarrow \omega_{out} = \omega_{in}$$

- This attribute is critical in using PLLs for frequency synthesis.

- In a stand-alone VCO, $\omega_{out} = \omega_{in} + K_{VCO} V_{cont}$




Xi'an Jiaotong-Liverpool University


西交利物浦大学

Phase Locked Loop

(transient response in V_{cont})

 

 From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.



- V_{cont} reveals more the transient behaviour of the PLL.




Phase Locked Loop

(transient response)

- ❑ The **transient response** of PLLs is generally a nonlinear phenomenon. (Do you know why?)
- ❑ It can be viewed with the voltage follower analogy.

slow input
sinusoid

fast input
sinusoid

   


little
attenuation





much attenuated
sinusoidal output

From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.

Slow Phase Change

 

Fast Phase Change

    

- How about a PLL's response to varying phase change?




Xi'an Jiaotong-Liverpool University
西交利物浦大学

Loop Dynamics

(phase domain)

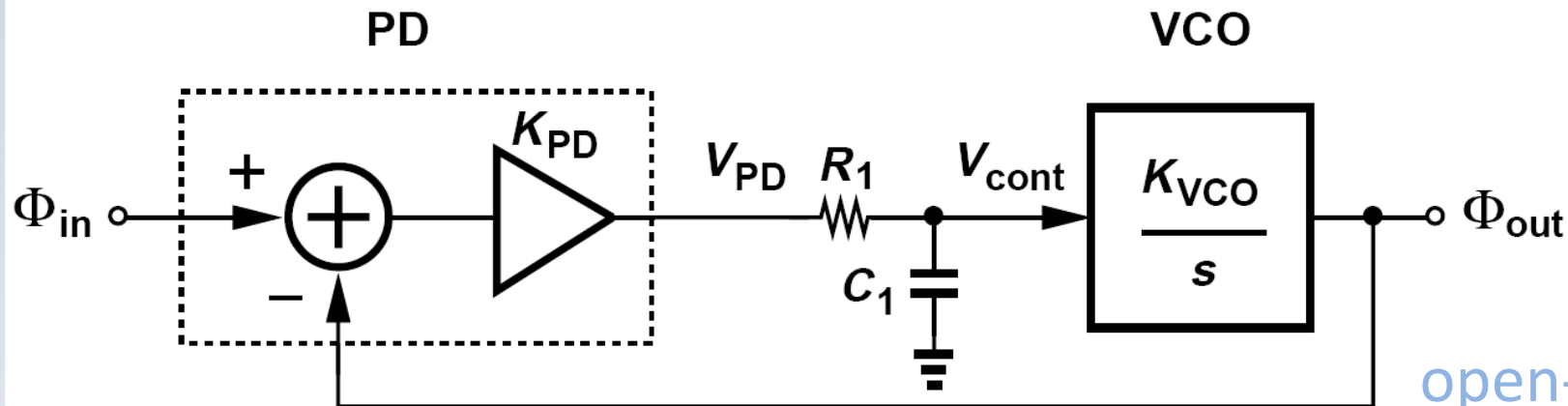- ❑ A “**phase-domain model**” can be constructed for studying PLLs’ transient response using a linear approximation.



From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.

open-loop
transfer function

- The closed-loop transfer function:

$$H(s) = \frac{\Phi_{out}(s)}{\Phi_{in}(s)} = \frac{K_{PD}K_{VCO}}{R_1C_1s^2 + s + K_{PD}K_{VCO}}$$

$$\frac{K_{PD}}{(R_1C_1s + 1)} \left(\frac{K_{VCO}}{s} \right)$$



Xi'an Jiaotong-Liverpool University
西交利物浦大学

Loop Dynamics


(transient responses in time domain)

- Based on the **closed-loop transfer function**, it can be seen that the PLL is a second-order feedback system.

From: Behzad Razavi, *Design of Integrated Circuits for Optical Communications*, 2e © 2012 Wiley, USA.


$$H(s) = \frac{\Phi_{out}(s)}{\Phi_{in}(s)} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

 - A system with a second-order transfer function can have the following transient responses:



- overdamped
- critically damped
- under-damped

depending on the damping factor

 

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD} K_{VCO}}}$$




Xi'an Jiaotong-Liverpool University
西交利物浦大学

PLL for Frequency Multiplication

(divided output fed back to input)

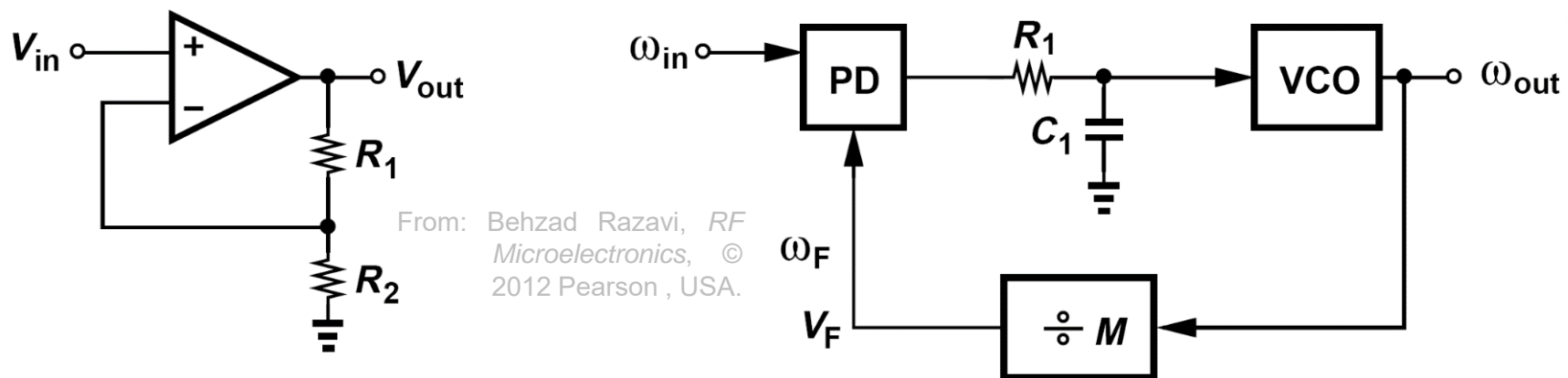- A PLL can be configured to generate an output frequency which is a **multiple** of the input frequency.
 - This is done by **dividing** the output frequency of the PLL and then feeding back to the input.
 - The analogy is the non-inverting amplifier.



- The $\div M$ circuit is a **counter** that generates one output pulse for every M input pulses.
 - The divide ratio, M , is called the “modulus”.



Xi'an Jiaotong-Liverpool University

西交利物浦大学

Limitations of Type I PLL

(unequal input frequencies)

- ❑ The type I PLL is rarely used for making modern frequency synthesizers for modern communication systems.
 - It suffers from a limited “**acquisition range**”. If the VCO frequency and the input frequency are very different at the startup, the type I PLLs may never achieve “**phase locking**”
 - The limitation is because phase detectors produce little information if sensing inputs of *unequal* frequencies.
- ❑ A **frequency detection** function needs to be added to the phase detector in the PLL.




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Phase/Frequency Detection

(sensing both phase & frequency difference)

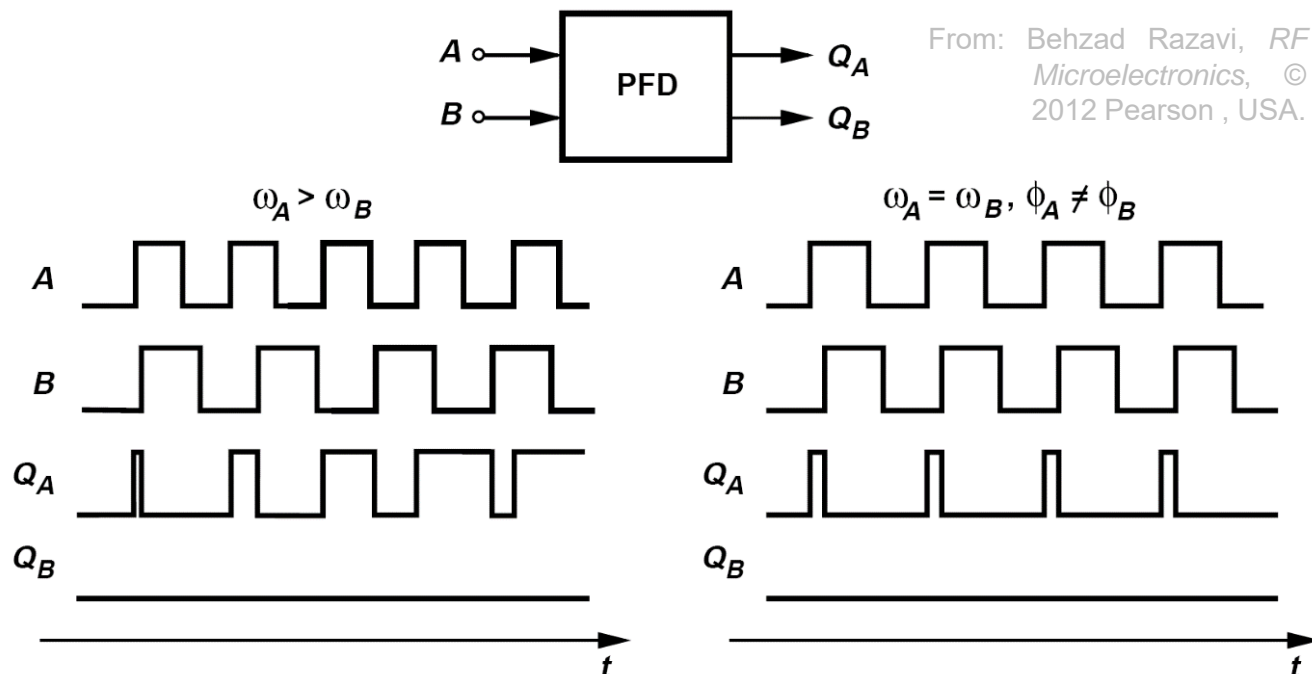- A phase/frequency detector has two outputs Q_A and Q_B , sensing both the phase and frequency of the two inputs A and B .
 - Sequential logic (vs. XOR as combinational logic) is used.





- Q_A outputs pulses whose width is proportional $\phi_A - \phi_B$ while $Q_B = 0$.
- If A has a lower frequency than B , Q_B outputs pulses.

Phase/Frequency Detector

(D-flipflop implementation)

  - ❑ The **phase/frequency detector** (PFD) can be realised using two **D-flipflops** and one AND logic gate.
 - Signals **A** & **B** are inputted as the clocks of the D-flipflops.



- The D-flipflop can be implemented using four cross-coupled NOR gates.




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Improved Type I PLL

(with phase/frequency detector)

 - ❑ Using a phase/frequency detector (PFD), the design of the type I PLL can be improved to resolve issue of the limited **acquisition range**.
 - The PFD has two outputs, Q_A and Q_B . A differential amplifier can be used to extract the DC component of ($Q_A - Q_B$) with two low-pass filters.




- Note the polarity of Q_A and Q_B fed to the differential inputs of the amplifier.

From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.

Charge Pump

(switched current sources)

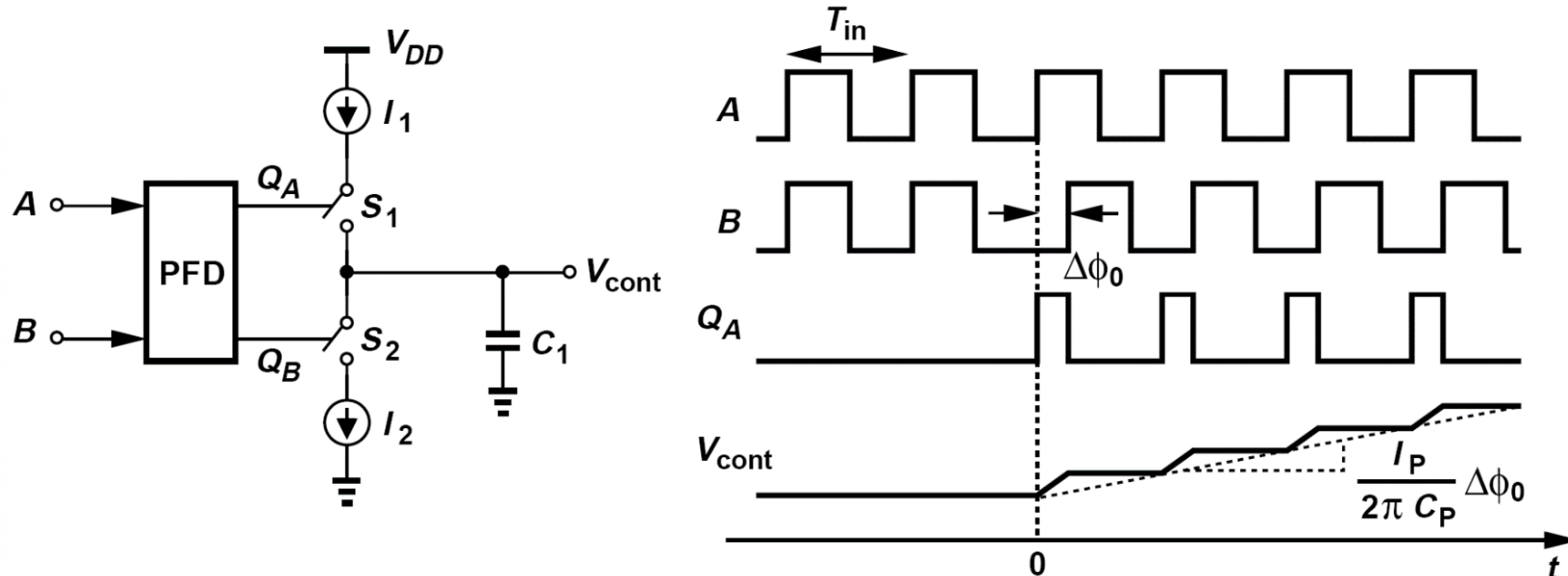- ❑ The more common approach to process the two outputs Q_A and Q_B using a **charge pump** interposed between the PFD and VCO in the PLL.




- A charge pump consists of two **switched** current sources that **pump charge** into or out of the loop filter according to the inputs.

Charge-Pump PLL

(added resistor for better stability)

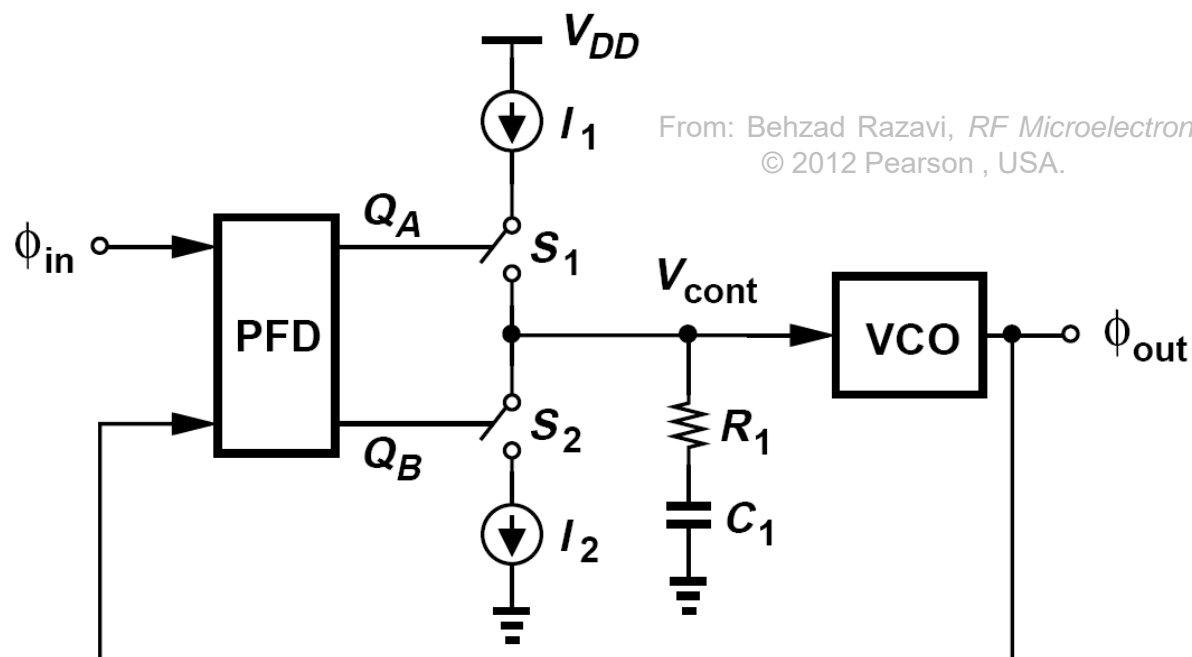- ❑ Skipping analysis of the loop dynamics, a better design of PLLs using a **charge pump** is obtained with an added resistor R_1 in series with the capacitor C_1 . This is called the **charge-pump PLL**.





- This is a type II PLL used to build frequency synthesizers.

Charge Pump CMOS Circuit

(implementation of switched current sources)

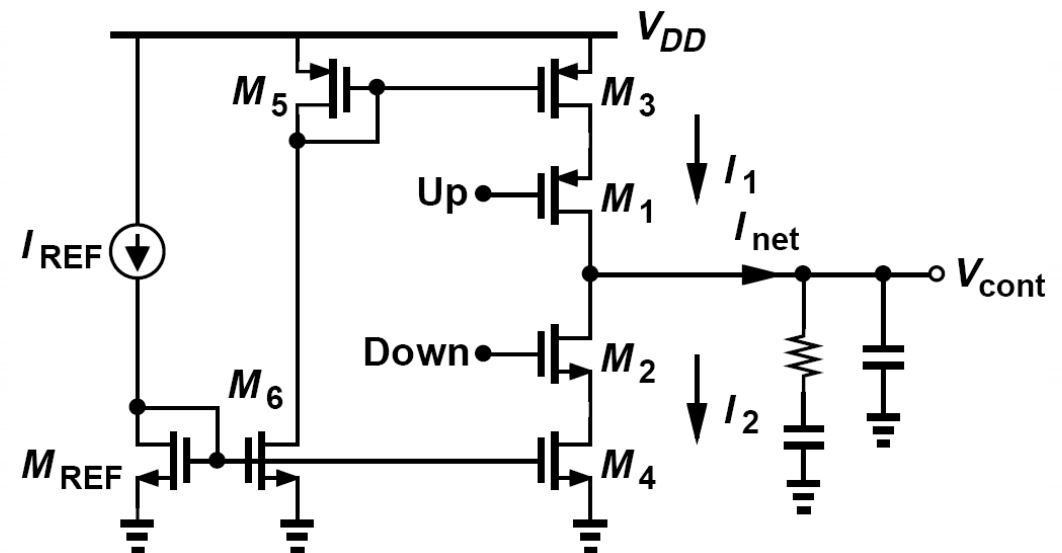 - ❑ The **charge pump** can be realised using MOS transistors as switches and to configure current mirrors.



- The design can be improved by suppressing the channel-length modulation.

From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大学

Frequency Synthesizer

(integer- N)

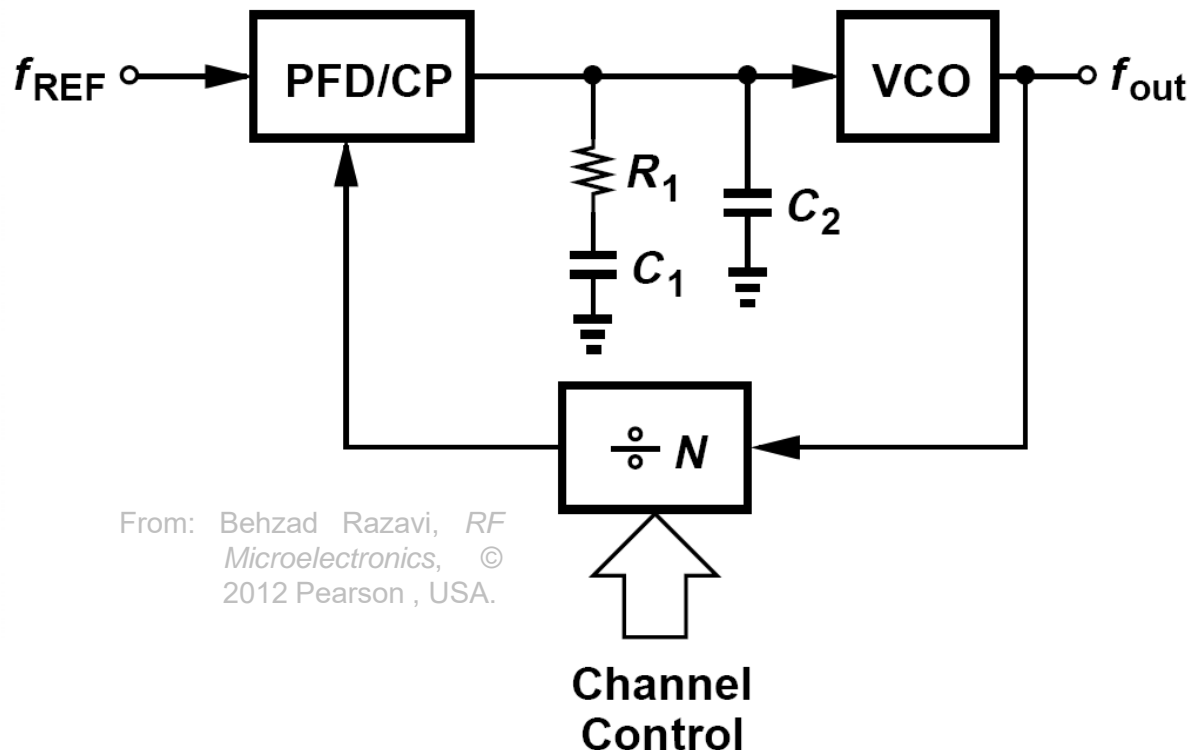- ❑ With the phase/frequency detector and the **charge pump** designs, a **PLL** can be configured to become a frequency synthesizer.




From: Behzad Razavi, *RF Microelectronics*, © 2012 Pearson, USA.

- An integer- N **frequency synthesizer** produces an output frequency that is an **integer multiple** of the reference frequency.
- This is frequency multiplication.

Frequency Synthesizer

(fractional- N)

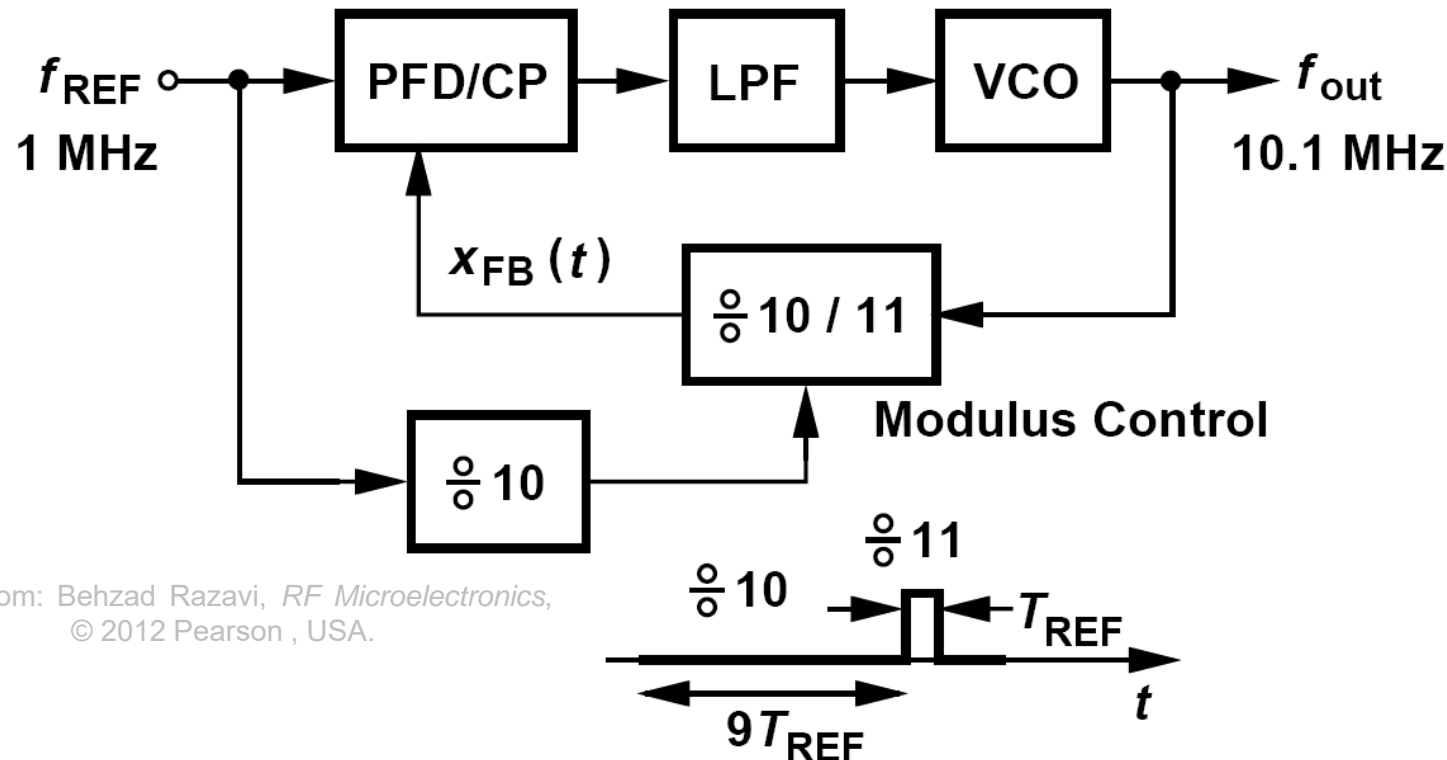- The integer- N frequency synthesizer can be revamped to a fractional- N frequency synthesizer.



From: Behzad Razavi, *RF Microelectronics*,
© 2012 Pearson, USA.