

EEE104 – Digital Electronics (I)

Lecture 15

Dr. Ming Xu
Dept of Electrical & Electronic Engineering
XJTLU


1

In This Session

- Counter Overview
- Asynchronous Counters

2

A Revision: J-K Flip-Flops

 

- When $J = 1$ and $K = 1$, the output will be toggled at the rising edge of the clock.

INPUTS			OUTPUTS		COMMENTS
J	K	CLK	Q	\bar{Q}	
0	0	\uparrow	Q_0	\bar{Q}_0	No change
0	1	\uparrow	0	1	RESET
1	0	\uparrow	1	0	SET
1	1	\uparrow	\bar{Q}_0	Q_0	Toggle

3

Counter Overview


A **counter** is a group of flip-flops connected together to perform counting operation.

Categories:


- **Asynchronous counters:** each flip-flop is clocked by the output of the preceding flip-flop.
- **Synchronous counters:** all the flip-flops are clocked by the same clock input.

4

2-Bit Asynchronous Binary Counters

 


 
- J and K are HIGH for all flip-flops.
- FF1 is clocked by the \bar{Q}_0 output of FF0.



CLOCK PULSE	Q_1	Q_0
Initially	0	0
1	0	1
2	1	0
3	1	1
4 (recycles)	0	0


5

3-Bit Asynchronous Binary Counters

  

6

4-Bit Asynchronous Binary Counters

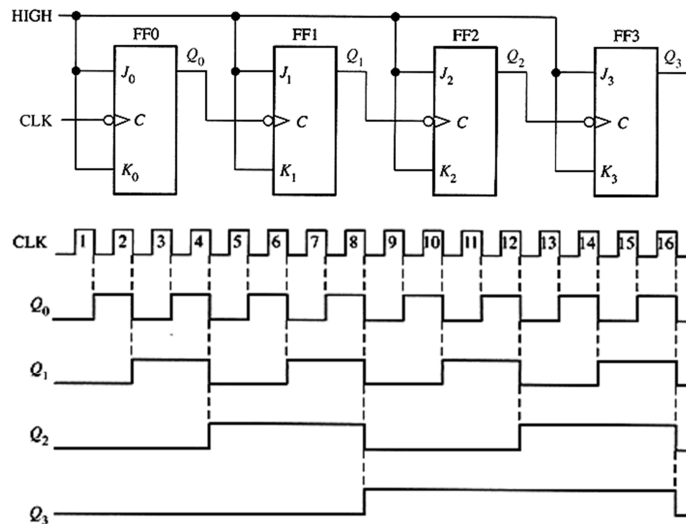


7

Asynchronous Decade Counters


- With n flip-flops, the maximum number of states of a counter is 2^n .
- A counter may be designed to go through less states or a **truncated** sequence, e.g. **decade counter** which counts from 0000 to 1001.
- The number of unique states that a counter will sequence through is called **modulus**.

8

Asynchronous Decade Counters

 

 
0000
0001
0010
0011
0100
0101
0110
0111
1000
1001
1010




- Once state 1010 appears, the decoder will reset the counter.
- Only Q_1 and Q_3 used – Partial Decoding

9

Asynchronous Modulus-12 Counters

 


 
0000
0001
0010
0011
0100
0101
0110
0111
1000
1001
1010
1011
1100



10

Cumulative Delay in Asynchronous Counters

  The **propagation delay time** is the time interval for the output to change after an input has been applied.





t_{PHL} 74HC74A 17 ns
 t_{PLH} 74HC74A 17 ns

t_{PHL} 74LS74A 40 ns
 t_{PLH} 74LS74A 25 ns

11

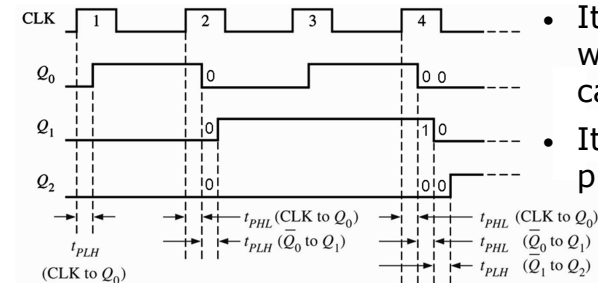 Cumulative Delay in Asynchronous Counters




- It limits the rate at which the counter can be clocked.
- It creates decoding problems.

12



IC Asynchronous Counters

74LS93A


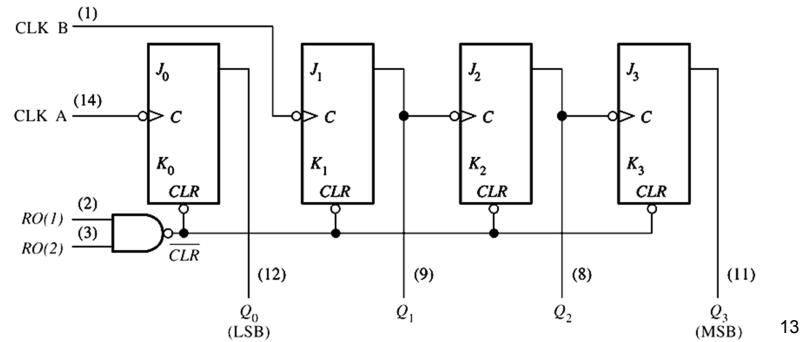
- Q_0 should be connected with CLK B when used as a counter.
- The NAND gate can be used as the decoder.



IC Asynchronous Counters

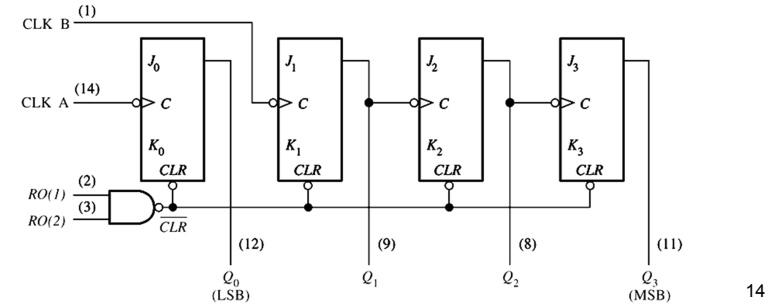 

IC Asynchronous Counters

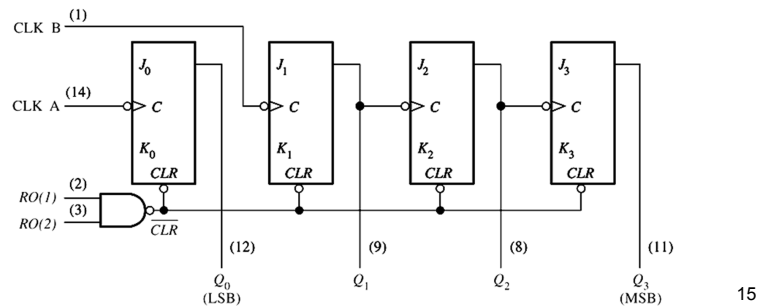 

IC Asynchronous Counters

