

EEE205 – Digital Electronics (II)

Lecture 5

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

1

In This Session

- Representing Data in AHDL
- Operators
- Truth Tables Using AHDL
- Decision Control Structures in AHDL

2

Identifiers

- Composed of legal characters
 - Letters (a–z, A–Z)
 - Digits (0–9)
 - Slash (/)
 - Underscore (_)
- Can begin with a digit
- Must not be a reserved word
- Identifiers and keywords are **case-insensitive**.

3

Representing Data in AHDL

- Binary, hexadecimal, and decimal values are represented in AHDL as shown, with a prefix to indicate the number system.

Number System	AHDL	Decimal Equivalent
Binary	B"101"	5
Hexadecimal	H"101"	257
Decimal	101	101

- Constants: **VCC** and **GND**

4

Representing Data in AHDL

Bit Arrays or **Bit Vectors** are used to describe a port or a node with more than one data bit.

Declaration

- Syntax – a name is followed by the index range.
- Example:

```
p1 [7..0]      :INPUT;  -- DEFINE AN 8-BIT INPUT
PORT
```

- Individual bits can be accessed by specifying the bits, e.g. p1[5].

5

Representing Data in AHDL

Bit Array Assignment

- To assign the 8-bit port p1 to a node named temp:

```
VARIABLE      temp[7..0]:NODE;
BEGIN
    temp[]=p1[];
END
```

- The empty braces mean that all bits in the array are being connected.
- Individual bits could also be connected, e.g. temp[0]=p1[0];

6

Operators

Boolean Operators

Operator	Alternate	Description
!	NOT	Inverter
&	AND	AND
! &	NAND	AND with Inverted Output
#	OR	OR
! #	NOR	OR with Inverted Output
\$	XOR	Exclusive OR
! \$	XNOR	Exclusive OR with Inverted Output

Arithmetic Operators

Operator	Description
- (unary)	Two's Complement Negation
+	Unsigned/Two's Complement Addition
-	Unsigned/Two's Complement Subtraction

Operators

Comparison Operators

Operator	Type	Description
==	Logical	Equal to
!=	Logical	Not equal to
<	Arithmetic	Less than
<=	Arithmetic	Less than or equal to
>	Arithmetic	Greater than
>=	Arithmetic	Greater than or equal to

8

Operators

The Concatenation Operator

- Combine nodes (and other groups) into a group by placing the node/group names in parentheses
`g[3..0] = (a, b, c, d);`
`(a, b, c, d) = g[3..0];`
- Can also be used to assign multiple ports in a single statement
`(a, b) = B"10";`

9

Truth Tables Using AHDL

- Circuits can be designed directly from truth tables in AHDL.
- The key point is to use the **TABLE** keyword.

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

10

Truth Tables Using AHDL

```
SUBDESIGN FIG4-50
(
    a,b,c :INPUT;    --define inputs to block
    y      :OUTPUT;  --define block output
)
BEGIN
    TABLE
        (a,b,c)  => y; --column headings
        (0,0,0)  => 0;
        (0,0,1)  => 0;
        (0,1,0)  => 0;
        (0,1,1)  => 1;
        (1,0,0)  => 0;
        (1,0,1)  => 1;
        (1,1,0)  => 1;
        (1,1,1)  => 1;
    END TABLE;
END;
```

11


Truth Tables Using AHDL

```
SUBDESIGN FIG4-50
(
    a,b,c :INPUT;    --define inputs to block
    y      :OUTPUT;  --define block output
)
VARIABLE in_bits[2..0] :NODE;
BEGIN
    in_bits[] = (a,b,c); --concatenating
    TABLE
        in_bits[] => y; --column headings
        b"000"    => 0;
        b"001"    => 0;
        b"010"    => 0;
        b"011"    => 1;
        b"100"    => 0;
        b"101"    => 1;
        b"110"    => 1;
        b"111"    => 1;
    END TABLE;
END;
```

12

Decision Control Structures in AHDL

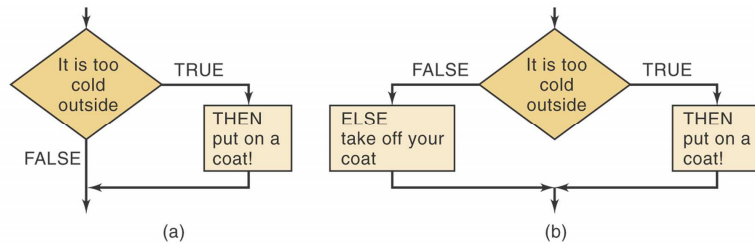- IF/THEN/ELSE statements provide a framework for making logical decisions in a system.
 - **IF/THEN** is used when there is a choice between doing something and doing nothing.
 - **IF/THEN/ELSE** is used when there is a choice between two possible actions.



13

Decision Control Structures in AHDL

- The IF/THEN/ELSE in AHDL:

```
SUBDESIGN FIG4_54
(
    digital_value[3..0] :INPUT;  -- define inputs to block
    z                   :OUTPUT; -- define block output
)
BEGIN
    IF digital_value[] > 6 THEN
        z = VCC;                -- output a 1
    ELSE z = GND;                -- output a 0
    END IF;
END;
```

14

Decision Control Structures in AHDL

- The **CASE** construct determines the value of an expression and then goes through a list of values (cases) to determine what action to take, e.g. to implement truth table:

p	q	r	s
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

15

Decision Control Structures in AHDL

- The CASE construct in AHDL:

```
SUBDESIGN fig4_60
(
    p, q, r      :INPUT;      -- define inputs to block
    s            :OUTPUT;     -- define outputs
)
VARIABLE
    status[2..0] :NODE;
BEGIN
    status[] = (p, q, r); -- link input bits in order
    CASE status[] IS
        WHEN b"100"    => s = GND;
        WHEN b"101"    => s = GND;
        WHEN b"110"    => s = GND;
        WHEN OTHERS    => s = VCC;
    END CASE;
END;
```

16