

EEE104 – Digital Electronics (I)

Lecture 16

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU


1

In This Session



- Synchronous Counters

2

2-Bit Synchronous Binary Counters


 


  - All the flip-flops are clocked by CLK.
- J and K of FF1 are connected to Q_0 output of FF0.




3

2-Bit Synchronous Binary Counters

  


4

3-Bit Synchronous Binary Counters

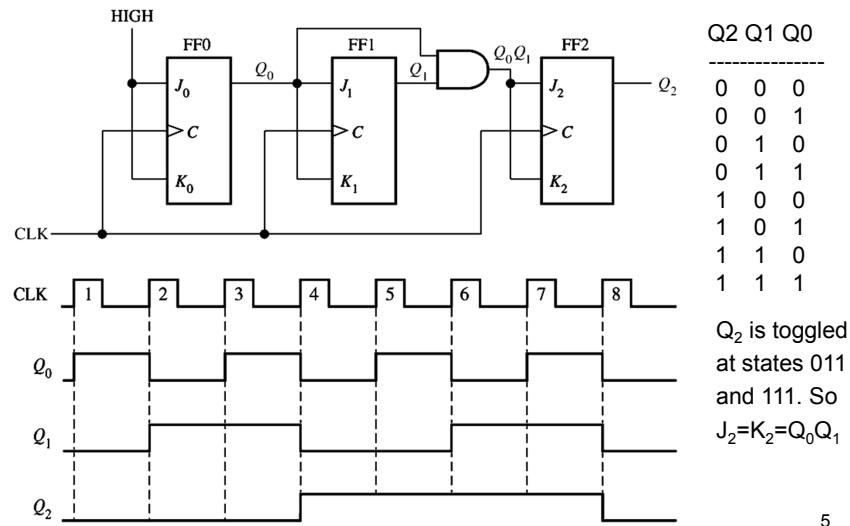

5

4-Bit Synchronous Binary Counters

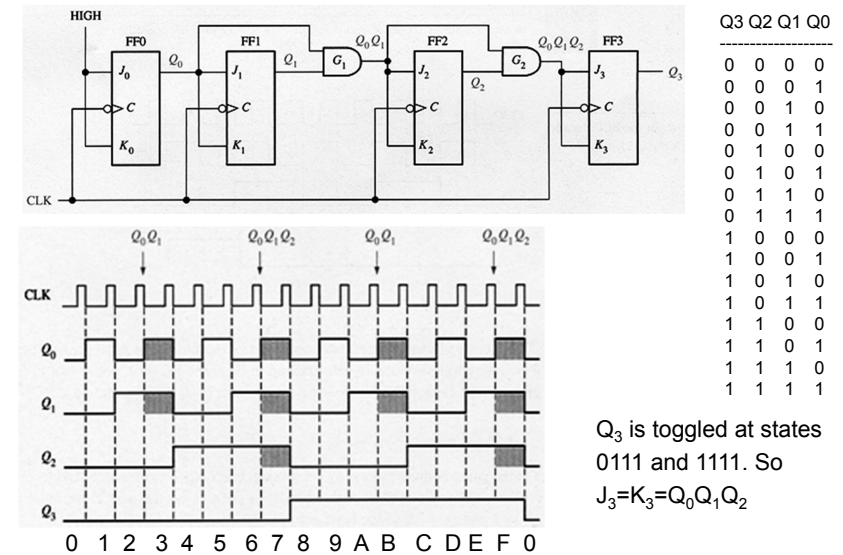

6

4-Bit Synchronous Decade Counters

Q3 Q2 Q1 Q0

0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

- Q₀ is always toggled.
- Q₁ is toggled at states 0001, 0011, 0101, 0111.
- Q₂ is toggled at states 0011, 0111.
- Q₃ is toggled at states 0111, 1001.

$$J_0 = K_0 = 1$$


$$J_1 = K_1 = Q_0 \bar{Q}_3$$

$$J_2 = K_2 = Q_0 Q_1$$

$$J_3 = K_3 = Q_0 Q_1 Q_2 + Q_0 Q_3$$

7


4-Bit Synchronous Decade Counters

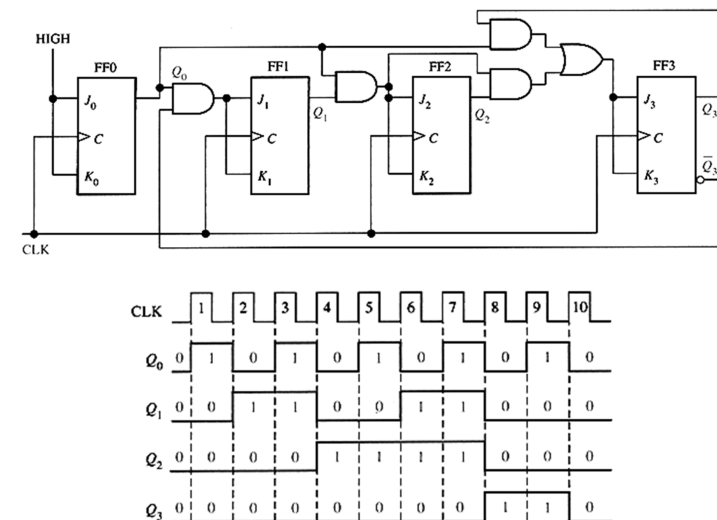

8

IC Synchronous Counters

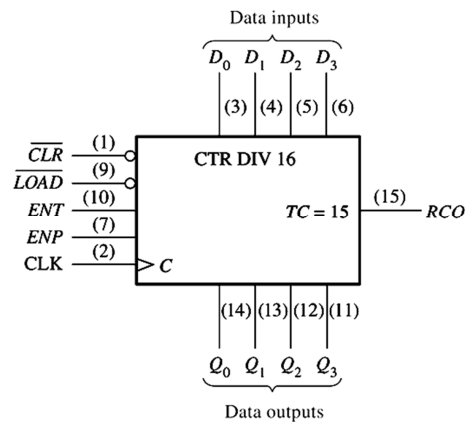
74HC163 — a 4-bit synchronous binary counter



- \overline{CLR} : synchronous clear
- \overline{LOAD} : synchronous preset
- ENT, ENP : enable
- RCO : ripple clock output, which goes to 1 at count 15

9


IC Synchronous Counters

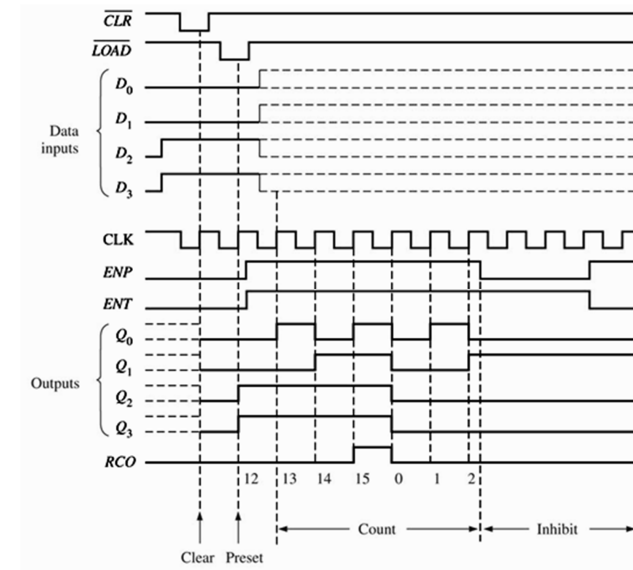

10

IC Synchronous Counters

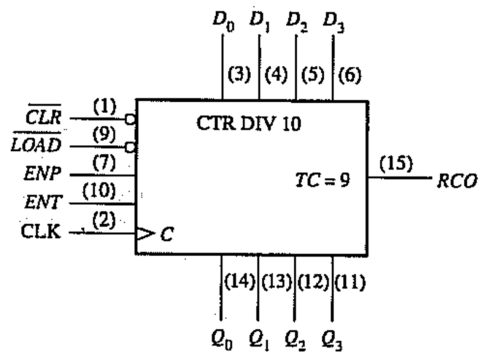
74HC160 — a 4-bit synchronous decade counter



- \overline{CLR} : asynchronous clear
- \overline{LOAD} : synchronous preset
- ENT, ENP : enable
- RCO : ripple clock output, which goes to 1 at count 9

11

IC Synchronous Counters

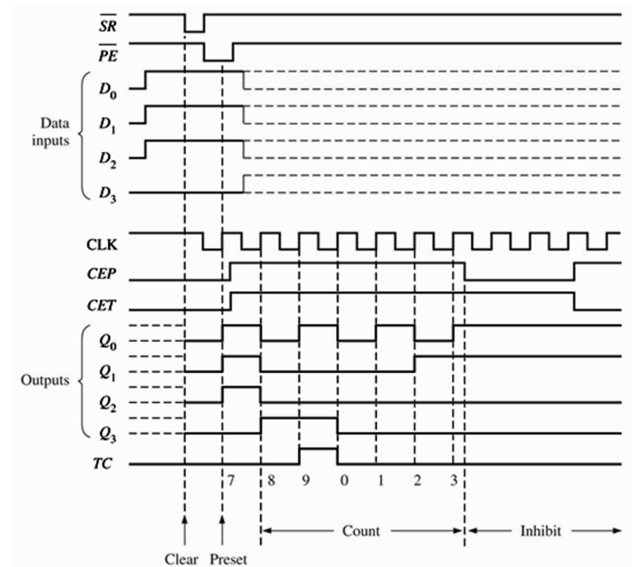

12

Up/Down Synchronous Counters

An **up/down counter** is one that is capable of progressing in either direction through a sequence.


CLOCK PULSE	UP	Q ₂	Q ₁	Q ₀	DOWN
0	↑	0	0	0	↓
1	↑	0	0	1	↓
2	↑	0	1	0	↓
3	↑	0	1	1	↓
4	↑	1	0	0	↓
5	↑	1	0	1	↓
6	↑	1	1	0	↓
7	↑	1	1	1	↓

In count-down mode:

- Q₀ is always toggled.
- Q₁ is toggled at states 110, 100, 010, 000. So $J_1 = K_1 = \neg Q_0$.
- Q₂ is toggled at states 100, 000. So $J_2 = K_2 = \neg Q_0 / Q_1$

13

Up/Down Synchronous Counters

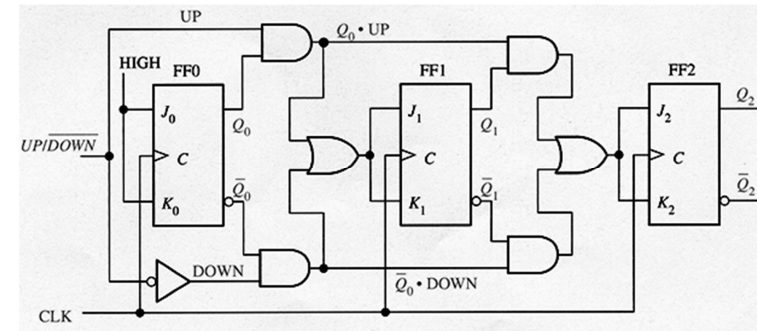


$$J_0 = K_0 = 1$$

$$J_1 = K_1 = (Q_0 \cdot UP) + (\bar{Q}_0 \cdot DOWN)$$

$$J_2 = K_2 = (Q_0 \cdot Q_1 \cdot UP) + (\bar{Q}_0 \cdot \bar{Q}_1 \cdot DOWN)$$


14

Up/Down Synchronous Counters

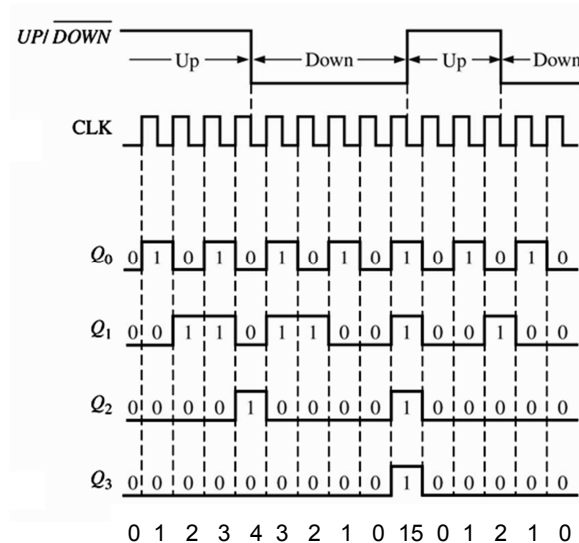

15

An IC Up/Down Decade Counter

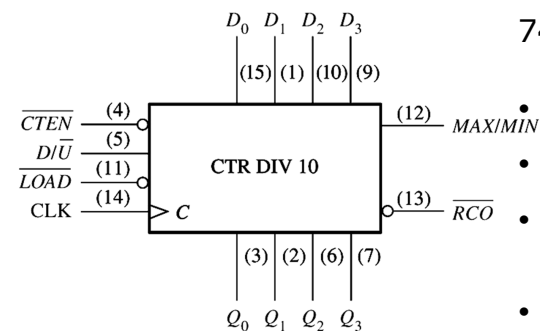

74LS190

- **CTEN**: enable
- **D/U**: down/up
- **LOAD**: synchronous preset
- **MAX/MIN**: HIGH when 1001 or 0000 is reached.
- **RCO**: ripple clock output, which is 0 at count 9

16