

EEE104 – Digital Electronics (I)

Lecture 19

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

1


In This Session

- Shift Registers
 - Bidirectional Shift Registers
 - Shift Register Counters

2


Bidirectional Shift Registers

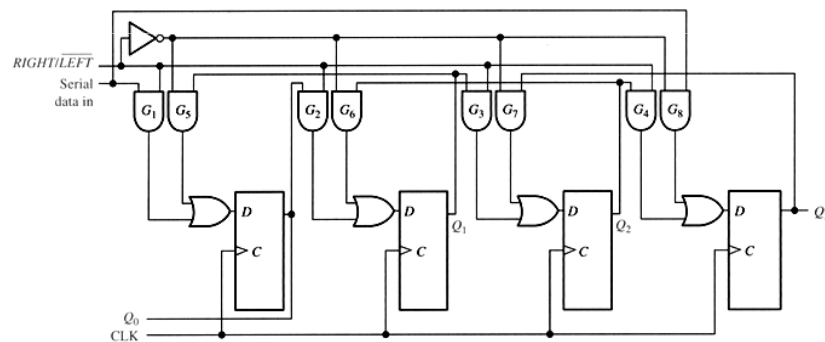- A HIGH on R/L will enable G_1 to G_4 .
- The output of a stage is fed to the D input of the next stage.




Bidirectional Shift Registers

 - A LOW on R/L will enable G_5 to G_8 .
- The output of a stage is fed to the D input of the preceding stage.




7

Bidirectional Shift Registers

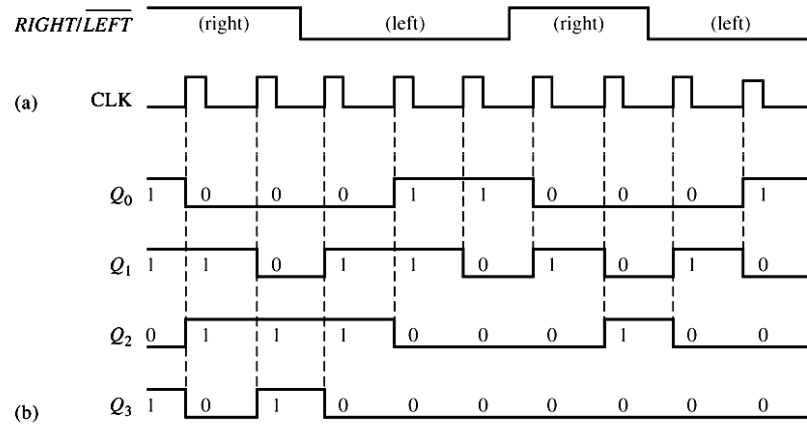

5

Bidirectional Shift Registers

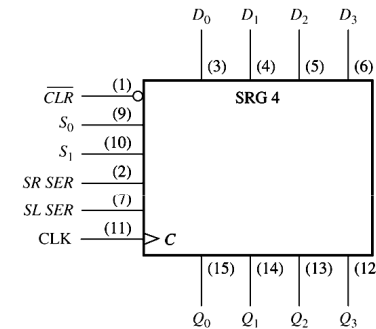

74HC194: A 4-bit universal shift register

Mode selection

S_1	S_0	Mode
0	0	Inhibit
0	1	Shift right
1	0	Shift left
1	1	Load


SR SER: Shift-right serial data in

SL SER: Shift-left serial data in

CLR: asynchronous clear

6

Bidirectional Shift Registers

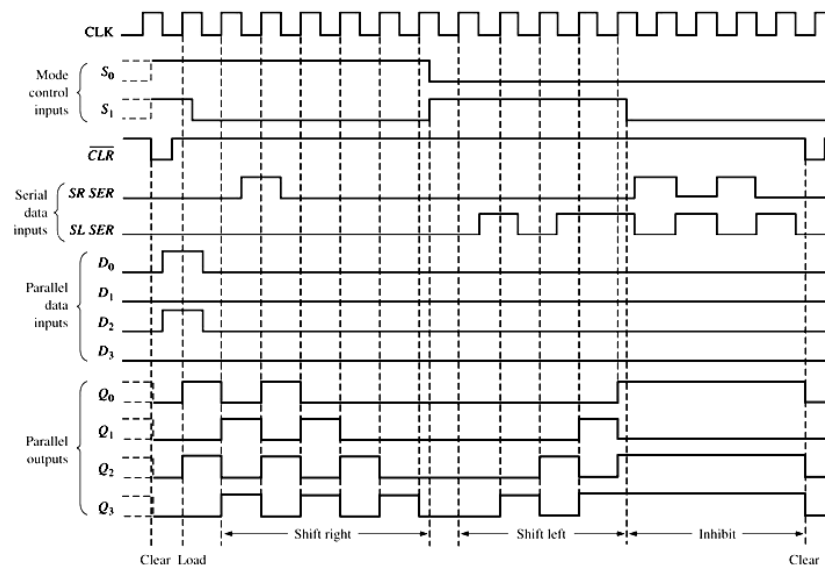

Shift Register Counters


- A **shift register counter** is a shift register with the serial output connected back to the serial input.
- It will produce a specified sequence of state **periodically**. Hence the name "counter".
- Two most common types are the Johnson counter and the ring counter.

8

The Johnson Counter

The **Johnson counter** – The **complemented** output of the last stage is connected back.

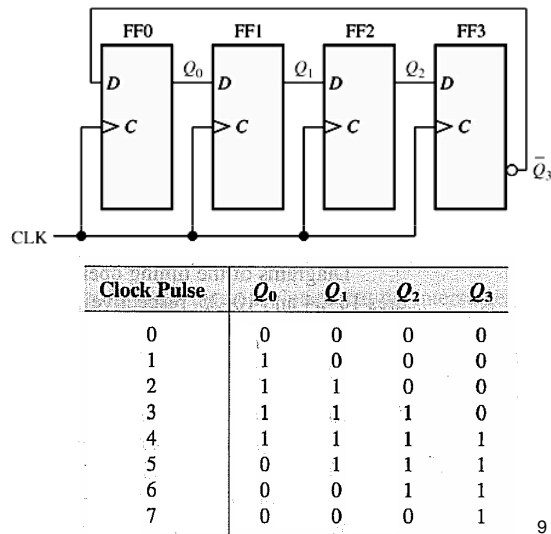The counter will fill up with 1s first and then with 0s.




9

The Johnson Counter


What will happen if the initial state are not one of the 8 states?

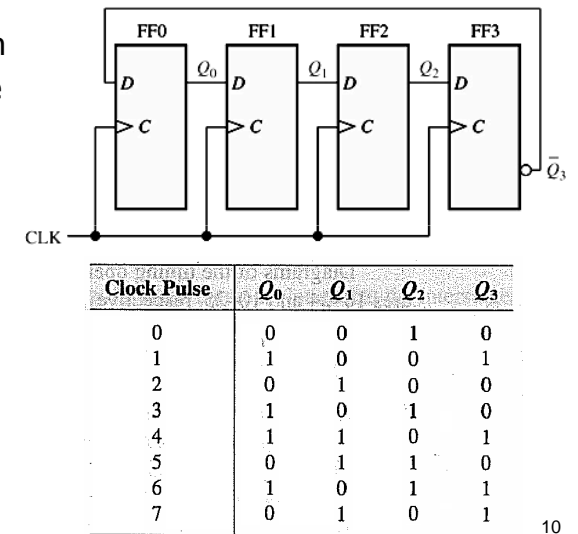The counter will loop through the other 8 states.



10


The Johnson Counter

 

A 4-bit Johnson counter has 8 states.


11

The Johnson Counter

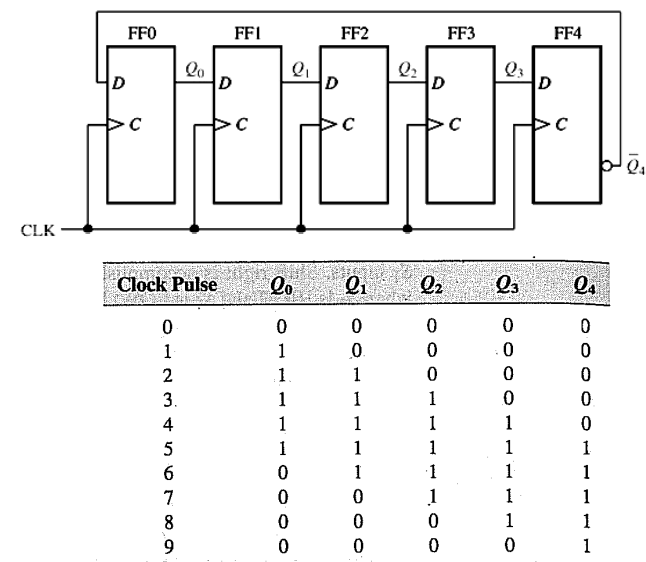

12


The Johnson Counter

 

A 5-bit Johnson counter has 10 states. So an n -stage Johnson counter will have $2n$ states.

13

The Ring Counter

 


Clock Pulse	Q_0	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7	Q_8	Q_9
0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	0	0	0	0
3	0	0	0	1	0	0	0	0	0	0
4	0	0	0	0	1	0	0	0	0	0
5	0	0	0	0	0	1	0	0	0	0
6	0	0	0	0	0	0	1	0	0	0
7	0	0	0	0	0	0	0	1	0	0
8	0	0	0	0	0	0	0	0	1	0
9	0	0	0	0	0	0	0	0	0	1

The output of the last stage is connected back.

14

The Ring Counter

 

15

Shift Register Counters

- The disadvantage is that the maximum available states are not fully utilized.
- Beware that both the Ring and the Johnson counter **must initially be forced into a valid state** in the count sequence, because they operate on a subset of the available number of states. Otherwise, the ideal sequence will not be followed.
- The advantage over a binary counter is that no extra decoding circuit is needed.

16