

EEE109: Electronic Circuits

The Field Effect Transistor

Contents

- Study and understand the operation and characteristics of the various types of MOSFETs.
- Understand and become familiar with the dc analysis and design techniques of MOSFET circuits.
- Examine three applications of MOSFET circuits.
- Investigate current source biasing of MOSFET circuits, such as those used in integrated circuits.
- Analyze the dc biasing of multistage or multitransistor circuits.
- Understand the operation and characteristics of the junction field-effect transistor, and analyze the dc response of JFET circuits.


General Overview


MOSFET

- Metal-Oxide-Semiconductor Field Effect Transistor -MOSFET
- Current is controlled by an electric field applied perpendicular to both semiconductor surface and to the direction of current.
- Field effect Phenomenon to control the current in the semiconductor by applying an electric field perpendicular to the surface.
- The basic transistor principle: The voltage between two terminals controls the current through the third terminal.

Types of Field-Effect Transistors

 - MOSFET (Metal-Oxide Semiconductor Field-Effect Transistor)
- Depletion and enhancement mode (Primary component in high-density VLSI chips such as memory chips and microprocessors)
- JFET (Junction Field-Effect Transistor) finds application especially in analog and RF circuit design
- MESFET (a MOSFET with no oxide)
- All device and circuit analysis are the same!




 

Types of MOSFETs

Туре	Cross Section	Output Characteristics	Transfer Characteristics		
n-Channel Enhancement (Normally Off)	$ \begin{array}{cccccccccccccccccccccccccccccccccccc$	$V_G = 4V$ $V_G = 4V$ V_D	I_D $ 0$ V_{Tn} +		
n-Channel Depletion (Normally On)	$ \begin{array}{cccccccccccccccccccccccccccccccccccc$	$V_G = 1V$ 0 -1 -2 V_D	V_{Tn} V_{G} V_{G}		
p-Channel Enhancement (Normally Off)	$ \begin{array}{cccccccccccccccccccccccccccccccccccc$	$-V_{D} = 0$ $V_{G} = -4V$ I_{D}	$\begin{array}{c c} V_G \\ -V_{Tp} & 0 \\ \hline \\ I_D \end{array}$		
p-Channel Depletion (Normally On)	$ \begin{array}{cccccccccccccccccccccccccccccccccccc$	$-V_{D} = -1 $ $V_{G} = -1 $ I_{D}	$\begin{array}{c c} & V_G \\ \hline - & 0 & + \\ \hline & V_{Tp} \\ \hline & I_D \\ \end{array}$		


Field Effect Transistor Tree

 


Biasing of the Gate for both the junction field effect transistor, (JFET) and the metal oxide semiconductor field effect transistor, (MOSFET) configurations are given as:

Туре	Juncti	on FET	Meta	Metal Oxide Semiconductor FET					
	Depletion	on Mode	Depletion	on Mode	Enhancen	nent Mode			
Bias	ON	OFF	ON	OFF	ON	OFF			
N-channel	0v	-ve	0v	-ve	+ve	0v			
P-channel	0v	+ve	0v	+ve	-ve	0v			

MOSFET Circuit Symbols

 

 




(c) NMOS depletion-mode device

 
 (g) and(i) are the most commonly used symbols in VLSI logic design.








(e) Three-terminal NMOS transistors

 


(f) Three-terminal PMOS transistors

MOS devices are symmetric.

 


 (g) Shorthand notation—NMOS enhancement-mode device




 (h) Shorthand notation—NMOS depletion-mode device

- In NMOS, n⁺ region at higher voltage is the drain.
- In PMOS p⁺ region at lower voltage is the drain




 
(i) Shorthand notation—PMOS enhancement-mode device





(j) Shorthand notation—PMOS depletion-mode device


FETs

 

 

 

 

 


Two-Terminal MOS Structure

Basic Structure of MOS Capacitor

First electrode-Gate: Consists of low-resistivity material such as polycrystalline silicon

Second electrode- Substrate or Body: *n*- or *p*-type semiconductor

 Dielectric-Silicon dioxide: stable high-quality electrical insulator between gate and substrate.




Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

Heart of MOSFET!

MOS Capacitor Under Bias: Electric Field and Charge

Parallel plate capacitor

 

 $C = \varepsilon A/d$

Negative gate bias:


Positive gate bias:

ε – permittivity

A – area of one plate

d – distance between plates

 Substrate Conditions for Different Biases



 Region of minority carrier electron inversion layer attracted to the oxide semiconductor surface!

n-Channel Enhancement-Mode MOSFET


Enhancement mode & n-Channel

 Enhancement-mode -> a voltage must be applied to the gate to create an inversion layer

n-type substrate -> positive gate voltage

p-type substrate -> negative gate voltage

 Schematic of n-Channel Enhancement Mode MOSFET




Copyright © The MoGray L'Companies. Inc.
Permission required for the Modray L'Companies. Inc.
Permission required for the Conder of 400 angstroms.

International System of Units


Standard prefixes for the SI units of measure


Multiples	Name		deca-	hecto-	kilo-	mega-	giga-	tera-	peta-	еха-	zetta-	yotta-
	Prefix		da	h	k	M	G	Т	Р	Е	Z	Y
	Factor	10 ⁰	10 ¹	10 ²	10 ³	10 ⁶	10 ⁹	10 ¹²	10 ¹⁵	10 ¹⁸	10 ²¹	10 ²⁴
Fractions	Name		deci-	centi-	milli-	micro-	nano-	pico-	femto-	atto-	zepto-	yocto-
	Prefix		d	С	m	μ	n	р	f	a	Z	у
	Factor	10 ⁰	10 ⁻¹	10 ⁻²	10 ⁻³	10 ⁻⁶	10 ⁻⁹	10 ⁻¹²	10 ⁻¹⁵	10 ⁻¹⁸	10 ⁻²¹	10 ⁻²⁴

NMOS Transistor: Structure

 

 
- 4 device terminals: Gate(G), Drain(D), Source(S) and Body(B).
- Source and drain regions form pn junctions with substrate.
- v_{SB} , v_{DS} and v_{GS} always positive during normal operation.
- v_{SB} always < v_{DS} and v_{GS} to reverse bias pn junctions



 

(c)

Basic Transistor Operation

 


Before electron inversion layer is formed

After electron inversion layer is formed

The current in MOSFET is the result of the flow of charge in the inversion layer!

For NMOS, the carrier in the inversion layer is the electron!


Basic Transistor Operation

 


Electrons flow from the source of the drain with an applied drain-to-source voltage!

The magnitude of current is a function of amount of charge in the inversion layer + a function of applied gate voltage.

 NMOS Transistor: Triode Region Characteristics




 Current Versus Voltage Characteristics: Enhancement-Mode nMOSFET



Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

 
NMOS Transistor: Triode Region Characteristics (contd.)



- Output characteristics appear to be linear.
- FET behaves like a gate-source voltage-controlled resistor between source and drain with


$$R_{on} = \frac{1}{K_n' \frac{W}{L} \left(V_{GS} - V_{TN} \right)}$$

 NMOS Transistor: Saturation Region (contd.)




$$v_{DSAT} = v_{GS} - V_{TN}$$
 is also called saturation or pinch-off voltage

 NMOS Transistor: Qualitative I-V Behavior



- $V_{GS} << V_{TN}$: Only small leakage current flows.
- V_{GS}<V_{TN}: Depletion region formed under gate merges with source and drain depletion regions. No current flows between source and drain.
- $V_{GS} > V_{TN}$: Channel formed between source and drain. If $v_{DS} > 0$,, finite i_D flows from drain to source.
- $i_B=0$ and $i_G=0$.

 
Family of i_D Versus v_{DS} Curves: Enhancement-Mode nMOSFET



Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display


p-Channel Enhancement-Mode MOSFET


p-Channel Enhancement-Mode MOSFET

 

Copyright @ The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

 
Enhancement-Mode PMOS Transistors: Structure



 


- *P*-type source and drain regions in *n*-type substrate.
- v_{GS} <0 required to create p-type inversion layer in channel region
- For current flow, $v_{GS} < v_{TP}$
- To maintain reverse bias on sourcesubstrate and drain-substrate junctions, v_{SB} <0 and v_{DB} <0
- Positive bulk-source potential causes V_{TP} to become more negative

 Enhancement-Mode PMOS Transistors: Output Characteristics





- For $V_{GS} \ge V_{TP}$, transistor is off.
- For more negative v_{GS}, drain current increases in magnitude
- PMOS is in triode region for small values of V_{DS} and in saturation for larger values.

 Symbols for n-Channel Enhancement-Mode MOSFET



 Symbols for p-Channel Enhancement-Mode MOSFET




 

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


n-Channel Depletion-Mode MOSFET

Depletion-Mode MOSFETS

 


- NMOS transistors with $V_{TN} \le 0$
- Ion implantation process used to form a built-in n-type channel in device to connect source and drain by a resistive channel
- Non-zero drain current for v_{GS} =0, negative v_{GS} required to turn device off.

n-Channel Depletion-Mode MOSFET

 

 
Family of i_D Versus v_{DS} Curves: Depletion-Mode nMOSFET




Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

p-Channel Depletion-Mode MOSFET


p-Channel Depletion-Mode MOSFET

 

 

Complementary MOSFETs (CMOS)

Cross-Section of nMOSFET and pMOSFET

 

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Both transistors are used in the fabrication of CMOS circuitry.

Summary of I-V Relationships

Region	NMOS	PMOS
Nonsaturation	v _{DS} <v<sub>DS(sat)</v<sub>	$v_{SD} < v_{SD}(sat)$
	$i_D = K_n [2(v_{GS} - V_{TN})v_{DS} - v_{DS}^2]$	$i_D = K_p [2(v_{SG} + V_{TP})v_{SD} - v_{SD}^2]$
Saturation	v _{DS} >v _{DS} (sat)	$v_{SD}>v_{SD}(sat)$
	$i_D = K_n [v_{GS} - V_{TN}]^2$	$i_D = K_p [v_{SG} + V_{TP}]^2$
Transition Pt.	$v_{DS}(sat) = v_{GS} - V_{TN}$	$v_{SD}(sat) = v_{SG} + V_{TN}$
Enhancement Mode	$V_{TN} > 0V$	$V_{TP} < 0V$
Depletion Mode	$V_{TN} < 0V$	$V_{TP} > 0V$

Conduction Parameters

NMOSFET

$$K_{n} = \frac{W\mu_{n}C_{ox}}{L} = k_{n} \frac{W}{L}$$

PMOSFET


$$K_{p} = \frac{W\mu_{p}C_{ox}}{L} = k_{p} \frac{W}{L}$$

where:


$$C_{ox} = \varepsilon_o / t_{ox}$$


Nonideal I-V Characteristics

Channel Length Modulation: Early Voltage

 

Channel-Length Modulation

 


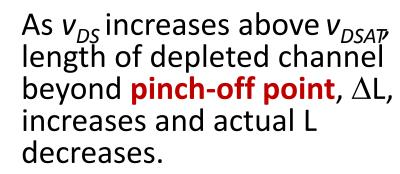

 i_D increases slightly with v_{DS} instead of being constant.

$$i_{D} = \frac{K_{n}}{2} \frac{W}{L} \left(v_{GS} - V_{TN} \right)^{2} \left(1 + \lambda v_{DS} \right)$$

 λ = channel length modulation parameter

 

 


Figure 3.20 Family of i_D versus v_{DS} curves showing the effect of channel length modulation producing a finite output resistance

The parameters λ and V_A are related. From Equation (3.7), we have $(1 + \lambda v_{DS}) = 0$ at the extrapolated point where $i_D = 0$. At this point, $v_{DS} = -V_A$, which means that $V_A = 1/\lambda$.

The output resistance due to the channel length modulation is defined as

$$r_o = \left(\frac{\partial i_D}{\partial v_{DS}}\right)^{-1} \bigg|_{v_{GS} = \text{const.}} \tag{3.8}$$

From Equation (3.7), the output resistance, evaluated at the Q-point, is


$$r_o = [\lambda K_n (V_{GSQ} - V_{TN})^2]^{-1}$$
(3.9(a))

 \mathbf{or}

$$r_o \cong [\lambda I_{DQ}]^{-1} = \frac{1}{\lambda I_{DQ}} = \frac{V_A}{I_{DQ}}$$
 (3.9(b))

The output resistance r_o is also a factor in the small-signal equivalent circuit of the MOSFET, which is discussed in the next chapter.

Body Effect

 


A zero or reverse-bias voltage exists across the source-substrate pn junction.

A change in the source-substrate junction voltage changes the threshold voltage.

Body Effect or Substrate Sensitivity

 The assumption that the body lead is connected to the source lead. In integrated circuit design. In this case, any signal voltage on the source lead causes an a signal voltage between the body and source. The effect of this voltage is called the body effect.



This non-zero V_{SB} changes threshold voltage, causing substrate sensitivity to be modeled by:

$$V_{TN} = V_{TO} + \gamma \left(\sqrt{V_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right)$$


Where

 V_{TO} = zero substrate bias for $\sqrt{V_{TN}}$ (V)

 γ = body-effect parameter ()

 $2F_F$ = surface potential parameter (V)

Subthreshold Condition

 


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


The drain current is non-zero; vgs is slightly less than VTN.

MOSFET DC Circuit Analysis


NMOS Common-Source Circuit

 V_{DD}

 


 



 V_{GS}

 


PMOS Common-Source Circuit

 

 

 

 Load Line and Modes of Operation: NMOS Common-Source Circuit





Problem-Solving Technique: NMOSFET DC Analysis

- 1. Assume the transistor is in saturation.
 - a. $V_{GS} > V_{TN}$, $I_{D} > 0$, & $V_{DS} \ge V_{DS}$ (sat)
- 2. Analyze circuit using saturation I-V relations.
- 3. Evaluate resulting bias condition of transistor.
 - a. If $V_{GS} < V_{TN}$, transistor is likely in cutoff
 - b. If $V_{DS} < V_{DS}(sat)$, transistor is likely in nonsaturation region
- 4. If initial assumption is proven incorrect, make new assumption and repeat Steps 2 and 3.

n-Channel Enhancement-Load Device

Enhancement Load Device

 


 

Copyright @ The McGraw-Hill Companies, Inc.

$$i_D = K_n (v_{GS} - V_{TN})^2 = K_n (v_{DS} - V_{TN})^2$$

 Circuit with Enhancement Load Device and NMOS Driver




 M_1 is always in **saturation**.

M_D can be biased either in saturation or nonsaturation region.

Voltage Transfer Characteristics:

 
NMOS Inverter with Enhancement Load Device




Permission required for reproduction or display.

n-Channel Depletion-Load Device

NMOS Inverter with Depletion Load Device

 


 


Permission required for reproduction or display.

p-Channel Enhancement-Load Device

CMOS Inverter

 


 

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


Basic MOSFET Applications

2-Input NMOS NOR Logic Gate

 


V ₁ (V)	V ₂ (V)	$V_O(V)$
0	0	High
5	0	Low
0	5	Low
5	5	Low

2-Stage Cascade Amplifier

 

Junction Field-Effect Transistor

 Cross Section of n-Channel Junction Field Effect Transistor (JFET)




JUNCTION FET: depletion layers of pn-junctions close the channel

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

Most important parameter: pinch-off voltage


The JFET

 
The width of the closed PN junction controls the conductivity of the channel




PN junction \Rightarrow junction FET

JFET with Gate-Source Bias

 


 


 


- v_{GS} =0, gate isolated from channel.
 - $V_P < v_{GS} < 0$, W'<W, channel resistance increases, gate-source junction reverse-biased, i_G almost 0.
- $v_{GS} = V_P < 0$, channel region pinchedoff, channel resistance infinite.

JFET Channel with Drain-Source Bias

 


 

 

- With constant v_{GS} , depletion region near drain increases with v_{DS} .
- At $v_{DSP} = v_{GS} V_P$, channel is totally pinched-off, i_D is saturated.
 - JFET also suffers from channel length modulation like MOSFET at larger values of v_{DS} .

N-Channel JFET: i-v Characteristics

 

Triode $-V_{GS} = 0 \text{ V}$ region 2 200 I_{DSS} 180 Pinch-off locus 160 → Pinch-off region Drain-source current (µA) 140 $V_{GS} = -1 \text{ V}$ 120 100 60 $V_{GS} = -2 \text{ V}$ $V_{GS} \leq V_P$ 20 10 Drain-source voltage (V)

Transfer Characteristics

Output Characteristics

Chapter 3

- •Study and understand the structure, operation and characteristics of MOSFETs.
- •Understand and become familiar with the dc analysis and design techniques of MOSFET circuits.
- Examine three applications of MOSFET circuits.
- •Investigate current source biasing of MOSFET circuits, such as those used in integrated circuits.
- Analyze the dc biasing of multistage or multi-transistor circuits.
- •Understand the operation and characteristics of the junction field-effect transistor, and analyze the dc response of JFET circuits.