

EEE213 Power Electronics and Electromechanism

Lab arrangement (Room EE411)

11th April Thursday (9:00-12:00 & 2:00 -5:00) ✓

Deadline: May 5th, 23:55pm

TA (PhD students) :

1. Chu Guanying: Guanying.chu@xjtlu.edu.cn

1. Wang Yuanchen: Yuanchen.wang@xjtlu.edu.cn



EEE213 Power Electronics and Electromechanism

Assignment 1

Deadline: **12th May 2019**. Time: 23.55.

Assignment 2

Deadline: **19th May 2019**. Time: 23.55.

ALL Tutorial questions (week11 &12) and all inquiries for Assignments

TA (PhD student) : room EE511

1. Yujie Liu: Yujie.liu@xjtlu.edu.cn



EEE213 Power Electronics and Electromechanism


Tutorial 2

Outline

- Full-wave converter (Lecture 6)
 - Problem 4.1
 - Problem 4.2
- Three-phase full bridge SCR rectifier (Lecture 5)
 - Problem 5.1
 - Problem 5.2





- A full-wave converter is connected to a 100V-50Hz supply v_s . The load is purely resistive with $R=10$ ohm.
 - (1) Draw the waveforms for the output voltage, the current, and the line current for a firing angle; (Refer to Lecture 6, page 8)
 - (2) Express the line current i_s in a Fourier series;
 - (3) Determine the THD of the line current; (Refer to Lecture 2, page 22)
 - (4) Determine the displacement power factor $\cos\phi$ and the line power factor f_p ; (Refer to Lecture 2, page 23)
 - (5) If the firing angle is $\alpha = \pi/3$, calculate V_o , THD, $\cos\phi$, f_p and the power dissipated by the load.

Full-wave controller

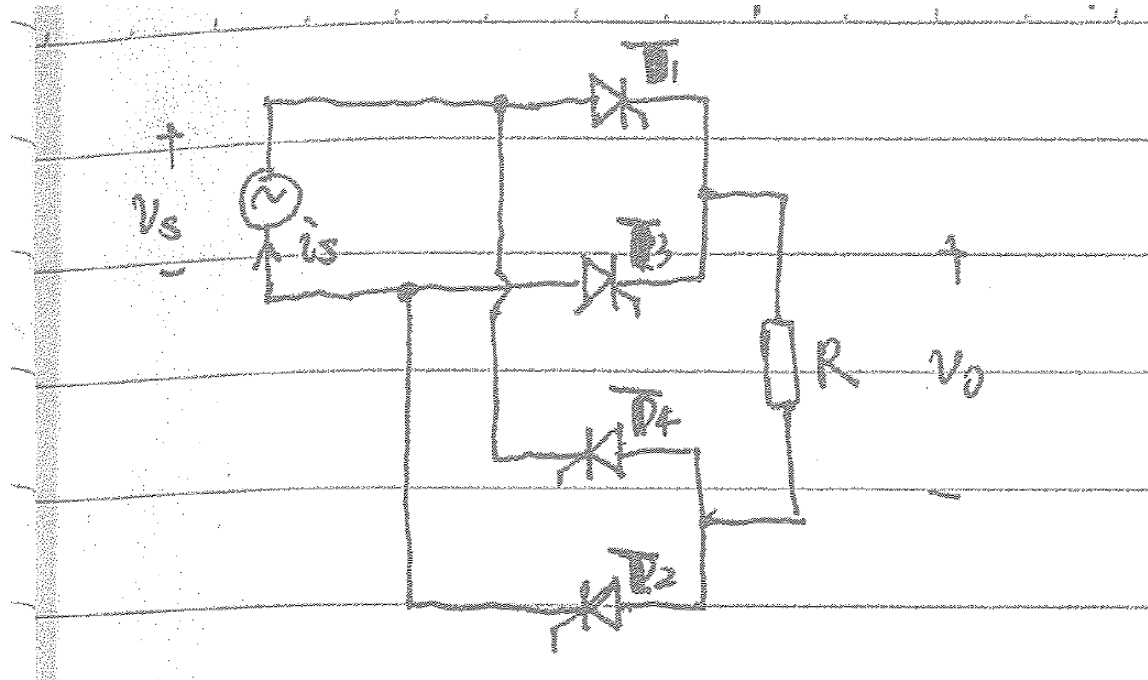





- The positive half-cycle goes through T_1 , R and T_2 , while the negative half-cycle goes through T_3 , R and T_4 .

Waveforms

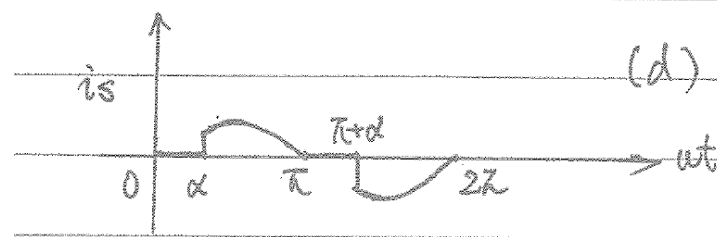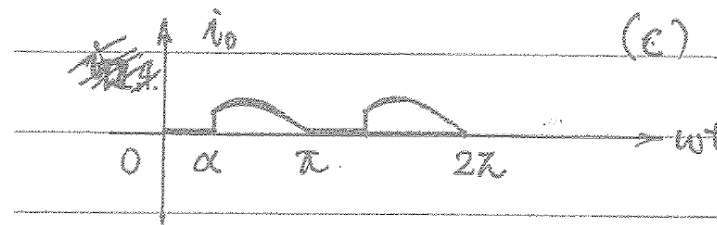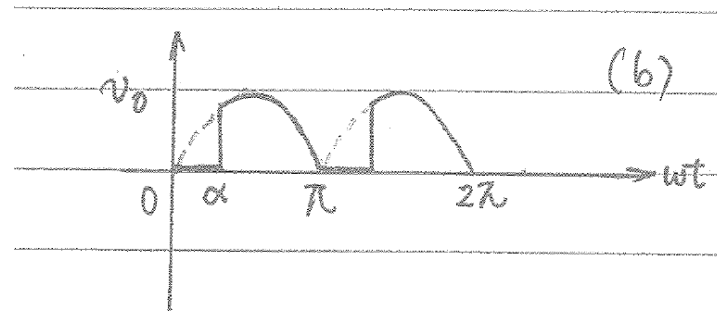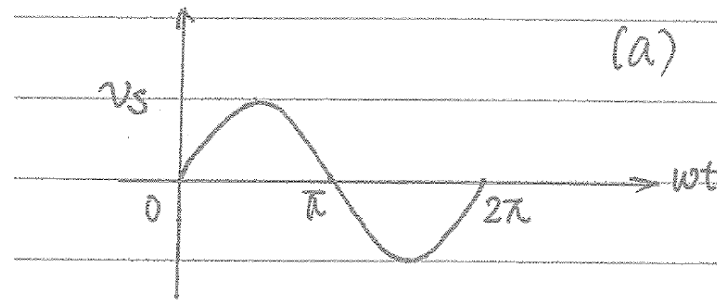

- Repeat the previous question when a very large inductor is put into series with the resistor.

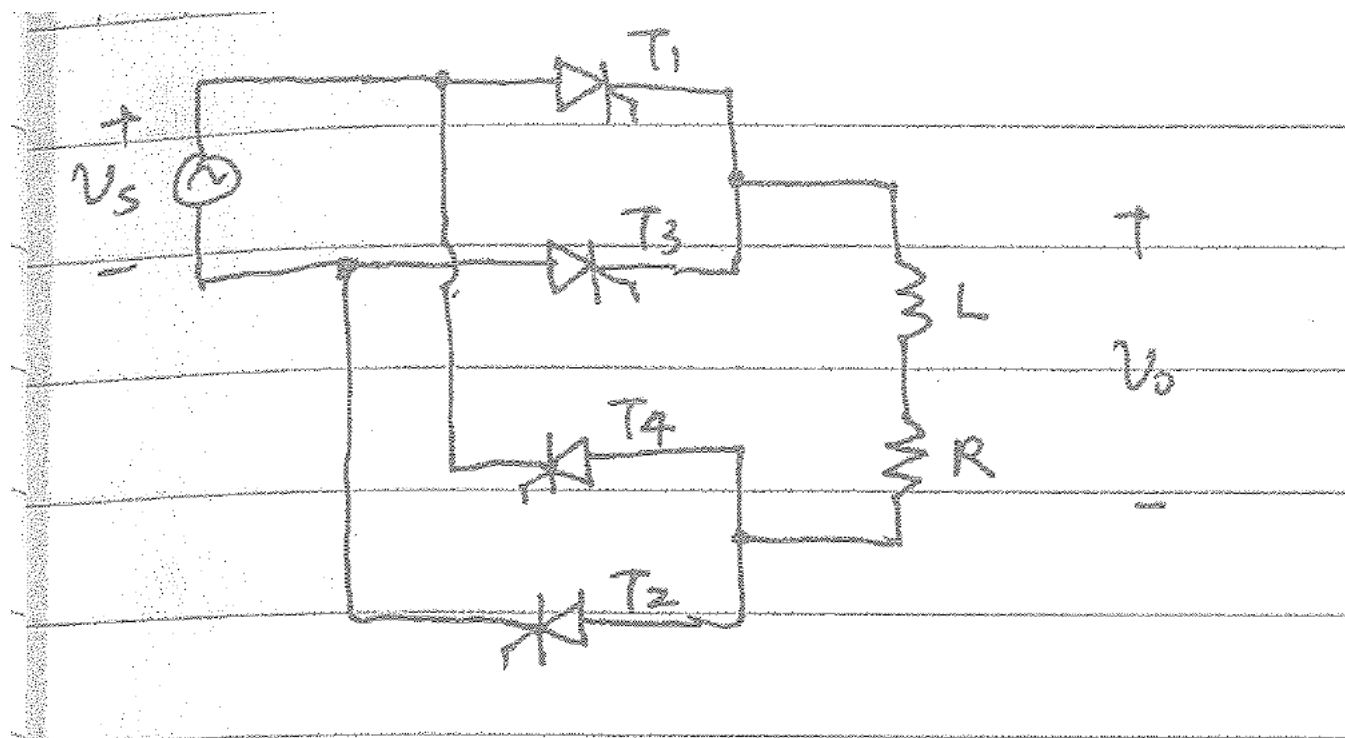


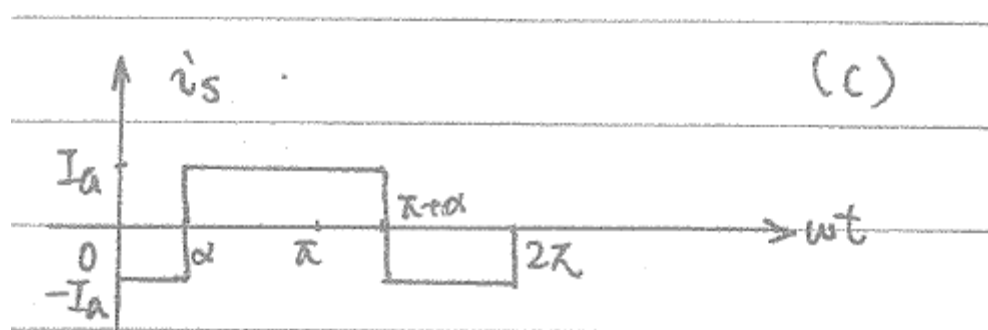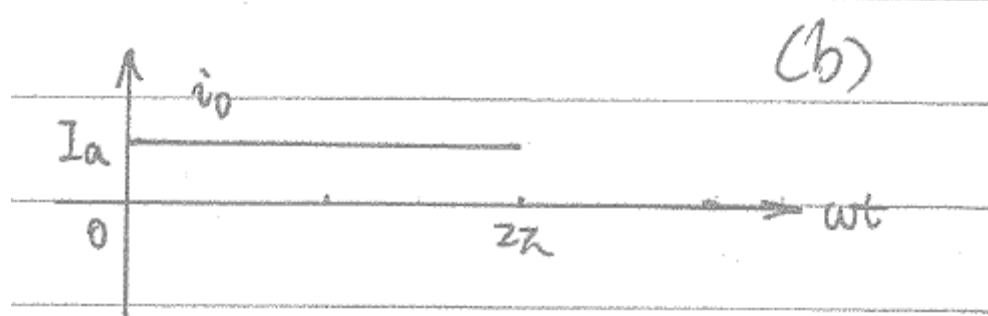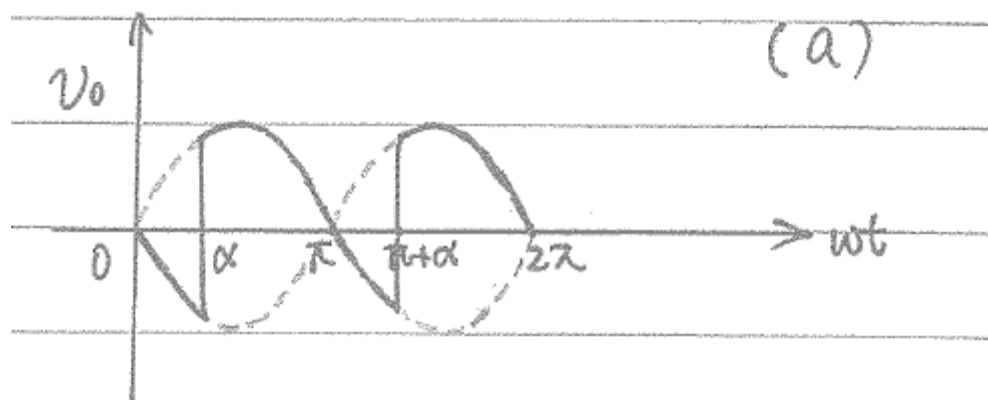




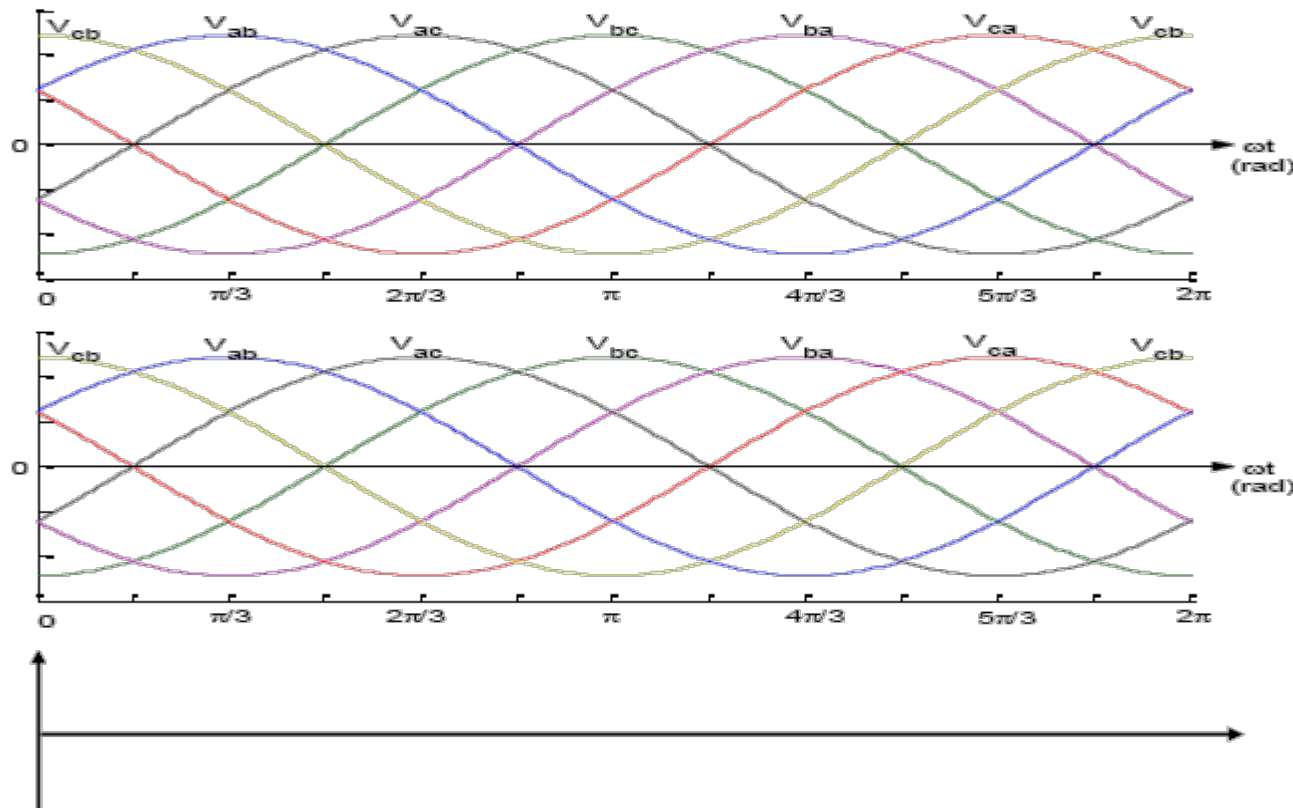
Problem 5.1

Lecture 5

- A three-phase full bridge SCR rectifier supplies a DC power to an RL load. The output current ripple is negligible. The firing angle is 45° .
 - Draw the waveforms for the output voltage, the voltage across SCR1, and the line current of phase A.



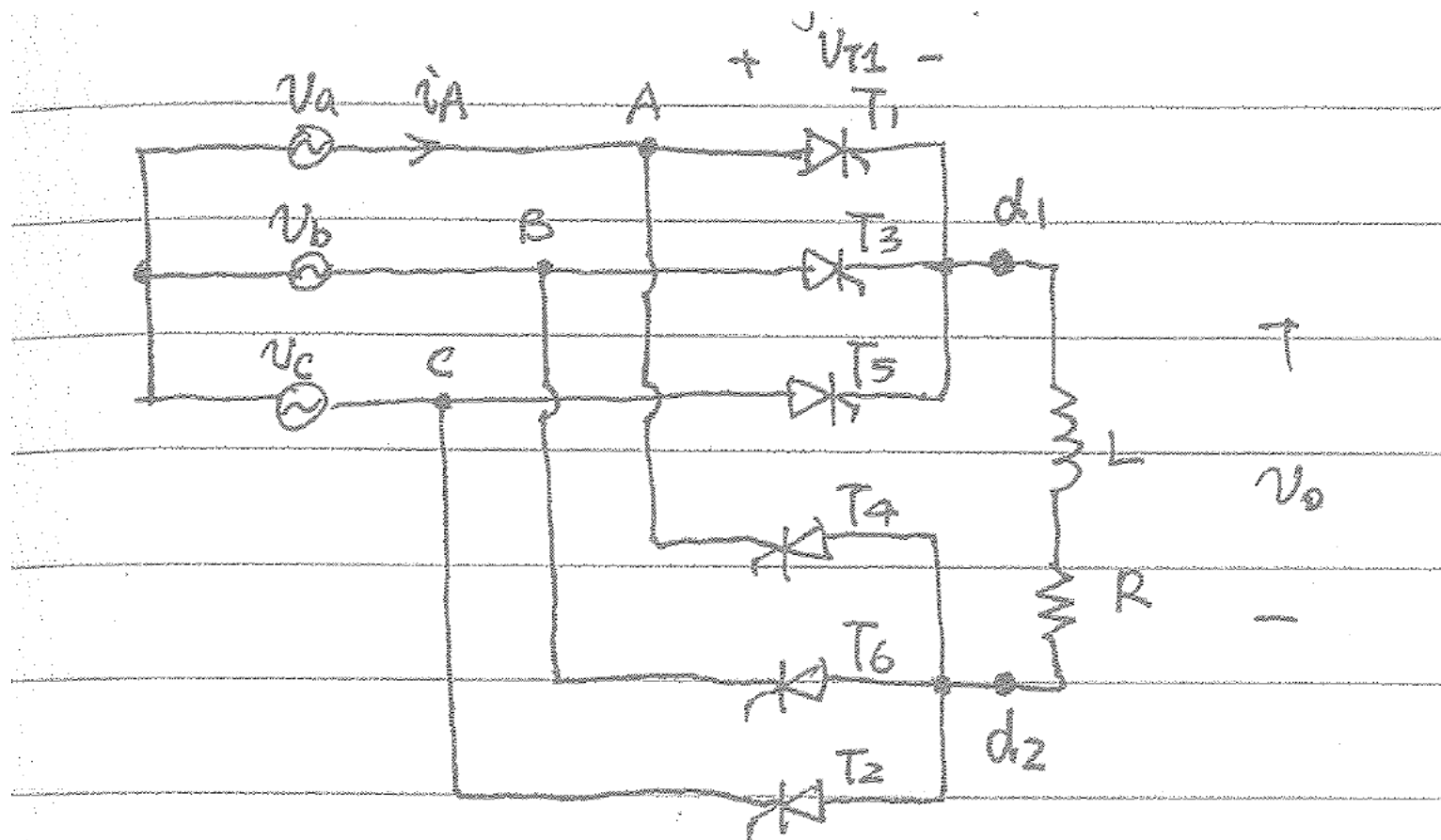

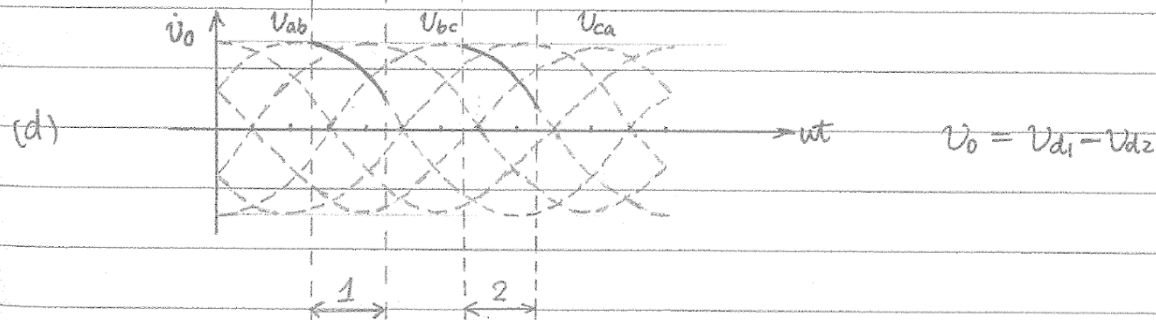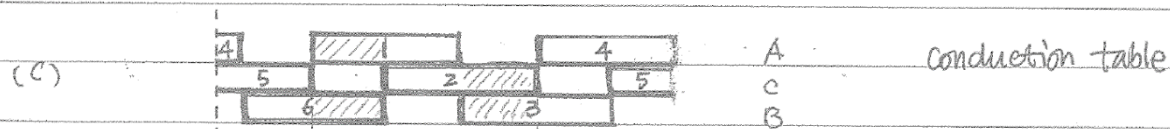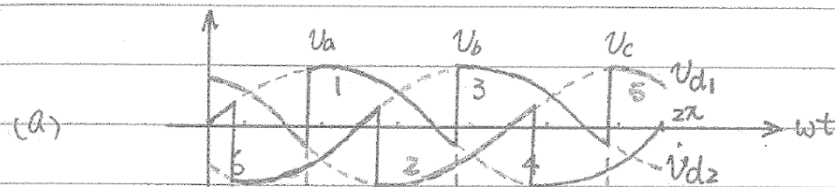

In this region 1 (75° ≤ wt ≤ 135°)

(c) → Thyristor 1 & 6 are conducting,
$$\left. \begin{array}{l} V_{d1} = V_a \\ V_{d2} = V_b \end{array} \right\} V_o = V_{ab}$$

In region 2 (195° ≤ wt ≤ 255°)

Thyristor 2 & 3 are conducting,
$$\left. \begin{array}{l} V_{d1} = V_b \\ V_{d2} = V_c \end{array} \right\} V_o = V_{bc}$$

The output voltage can be drawn according to this analysis.

(e) The voltage across ~~T~~T1. $\star U_T = V_{anode} - V_{cathode}$

There are situations:

<1> ~~T~~T1 is conducting $\Rightarrow U_{T1} = 0$.
range: $75^\circ \sim 195^\circ$.

<2> T1 closed, T3 is conducting.

$$-U_{T1} = V_{d1} - V_a = V_b - V_a$$

$$\Rightarrow U_{T1} = V_a - V_b = V_{ab}$$


range: $195^\circ \sim 315^\circ$.

<3> T1, T3 closed, T5 is conducting.


$$U_{T1} = V_a - V_{d1} = V_a - V_c = V_{ac}$$

range: $315^\circ \sim 435^\circ$

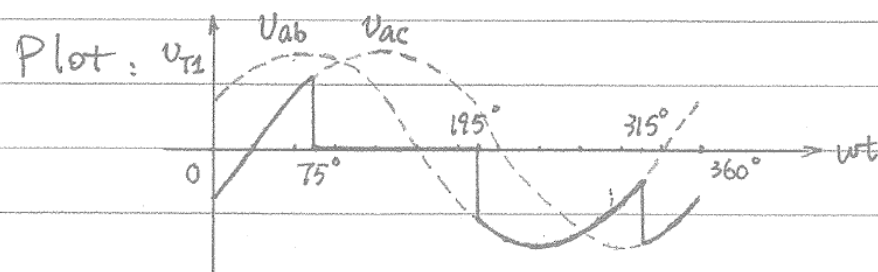$\Leftrightarrow 315^\circ \sim 360^\circ + 0^\circ \sim 75^\circ$.



(f) Line current for phase A.

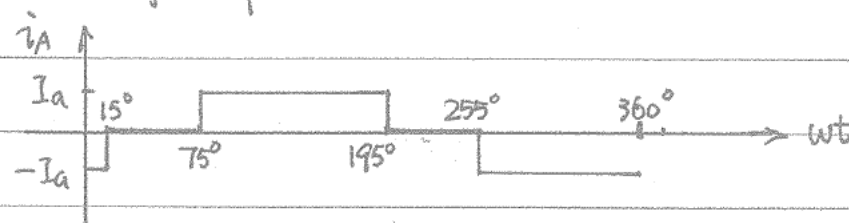

- A resistive load $R=10$ in series with a very large inductor is supplied by a bridge rectifier connected to a three-phase power supply with a phase voltage of 100V. It is required to obtain an average voltage of 150V. Calculate
 - 1)The firing angle needed; (Lecture 5, page 24)
 - 2)The average current;
 - 3)The rms output voltage and current; (Lecture 5, page 24)
 - 4)The power consumed by R;
 - 5)The average and rms values of a thyristor current; (Lecture 5, page 11)
 - 6)The rms line current;
 - 7)The input power factor.
 - Draw the waveforms for the output voltage, a thyristor voltage and a line current.



