

# EEE104 – Digital Electronics (I)

## Lecture 10

Dr. Ming Xu  
Dept of Electrical & Electronic Engineering  
XJTLU

1

## In This Session

- Combinational Logic
  - Basic Combinational Logic Circuits
  - Implementation
  - Universal NAND and NOR Gates
  - Using NAND and NOR Gates

2

## Basic Combinational Logic Circuits

- A **combinational logic** circuit is one in which
  - Logic gates are connected together to implement a certain function (in contrast to *basic logic gates*).
  - There is no storage involved (in contrast to *sequential circuits*).
- Examples of combinational logic
  - Exclusive-OR gates
  - The AND-OR logic in an SOP implementation.

3

## Basic Combinational Logic Circuits

### Exclusive-OR Logic

- The output X is HIGH only when the two inputs are at **opposite** levels.

$$X = \bar{A}B + A\bar{B} \\ = A \oplus B$$

### Exclusive-NOR Logic

- The output of an Exclusive-OR circuit is inverted.
- The output X is HIGH only when the two inputs are at the **same** levels.


$$X = \overline{\bar{A}B + A\bar{B}} = \overline{(\bar{A}B)(A\bar{B})} = (\bar{A} + B)(A + \bar{B}) = \bar{A}\bar{B} + AB$$

4

## Basic Combinational Logic Circuits
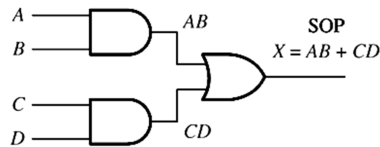
### AND-OR Logic

- The outputs of a number of AND gates connect to the inputs of an OR gate.
- It implements an SOP expression.



- An AND-OR-Invert logic implements a POS expression.  



$$\overline{AB + CD} = \overline{AB} \overline{CD} = (\overline{A} + \overline{B})(\overline{C} + \overline{D})$$

5

## Implementation

### From a Boolean Expression to a Logic Circuit

$$X = AB(C\overline{D} + EF)$$

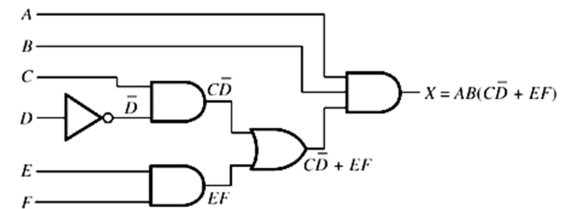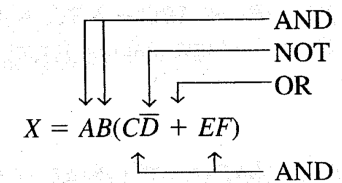

6

## Universal NAND and NOR Gates

- The NAND and NOR gates are **universal** because they can be used to produce any of other logic functions

### NAND gate

- NOT
- AND
- OR
- NOR


### NOR gate

- NOT
- AND
- OR
- NAND


7

## Universal NAND and NOR Gates

- NAND Gate as an Inverter

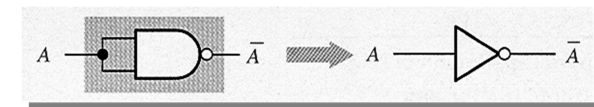


- Two NAND Gates as an AND Gate

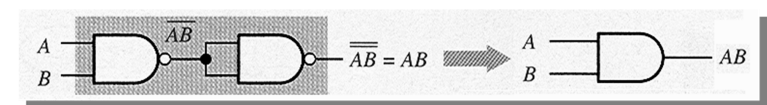


8

## Universal NAND and NOR Gates

- Three NAND Gates as an OR Gate

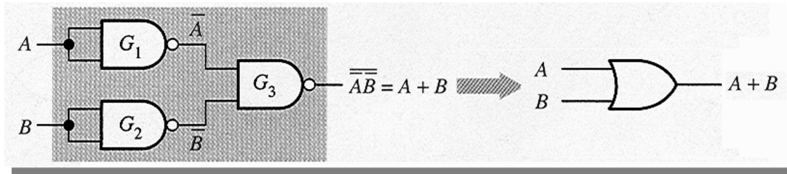

- Four NAND Gates as a NOR Gate

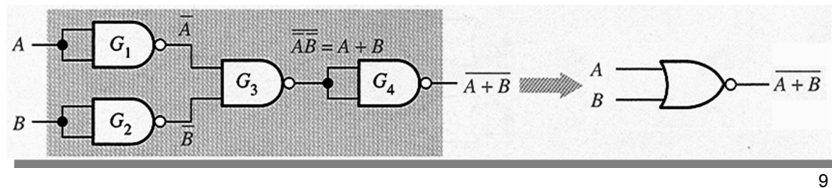


9

## Universal NAND and NOR Gates

- NOR Gate as an Inverter




- Two NOR Gates as an OR Gate

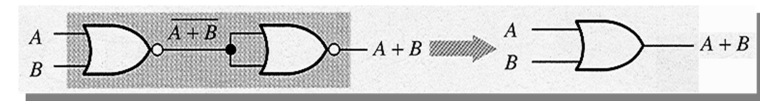


10

## Universal NAND and NOR Gates

- Three NOR Gates as an AND Gate

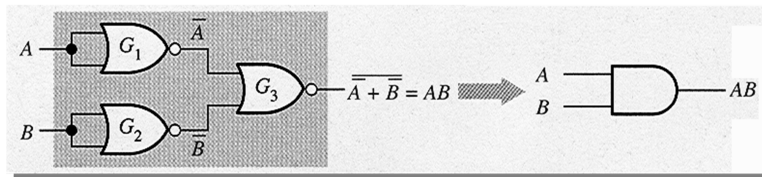


- Four NOR Gates as a NAND Gate

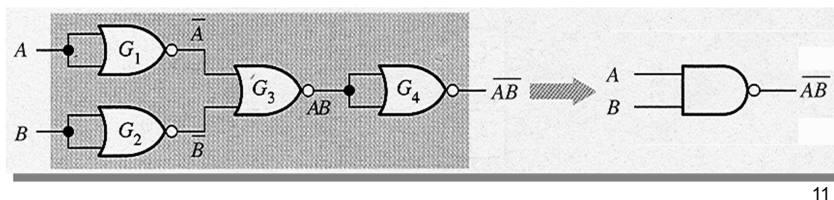


11
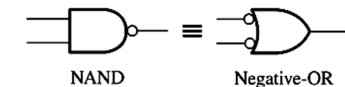
## Using NAND and NOR Gates

- The **NAND** gate is equivalent to the **negative-OR** gate. (dual symbols)



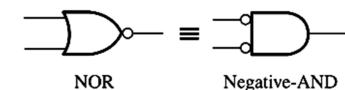- The **NOR** gate is equivalent to the **negative-AND** gate. (dual symbols)




- To use the appropriate symbols will make "reading" a logic diagram easier.


12

## Using NAND and NOR Gates

- To read this logic diagram.

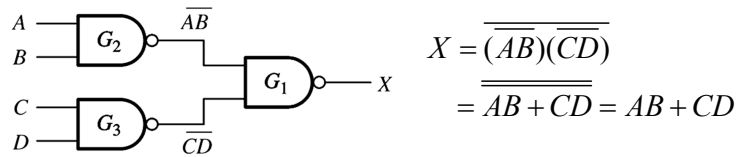


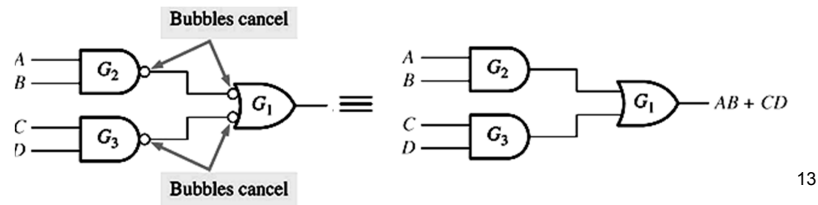- If a negative-AND symbol is used for  $G_1$ , the two bubbles (inversion) will cancel each other.



## Using NAND and NOR Gates

- To read this logic diagram.

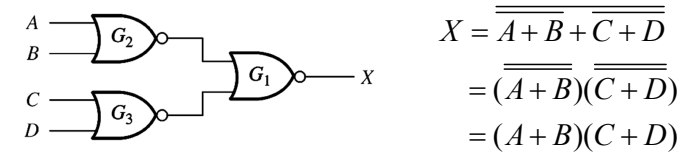

- If a negative-AND symbol is used for  $G_1$ , the two bubbles (inversion) will cancel each other.

