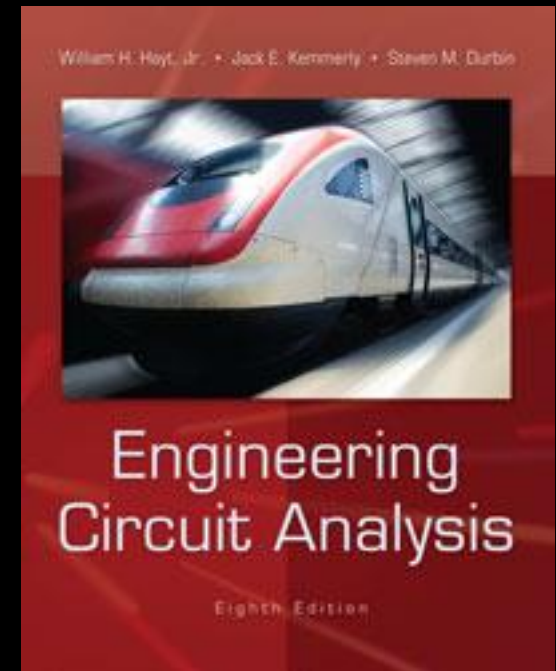


# Chapter 2

## Basic Components and Electric Circuits



# The SI System

## Base units:

- meter (m), kilogram (kg), second (s), ampere (A)
- also: kelvin, mole, and candela

## Derived units:

- work or energy: joule (J)
- power (rate of doing work): watt (W)
- $1 \text{ W} = 1 \text{ J/s}$

# SI: Units and Prefixes

Any measurement can be expressed in terms of a unit, or a unit with a “prefix” modifier.

FACTOR	NAME	SYMBOL
$10^{-9}$	nano	n
$10^{-6}$	micro	$\mu$
$10^{-3}$	milli	m
$10^3$	kilo	k
$10^6$	mega	M

Example:  $12.3 \text{ mW} = 0.0123 \text{ W} = 1.23 \times 10^{-2} \text{ W}$


# Charge

- charge is *conserved*: it is neither created nor destroyed
- symbol:  $Q$  or  $q$ ; units are coulomb (C)
- the smallest charge, the *electronic charge*, is carried by an electron ( $-1.602 \times 10^{-19}$  C) or a proton ( $+1.602 \times 10^{-19}$  C)
- in most circuits, the charges in motion are electrons
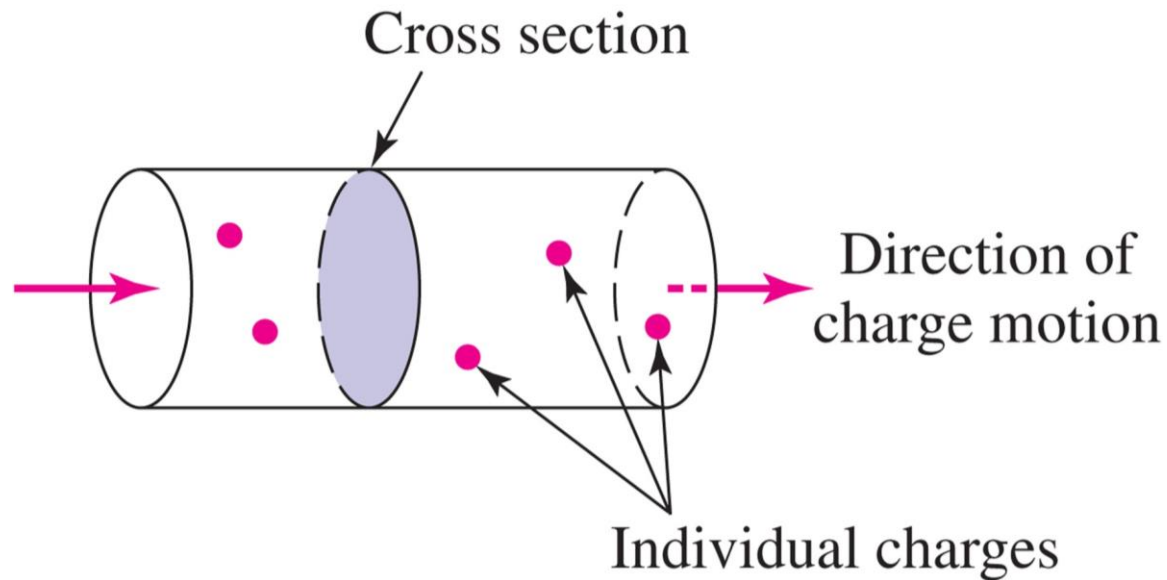
# Current and Charge


Current is the rate of charge flow:

1 ampere = 1 coulomb/second (or  $1 \text{ A} = 1 \text{ C/s}$ )



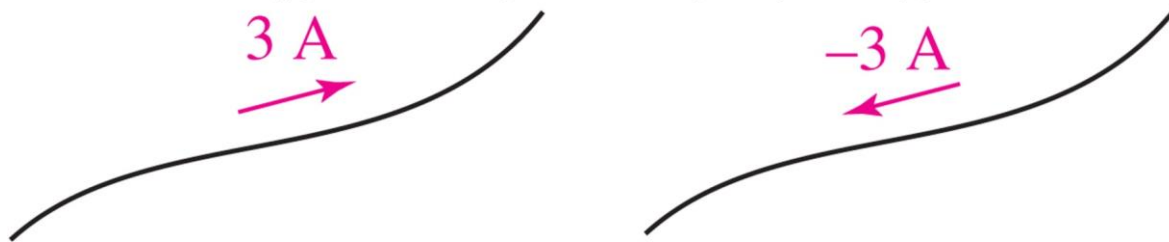
# Current and Charge

- Current (designated by  $I$  or  $i$ ) is the rate of flow of charge
- Current must be designated with both a direction and a magnitude
- These two currents are the same:




# Current and Charge: $i = dq/dt$

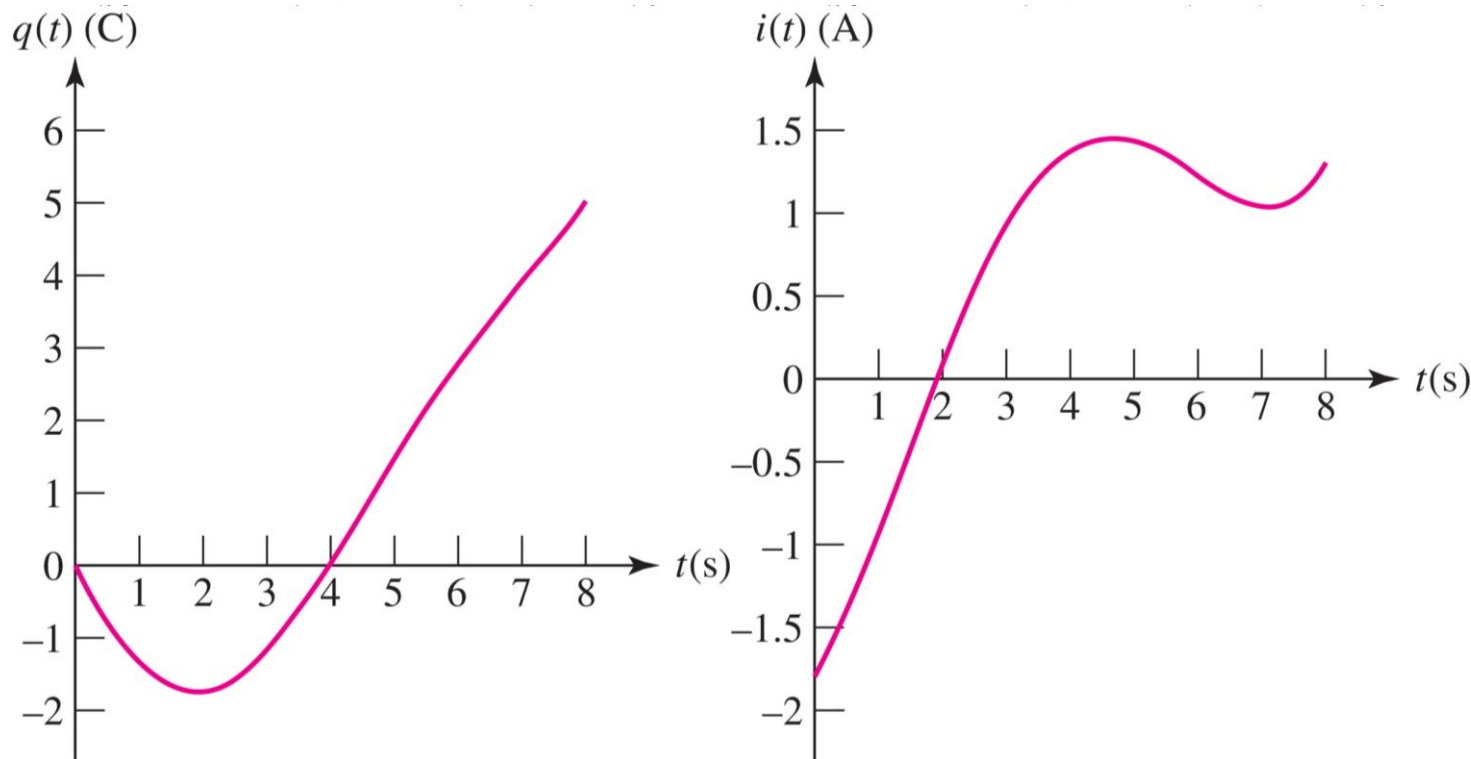

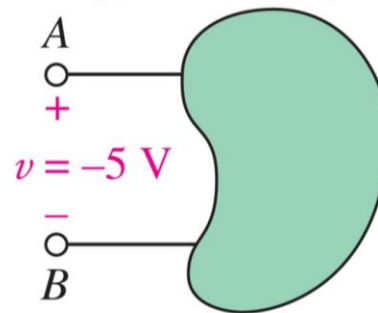
# Voltage


- When 1 J of work is required to move 1 C of charge from A to B, there is a voltage of 1 volt between A and B.
- Voltage ( $V$  or  $v$ ) across an element requires both a magnitude and a polarity.
- Example: (a)=(b), (c)=(d)




(a)

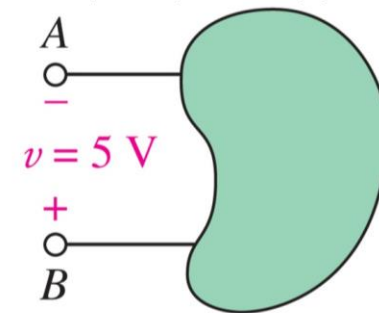

(b)

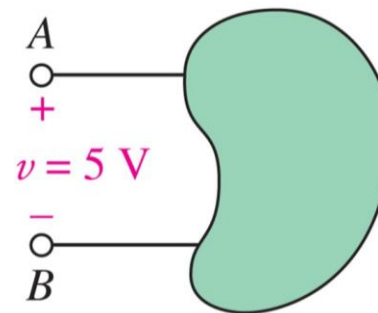

(c)

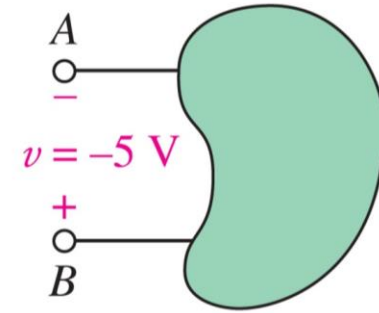

(d)




# Power: $p = v i$


The power required to push a current  $i$  (C/s) into a voltage  $v$  (J/C) is  $p = vi$  (J/s = W).

When power is positive, the element is *absorbing* energy.

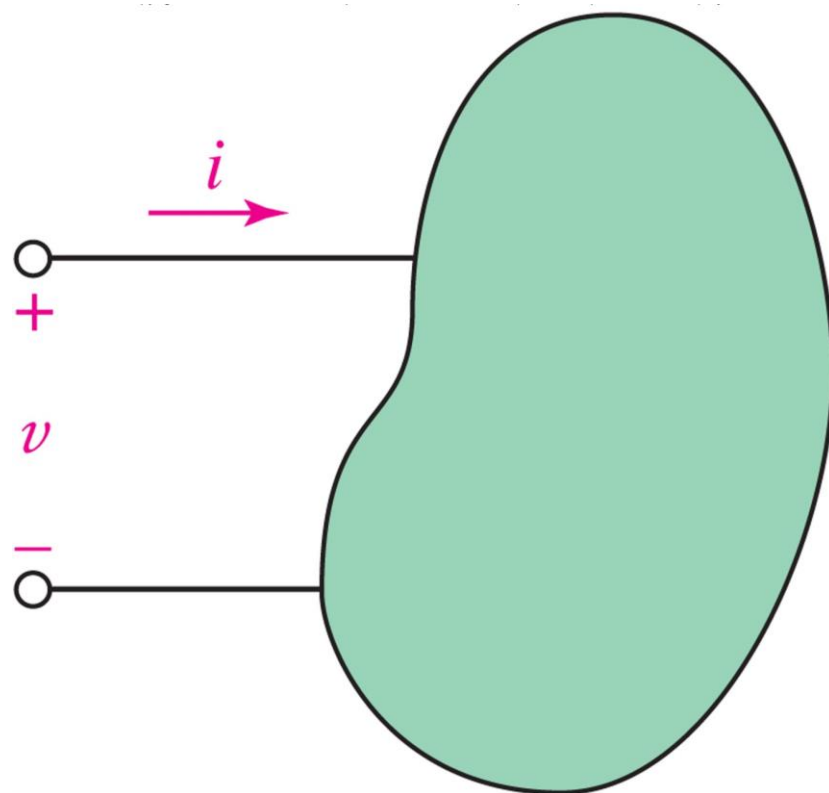
When power is negative, the element is *supplying* energy.




# Example: Power

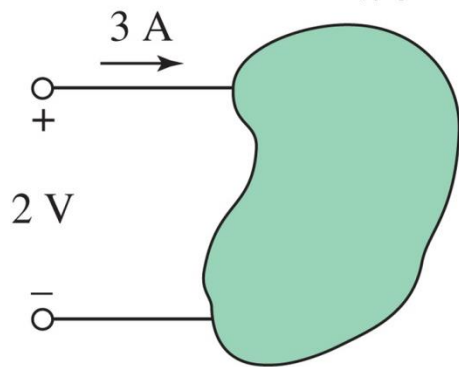

(a)

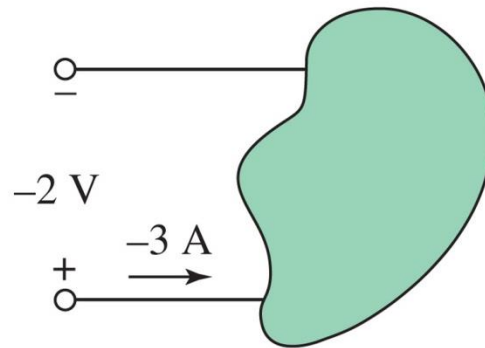

(b)

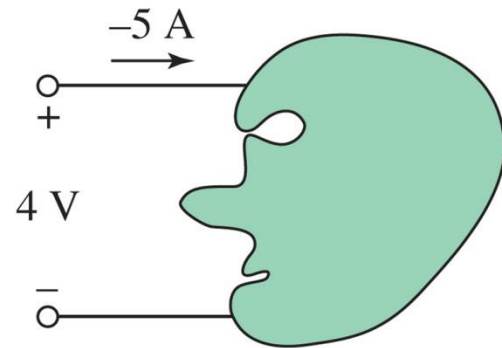

(c)


How much power is absorbed by the three elements above?

$$P_a = +6 \text{ W}, P_b = +6 \text{ W}, P_c = -20 \text{ W}.$$

(Note: (c) is actually supplying power)

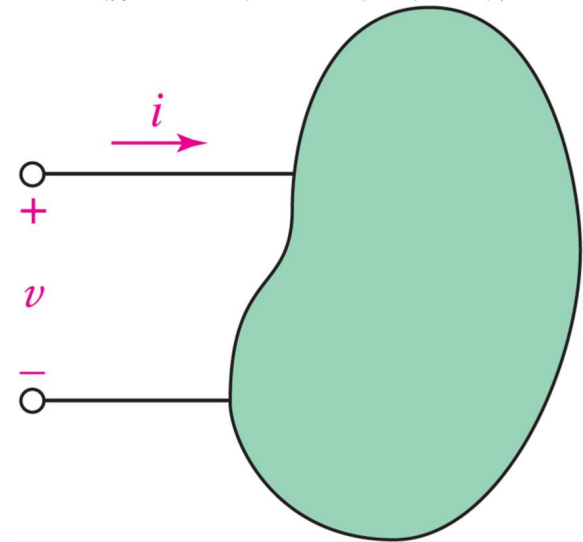
# Circuit Elements

- A circuit element usually has two terminals (sometimes three or more).
- The relationship between the voltage  $v$  across the terminals and the current  $i$  through the device defines the circuit element model.



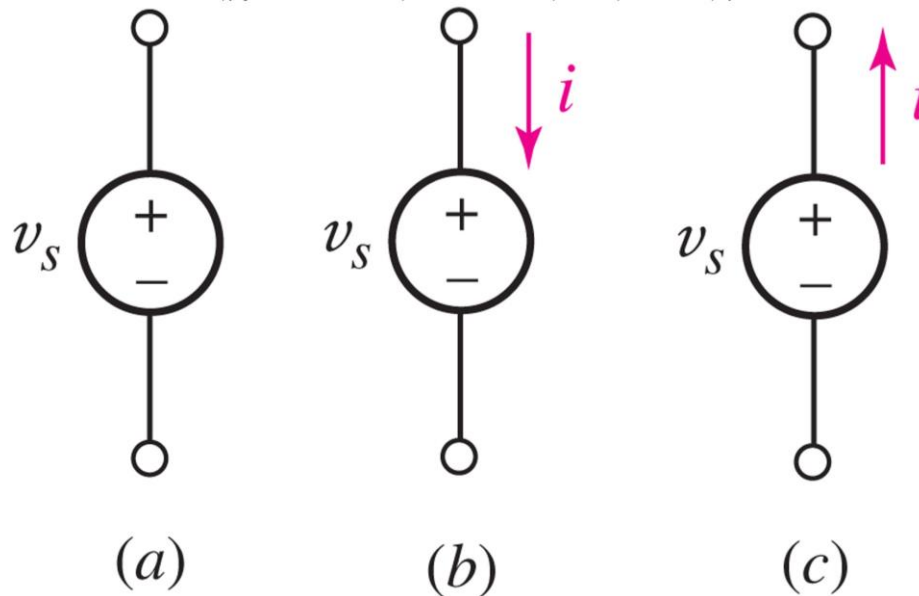
# Voltage Sources

- An ideal voltage source is a circuit element that will maintain the specified voltage  $v_s$  across its terminals.
- The current will be determined by other circuit elements.



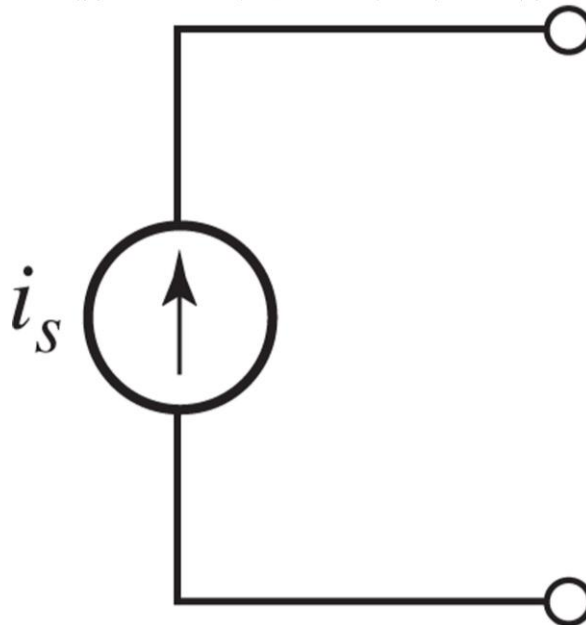
# Current Sources

- An ideal current source is a circuit element that maintains the specified current flow  $i_s$  through its terminals.
- The voltage is determined by other circuit elements.


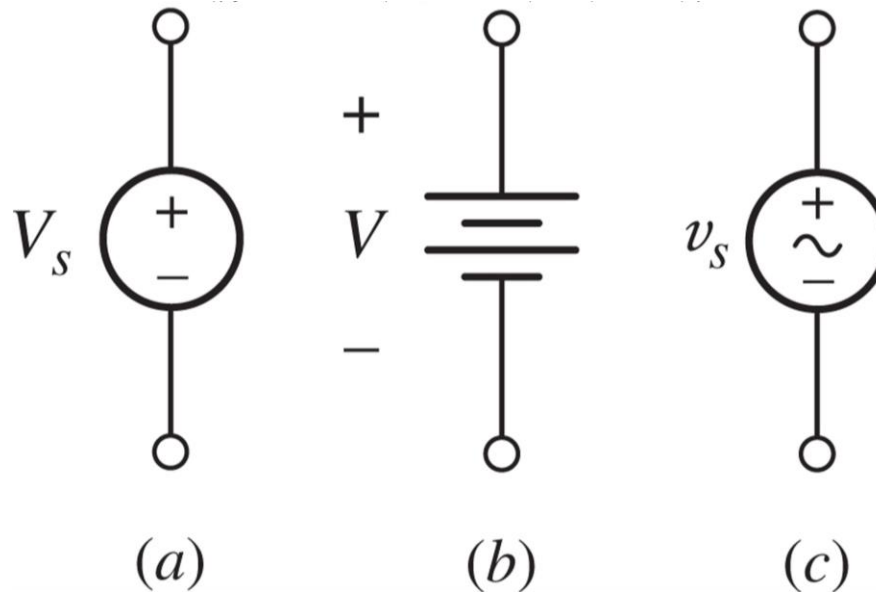
# Battery as Voltage Source


- A voltage source is an idealization (no limit on current) and generalization (voltage can be time-varying) of a battery.
- A battery supplies a constant “dc” voltage  $V$  but in practice a battery has a maximum power.


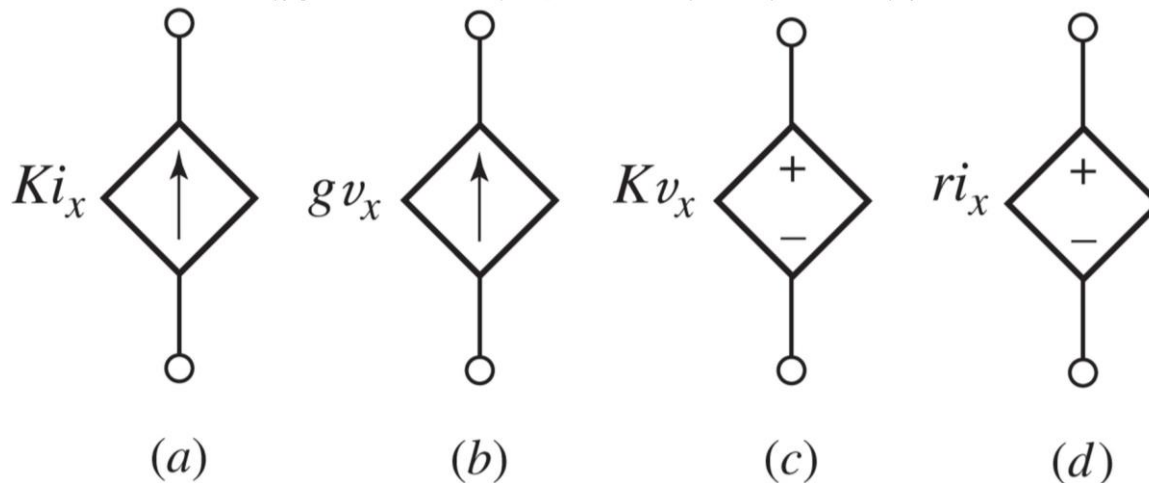
# Dependent Sources


Dependent current sources (a) and (b) maintain a *current* specified by another circuit variable.

Dependent voltage sources (c) and (d) maintain a *voltage* specified by another circuit variable.


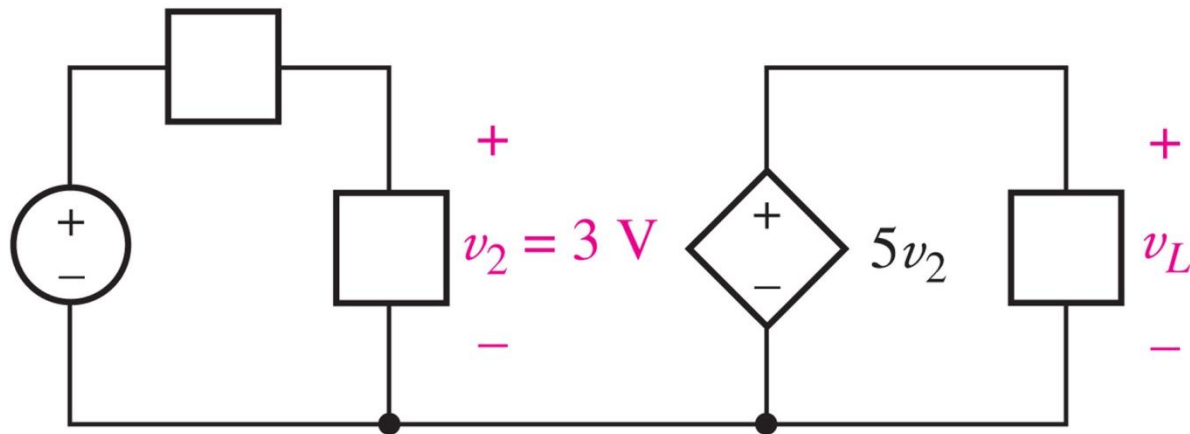
# Example: Dependent Sources

Find the voltage  $v_L$  in the circuit below.






# Ohm's Law: Resistance

- A (linear) resistor is an element for which
  - $v = iR$
- where the constant  $R$  is a resistance.
- The equation is known as “Ohm’s Law.”
- The unit of resistance is ohm ( $\Omega$ ).




# Resistors

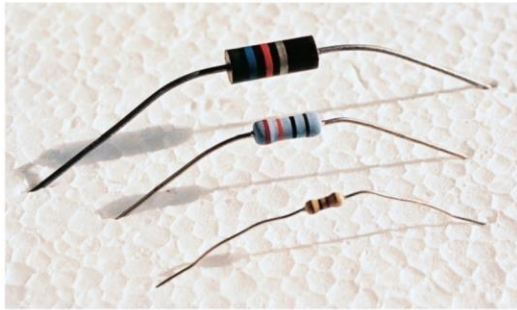
(a) typical resistors (b) power resistor  
(c) a 10 T $\Omega$  resistor (d) circuit symbol



(a)

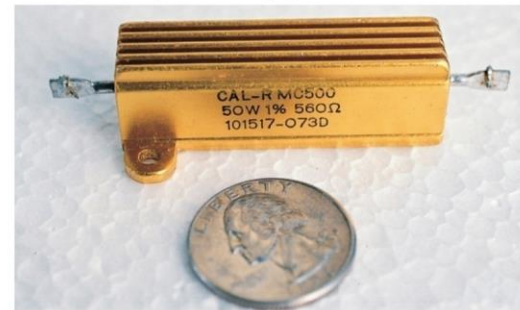

(b)

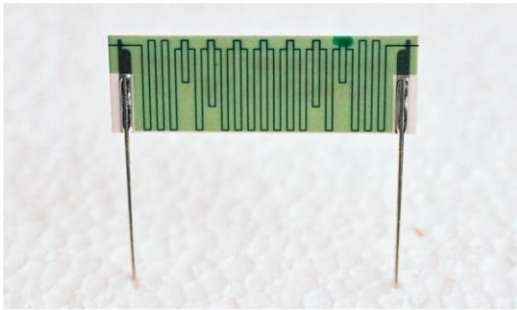


(c)



(d)
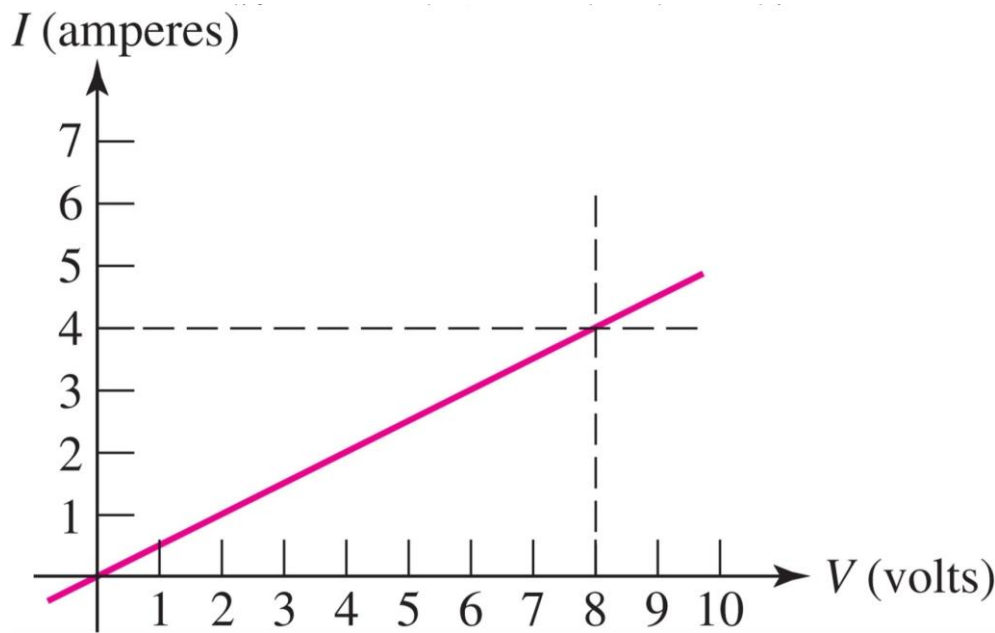
# The i-v Graph for a Resistor

For a resistor, the plot of current versus voltage is a straight line:



In this example, the slope is  $4 \text{ A} / 8 \text{ V}$  or  $0.5 \Omega^{-1}$ .


This is the graph for a 2 ohm resistor.

# Power Absorption

Resistors absorb power: since  $v=iR$

$$p=vi = v^2/R = i^2R$$

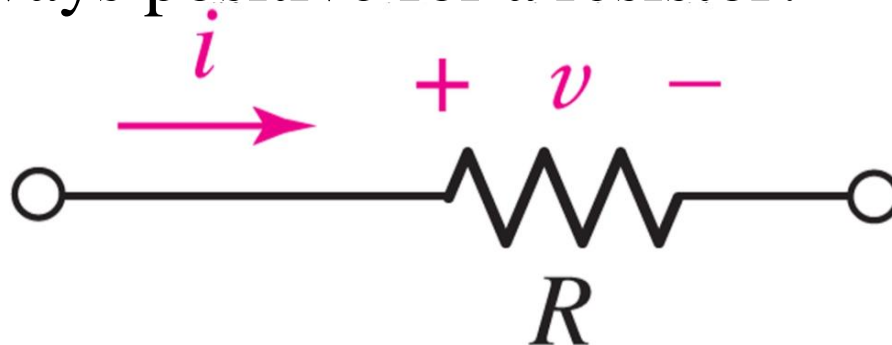Positive power means the device is absorbing energy.  
Power is always positive for a resistor!



# Example: Resistor Power

A  $560\ \Omega$  resistor is connected to a circuit which causes a current of  $42.4\ \text{mA}$  to flow through it. Calculate the voltage across the resistor and the power it is dissipating.


$$v = iR = (0.0424)(560) = 23.7\ \text{V}$$

$$p = i^2 R = (0.0424)^2(560) = 1.007\ \text{W}$$

# Wire Gauge and Resistivity

The resistance of a wire is determined by the resistivity of the conductor as well as the geometry:

$$R = \rho l / A$$

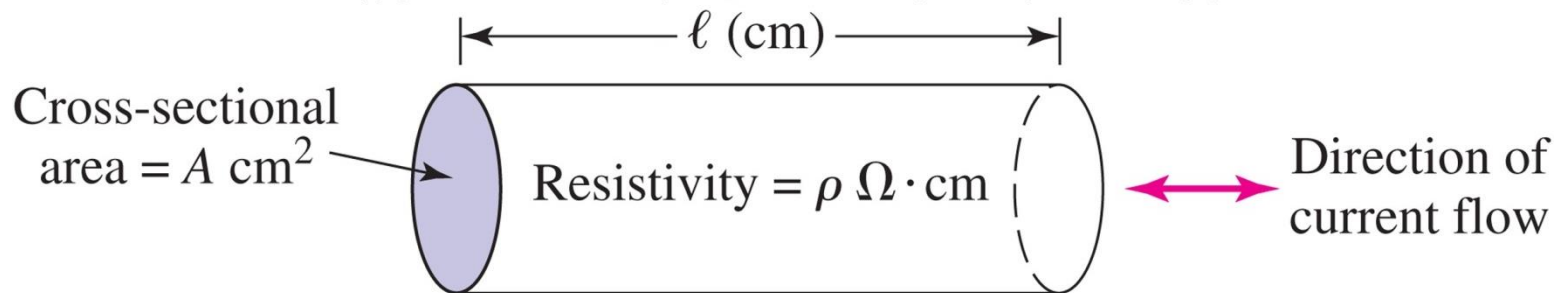

[In most cases, the resistance of wires can be assumed to be 0 ohms.]

# Conductance

- We sometimes prefer to work with *the reciprocal of resistance* ( $1/R$ ), which is called conductance (symbol  $G$ , unit siemens (S)).
- A resistor  $R$  has conductance  $G=1/R$ .
- The  $i$ - $v$  equation (i.e. Ohm's law) can be written as

$$i = Gv$$

# Open and Short Circuits

- An open circuit between A and B means  $i=0$ .
- *Voltage across* an open circuit: any value.
- An open circuit is equivalent to  $R = \infty \Omega$ .
  
- A short circuit between A and B means  $v=0$ .
- *Current through* a short circuit: any value.
- A short circuit is equivalent to  $R = 0 \Omega$ .