

EEE213 Power Electronics and Electromechanism




1a. Review of Three-phase system

Rectification
Controllability
Uncontrolled and Controlled
vs
Input power (source)
Single phase and Three phase





Single-phase voltage

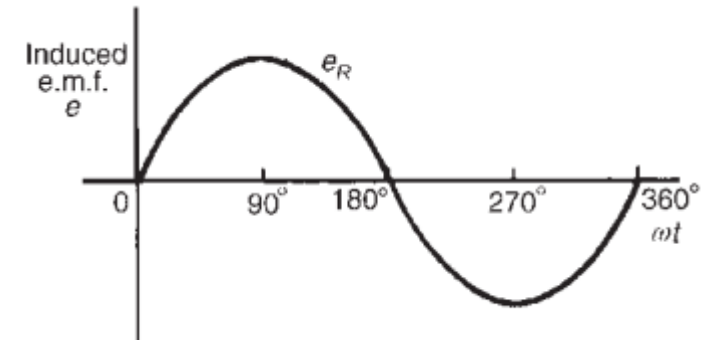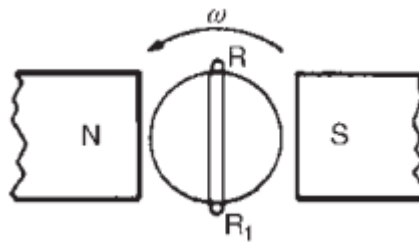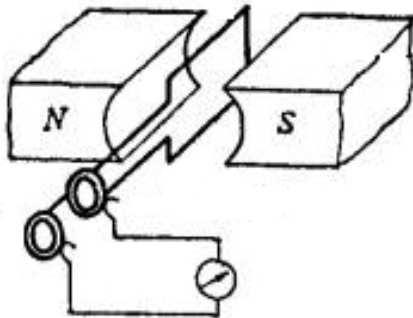- The voltage induced by a single coil when rotated in a uniform magnetic field is known as a **single-phase voltage**.





Single-phase voltage

- The standard voltage for a single-phase a.c. supply is:
 - 220V (r.m.s.) in Chinese system;
 - 240V (r.m.s.) in UK system.
- When electric power is supplied to consumers, two wires are used, one called *the live conductor (usually coloured red, L)* and the other is called *the neutral conductor (usually coloured black, N)*. The neutral is usually connected via protective gear to earth, *the earth wire being coloured green, E*.

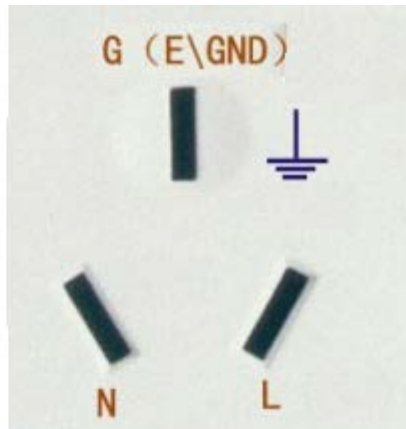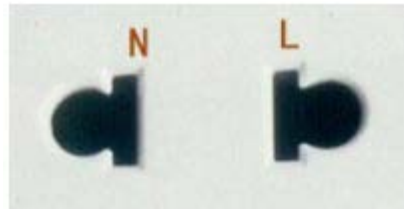


Three-phase voltage

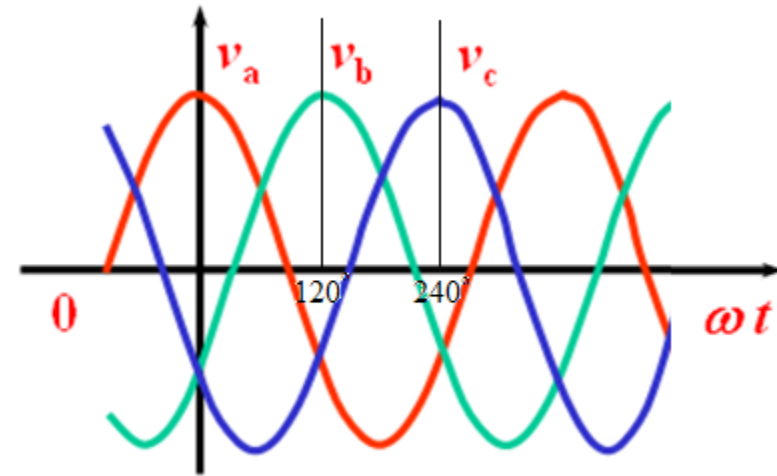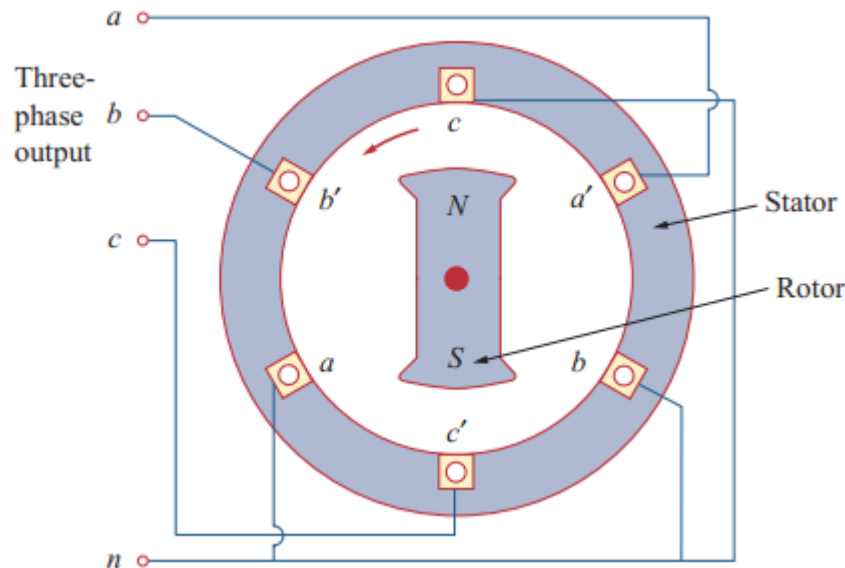- A three-phase supply is generated when three coils are placed 120° apart and the whole rotated in a uniform magnetic field.
- The result is three independent supplies of equal volt-ages which are each displaced by 120° from each other.




Connections of three-phase supply

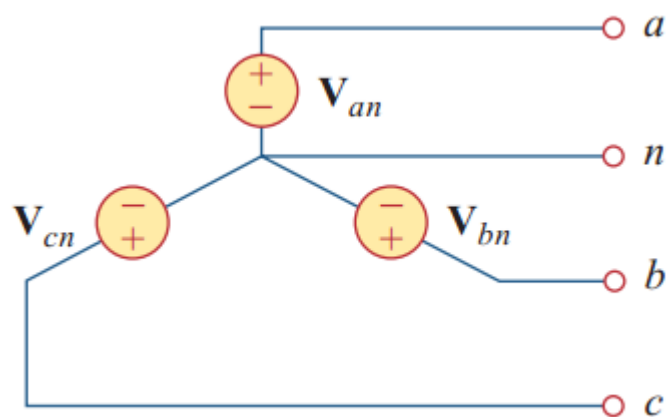- A typical three-phase system consists of three voltage sources connected to loads by three or four wires.
- A three-phase system is equivalent to three single-phase circuits.
- The voltage sources can be either Y-connected or Δ -connected.



Y-connection

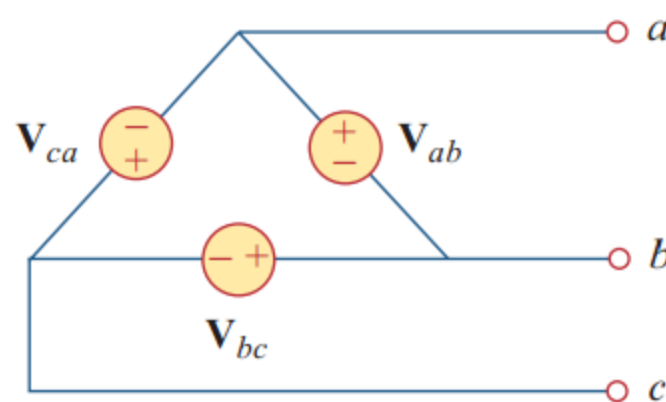

Δ -connection

(not used in this module)

Y-connection

- The voltages v_{an} and v_{bn} are respectively between lines a, b, and c, and the neutral line n.
- These voltages are called *phase voltages*.

Time domain

$$v_{an}(t) = V \cos(\omega t)$$

$$v_{bn}(t) = V \cos(\omega t - 120^\circ)$$

$$\begin{aligned} v_{cn}(t) &= V \cos(\omega t - 240^\circ) \\ &= V \cos(\omega t + 120^\circ) \end{aligned}$$


Phasor domain

$$\mathbf{V}_{an} = V \angle 0^\circ$$

$$\mathbf{V}_{bn} = V \angle (-120^\circ)$$

$$\mathbf{V}_{cn} = V \angle (-240^\circ) = V \angle 120^\circ$$


Phasor plane

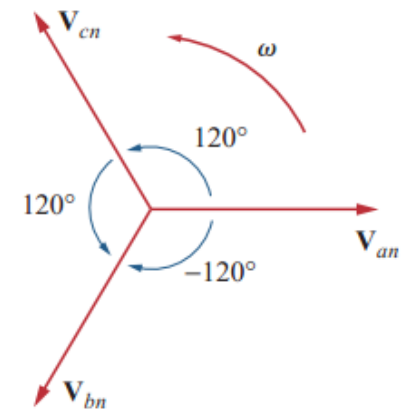


- This is known as the *abc sequence* or *positive sequence*. In this phase sequence, \mathbf{V}_{an} leads \mathbf{V}_{bn} , which in turn leads \mathbf{V}_{cn} .

Connections of three-phase load

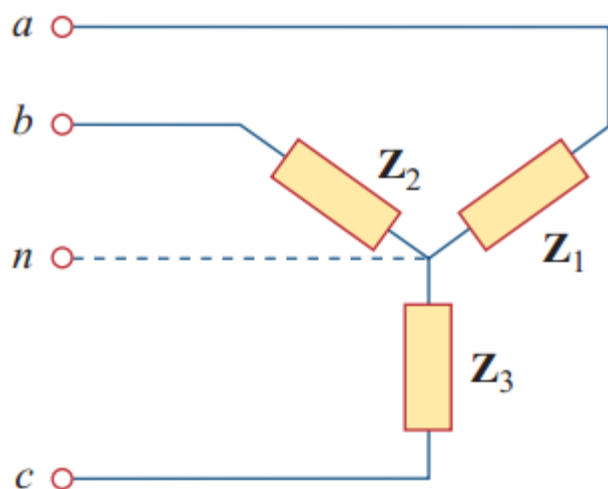- Like the generator connections, a three-phase load can be either Y-connected or Δ -connected, depending on the end application.



Y-connection

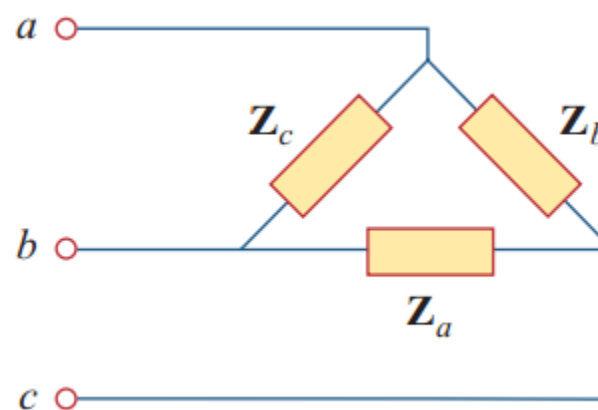


Δ -connection

(not used in this module)

- A balanced load is one in which the phase impedances are equal in magnitude and in phase, i.e. $Z_1=Z_2=Z_3=Z_Y$.

A balanced Y-Y connected circuit

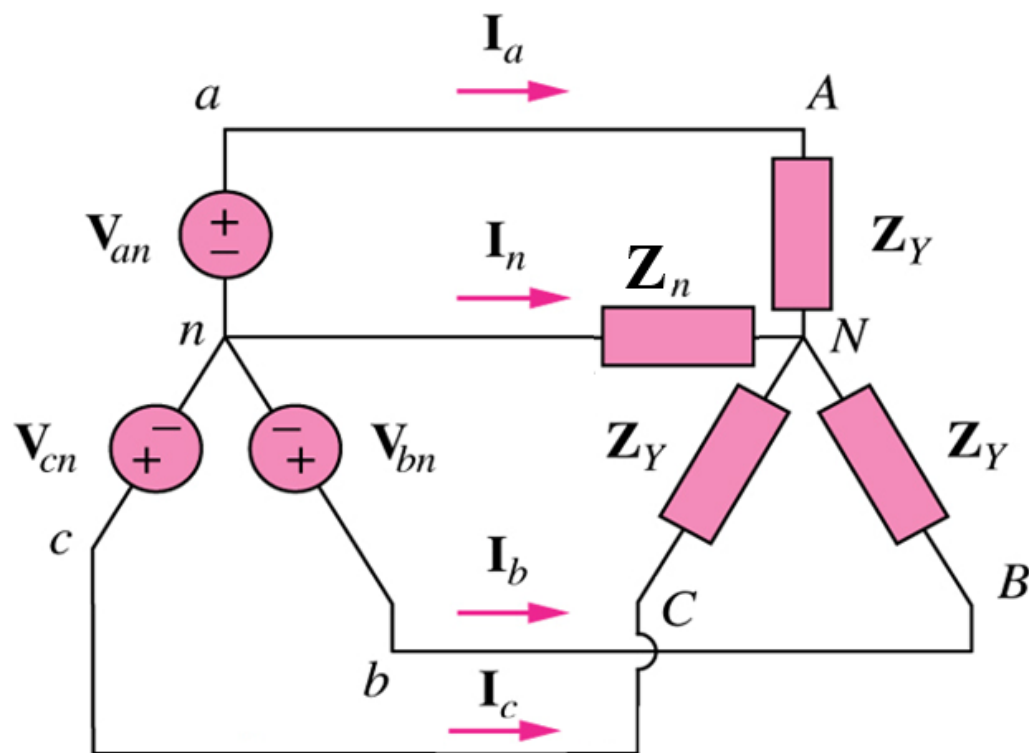- A **balanced Y-Y** system is a three-phase system with a balanced Y-connected source and a balanced Y-connected load.



Phase voltages V_p :

V_{an} , V_{bn} and V_{cn} ;

Line voltages V_L :

V_{ab} , V_{bc} and V_{ca} ;

Phase currents I_p :

I_a , I_b and I_c ;

Line currents $I_L = I_p$.


Voltages in Y-Y connected circuit

- Phase voltage V_p : The voltage across the ends of each coil
- Line voltage V_L : The voltage between any two lines


$$\begin{aligned} \mathbf{V}_a &= V \angle 0^\circ \text{ V} \\ \mathbf{V}_b &= V \angle -120^\circ \text{ V} \\ \mathbf{V}_c &= V \angle -240^\circ \text{ V} \end{aligned}$$


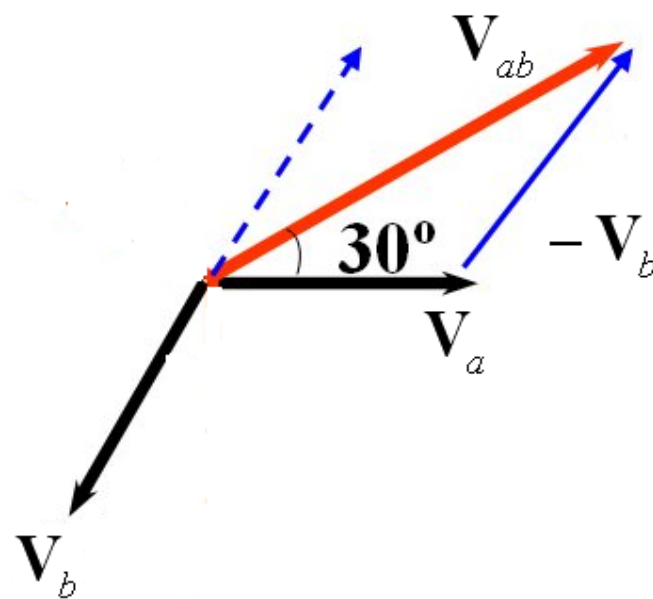
$$\begin{aligned} \mathbf{V}_{ab} &= \mathbf{V}_a - \mathbf{V}_b \\ &= V \angle 0^\circ - V \angle -120^\circ = \sqrt{3}V \angle 30^\circ \\ &= \sqrt{3}V (\cos 30^\circ + j \sin 30^\circ) \end{aligned}$$


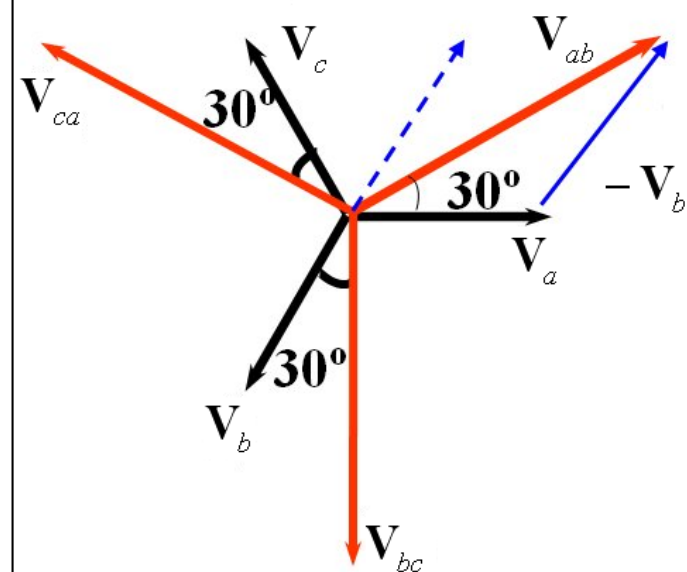
$$\begin{aligned} \mathbf{V}_{ab} &= \mathbf{V}_a - \mathbf{V}_b = \sqrt{3}V_p \angle 30^\circ \\ \mathbf{V}_{bc} &= \mathbf{V}_b - \mathbf{V}_c = \sqrt{3}V_p \angle (-90^\circ) \\ \mathbf{V}_{ca} &= \mathbf{V}_c - \mathbf{V}_a = \sqrt{3}V_p \angle (-210^\circ) \end{aligned}$$



Currents in Y-Y connected circuit

- In the balanced Y-Y circuit, Line currents are the same as phase currents, $I_p = I_L$.

$$I_a = \frac{V_a}{Z_Y}$$

$$I_b = \frac{V_b}{Z_Y} = \frac{V_a \angle (-120^\circ)}{Z_Y} = I_a \angle (-120^\circ)$$

$$I_c = \frac{V_c}{Z_Y} = \frac{V_a \angle (-240^\circ)}{Z_Y} = I_a \angle (-240^\circ)$$

$$I_n = I_a + I_b + I_c = 0$$

$$V_{nN} = Z_n I_n = 0$$





The neutral line could be removed without any influence to the circuit.
(The source and the load must be balanced!!!)




Power in AC circuit

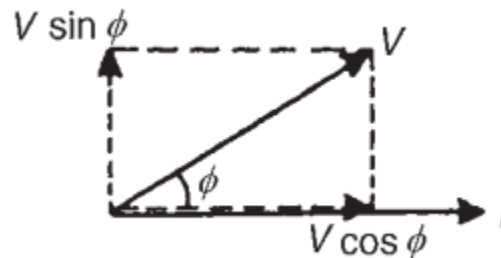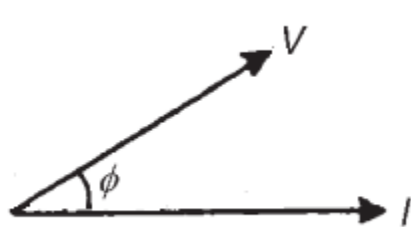- The power at any instant is given by the product of the voltage and current at that instant, i.e. the instantaneous power: $p(t) = v(t)i(t)$.
- In the case where the current I lags the applied voltage V by angle ϕ .



Phasor diagram

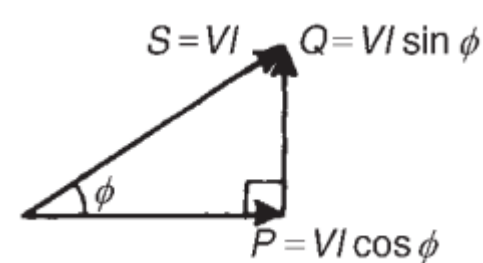

Power triangle

- Average power dissipated in the circuit (the real power) is calculated by: $P = VI \cos \phi$.

Real Power in a Balanced 3-phase System

- The power in a three-phase system is the sum of the power in each phase.

- Real power in phase A:

If $v_A(t) = \sqrt{2}V_p \sin \omega t$

$$i_A(t) = \sqrt{2}I_p \sin(\omega t - \varphi)$$

So

$$\begin{aligned} p_A &= v_A i_A = 2V_p I_p \sin \omega t \sin(\omega t - \varphi) \\ &= V_p I_p \cos \varphi - V_p I_p \cos(2\omega t - \varphi) \text{ (W)} \end{aligned}$$

- Similarly for phase B and C:

$$p_B = v_B i_B = V_p I_p \cos \varphi - V_p I_p \cos[2(\omega t - 120^\circ) - \varphi]$$


$$p_C = v_C i_C = V_p I_p \cos \varphi - V_p I_p \cos[2(\omega t + 120^\circ) - \varphi]$$

Real Power in a Balanced 3-phase System

- Total power:

$$p = p_A + p_B + p_C = 3V_p I_p \cos \varphi = P$$

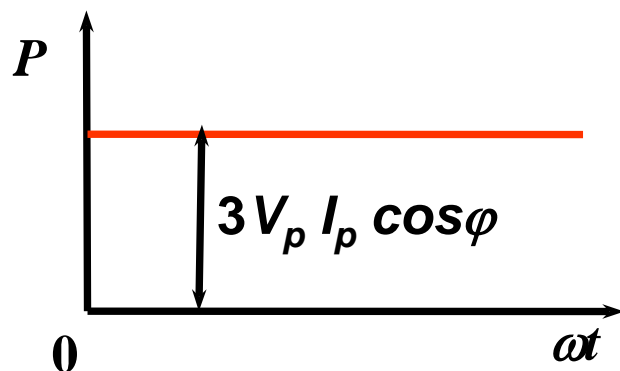- The instantaneous total power is not function of time



- Expressed in line voltages and currents:

$$V_L = \sqrt{3} V_p \quad I_L = I_p$$

$$P = 3 \frac{V_L}{\sqrt{3}} I_L \cos \varphi = \sqrt{3} V_L I_L \cos \varphi$$

$$P = 3V_p I_p \cos \varphi$$



Virtual power and Apparent power

- Virtual power (Reactive power): Reactive power is the product of the voltage, current and the sine of the phase angle between them:


$$Q = \sqrt{3}V_L I_L \sin \varphi \quad \text{Volt amperes reactive (Var)}$$

- Inductive reactive power is defined as positive power
 - Capacitive reactive power is defined as negative reactive power.
- Apparent power: Apparent power is the product of the voltage and current without accounting of the phase angle:

$$S = \sqrt{3}V_L I_L \quad \text{Volt amperes (V A)}$$

Power Triangle & Power Factor

Power triangle

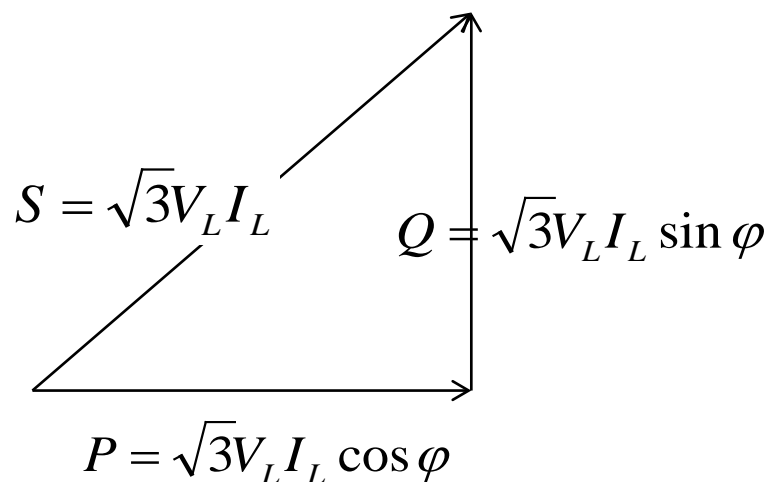

Power complex form

$$\mathbf{S} = \mathbf{P} + j\mathbf{Q}$$

$$\mathbf{S} = 3\mathbf{V}_p \mathbf{I}_p^*$$

Power factor

$$\begin{aligned} \text{Power Factor} &= \frac{\text{Real Power } P}{\text{Apparent Power } S} \\ &= \cos \varphi \end{aligned}$$