

# EEE225 Advanced Electrical Circuits and Electromagnetics

## Lecture 8 Transient Analysis – 2<sup>nd</sup> order circuits

Dr. Zhao Wang

zhao.wang@xjtlu.edu.cn

Room EE322





# Content

---

- Natural response
  - Parallel RLC circuit
    - SODE (Second Order Differential Equation)
    - Initial conditions
    - Damping factor and damping systems
  - Series RLC circuit
    - SODE
    - Step of solving SODE questions
  - Comparison between parallel and series RLC circuits
- Step response
  - Parallel RLC circuit
  - Series RLC circuit
  - Summary
- General Second order circuit
  - Solving procedure
- Practical application
  - Automobile ignition circuit
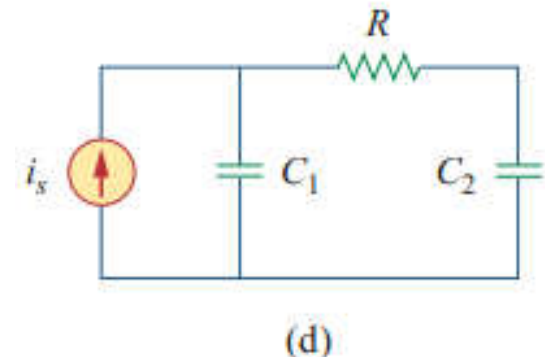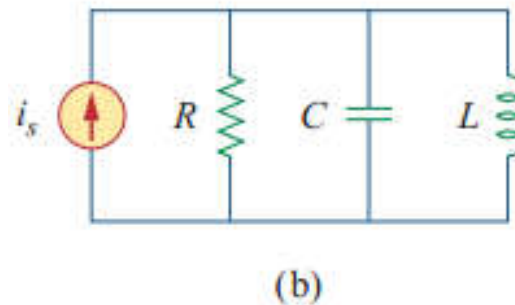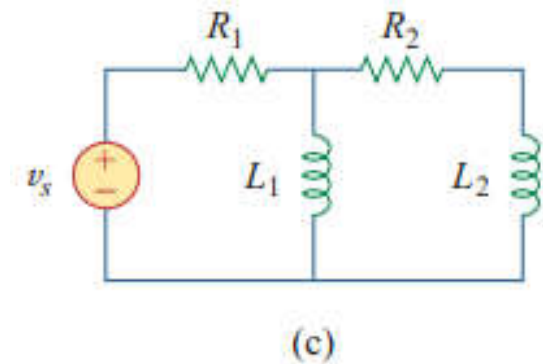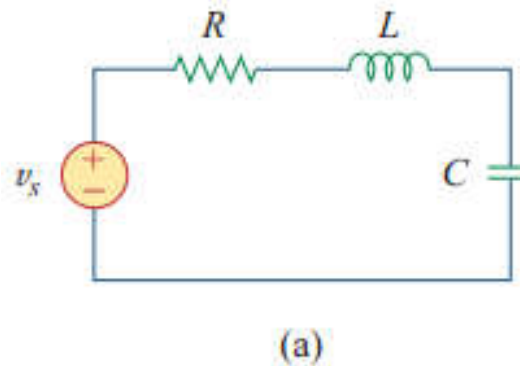
# Second-order Circuits

- A second order circuit is characterized by a second order differential equation. It consists of resistors and the equivalent of **TWO** energy storage elements.
- Typical examples of second order circuits:
  - Series RLC circuit
  - Parallel RLC circuit
  - RLL circuit
  - RCC circuit



# Parallel RLC Circuit - Obtaining the SODE

## SODE - Second Order Differential Equation

- By applying the KCL at the node:

$$i_R(t) + i_L(t) + i_C(t) = 0$$


- Where we have

$$i_R(t) = \frac{v}{R}$$

$$i_C(t) = C \frac{dv}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{t_0}^t v dt' - i(t_0)$$
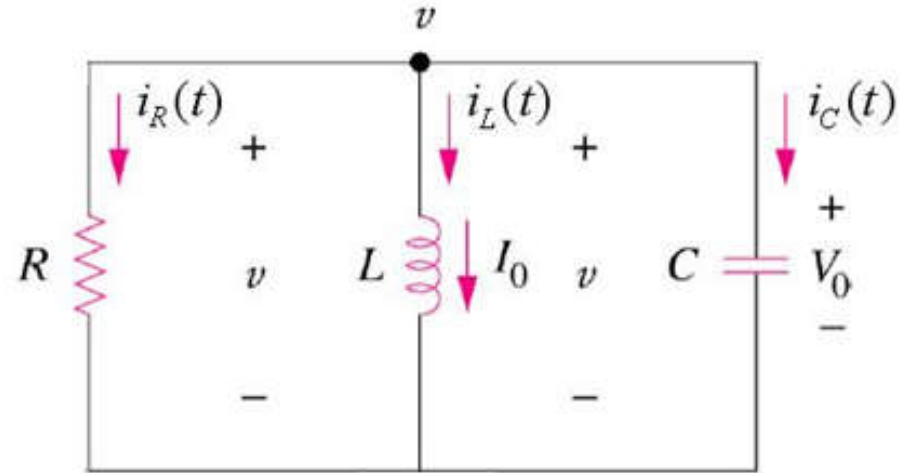
$$\left. \begin{array}{l} i_R(t) = \frac{v}{R} \\ i_C(t) = C \frac{dv}{dt} \\ i_L(t) = \frac{1}{L} \int_{t_0}^t v dt' - i(t_0) \end{array} \right\} \frac{v}{R} + C \frac{dv}{dt} + \frac{1}{L} \int_{t_0}^t v dt' - i(t_0) = 0$$



- Take derivative of both sides, then divide by C, we get

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

# Parallel RLC Circuit - Solving the SODE

- By assuming the solution of the form  $Ae^{st}$ ,
  - $A$  is a constant determined by initial conditions
  - $s$  is a constant determined by the coefficients of the differential equation (by circuit components)

- The *characteristic equation* is

$$As^2e^{st} + \frac{1}{RC}Ase^{st} + \frac{A}{LC}e^{st} = 0 \quad \longrightarrow \quad s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

- The two solutions are:

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \quad \text{and} \quad s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

- The general form of the natural response

$$v_n(t) = A_1e^{s_1t} + A_2e^{s_2t}$$

Where  $A_1$  and  $A_2$  must be found by applying the given initial condition

# Parallel RLC Circuit - Determining $A_1$ and $A_2$

- Since  $v_n(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ 
  - 1)  $v_n(0^+) = A_1 + A_2$
  - 2)  $\frac{dv_n(0^+)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t} \Big|_{t=0^+} = A_1 s_1 + A_2 s_2$
- Therefore, with the knowledge of  $s_1$  and  $s_2$ , we need two initial conditions to determine the value of  $A_1$  and  $A_2$ :

$$v_n(0^+) \quad \text{and} \quad \frac{dv_n(0^+)}{dt}$$

- Where  $0^+$  is the time just after the changes in circuit, i.e. switch movement.

## Parallel RLC Circuit – SODE of $i_L(t)$

- Similarly, we can solve for the inductor current  $i_L(t)$ , and get the SODE like:

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L = 0$$

- By assuming the exponential solution  $Ae^{st}$ , it can also be written as

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

- Whose solution also has the form

$$i_{L,n}(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

where  $A_1$  and  $A_2$  are determined by the given initial conditions.



# Parallel RLC Circuit - Finding initial values

---

- Two key points:
  - Polarity of voltage across the capacitor, and the direction of the current through the inductor.
  - The capacitor voltage is always continuous, and the inductor current is always continuous

$$v_C(t = 0^+) = v_C(t = 0^-)$$


$$i_L(t = 0^+) = i_L(t = 0^-)$$

Normally start from finding variables that cannot change abruptly.






# Parallel RLC Circuit - Finding initial values

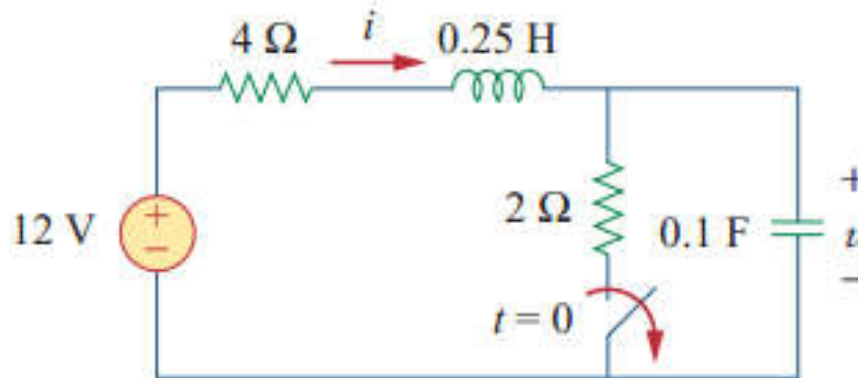- Example:
- The switch has been closed for a long time. It is open at  $t = 0$ .
  - Find:  $i(0^+)$ ,  $v_C(0^+)$ ,  $\frac{di(0^+)}{dt}$ ,  $\frac{dv_C(0^+)}{dt}$ ,  $i(\infty)$  and  $v_C(\infty)$




Ref. 3, example 8.1

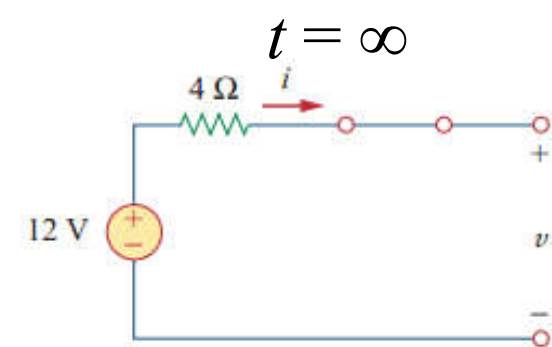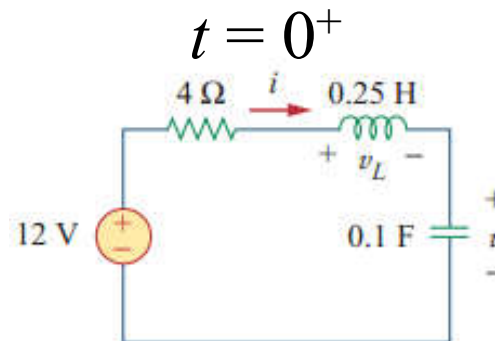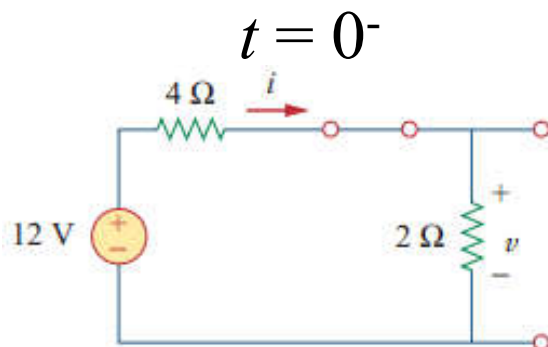
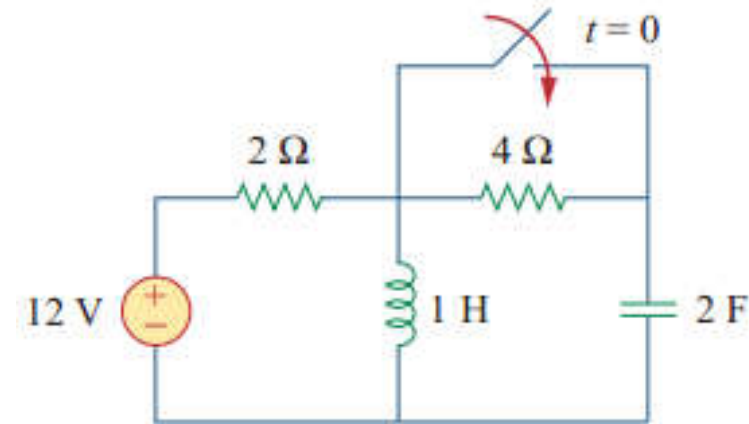
# Quiz

- For the circuit as shown, the capacitor voltage at  $t = 0^+$  (just after the switch is closed) is:
  - (a) 0 V; (b) 4 V; (c) 8 V; (d) 12 V.
- For the same circuit as shown, the inductor voltage at  $t = 0^+$  (just after the switch is closed) is:
  - (a) 0 V; (b) 4 V;
  - (c) 8 V; (d) 12 V.



# Parallel RLC Circuit - Definition of Frequency Terms

- Define  $\omega_0$  as the *resonant frequency*, and  $\alpha$  as the *neper frequency*, or the *exponential damping coefficient*:

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \alpha = \frac{1}{2RC}$$

- The characteristic equation can also be written as

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

- Then the  $s_1$  and  $s_2$  are called *complex frequencies*

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

- The natural response is still

$$v_n(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$



# Parallel RLC Circuit - Damping factors

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

- The value of the term  $\sqrt{\alpha^2 - \omega_0^2}$  determines the behavior of the response.
  - 1. Over Damped System:  $\alpha > \omega_0$ ,  $s_1$  and  $s_2$  are two unequal real numbers;
  - 2. Critical Damped System:  $\alpha = \omega_0$ ,  $s_1$  and  $s_2$  are two equal real numbers;
  - 3. Under Damped System:  $\alpha < \omega_0$ ,  $s_1$  and  $s_2$  are two complex numbers,  
$$s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2}, \quad s_2 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2}$$

The system exhibits oscillatory behavior.




# Parallel RLC Circuit - 1. Over Damped System

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{and} \quad \alpha = \frac{1}{2RC}$$

- Over Damped System:  $\alpha > \omega_0$ , implies  $L > 4R^2C$ .
- Both  $s_1$  and  $s_2$  are two negative real numbers, the response is

$$v_n(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

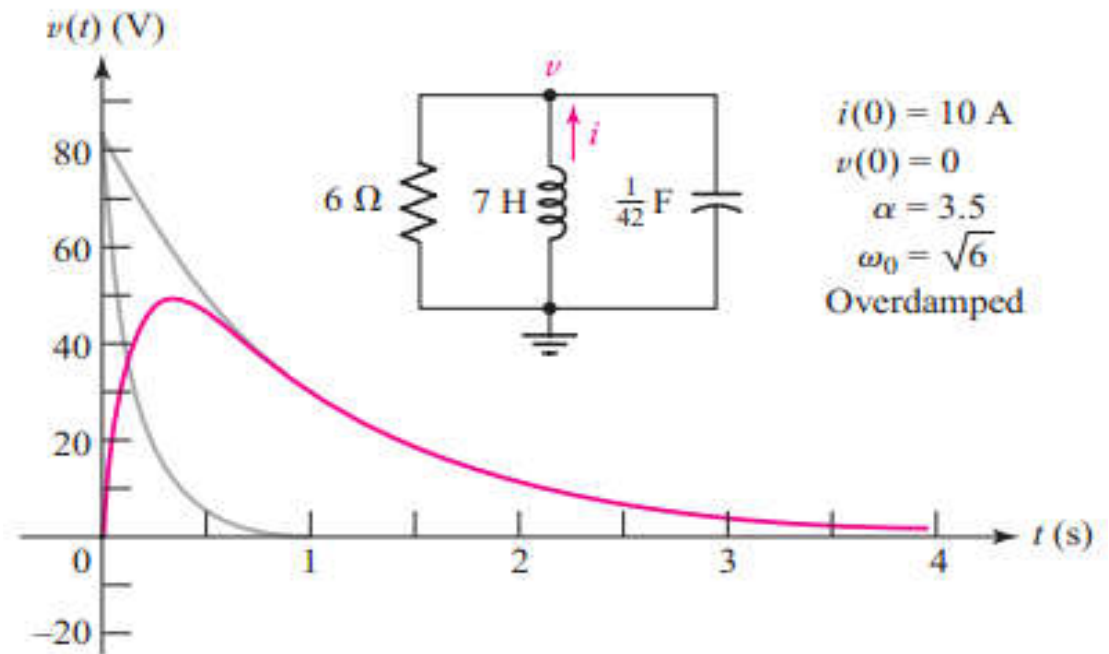- Thus,  $v_n(t)$  decays and approach zero as time increases  $t \rightarrow \infty$ .




# Parallel RLC Circuit - 2. Critical Damped System

- Critical Damped System:  $\alpha = \omega_0$ , implies  $L = 4R^2C$ .
- Since  $s_1$  and  $s_2$  are two equal real numbers,  $s_1 = s_2 = -\alpha$ , the response is

$$v_n(t) = e^{-\alpha t} (A_1 t + A_2)$$

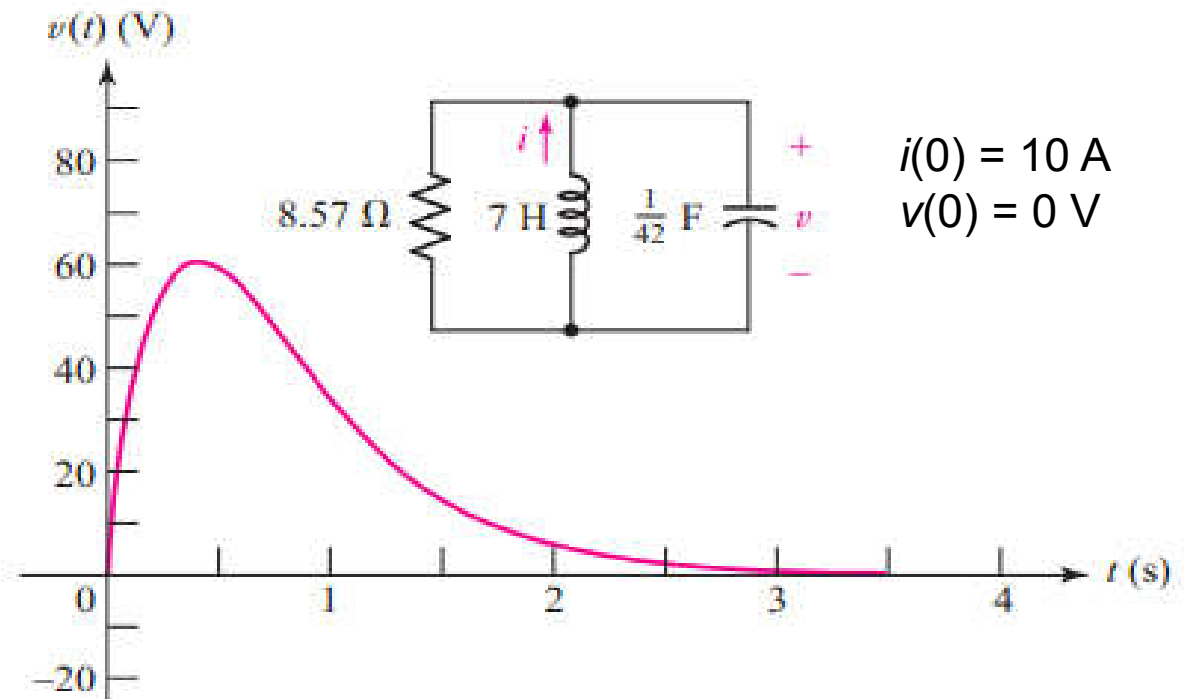- $v_n(t)$  also decays and approach zero as time increases  $t \rightarrow \infty$ .



# Parallel RLC Circuit - 3. Under Damped System

- Under Damped System:  $\alpha < \omega_0$ , implies  $L < 4R^2C$ .
- Since  $s_1$  and  $s_2$  are two complex numbers,

$$s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2}, s_2 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2}$$

- Define  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ , the response now be written as

$$\begin{aligned} v_n(t) &= e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t}) \\ &= e^{-\alpha t} \left[ \underbrace{(A_1 + A_2)}_{B_1} \cos \omega_d t + \underbrace{j(A_1 - A_2)}_{B_2} \sin \omega_d t \right] \end{aligned}$$

- Therefore,  $v_n(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$


Where  $B_1$  and  $B_2$  are determined by the initial conditions

# Parallel RLC Circuit - 3. Under Damped System

$$v_n(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$


Where  $B_1$  and  $B_2$  are determined by the initial conditions
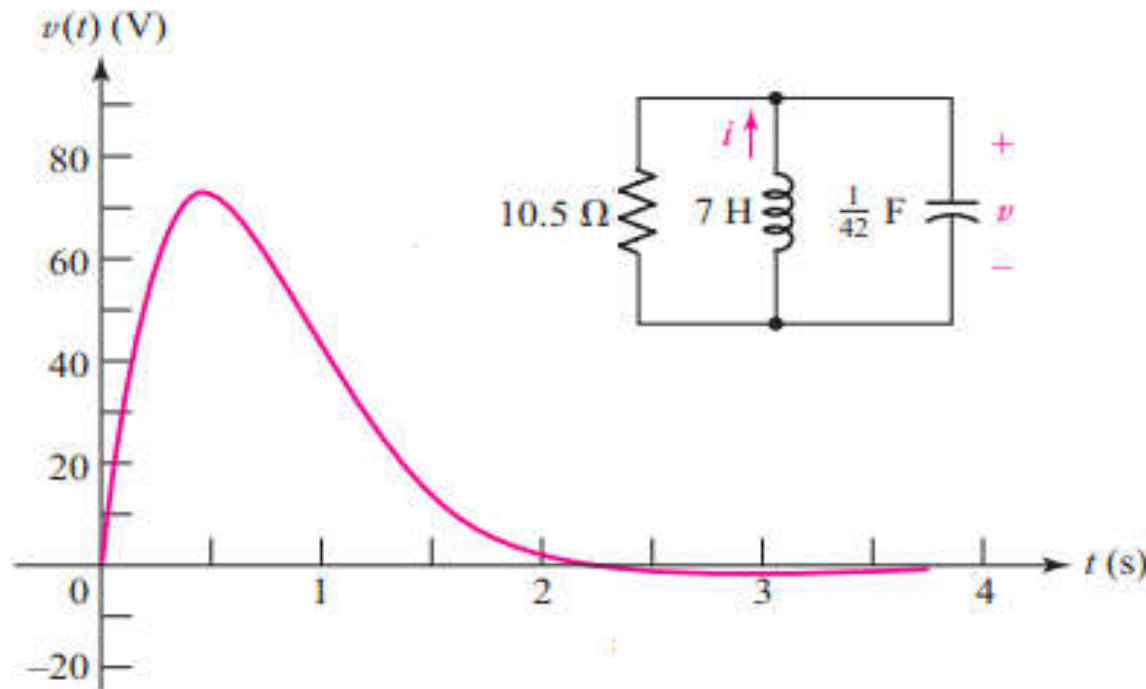
$$\begin{aligned} i(0) &= 10 \text{ A} \\ v(0) &= 0 \text{ V} \end{aligned}$$





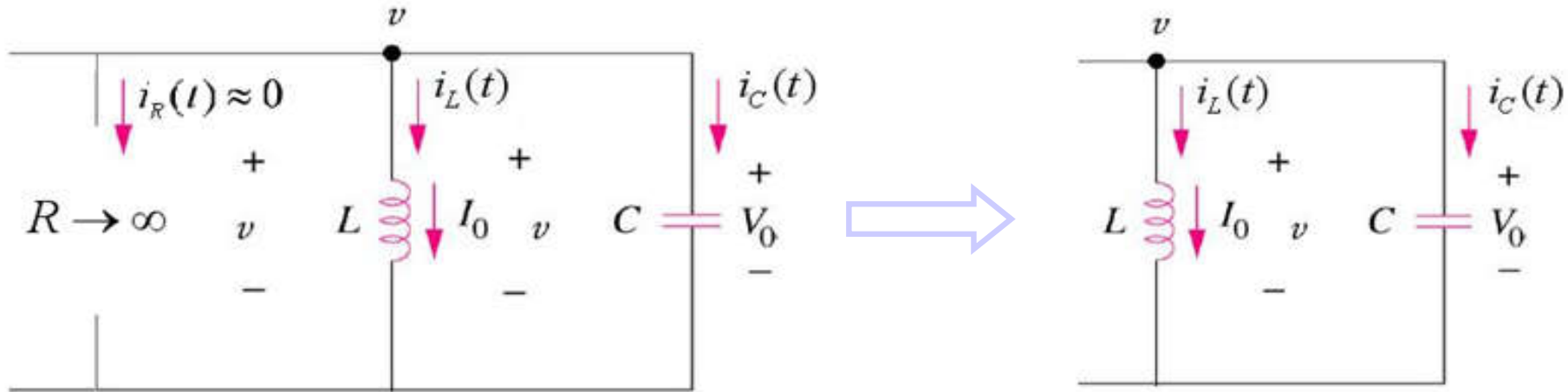
# Parallel RLC Circuit - Role of the Resistor



$$\alpha = \frac{1}{2RC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

when  $R \rightarrow \infty$ ,  $\alpha \rightarrow 0$ ,  $\alpha \ll \omega_0$ ,
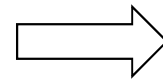
$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \approx \omega_0$$



$$v_n(t) = B_1 \cos \omega_0 t + B_2 \sin \omega_0 t$$

$$i_L(t) = K_1 \sin \omega_0 t + K_2 \cos \omega_0 t$$

Actual parallel RLC circuits can be made to have effective values of  $R$  so large that a natural **undamped** sinusoidal response can be maintained for years without supplying any additional energy.

# Parallel RLC Circuit – Summary of solving procedure

- 1. Obtain the SODE:  $\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$
- 2. With  $\omega_0 = \frac{1}{\sqrt{LC}}$  and  $\alpha = \frac{1}{2RC}$ , evaluate the damped condition:
  - 1) Over Damped System:  $\alpha > \omega_0$ ,  $s_1$  and  $s_2$  are two unequal real numbers,  $v_n(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
  - 2) Critical Damped System:  $\alpha = \omega_0$ ,  $s_1$  and  $s_2$  are two equal real numbers  $\alpha$ ,  $v_n(t) = e^{-\alpha t} (A_1 t + A_2)$
  - 3) Under Damped System:  $\alpha < \omega_0$ ,  $s_1$  and  $s_2$  are two complex numbers  $s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2}$ ,  $s_2 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2}$  and  $v_n(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$



# Parallel RLC Circuit – Summary of solving procedure

- 3. Determine coefficients  $A_1$  and  $A_2$  (or  $B_1$  and  $B_2$ ) according to the initial conditions  $v_n(0^+)$  and  $\frac{dv_n(0^+)}{dt}$  :

- 1) Over damped system:

$$v_n(0^+) = A_1 + A_2, \text{ and } \frac{dv_n(0^+)}{dt} = A_1 s_1 + A_2 s_2$$

- 2) Critical damped system:

$$v_n(0^+) = A_2, \text{ and } \frac{dv_n(0^+)}{dt} = A_1 - A_2 \alpha$$

- 3) Under damped system:

$$v_n(0^+) = B_1, \text{ and } \frac{dv_n(0^+)}{dt} = -\alpha B_1 + \omega_d B_2$$

# Parallel RLC Circuit - Example 1

In a parallel RLC circuit:  $R = 500 \, \Omega$ ,  $C = 1 \, \mu\text{F}$ ,  $L = 0.2 \, \text{H}$ . The initial conditions are  $i_L(0) = 50 \, \text{mA}$  and  $v(0) = 0 \, \text{V}$ .

Find  $i_L(t)$ ,  $i_R(t)$  and  $v_c(t)$ .

## Solution

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 500 \times 1 \times 10^{-6}} = 10^3, \quad \omega_0^2 = \frac{1}{LC} = \frac{1}{0.2 \times 1 \times 10^{-6}} = 5 \times 10^6$$

$$\alpha^2 < \omega_0^2, \text{ underdamped}$$

From the characteristic equation:  $s^2 + 2\alpha s + \omega_0^2 = 0$ , we have

$$s^2 + 2 \times 10^3 s + 5 \times 10^6 = 0$$

$$s_1 = -1000 + j2000, \quad s_2 = -1000 - j2000$$

The response of  $i_L(t)$ :  $i_L(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{5 \times 10^6 - 10^6} = 2000$$



# Parallel RLC Circuit - Example 1 (cont.)

$$i_L(0) = 1 \times (B_1 \cos 0 + B_2 \sin 0) = 50 \times 10^{-3} \text{ A} \Rightarrow B_1 = 50 \times 10^{-3}$$

$$v(0) = L \left. \frac{di_L(t)}{dt} \right|_{t=0} \Rightarrow -1000 B_1 + 2000 B_2 = 0$$

$\Downarrow$

$$B_2 = 25 \times 10^{-3}$$

$$\text{So } i_L(t) = e^{-1000t} (50 \cos 2000t + 25 \sin 2000t) \text{ mA} \quad t \geq 0$$



$$v_L(t) = L \frac{di_L}{dt} = -25e^{-1000t} \sin 2000t \text{ V} \quad t \geq 0$$

$$v_C(t) = v_L(t) \quad t \geq 0$$

$$i_R = \frac{v_R(t)}{R} = \frac{v_L(t)}{R} = -50e^{-1000t} \sin 2000t \text{ mA} \quad t \geq 0$$


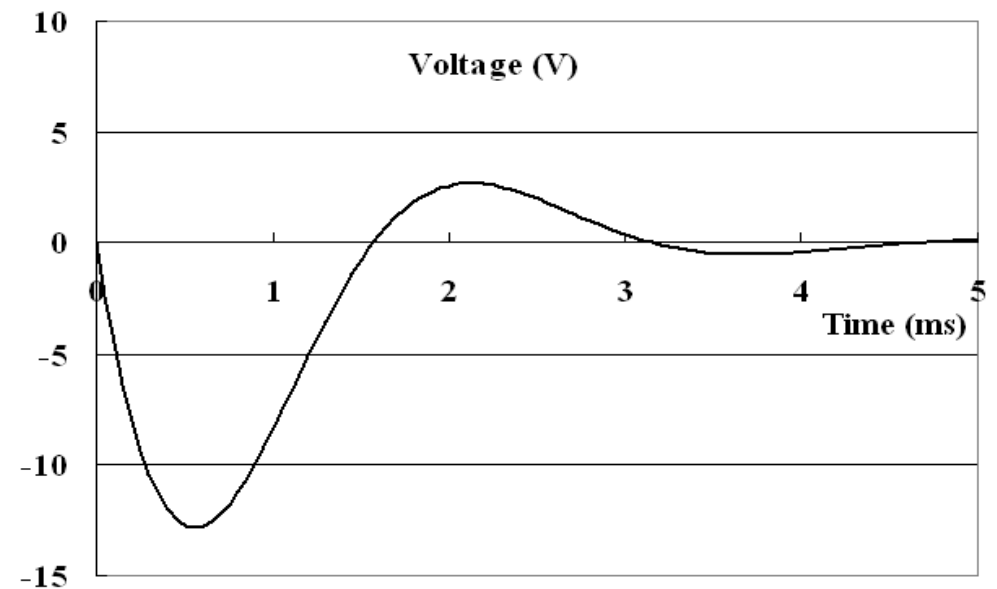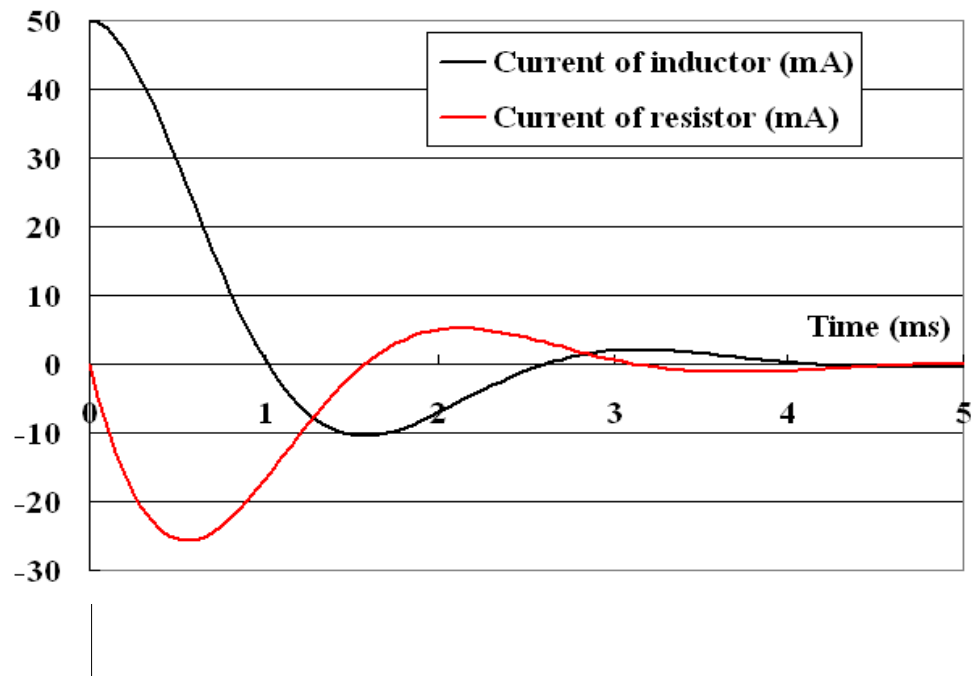
# Parallel RLC Circuit - Example 1 (cont.)



# Quiz

---

- If the roots of the characteristic equation of an RLC circuit are -2 and -3, the response is:
  - (a)  $(A \cos 2t + B \sin 2t)e^{-3t}$
  - (b)  $(A + 2Bt)e^{-3t}$
  - (c)  $Ae^{-2t} + Bte^{-3t}$
  - (d)  $Ae^{-2t} + Be^{-3t}$
- A parallel RLC circuit has  $L = 4$  H and  $C = 0.25$  F. The value of R that will produce under damping factor is:
  - (a)  $0.5 \Omega$ ;                      (b)  $1 \Omega$ ;
  - (c)  $2 \Omega$ ;                        (d)  $4 \Omega$ .



# Series RLC Circuit – Obtaining the SODE

By using KVL :  $v_R + v_C + v_L = v_s$

The current flowing in the circuit :

$$i = C \frac{dv_C}{dt}$$


The voltage  $v_R$  and  $v_L$  are given by

$$v_R = iR = RC \frac{dv_C}{dt}$$

$$v_L = L \frac{di}{dt} = LC \frac{d^2 v_C}{dt^2}$$

Then we have :
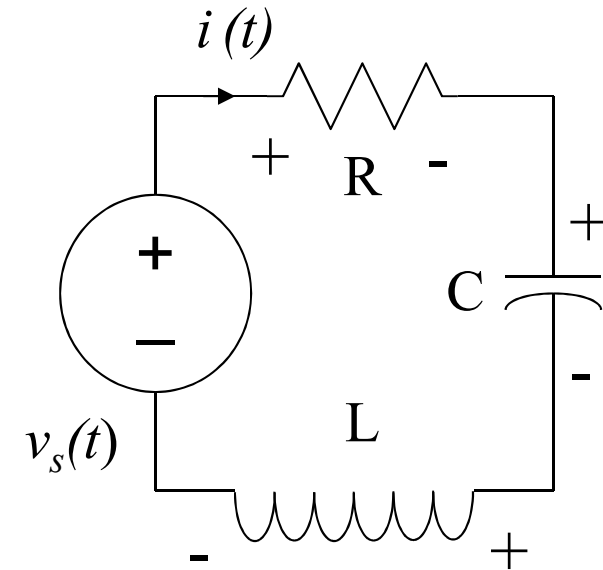
$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{1}{LC} v_s \quad (1)$$



Simpler we have:

$$v_C = v_{C,p} + v_{C,h}$$

where

$v_C$  : the complete solution

$v_{C,p}$  : the particular solution

$v_{C,h}$  : the homogeneous solution



# Series RLC Circuit – Solving the SODE

$$\frac{d^2 v_{C,h}}{dt^2} + \frac{R}{L} \frac{dv_{C,h}}{dt} + \frac{1}{LC} v_{C,h} = 0 \quad (2)$$

Assuming a homogeneous solution has the following form :

$$v_{C,h} = Ae^{st} \quad (A \neq 0)$$

$A$  is a constant determined by initial conditions.

$s$  is a constant determined by the coefficients of the differential equation.

Substituting  $v_{c,h} = Ae^{st}$  into Eq. (2) :

$$As^2 e^{st} + \frac{R}{L} Ase^{st} + \frac{A}{LC} e^{st} = 0 \quad \text{or}$$

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 \quad (3) \quad \text{usually called the } \textit{characteristic equation}$$



# Series RLC Circuit – Solving the SODE

Two solutions obtained for the *characteristic equation* :

$$s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Replace  $s$  by  $s_1$ , and  $s_2$  :

$$v_{C,h1} = A_1 e^{s_1 t} \quad v_{C,h2} = A_2 e^{s_2 t}$$

Both  $v_{C,h1}$ , and  $v_{C,h2}$  satisfy the Eq. (2),

so we have  $v_{C,h} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$  (4)

The two constants  $A_1$  and  $A_2$  can be obtained by two initial conditions :


$$v_{C,h}(0) = V_0 \text{ and } \frac{dv_{C,h}(0)}{dt} = \frac{1}{C} i(0) = \frac{I_0}{C}$$

$$\text{From } v_{C,h} = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (4)$$

$$\text{with } v_{C,h}(0) = V_0 ,$$

$$\text{and by } \frac{dv_{C,h}(0)}{dt} = \frac{1}{C} i(0) = \frac{I_0}{C}, \quad \begin{cases} A_1 + A_2 = V_0 \\ A_1 s_1 + A_2 s_2 = \frac{I_0}{C} \end{cases}$$
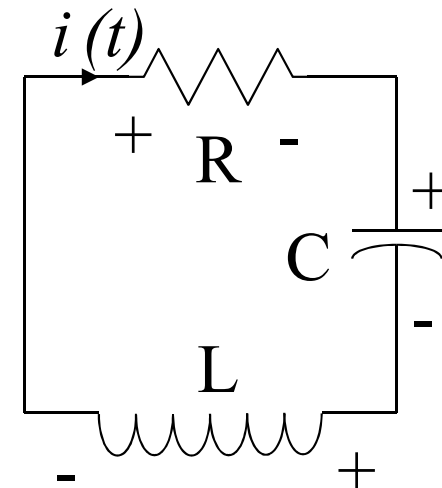
$$A_1 = \frac{V_0 s_2 - \frac{I_0}{C}}{s_2 - s_1} \quad A_2 = \frac{\frac{I_0}{C} - V_0 s_1}{s_2 - s_1}$$



# Series RLC Circuit – SODE of $i_L(t)$

By using KVL  $v_R + v_C + v_L = 0$ ,

instead of  $i(t) = C \frac{dv_c(t)}{dt}$


we use  $v_C(t) = \frac{q(t)}{C} = \frac{1}{C} \int_{-\infty}^t i(t) dt$

we can have:


$$iR + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i dt = 0$$

$\Downarrow$
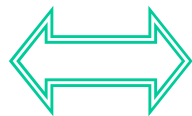
$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$


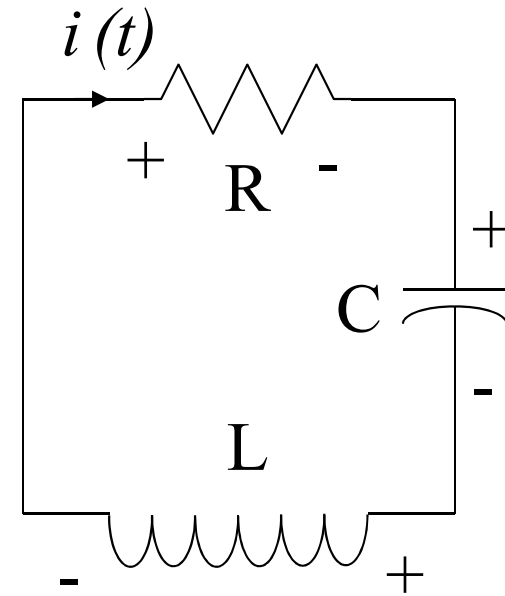
$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = 0 \quad (1)$$



# Series RLC Circuit – Damping factor

$$s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Definition of  $\alpha$  and  $\omega_0$  :

$$\alpha = \frac{R}{2L}, \quad \text{called damping factor}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ (rad / sec) : Called the undamped natural frequency,}$$

or the resonant frequency

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

# Series RLC Circuit – Damping factor

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

The value of the term  $\sqrt{\alpha^2 - \omega_0^2}$  determines the behavior of the response :

1. Over Damped System :  $\alpha > \omega_0$ ,  $s_1$  and  $s_2$  are two unequal real numbers
2. Critically Damped System:  $\alpha = \omega_0$ ,  $s_1$  and  $s_2$  are two equal real numbers
3. Under Damped System:  $\alpha < \omega_0$ ,  $s_1$  and  $s_2$  are complex numbers:

$$s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2}, \quad s_2 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2}$$

System exhibits oscillatory behavior

Special case :  $R = 0 \Rightarrow \alpha = 0$

$$s_1 = j\omega_0, \quad s_2 = -j\omega_0$$



# Series RLC Circuit – Over damped

## 1. Over Damped System :

$$\alpha > \omega_0, \text{ implies } C > 4L/R^2$$


$s_1$  and  $s_2$  are two unequal real numbers

The response is :

$$v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$v_C(t)$  decays and approaches zero as time increases.
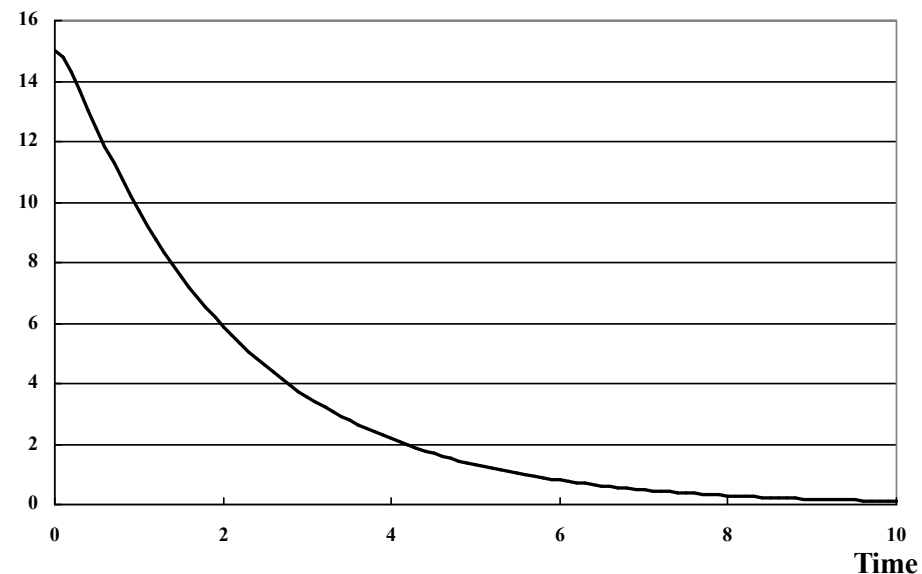
$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$



# Series RLC Circuit – Critical damped

When  $\alpha = \omega_0$ ,  $R = 2\sqrt{\frac{L}{C}}$ ,  $\Rightarrow C = 4L/R^2$  and  $s_1 = s_2 = -\alpha = -\frac{R}{2L}$ , the differential equation

$$\frac{d^2 v_{C,h}}{dt^2} + \frac{R}{L} \frac{dv_{C,h}}{dt} + \frac{1}{LC} v_{C,h} = 0 \quad (2) \text{ becomes: } \frac{d^2 v_{C,h}}{dt^2} + 2\alpha \frac{dv_{C,h}}{dt} + \alpha^2 v_{C,h} = 0 \quad (2a)$$

Then we have 
$$\frac{d}{dt} \left( \frac{dv_{C,h}}{dt} + \alpha v_{C,h} \right) + \alpha \left( \frac{dv_{C,h}}{dt} + \alpha v_{C,h} \right) = 0 \quad (3)$$

Let  $f = \frac{dv_{C,h}}{dt} + \alpha v_{C,h}$  (4), the equation (3) becomes:  $\frac{df}{dt} + \alpha f = 0$  (5)

For the first - order equation (5), we have  $f = A_1 e^{-\alpha t}$

$$\begin{aligned} \text{Then: } \frac{dv_{C,h}}{dt} + \alpha v_{C,h} &= A_1 e^{-\alpha t} \Rightarrow e^{\alpha t} \frac{dv_{C,h}}{dt} + e^{\alpha t} \alpha v_{C,h} = A_1 \\ &\Rightarrow \frac{d(e^{\alpha t} v_{C,h})}{dt} = A_1 \Rightarrow e^{\alpha t} v_{C,h} = A_1 t + A_2 \end{aligned}$$

The solution finally is :

$$v_{C,h}(t) = e^{-\alpha t} (A_1 t + A_2)$$



# Series RLC Circuit – Under damped

When  $\alpha < \omega_0$ ,  $C < 4L / R^2$ , we define

$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$  called *natural resonant frequency*

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$s_1 = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha + j\omega_d$$

$$s_2 = -\alpha - \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha - j\omega_d$$


The solution may be:

$$\begin{aligned} v_{C,h}(t) &= A_1 e^{-(\alpha - j\omega_d)t} + A_2 e^{-(\alpha + j\omega_d)t} \\ &= e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t}) \end{aligned}$$

The final form is:

$$v_{C,h}(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

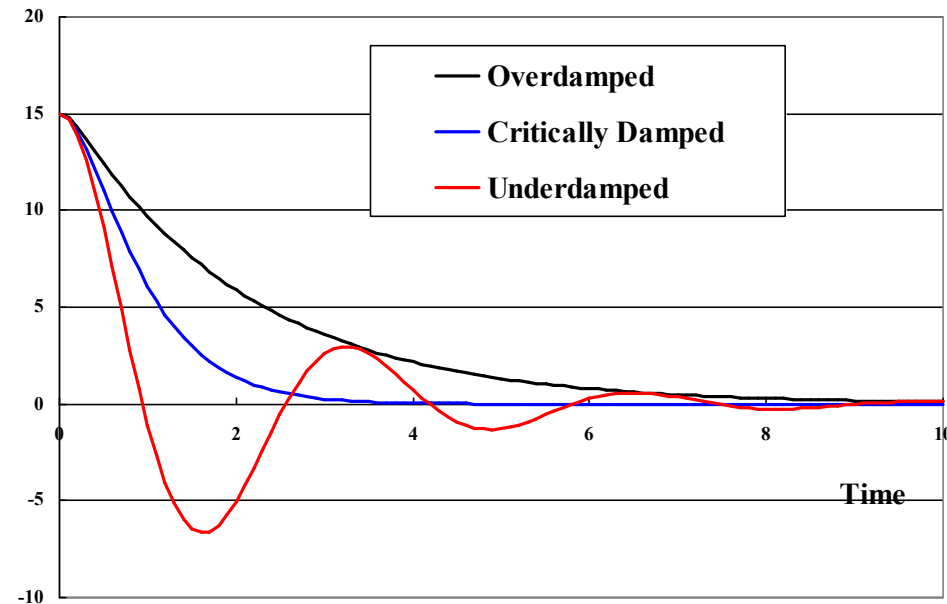The constants of  $B_1$  and  $B_2$  are also determined by initial conditions





# Series RLC Circuit – Example

The circuit below has  $C = 0.25 \mu\text{F}$  and  $L = 1 \text{ H}$ .

The switch has been open for a long time and is closed at  $t = 0$ .

Find the capacitor voltage for  $t \geq 0$  for


1.  $R = 8.5 \text{ k}\Omega$

2.  $R = 4 \text{ k}\Omega$  and

3.  $R = 1 \text{ k}\Omega$ .

The initial conditions are

$I_0 = 0$  and  $V_0 = 15 \text{ V}$ .

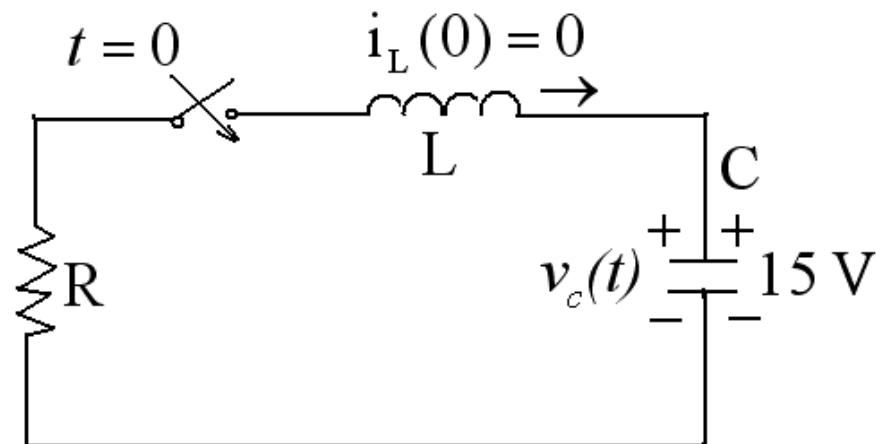


# Series RLC Circuit – Step of solving 2<sup>nd</sup> problems

- 0. Get the SODE of the circuit;
- 1. Find out the initial conditions  $i_L(0^+)$ ,  $v_C(0^+)$ ,  $v_L(0^+)$ ,  $i_C(0^+)$ ;
- 2. Get the characteristic equation from SODE (SODE  $\rightarrow s$ );
- 3. Evaluate  $\alpha$  and  $\omega_0$ ;
  - Compare  $\alpha^2 - \omega_0^2$  with 0, determine the damping case, which determines the general form of the solution.
- 4. Solve for  $s_1$  and  $s_2$ , substitute into the general form of the solution;
- 5. using initial conditions to solve for coefficients  $A_1$ ,  $A_2$  or  $B_1$ ,  $B_2$ ;
- 6. Get final expression of  $v_C(t)$  or  $i_L(t)$ .



# Series RLC Circuit – Example solution

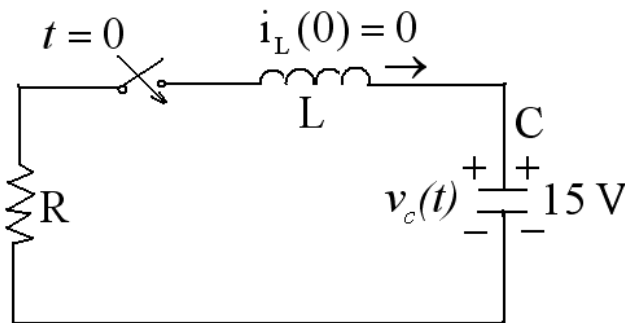

$$C = 0.25 \mu F, L = 1 H$$

$$1. R = 8.5 \text{ k}\Omega$$

The characteristic equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad (3)$$

$$s^2 + \frac{8.5 \times 10^3}{1}s + \frac{1}{1 \times 0.25 \times 10^{-6}} = 0$$

$$0.25 \times 10^{-6} s^2 + 2.125 \times 10^{-3} s + 1 = 0$$

$$s_1 = -500, \quad s_2 = -8000$$

$s_1$  and  $s_2$  are two unequal real numbers

$$v_{C,h}(t) = A_1 e^{-500t} + A_2 e^{-8000t} \quad t \geq 0$$

By initial conditions :

$$v_{C,h}(0) = 15 \text{ V and } i_L(0) = 0$$

$$\begin{cases} 15 = A_1 + A_2 \\ \frac{dv_C(0)}{dt} = \frac{i_L(0)}{C} = 0 \end{cases} \quad \left\{ \begin{array}{l} A_1 + A_2 = 15 \\ -500A_1 - 8000A_2 = 0 \end{array} \right.$$

$A_1 = 16$  and  $A_2 = -1$ , so we have

$$v_{C,h}(t) = 16e^{-500t} - e^{-8000t} \text{ V} \quad t \geq 0$$

$s_1$  and  $s_2$  are two unequal real numbers

-- Over Damped System



# Series RLC Circuit – Example solution (cont.)

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad (3)$$

$$s^2 + \frac{4 \times 10^3}{1}s + \frac{1}{1 \times 0.25 \times 10^{-6}} = 0$$

$$0.25 \times 10^{-6} s^2 + 10^{-3} s + 1 = 0$$

$$s_1 = s_2 = -2000$$

$$v_{c,h}(t) = A_1 e^{-2000t} + A_2 t e^{-2000t} \quad t \geq 0$$

By initial conditions :  $v_{c,h}(0) = 15 \text{ V}$  and  $i_L(0) = 0$

$$15 = A_1$$

$$\frac{dv_c(0)}{dt} = \frac{i_L(0)}{C} = 0 \quad \left\{ \begin{array}{l} A_1 = 15 \\ -2000A_1 - A_2 = 0 \end{array} \right.$$


$A_1 = 15$  and  $A_2 = 15 \times 2000$ , so we have

$$\underline{v_{c,h}(t) = 15e^{-2000t} + 15(2000t)e^{-2000t} \text{ V} \quad t \geq 0}$$

$s_1$  and  $s_2$  are two equal real numbers -- Critically Damped System

$$C = 0.25 \mu\text{F}, L = 1\text{H}$$

$$2. R = 4 \text{ k}\Omega$$

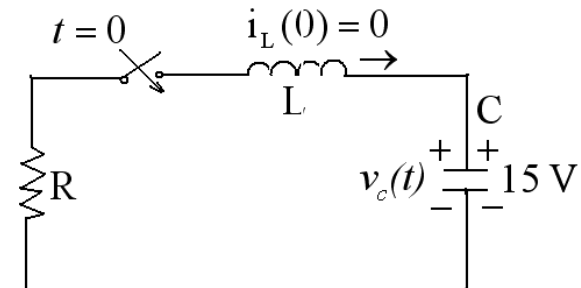

# Series RLC Circuit – Example solution (cont.)

The characteristic equation

$$s^2 + \frac{1 \times 10^3}{1}s + \frac{1}{1 \times 0.25 \times 10^{-6}} = 0$$

$$0.25 \times 10^{-6} s^2 + 0.25 \times 10^{-3} s + 1 = 0$$

$$s_1 = -500 + j500\sqrt{15}, \quad s_2 = -500 - j500\sqrt{15}$$

$$v_{C,h}(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) \quad t \geq 0$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{\left(\frac{1}{\sqrt{LC}}\right)^2 - \left(\frac{R}{2L}\right)^2} = 500\sqrt{15}$$

By initial conditions:

$$v_{C,h}(0) = 15 \text{ V and } i_L(0) = 0$$

$$15 = B_1 \quad \left\{ \begin{array}{l} B_1 = 15 \\ -500B_1 + 500\sqrt{15}B_2 = 0 \end{array} \right. \Rightarrow B_2 = \sqrt{15}$$


$$\frac{dv_{C,h}(0)}{dt} = \frac{i_L(0)}{C} = 0$$

so we have  $v_{C,h}(t) = e^{-500t} (15 \cos 500\sqrt{15}t + \sqrt{15} \sin 500\sqrt{15}t) \text{ V}$   $t \geq 0$


$s_1$  and  $s_2$  are complex numbers -- Under Damped System

$$C = 0.25 \mu\text{F}, L = 1 \text{ H}$$

$$3. R = 1 \text{ k}\Omega$$

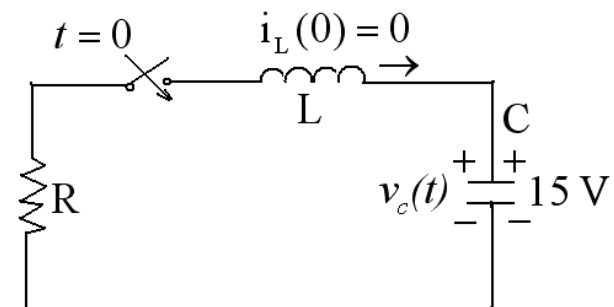
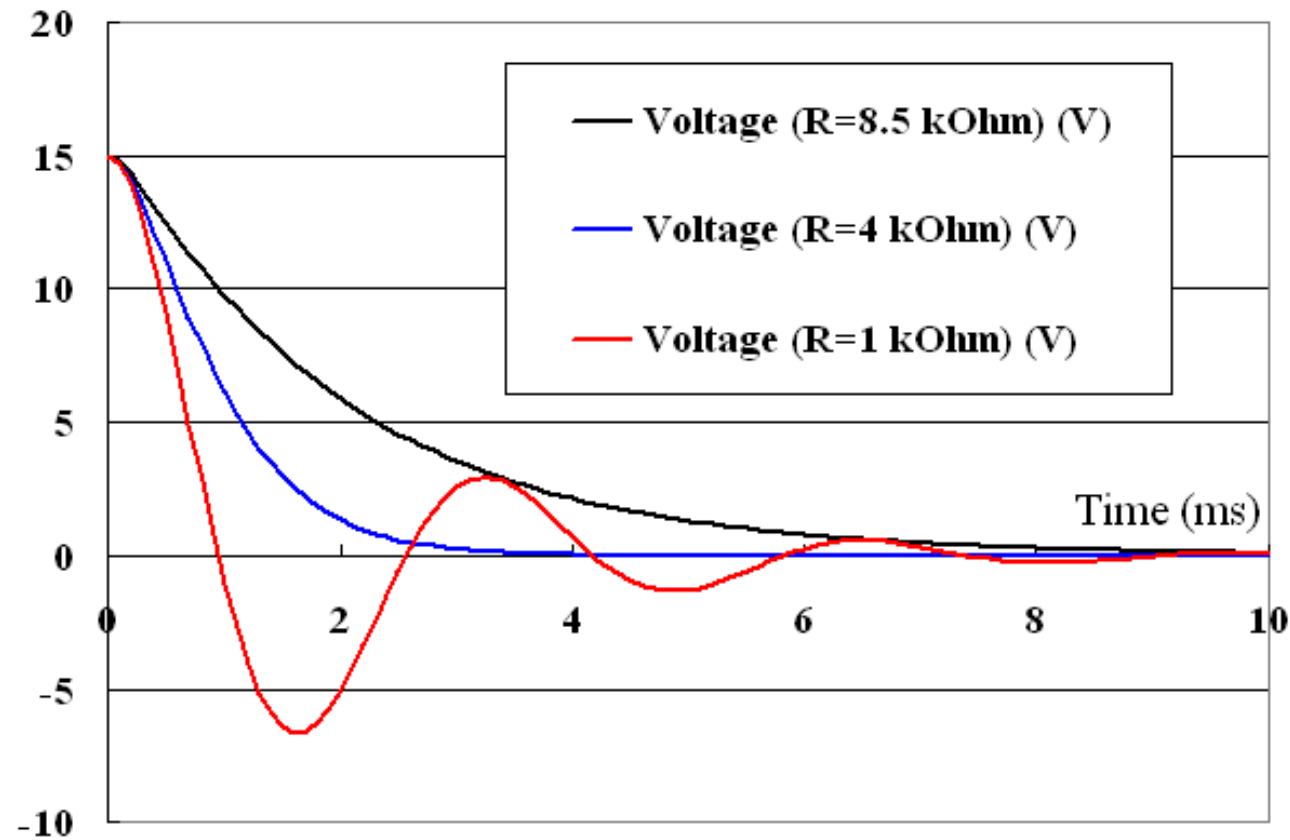
# Series RLC Circuit – *Example solution (cont.)*



# Series RLC Circuit – Example solution (cont.)

$$C = 0.25\mu\text{F}, L = 1\text{H}$$

$$R=0$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad (3) \rightarrow s^2 + \frac{1}{LC} = 0 \quad (3a)$$


$$s_{1,2} = \pm \sqrt{-\frac{1}{LC}} = \pm j\omega_0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 0.25 \times 10^{-6}}} = 20$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{\left(\frac{1}{\sqrt{LC}}\right)^2 - \left(\frac{R}{2L}\right)^2} = \omega_0$$

$$v_{C,h}(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) \quad t \geq 0$$
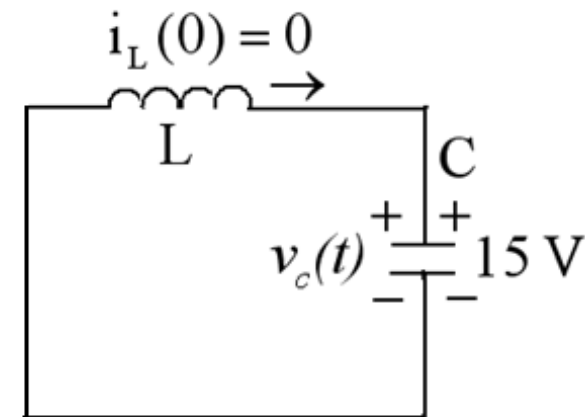
$$\rightarrow v_{C,h}(t) = B_1 \cos \omega_0 t + B_2 \sin \omega_0 t \quad t \geq 0$$



$$\omega_d = \omega_0$$



# Series RLC Circuit – Example solution (cont.)

By initial conditions :  $v_{C,h}(0) = 15 \text{ V}$  and  $i_L(0) = 0$

$$C = 0.25 \mu\text{F}, L = 1\text{H}$$

$$15 = B_1 \quad B_1 = 15$$

$$R=0$$


$$\frac{dv_{C,h}(0)}{dt} = \frac{i_L(0)}{C} = 0 \quad B_2 = 0$$

so we have

$$v_{C,h}(t) = 15 \cos 20t \text{ V} \quad t \geq 0$$
$$= V_0 \cos \omega_0 t \text{ V}$$

$$i_{L,h} = C \frac{dv_{C,h}}{dt} = -V_0 C \omega_0 \sin(\omega_0 t) \text{ A} \quad t \geq 0$$


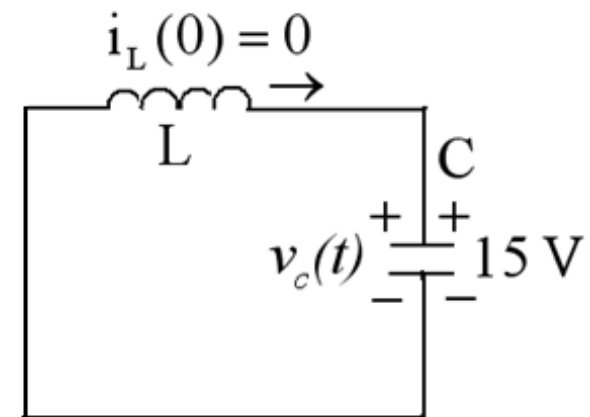
$$v_{L,h} = L \frac{di_{L,h}}{dt} = -V_0 \cos \omega_0 t \text{ V} \quad t \geq 0$$










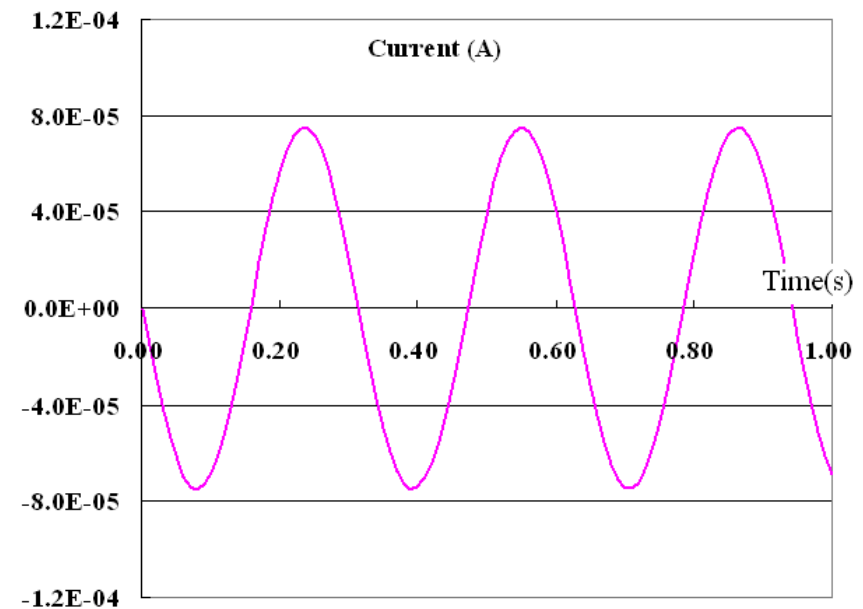
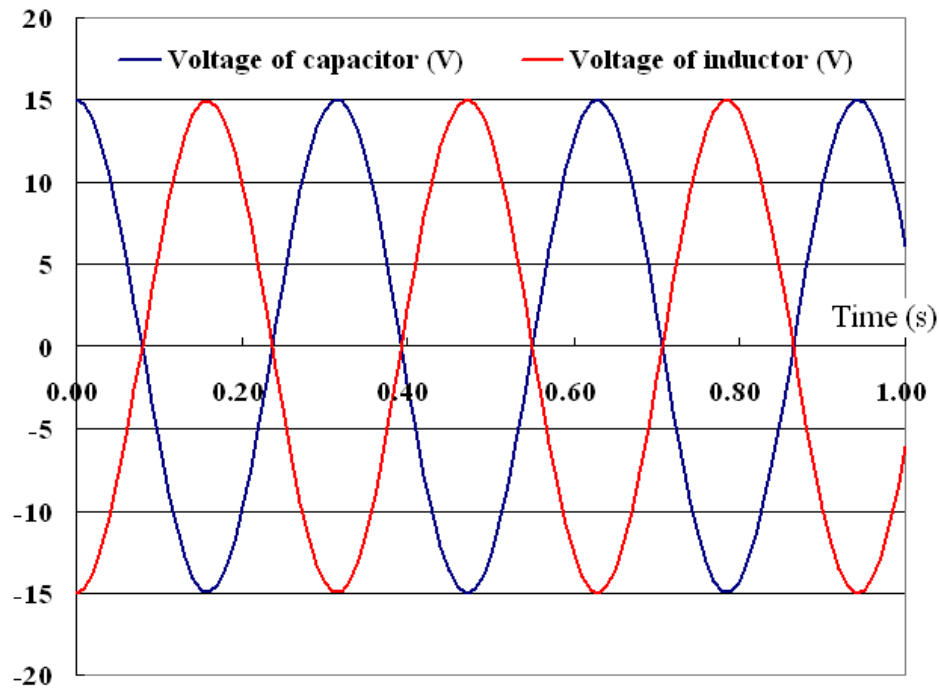
# Series RLC Circuit – Example solution (cont.)

$$C = 0.25\mu\text{F} \quad L = 1\text{H} \quad R = 0$$
$$I_0 = 0 \quad V_0 = 15\text{V}$$


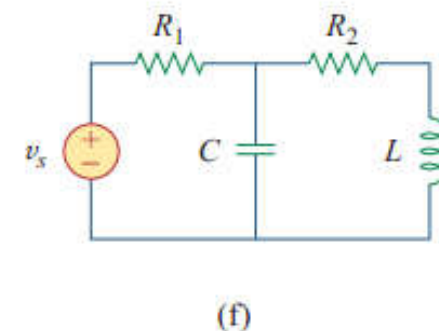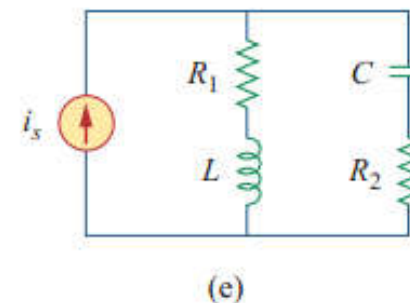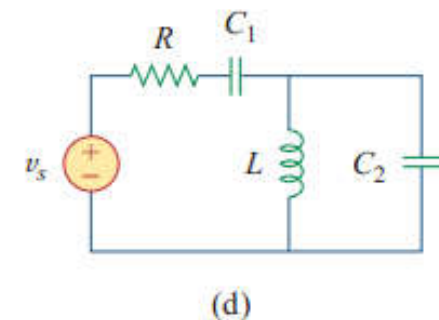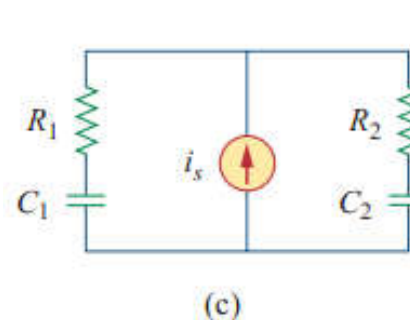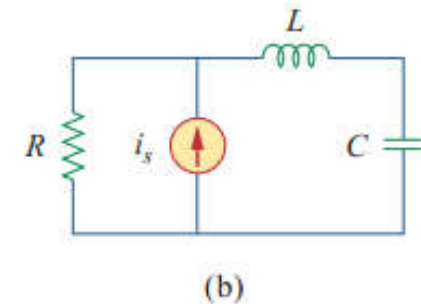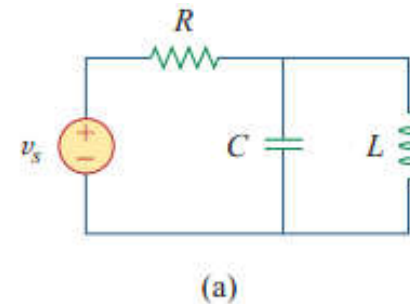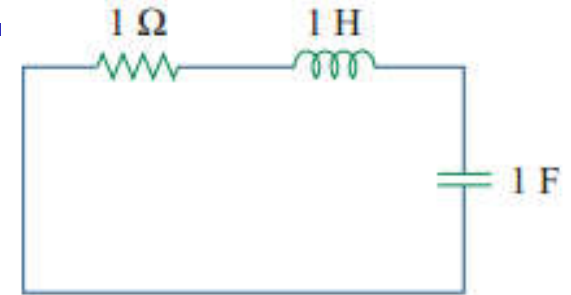
# Quiz

- Refer to the series RLC circuit, what kind of response will it produce?
  - (a) over damped;
  - (b) under damped;
  - (c) critically damped;
  - (d) none of the above.
- Match the circuits shown on the right with the following items:
  - (i) first-order circuit
  - (ii) second-order series circuit
  - (iii) second-order parallel circuit
  - (iv) none of the above



# Second Order Circuit – Source free summary

	Series	Parallel
$\alpha$	$\alpha = \frac{R}{2L}$	$\alpha = \frac{1}{2RC}$
$\omega_0$	$\frac{1}{\sqrt{LC}}$	$\frac{1}{\sqrt{LC}}$
Over Damped	$\alpha > \omega_0$ Response: $A_1 e^{s_1 t} + A_2 e^{s_2 t}$	
Critically Damped	$\alpha = \omega_0$ Response: $e^{-\alpha t} (A_1 t + A_2)$	
Under Damped	$\alpha < \omega_0$ Response: $e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$	
Undamped	$R=0$	$R \rightarrow \infty$
	Response: $B_1 \cos \omega_0 t + B_2 \sin \omega_0 t$	



# Complete response

- The complete response of a second order system consists of a forced response  $x_f(t)$  and a natural response  $x_n(t)$  which is the same form as source-free natural response.)
- If the input is not zero, we need to find the complete solution  $x(t)$

$$x(t) = x_f(t) + x_n(t)$$

↙                      ↘  
Forced                      natural

- Remember the output follows the form of the input

input function	Constant	Exponential	Sinusoid
particular solution	$A$	$Ae^{-\alpha t} + Bte^{-\alpha t}$	$A \cos(\omega t) + B \sin(\omega t)$

Step-function → Step-response



# Step response

---

- Now consider those RLC circuits in which dc sources are switched into the network and produce forced responses that do not necessarily vanish as time becomes infinite. – *Step response*.
- The basic steps are (not necessarily in this order) as follows:
  - 1. Determine the initial conditions.
  - 2. Obtain a numerical value for the forced response.
  - 3. Write the appropriate form of the natural response with the necessary number of arbitrary constants.
  - 4. Add the forced response and natural response to form the complete response.
  - 5. Evaluate the response and its derivative at  $t = 0$ , and employ the initial conditions to solve for the values of the unknown constants.

# Step response – parallel RLC circuit

By applying KCL at the indicated node :

$$i_s(t) = i_R(t) + i_L(t) + i_C(t)$$



The voltage across the inductor :  $v = L \frac{di_L}{dt}$

The currents  $i_R(t)$  and  $i_C(t)$  :

$$i_R(t) = \frac{v}{R} = \frac{L}{R} \frac{di_L}{dt}, \quad i_C(t) = C \frac{dv}{dt} = LC \frac{d^2 i_L}{dt^2}$$

Then we can have :
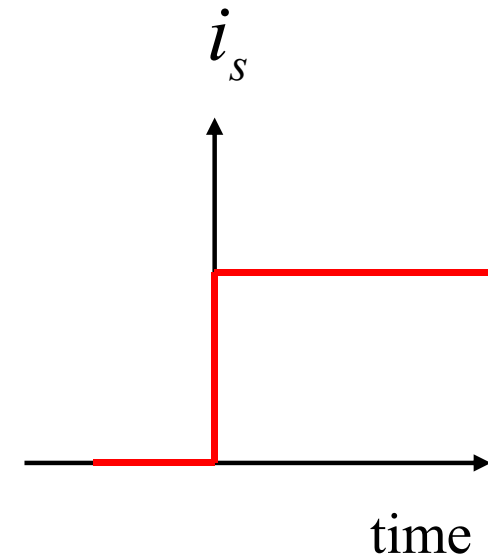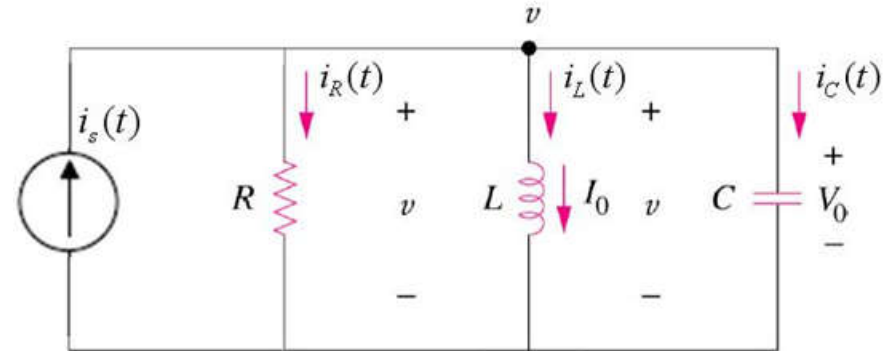
$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L = \frac{1}{LC} i_s \quad (1)$$



# Step response – parallel RLC circuit


$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L = \frac{1}{LC} i_s \quad (1)$$

The solution is :

$$i_L(t) = i_{L,f}(t) + i_{L,n}(t)$$

The natural response is the same as the source free case, the forced response of the current should be the value at  $t = \infty$ , in this case,  $i_s$

$i_L(t) = i_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}$	→	Over damped
$i_L(t) = i_s + (A_1 + A_2 t) e^{-\alpha t}$	→	Critical damped
$i_L(t) = i_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t}$	→	Under damped

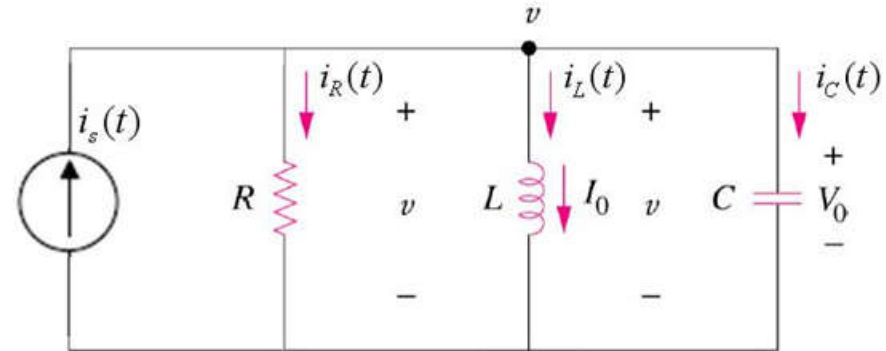



# Step response – Example 1 (parallel RLC circuit )

In a parallel  $RLC$  circuit  $R = 500\Omega$ ,  $C = 1\mu\text{F}$ ,  $L = 0.2\text{H}$

The initial conditions are  $i_L(0) = 50\text{ mA}$  and  $v(0) = 0$

Input current  $i_s = 100\text{ mA}$

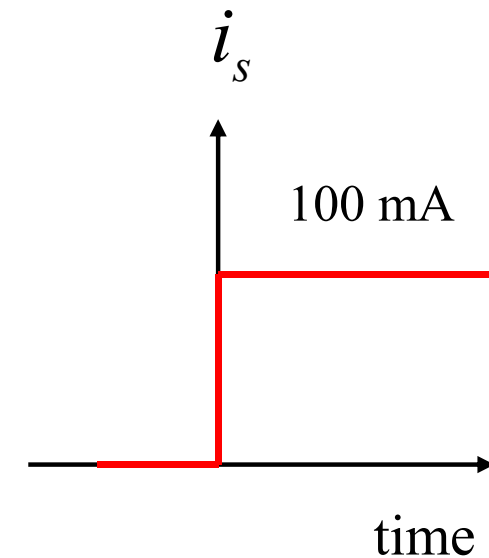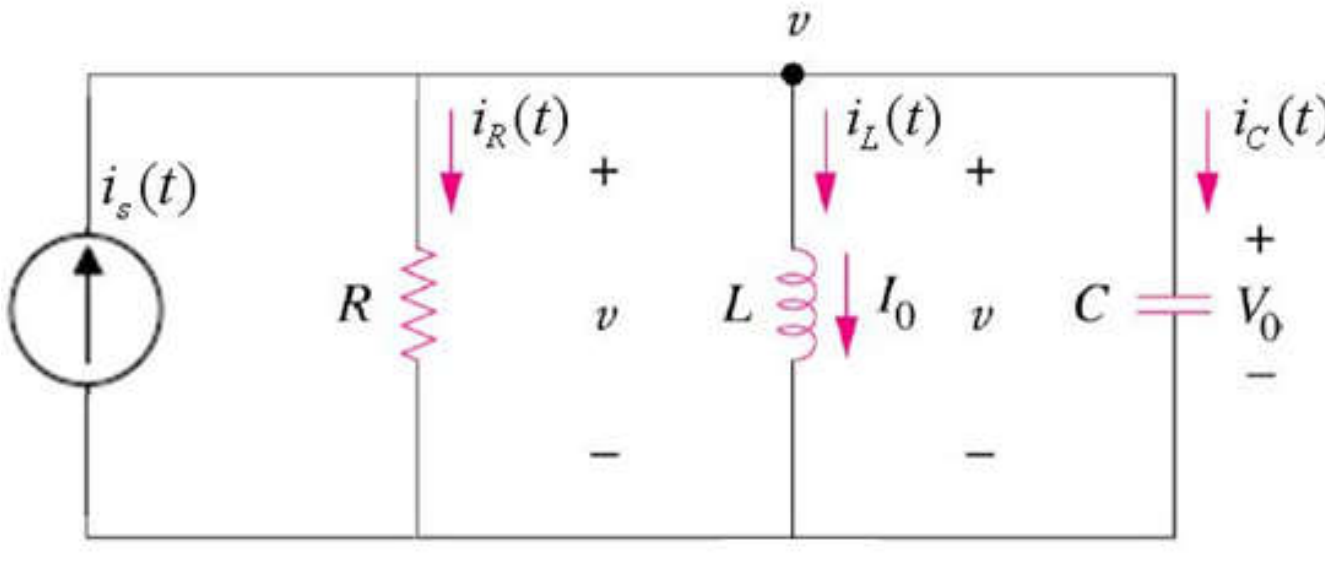Find the response of  $i_L(t)$ ,  $i_R(t)$  and  $v_C(t)$






# Recall – parallel RLC circuit (source free) – Example 1

Lect.3, p25

In a parallel RLC circuit:  $R = 500 \Omega$ ,  $C = 1 \mu\text{F}$ ,  $L = 0.2\text{H}$ .

The initial conditions are  $i_L(0) = 50\text{mA}$  and  $v(0)=0$ .

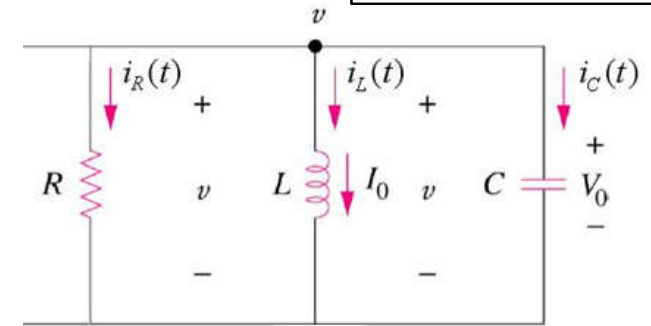Find the zero-input response of  $i_L(t)$ ,  $i_R(t)$  and  $v_c(t)$ .



## Solution

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 500 \times 1 \times 10^{-6}} = 10^3, \quad \omega_0^2 = \frac{1}{LC} = \frac{1}{0.2 \times 1 \times 10^{-6}} = 5 \times 10^6$$

$$\alpha^2 < \omega_0^2, \text{ underdamped}$$

From the characteristic equation:  $s^2 + 2\alpha s + \omega_0^2 = 0$ , we have

$$s^2 + 2 \times 10^3 s + 5 \times 10^6 = 0$$

$$s_1 = -1000 + j2000, \quad s_2 = -1000 - j2000$$

The response of  $i_L(t)$ :  $i_L(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{5 \times 10^6 - 10^6} = 2000$$

$$i_L(0) = 1 \times (B_1 \cos 0 + B_2 \sin 0) = 50 \times 10^{-3} \text{ A} \Rightarrow B_1 = 50 \times 10^{-3}$$

} ?



# Step response – Example 1 solution

The response of  $i_{L,n}(t)$ :  $i_{L,n}(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$

The complete response:  $i_L(t) = i_{L,f}(t) + i_{L,n}(t)$

$$i_L(t) = i_s + e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

Now let's determine the constants  $B_1$  and  $B_2$

$$i_L(0) = 50 \text{ mA} \quad i_s + B_1 = 50 \text{ mA} \Rightarrow \underline{B_1} = 50 \times 10^{-3} - 100 \times 10^{-3} = \underline{-50 \times 10^{-3}}$$

$$\frac{di_L(t)}{dt} = -\alpha e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) + e^{-\alpha t} (-B_1 \omega_d \sin \omega_d t + B_2 \omega_d \cos \omega_d t)$$

$$v(0) = L \left. \frac{di_L(t)}{dt} \right|_{t=0} = 0 \quad \Rightarrow \quad -\alpha B_1 + B_2 \omega_d = 0$$

$\Downarrow$

$$\underline{B_2} = \frac{\alpha}{\omega_d} B_1 = \frac{1000}{2000} (-50 \times 10^{-3}) = \underline{-25 \times 10^{-3}}$$



# Step response – Example 1 solution (cont.)

## Step Response

$$i_L(t) = 100 + e^{-1000t}(-50 \cos 2000t - 25 \sin 2000t) \text{ mA} \quad t \geq 0$$

$$v_L(t) = L \frac{di_L}{dt} = 25e^{-1000t} \sin 2000t \text{ V} \quad t \geq 0$$

$$v_C(t) = v_L(t) \quad t \geq 0$$

$$i_R = \frac{v_R(t)}{R} = \frac{v_L(t)}{R} = 50e^{-1000t} \sin 2000t \text{ mA} \quad t \geq 0$$

## Source Free

$$i_L(t) = e^{-1000t}(50 \cos 2000t + 25 \sin 2000t) \text{ mA} \quad t \geq 0$$

$$v_L(t) = L \frac{di_L}{dt} = -25e^{-1000t} \sin 2000t \text{ V} \quad t \geq 0$$



$$v_C(t) = v_L(t) \quad t \geq 0$$

$$i_R = \frac{v_R(t)}{R} = \frac{v_L(t)}{R} = -50e^{-1000t} \sin 2000t \text{ mA} \quad t \geq 0$$





# Step response – Example 1 solution (cont.)



Step Response

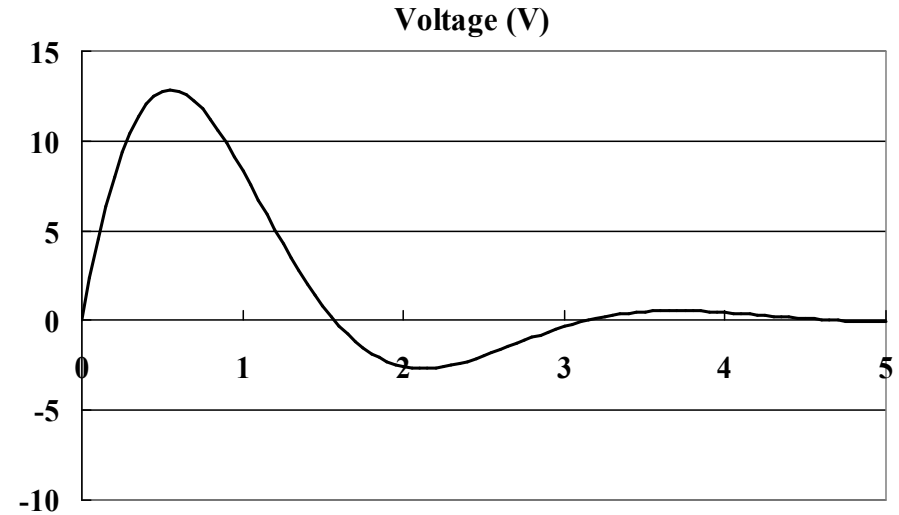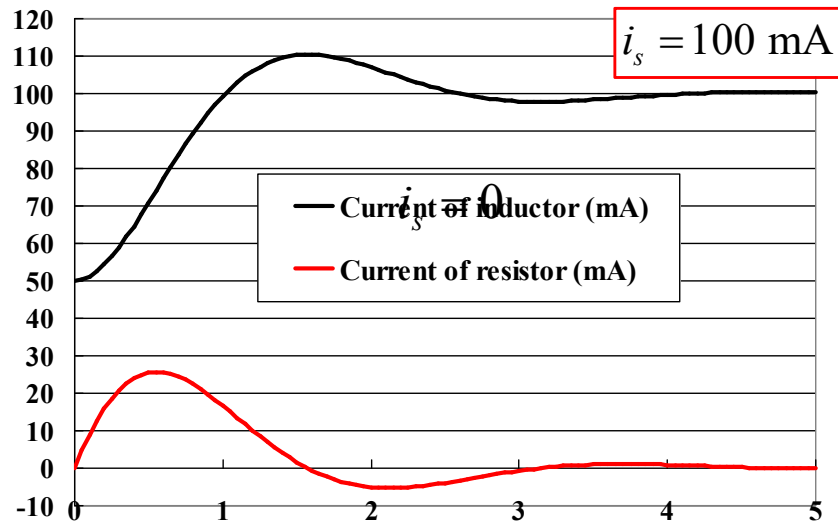

Source Free

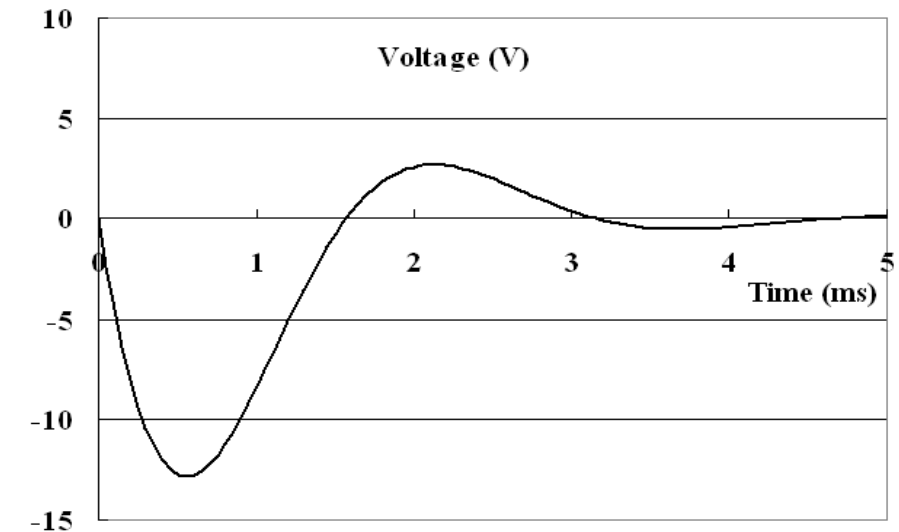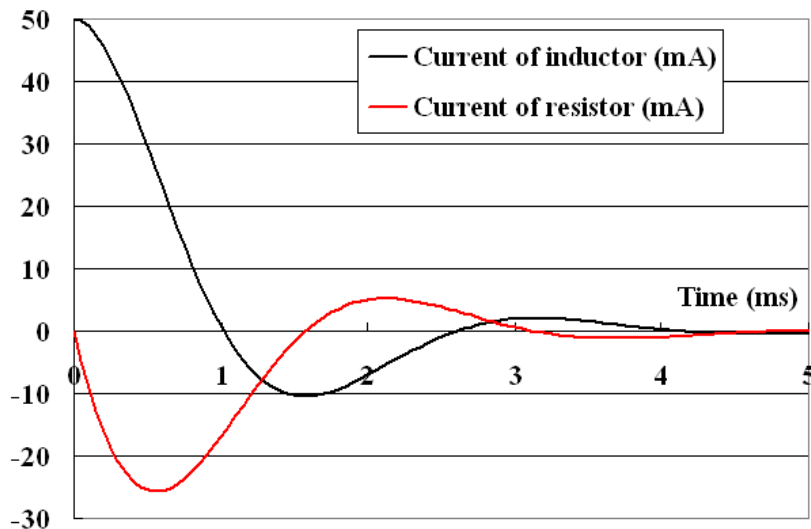

# Step response – series RLC circuit

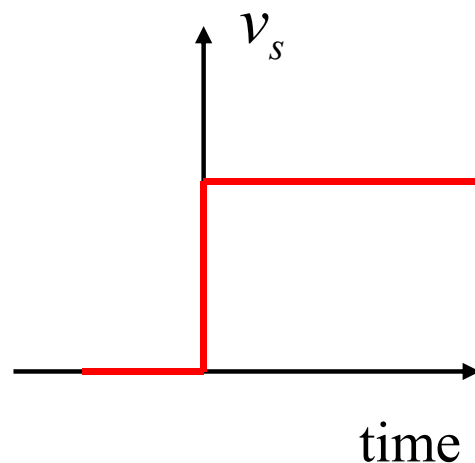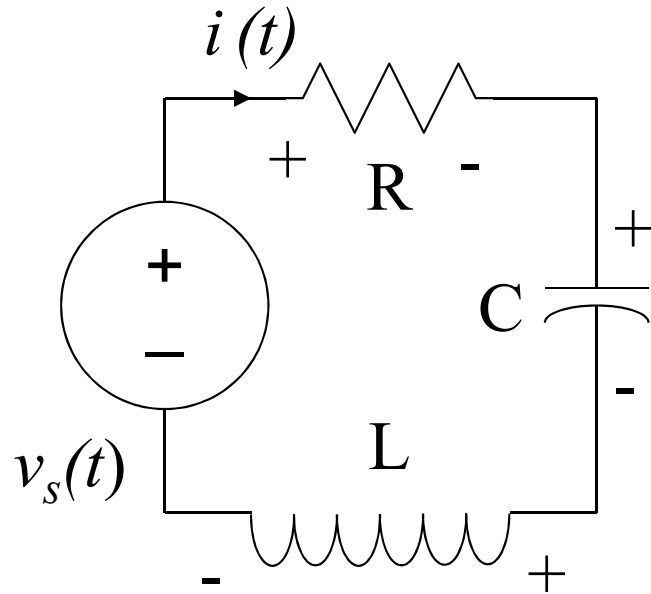

By using KVL:  $v_R + v_C + v_L = v_s$

The current flowing in the circuit :

$$i = C \frac{dv_C}{dt}$$

The voltage  $v_R$  and  $v_L$  are given by

$$v_R = iR = RC \frac{dv_C}{dt}$$

$$v_L = L \frac{di}{dt} = LC \frac{d^2v_C}{dt^2}$$

Then we have :


$$\frac{d^2v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{1}{LC} v_s \quad (1)$$

# Step response – series RLC circuit

$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{1}{LC} v_s \quad (1)$$

The solution is :

$$v_C(t) = v_{C,f}(t) + v_{C,n}(t)$$

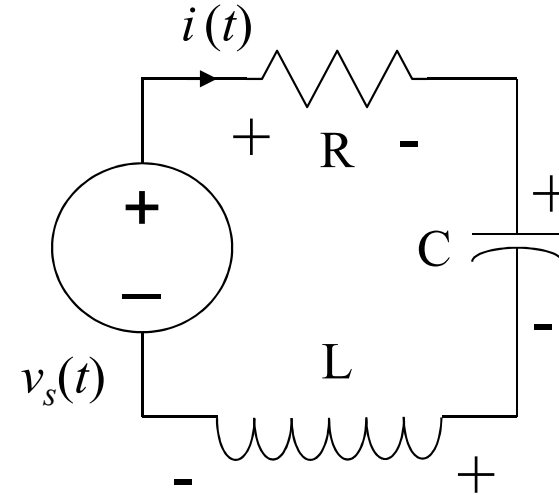

The natural response is the same as the source free case, the forced value of the voltage across the capacitor should be the voltage at  $t = \infty$ , in this circuit, the same as the source voltage  $v_s$

$$v_C(t) = v_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$v_C(t) = v_s + (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically damped})$$

$$v_C(t) = v_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$




# Step response – Example 2 (series RLC circuit )

For the circuit below, the switch is closed for a long time before it is opened. Find  $v(t)$  and  $i(t)$  for  $t > 0$ . Consider these cases:  $R = 5\Omega$ ,  $R = 4\Omega$ ,  $R = 1\Omega$
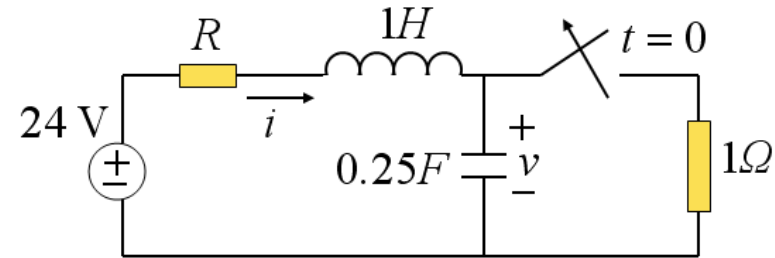
## Solution Case 1: $R = 5\Omega$

$$\begin{aligned}\text{When } t < 0: \quad i(0) &= \frac{24}{5+1} = 4 \text{ A} \\ v(0) &= 1 \times i(0) = 4 \text{ V}\end{aligned}$$



$$\begin{aligned}t > 0: \quad \alpha &= \frac{R}{2L} = \frac{5}{2 \times 1} = 2.5 \\ \omega_0 &= \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 0.25}} = 2\end{aligned}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -1, \quad -4 \Rightarrow \text{Overdamped response}$$

$$v(t) = 24 + A_1 e^{-t} + A_2 e^{-4t}$$

$$v(0) = 4 = 24 + A_1 + A_2 \Rightarrow -20 = A_1 + A_2$$

# Step response – Example 2 solution

The current through the inductor cannot change abruptly,  
and is the same current through the capacitor at  $t = 0_+$

$$i(0) = C \frac{dv(0)}{dt} = 4 \Rightarrow \frac{dv(0)}{dt} = \frac{4}{C} = 16$$

$$\frac{dv(t)}{dt} = -A_1 e^{-t} - 4A_2 e^{-4t} \quad \text{At } t = 0, \quad \frac{dv(0)}{dt} = 16 = -A_1 - 4A_2$$

$$A_1 = -64/3, \quad A_2 = 4/3$$

$$\begin{cases} A_1 + A_2 = -20 \\ -A_1 - 4A_2 = 16 \end{cases}$$


$$v(t) = 24 + \frac{4}{3}(-16e^{-t} + e^{-4t}) \quad \text{V}$$

As the inductor and the capacitor are in series when  $t > 0$ ,

The current through the inductor is the same as one through the capacitor :

$$i(t) = C \frac{dv}{dt} = 0.25 \times \frac{4}{3} (16e^{-t} - 4e^{-4t})$$
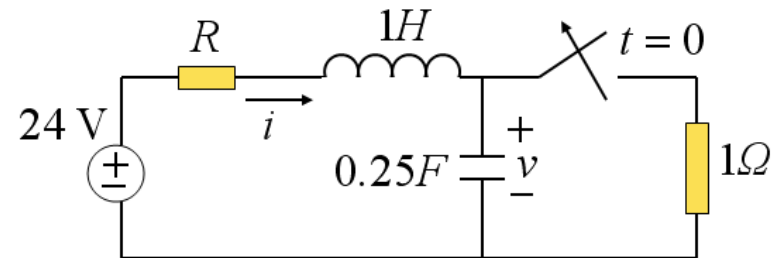
$$i(t) = \frac{4}{3} (4e^{-t} - e^{-4t}) \quad \text{A}$$





# Step response – Example 2 solution (cont.)

## Solution Case 2: $R = 4\Omega$

$$t < 0: \quad i_L(0) = 24/(4+1) = 4.8 \text{ A}, \quad v(0) = 1 \times i(0) = 4.8 \text{ V}$$

$$\alpha = R/2L = 4/(4 \times 1) = 2, \quad \omega_0 = 2 \Rightarrow s_1 = s_2 = -\alpha = -2$$

As  $s_1 = s_2$ , we have the critically damped response.

$$\text{And } v(t) = 24 + (A_1 + A_2 t)e^{-2t} \text{ V}$$

$$v(0) = 4.8 = 24 + A_1 \Rightarrow \underline{A_1 = -19.2}$$


$$\frac{dv(0)}{dt} = \frac{4.8}{C} = 19.2$$

$$\frac{dv(t)}{dt} = (-2A_1 - 2tA_2 + A_2)e^{-2t} \Rightarrow \frac{dv(0)}{dt} = -2A_1 + A_2 = 19.2 \Rightarrow \underline{A_2 = -19.2}$$

$$\text{Thus } \underline{v(t) = 24 - 19.2(1+t)e^{-2t}} \text{ V}$$

The current through the inductor is the same as one through the capacitor :
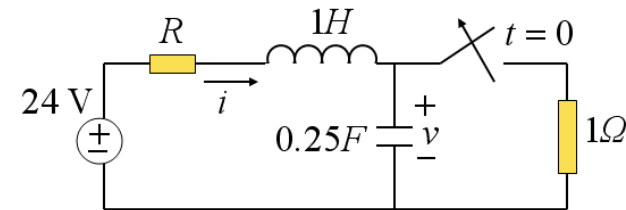
$$\underline{i(t) = C \frac{dv}{dt} = (4.8 + 9.6t)e^{-2t}} \text{ A}$$



## Step response – Example 2 solution (cont.)

$$t < 0: \quad i_L(0) = 24/(1+1) = 12 \text{ A}, \quad v(0) = 1 \times i(0) = 12 \text{ V}$$

$$\alpha = R/2L = 1/(2 \times 1) = 0.5, \quad \omega_0 = 2 \Rightarrow s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -0.5 \pm j1.936$$

$\alpha < \omega_0$  : the underdamped response

$$\text{then: } v(t) = 24 + (A_1 \cos 1.936t + A_2 \sin 1.936t)e^{-0.5t} \text{ V}$$

$$v(0) = 12 = 24 + A_1 \Rightarrow \underline{A_1 = -12} \quad \text{and} \quad \frac{dv(0)}{dt} = \frac{12}{C} = 48$$

$$\frac{dv(t)}{dt} = e^{-0.5t} (-1.936A_1 \sin 1.936t + 1.936A_2 \cos 1.936t) - 0.5e^{-0.5t} (A_1 \cos 1.936t + A_2 \sin 1.936t)$$

$$\frac{dv(0)}{dt} = (-0 + 1.936A_2) - 0.5(A_1 + 0) = 48 \Rightarrow \underline{A_2 = 21.694}$$



$$\text{Thus } \underline{v(t) = 24 + (21.694 \sin 1.936t - 12 \cos 1.936t)e^{-0.5t}} \text{ V}$$

The current through the inductor is the same as one through the capacitor :

$$\underline{i(t) = C \frac{dv}{dt} = (3.1 \sin 1.936t + 12 \cos 1.936t)e^{-0.5t} \text{ A}}$$


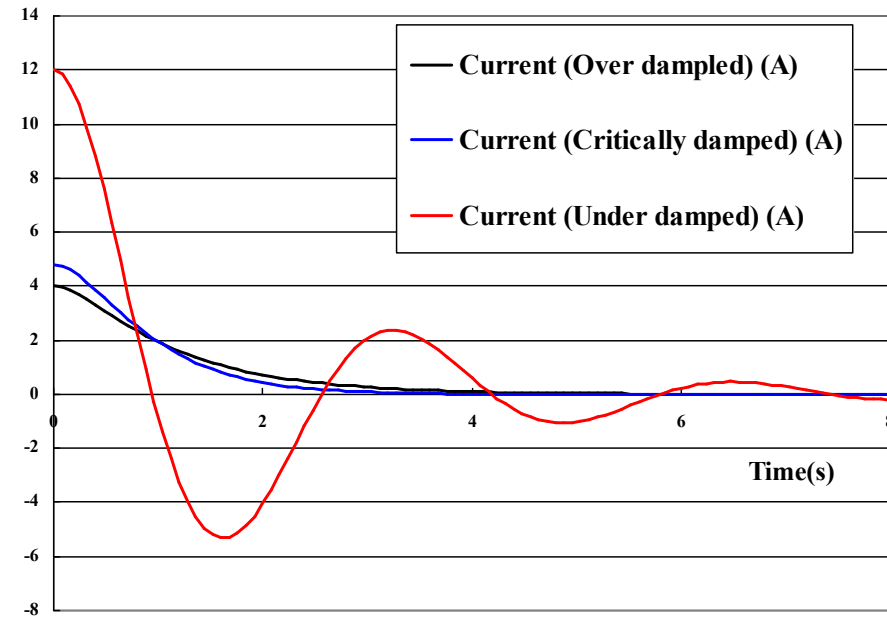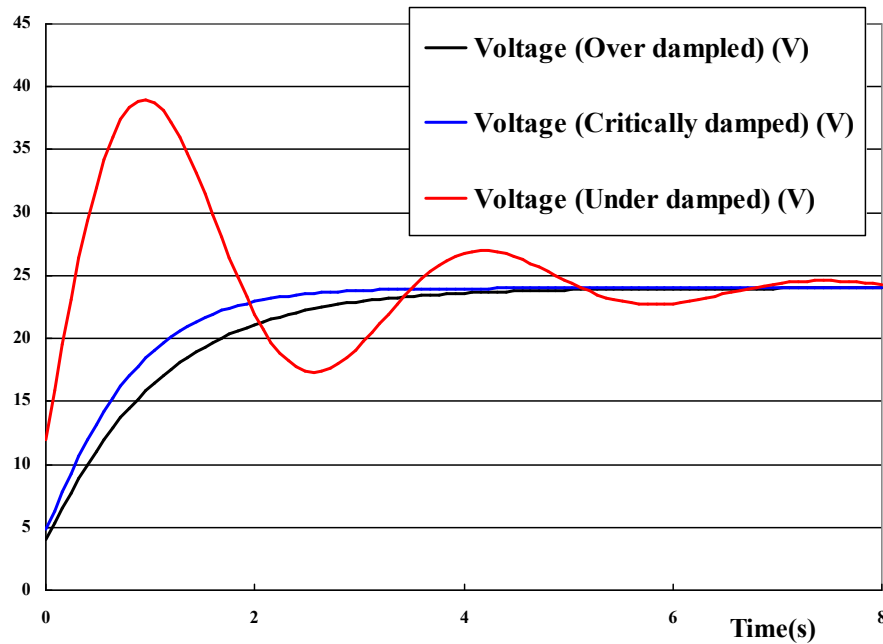
# Step response – Example 2 solution (cont.)



# Second Order Circuit – Step response summary


	Series	Parallel
$\alpha$	$\alpha = \frac{R}{2L}$	$\alpha = \frac{1}{2RC}$
$\omega_0$	$\frac{1}{\sqrt{LC}}$	$\frac{1}{\sqrt{LC}}$
Over Damped	$\alpha > \omega_0$ Response: $A_1 e^{s_1 t} + A_2 e^{s_2 t}$	
Critically Damped	$\alpha = \omega_0$ Response: $e^{-\alpha t} (A_1 t + A_2)$	
Under Damped	$\alpha < \omega_0$ Response: $e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$	
Undamped	$R=0$	$R \rightarrow \infty$
	Response: $B_1 \cos \omega_0 t + B_2 \sin \omega_0 t$	



# Quiz


- For the circuit in the figure on the right, the initial value of  $i(0^+)$  and  $di(0^+)/dt$  are:

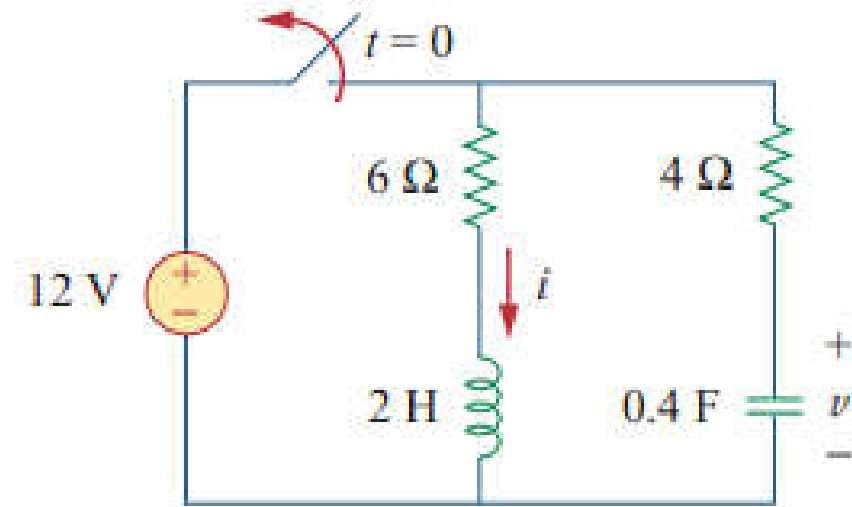- (a)  $i(0^+) = 2 \text{ A}$ ,  $di(0^+)/dt = -4 \text{ A/s}$ ;
- (b)  $i(0^+) = 2 \text{ A}$ ,  $di(0^+)/dt = 0 \text{ A/s}$ ;
- (c)  $i(0^+) = 1.2 \text{ A}$ ,  $di(0^+)/dt = 2 \text{ A/s}$ ;
- (d)  $i(0^+) = 1.2 \text{ A}$ ,  $di(0^+)/dt = 1.2 \text{ A/s}$ ;



- For the circuit in the figure on the right, determine its damping case:

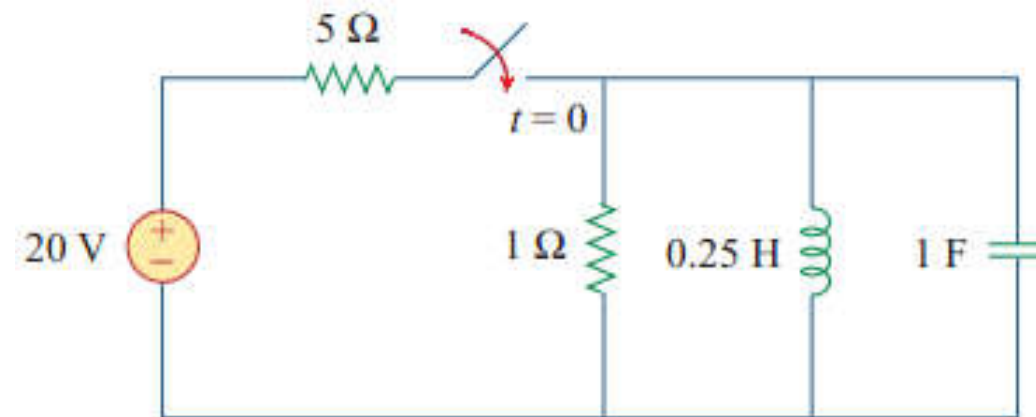- (a) over damped;
- (b) critical damped;
- (c) under damped;
- (d) un-damped.




# General Second Order Circuits

---

- The idea of parallel/series RLC circuits can be extended to any second order circuits.
- Find the step response of a 2<sup>nd</sup> order system takes five steps:
  - 1. First determine the initial conditions  $x(0)$  and  $dx(0)/dt$ , and the final value  $x(\infty)$ .
  - 2. Turn off the independent sources and find the form of the natural response  $x_n(t)$  by applying KCL and KVL.
  - 3. We obtain the forced response as  $x_f(t) = x(\infty)$
  - 4. The total response is now found as the sum of the natural response and forced response  $x(t) = x_n(t) + x_f(t)$
  - 5. We finally determine the constants associated with the natural response by imposing the initial conditions  $x(0)$  and  $dx(0)/dt$  determined in step 1.
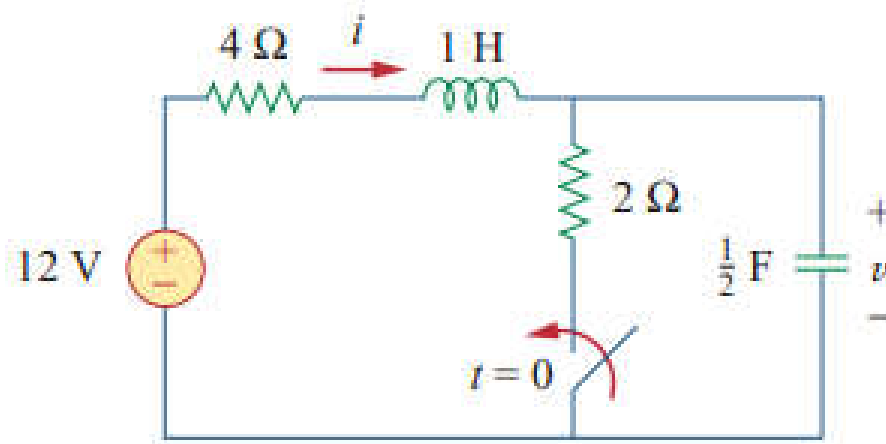
# General Second Order Circuits – Example 3


- Find the complete response  $v$  and then  $i$  for  $t > 0$  in the following circuit.



Ref.3, example 8.9
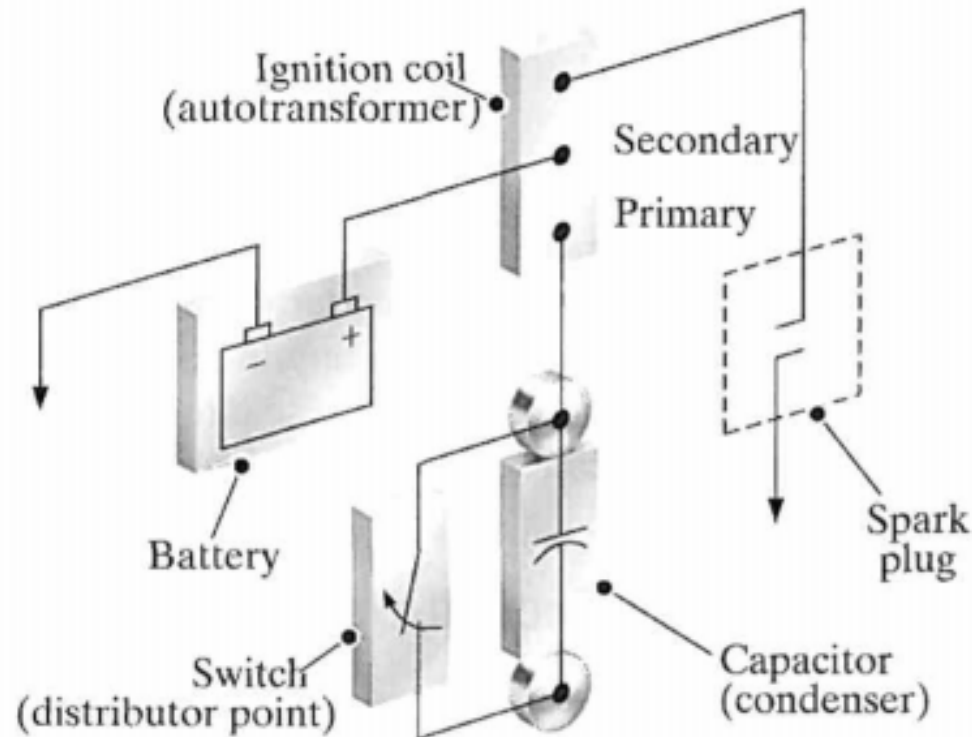
# Practical Application – Automobile Ignition Circuit


- An automobile ignition circuit is based on the transient response of an RLC circuit.
- In such a circuit, a switching operation causes a rapid change in the current in an inductive winding known as an *ignition coil* (also called the *spark coil*).





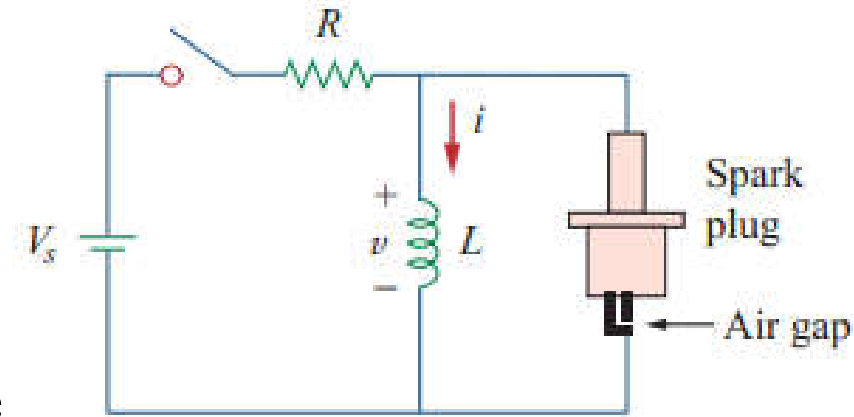
# Automobile Ignition Circuit – 1<sup>st</sup> order model

- In gasoline engine, the ignition of the fuel-air mixture in each cylinder is achieved by means of a spark plug.
  - By creating a large voltage (thousands of volts) between the electrodes, a spark is formed across the air gap, thereby igniting the fuel.
  - Question: how can such a large voltage be obtained from the car battery, which supplies only 12 V?
- This is achieved by means of an inductor (the spark coil)  $L$ .
  - Voltage across the inductor is  $v = L di/dt$
  - So rapidly changing current  $i(t)$  can generate large voltage  $v$ .
  - After the switching, the current increases and reaches the final value of  $i = V_s/R$ , where  $V_s = 12\text{V}$ .


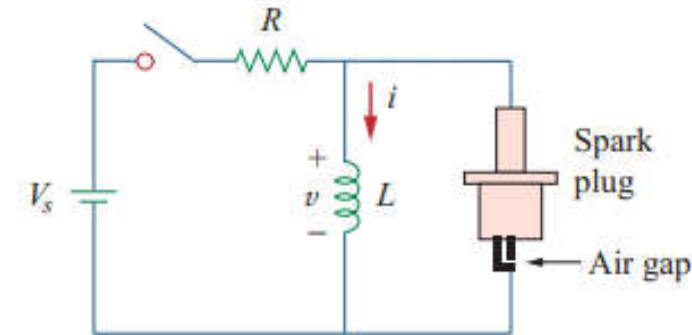
# Automobile Ignition Circuit – 1<sup>st</sup> order model

- A solenoid with resistance  $4\Omega$  and inductance  $6\text{ mH}$  is used in an auto-mobile ignition circuit.
- If the battery supplies  $12\text{ V}$ , determine:
  - the final current through the solenoid when the switch is closed;
  - the energy stored in the coil, and the voltage across the air gap assuming that the switch takes  $1\text{ }\mu\text{s}$  to open.




- Solution:
  - The final current through the coil is  $I = \frac{V_s}{R} = \frac{12}{4} = 3\text{ A}$
  - The energy stored in the coil is  $W = \frac{1}{2}LI^2 = \frac{1}{2} \times 6 \times 10^{-3} \times 3^2 = 27\text{ mJ}$
  - The voltage across the gap is

$$V = L \frac{\Delta I}{\Delta t} = 6 \times 10^{-3} \times \frac{3}{1 \times 10^{-6}} = 18\text{ kV}$$

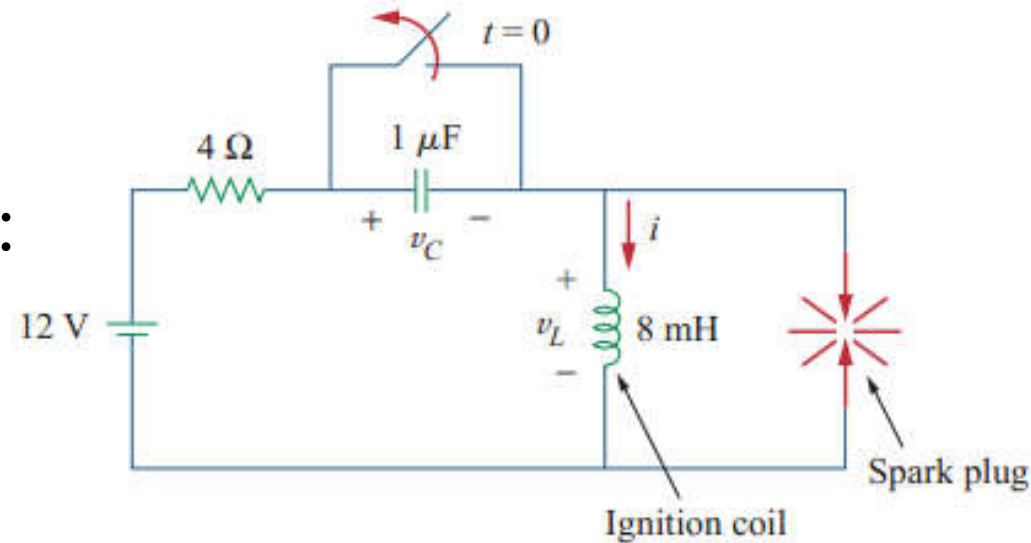
# Automobile Ignition Circuit – 2<sup>nd</sup> order model

- In 1<sup>st</sup> order model, we considered the automobile ignition system as a charging system.
- Here, we consider another part:  
the voltage generating system.
  - The 12-V source is due to the battery and alternator.
  - The resistor represents the resistance of the wiring.
  - The ignition coil is modelled by the 8-mH inductor.
  - The capacitor (known as the condenser to automechanics) is in parallel with the switch (known as the breaking points or electronic ignition).


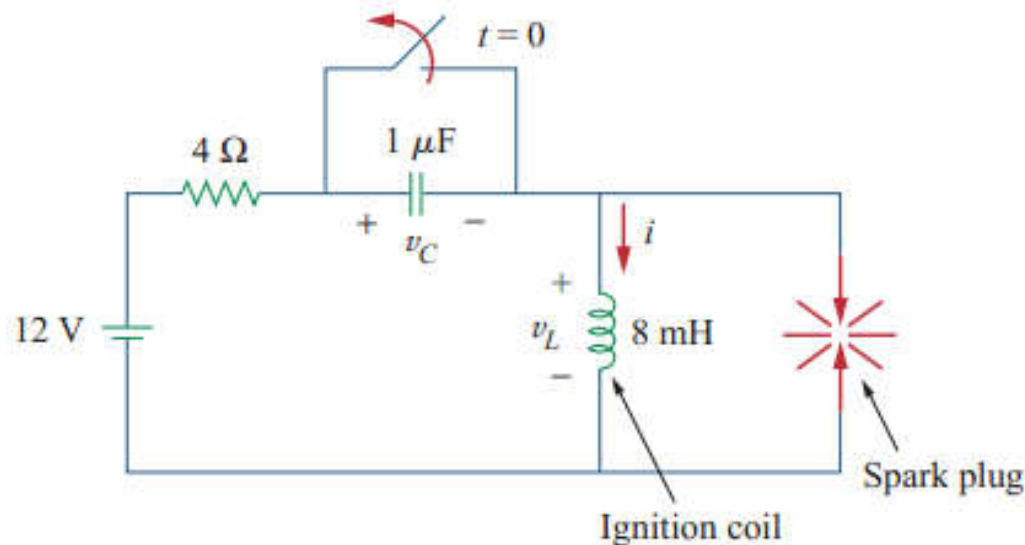
# Automobile Ignition Circuit – 2<sup>nd</sup> order model

- Assuming that the switch in the figure is closed prior to  $t = 0^-$ . Find the inductor voltage  $v_L$  for  $t > 0$ .





Ref.3, example 8.16

- After calculation, the inductor voltage's peak value is  $-259\text{V}$ .
  - Still far less than the voltage range of 6000 to 10,000 V required to fire the spark plug in a typical automobile
  - A device known as a transformer is used to step up the inductor voltage to the required level.
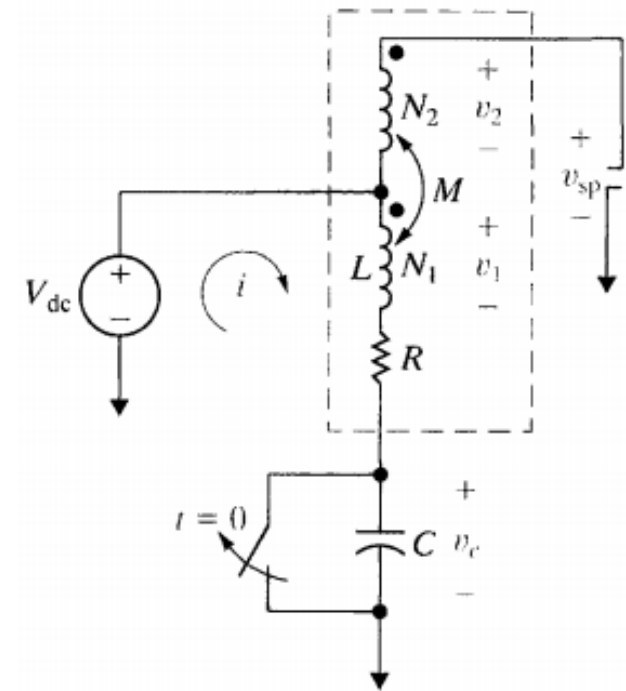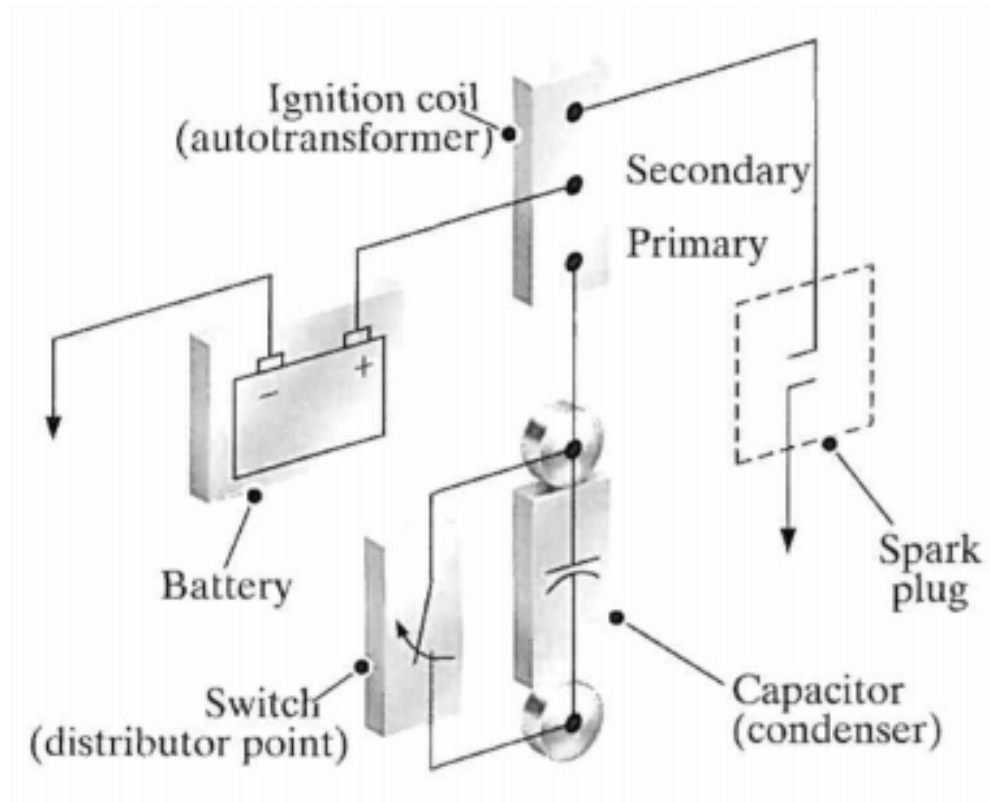
# Automobile Ignition Circuit – 2<sup>nd</sup> order model

- By using a transformer (autotransformer in this case), the voltage on the spark plug can be boosted up to 40 kV to ignite the fuel-air mixture in the cylinder.



# Practice

- The switch in the circuit shown in Figure Q2 has been closed for a long time before it is opened at  $t = 0$ .
  - Draw the equivalent circuit at  $t = 0^-$  and  $t = \infty$ ;
  - Find  $i_L(t)$  for  $t \geq 0$ ;
  - How many microseconds after the switch opens is the inductor voltage  $v_L(t)$  maximum?
  - If resistor is removed from the circuit at  $t = 0$  s, draw  $i_L(t)$ .

