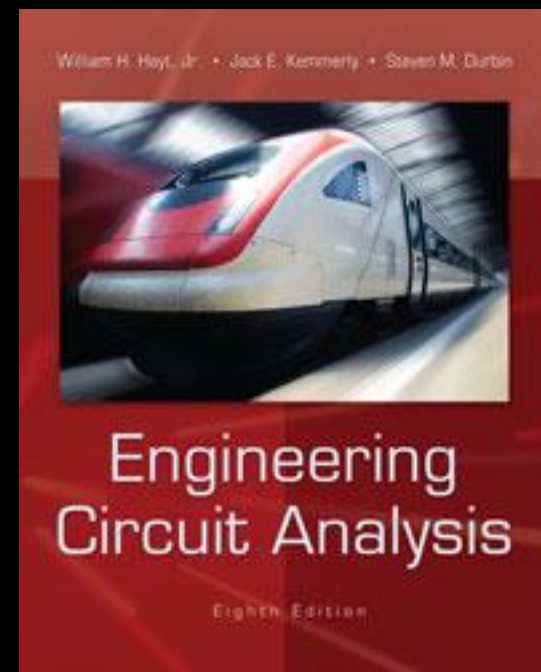


# Chapter 8


## Basic RL and RC Circuits



# The Source-Free RL Circuit

Applying KVL:


$$\frac{di}{dt} + \frac{R}{L}i = 0$$

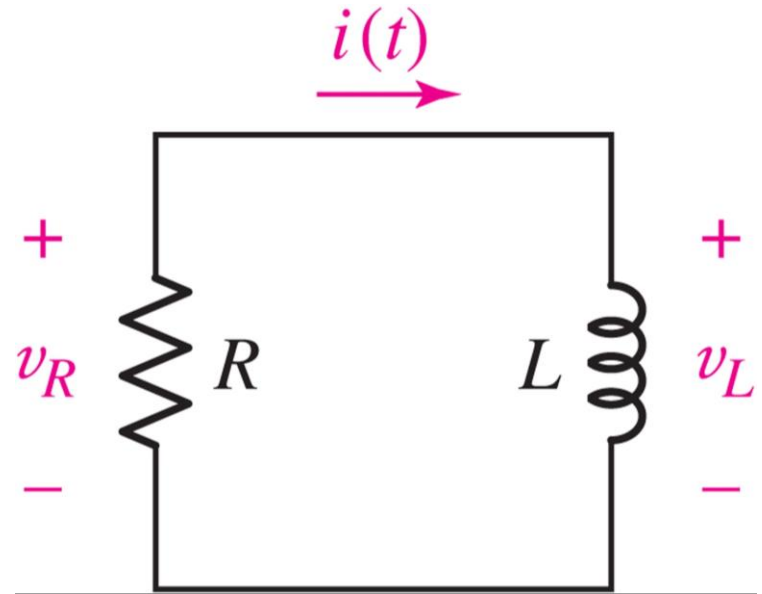

We can solve for the *natural response* if we know the *initial condition*  $i(0)=I_0$ :

$$i(t)=I_0e^{-Rt/L} \quad \text{for } t>0$$

# Example: RL with a Switch


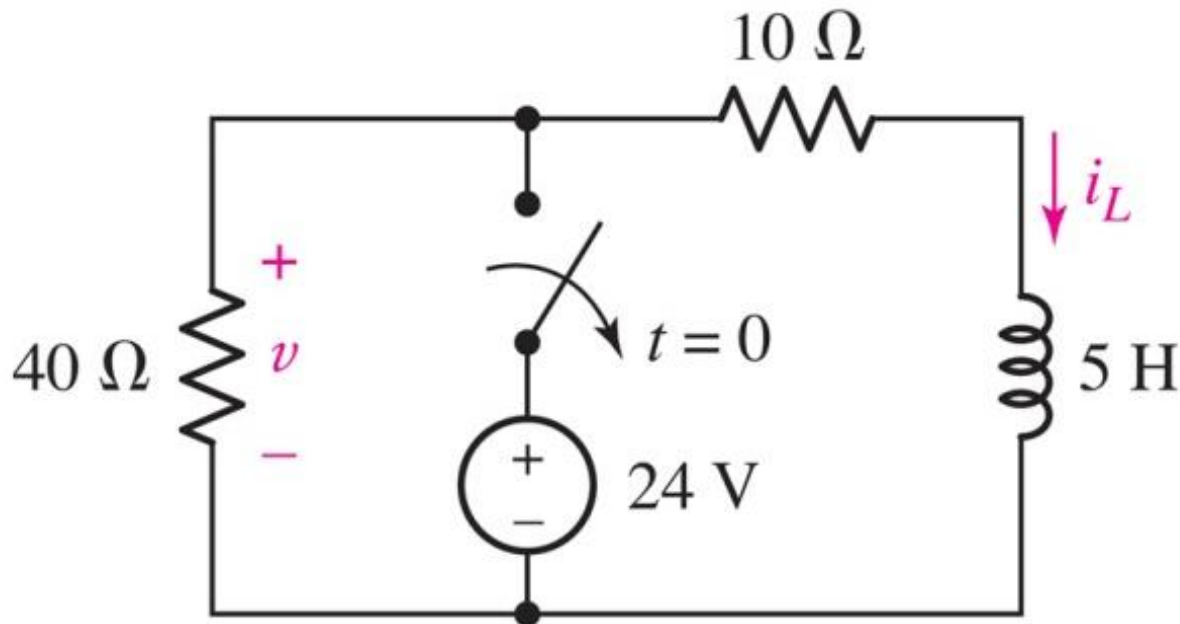


Show that the voltage  $v(t)$  will be -12.99 volts at  $t=200\ \text{ms}$ .

# The Exponential Response

The time constant  
 $\tau = L/R$   
determines the rate of  
decay.


$$i(t) = I_0 e^{-t/\tau}$$

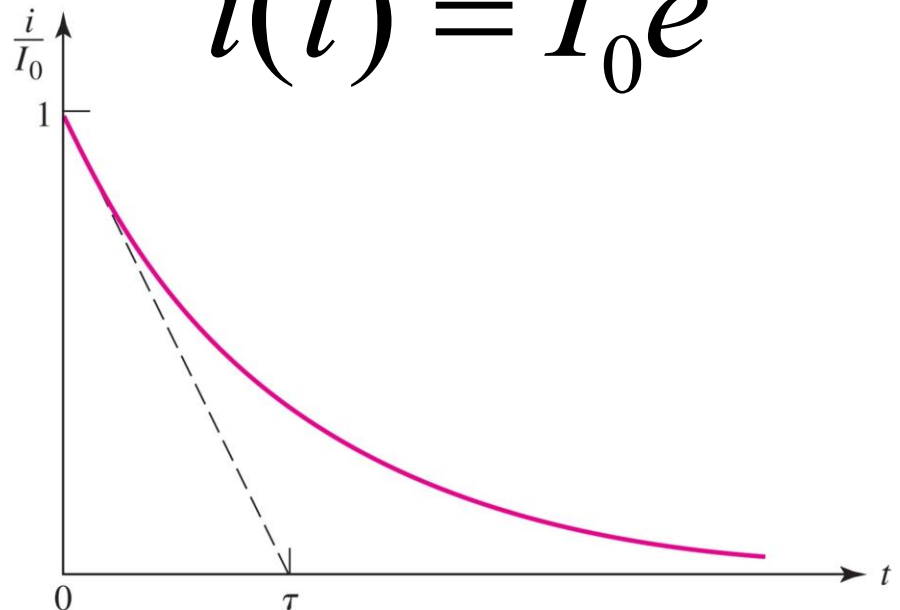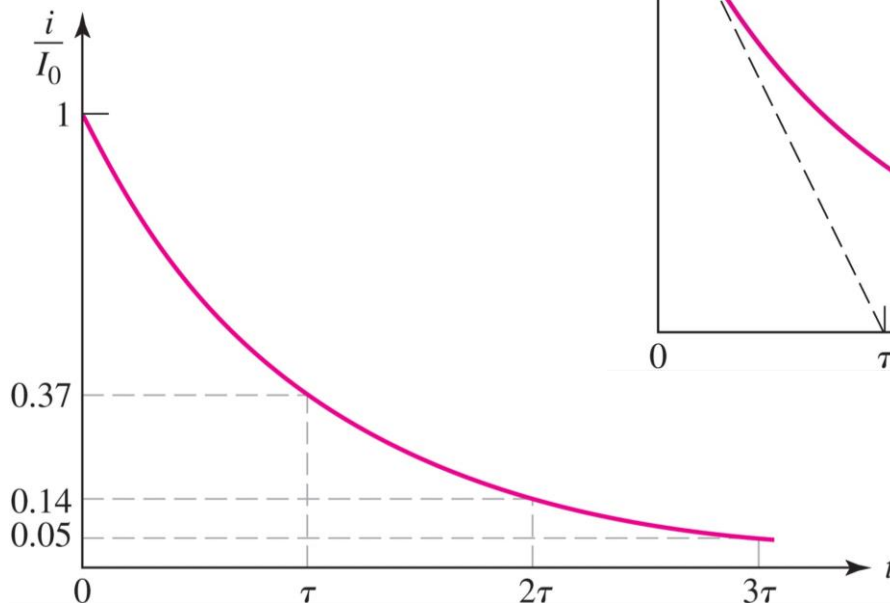

# The Source-Free RC Circuit

Applying KCL:


$$\frac{dv}{dt} + \frac{1}{RC}v = 0$$

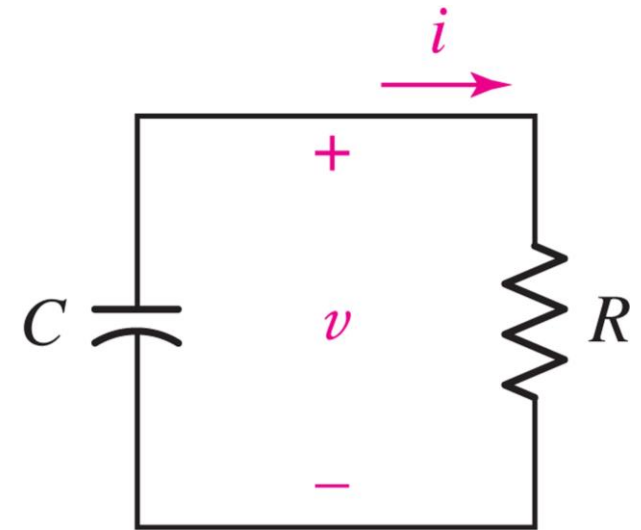

We can solve for the *natural response*  
if we know the *initial condition*  $v(0)=V_0$

$$v(t)=V_0e^{-t/RC} \quad \text{for } t>0$$


# RC Natural Response

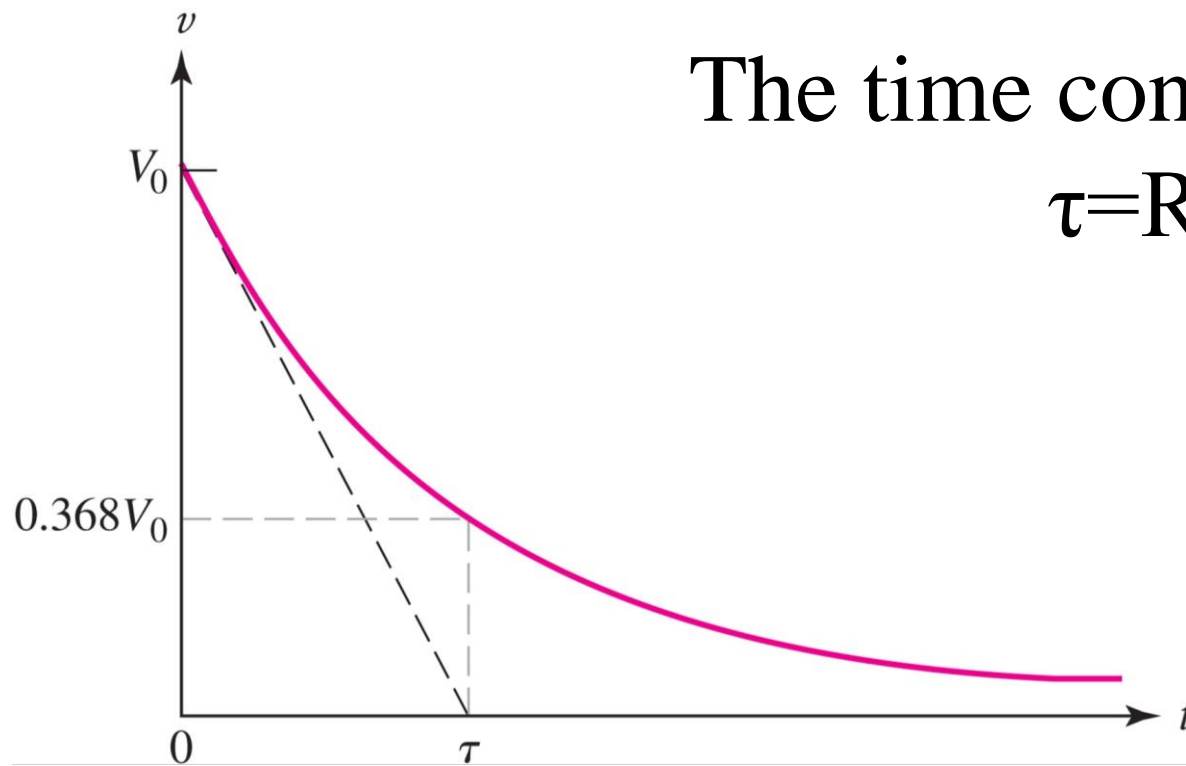

The time constant is  
 $\tau=RC$

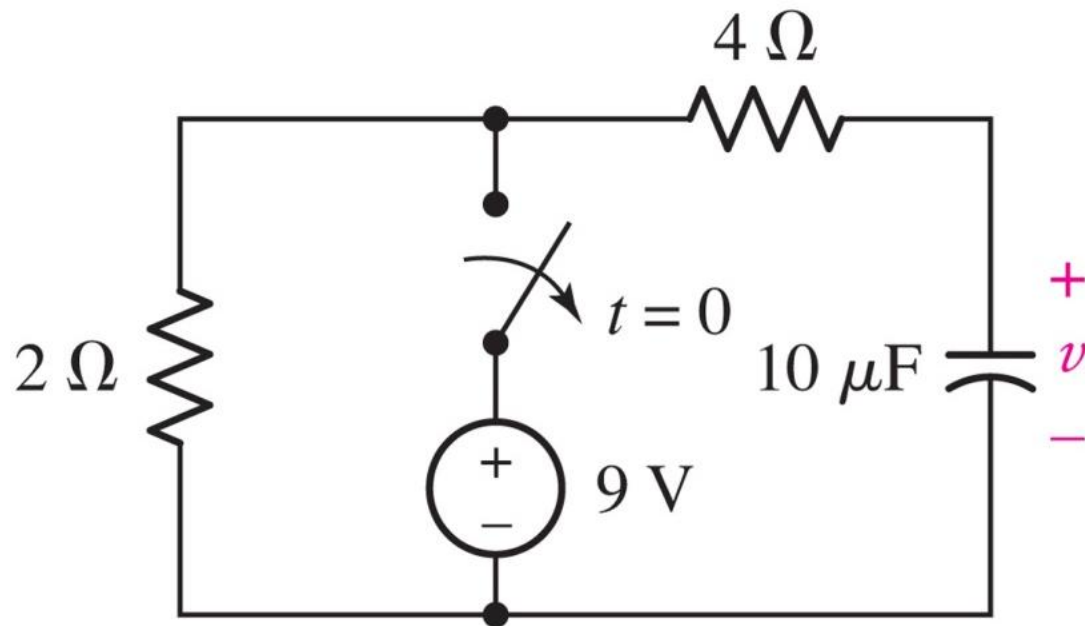
# The Source Free RC Circuit

Show that the voltage  $v(t)$   
is 321 mV at  $t=200\text{ }\mu\text{s}$ .


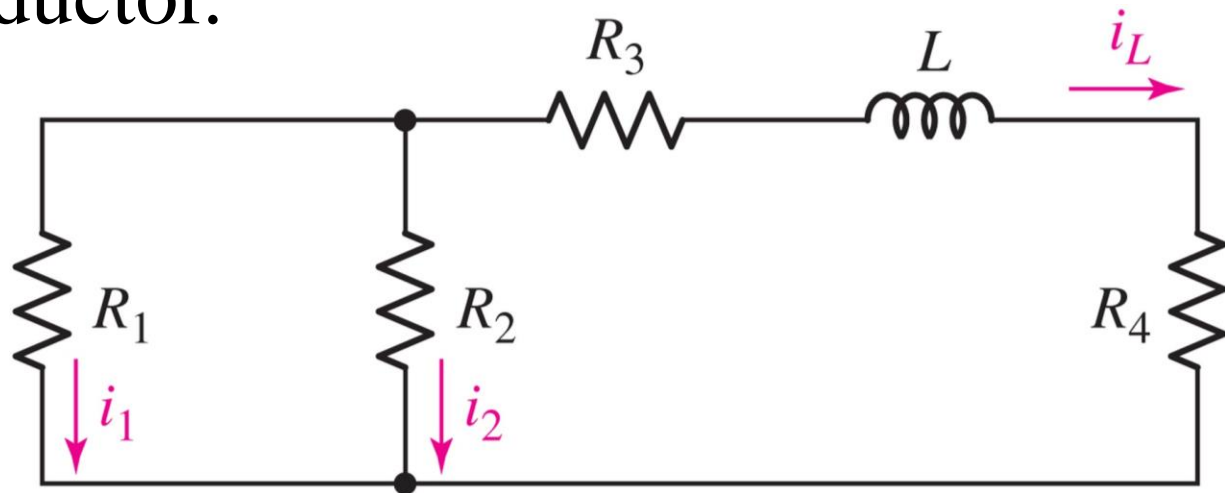
# General RL Circuits

The time constant of a single-inductor circuit will be  $\tau = L/R_{eq}$  where  $R_{eq}$  is the resistance seen by the inductor.




*Example:*  $R_{eq} = R_3 + R_4 + R_1 R_2 / (R_1 + R_2)$


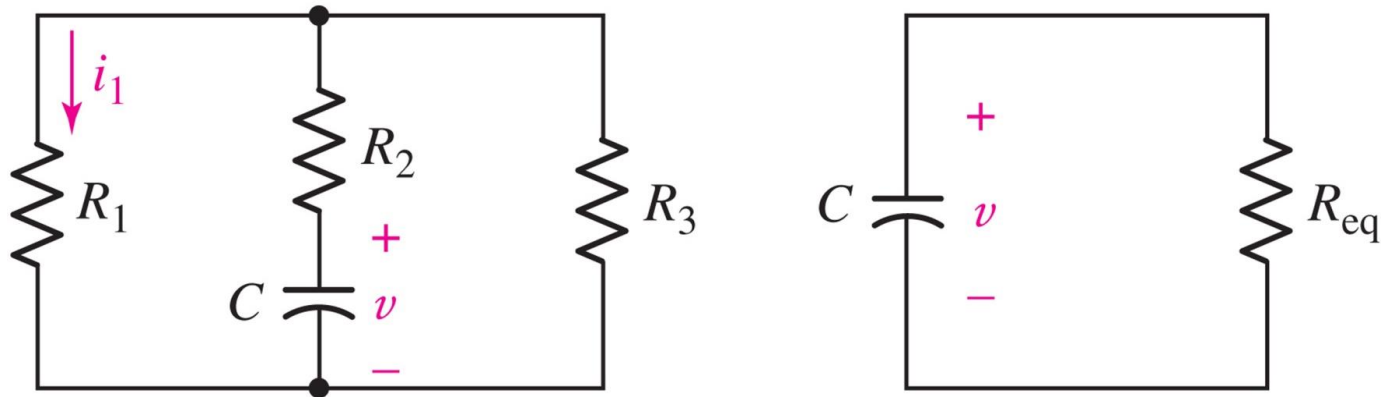
# General RC Circuits

The time constant of a single-capacitor circuit will be  $\tau = R_{eq}C$  where  $R_{eq}$  is the resistance seen by the capacitor.




*Example:*  $R_{eq} = R_2 + R_1 R_3 / (R_1 + R_3)$

# 1<sup>st</sup> Order Response Observations

- The voltage on a capacitor or the current through an inductor is the same *prior to* and *after* a switch at  $t=0$ .
- Resistor voltage (or current) prior to the switch  $v(0^-)$  can be different from the voltage after the switch  $v(0^+)$ .
- All voltages and currents in an RC or RL circuit follow the same natural response  $e^{-t/\tau}$ .
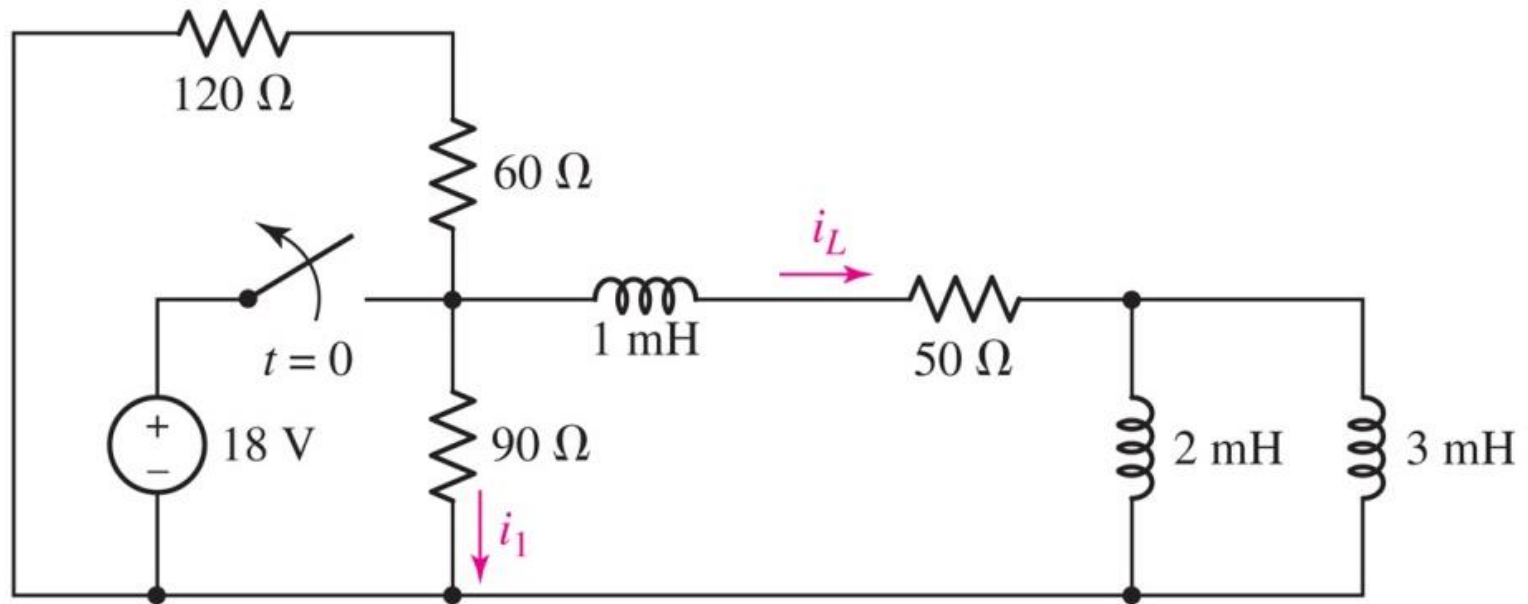
# Example: L and R Current


Find  $i_1(t)$  and  $i_L(t)$  for  $t > 0$ .



Answer:  $\tau = 20\ \mu\text{s}$ ;  $i_1 = -0.24e^{-t/\tau}$ ,  $i_L = 0.36e^{-t/\tau}$  for  $t > 0$

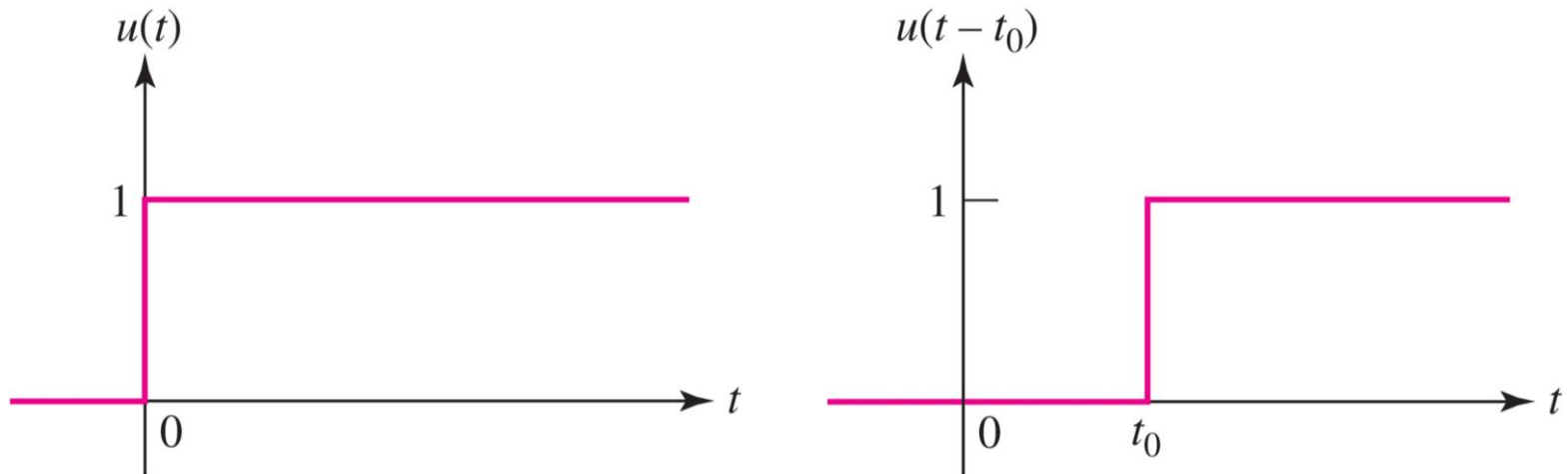
# The Unit Step Function

The unit-step function  $u(t)$  is a convenient notation to represent change:



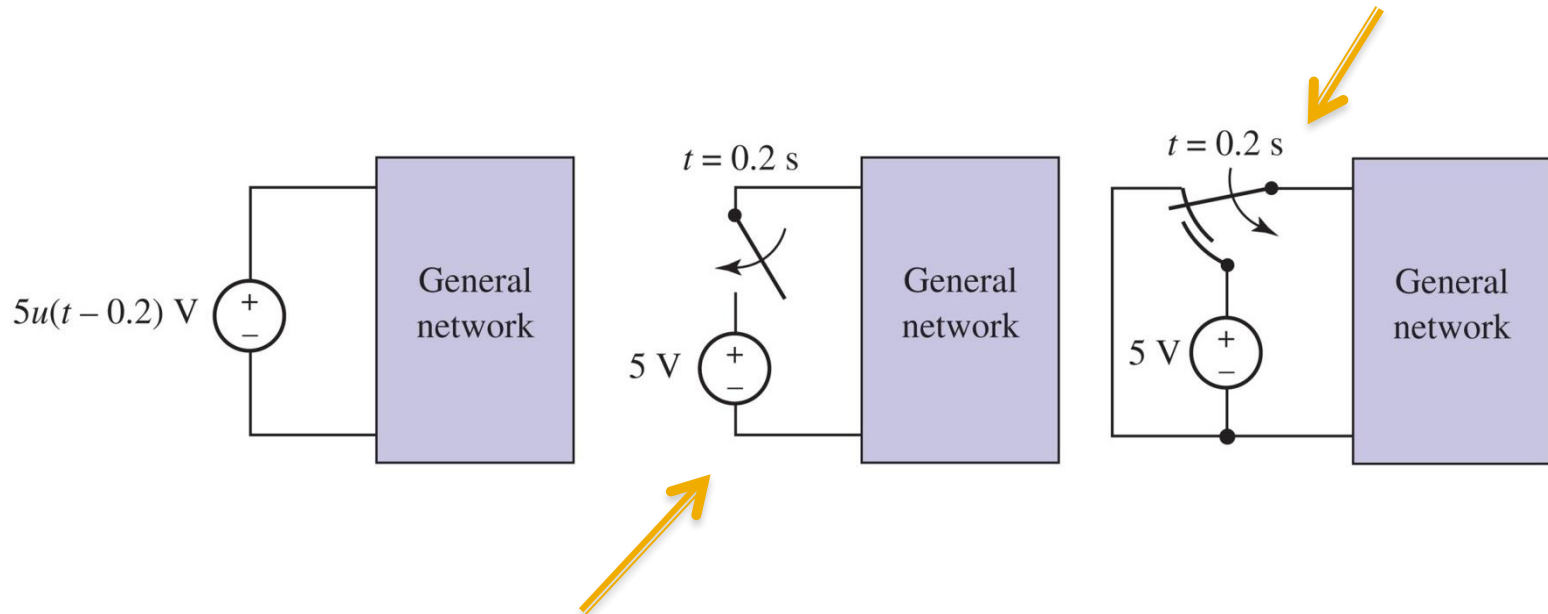
# Switches and Steps

- The unit step models a double-throw switch.




- A single-throw switch is open circuit for  $t < 0$ , not short circuit.

# Modeling Pulses using $u(t)$

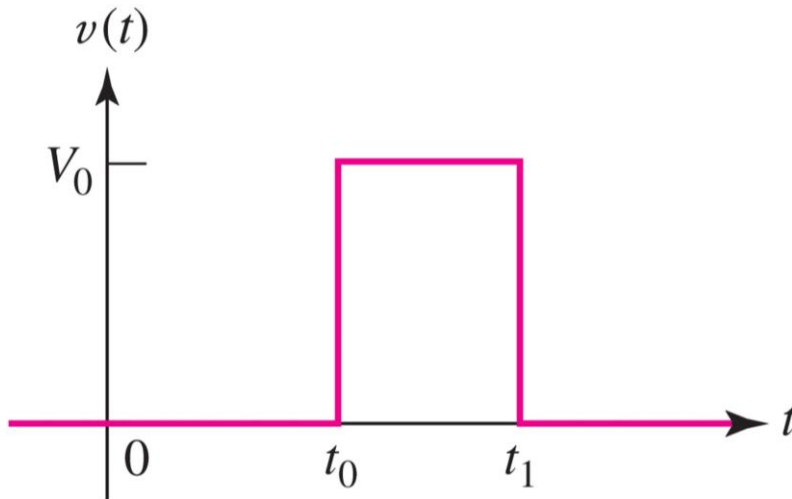



Rectangular  
pulse

Pulsed  
sinewave:

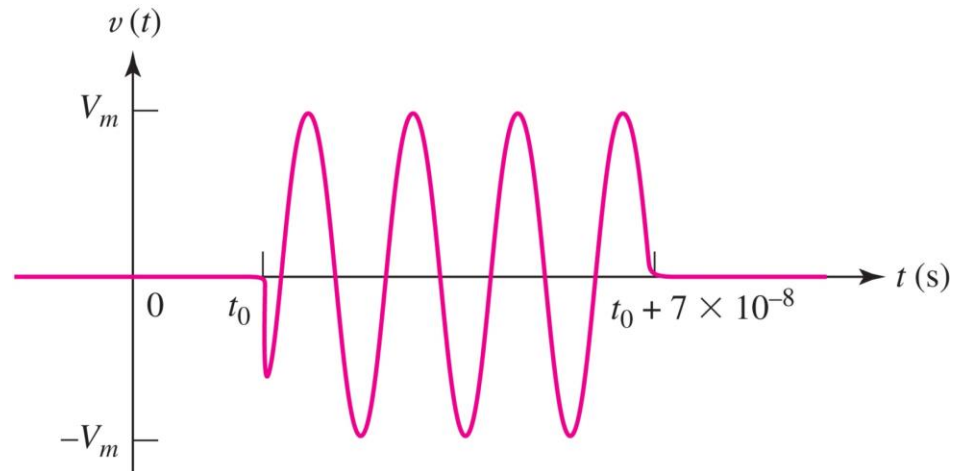
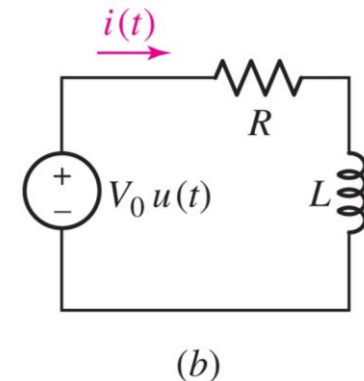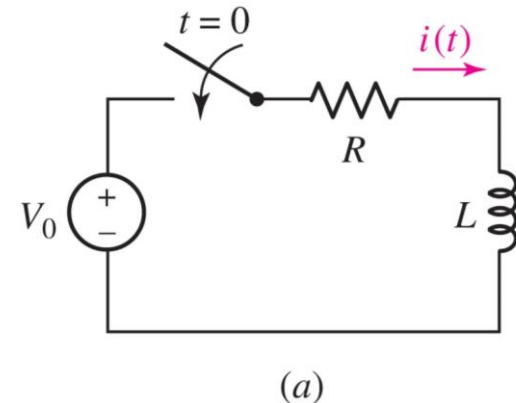
# Driven RL Circuits



- The two circuits shown both have  $i(t)=0$  for  $t<0$  and are also the same for  $t>0$ . Both are similar
- We now have to find both the *natural response* and the *forced response* due to the source  $V_0$


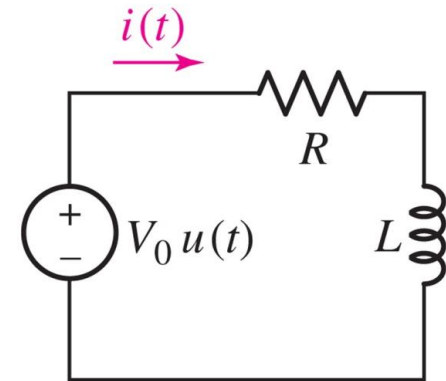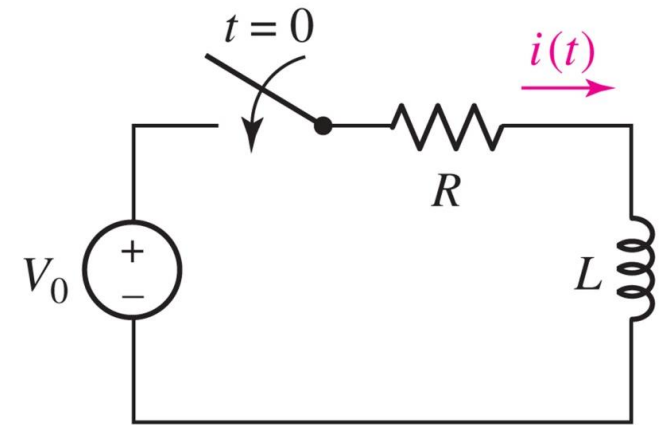
# Driven RL Circuits


The total response is the combination of the transient/natural response and the forced response:

$$i(t) = \frac{V_0}{R} \left( 1 - e^{-Rt/L} \right) u(t)$$








# Driven RL Circuits

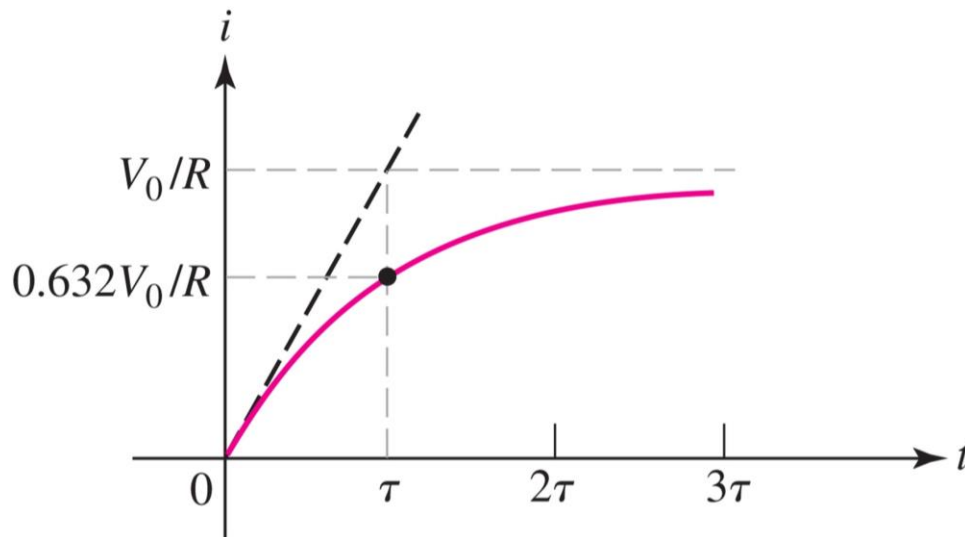
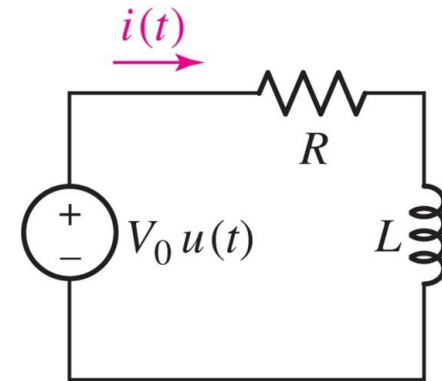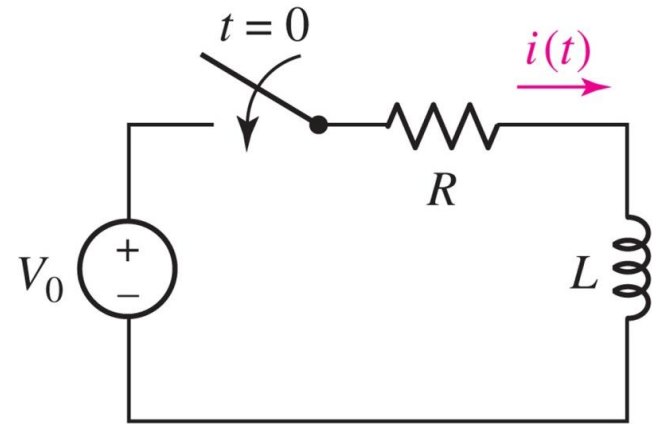
$$i(t) = \frac{V_0}{R} \left(1 - e^{-Rt/L}\right) u(t)$$




# Example: RL Circuit with Step

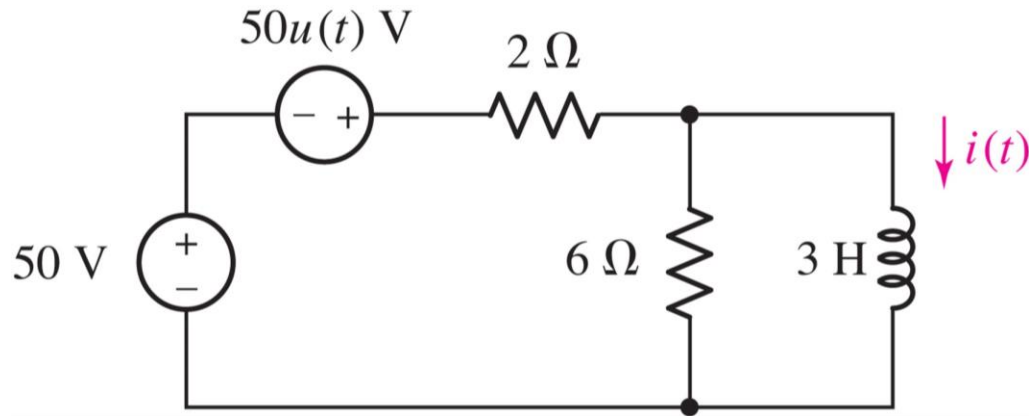


Show that


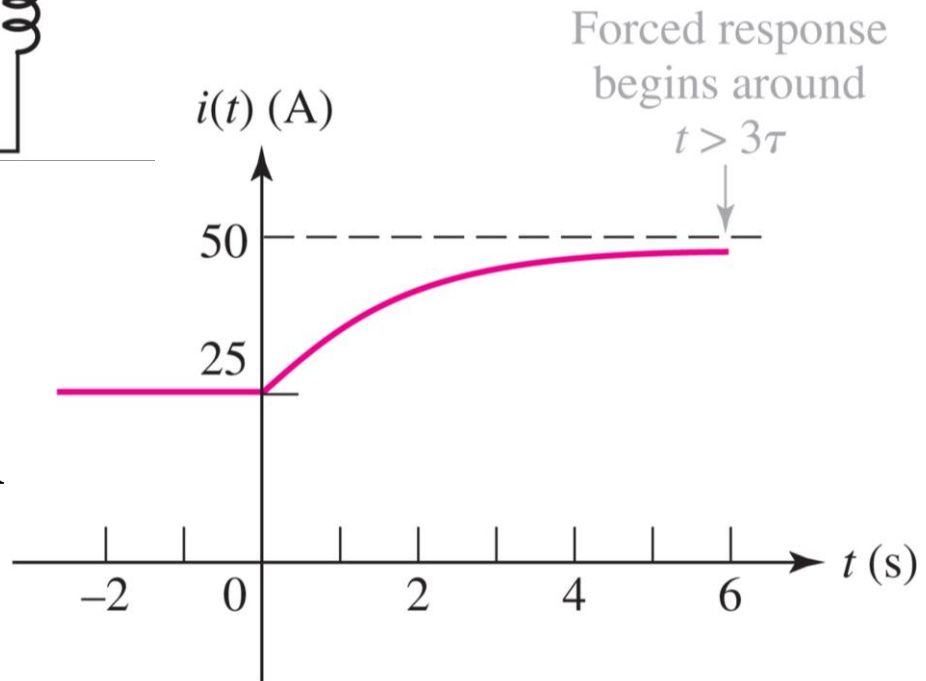
$$i(t) = 25 + 25(1 - e^{-t/2})u(t) \text{ A}$$




# Example: Voltage Pulse

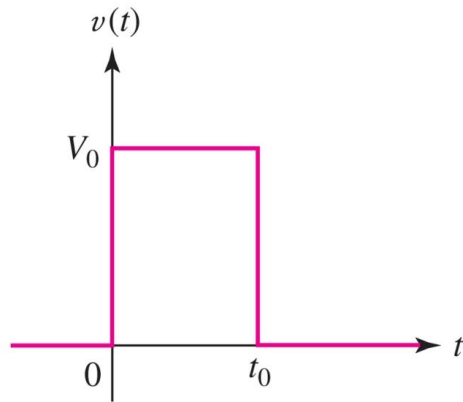

(a)

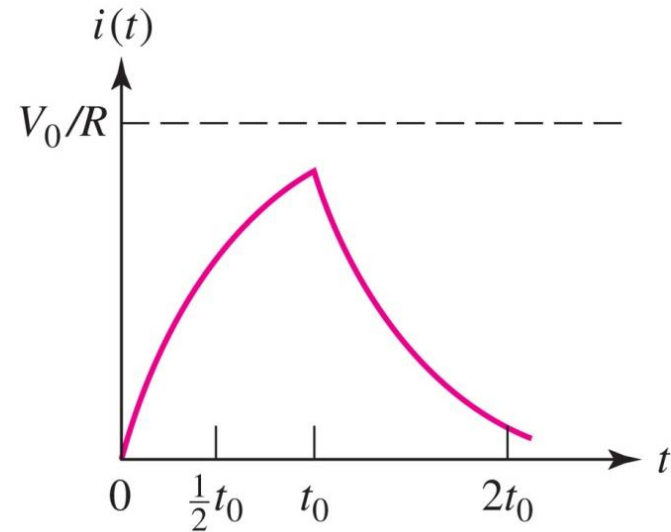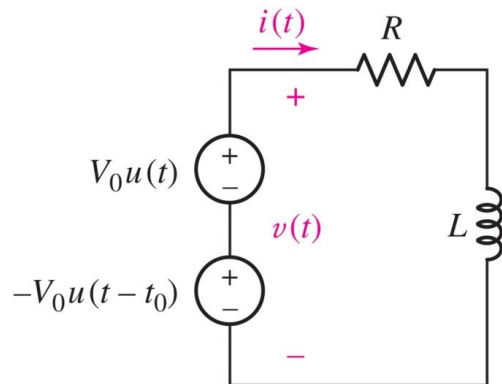


# Driven RC Circuits (part 1 of 2)

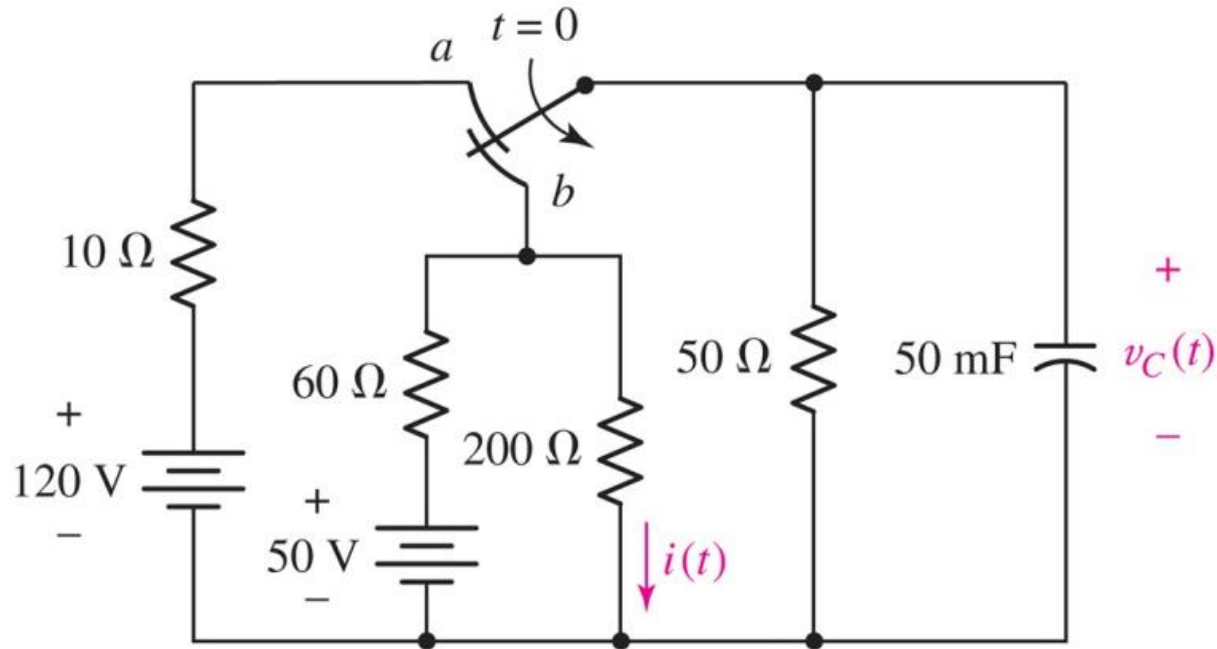


$$v_C = 20 + 80e^{-t/1.2} \text{ V and } i = 0.1 + 0.4e^{-t/1.2} \text{ A}$$

# Driven RC Circuits (part 2 of 2)

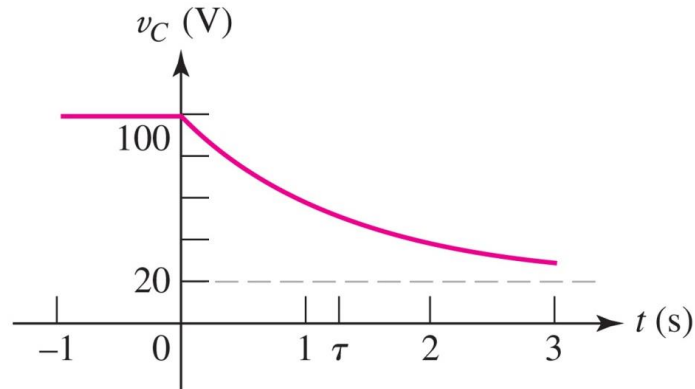

(a)

$$v_C = 20 + 80e^{-t/1.2} \text{ V}$$

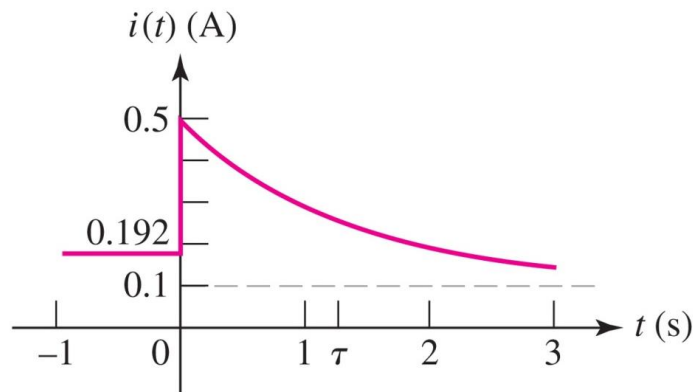

(b)

$$i = 0.1 + 0.4e^{-t/1.2} \text{ A}$$

# RL Driven Circuit

1. With all independent sources zeroed out, simplify the circuit to determine  $R_{eq}$ ,  $L_{eq}$ , and the time constant  $\tau = L_{eq}/R_{eq}$ .
2. Viewing  $L_{eq}$  as a short circuit, use dc analysis methods to find  $i_L(0^-)$ , the inductor current just prior to the discontinuity.
3. Again viewing  $L_{eq}$  as a short circuit, use dc analysis methods to find the forced response. This is the value approached by  $f(t)$  as  $t \rightarrow \infty$ ; we represent it by  $f(\infty)$ .
4. Write the total response as the sum of the forced and natural responses:  $f(t) = f(\infty) + Ae^{-t/\tau}$ .
5. Find  $f(0^+)$  by using the condition that  $i_L(0^+) = i_L(0^-)$ . If desired,  $L_{eq}$  may be replaced by a current source  $i_L(0^+)$  [an open circuit if  $i_L(0^+) = 0$ ] for this calculation. With the exception of inductor currents (and capacitor voltages), other currents and voltages in the circuit may change abruptly.
6.  $f(0^+) = f(\infty) + A$  and  $f(t) = f(\infty) + [f(0^+) - f(\infty)]e^{-t/\tau}$ , or total response = final value + (initial value – final value)  $e^{-t/\tau}$ .

# RC Driven Circuit

1. With all independent sources zeroed out, simplify the circuit to determine  $R_{eq}$ ,  $C_{eq}$ , and the time constant  $\tau = R_{eq}C_{eq}$ .
2. Viewing  $C_{eq}$  as an open circuit, use dc analysis methods to find  $v_C(0^-)$ , the capacitor voltage just prior to the discontinuity.
3. Again viewing  $C_{eq}$  as an open circuit, use dc analysis methods to find the forced response. This is the value approached by  $f(t)$  as  $t \rightarrow \infty$ ; we represent it by  $f(\infty)$ .
4. Write the total response as the sum of the forced and natural responses:  $f(t) = f(\infty) + Ae^{-t/\tau}$ .
5. Find  $f(0^+)$  by using the condition that  $v_C(0^+) = v_C(0^-)$ . If desired,  $C_{eq}$  may be replaced by a voltage source  $v_C(0^+)$  [a short circuit if  $v_C(0^+) = 0$ ] for this calculation. With the exception of capacitor voltages (and inductor currents), other voltages and currents in the circuit may change abruptly.
6.  $f(0^+) = f(\infty) + A$  and  $f(t) = f(\infty) + [f(0^+) - f(\infty)]e^{-t/\tau}$ ,  
or total response = final value + (initial value – final value)  $e^{-t/\tau}$ .