

EEE205 – Digital Electronics (II)

Lecture 13

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU


1

In This Session

- We have learned how to derive the state graph from a given circuit and to analyze the circuit.
- Next we will learn how to derive the state table or graph from a problem statement and to design the circuit.
- State Assignment

2

General Form of A Sequential Circuit.

 

- The sequential circuits whose outputs depend only on the state of the circuit are of **Moore type**.
- Those whose outputs depend on both the state and the inputs are of **Mealy type**.

3

Moore State Model.

We wish to design such a circuit:

- The circuit has one input w and one output z.
- All changes in the circuit occur on the positive edge of a clock signal.
- The output z is 1 if during the past two clock cycles w was 1. Otherwise z is 0.

| | | | | | | | | | | | |
|--------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|-----------------|
| Clock cycle: | t ₀ | t ₁ | t ₂ | t ₃ | t ₄ | t ₅ | t ₆ | t ₇ | t ₈ | t ₉ | t ₁₀ |
| w: | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z: | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |


Input w changes slightly after clock edges, as it is often an output of another circuit synchronized by the same clock.

4

Moore State Model.

State Diagram

 - State A: w is 0 during past 1 clock cycle.
- State B: w has been 1 for just 1 clock cycle.
- State C: w has been 1 for 2 clock cycles.



5

Moore State Model.

State Table


| Present state | Next state | | Output z |
|---------------|------------|---------|------------|
| | $w = 0$ | $w = 1$ | |
| A | A | B | 0 |
| B | A | C | 0 |
| C | A | C | 1 |

| | Present state $y_2 y_1$ | Next state | | Output z |
|---|----------------------------|------------|-----------|---------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2 Y_1$ | $Y_2 Y_1$ | |
| A | 00 | 00 | 01 | 0 |
| B | 01 | 00 | 10 | 0 |
| C | 10 | 00 | 10 | 1 |
| | 11 | <i>dd</i> | <i>dd</i> | <i>d</i> |

6

Moore State Model.

Next-State and Output Expressions

 


7

Moore State Model.

Implementation


Output z depends on the state only.
 
$$\begin{aligned}
 Y_1 &= w \bar{y}_1 \bar{y}_2 \\
 Y_2 &= w y_1 + w y_2 \\
 &= w(y_1 + y_2) \\
 z &= y_2
 \end{aligned}$$



8

Moore State Model - Timing Diagram

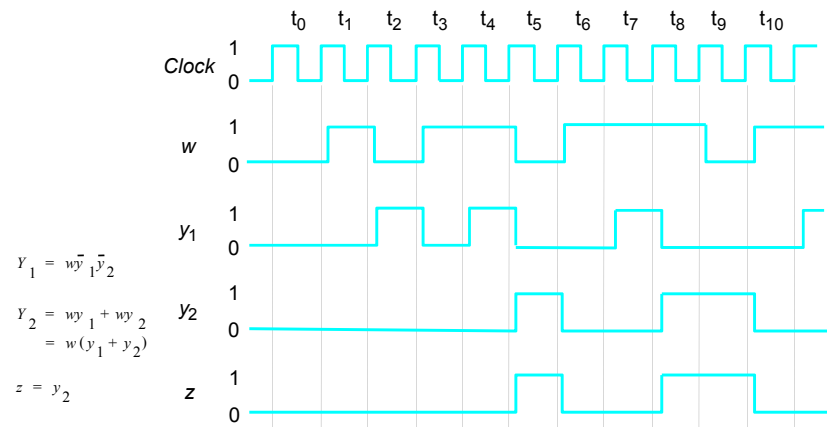

Input w changes slightly after the clock edges, because it is often an output of another circuit synchronized by the same clock.

9

Moore State Model.


Alternative State Assignment

| | Present state y_2y_1 | Next state | | Output z |
|---|---------------------------|------------|-----------|---------------|
| | | $w = 0$ | $w = 1$ | |
| | | Y_2Y_1 | Y_2Y_1 | |
| A | 00 | 00 | 01 | 0 |
| B | 01 | 00 | 11 | 0 |
| C | 11 | 00 | 11 | 1 |
| | 10 | <i>dd</i> | <i>dd</i> | <i>d</i> |

10

Moore State Model.

Improved Implementation

 

11

Mealy State Model.

We wish to design such a circuit:

- The circuit has one input w and one output z .
- The output z is 1 in the clock cycle when the second occurrence of $w = 1$ is detected. Otherwise z is 0.

| | | | | | | | | | | | |
|--------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |


Sequences of input and output signals.

12

Mealy State Model.

State Diagram

 - State A: w is 0, producing an output $z = 0$.
- State B: w is 1.
- If $w = 1$ for two or consecutive clock cycles, the machine remains in state B and produce an output $z = 1$.



13

Mealy State Model.

State Table

| Present state | Next state | | Output z | |
|---------------|------------|---------|------------|---------|
| | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| A | A | B | 0 | 0 |
| B | A | B | 0 | 1 |

| Present state | Next state | | Output | |
|---------------|------------|---------|---------|---------|
| | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| y | Y | Y | z | z |
| A | 0 | 0 | 0 | 0 |
| B | 1 | 0 | 0 | 1 |


14

Mealy State Model.

Implementation

$$Y = D = w$$

$$z = wy$$

 


Output z depends on both the state and the input.

15

Mealy State Model - Timing Diagram

$$Y = D = w$$

$$z = wy$$

 

16

State Assignments

- The state assignment should be made so as to minimize the cost of the logic.
- If the number of states is small, it may be possible to try all possible state assignments.
- For a state table with 3 states, there are $4 \times 3 \times 2 = 24$ possible state assignments.
- But many of these are equivalent in cost of realization.

| | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 19 | 20 | 21 | 22 | 23 | 24 |
|-------|----|----|----|----|----|----|----|----|----|----|----|----|----|
| S_0 | 00 | 00 | 00 | 00 | 00 | 00 | 01 | 11 | 11 | 11 | 11 | 11 | 11 |
| S_1 | 01 | 01 | 10 | 10 | 11 | 11 | 00 | 00 | 00 | 01 | 01 | 10 | 10 |
| S_2 | 10 | 11 | 01 | 11 | 01 | 10 | 10 | 01 | 10 | 00 | 10 | 00 | 01 |

17

State Assignments

- If we interchange two columns in an assignment, the cost will be unchanged, e.g. 1/3, 2/4, 5/6.
- If symmetrical flip-flops such as J-K, S-R or T are used, complementing one or more columns of an assignment will not change the cost, e.g. 2/7, 6/19.
- So there are only 3 non-equivalent assignments for 3 or 4 states.

| States | 3-State Assignments | | | 4-State Assignments | | |
|--------|---------------------|----|----|---------------------|----|----|
| | 1 | 2 | 3 | 1 | 2 | 3 |
| a | 00 | 00 | 00 | 00 | 00 | 00 |
| b | 01 | 01 | 11 | 01 | 01 | 11 |
| c | 10 | 11 | 01 | 10 | 11 | 01 |
| d | — | — | — | 11 | 10 | 10 |

18

State Assignments

One-Hot State Assignment

- For FPGAs it may not be important to minimize the number of flip-flops used in the design.
- Instead, it is desirable to reduce the number of logic cells used and make the design faster.
- The one-hot assignment uses one flip-flop for each state and only one flip-flop is set to 1 in each state.


e.g. a system with 4 states could use 4 flip-flops (Q_0, Q_1, Q_2, Q_3) with the state assignment:

$S_0: Q_0 Q_1 Q_2 Q_3 = 1000, S_1: 0100, S_2: 0010, S_3: 0001$

19

State Assignments
 
$$Q_3^+ = X_1 (Q_0 Q_1' Q_2' Q_3') + X_2 (Q_0' Q_1 Q_2' Q_3') + X_3 (Q_0' Q_1' Q_2 Q_3') + X_4 (Q_0' Q_1' Q_2' Q_3)$$



$Q_0 = 1$ implies $Q_1 = Q_2 = Q_3 = 0$, the $Q_1' Q_2' Q_3'$ term is redundant

$$Q_3^+ = X_1 Q_0 + X_2 Q_1 + X_3 Q_2 + X_4 Q_3$$

Each term in the next-state equation contains exactly one state variable, which can be determined by inspecting the state graph.

20

$$Z_2 = X_2 Q_1 + X_4 Q_3$$