

# Digital System Design with HDL (I)

## Lecture 5

Dr. Ming Xu

Dept of Electrical & Electronic Engineering  
XJTLU

1

## In This Session

- Primitive Instantiations
- Continuous Assignments
- Procedural Statements
  - Procedural Assignment Statements

2

## Primitive Instantiations

A circuit can be described using predefined modules.

```
gate_type [instance_name] (output_port, input_port {,  
input_port });
```

```
gate_type # (delay) [instance_name] (output_port,  
input_port {, input_port });
```

- *gate\_type*: the type of gate
- *Instance\_name*: optional.
- *delay*: propagation delay in time units.

3

## Primitive Instantiations

Example: Structural specification of a full-adder

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  wire z1, z2, z3, z4;  
  
  and And1 (z1, x, y);  
  and And2 (z2, x, Cin);  
  and And3 (z3, y, Cin);  
  or Or1 (Cout, z1, z2, z3);  
  xor Xor1 (z4, x, y);  
  xor Xor2 (s, z4, Cin);  
  
endmodule
```

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  
  and (z1, x, y);  
  and (z2, x, Cin);  
  and (z3, y, Cin);  
  or (Cout, z1, z2, z3);  
  xor (z4, x, y);  
  xor (s, z4, Cin);  
  
endmodule
```

4

## Primitive Instantiations

### Gate Types

| Name | Description                        | Usage                            |
|------|------------------------------------|----------------------------------|
| and  | $f = (a \cdot b \dots)$            | <b>and</b> ( $f, a, b, \dots$ )  |
| nand | $f = \overline{(a \cdot b \dots)}$ | <b>nand</b> ( $f, a, b, \dots$ ) |
| or   | $f = (a + b + \dots)$              | <b>or</b> ( $f, a, b, \dots$ )   |
| nor  | $f = \overline{(a + b + \dots)}$   | <b>nor</b> ( $f, a, b, \dots$ )  |
| xor  | $f = (a \oplus b \oplus \dots)$    | <b>xor</b> ( $f, a, b, \dots$ )  |
| xnor | $f = (a \odot b \odot \dots)$      | <b>xnor</b> ( $f, a, b, \dots$ ) |
| not  | $f = \bar{a}$                      | <b>not</b> ( $f, a$ )            |

## Primitive Instantiations

### Gate Types

- notif** and **bufif** gates are tri-state buffers.

| Name   | Description                | Usage                       |
|--------|----------------------------|-----------------------------|
| buf    | $f = a$                    | <b>buf</b> ( $f, a$ )       |
| notif0 | $f = (!e ? \bar{a} : 'bz)$ | <b>notif0</b> ( $f, a, e$ ) |
| notif1 | $f = (e ? \bar{a} : 'bz)$  | <b>notif1</b> ( $f, a, e$ ) |
| bufif0 | $f = (!e ? a : 'bz)$       | <b>bufif0</b> ( $f, a, e$ ) |
| bufif1 | $f = (e ? a : 'bz)$        | <b>bufif1</b> ( $f, a, e$ ) |

6

## Continuous Assignments

- Continuous assignments model combinational logic.
- Each time a signal on the right-hand side changes, the net on the left-hand side is re-evaluated.

### Explicit Continuous Assignment

```
net_type [size] net_name;
assign net_name = expression;
```


### Implicit Continuous Assignment

```
net_type [size] net_name = expression;
```

7

## Continuous Assignments

### Example

 

```
module example3 (x1, x2, x3, f);
  input x1, x2, x3;
  output f;

  assign f = (x1 & x2) | (~x2 & x3);

endmodule
```

8

## Continuous Assignments

- Multiple assignments can be specified in one assign statement (separated by commas)  
**assign** Cout = (x & y) | (x & Cin) | (y & Cin),  
          s = x ^ y ^ z;
- Multiple assignments can be combined with a net (wire, tri) declaration.  
**wire** s = x ^ y,  
      c = x & y;
- Continuous assignments are **concurrent** statements; their ordering in the code does not matter.

9

## Procedural Statements

- Procedural statements are evaluated in the order in which they appear.
- Procedural statements must be contained in **always** (or **initial**) blocks, or **function** or **task** blocks that are called only from inside **always** (or **initial**) blocks.
- always** procedural blocks process statements *repeatedly*.
- initial** procedural blocks process statements *one time*.

10

## always Block

**always** @(sensitivity\_list)

[begin]

  [procedural assignment statements]

  [programming constructs]

[end]

- If the value of a signal in the *sensitive list* changes, all the statements are evaluated sequentially.
- The signals are separated by keyword **or** or **comma** in Verilog 2001.

11


## always Block

- Level-sensitive **always** block
  - always** @ (signal1 or signal2)
  - Used for combinational circuits and latches
- Edge-sensitive **always** block
  - always** @ (posedge clk)
    - Response to positive edge of clk signal
  - always** @ (negedge clk)
    - Response to negative edge of clk signal
  - Used for sequential circuits and flip-flops

12

## always Block

 **Example:**  
a combinational logic circuit



```

module example5 (x1, x2, x3, f);
  input x1, x2, x3;
  output f;
  reg f;

  always @(x1 or x2 or x3)
    if (x2 == 1)
      f = x1;
    else
      f = x3;


endmodule

```

13

## always Block

**Example:** D-type flip-flop

 

```

module flipflop (D, Clock, Q);
  input D, Clock;
  output Q;
  reg Q;

  always @(posedge Clock)
    Q = D;

endmodule

```

14

## Procedural Assignment Statements

- **=**  
**Blocking assignments** – evaluate *in order*  
  **begin**  
    Q1 = D;  
    Q2 = Q1; // new Q1 goes to Q2.  
  **end**
- **<=**  
**No-blocking assignments** – evaluate *in parallel*  
  **begin**  
    Q1<= D;  
    Q2<= Q1; // old Q1 goes to Q2  
  **end**  
  The order of statements doesn't matter

15


## Procedural Assignment Statements

- For *blocking assignments*, the values of variables in each statement are the new values set by any preceding statements in the **always** block.
- For *non-blocking assignments*, the values of variables are the values at the beginning of the **always** block.
- Although the statements inside each **always** block are evaluated in order, each entire **always** block is still like a concurrent statement.

16

## Procedural Assignment Statements

Blocking and non-blocking assignments

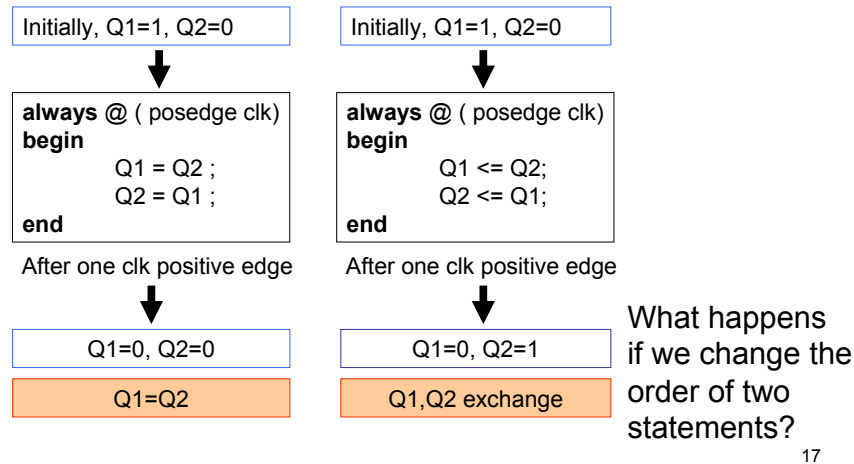


## Procedural Assignment Statements

**Example:** Blocking assignments

```
module example7_3 (D, Clock, Q1, Q2);
    input D, Clock;
    output Q1, Q2;
    reg Q1, Q2;

    always @(posedge Clock)
    begin
        Q1 = D;
        Q2 = Q1;
    end

endmodule
```

 


## Procedural Assignment Statements

**Example:** No-blocking assignments

```
module example7_4 (D, Clock, Q1, Q2);
    input D, Clock;
    output Q1, Q2;
    reg Q1, Q2;

    always @(posedge Clock)
    begin
        Q1 <= D;
        Q2 <= Q1;
    end

endmodule
```

 

## Procedural Assignment Statements

Recommendations

- It is better to use **blocking** assignments when describing **combinational** circuits
- It is better to using **no-blocking** assignments to describe **sequential** circuits