

Digital System Design with HDL (I)

Lecture 9

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

1

In This Session

- Verilog for Combinational Circuits
 - Adders
 - Arithmetic Overflow

2

Half-Adders


The half-adder does not add an input carry.

A	B	C _{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Σ = sum

C_{out} = output carry

A and B = input variables (operands)

 


- The sum is 1 only when the inputs are different — an XOR operation.
- The output carry is 1 only when both the inputs are 1 — an AND operation.

3

Full Adders

A	B	C _{in}	C _{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$\Sigma = (A \oplus B) \oplus C_{in}$$

$$\begin{aligned}
 C_{out} &= ABC_{in} + AB\bar{C}_{in} + A\bar{B}C_{in} + \bar{A}BC_{in} \\
 &= (ABC_{in} + AB\bar{C}_{in}) + (A\bar{B}C_{in} + \bar{A}BC_{in}) \\
 &= AB + AC_{in} + BC_{in}
 \end{aligned}$$

4

Full Adders

Exclusive-OR operation satisfies associative rule:

$$\begin{aligned} x \oplus (y \oplus z) &= x \oplus (\bar{y}z + y\bar{z}) \\ &= \bar{x}(\bar{y}z + y\bar{z}) + x(\bar{y} \cdot \bar{z} + yz) \\ &= \bar{x} \cdot \bar{y}z + \bar{x}y\bar{z} + x\bar{y} \cdot \bar{z} + xyz \end{aligned}$$


$$\begin{aligned} (x \oplus y) \oplus z &= (\bar{x}y + x\bar{y}) \oplus z \\ &= (\bar{x} \cdot \bar{y} + xy)z + (\bar{x}y + x\bar{y})\bar{z} \\ &= \bar{x} \cdot \bar{y}z + xyz + \bar{x}y\bar{z} + x\bar{y} \cdot \bar{z} \end{aligned}$$

We have

$$s = (x \oplus y) \oplus c = x \oplus y \oplus c$$

5

Full Adders

 

6

Full Adders

What is the output for an XOR gate with multiple inputs?

- If there are **even** 1s in the inputs, output a 0.
- If there are **odd** 1s in the input, output a 1.

Example:

$$0 \oplus 0 \oplus 0 = 0$$

$$1 \oplus 0 \oplus 0 = 1$$

$$1 \oplus 1 \oplus 0 = 0$$

$$1 \oplus 1 \oplus 1 = 1$$

7

Arithmetic Overflow

- Arithmetic **overflow** occurs when the outcome of addition does not fit within the magnitude bits used to represent the numbers.

(+7)	0 1 1 1	(-7)	1 0 0 1
+ (+2)	+ 0 0 1 0	+ (+2)	+ 0 0 1 0
(+9)	1 0 0 1	(-5)	1 0 1 1
	$c_4 = 0$		$c_4 = 0$
	$c_3 = 1$		$c_3 = 0$
(+7)	0 1 1 1	(-7)	1 0 0 1
+ (-2)	+ 1 1 1 0	+ (-2)	+ 1 1 1 0
(+5)	1 0 1 0 1	(-9)	1 0 1 1 1
	$c_4 = 1$		$c_4 = 1$
	$c_3 = 1$		$c_3 = 0$

8

Arithmetic Overflow

- It is important to be able to detect the overflow.
- In this example, $\text{Overflow} = c_3 \oplus c_4$
- For n-bit numbers we have

$$\text{Overflow} = c_n \oplus c_{n-1} = c_n \oplus x_{n-1} \oplus y_{n-1} \oplus s_{n-1}$$

Since $s_k = x_k \oplus y_k \oplus c_k$, it follows that

$$\begin{aligned} x_k \oplus y_k \oplus s_k &= (x_k \oplus y_k) \oplus (x_k \oplus y_k \oplus c_k) \\ &= (x_k \oplus y_k) \oplus (x_k \oplus y_k) \oplus c_k \\ &= 0 \oplus c_k \\ &= c_k \end{aligned}$$

9

Full-Adders

Using continuous assignment

```
module fulladd (Cin, x, y, s, Cout);
    input Cin, x, y;
    output s, Cout;

    assign s = x ^ y ^ Cin;
    assign Cout = (x & y) | (x & Cin) | (y & Cin);

endmodule
```

10

Full-Adders

A 4-bit adder using module instantiation

```
module adder4 (carryin, X, Y, S, carryout);
    input carryin;
    input [3:0] X, Y;
    output [3:0] S;
    output carryout;
    wire [3:1] C;

    fulladd stage0 (carryin, X[0], Y[0], S[0], C[1]);
    fulladd stage1 (C[1], X[1], Y[1], S[1], C[2]);
    fulladd stage2 (C[2], X[2], Y[2], S[2], C[3]);
    fulladd stage3 (C[3], X[3], Y[3], S[3], carryout);

endmodule
```

11

The **generate** Construct

- n instances of the *fulladd* subcircuit are required to build a n-bit ripple-carry adder.
- The **generate** construct (Verilog 2001) allows subcircuits to be instantiated in a loop.
- The loop index must be declared of type **genvar** – a positive integer that appears only in **generate** blocks.

Syntax:

```
generate
    [procedural statements]
    [instantiation statements]
endgenerate
```

12

The generate Construct

- Each instance has an instance name addbit[i].stage.

```
module ripple_g (carryin, X, Y, S, carryout);
    parameter n = 4;
    input carryin;
    input [n-1:0] X, Y;
    output [n-1:0] S;
    output carryout;
    wire [n:0] C;

    genvar i;
    assign C[0] = carryin;
    assign carryout = C[n];

    generate
        for (i = 0; i <= n-1; i = i+1)
            begin:addbit
                fulladd stage (C[i], X[i], Y[i], S[i], C[i+1]);
            end
        endgenerate
    endmodule
```

13

Full-Adders

An n-bit adder using procedural statements

```
module addern (carryin, X, Y, S, carryout);
    parameter n=32;
    input carryin;
    input [n-1:0] X, Y;
    output reg [n-1:0] S;
    output reg carryout;
    reg [n:0] C;
    integer k;

    always @(X, Y, carryin)
        begin
            C[0] = carryin;
            for (k = 0; k < n; k = k+1)
                begin
                    S[k] = X[k] ^ Y[k] ^ C[k];
                    C[k+1] = (X[k] & Y[k]) | (X[k] & C[k]) | (Y[k] & C[k]);
                end
            carryout = C[n];
        end
    endmodule
```

14

Full-Adders

An alternative n-bit adder with the overflow signal

```
module addern (carryin, X, Y, S, carryout, overflow);
    parameter n = 32;
    input carryin;
    input [n-1:0] X, Y;
    output reg [n-1:0] S;
    output reg carryout, overflow;

    always @(X, Y, carryin)
        begin
            {carryout, S} = X + Y + carryin;
            overflow = carryout ^ X[n-1] ^ Y[n-1] ^ S[n-1];
        end
    endmodule
```

15

Full-Adders

A one-digit BCD adder

0111	7
+ 0101	+ 5
1100	12
+ 0110	
10010	

1000	8
+ 1001	+ 9
10001	17
+ 0110	
10111	

```
module bcdadd(Cin, X, Y, S, Cout);
    input Cin;
    input [3:0] X, Y;
    output reg [3:0] S;
    output reg Cout;
    reg [4:0] Z;

    always@ (X, Y, Cin)
        begin
            Z = X + Y + Cin;
            if (Z < 10)
                {Cout, S} = Z;
            else
                {Cout, S} = Z + 6;
        end
    endmodule
```

16