
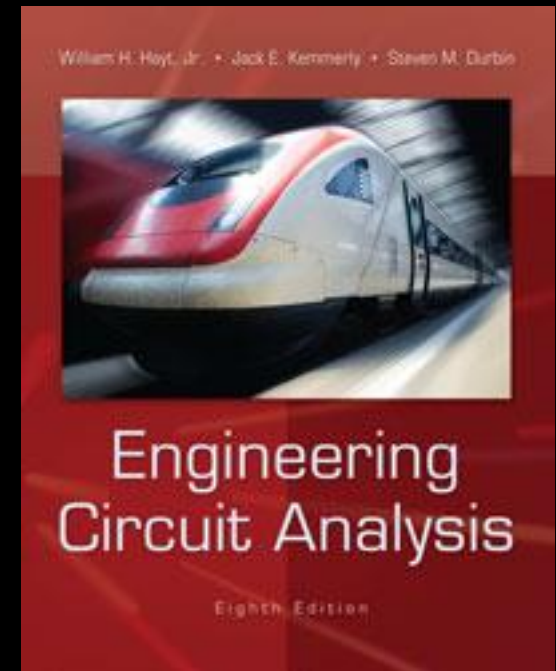


# Chapter 10

## Sinusoidal Steady-State Analysis

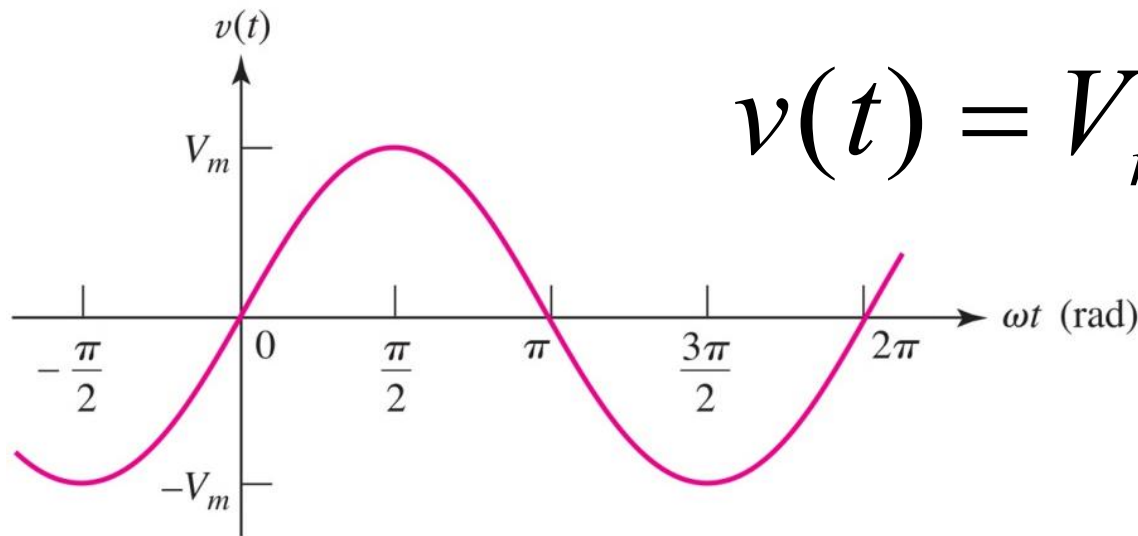


# Sinusoids: Defining Terms



$$v(t) = V_m \sin(\omega t)$$

- the *amplitude* of the wave is  $V_m$
- the *argument* is  $\omega t$
- the *radian or angular frequency* is  $\omega$
- note that  $\sin()$  is *periodic*

# Period of Sine Wave

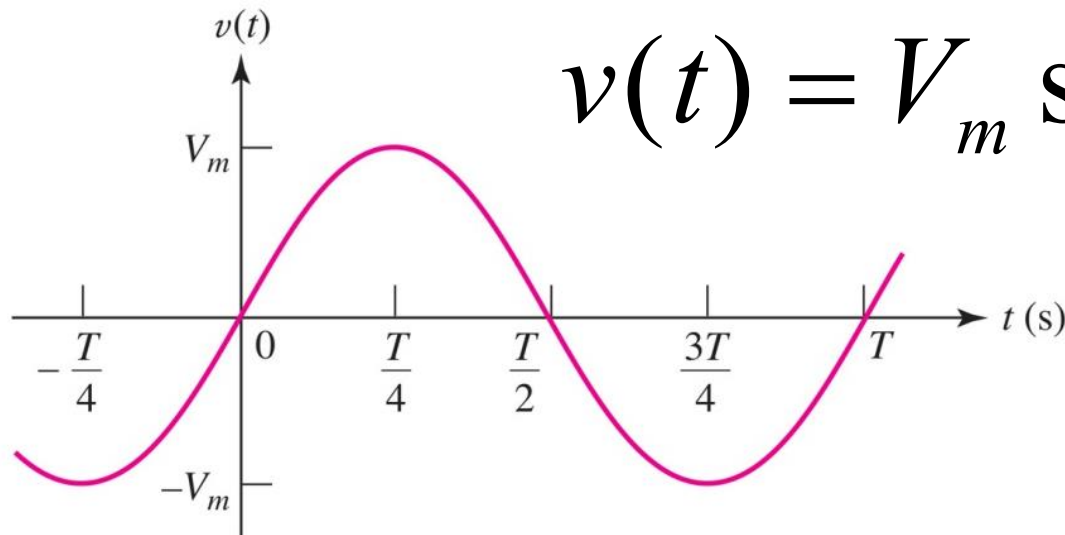


$$v(t) = V_m \sin(\omega t)$$

- the period of the wave is  $T$
- the frequency  $f$  is  $1/T$ : units Hertz (Hz)

$$f = \frac{1}{T} = \frac{\omega}{2\pi} \quad \omega = 2\pi f$$
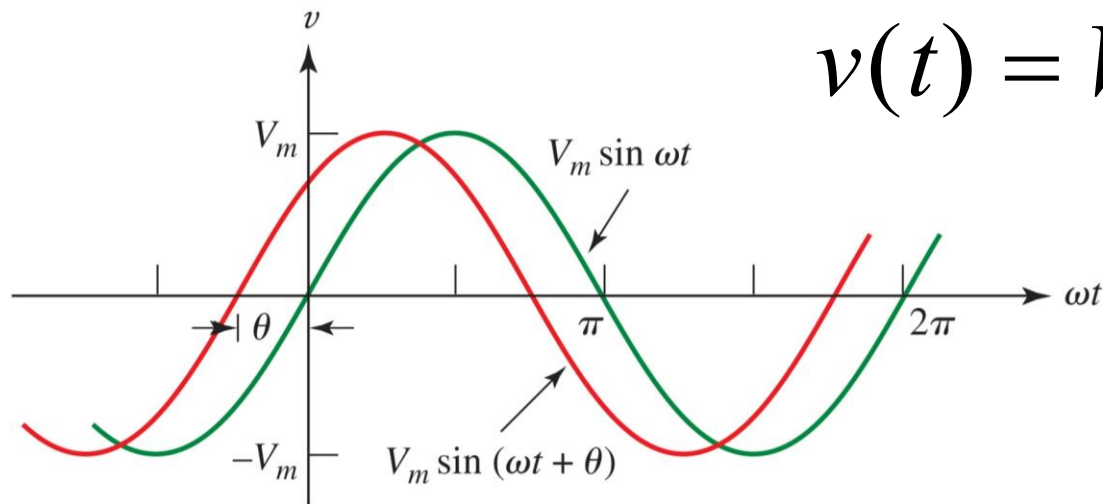
# Sine Wave Phase

A more general form of a sine wave includes a *phase*  $\theta$




$$v(t) = V_m \sin(\omega t + \theta)$$

- The new wave (in red) is said to *lead* the original (in green) by  $\theta$ .
- The original  $\sin(\omega t)$  is said to *lag* the new wave by  $\theta$ .
- $\theta$  can be in degrees or radians, but the argument of  $\sin()$  is always *radians*.
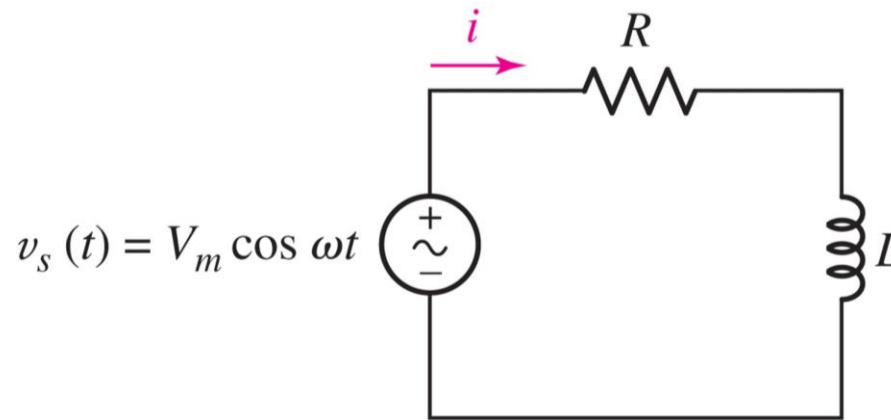
# Forced Response to Sine Sources

When the source is sinusoidal, we often ignore the transient/natural response and consider only the forced or “steady-state” response.



The source is assumed to exist forever:  $-\infty < t < \infty$

# Finding the Steady-State Response

1. Apply KVL:


$$L \frac{di}{dt} + Ri = V_m \cos(\omega t)$$

2. Make a good guess:

$$i(t) = I_1 \cos \omega t + I_2 \sin \omega t$$

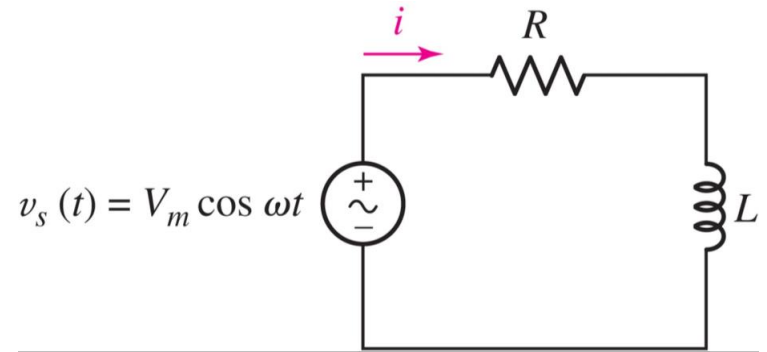
3. Solve for the constants:

$$i(t) = \frac{RV_m}{R^2 + \omega^2 L^2} \cos \omega t + \frac{\omega L V_m}{R^2 + \omega^2 L^2} \sin \omega t$$


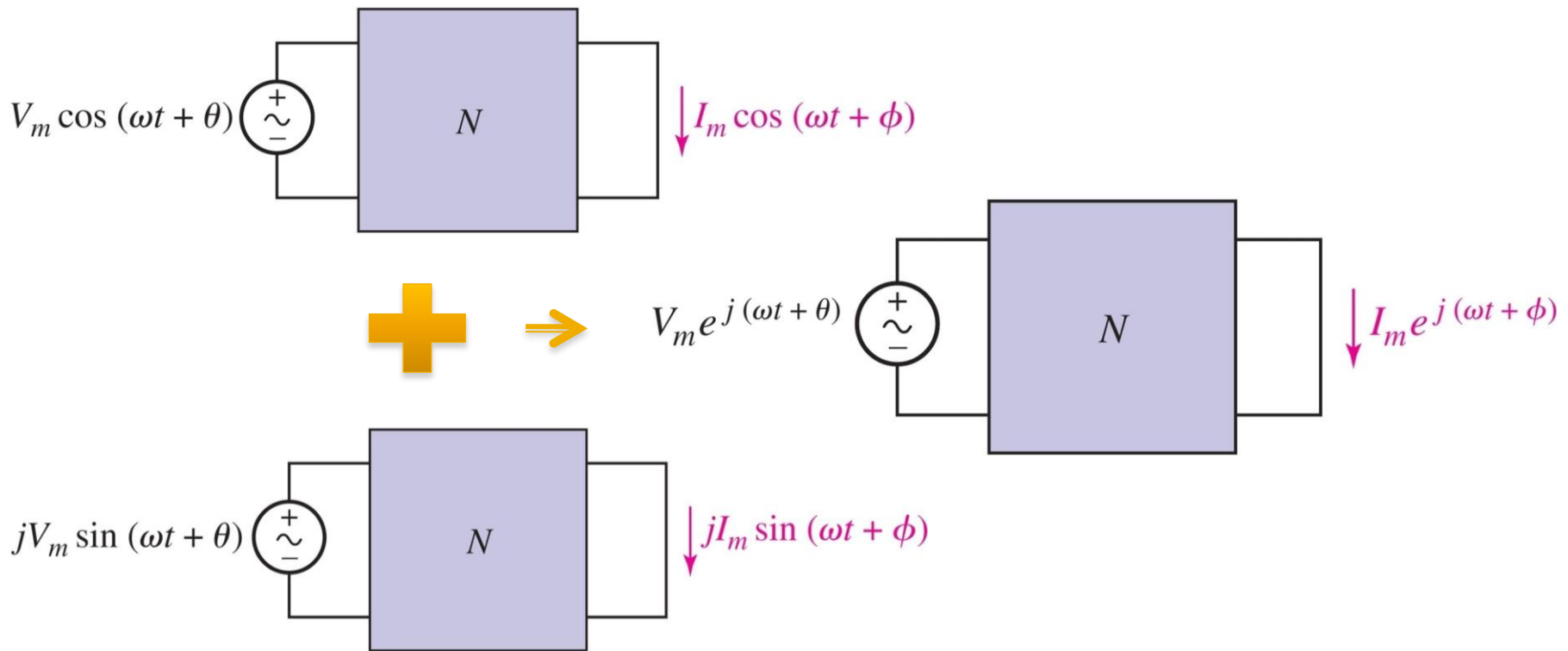
# The Complex Forcing Function


Apply superposition and use  $e^{j\theta} = \cos(\theta) + j \sin(\theta)$



# The Steady-State Response via Complex Forcing Function

1. Apply KVL, assume  $v_s = V_m e^{j\omega t}$ .

$$L \frac{di}{dt} + Ri = v_s$$

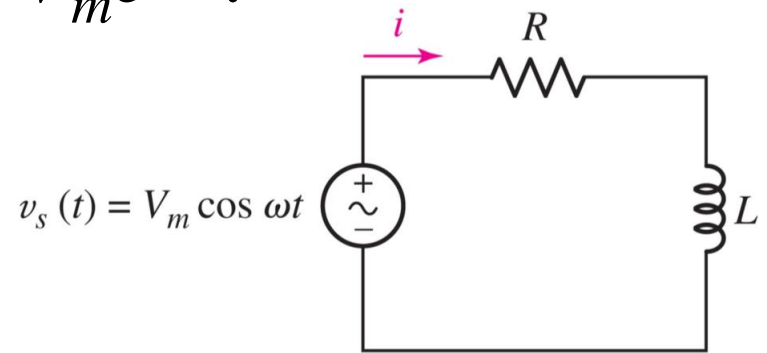

2. Find the complex response

$$i(t) = I_m e^{j\omega t + \theta}$$



3. Find  $I_m$  and  $\theta$ , (*discard the imaginary part*)

$$i(t) = I_m \cos(\omega t + \phi) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos \left( \omega t - \tan^{-1} \frac{\omega L}{R} \right)$$



# Example: Sine Wave Analysis

Find the voltage on the capacitor.

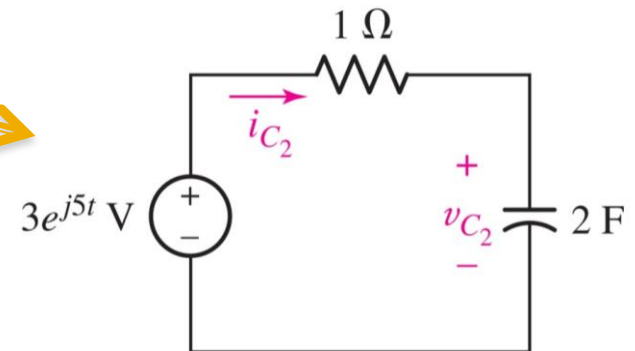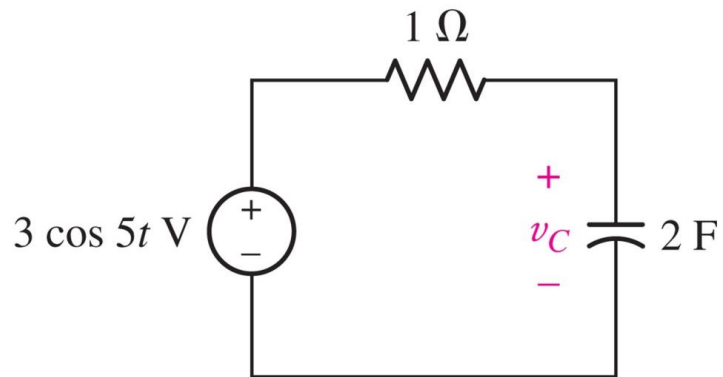


Answer:  $v_c(t) = 298.5 \cos(5t - 84.3^\circ) \text{ mV}$

# The Phasor

The term  $e^{j\omega t}$  is common to all voltages and currents and can be ignored in all intermediate steps, leading to the phasor:


$$\mathbf{I} = I_m e^{j\phi} = I_m \angle \phi$$

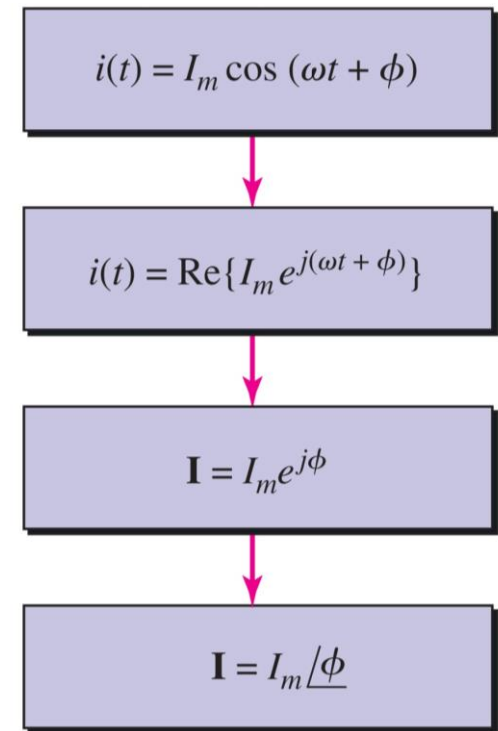The phasor representation of a current (or voltage) is in the *frequency domain*




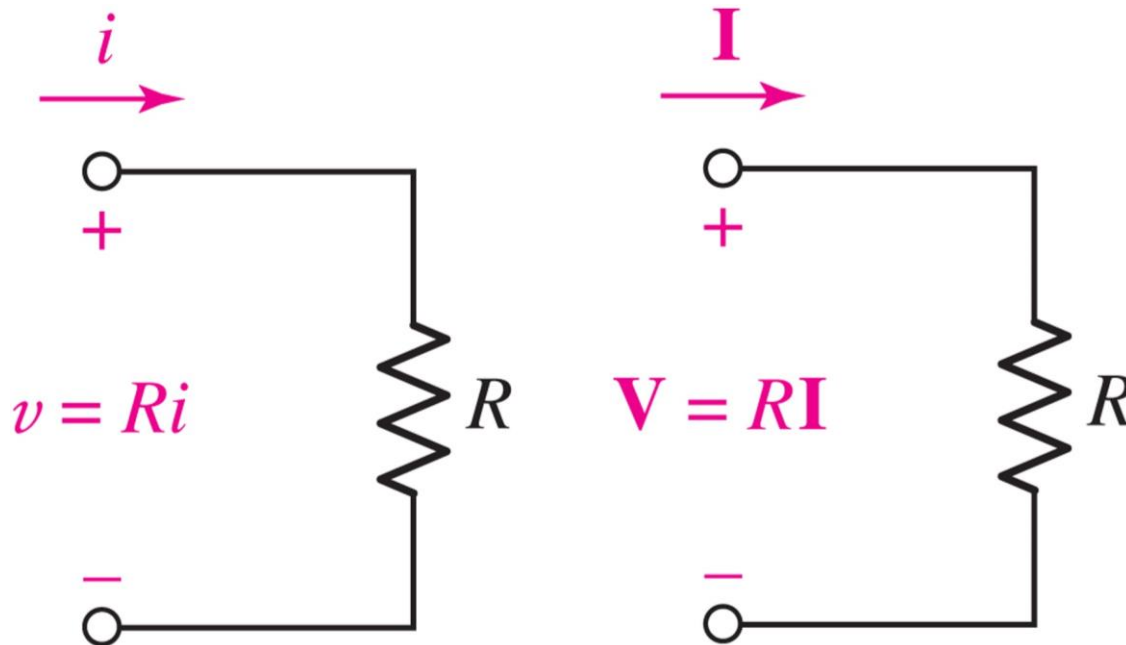
# Phasors: The Resistor

In the frequency domain, Ohm's Law takes the same form:



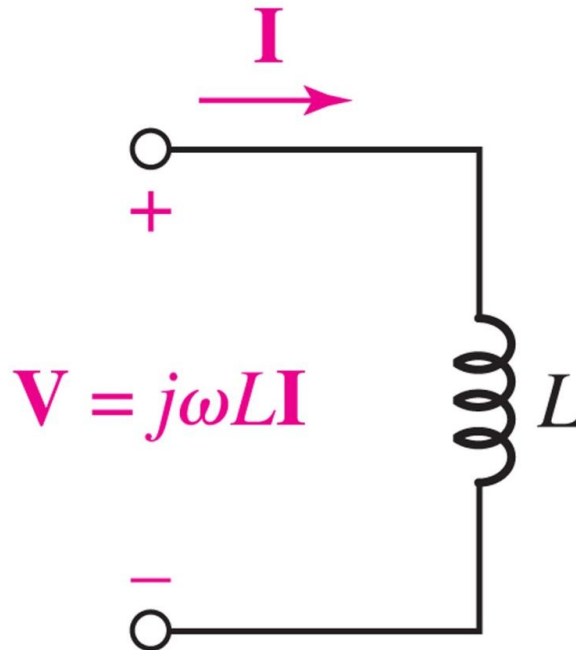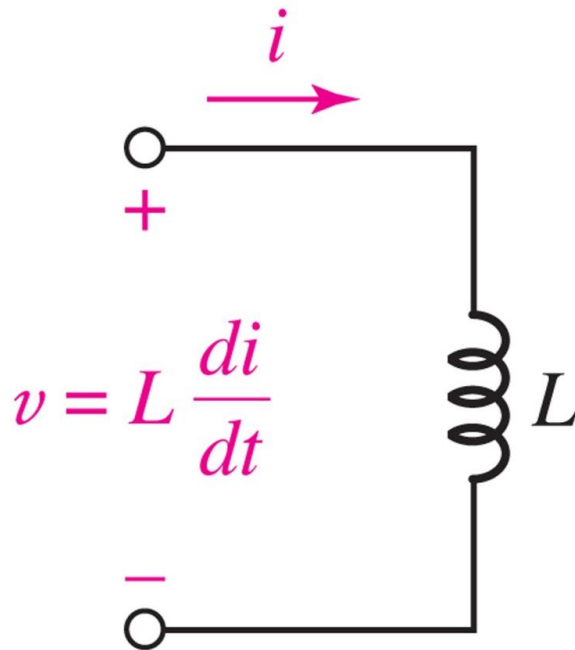
# Phasors: The Inductor

Differentiation in time becomes multiplication in phasor form: (calculus becomes algebra!)



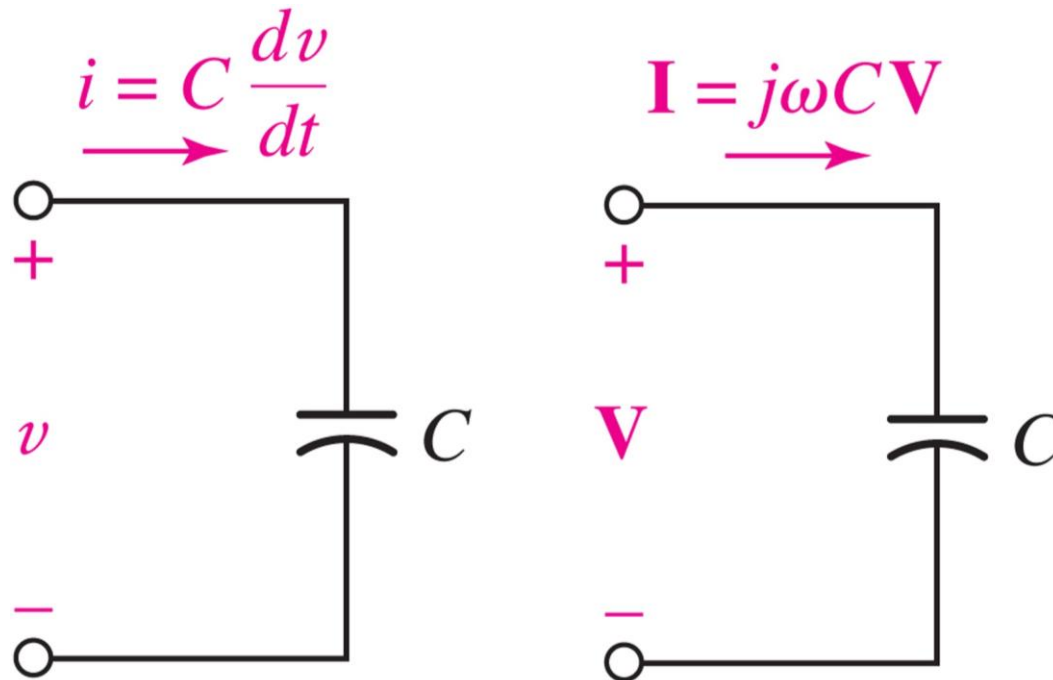
# Phasors: The Capacitor

Differentiation in time becomes multiplication in phasor form: (calculus becomes algebra!)




# Summary: Phasor Voltage/Current Relationships


## Time Domain

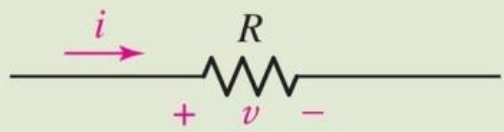

$v = Ri$

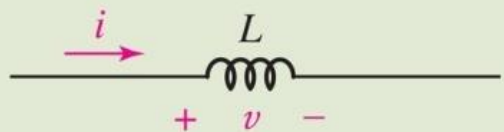

$v = L \frac{di}{dt}$

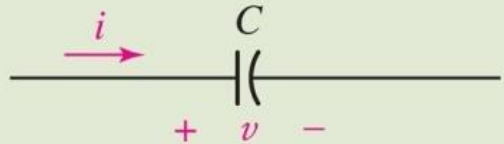


$v = \frac{1}{C} \int i dt$


Calculus (hard but real)

## Frequency Domain


$V = RI$

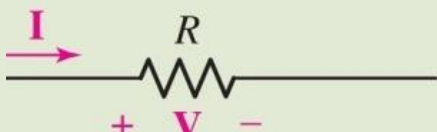

$V = j\omega LI$

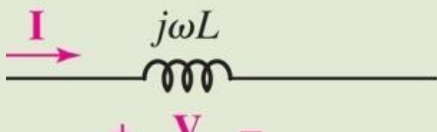

$V = \frac{1}{j\omega C} I$

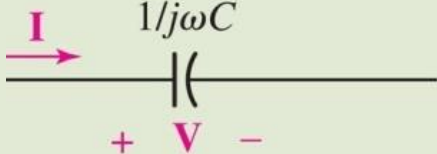

Algebra (easy but complex)

# Kirchhoff's Laws for Phasors

Applying KVL in time implies KVL for phasors:

$$V_1 + V_2 + \dots + V_N = 0$$

Applying KCL in time implies KCL for phasors:

$$I_1 + I_2 + \dots + I_N = 0$$

# Impedance

- Define impedance as  $Z=V/I$ , i.e.  $V=IZ$

$$Z_R=R$$

$$Z_L=j\omega L$$

$$Z_C=1/j\omega C$$

- Impedance is the equivalent of resistance in the frequency domain.
- Impedance is a complex number (unit ohm).
- Impedances in series or parallel can be combined using “resistor rules.”



# Impedance Relationships

- the admittance is  $Y=1/Z$

$$Y_R=1/R$$



$$Y_L=1/j\omega L$$

$$Y_C=j\omega C$$

- if  $Z=R+jX$ ;  $R$  is the *resistance*,  $X$  is the *reactance* (unit ohm  $\Omega$ )
- if  $Y=G+jB$ ;  $G$  is the *conductance*,  $B$  is the *susceptance*: (unit siemen S)
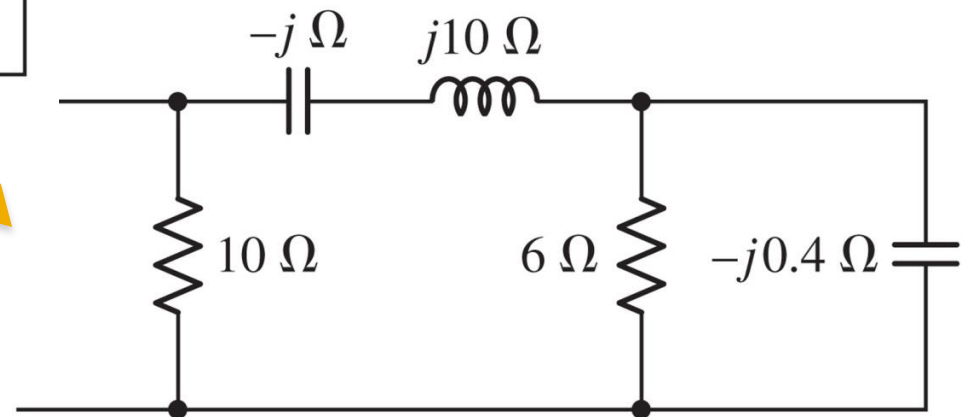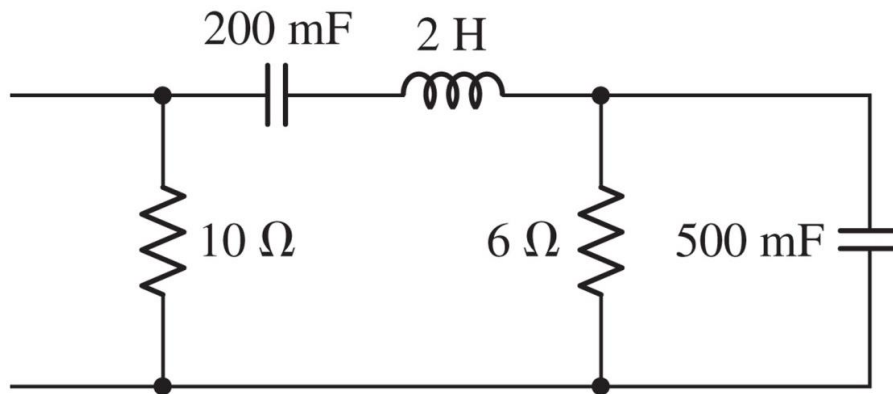
# Example: Equivalent Impedance


Find the impedance of the network at 5 rad/s.



*Answer:  $4.255 + j4.929 \Omega$*
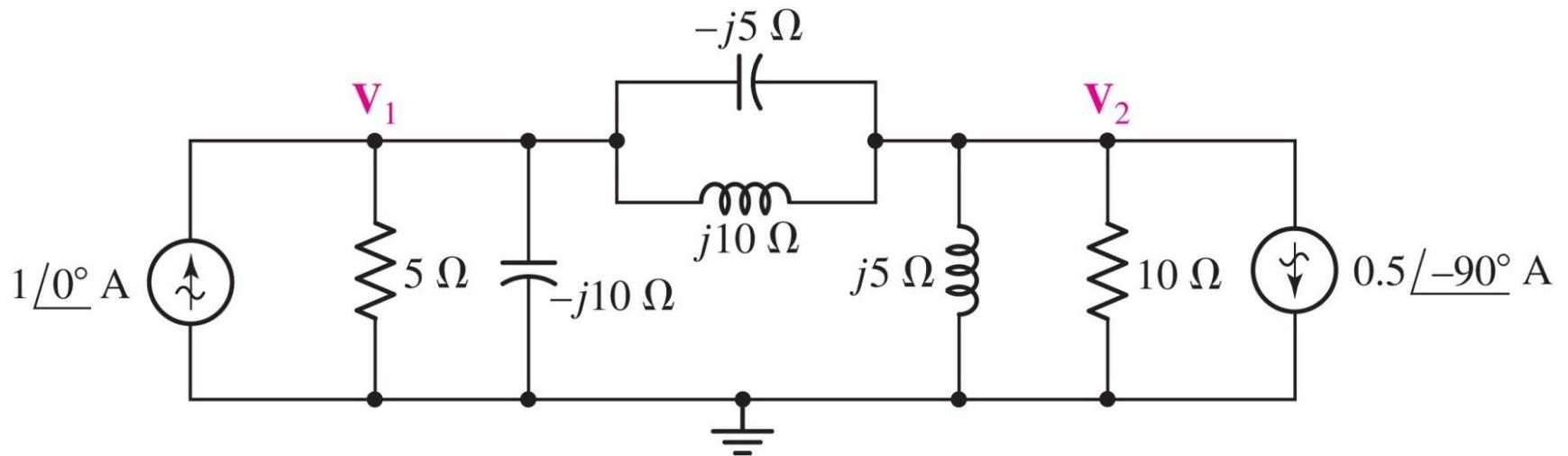
# Nodal and Mesh Analysis


Find the phasor voltages  $V_1$  and  $V_2$ .



*Answer:  $V_1 = 1 - j2 \text{ V}$  and  $V_2 = -2 + j4 \text{ V}$*
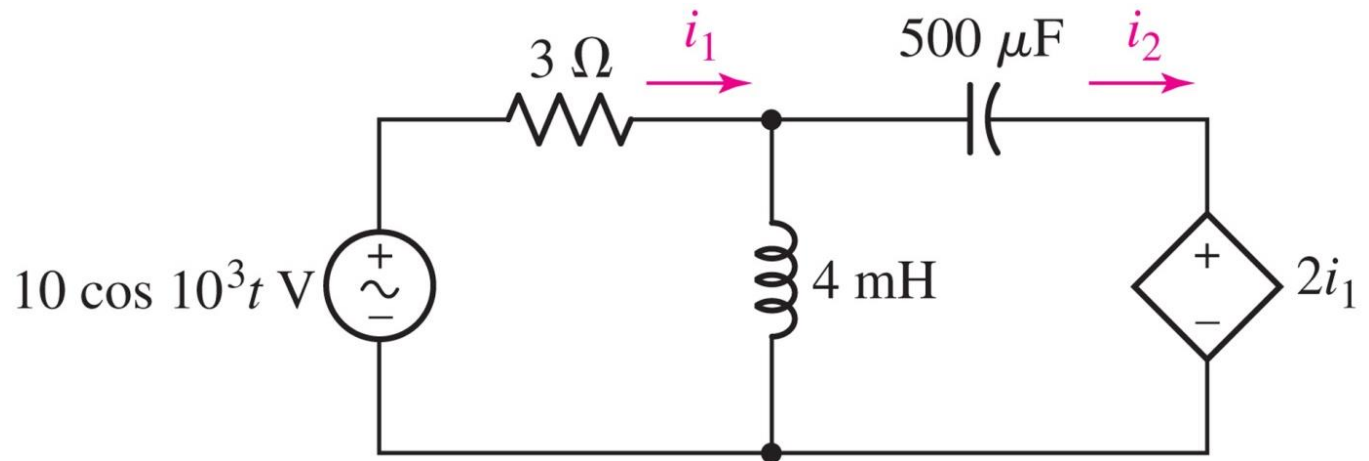
# Nodal and Mesh Analysis

Find the currents  $i_1(t)$  and  $i_2(t)$ .




*Answer:*

$$i_1(t) = 1.24 \cos(10^3 t + 29.7^\circ) \text{ A}$$

$$i_2(t) = 2.77 \cos(10^3 t + 56.3^\circ) \text{ A}$$
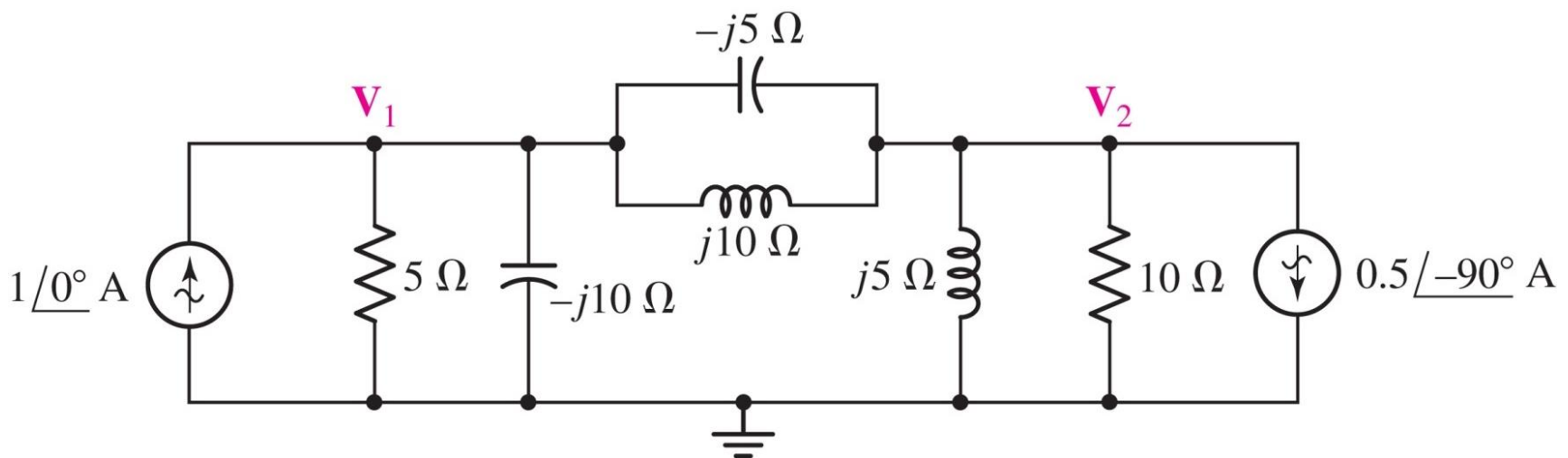
# Superposition Example

The superposition principle applies to phasors;  
use it to find  $V_I$ .




*Answer:*  $V_I = V_{IL} + V_{IR} = (2 - j2) + (-1) = 1 - j2 \text{ V}$

# Thévenin Example


Thévenin's theorem also applies to phasors; we can use it to find  $V_I$ .

The setup is shown below:

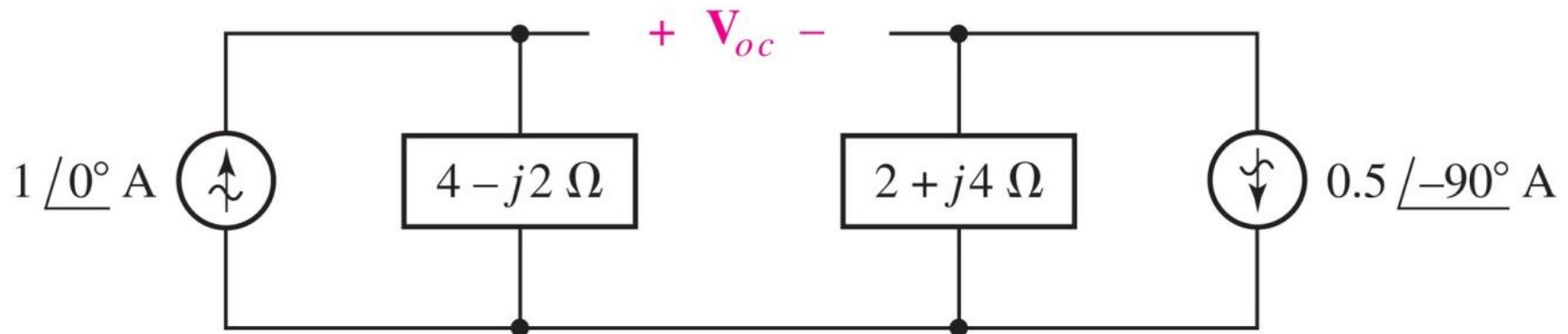


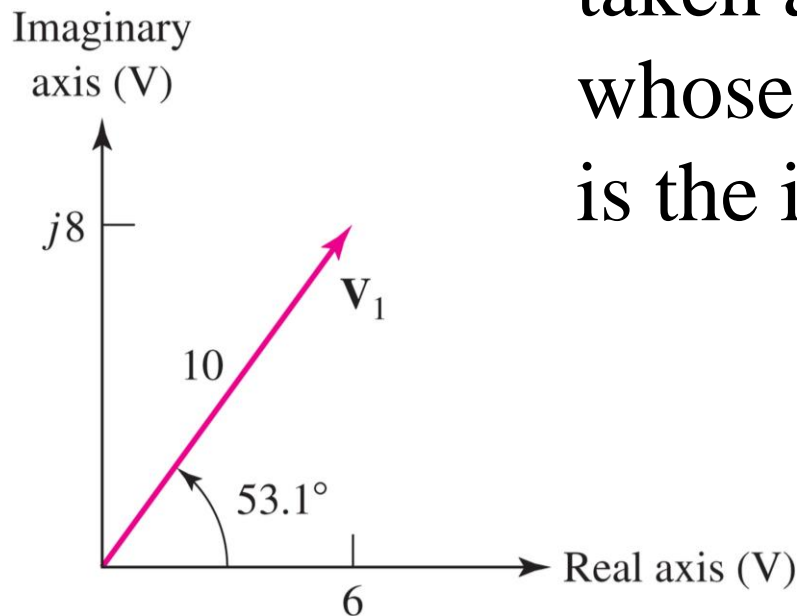
# Phasor Diagrams

The arrow for the phasor  $\mathbf{V}$  on the phasor diagram is a photograph, taken at  $\omega t = 0$ , of a rotating arrow whose projection on the real axis is the instantaneous voltage  $v(t)$ .


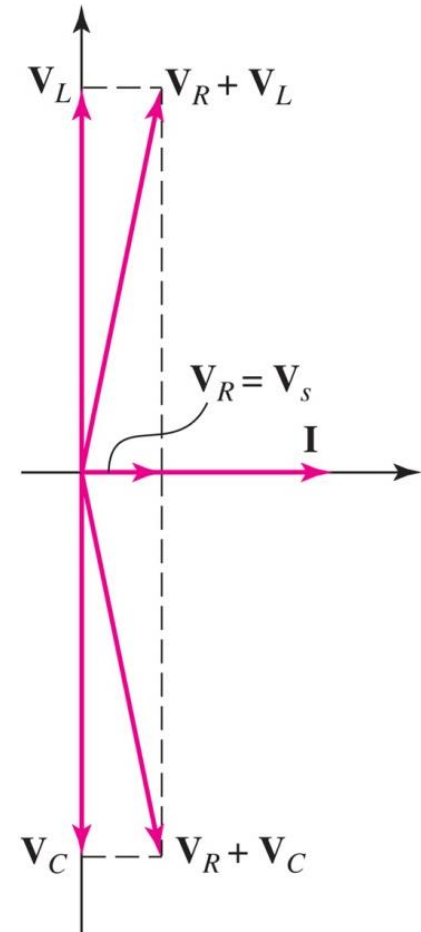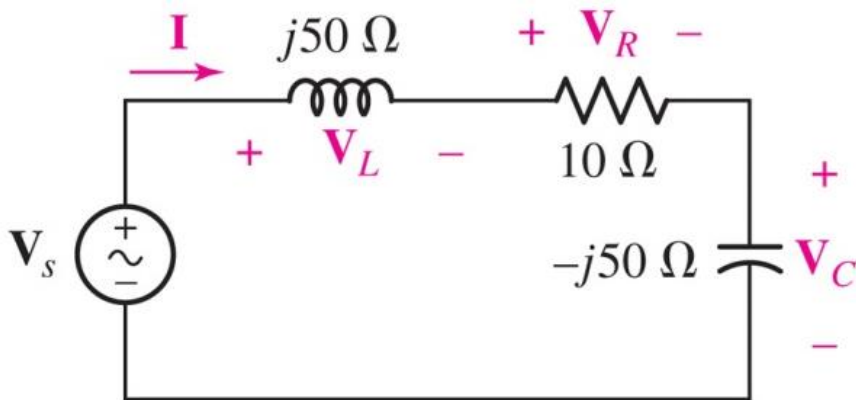
# Example Phasor Diagram

If we assume  $\mathbf{I} = 1 \angle 0^\circ$  A





# Phasor Diagram: Parallel RLC

Assume  $\mathbf{V} = 1 \angle 0^\circ \text{ V}$

