

EEE116 Experimental, Computer Skills and Sustainability


Week 3 Digital clock pre-lab tutorial



Xi'an Jiaotong-Liverpool University

西交利物浦大學

Processing of Time Information

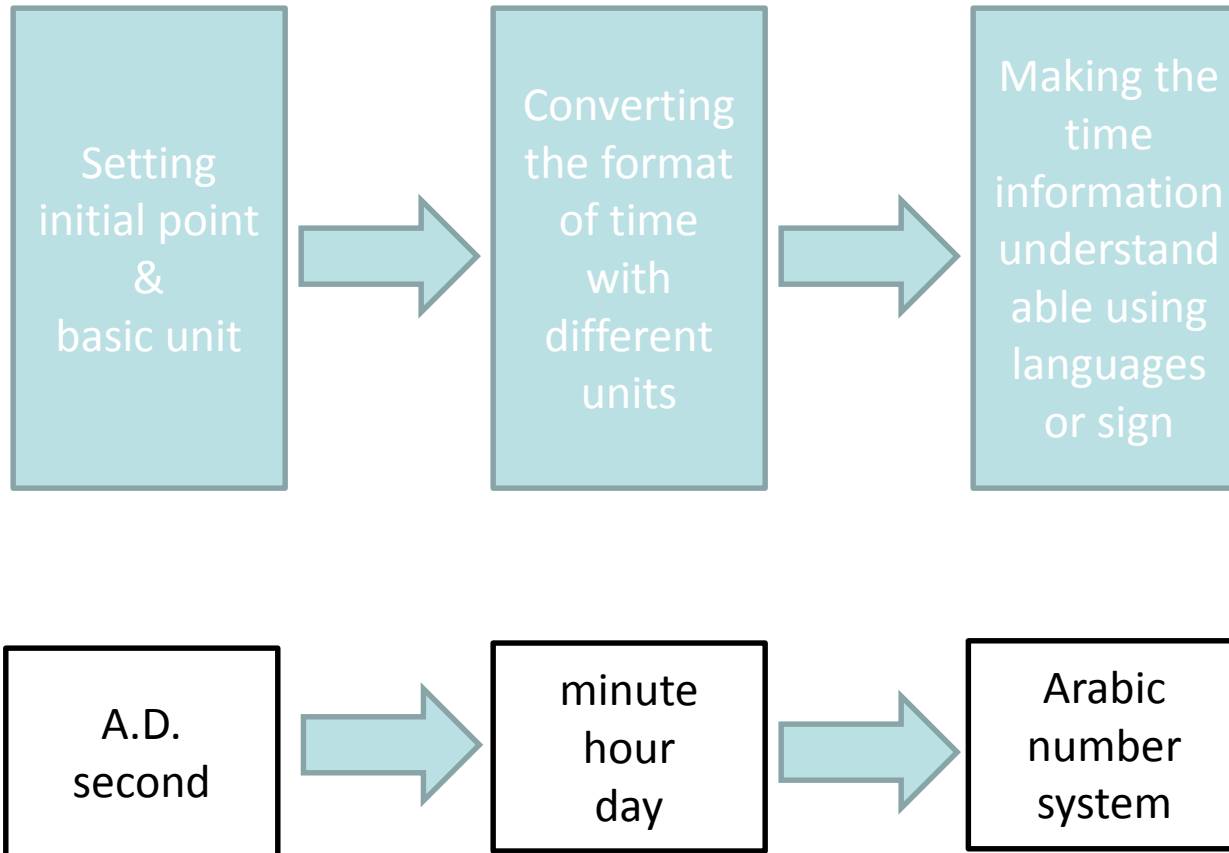

To design a digital clock which can be started, stopped and reset. It should be able to count up to a certain number, such as, 59 seconds (i.e. from 0,1,2,3....57, 58, 59, 0, 1, 2, 3....) and output the seconds by a pair of 7-segment LED displays.

This is a design project, there is no step by step instruction for you to follow.

Functional blocks

To start on the design of your clock, break the whole system down into functional blocks such as the timing generator, the decoder, the display, the set logic, etc.

Complete design

Specify how the functional blocks interface with each other. At this point you can have a completed design with a full schematic in Multisim or online simulation tools. (Optional)

<https://circuits.io>




Building and testing

A good approach is to build each of your functional blocks from milestone M1 and test them independently. For example, use a function generator as input signal for a block and look at the output of the block using the oscilloscope.

Demonstration of Working Clock.

You must demonstrate your working clock to your TA before the end of the lab. Take a short video clip for your work (as backup).

Basic Structure

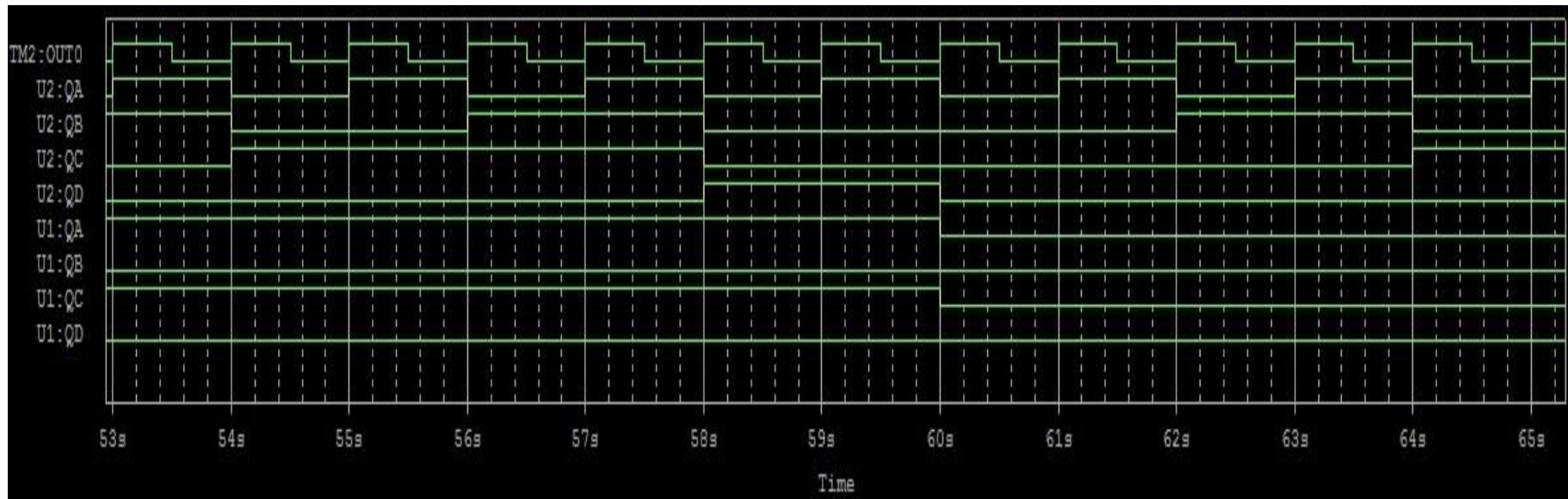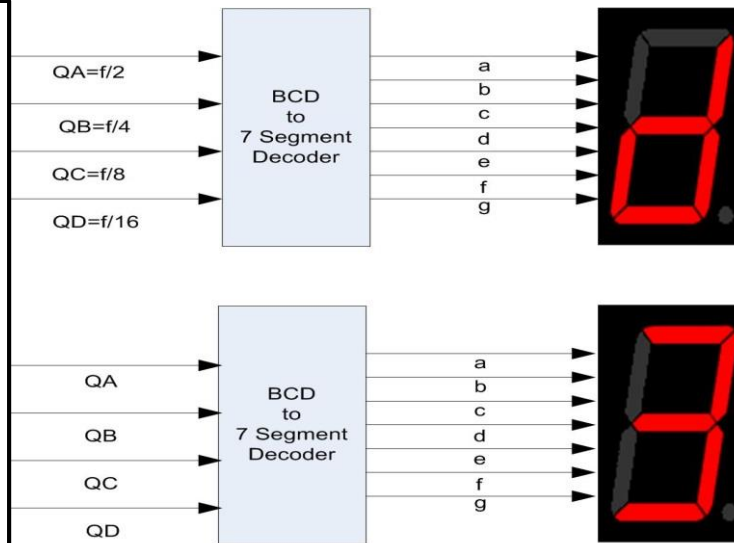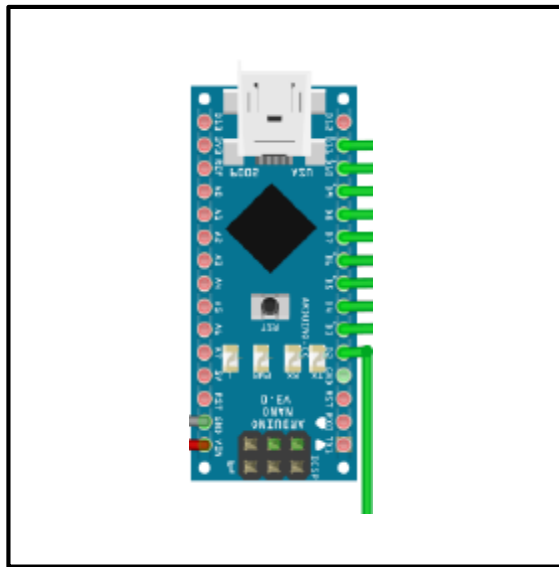

Generate time signal from Arduino




```
SingleDig_0_to_10_v1 | Arduino 1.8.1
File Edit Sketch Tools Help
SingleDig_0_to_10_v1 $
int inputs[4] = {8,9,10,11}; // A,B,C,D inputs
byte BCD[16][4] ={{0,0,0,0},
{1,0,0,0},
{0,1,0,0},
{1,1,0,0},
{0,0,1,0},
{1,0,1,0},
{0,1,1,0},
{1,1,1,0},
{0,0,0,1},
{1,0,0,1},
{0,1,0,1},
{1,1,0,1},
{0,0,1,1},
{1,0,1,1},
{0,1,1,1},
{1,1,1,1}}; //BCD code

void setup() {
  for(int a = 0; a < 4; a++){
    pinMode(inputs[a], OUTPUT);} //set outputs
  }
  void loop() {
    static int num = 0;
    for(int c = 0; c < 4; c++){
      digitalWrite(inputs[c], BCD[num][c]);
    }
    num++;
    num = num % 10;
    delay(1000);}
  }
```




```
digitalNum | Arduino 1.8.1
File Edit Sketch Tools Help
digitalNum
void setup() {
  // put your setup code here, to run once:
  pinMode(9, OUTPUT);
  pinMode(10, OUTPUT);
  pinMode(11, OUTPUT);
  pinMode(12, OUTPUT);
}

void loop() {
  static int num = 0;
  // put your main code here, to run repeatedly:
  digitalWrite(9, !(num & (0x01<<0)));
  digitalWrite(10, !(num & (0x01<<1)));
  digitalWrite(11, !(num & (0x01<<2)));
  digitalWrite(12, !(num & (0x01<<3)));
  num++;
  num = num % 10;
  delay(1000);}
}
```

Breadboard

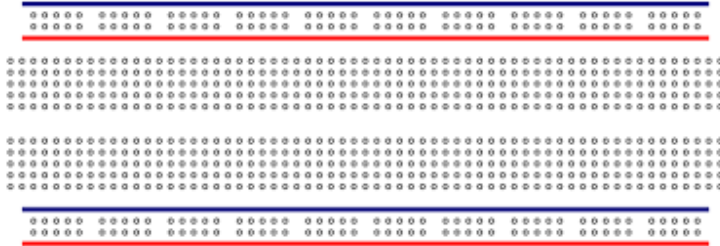


Schematic diagram

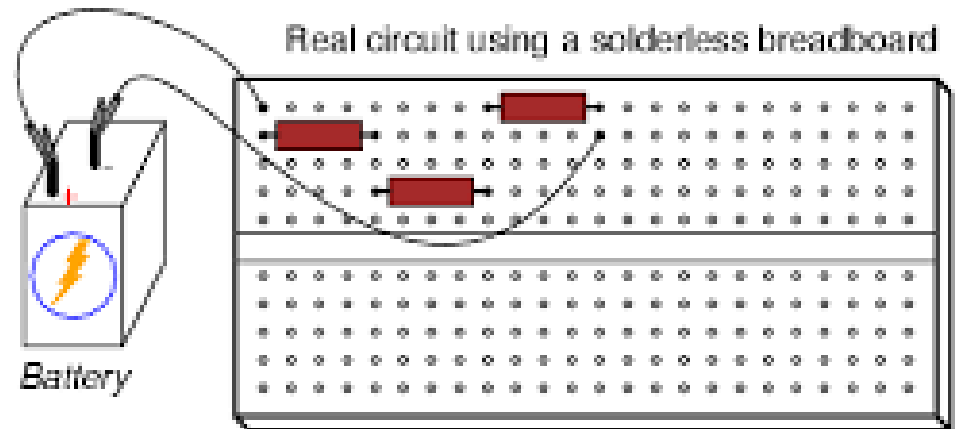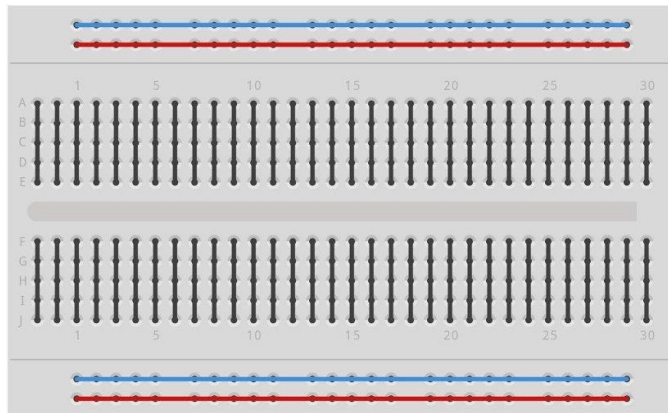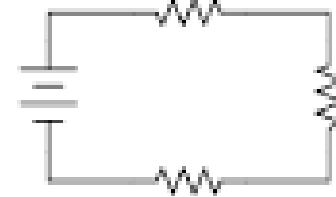

Use DC power supply on your bench to power the circuit and arduino, don't use Arduino as power source. (to protect your Arduino and your laptop)

Connect 5V to the **red line** and Ground to the **blue line**.

BCD-7 Segment Decoder

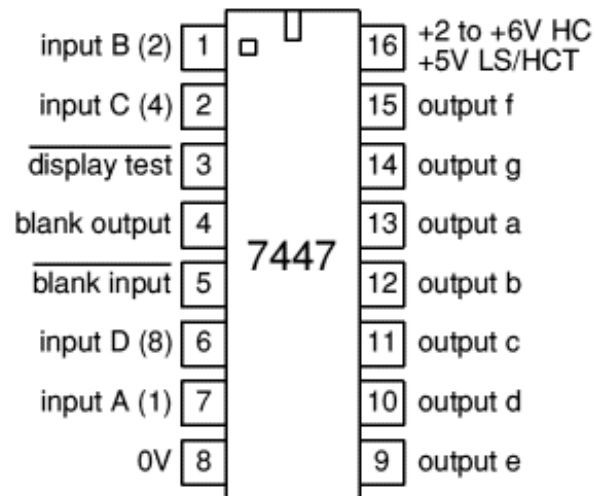

BCD--Binary Coded Decimal

- Before signals go to LED, a 330ohms **resistor** is needed for each output of 7447 (To limit the current, protect the LED light and your eyes)
- Every IC need to be powered. Connect **Vcc (Pin 16) to 5V**, and **GND (Pin 8) to ground**.

Read the datasheet



SN5446A, '47A, '48, SN54LS47, 'LS48, 'LS49 SN7446A, '47A, '48, SN74LS47, 'LS48, 'LS49 BCD-TO-SEVEN-SEGMENT DECODERS/DRIVERS SOL5111 - MARCH 1974 - REVISED MARCH 1988

'46A, '47A, 'LS47 feature

- Open-Collector Outputs Drive Indicators Directly
- Lamp-Test Provision
- Leading/Trailing Zero Suppression


'48, 'LS48 feature

- Internal Pull-Ups Eliminate Need for External Resistors
- Lamp-Test Provision
- Leading/Trailing Zero Suppression


'LS49 feature

- Open-Collector Outputs
- Blanking Input

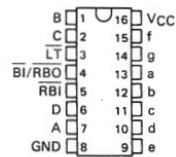
SN5446A, SN5447A, SN54LS47, SN5448,
SN54LS48 . . . J PACKAGE
SN7446A, SN7447A,
SN7448 . . . N PACKAGE
SN74LS47, SN74LS48 . . . D OR N PACKAGE
(TOP VIEW)



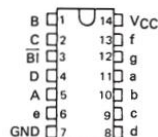
SN54LS49 . . . J OR W PACKAGE
SN74LS49 . . . D OR N PACKAGE
(TOP VIEW)



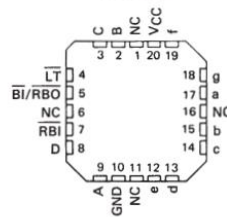SN54LS47, SN54LS48 . . . FK PACKAGE
(TOP VIEW)



SN54LS49 . . . FK PACKAGE
(TOP VIEW)

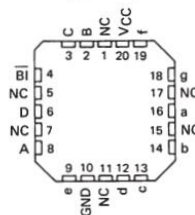

NC - No internal connection

description

The '46A, '47A, and 'LS47 feature active-low outputs designed for driving common-anode LEDs or incandescent indicators directly. The '48, 'LS48, and 'LS49 feature active-high outputs for driving lamp buffers or common-cathode LEDs. All of the circuits except 'LS49 have full ripple-blanking input/output controls and a lamp test input. The 'LS49 circuit incorporates a direct blanking input. Segment identification and resultant displays are shown below. Display patterns for BCD input counts above 9 are unique symbols to authenticate input conditions.

The '46A, '47A, '48, 'LS47, and 'LS48 circuits incorporate automatic leading and/or trailing-edge zero-blanking control (RBI and RBO). Lamp test (LT) of these types may be performed at any time when the BI/RBO node is at a high level. All types (including the '49 and 'LS49) contain an overriding blanking input (BI), which can be used to control the lamp intensity by pulsing or to inhibit the outputs. Inputs and outputs are entirely compatible for use with TTL logic outputs.

The SN54246/SN74246 and '247 and the SN54LS247/SN74LS247 and 'LS248 compose the 6 and the 9 with tails and were designed to offer the designer a choice between two indicator fonts.



SEGMENT IDENTIFICATION



NUMERICAL DESIGNATIONS AND RESULTANT DISPLAYS

'46A, '47A, 'LS47 FUNCTION TABLE (T1)

DECIMAL OR FUNCTION	INPUTS						BI/RBO†	OUTPUTS							NOTE
	LT	RBI	D	C	B	A		a	b	c	d	e	f	g	
0	H	H	L	L	L	L	H	ON	ON	ON	ON	ON	ON	OFF	1
1	H	X	L	L	L	H	H	OFF	ON	OFF	OFF	OFF	OFF	OFF	
2	H	X	L	L	H	L	H	ON	ON	OFF	ON	ON	OFF	ON	
3	H	X	L	L	H	H	H	ON	ON	ON	OFF	OFF	OFF	ON	
4	H	X	L	H	L	L	H	OFF	ON	ON	OFF	OFF	ON	ON	
5	H	X	L	H	L	H	H	ON	OFF	ON	ON	OFF	ON	ON	
6	H	X	L	H	H	L	H	OFF	OFF	ON	ON	ON	ON	ON	
7	H	X	L	H	H	H	H	ON	ON	ON	OFF	OFF	OFF	OFF	
8	H	X	H	L	L	L	L	H	ON	ON	ON	ON	ON	ON	
9	H	X	H	L	L	H	H	ON	ON	ON	OFF	OFF	ON	ON	
10	H	X	H	L	H	L	H	OFF	OFF	OFF	ON	ON	OFF	ON	
11	H	X	H	L	H	H	H	OFF	OFF	ON	ON	OFF	OFF	ON	
12	H	X	H	H	L	L	L	H	OFF	ON	OFF	OFF	ON	ON	
13	H	X	H	H	L	H	H	ON	OFF	OFF	ON	OFF	ON	ON	
14	H	X	H	H	H	L	H	OFF	OFF	OFF	ON	ON	ON	ON	
15	H	X	H	H	H	H	H	OFF	OFF	OFF	OFF	OFF	OFF	OFF	
BI	X	X	X	X	X	X	L	OFF	OFF	OFF	OFF	OFF	OFF	OFF	2
RBI	H	L	L	L	L	L	L	OFF	OFF	OFF	OFF	OFF	OFF	OFF	3
LT	L	X	X	X	X	X	H	ON	ON	ON	ON	ON	ON	ON	4

H = high level, L = low level, X = irrelevant

NOTES: 1. The blanking input (BI) must be open or held at a high logic level when output functions 0 through 15 are desired. The

other input.




2. When a low logic level is applied directly to the blanking input (BI), all segment outputs are off regardless of the level of any other input.

3. When ripple-blanking input (RBI) and inputs A, B, C, and D are at a low level with the lamp test input high, all segment outputs go off and the ripple-blanking output (RBO) goes to a low level (response condition).

4. When the blanking input/ripple blanking output (BI/RBO) is open or held high and a low is applied to the lamp-test input, all segment outputs are on.

† BI/RBO is wire AND logic serving as blanking input (BI) and/or ripple-blanking output (RBO).

7 Segment Indicator

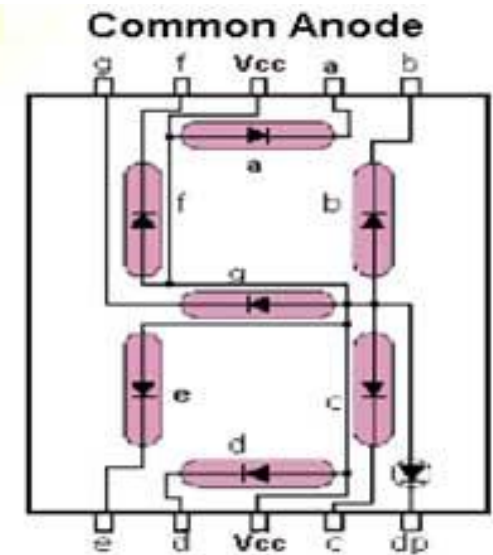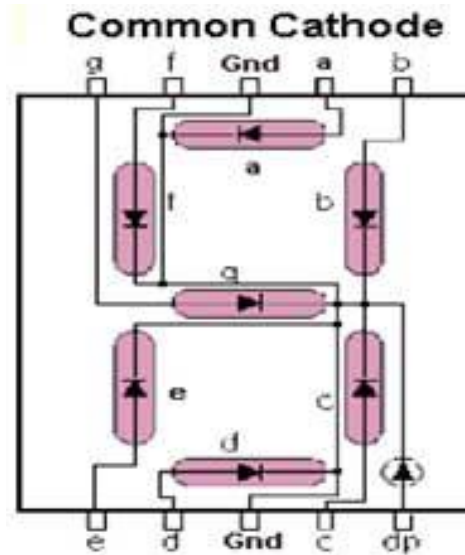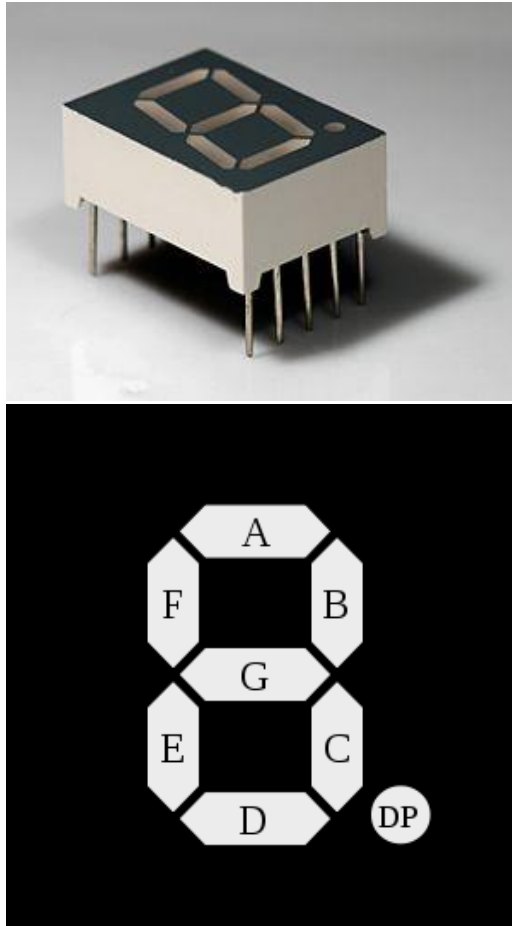

How to light up number '7' in Common Cathode LED.




a	b	c	d	e	f	g
1	1	1	0	0	0	0

How to light up number '4' in Common Anode LED ?


Using switch



6pin self-locking push button switch

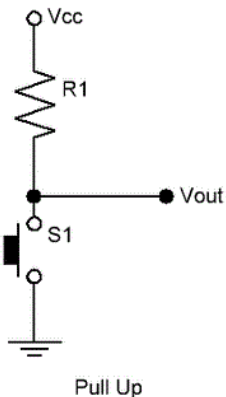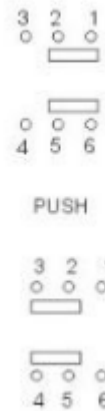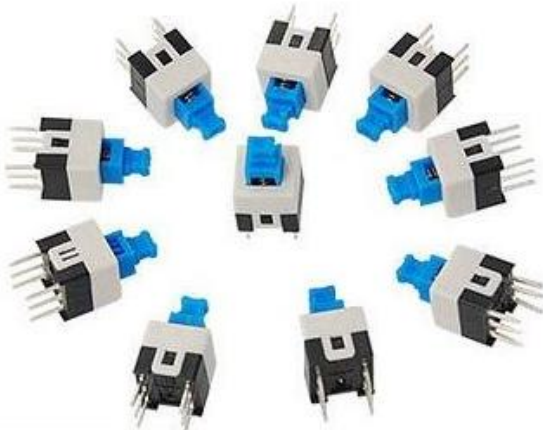

Pull Up

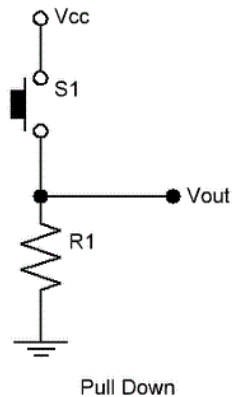

Pull Down

```
digitalRead_key | Arduino 1.8.1
File Edit Sketch Tools Help
digitalRead_key $
void setup() {
  Serial.begin(9600);
  pinMode(7, INPUT); //Stop key
  pinMode(6, INPUT); //Reset key
}
void loop() {
  int StopKey = digitalRead(7);
  int ResetKey = digitalRead(6);

  Serial.print("Stop Key"); //test Only
  Serial.println(StopKey); //click the serial monitor to see
                          //the value of this variable
  Serial.print("Reset Key"); //test Only
  Serial.println(ResetKey); //test Only
}
```

A Pull up or Pull down **Resistor**
MUST (around 10K Ω) be used.

1. Two digit displays:

Your clock has to display two digit numbers. Each digit should roll over at a certain time.

The roll over time is your group number, if you are group number is single digit, then your roll over time is 50 + group number.

For example,

- You are in group B34, roll over time is 34. Your clock should count 33, 34, 00, 01, 02 ...
- You are in group A05, roll over time is $50+05=55$. Your clock should count 54, 55, 00, 01, 02 ...

2. Pause and reset:

Your clock must can be stopped and reset by press bottoms.

On behalf of the whole team, the team leader should upload **one** video clip to ICE.

MAXIMUM SIZE FOR UPLOADING: 20MB

Week	Lab name	Student group	Assessment
Week-8	Digital clock	Group A	Bench inspection for Digital clock (Group A)
	Matlab computer lab 2	Group B	
Week-9	Digital clock	Group B	Bench inspection for Digital clock (Group B)
	Matlab computer lab 2	Group A	

Assessment (5%)

Group marks - Bench inspection			Total
Two-digit roll over (2%)	Stop and reset (2%)	Circuit layout (1%)	5%

Bench inspection: demonstration of stopwatch **function** and circuit **layout**.