

EEE104 – Digital Electronics (I)

Lecture 12

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

1


In This Session

- Functions of Combinational Logic Gates
 - Encoders
 - Multiplexers
 - Demultiplexers

2

Encoders

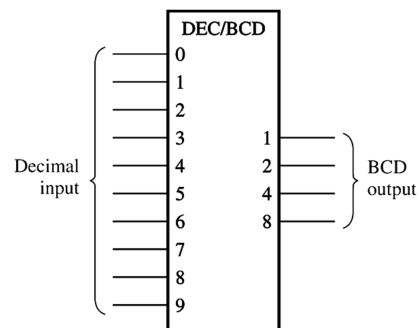- *Encoding* is the process of converting from familiar symbols or numbers to a coded format.
- An encoder performs a “reverse” decoder function.



The Decimal-to-BCD Encoder:

If any input is high, it will output a BCD code for that decimal digit, e.g. 4 to 0100.

3

Encoders

The Decimal-to-BCD Encoder

DECIMAL DIGIT	BCD CODE			
	A ₃	A ₂	A ₁	A ₀
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

$$A_3 = 8 + 9$$

$$A_2 = 4 + 5 + 6 + 7$$

$$A_1 = 2 + 3 + 6 + 7$$


$$A_0 = 1 + 3 + 5 + 7 + 9$$

So an OR gate can be used for each output.

4

Encoders

An MSI Decimal-to-BCD Encoder – 74HC147

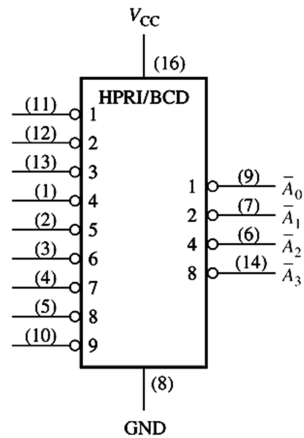


- Active-LOW inputs and outputs.
- A *priority encoder*: when more than one inputs are active, the highest-order decimal digit input will be active.

5


Encoders

Applications:
A keyboard encoder

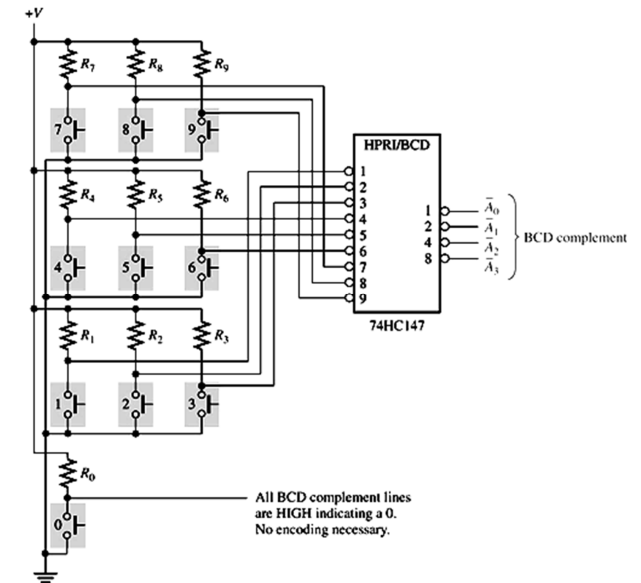

Multiplexers

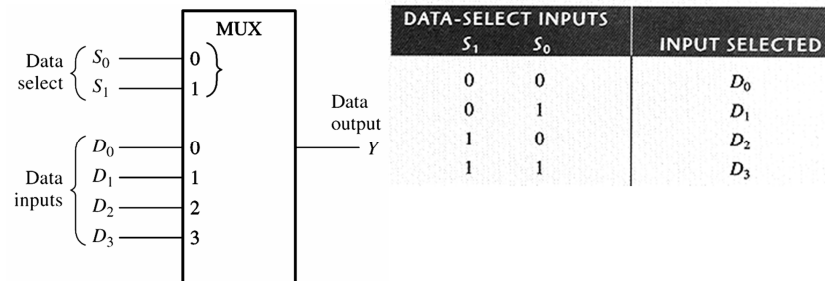
- A *multiplexer (MUX)*, also known as a *data selector*, outputs one of its multiple data inputs.
- The *data select* inputs will decide which data input is to be switched to the output line.



7

Multiplexers

DATA-SELECT INPUTS		INPUT SELECTED
S_1	S_0	
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

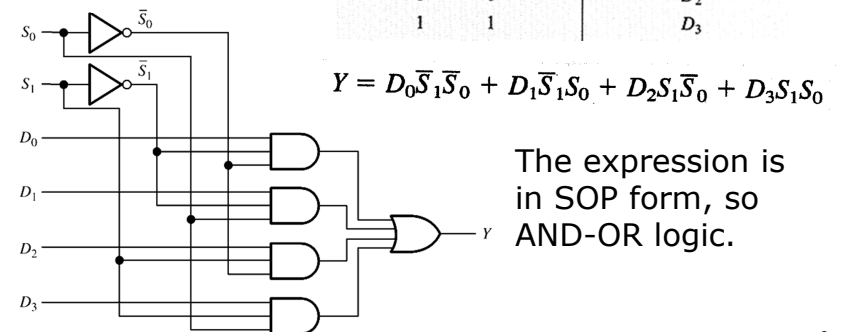


The expression is in SOP form, so AND-OR logic.

8

Multiplexers

MSI 8-Input Multiplexers

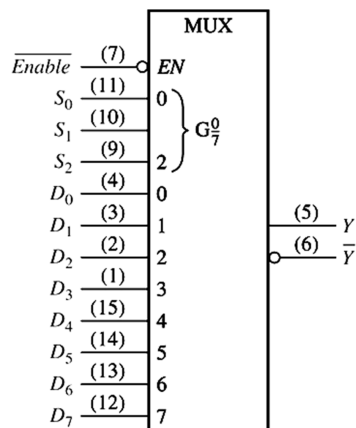- When EN is LOW, the selected data input appears in Y.
- When EN is HIGH, Y is LOW and /Y is HIGH.




9

Multiplexers

Application Examples: A Logic Function Generator

Inputs			Output
A_2	A_1	A_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0
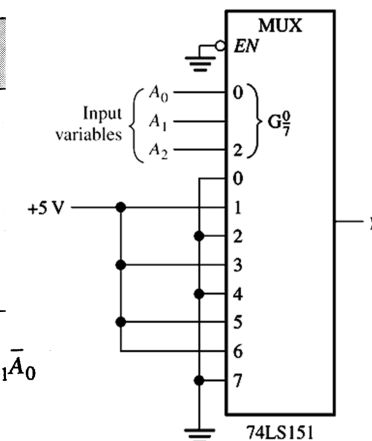
$$Y = \bar{A}_2 \bar{A}_1 A_0 + \bar{A}_2 A_1 A_0 + A_2 \bar{A}_1 A_0 + A_2 A_1 \bar{A}_0$$



10

Multiplexers

Decimal Digit	A_3	A_2	A_1	A_0	Output Y
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	1

Application Examples:

A 4-Variable Logic Function Generator

The $A_3 A_2 A_1$ are used as data select inputs.

For each pair of rows:

- A_0 01 Y 00 : $Y = 0$
- A_0 01 Y 11 : $Y = 1$
- A_0 01 Y 01 : $Y = A_0$
- A_0 01 Y 10 : $Y = \bar{A}_0$


11

Multiplexers

Application Examples:

4-Variable Logic Function Generator


$A_3 A_2 A_1$	Y
000	A_0
001	\bar{A}_0
010	A_0
011	1
100	\bar{A}_0
101	\bar{A}_0
110	1
111	A_0

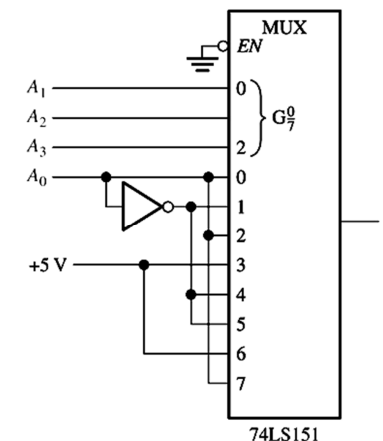

12


Demultiplexers

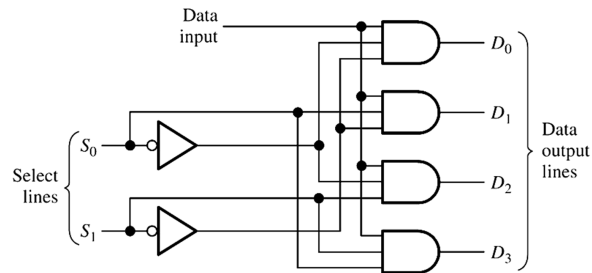- A *demultiplexer (DEMUX)* takes data from one line and distributes them to one of the output lines.
- It reverses the multiplexing function.



13

Demultiplexers

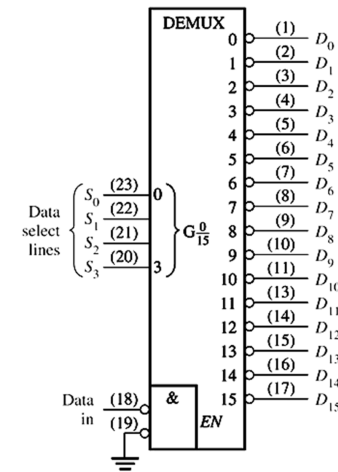

74HC154 (a 4-line-to-16-line decoder) can also be used as an MSI demultiplexer.

The data is input to chip select pins.

14

Demultiplexers

- MUXs and DEMUXs are often used when data from *multiple sources* are to be transmitted over *one line* and redictributed to *multiple destinations*.

