

# EEE205 – Digital Electronics (II)

## Lecture 6

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

1

## In This Session

### Combinational Logic in AHDL


- AHDL Decoders and Encoders
- AHDL MUX and DEMUX
- AHDL Comparators
- ADHL Adders

2
 
## AHDL Decoders

74LS138 — a 3-to-8 decoder or a 1-in-8 decoder:

- The outputs are active-LOW.
- The decoder responds to the input code only when  $\bar{E}_1 = \bar{E}_2 = 0$  and  $E_3 = 1$ .



$\bar{E}_1$	$\bar{E}_2$	$E_3$	Outputs
0	0	1	Respond to input code $A_2A_1A_0$
1	X	X	Disabled – all HIGH
X	1	X	Disabled – all HIGH
X	X	0	Disabled – all HIGH

3

```
1  SUBDESIGN fig9_52
2  (
3      a[2..0]           :INPUT;      -- binary inputs
4      e3, e2bar, e1bar   :INPUT;      -- enable inputs
5      y7,y6,y5,y4,y3,y2,y1,y0 :OUTPUT; -- decoded outputs
6  )
7  VARIABLE
8      enable             :NODE;
9  BEGIN
10     DEFAULTS
11         y7=VCC;y6=VCC;y5=VCC;y4=VCC;
12         y3=VCC;y2=VCC;y1=VCC;y0=VCC; -- defaults all HIGH out
13     END DEFAULTS;
14     enable = e3 & !e2bar & !e1bar; -- all enables activated
15     IF enable THEN
16         CASE a[] IS
17             WHEN 0 => y0 = GND;
18             WHEN 1 => y1 = GND;
19             WHEN 2 => y2 = GND;
20             WHEN 3 => y3 = GND;
21             WHEN 4 => y4 = GND;
22             WHEN 5 => y5 = GND;
23             WHEN 6 => y6 = GND;
24             WHEN 7 => y7 = GND;
25         END CASE;
26     END IF;
27 END;
```

4


## AHDL Decoders

- The **DEFAULTS** keyword is to establish a value for variable that are not specified elsewhere in the code.
- This allows each case to force one bit LOW without stating that the others must go HIGH.

5
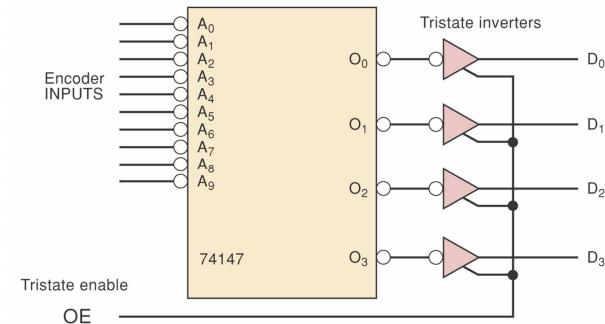
## AHDL Encoders

- When one of the inputs is activated, it produces a binary number corresponding to that input.
- When more than one of its inputs is activated, it ignores the input of lower significance.



6

```

1  SUBDESIGN fig9_58
2  (
3      a[9..0], oe      :INPUT;
4      d[3..0]          :OUTPUT;
5  )
6  VARIABLE buffer[3..0] :TRI;
7  BEGIN
8      TABLE
9          a[]           => buffer[].in;
10         B"111111111" => B"1111"; -- no input active
11         B"111111110" => B"0000"; -- 0
12         B"11111110X" => B"0001"; -- 1
13         B"11111110XX" => B"0010"; -- 2
14         B"1111110XXX" => B"0011"; -- 3
15         B"111110XXXX" => B"0100"; -- 4
16         B"11110XXXXX" => B"0101"; -- 5
17         B"1110XXXXXX" => B"0110"; -- 6
18         B"110XXXXXXX" => B"0111"; -- 7
19         B"10XXXXXXXX" => B"1000"; -- 8
20         B"0XXXXXXXXX" => B"1001"; -- 9
21     END TABLE;
22     buffer[].oe = oe; -- hook up enable line
23     d[] = buffer[].out; -- hook up outputs
24 END;
```

7

## AHDL Encoders

- AHDL has a library **primitive** called **TRI** for tristate buffers.
- A primitive can be imagined as a component in a store and is similar to a structure in C.
- This makes the implementation easier — just to connect the primitive's ports to the appropriate signals.


```
VARIABLE buffer[3..0] :TRI;
```

```
buffer[].in = B"0000";
buffer[].oe = oe;
d[] = buffer[].out;
```

8
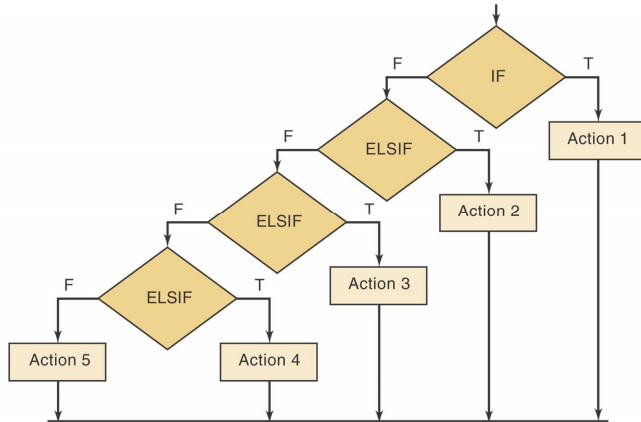
## AHDL Encoders

- The AHDL encoder can also be implemented using **IF/ELSIF**, which choose one of many possible outcomes.



9

```


1  SUBDESIGN fig9_59
2  (
3      sw[9..0], oe    :INPUT;
4      d[3..0]         :OUTPUT;
5  )
6  VARIABLE
7      buffers[3..0]   :TRI;
8  BEGIN
9      IF !sw[9] THEN buffers[].in = 9;
10     ELSIF !sw[8] THEN buffers[].in = 8;
11     ELSIF !sw[7] THEN buffers[].in = 7;
12     ELSIF !sw[6] THEN buffers[].in = 6;
13     ELSIF !sw[5] THEN buffers[].in = 5;
14     ELSIF !sw[4] THEN buffers[].in = 4;
15     ELSIF !sw[3] THEN buffers[].in = 3;
16     ELSIF !sw[2] THEN buffers[].in = 2;
17     ELSIF !sw[1] THEN buffers[].in = 1;
18     ELSE buffers[].in = 0;
19     END IF;
20     buffers[].oe = oe & sw[0] != b"1111111111"; -- enable on any input
21     d[] = buffers[].out; -- connect to outputs
22 END;

```

10
 
## AHDL MUX and DEMUX

- A multiplexer selects and connects one of the inputs to the output.
- A demultiplexer distributes an input to one of its outputs.



11

## AHDL MUX and DEMUX

```

1  SUBDESIGN fig9_62
2  (
3      ch0[3..0], ch1[3..0], ch2[3..0], ch3[3..0]:INPUT;
4      s[1..0]                                     :INPUT; -- select inputs
5      dout[3..0]                                  :OUTPUT;
6  )
7  BEGIN
8      CASE S[] IS
9          WHEN 0 => dout[] = ch0[];
10         WHEN 1 => dout[] = ch1[];
11         WHEN 2 => dout[] = ch2[];
12         WHEN 3 => dout[] = ch3[];
13     END CASE;
14 END;

```

12

## AHDL MUX and DEMUX


```

1  SUBDESIGN fig9_63
2  (
3      ch0[3..0], ch1[3..0], ch2[3..0], ch3[3..0] :OUTPUT;
4      s[1..0] :INPUT;
5      din[3..0] :INPUT;
6  )
7  BEGIN
8      DEFAULTS
9          ch0[] = B"1111";
10         ch1[] = B"1111";
11         ch2[] = B"1111";
12         ch3[] = B"1111";
13     END DEFAULTS;
14
15     CASE s[] IS
16         WHEN 0 => ch0[] = din[];
17         WHEN 1 => ch1[] = din[];
18         WHEN 2 => ch2[] = din[];
19         WHEN 3 => ch3[] = din[];
20     END CASE;
21 END;

```

13

## AHDL Comparators

 

If we need to compare bigger values, we can simply adjust the size of the input ports, rather than cascade MSI chips.

```


1  SUBDESIGN fig9_66
2  (
3      a[3..0], b[3..0] :INPUT;
4      agtb, altb, aeqb :OUTPUT;
5  )
6  BEGIN
7      IF a[] > b[] THEN
8          agtb = VCC; altb = GND; aeqb = GND;
9      ELSIF a[] < b[] THEN
10         agtb = GND; altb = VCC; aeqb = GND;
11      ELSE
12         agtb = GND; altb = GND; aeqb = VCC;
13      END IF;
14 END;

```

14

## AHDL Adders

A	B	C <sub>in</sub>	C <sub>out</sub>	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$\Sigma = (A \oplus B) \oplus C_{in}$$

$$C_{out} = AB + (A \oplus B)C_{in}$$

$$C_{out} = ABC_{in} + AB\bar{C}_{in} + A\bar{B}C_{in} + \bar{A}BC_{in}$$

$$= (ABC_{in} + AB\bar{C}_{in}) + (A\bar{B}C_{in} + \bar{A}BC_{in})$$

$$= AB + AC_{in} + BC_{in}$$

15

## AHDL Adders

```

SUBDESIGN fig6_21
(
    cin      :INPUT;      -- carry in
    a[3..0]  :INPUT;      -- augend
    b[3..0]  :INPUT;      -- addend
    s[3..0]  :OUTPUT;      -- sum
    cout     :OUTPUT;      -- carry OUT
)
VARIABLE
    c[4..0] :NODE;      -- carry array is 5 bits long!

BEGIN
    c[0] = cin;
    s[] = a[] $ b[] $ c[3..0]; -- generate sum
    c[4..1] = (a[] & b[]) # (a[] & c[3..0]) # (b[] & c[3..0]);
    cout = c[4];          -- carry out
END;

```

16